

ASSIGNMENT # 1

Analog CMOS Circuit Design (ECE315 / ECE515)

Total Marks: 10 (each questions carry equal marks)

1. A three terminal Non linear device shown in Figure - 1 exhibits definite I_1 vs V_1 , I_1 vs V_2 , I_2 vs V_2 and I_2 vs V_1 characteristics.

Assume that the Non Linear Device shown in Figure (1) can be modelled as,

$$I_1 = f(V_1, V_2)$$

$$I_2 = g(V_1, V_2)$$

 


Figure 1

Now answer the following Questions (Your Answers must be Qualitative. An intuitive answer leads blunders)

- a. Figure (2) shown below depicts I_1 vs V_1 characteristics of two Non Linear devices (Device (i) and Device (ii)). Assume that the characteristics I_1 vs V_2 , I_2 vs V_2 and I_2 vs V_1 are identical for both the amplifiers. Find out which of the Non Linear devices will yield maximum gain at the given operating point shown in the figure (**Green Circle**).

 


Figure 2

 


Figure 3

- b. Figure (3) shown below depicts I_2 vs V_1 characteristics of two Non Linear devices (Device (i) and Device (ii)). Assume that the characteristics I_1 vs V_2 , I_2 vs V_2 and I_1 vs V_1 are identical for both the amplifiers. Find out which of the Non Linear devices will yield maximum gain at the given operating point shown in the figure (**Green Circle**).

2. Circuit shown in Figure 4 is designed for small signal gain of -4 . Consider $R_1, R_2 \gg 100K$ and R_D and R_L are same. The supply voltage V_{DD} must be chosen in such a way that at the operating point V_{DS} should be $V_{GS} + 1$. You have carried out the design assuming $\lambda = 0$. However, after analysis you realized that $\lambda = 0.0625V^{-1}$.

- What is the actual small signal gain.
- What is the value of R_D to be used to restore the small signal gain to -4 .

 


Figure 4

3. Assume that you have got two NMOSFET's with one at nominal threshold voltage (V_T) and other having a variation ΔV_T from its nominal value. How the transconductance (g_m) and Drain Current (I_{DS}) of the device varies with ΔV_T .

Repeat the same by assuming there is a variation in process parameter (K) = $\mu C_{ox}(W/L)$ and **no variation** in threshold voltage.

4. For the circuit shown in **Figure 5**: ($R_s = 50K\Omega$, $R_g = 50M\Omega$, $R_L = 100K\Omega$, $I = 128 \mu A$, $V_T = 1V$, $\mu C_{ox}(W/L) = 100\mu A/V^2$)

- What kind of biasing scheme is incorporated and explain how DC biasing occurs in the circuit.
- Determine the constraints on C_1 and C_2 such that the circuit behaves as an Amplifier.
- For the same circuit an Input signal is applied with a frequency of 10KHz what are the values of C_1 and C_2 such that the AC coupling will not disturb in AC incremental analysis.
- Implement the same using Cadence or SPICE and ELDO simulator for the values you got in **Part.3** and compare the gain of the amplifier with theoretical gain.
- Calculate the Input and output Impedence of the Amplifier for the same figure 2

 


Figure 5