

## Home Assignment # 2

Scheme of Marking: Binary Marking

(Please highlight your answer in a box)

Data:  $\mu_n C_{ox} = 100 \mu A/V^2$ ,  $W/L = 1$ ,  $V_t = 1V$ .

*All the Simulations must be carried out in ELDO*

**Total Marks: 10**


**Q1:**

(a) Name the type of circuit in Fig. 1 (a).

Now, circuit shown in Fig. 1 (a) is required to have output impedance of **5Kohms**.

b) Determine the biasing **current  $I_0$** .

c) Then Fig. 1(a) is actually implemented as Fig. 1 (b). The Quiescent voltage across the resistor  $R_0$  is 5V. Determine the small signal gain for very high frequencies (Neglect all the device capacitances)

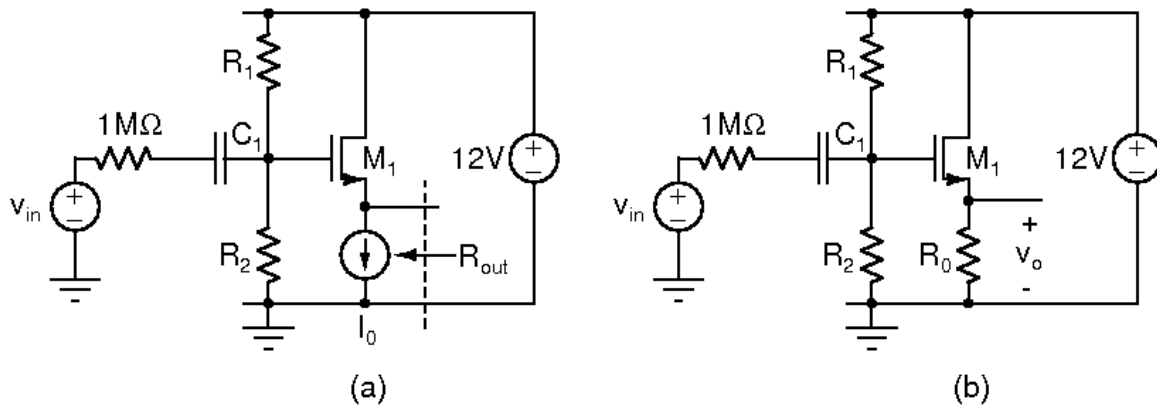

**Figure 1**

**Q2:** Transistor  $M_1$  in the Fig. 2 is biased using  $M_{00}$ - $M_0$ . Assuming  $C_1$ ,  $R_1$ , and  $R_2$  very large and  $i_d/v_i = 20 \mu S$  where  $i_d$  is small signal drain current.

(a) Determine bias current  $I_0$  by assuming all the devices are in saturation.

(b) If  $M_0$  is at the verge of saturation, determine  $R_1/R_2$ .

(c) Assume  $v_o/v_i = -4$ . Determine  $R_L$  assuming  $L_2$ ,  $C_2$  being very large.

Determine condition for  $L_2$  at signal frequency of 1MHz

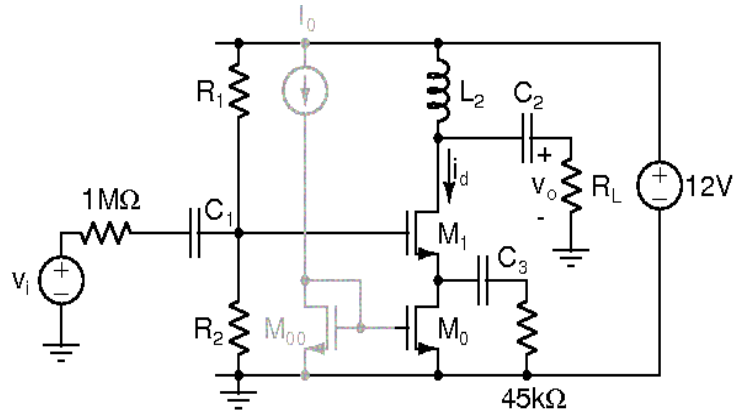


Figure 2

**Q3:** Find out the output impedance and input impedance for the circuit shown in Fig. 3

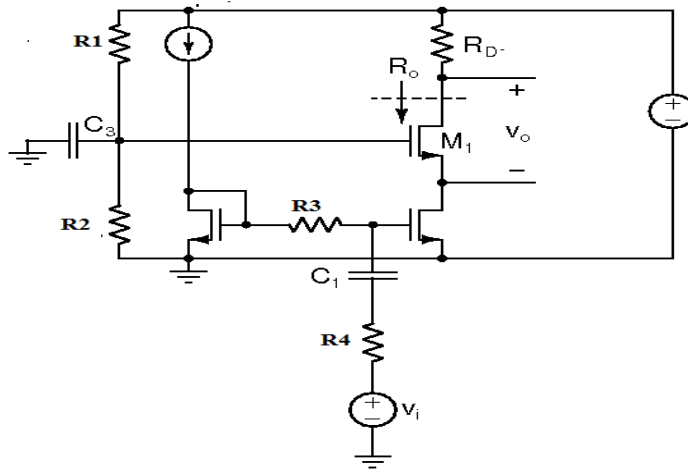


Figure 3

**Q4:** Fig.4 shows MOS transistors in various bias conditions. Identify the region of operations of devices (Marks will be awarded only if all are correct).

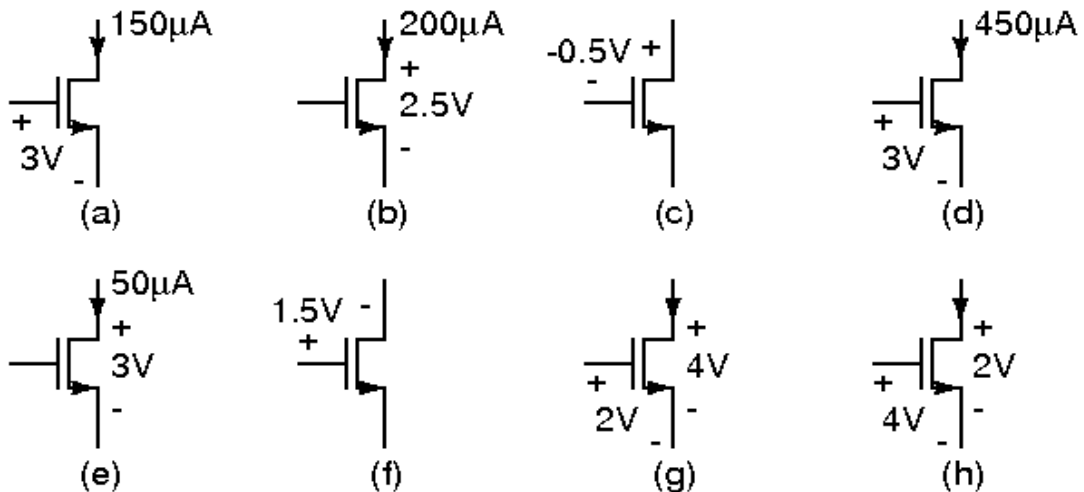


Figure 4

5) Refer Fig.5 and answer the following:

- Perform DC Analysis (Operating point Analysis) and write down the values of  $V_{gs}$ ,  $V_{ds}$ ,  $V_{gd}$
- Discuss the effect of  $R_{gl}$  on biasing (Plot trends)
- Discuss how the gain changes with variable  $R_D$
- Plot the trends of gain of the Amplifier with  $R_{gl}$  and discuss with appropriate explanation
- Plot Gain with variable  $C_1$  ( $1\mu\text{f}$  to  $100\mu\text{f}$  at  $10\mu\text{f}$  step) and variable  $R_L$  ( $1\text{K}$  to  $100\text{K}$  at a step of  $10\text{K}$ )

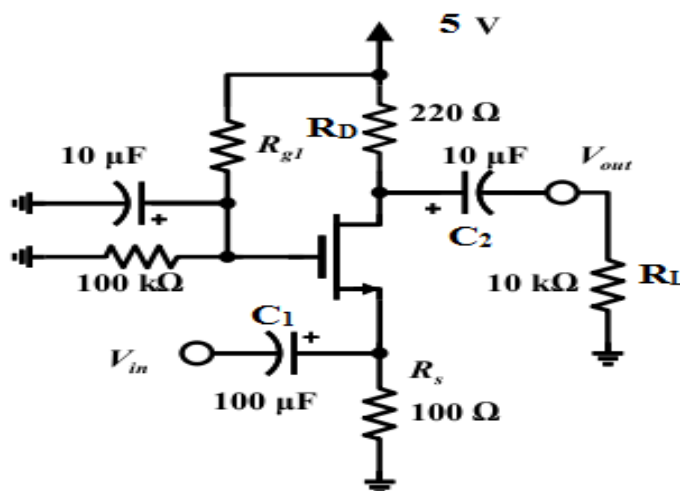


Figure 5