

Assignment 3

(Please highlight your answer in a box)

- 1) Find the a.c incremental current I_{out} flowing from node A to ground when $\lambda=0$ and $\lambda \neq 0$.
 (Assuming all devices are equal in size and the tail current source is Ideal)

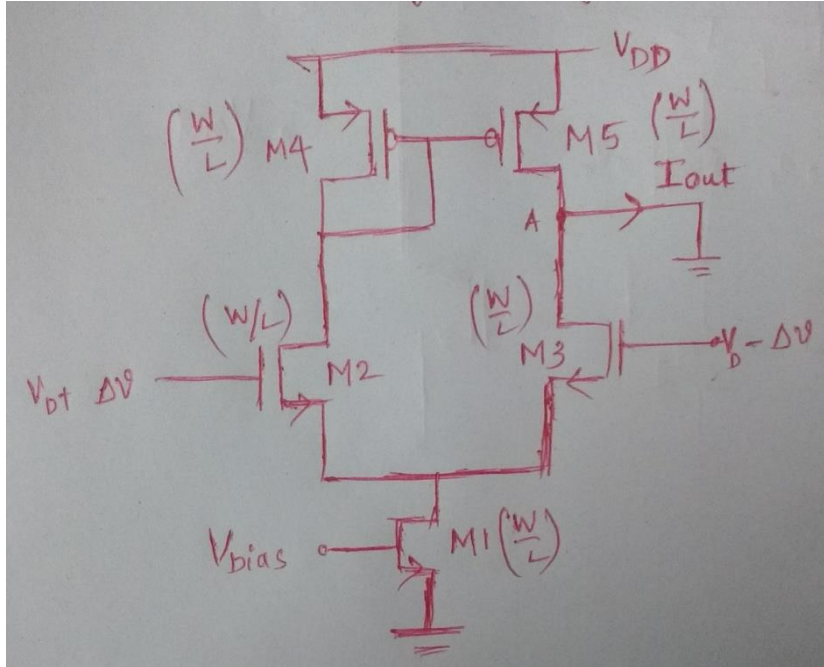


Figure 1

- 2) $I_{bias} = 25\mu A$, $V_{DD} = 1.8V$, $(W/L)_{3,4} = 50$ and $(W/L)_{1,2,5,6,10} = 100$. Consider the other transistor size (w/L) which are not mentioned as 100.

- Calculate the gain of this amplifier?
- Slew rate of the amplifier when $C_L = 5pF$
- Simulate in ELDO and compare (Download 130nm PTM file for VDD Supply 2V and calculate all parameters required and proceed)

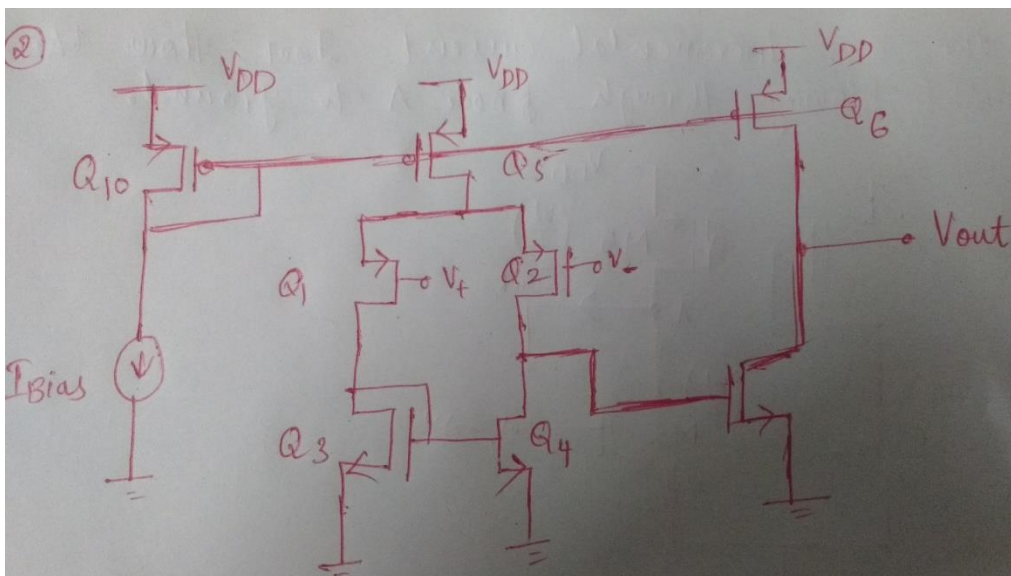


Figure 2

3) In Fig.3, $V_{DD} = 1.8$, $R_D = 2K$. Initially it was designed for a gain of 4 (Pick your own 130nm technology file and get gain of 4). Now bias the transistor which you have used to achieve gain 4 in order to achieve maximum gain without distortions.

Calculate the:

- D.C level of Input
- D.C level of output node
- Power Dissipation
- Threshold voltage of M1
- Value of parameter K

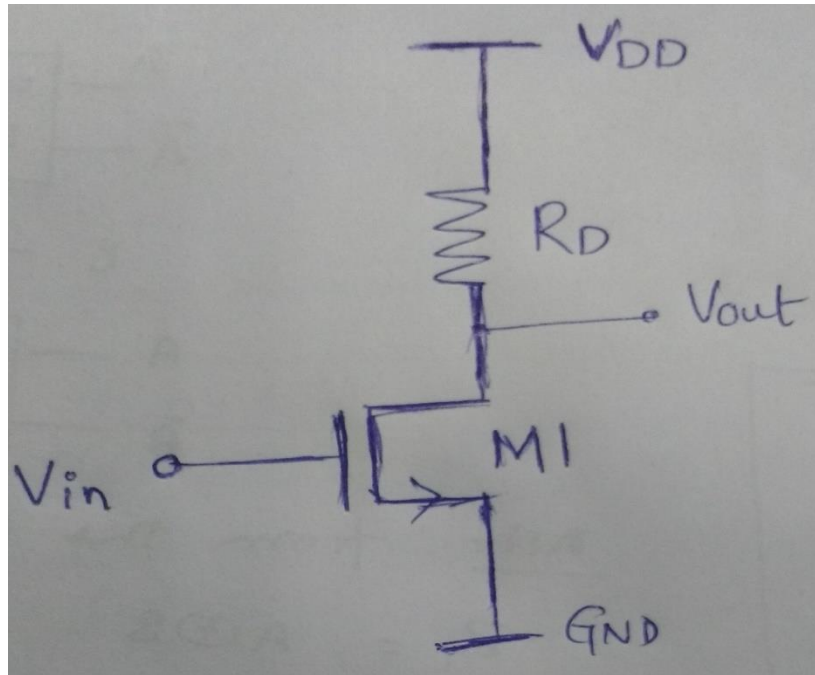


Figure 3