

Lecture-13

Date: 05.10.2015

- Differential Amplifier (contd.)

Differential Pair (contd.)

Alternative Approach:


Drain current is given by:

$$i_{d1} = i_{d2} = \frac{v_{id}}{2/g_m}$$

Therefore,

$$v_{o1} = -g_m \frac{v_{id}}{2} R_D \quad v_{o2} = g_m \frac{v_{id}}{2} R_D$$

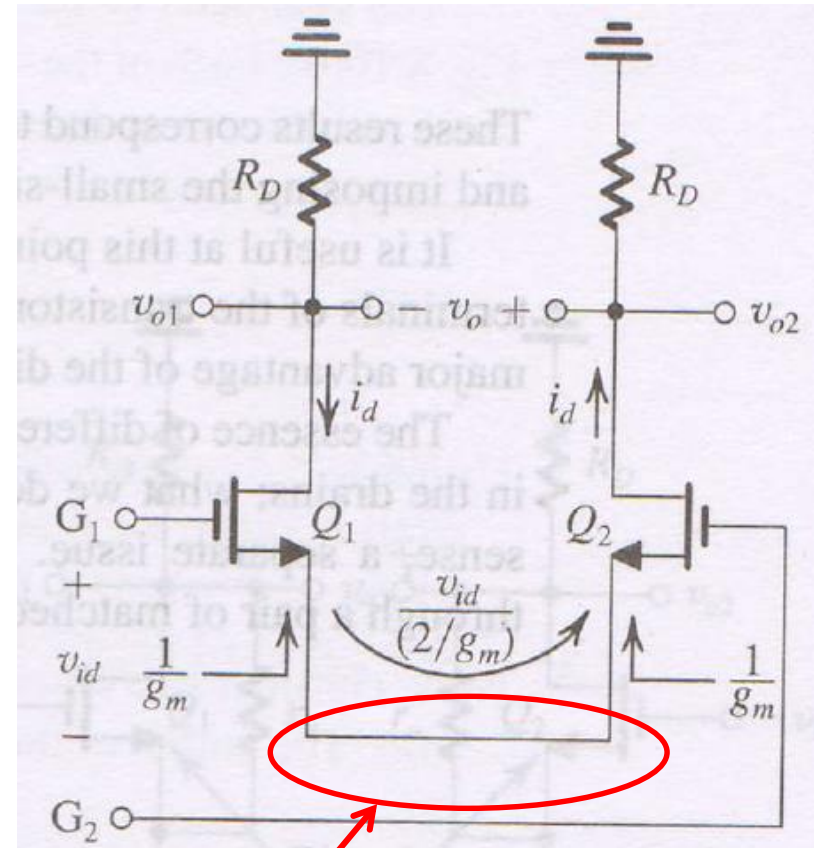
$$\therefore A_d = \frac{v_{o2} - v_{o1}}{v_{id}} = g_m R_D$$



Total Impedance = $\frac{1}{g_m} + \frac{1}{g_m} = \frac{2}{g_m}$

Differential Pair – Small-Signal Operation (contd.)

- Effect of r_o on the gain

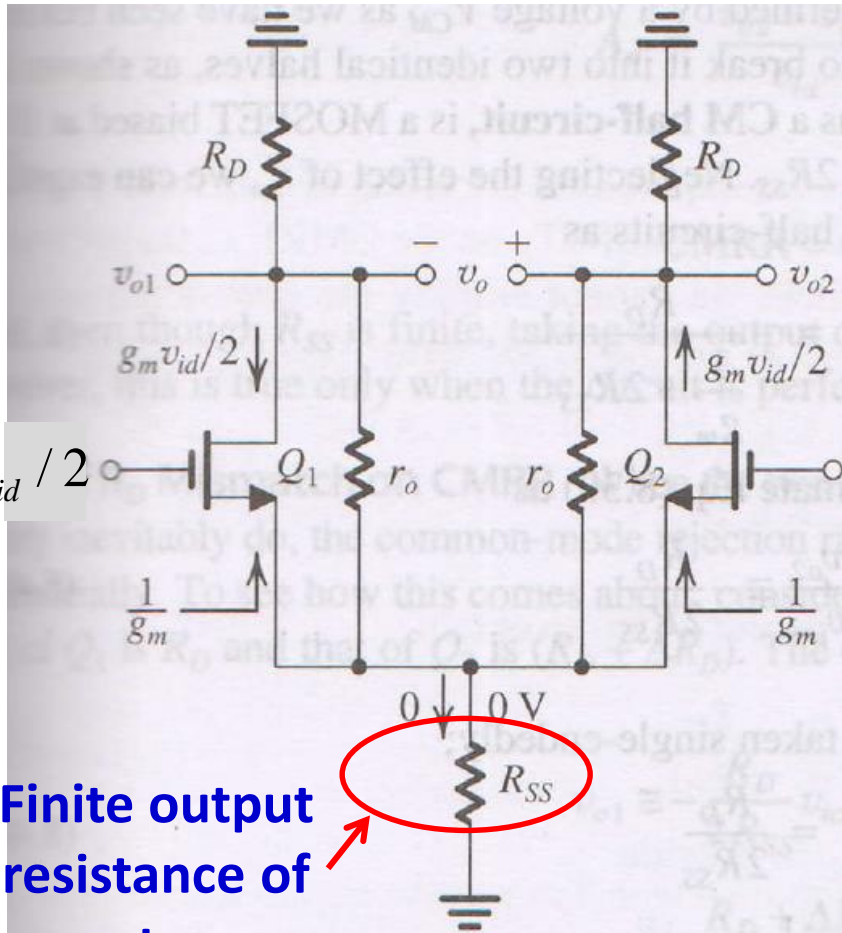

Finite output
resistance of
current source

How will the gain be affected if channel length modulation is considered?


→ the circuit is still symmetric → **the voltage at common source connection will be zero**

NO current through R_{SS}

R_{SS} plays no role in differential gain

Differential Pair – Small-Signal Operation (contd.)

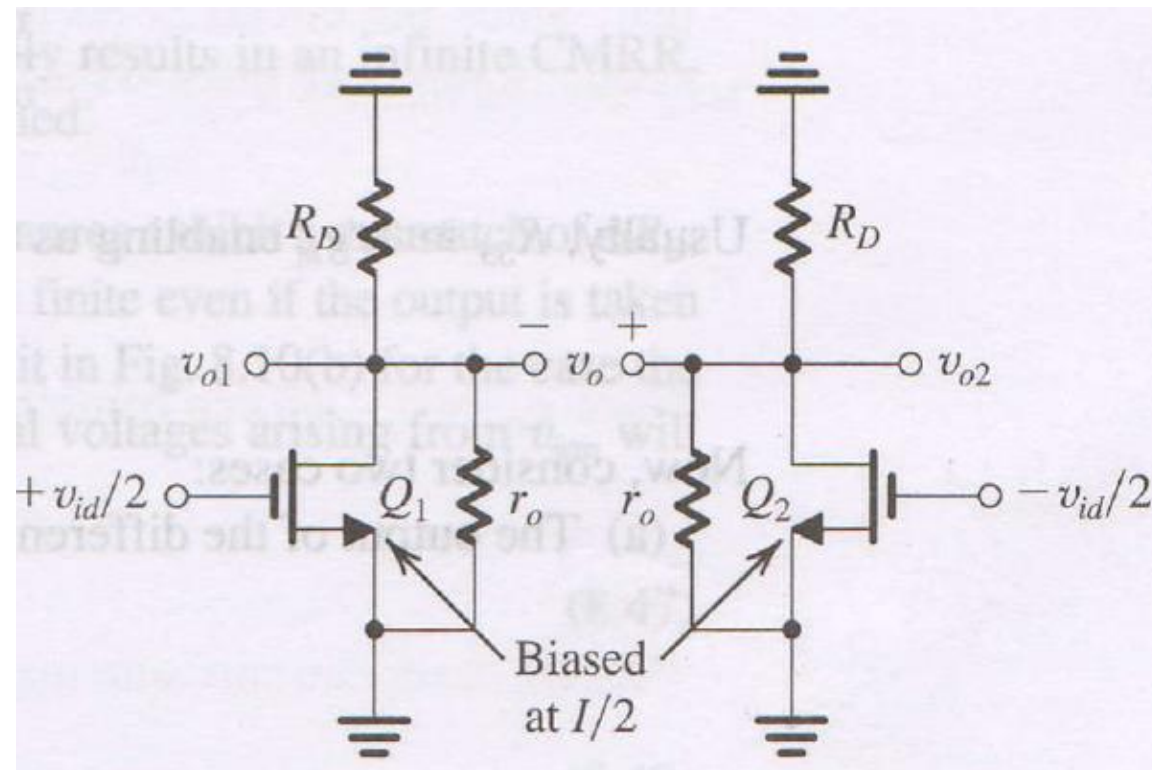- The virtual ground on the source allows division of two identical CS amplifiers: **→ differential half circuits**



$$v_{o1} = -g_m \frac{v_{id}}{2} (R_D \parallel r_o)$$

$$v_{o2} = g_m \frac{v_{id}}{2} (R_D \parallel r_o)$$

$$\Rightarrow v_o = g_m v_{id} (R_D \parallel r_o)$$

$$\therefore A_d = \frac{v_o}{v_{id}} = g_m (R_D \parallel r_o)$$

Differential Pair – Small-Signal Operation (contd.)

Question: A MOS differential amplifier is operated at a total bias current of 0.8 mA, using transistors with a W/L ratio of 100, $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$, $V_A = 20 \text{ V}$, and $R_D = 5 \text{ k}\Omega$. Find V_{OV} , g_m , r_o , and A_d .

$$\frac{I}{2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) V_{OV}^2 \quad \Rightarrow V_{OV} = 0.2 \text{ V}$$

$$r_o = \frac{V_A}{I_D} = \frac{V_A}{(I/2)} = \frac{20 \text{ V}}{0.4 * 10^{-3}} = 50 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{OV}}$$

$$\Rightarrow g_m = \frac{I}{V_{OV}} = \frac{0.8 * 10^{-3}}{0.2} \text{ A/V}$$

$$\therefore g_m = 4 \text{ mA/V}$$


$$A_d = g_m (R_D \parallel r_o) = (4 \text{ mA/V}) * (5 \text{ k}\Omega \parallel 50 \text{ k}\Omega) = 18.18$$

$$(A_d)_{no_r_o} = g_m (R_D \parallel r_o) = (4 \text{ mA/V}) * 5 \text{ k}\Omega = 20$$

Common-Mode Gain and CMRR

- The objective of differential amplifier is to amplify only the difference between two different potentials regardless of the common-mode value.
- CMRR is the ratio of the magnitude of the differential gain to the common-mode gain.
- The input common mode range (ICMR) specifies over what range of common-mode voltages the differential amplifier continues to sense and amplify the difference signal with the same gain.
- In CMOS differential amplifier, the most serious problem is of offset voltage.
- In theory, the output offset voltage should be zero.
- However, in practical differential amplifier, there is always some output offset voltage due to several constraints.


Common-Mode Gain and CMRR (contd.)

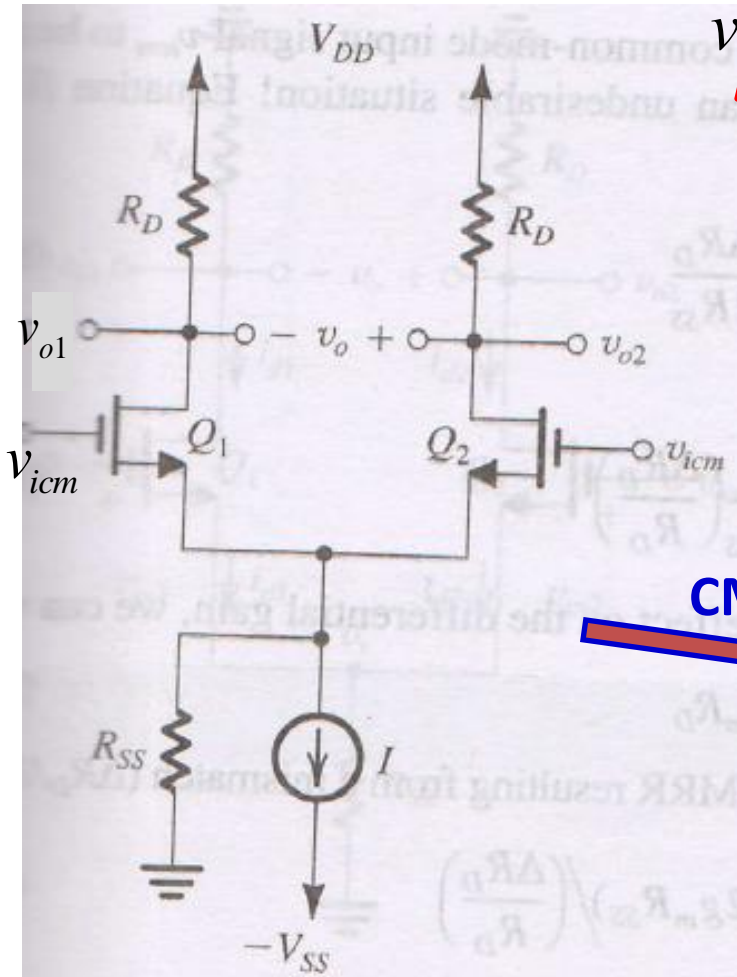


v_{icm} : represents a disturbance or interference signal coupled to both the inputs

Unrelated to common mode dc level V_{CM}

CM Half-Circuit

 

Common-Mode Gain and CMRR (contd.)

 

If r_o is ignored then single ended gains are given by:

$$\frac{v_{o1}}{v_{icm}} = \frac{v_{o2}}{v_{icm}} = -\frac{R_D}{\frac{1}{g_m} + 2R_{SS}}$$

Usually, $R_{SS} \gg 1/g_m$

$$\Rightarrow \frac{v_{o1}}{v_{icm}} = \frac{v_{o2}}{v_{icm}} = -\frac{R_D}{2R_{SS}}$$

If the output is taken single-endedly then: $|A_{cm}| = \frac{R_D}{2R_{SS}}$ and $|A_d| = \frac{1}{2} g_m R_D$

$$\Rightarrow \left| \frac{A_d}{A_{cm}} \right| = g_m R_{SS}$$

Common-Mode Rejection Ratio (CMRR)

Common-Mode Gain and CMRR (contd.)

If the output is taken differentially then: $|A_{cm}| = \frac{v_{o2} - v_{o1}}{v_{icm}} = 0$

and $|A_d| = \frac{v_{o2} - v_{o1}}{v_{id}} = g_m R_D$

$$\Rightarrow CMRR = \left| \frac{A_d}{A_{cm}} \right| = \infty$$

CMRR is infinite even for finite R_{SS} → for matched and balanced differential pair

- Effect of R_D mismatch: suppose the mismatch is to the tune of ΔR_D

$$v_{o1} = -\frac{R_D}{2R_{SS}} v_{icm}$$

$$v_{o2} = -\frac{R_D + \Delta R_D}{2R_{SS}} v_{icm}$$

Common-Mode Gain and CMRR (contd.)

$$\Rightarrow v_{o2} - v_{o1} = -\frac{\Delta R_D}{2R_{SS}} v_{icm} \quad \therefore A_{cm} = \frac{v_{o2} - v_{o1}}{v_{icm}} = -\frac{\Delta R_D}{2R_{SS}}$$

- The mismatch in R_D will have negligible effect on the differential gain:

$$A_d = \frac{v_{o2} - v_{o1}}{v_{id}} \cong -g_m R_D$$

$$\therefore CMRR = \left| \frac{A_d}{A_{cm}} \right| = \frac{g_m R_D}{(\Delta R_D / 2R_{SS})}$$

Some finite value \rightarrow unwanted!


Similarly, mismatch in g_m also affects CMRR




Revisit

Advantages of Differential Signaling

1. Immunity to Environmental Noise

 


 
- Line L_1 carries a small and sensitive signal
- Line L_2 carries a large clock waveform
- Due to capacitive coupling between the lines, the transitions on line L_2 corrupt signal on line L_1



- The small and sensitive signal is distributed as two equal and opposite phases
- The clock signal is placed between the two
- The transition disturb the differential phases by equal amounts, leaving the difference intact

Advantages of Differential Signaling

2. Immunity to Supply Noise

  


- If V_{DD} changes by ΔV , V_{out} changes by the same amount.

- Noise in V_{DD} affects V_X and V_Y , but not $V_X - V_Y$

Advantages of Differential Signaling

 3. Reduction of Coupled Noise






- Differential signaling can also be employed in noisy lines → for example, distributed clock can help in removing noise from signals



Noise coupled from L_3 to L_1 and L_2 to L_1 cancel each other.

Issues with Differential Signaling

- Sensitivity to the Common Mode Level

    
 


- Excessive low $V_{in,CM}$ turns off Devices \rightarrow leads to clipping at the output**
- Solution?**

MOS Differential Pair

M_1 and M_2 are perfectly matched (at least in theory!)

ensures M_1 and M_2 in saturation

  

Variation of input CM level regulates the bias currents of M_1 and M_2 → Undesired!!!

Solution??

Need?

Current source is ideal: constant current, infinite output impedance


To overcome the issues emanating from non-ideal CM level

$R_{D1} = R_{D2} = R_D$

MOS Differential Pair

Qualitative Analysis – differential input

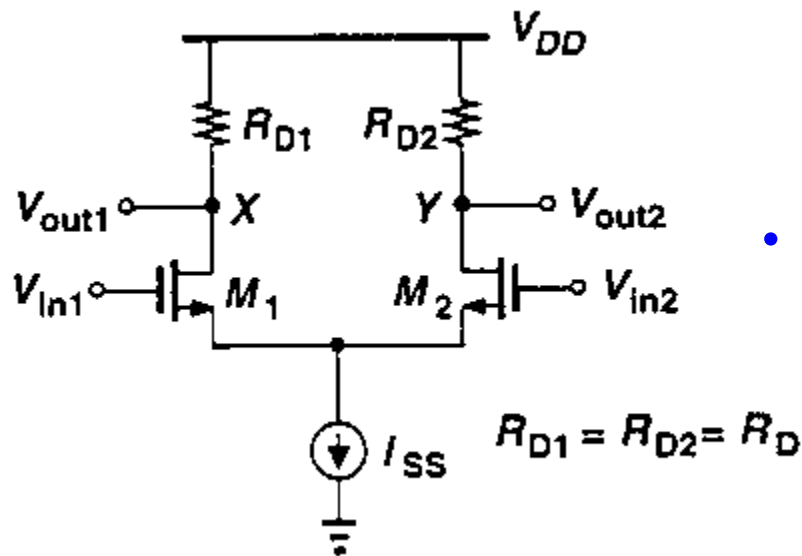- Let us check the effect of $V_{in1} - V_{in2}$ variation from $-\infty$ to ∞




- V_{in1} is much more **-ve** than V_{in2} then:
 - M_1 is OFF and M_2 is ON
 - $I_{D2} = I_{SS}$
 - $V_{out1} = V_{DD}$ and $V_{out2} = V_{DD} - I_{SS}R_D$
- V_{in1} is brought closer to V_{in2} then:
 - M_1 gradually turns ON and M_2 is ON
 - Draws a fraction of I_{SS} and lowers V_{out1}
 - I_{D2} decreases and V_{out2} rises
- $V_{in1} = V_{in2}$
 - $V_{out1} = V_{out2} = V_{DD} - I_{SS}R_D/2$

MOS Differential Pair

Qualitative Analysis – differential input

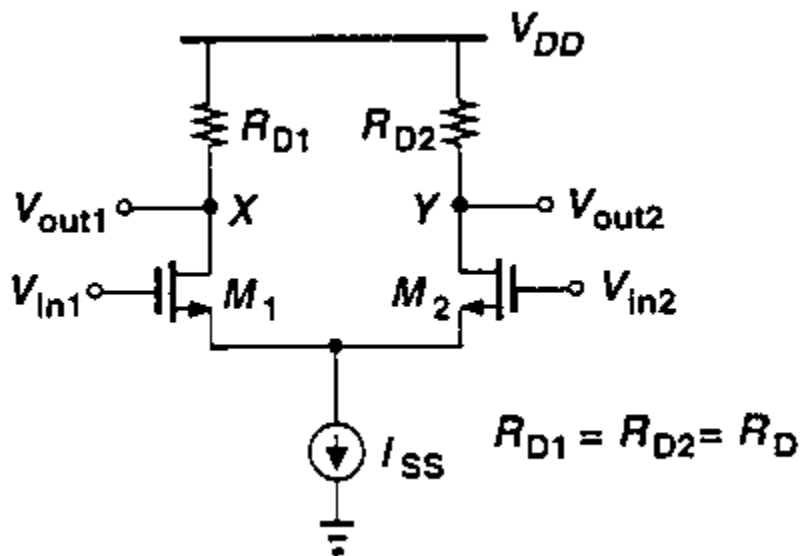- Let us check the effect of $V_{in1} - V_{in2}$ variation from $-\infty$ to ∞




- V_{in1} becomes more +ve than V_{in2} then:
 - M_1 is ON and M_2 is OFF
 - M_1 carries greater I_{SS} than M_2
- For sufficiently large $V_{in1} - V_{in2}$:
 - All of the I_{SS} goes through $M_1 \rightarrow M_2$ is OFF
 - $V_{out1} = V_{DD} - I_{SS}R_D$ and $V_{out2} = V_{DD}$

MOS Differential Pair

Qualitative Analysis – differential input

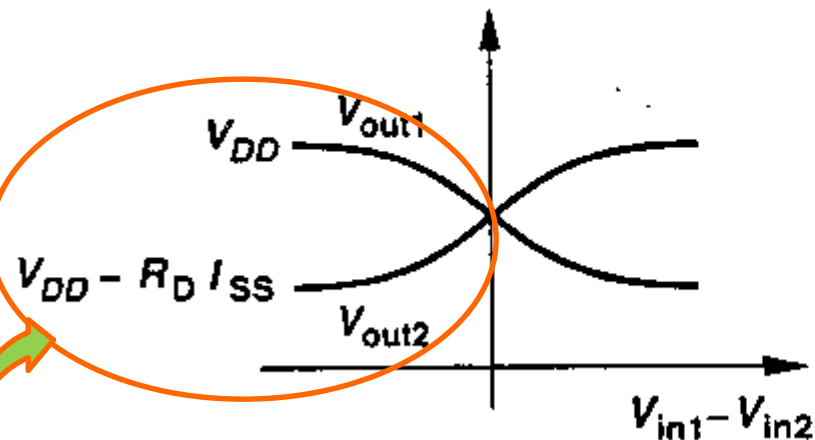
- Plotting $V_{out1} - V_{out2}$ versus $V_{in1} - V_{in2}$



The maximum and minimum levels at the output are well defined and is independent of input CM level ($V_{in,cm}$)

Minimum Slope \leftrightarrow Minimum Gain

 Maximum Slope \leftrightarrow Maximum Gain



The circuit becomes more nonlinear as the input voltage swing increases (i.e., $V_{in1} - V_{in2}$ increases) \leftrightarrow at $V_{in1} = V_{in2}$, the circuit is said to be in equilibrium

MOS Differential Pair


Qualitative Analysis – common mode input

- Now let us consider the common mode behavior of the circuit

As mentioned, the tail current source is used to suppress the effect of input CM level variation ($V_{in,cm}$)



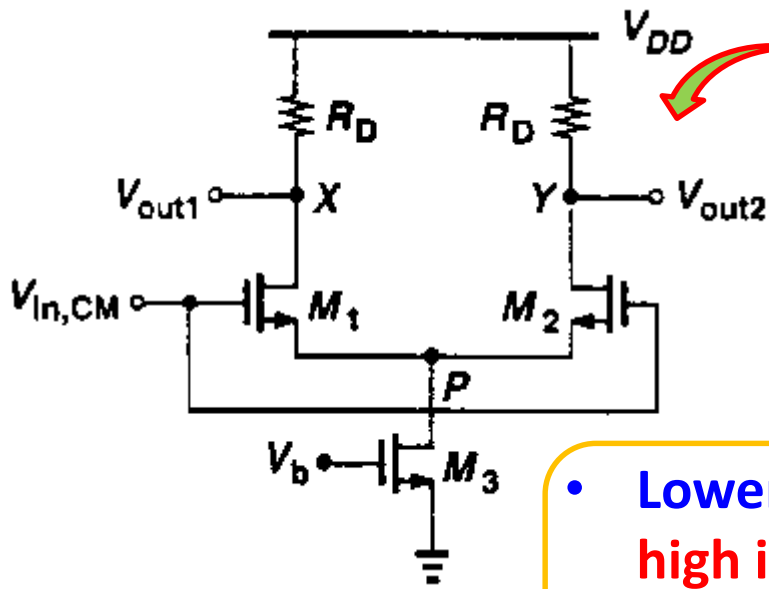Does this enable us to set any arbitrary level of input CM ($V_{in,cm}$)



To understand this:


- Set $V_{in1} = V_{in2} = V_{in,CM}$
- Then vary $V_{in,CM}$ from 0 to V_{DD}
- Also implement I_{SS} with an NFET

- Lower bound of $V_{in,cm}$: V_p should be sufficiently high in order for M_3 to act as a current source.
- Upper bound of $V_{in, cm}$: M_1 and M_2 need to remain in saturation.

MOS Differential Pair

Qualitative Analysis – common mode input

 - What happens when $V_{in,CM} = 0$?
 - M_1 and M_2 will be OFF and M_3 can be in triode for high enough V_b
 - $I_{D1} = I_{D2} = 0$ ← circuit is incapable of amplification



- Now suppose $V_{in,CM}$ becomes more +ve
 - M_1 and M_2 will turn ON if $V_{in,CM}$ exceeds V_T
 - I_{D1} and I_{D2} will continue to rise with the increase in $V_{in,CM}$
 - V_P will track $V_{in,CM}$ as M_1 and M_2 work like a source follower
 - For high enough $V_{in,CM}$, M_3 will be in saturation as well

$$V_{in,CM} \geq V_{GS1,2} + (V_{GS3} - V_{T3})$$

- If $V_{in,CM}$ rises further
 - M_1 and M_2 will remain in saturation if:

$$V_{in,CM} - V_T \leq V_{out1} \implies V_{in,CM} \leq V_{DD} - \frac{I_{SS}}{2} R_D + V_T$$

MOS Differential Pair

Qualitative Analysis – common mode input

- **Alternatively:** the common-mode input range can be identified as:
- **For M_1 and M_2 to remain in saturation:**

$$V_{GS1,2} - V_T \leq V_{DS1,2} \quad \Rightarrow V_{in,CM} - V_T \leq V_{DD} - \frac{I_{SS}}{2} R_D$$

$$\Rightarrow V_{in,CM} \leq V_T + V_{DD} - \frac{I_{SS}}{2} R_D$$

$$\therefore (V_{in,CM})_{\max} = V_T + V_{DD} - \frac{I_{SS}}{2} R_D$$

- **The lowest value of $V_{in,CM}$ is determined by the need to keep the constant current source operational:**

$$V_{in,CM} - V_{GS1,2} \geq V_{GS3} - V_T \quad \Rightarrow V_{in,CM} \geq V_{GS1,2} + (V_{GS3} - V_T)$$

$$V_{GS1,2} + (V_{GS3} - V_T) \leq V_{in,CM} \leq \min \left[V_{DD} - \frac{I_{SS}}{2} R_D + V_T, V_{DD} \right]$$


MOS Differential Pair

Qualitative Analysis – common mode input

- Thus, $V_{in,CM}$ is bounded as:

$$V_{GS1,2} + (V_{GS3} - V_T) \leq V_{in,CM} \leq \min \left[V_{DD} - \frac{I_{SS}}{2} R_D + V_T, V_{DD} \right]$$


- Summary:

 

MOS Differential Pair

Qualitative Analysis – common mode input

 - How large can the output voltage swings of a differential pair be?




$$V_{out,max} = V_{DD}$$

$$V_{out,min} = V_{in,CM} - V_T$$

The higher the input CM level, the smaller the allowable output swings.

MOS Differential Pair

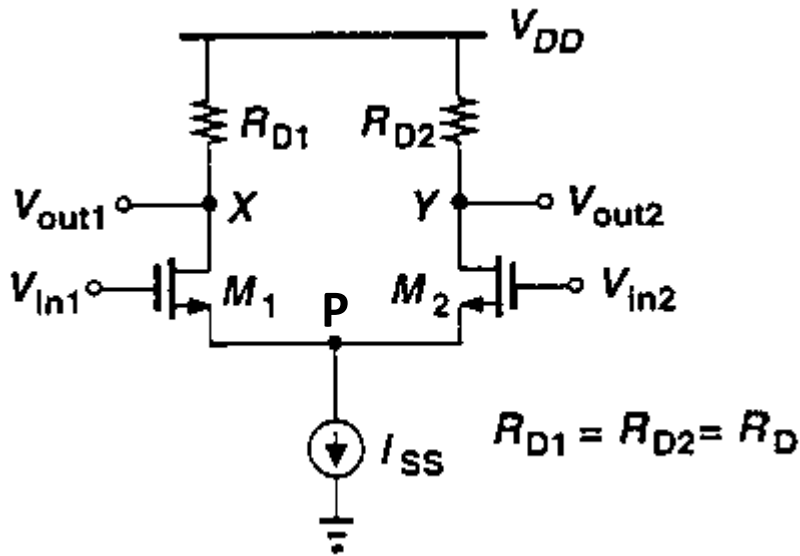Quantitative Analysis – differential input



- For +ve $V_{in1} \rightarrow V_{GS1}$ is greater than $V_{GS2} \rightarrow I_{D1}$ will be greater than I_{D2}



$$V_{out2} (= V_{DD} - I_{D2}R_D) > V_{out1} (= V_{DD} - I_{D1}R_D)$$

- For +ve $V_{in2} \rightarrow V_{GS2}$ is greater than $V_{GS1} \rightarrow I_{D2}$ will be greater than I_{D1}




$$V_{out1} (= V_{DD} - I_{D1}R_D) > V_{out2} (= V_{DD} - I_{D2}R_D)$$

It is thus apparent that the differential pair respond to differential-mode signals \rightarrow by providing differential output signal between the two drains

Differential Pair – Large Signal Analysis

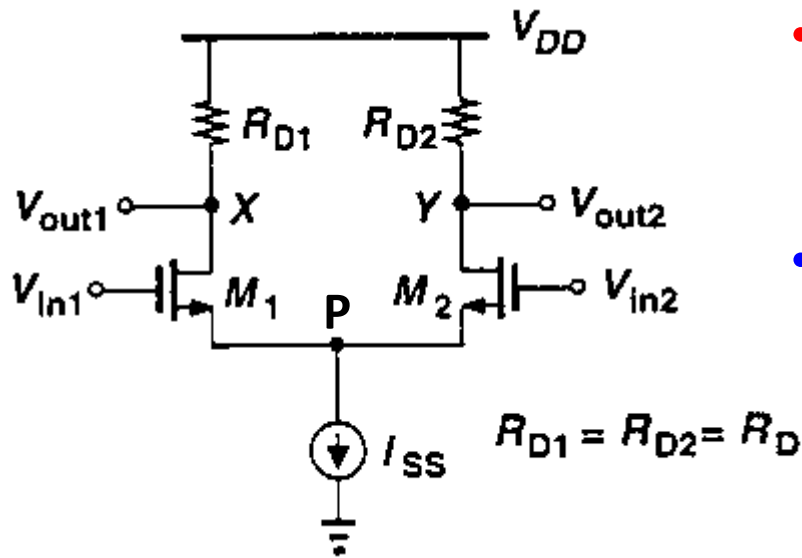Quantitative Analysis – differential input




- The idea is to define I_{D1} and I_{D2} in terms of input differential signal $V_{in1} - V_{in2}$
- The circuit doesn't include connection details considering that these drain current equations do not depend on the external circuitries

Assumptions: M_1 and M_2 are always in saturation;
differential pair is perfectly matched; channel length
modulation is not present

Differential Pair – Large Signal Analysis

 Quantitative Analysis – differential input



$$V_P = V_{in1} - V_{GS1} = V_{in2} - V_{GS2}$$

$$\therefore V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$

We also know:

$$R_{D1} = R_{D2} = R_D \quad (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}} \Rightarrow V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_T$$

Therefore:

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

Squaring

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}})$$

Differential Pair – Large Signal Analysis

Quantitative Analysis – differential input

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} \left(I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}} \right)$$

$= I_{SS}$

$$\therefore (V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} \left(I_{SS} - 2\sqrt{I_{D1}I_{D2}} \right)$$

$$\frac{1}{2} \left(\mu_n C_{ox} \frac{W}{L} \right) (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}}$$

Squaring


$$\frac{1}{4} \left(\mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 = 4I_{D1}I_{D2}$$

$$\frac{1}{4} \left(\mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2$$

Differential Pair – Large Signal Analysis

Quantitative Analysis – differential input
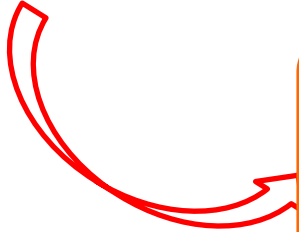
$$(I_{D1} - I_{D2})^2 = -\frac{1}{4} \left(\mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2$$



$$I_{D1} - I_{D2} = \frac{1}{2} \left(\mu_n C_{ox} \frac{W}{L} \right) (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

Observations

- $I_{D1} - I_{D2}$ falls to zero for $V_{in1} = V_{in2}$ and $|I_{D1} - I_{D2}|$ increases with increase in $|V_{in1} - V_{in2}|$
- Therefore, $I_{D1} - I_{D2}$ is an odd function of $V_{in1} - V_{in2}$
- Its important to notice that I_{D1} and I_{D2} are even functions of their respective gate-source voltage

Differential Pair – Large Signal Analysis


Quantitative Analysis – differential input

- Equivalent G_m of M_1 and $M_2 \rightarrow$ its effectively the slope of the characteristics

Lets denote: $I_{D1} - I_{D2} = \Delta I_D$

$V_{in1} - V_{in2} = \Delta V_{in}$

$$\Delta I_D = \frac{1}{2} \left(\mu_n C_{ox} \frac{W}{L} \right) \Delta V_{in} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}$$



$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2} \left(\mu_n C_{ox} \frac{W}{L} \right) \frac{\mu_n C_{ox} \frac{W}{L}}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}}$$

For $\Delta V_{in} = 0$: $G_m = \frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$

Furthermore: $V_{out1} - V_{out2} = R_D \Delta I = R_D G_m \Delta V_{in}$

$$\therefore |A_v| = \frac{V_{out1} - V_{out2}}{\Delta V_{in}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} R_D}$$

Differential Pair – Large Signal Analysis



Quantitative Analysis – differential input

$$G_m = \frac{1}{2} \left(\mu_n C_{ox} \frac{W}{L} \right) \frac{\frac{4I_{SS}}{W} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{W} - \Delta V_{in}^2}}$$

G_m falls to zero for

$$\Delta V_{in} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

  
ΔV_{in1} represents the maximum differential signal a differential pair can handle.



Beyond $|\Delta V_{in1}|$, only one transistor is ON and therefore draws all of the I_{SS}

Differential Pair – Large Signal Analysis

 Quantitative Analysis – differential input




W/L Constant


Increase $\Delta V_{in1} \rightarrow$ by
increasing I_{SS}

I_{SS} Constant

 Reduce $\Delta V_{in1} \rightarrow$ by
increasing W/L



**Linearity
Improves**

 

**Linearity
Improves**

Linearity of a differential pair can be improved by decreasing W/L and/or
increasing I_{SS}

Differential Pair – Large Signal Analysis

Quantitative Analysis – differential input

- The equilibrium overdrive (i.e, when M_1 and M_2 are drawing equal portion of I_{SS}) is given by:

$$(V_{GS} - V_T)_{1,2} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \quad \longrightarrow \quad (V_{OV})_{1,2} = \frac{\Delta V_{in1}}{\sqrt{2}}$$

