

Lecture-14

Date: 08.10.2015

- MOS Differential Pair – Small Signal Analysis
- Differential Pair with Common Mode Input
- Examples

Lecture 13 - Review



Quantitative Analysis – differential input

$$G_m = \frac{1}{2} \left(\mu_n C_{ox} \frac{W}{L} \right) \frac{\frac{4I_{SS}}{W} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{W} - \Delta V_{in}^2}}$$

G_m falls to zero for

$$\Delta V_{in} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

  
ΔV_{in1} represents the maximum differential signal a differential pair can handle.



Beyond $|\Delta V_{in1}|$, only one transistor is ON and therefore draws all of the I_{SS}

Lecture 13 - Review

 Quantitative Analysis – differential input




W/L Constant


Increase $\Delta V_{in1} \rightarrow$ by
increasing I_{SS}

I_{SS} Constant

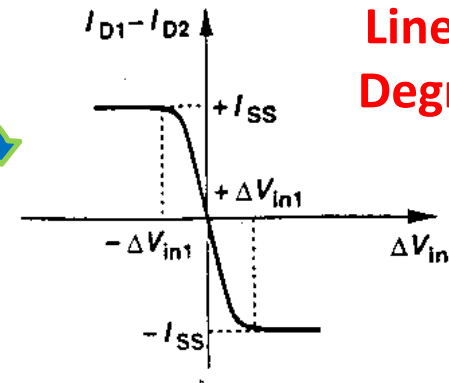Reduce $\Delta V_{in1} \rightarrow$ by
increasing W/L



**Linearity
Degrades**

 

**Linearity
Improves**


Linearity of a differential pair can be improved by decreasing W/L and/or increasing I_{SS}

Lecture 13 - Review

Quantitative Analysis – differential input

- The equilibrium overdrive (i.e, when M_1 and M_2 are drawing equal portion of I_{SS}) is given by:
 
$$(V_{GS} - V_T)_{1,2} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \quad \longrightarrow \quad (V_{OV})_{1,2} = \frac{\Delta V_{in1}}{\sqrt{2}}$$



MOS Differential Pair – small signal analysis

Quantitative Analysis – differential input

- From large signal analysis we achieved:

$$\therefore |A_v| = \frac{V_{out1} - V_{out2}}{\Delta V_{in}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} R_D$$


$$\therefore |A_v| = \frac{V_{out1} - V_{out2}}{\Delta V_{in}} = g_m R_D$$

At equilibrium, this is g_m

- How to arrive at this result using small signal analysis?
 - Two techniques**
 - Superposition method
 - Half-circuit concept


MOS Differential Pair – small signal analysis

 - We apply **small signals** to V_{in1} and V_{in2} and assume M_1 and M_2 are already operating in saturation.



MOS Differential Pair – small signal analysis

 
- **Method-I:** Superposition technique – in this the idea is to see the effect of V_{in1} and V_{in2} on the overall output and then combine them to get the differential small signal voltage gain
- First set, $V_{in2} = 0$
- Then let us calculate V_x/V_{in1}



CS-stage

This is open for
small signal
analysis


Simplified Circuit

 

Input impedance of M_2 Provides
degeneration resistance to CS-
stage of M_1

MOS Differential Pair – small signal analysis

- Superposition technique

 


Apply the CS-stage
formulation

$$\frac{V_X}{V_{in1}} = \frac{-R_{D1}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\therefore \frac{V_X}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

MOS Differential Pair – small signal analysis

 
- Superposition technique
 - Now calculate V_Y/V_{in1}



Replace M_1 by its
Thevenin Equivalent
Circuit

This is open for
small signal
analysis

Simplified Circuit

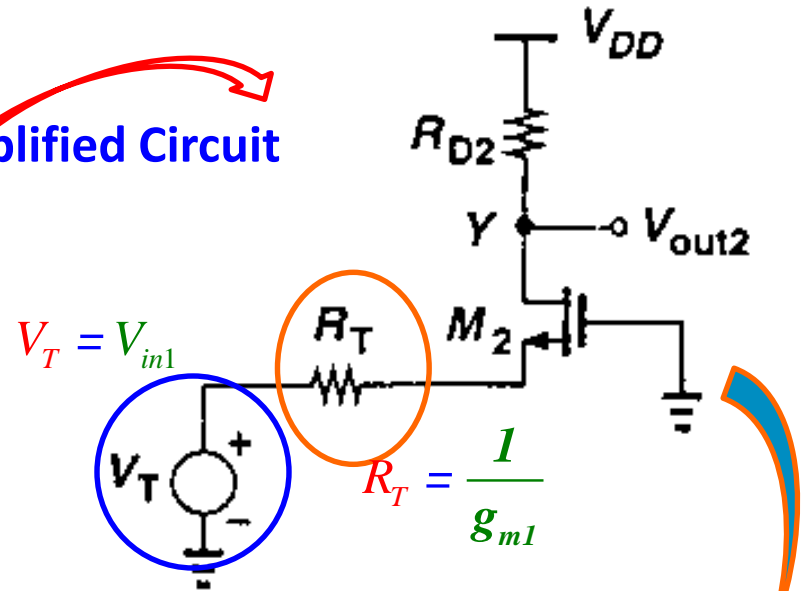

CG-Stage

$$\therefore \frac{V_Y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

MOS Differential Pair – small signal analysis

- Superposition technique

- Now combine the expressions to calculate small signal voltage only due to V_{in1}

For matched transistors

$$\frac{(V_X - V_Y)|_{due_to_V_{in1}}}{V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$(V_X - V_Y)|_{due_to_V_{in1}} = -g_m R_D V_{in1}$$

- Similarly: $(V_X - V_Y)|_{due_to_V_{in2}} = g_m R_D V_{in2}$


- Superposition gives $A_v = \frac{(V_X - V_Y)_{total}}{V_{in2} - V_{in1}} = -g_m R_D$

- The magnitude of differential gain is $g_m R_D$ regardless of how the inputs are applied
- The gain will be halved if single ended output is considered

MOS Differential Pair – small signal analysis


- **Half Circuit Approach**

 - If a fully symmetric differential pair senses differential inputs (i.e, the two inputs change by equal and opposite amounts from the equilibrium condition), then the concept of half circuit can be applied.



MOS Differential Pair – small signal analysis

- Half Circuit Approach

 

We can write:

$$\frac{V_X}{V_{in1}} = -g_m R_D$$

$$\frac{V_Y}{-V_{in1}} = -g_m R_D$$

Therefore the differential output can be expressed as:

$$V_X - V_Y = 2V_{in1} (-g_m R_D)$$

Thus the small signal voltage given is:


$$A_v = \frac{V_X - V_Y}{2V_{in1}} = -g_m R_D$$

MOS Differential Pair – small signal analysis

- How does the gain of a differential amplifier compare with a CS stage?
 - For a given total bias current I_{SS} , the value of equivalent g_m of a differential pair is $1/\sqrt{2}$ times that of g_m of a single transistor biased at the I_{SS} with the same dimensions. Thus the total gain is proportionally less.
 - Equivalently, for given device dimensions and load impedance, a differential pair achieves the same gain as a CS stage at the cost of twice the bias current.
- What is the advantage of differential stage then?
 - Definitely the noise suppression capability. Right?

MOS Differential Pair – small signal analysis

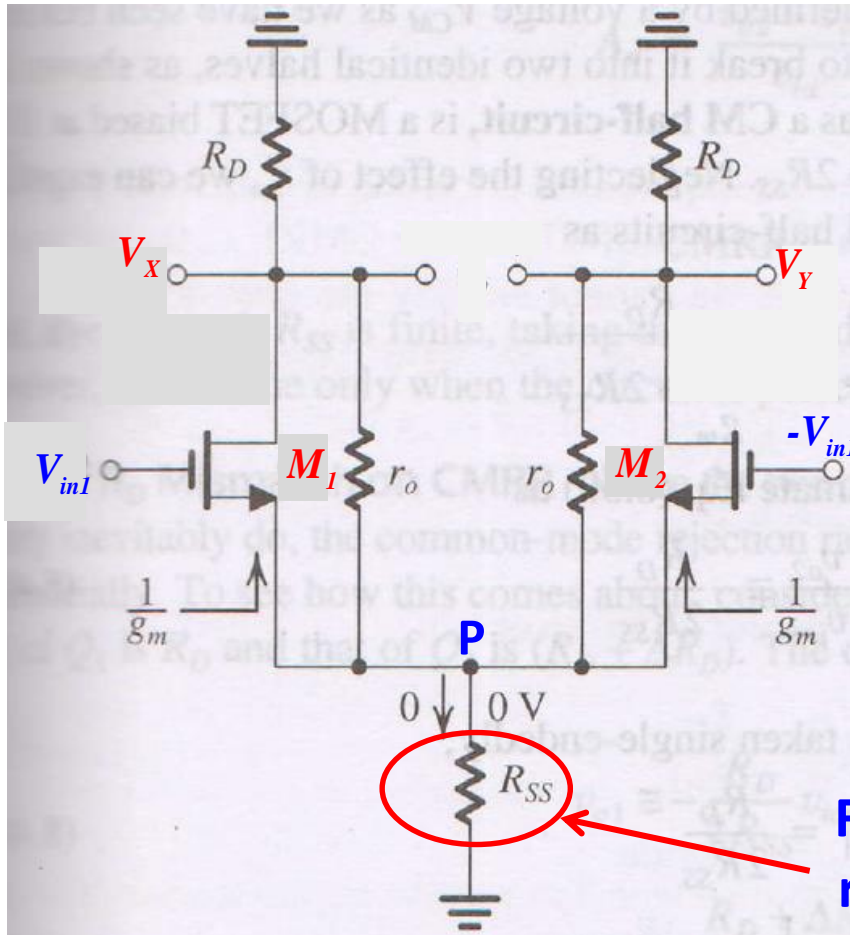- How is gain affected if channel length modulation is considered?



- Effect of r_o on the gain

→ the circuit is still symmetric → the voltage at node P will be zero



No current through R_{SS}




R_{SS} plays no role in differential gain

Finite output resistance of current source

MOS Differential Pair – small signal analysis

 - The virtual ground on the source allows division of two identical CS amplifiers: → differential half circuits




$$V_X = -g_m V_{in1} (R_D \parallel r_o)$$

$$V_Y = g_m V_{in1} (R_D \parallel r_o)$$


$$\Rightarrow V_X - V_Y = -g_m (2V_{in1}) (R_D \parallel r_o)$$

$$\therefore A_v = \frac{V_X - V_Y}{2V_{in1}} = -g_m (R_D \parallel r_o)$$

 
Small signal analysis – asymmetric inputs



 Small signal analysis – asymmetric inputs



Circuit for Differential Mode

 

Circuit for Common Mode

$$V_X - V_Y = -g_m (R_D \parallel r_o) (V_{in1} - V_{in2})$$


If the circuit is fully symmetric and I_{SS} is ideal current source, then M_1 and M_2 draws half of I_{SS} and is independent of $V_{in,CM}$. The V_X and V_Y experience no change as $V_{in,CM}$ varies. In essence, the circuit simply amplifies the difference between V_{in1} and V_{in2} while eliminating the effect of $V_{in,CM}$.

MOS Differential Pair – Common Mode Response


Quantitative Analysis

- In ideal condition, differential pair has the ability to suppress variations in the common-mode voltage
- However, in practical scenarios there is always some CM output

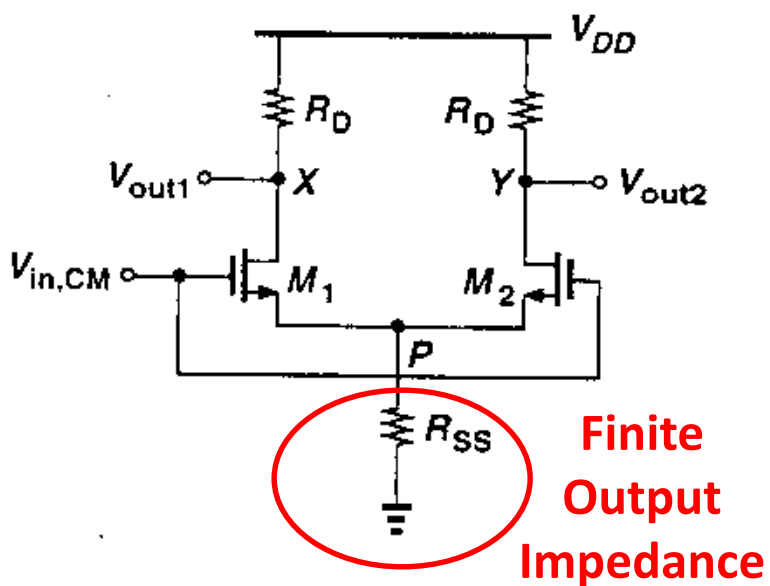Case-I: differential pair is symmetric but the current source has finite output impedance.




 Symmetry
allows shorting
of node X and Y
as $V_X = V_Y$



MOS Differential Pair – Common Mode Response (contd.)

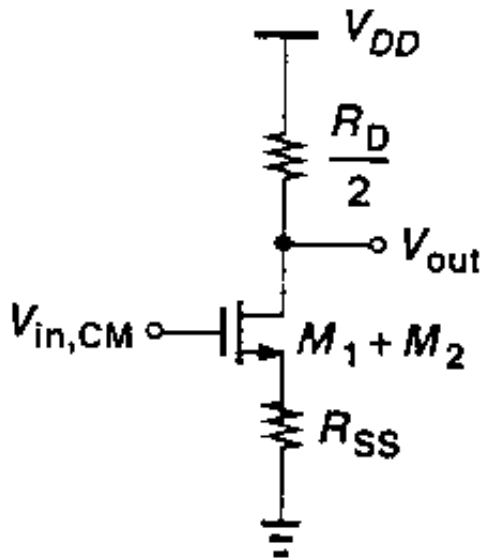- Shorting of X and Y brings M_1 and M_2 in parallel \rightarrow they share all of their respective terminals



The CM gain is then:

$$A_{v,CM} = \frac{V_{out}}{V_{in,CM}} = -\frac{R_D / 2}{1 / (2g_m) + R_{SS}}$$


This shows that in a symmetric differential pair, input CM variations disturb the bias points altering the gain

Thus the finite output impedance of the tail current source results in some common-mode gain in a symmetric differential pair

In addition, input CM variations also limit the output voltage swings

MOS Differential Pair – Common Mode Response (contd.)

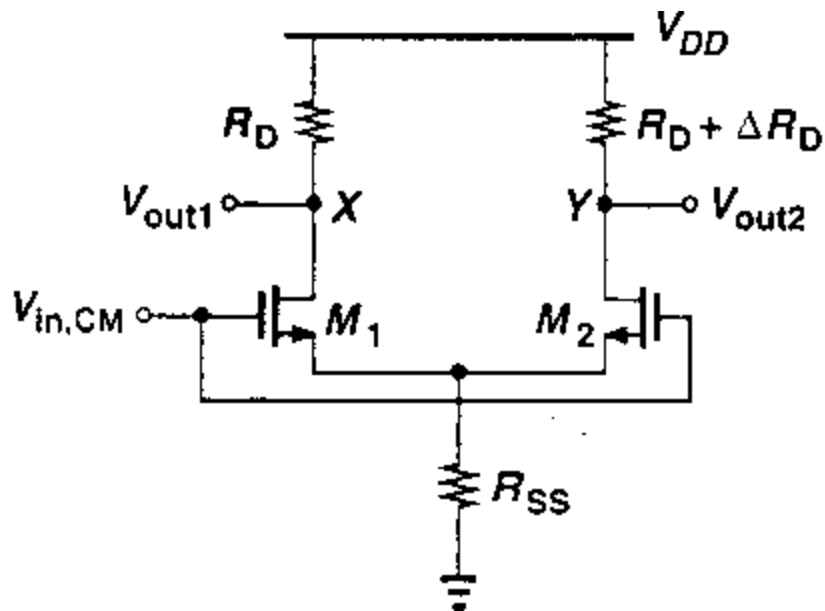Case-II: Effect of input common-mode variation when there is mismatch in R_D and the differential pair suffers from finite output impedance of current source.



- What happens to V_X and V_Y as $V_{in,CM}$ increases?
- Since M_1 and M_2 are symmetric $\rightarrow I_{D1}$ and I_{D2} increases by same amount:

$$\Delta I_D = \frac{g_m}{1 + 2g_m R_{SS}} \Delta V_{in,CM}$$

- The respective change in V_X and V_Y are given by:


$$\Delta V_X = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} R_D$$

$$\Delta V_Y = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$

MOS Differential Pair – Common Mode Response (contd.)

- Therefore the differential output due to mis-matched R_D is:

$$\Rightarrow \Delta V_X - \Delta V_Y = -\Delta V_{in,CM} \left[\frac{g_m}{1 + 2g_m R_{SS}} R_D - \frac{g_m}{1 + 2g_m R_{SS}} R_D - \frac{g_m}{1 + 2g_m R_{SS}} \Delta R_D \right]$$

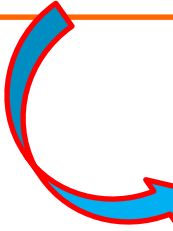
$$\therefore \Delta V_X - \Delta V_Y = \left(\frac{g_m}{1 + 2g_m R_{SS}} \Delta R_D \right) \Delta V_{in,CM}$$

- It is apparent that a small common-mode input can generate a differential mode output \rightarrow usually denoted by a metric called A_{CM-DM}


$$A_{CM-DM} = \frac{\Delta V_X - \Delta V_Y}{\Delta V_{in,CM}} = \frac{g_m}{1 + 2g_m R_{SS}} \Delta R_D$$

MOS Differential Pair – Common Mode Response (contd.)

Thus a common-mode input introduces a differential component, when the load is mis-matched, at the output

circuit exhibits common-mode to differential conversion

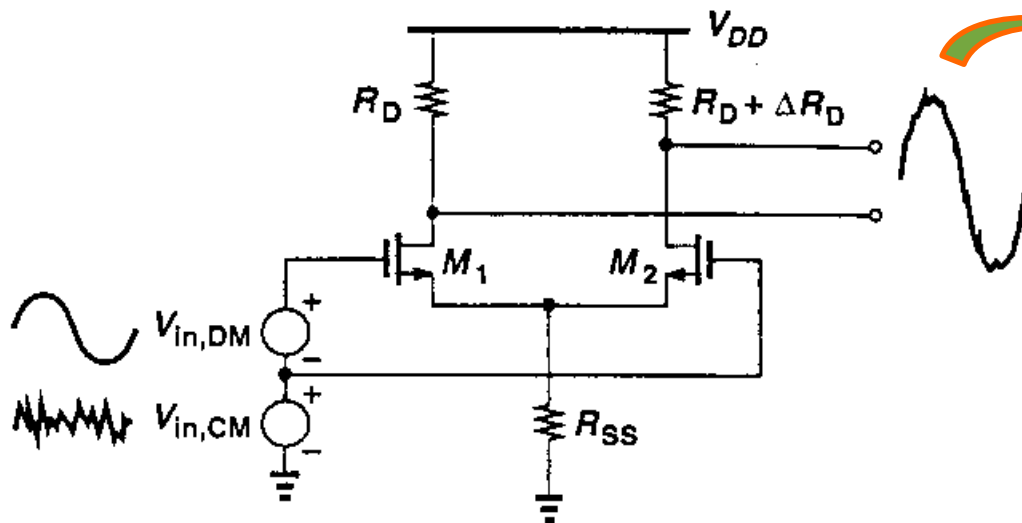if the input of a differential pair includes both a differential signal and common-mode noise, the output is corrupted version of the input




Big concern for Analog
Circuits

Common-Mode Response (contd.)

Impact of common-mode to differential conversion

 - With the increase in frequency of operation, the total capacitance (arising from the parasitics of the current source and the source-bulk junctions of M_1 and M_2) shunting the tail current source introduces larger tail current variations \rightarrow **This large variation causes substantial common-mode to differential conversion even for very high output impedance of current source**



Furthermore, The asymmetry due to load impedance mismatch (and hence the resulting common-mode to differential conversion) corrupts the amplified differential output

Common-Mode Response (contd.)


Impact of common-mode to differential conversion

- **Summary: the common mode response of differential pairs depend on the output impedance of the tail current and the asymmetries in the circuit** → manifestation of two effects
 - Variation of the output CM level (in the absence of mismatches)
 - Shifting of **input common-mode variations** to **higher level at the output**
- **How about presence of mismatches?**
 - Mismatches in R_D and **mismatches in transistors (i.e, mismatches in transconductance)**
 - **The impact of transconductance mismatch on common-mode to differential conversion** is more significant

Common-Mode Response (contd.)

Case-III: Effect of mismatches between M_1 and M_2 (dimension and V_T mismatches)

 The asymmetry due to mismatch in the transistors generates slightly different currents in the two paths \rightarrow leads to unequal transconductance



$$I_{D1} = g_{m1} (V_{in,CM} - V_P)$$

$$I_{D2} = g_{m2} (V_{in,CM} - V_P)$$

$$V_P = (I_{D1} + I_{D2}) R_{SS}$$

No more AC
grounded

$$\Rightarrow V_P = \frac{(g_{m1} + g_{m2}) R_{SS}}{(g_{m1} + g_{m2}) R_{SS} + 1} V_{in,CM}$$

Common-Mode Response (contd.)

$$V_X = V_{DD} - I_{D1}R_D = V_{DD} - g_{m1}(V_{in,CM} - V_P)R_D$$

$$\Rightarrow V_X = V_{DD} - \frac{g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$\Rightarrow V_Y = V_{DD} - \frac{g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

$$\therefore V_X - V_Y = -\frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$

- The mismatch in the transistors convert the input CM variations to a differential error by a factor:

$$A_{CM-DM} = \frac{V_X - V_Y}{V_{in,CM}} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1} \text{ Unwanted}$$

Common-Mode Response (contd.)

- Ideally, this unwanted A_{CM-DM} is normalized to the wanted A_{DM} \rightarrow the normalization factor is called CMRR

$$CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right|$$

- For a differential pair with mis-matched transistor but operating at equilibrium, the differential gain is given by:

$$|A_{DM}| = \frac{R_D}{2} \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{1 + (g_{m1} + g_{m2})R_{SS}}$$

$$\Rightarrow CMRR = \left| \frac{A_{DM}}{A_{CM-DM}} \right| = \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m} = \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS})$$

- Where, $g_m = (g_{m1} + g_{m2}) / 2$

Example – 1

- In the following circuit, $(W/L)_{1,2} = 50/0.5$, $(W/L)_{3,4} = 10/0.5$ and $I_{SS} = 0.5mA$. Also, I_{SS} is implemented with an NMOS having $(W/L)_{SS} = 50/0.5$ while $V_{DD} = 3V$.
 - What are the minimum and maximum allowable input CM levels if the differential swings at the input and output are small.

 


Table 2.1 Level 1 SPICE Models for NMOS and PMOS Devices.

NMOS Model

LEVEL = 1	VTO = 0.7	GAMMA = 0.45	PHI = 0.9
NSUB = 9e+14	LD = 0.08e-6	UO = 350	LAMBDA = 0.1
TOX = 9e-9	PB = 0.9	CJ = 0.56e-3	CJSW = 0.35e-11
MJ = 0.45	MJSW = 0.2	CGDO = 0.4e-9	JS = 1.0e-8

PMOS Model

LEVEL = 1	VTO = -0.8	GAMMA = 0.4	PHI = 0.8
NSUB = 5e+14	LD = 0.09e-6	UO = 100	LAMBDA = 0.2
TOX = 9e-9	PB = 0.9	CJ = 0.94e-3	CJSW = 0.32e-11
MJ = 0.5	MJSW = 0.3	CGDO = 0.3e-9	JS = 0.5e-8

Example – 1 (contd.)

$$\left(\frac{W}{L}\right)_{SS} = \frac{50}{0.5} \quad I_{SS} = 05mA \quad \longrightarrow \quad (V_{OV})_{SS} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{SS}}} = 0.273V$$

$$I_{D1} = \frac{I_{SS}}{2} = 0.25mA \quad \longrightarrow \quad (V_{OV})_1 = 0.193V$$

$$(V_{in,CM})_{\min} = V_{GS1} + (V_{OV})_{SS} = 0.7 + 0.193 + 0.273 = 1.17V$$

$$\longrightarrow (V_{in,CM})_{\max} = V_{DD} - |V_{GS3}| + V_{TN} \quad |V_{GS3}| = |V_{TP}| + \sqrt{\frac{2I_{D3}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} = 1.61V$$

$$\therefore (V_{in,CM})_{\max} = 3 - 1.61 + 0.7 = 2.09V$$

Example – 2

- In the following circuit, $(W/L)_{1,2} = 50/0.5$ and $R_D = 2k\Omega$. Suppose R_{SS} represents the output impedance on an NMOS current source with $(W/L)_{SS} = 50/0.5$ and a drain current of 1mA. The input signal consists of $V_{in,DM} = 1.5V + V_n(t)$, where $V_n(t)$ denotes noise with a peak-to-peak amplitude of 100mV. Assume $\Delta R/R = 0.5\%$.
 - Calculate CMRR

