


## **Lecture – 16**

**Date: 12.10.2015**


- Differential Pair with Active Load
- Differential Pair with Current Mirror
- Gilbert Cell
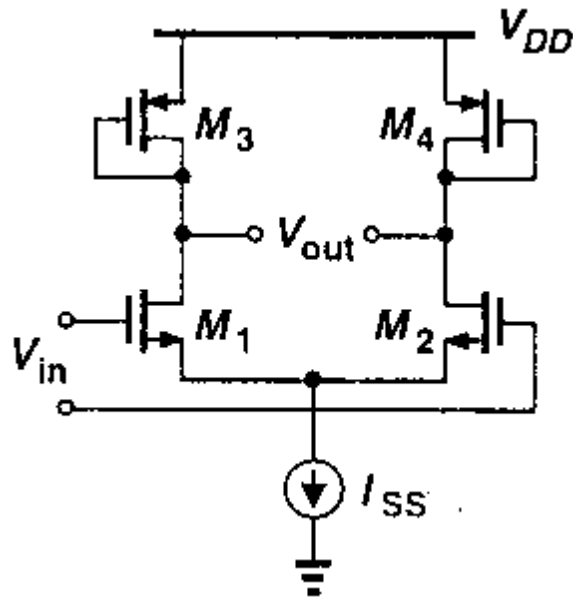
## Differential Amplifier with Active Load

- By now we know, the load resistors in differential pair can be replaced by diode-connected or source-connected loads
- It can help in mitigating the common-mode to differential conversion arising out from  $R_D$  mismatch



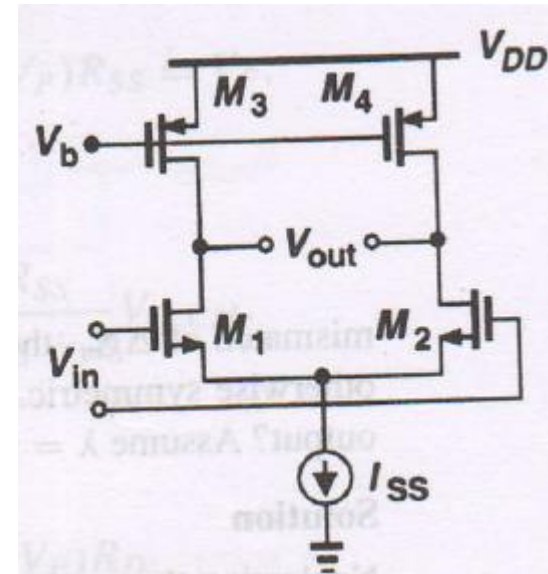
Its easier to define output CM level as  $M_3/M_4$  are in saturation by default




$M_3/M_4$  are not in saturation by default & therefore output CM level not well defined

## Differential Pair with Active Load

- Using half-circuit approach:

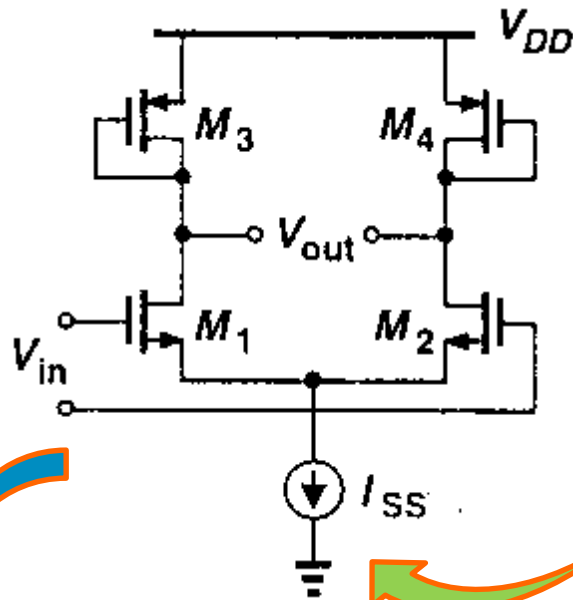

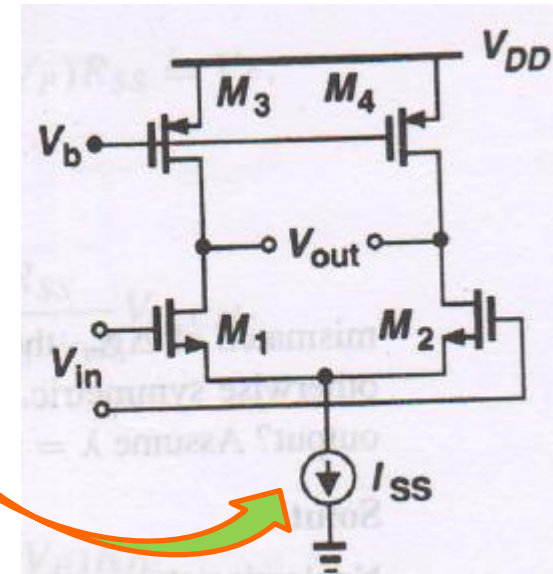Differential pair with  
ideal current source



$$A_v = -g_{mN} (r_{oN} \parallel r_{oP})$$


$$A_v = -g_{mN} (g_{mP}^{-1} \parallel r_{oN} \parallel r_{oP})$$

$$\therefore A_v \approx -\frac{g_{mN}}{g_{mP}} = -\sqrt{\frac{\mu_n (W/L)_N}{\mu_P (W/L)_P}}$$

## Gilbert Cell

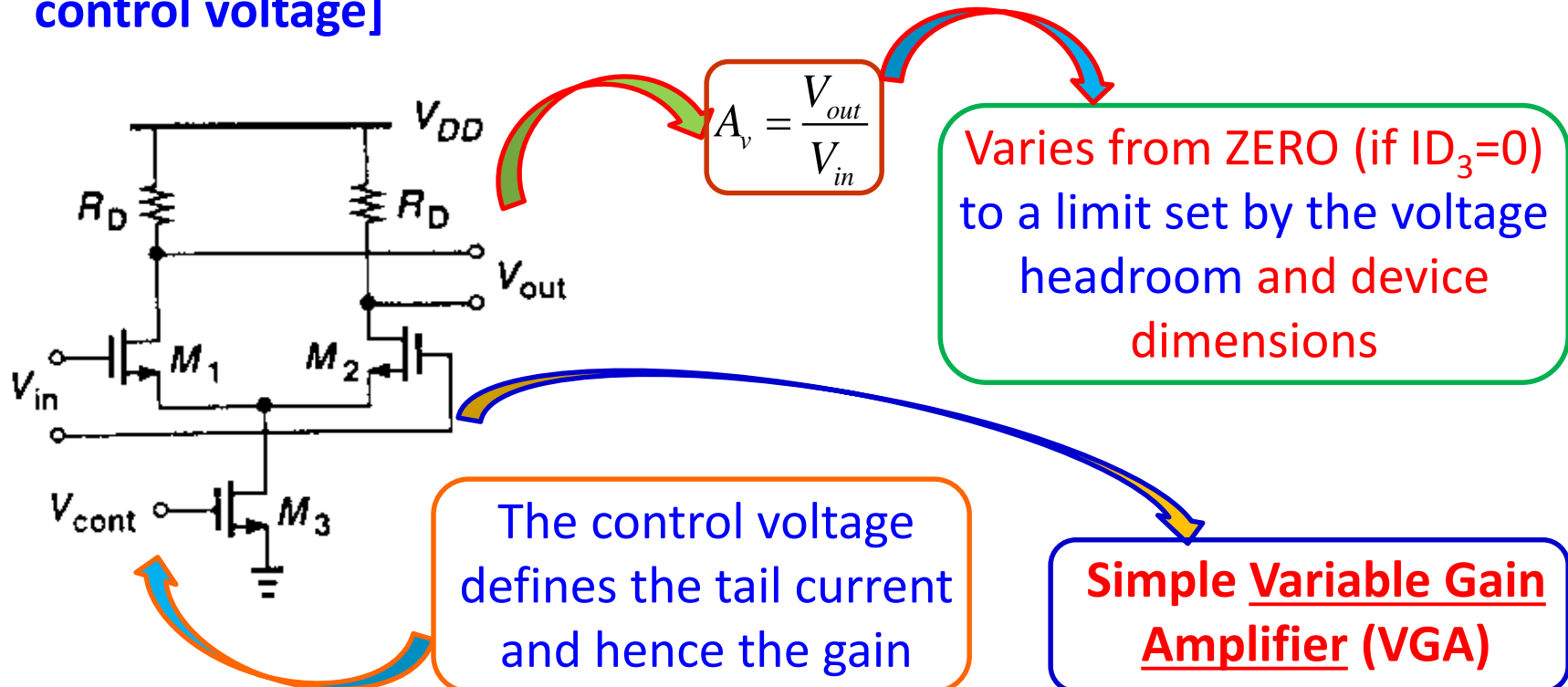
### Two important aspects of differential pair

- **small signal gain is function of tail current**
- **the whole tail current can be steered to one of two paths by some means**
- These features can be utilized to design very interesting and useful circuit known as Gilbert Cell [a differential pair whose gain can be varied by control voltage]


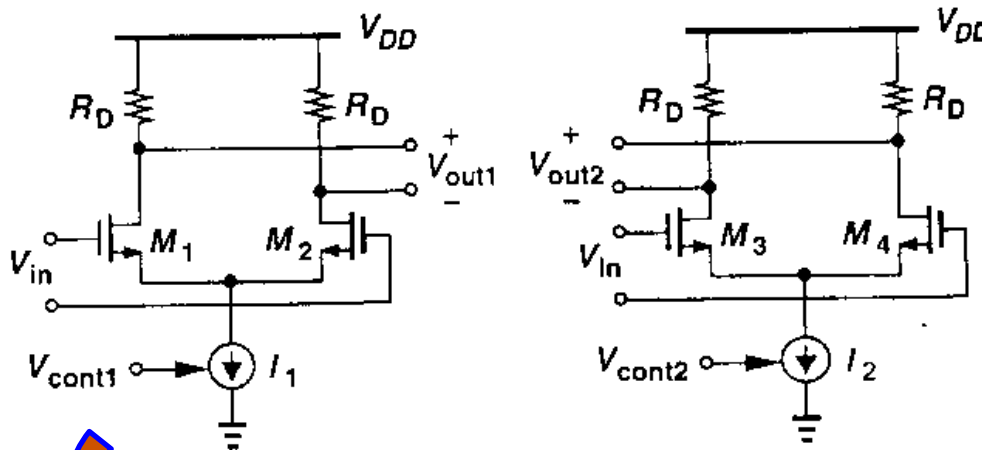
## Gilbert Cell (contd.)

- Suppose we require an amplifier whose gain can be continuously varied from a **NEGATIVE** value to a **POSITIVE** value.
- **Definitely, two VGA with opposite gains.**




This pair of VGA should be designed in such a way that they give opposite gains

$V_{out1}/V_{in} = -g_m R_D$  and  $V_{out2}/V_{in} = +g_m R_D \leftrightarrow$  require variation of  $I_1$  and  $I_2$  in opposite directions


How to combine  $V_{out1}$  and  $V_{out2}$  in a single output?
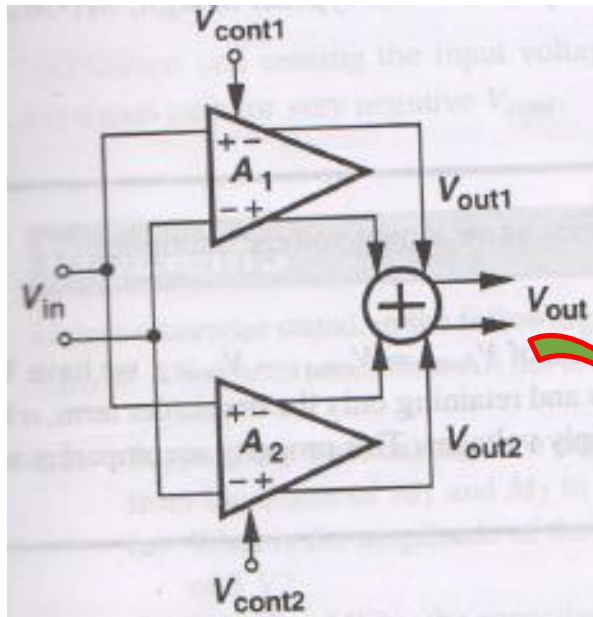
## Gilbert Cell (contd.)

How to combine  $V_{out1}$  and  $V_{out2}$  in a single output?



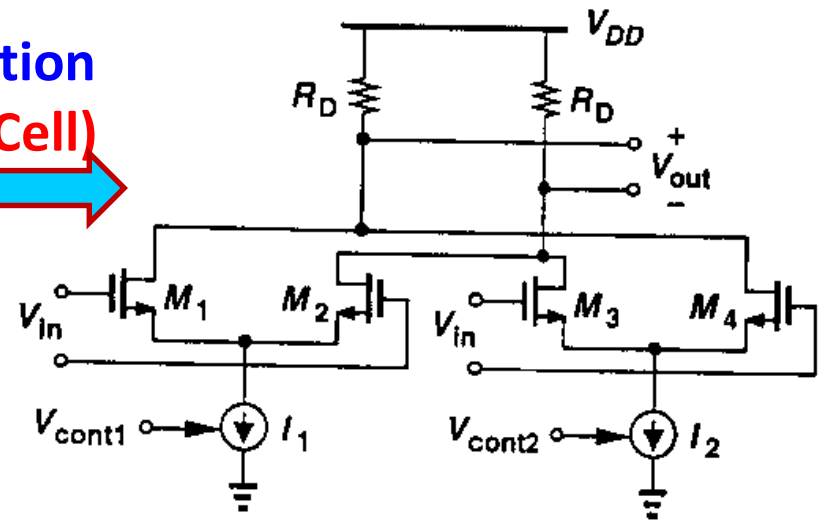Actual  
Implementation  
(i.e, Gilbert Cell)




$$V_{out} = V_{out1} + V_{out2} = A_1 V_{in} + A_2 V_{in}$$

$A_1$  and  $A_2$  controlled by  $V_{cont1}$  and  $V_{cont2}$  respectively

Here, instead of adding  $V_{out1}$  and  $V_{out2}$ , the drain terminals are shorted to sum the currents and subsequently generate the output voltage
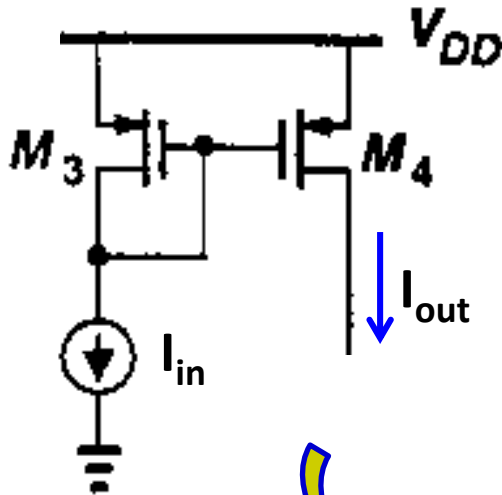
## Active Current Mirror

- We know: CM can also process signals i.e, operate as “active” elements




Here,  $I_{out} = I_{in}$  if we assume  $M_1$  and  $M_2$  are identical and  $\lambda = 0$

With the direction shown, this circuit performs no inversion → for small signal point of view, if  $I_{in}$  increases by  $\Delta I$  then  $I_{out}$  also increases by  $\Delta I$
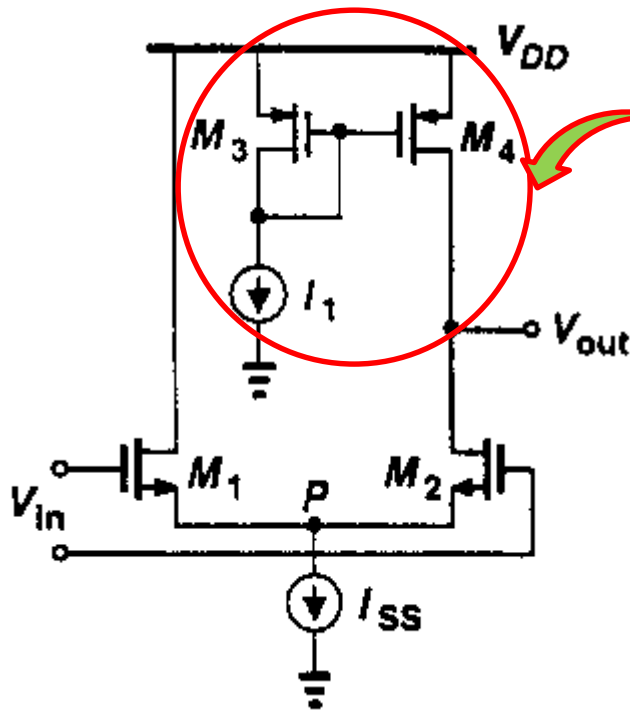
## Active Current Mirror (contd.)

- Now, let us consider following configuration in which a differential amplifier is loaded with a CM and the output is single ended




Current Mirror

$$G_m = \frac{I_{in}}{V_{in}} = \frac{(g_{m1} V_{in}) / 2}{V_{in}} = \frac{g_{m1}}{2}$$


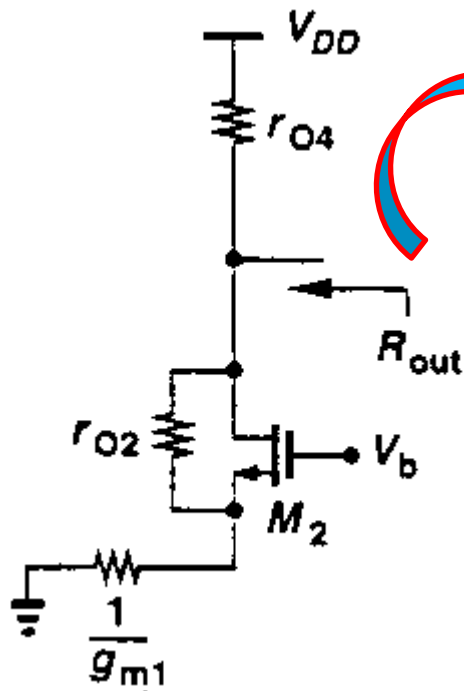
## Active Current Mirror (contd.)

- For output impedance, the circuit can be simplified into following:



$$R_{out} = \left( (1 + g_{m2}r_{o2}) \left( \frac{1}{g_{m1}} + r_{o2} \right) \parallel r_{o4} \right) \approx \left( \frac{1}{g_{m1}} + 2r_{o2} \right) \parallel r_{o4} \approx 2r_{o2} \parallel r_{o4}$$

$$\therefore A_v = G_m R_{out} \approx \frac{g_{m1}}{2} (2r_{o2} \parallel r_{o4})$$


Smaller than a simple  
differential pair

If  $r_{o4} \rightarrow \infty$ , then  $A_v \rightarrow g_{m1}r_{o2}$


In this configuration, the small-signal drain current of  $M_1$  is wasted  
→ this is partly responsible for reduction in gain
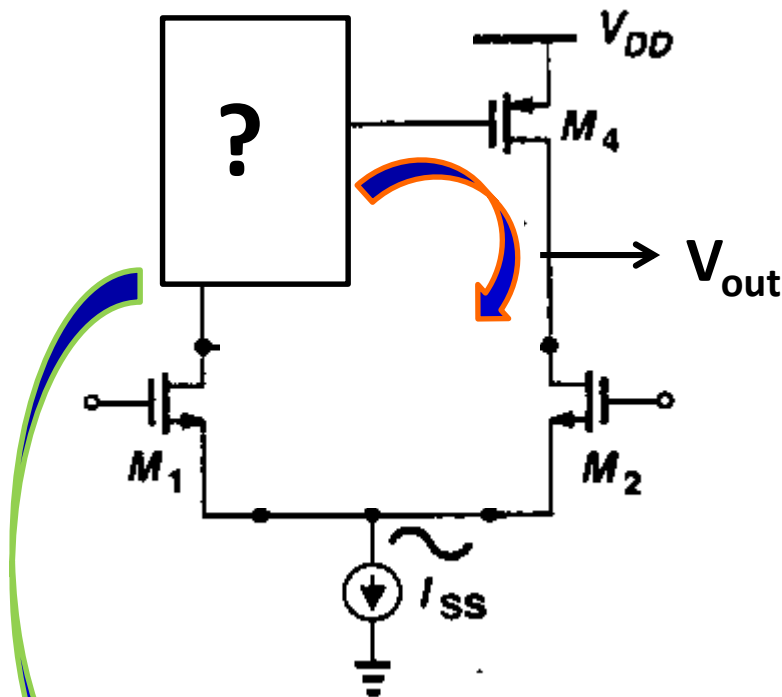
## Active Current Mirror (contd.)

- Therefore it is desirable to **utilize the drain current of  $M_1$**  to enhance  $A_v$
- Following configuration depicts a scenario:



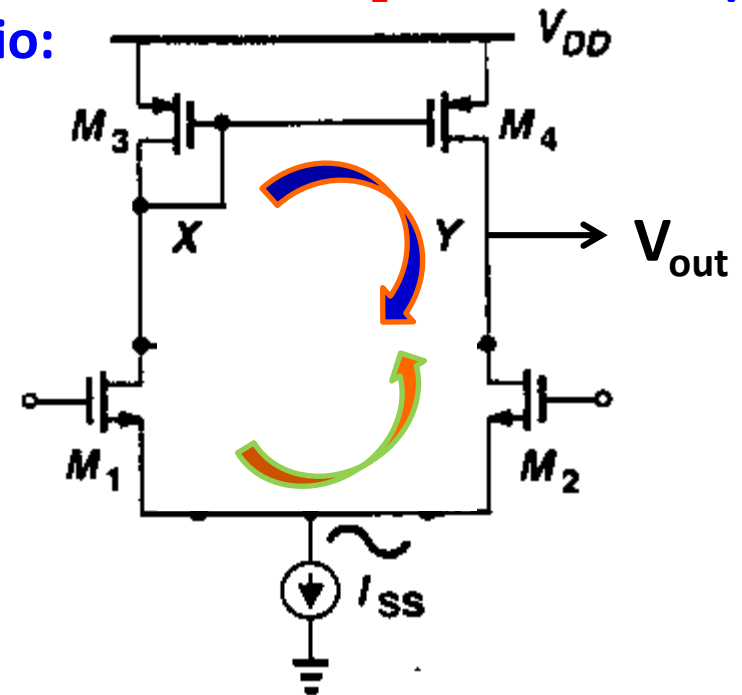This block has to be designed to provide the required functionality





To see how  $M_3$  enhances the gain

Suppose  $V_{G1}$  increases by small amount  $\rightarrow$  leads to increase in  $I_{D1}$  by  $\Delta I$  and decrease in  $I_{D2}$  by  $\Delta I$   
 $\rightarrow I_{D3}$  and  $I_{D4}$  increases by  $\Delta I$  and decreases the  $V_{DS}$  of  $M_2$   $\rightarrow$  increases  $V_{out}$   $\rightarrow$  active current mirror functionality


## Active Current Mirror (contd.)

Combine Drain Currents to Enhance Gain

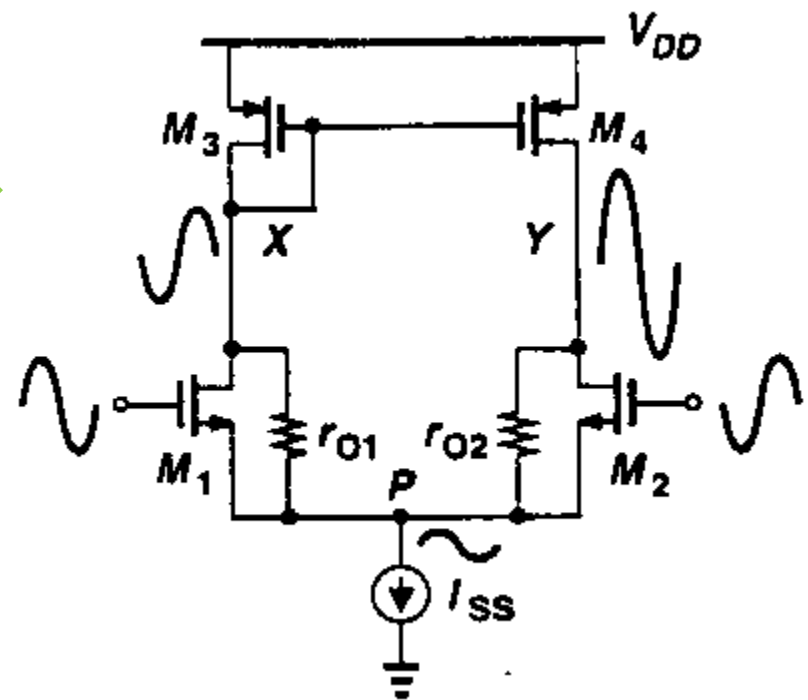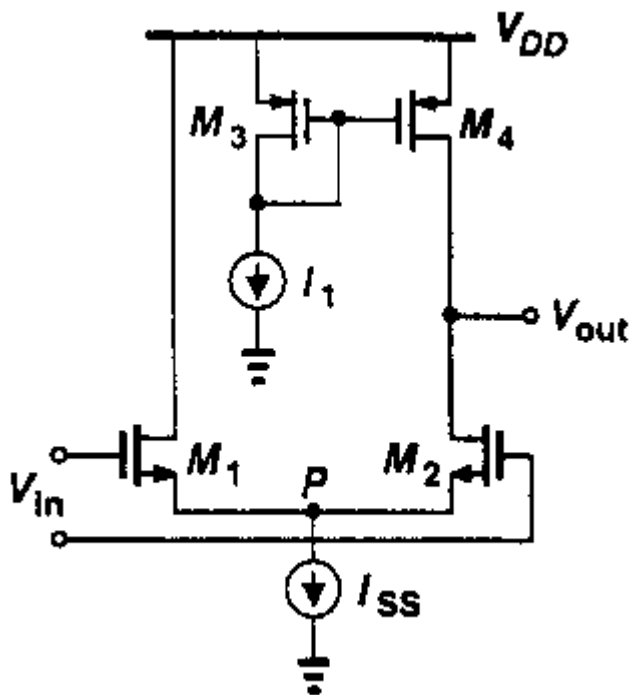

## Active Current Mirror (contd.)

### Small Signal Analysis

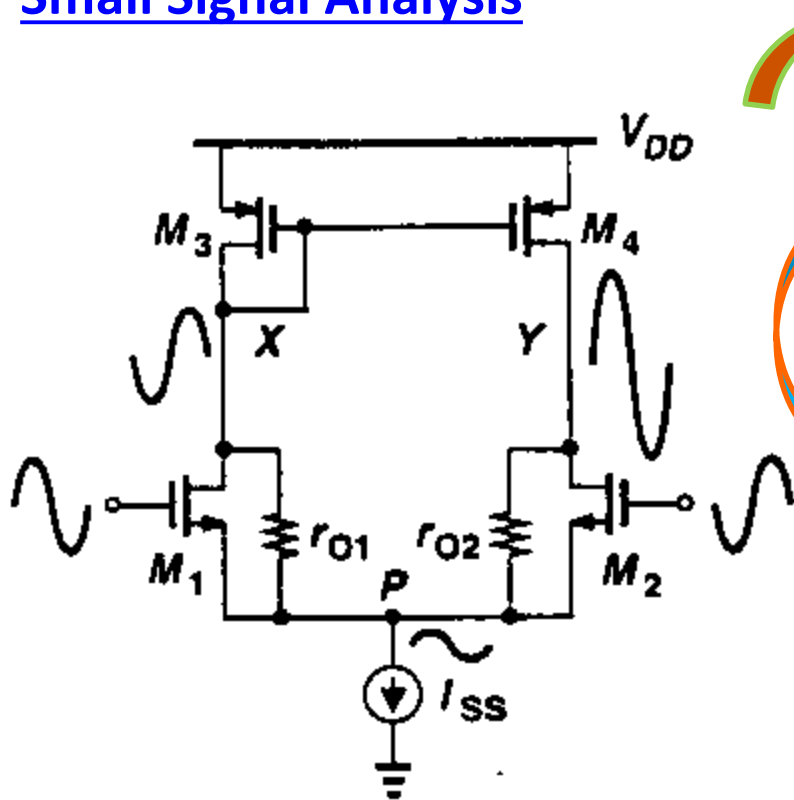


The voltage swings at both X and Y nodes are different

Because the diode-connected  $M_3$  yields a much lower gain from the input to node X as compared to gain from input to node Y

The effects of  $V_x$  and  $V_y$  are different at node P  $\leftrightarrow$  therefore the node P isn't really ac-grounded

## Active Current Mirror (contd.)

### Small Signal Analysis

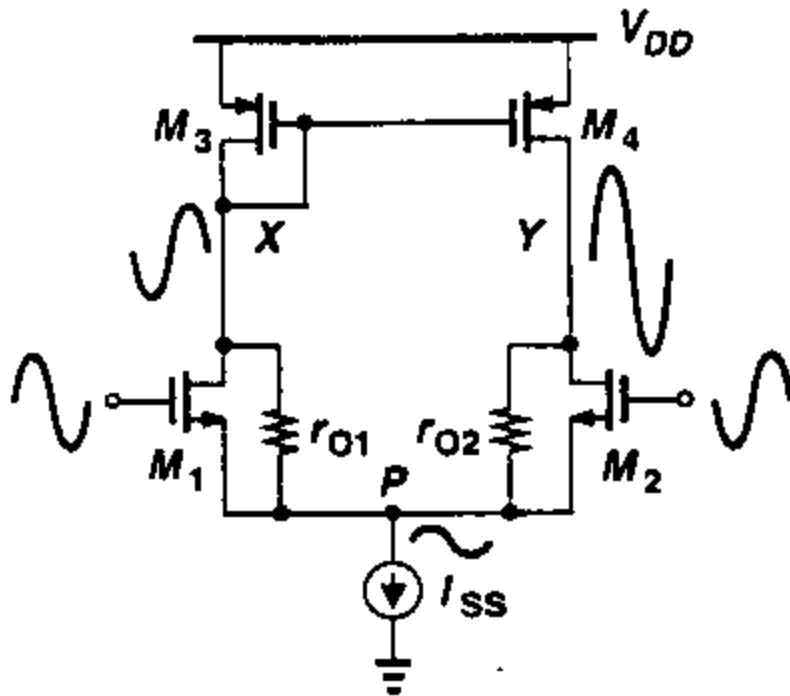


$$\therefore A_v = g_{m1} (r_{o2} \parallel r_{o4})$$

Higher than the  
earlier circuit

# Active Current Mirror (contd.)


## Common Mode Analysis

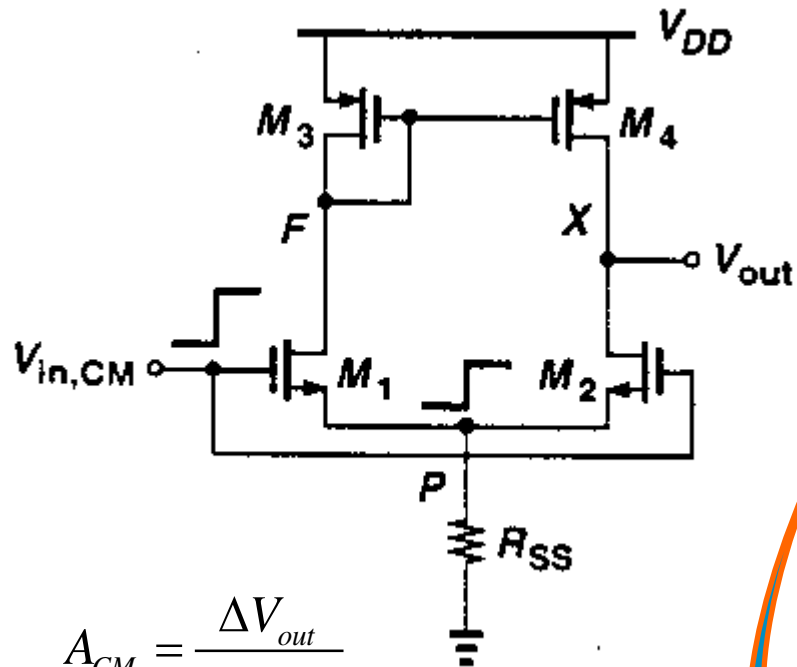

$$A_{CM} = \frac{\Delta V_{out}}{\Delta V_{in,CM}}$$

With perfect symmetry  $V_{X,DC} = V_{F,DC}$


Allows shorting  
of node X and  
node F

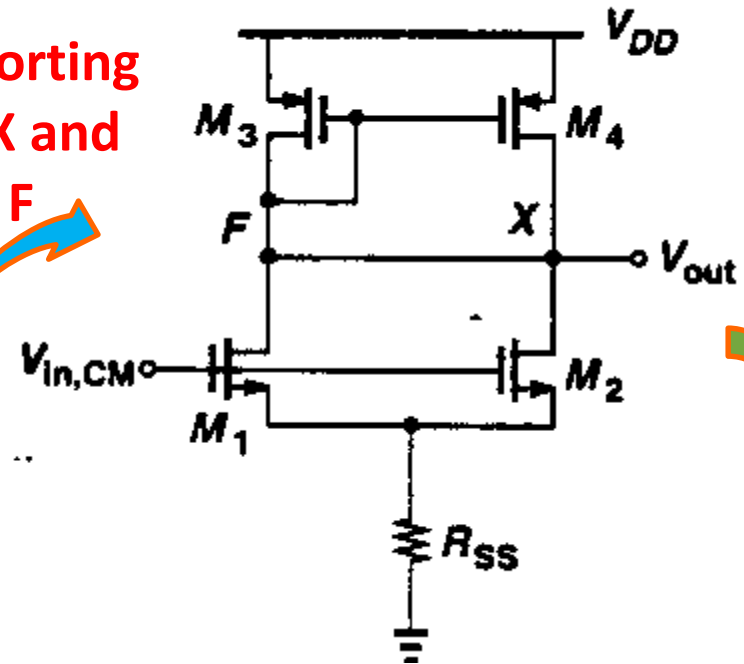

This is for any input CM level. For example, as  $V_{in,CM}$  increases,  $V_F$  drops and so does  $V_{out}$

# Active Current Mirror (contd.)

## Common Mode Analysis

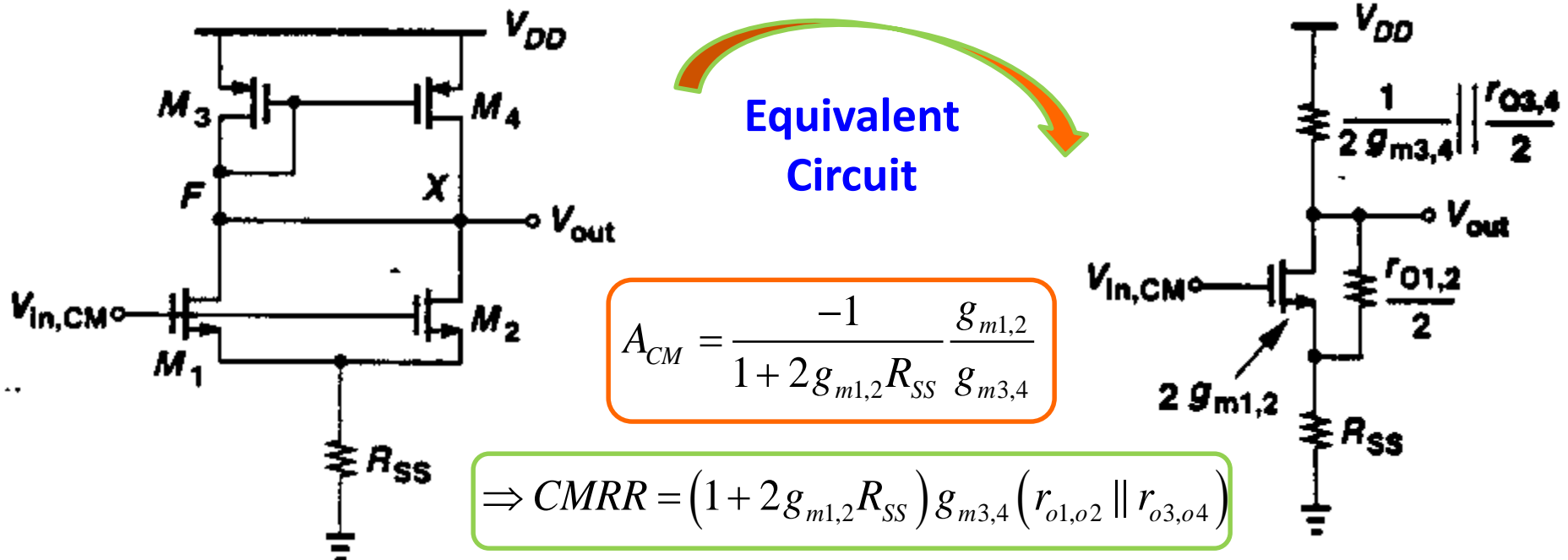

Even with perfect symmetry, the output signal will be corrupted by input CM variations, a drawback that is smaller in fully differential circuits. The problem will be more serious at high frequencies