


## Lecture – 19

Date: 31.10.2015

- CS Stage (contd.)
- CS stage with Degeneration Resistor  $R_{deg}$
- Common Drain (CD) Stage
- Common Gate Topology
- Cascode Configuration

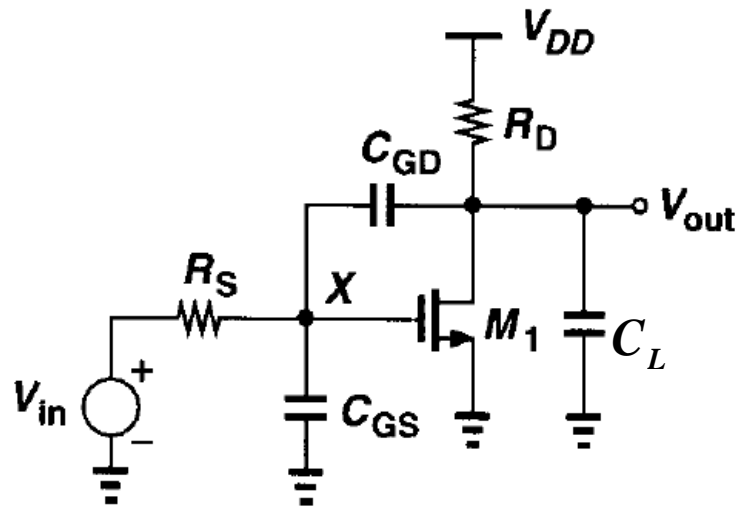
## Quiz – 6

Q: For the CS Topology, find the poles and zeros using Miller's Approximation, OCTC, and Exact Analysis.



## Common Source Amplifier (contd.)
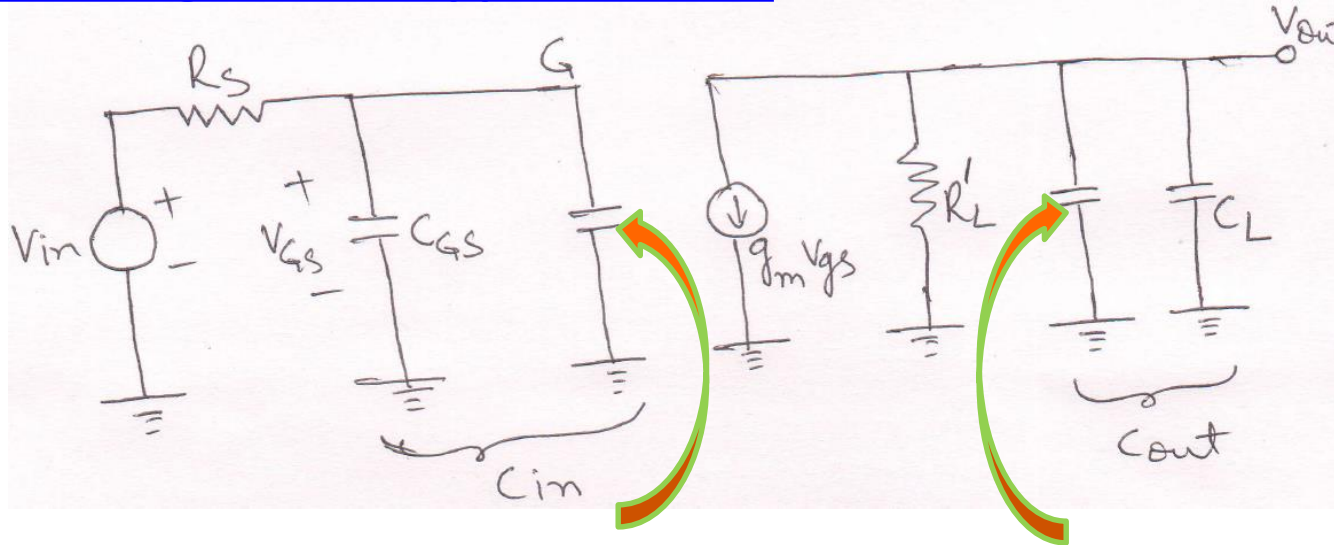
### Analysis using Miller's Approximation



$$C_A = (1 - A_v)C_{GD} = (1 + g_m R_L')C_{GD} \quad C_B = (1 - A_v^{-1})C_{GD} \approx C_{GD}$$

Therefore the poles are:

$$\omega_{in} = \frac{1}{R_S C_{in}} = \frac{1}{R_S (C_{GS} + C_A)} = \frac{1}{R_S (C_{GS} + (1 + g_m R_L')C_{GD})}$$

$$\omega_{out} = \frac{1}{R_L' C_{out}} = \frac{1}{R_L' (C_L + C_B)} = \frac{1}{R_L' (C_L + C_{GD})}$$

## Common Source Amplifier (contd.)

Then the transfer function is given by:

$$H(s) = \frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

When  $R_S$  is large  
and  $C_L$  is small



$\omega_{in}$  dominates, and the transfer function becomes:

$$H(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right)}$$



$$H(s) = \frac{A_M}{1 + \frac{s}{\omega_H}}$$

**Dominant Pole**

3-dB Frequency:

$$f_H = \frac{1}{2\pi C_{in} R_S}$$

Where,


$$C_{in} = C_{GS} + C_{GD}(1 + g_m R'_L)$$

The main error in this expression is that the presence of zero has not been considered

## Common Source Amplifier (contd.)
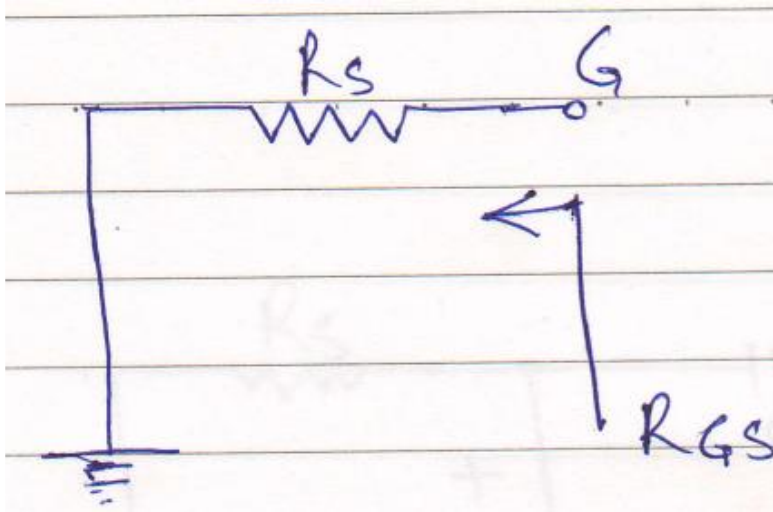
### Analysis using OCTC Method


- Considering only  $C_{GS}$  → open other capacitances and short the voltage sources and open the current sources
- For  $R_{GS}$  we get:



$$R_{GS} = R_S$$
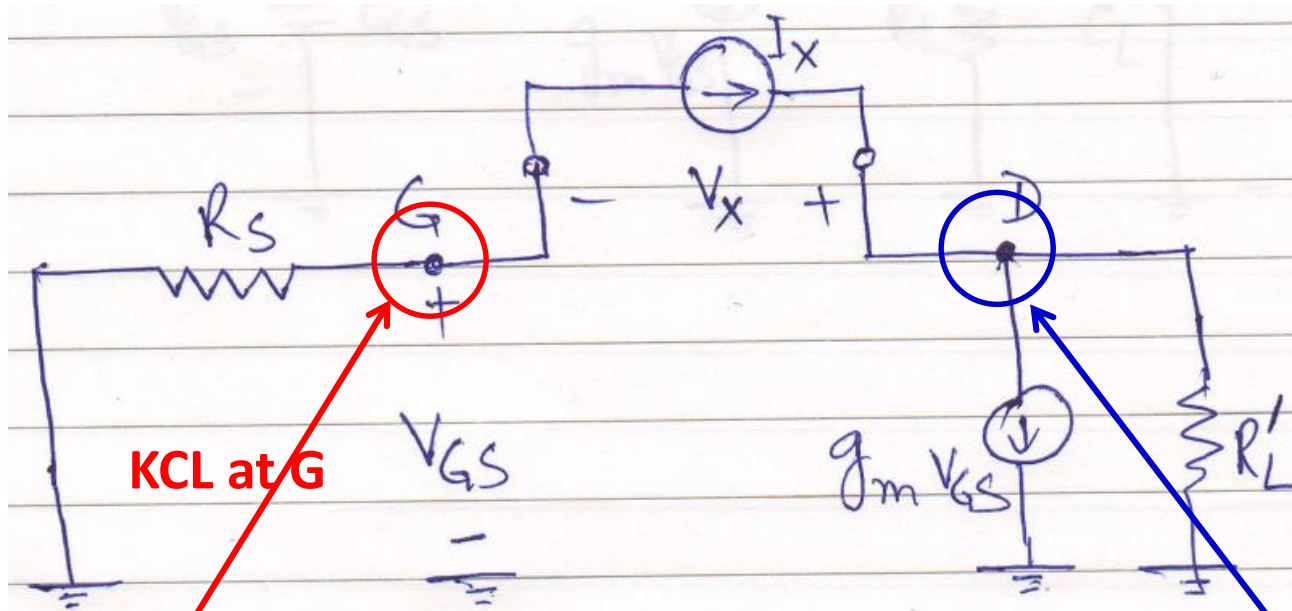
## Common Source Amplifier (contd.)

- Considering only  $C_{GD} \rightarrow$  open  $C_{GS}$  and  $C_L$



Then,  $R_{GD} = \frac{V_X}{I_X}$


$$\frac{V_{GS}}{R_S} + I_X = 0$$

$$I_X = g_m V_{GS} + \frac{V_{GS} + V_X}{R'_L}$$

$$\Rightarrow R_{GD} = \frac{V_X}{I_X} = R_S + (1 + g_m R_S) R'_L$$
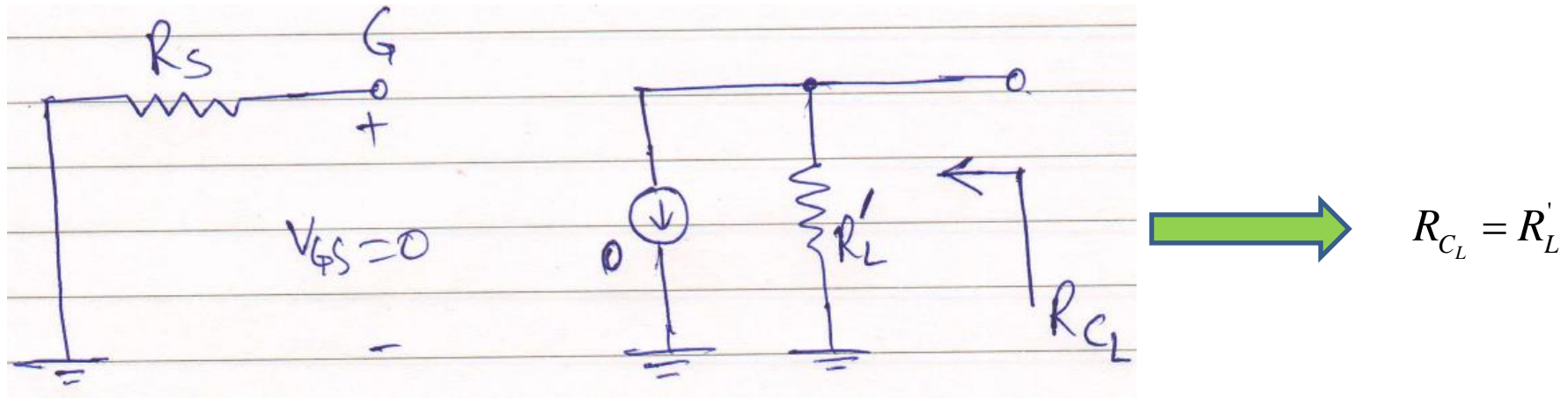
## Common Source Amplifier (contd.)

- Considering only  $C_L \rightarrow$  open  $C_{GS}$  and  $C_{GD}$



Thus, the effective time constant:  $\tau_H = C_{GS}R_{GS} + C_{GD}R_{GD} + C_L R_{C_L}$

Therefore the 3-dB roll-off frequency is:


$$f_H = \frac{1}{2\pi\tau_H}$$

**Provides a better  
estimate than Miller's  
approximation**

## Common Source Amplifier (contd.)
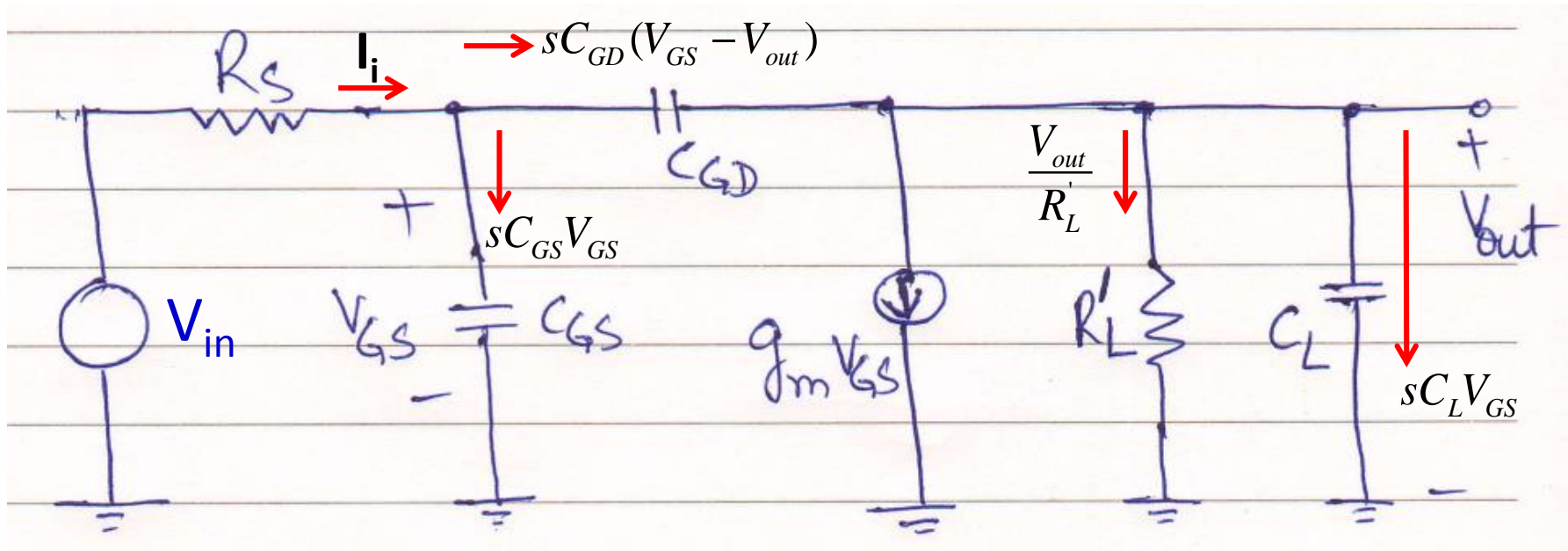
### Exact Analysis

- Miller's Approximation and OCTC Technique provides insight about the impact of various capacitances on the high frequency response of amplifier
- However, for simple circuits its imperative to carry out exact analysis



KCL at the drain: 
$$sC_{GD}(V_{GS} - V_{out}) = g_m V_{GS} + \frac{V_{out}}{R'_L} + sC_L V_{out}$$



## Common Source Amplifier (contd.)

KCL at the drain:  $sC_{GD}(V_{GS} - V_{out}) = g_m V_{GS} + \frac{V_{out}}{R'_L} + sC_L V_{out}$

$$V_{GS} = \frac{-V_{out}}{g_m R'_L} \frac{1 + s(C_L + C_{GD})R'_L}{1 - (sC_{GD} / g_m)}$$

KVL at the gate:  $V_{in} = I_i R_S + V_{GS}$

KCL at the gate:  $I_i = sC_{GS} V_{GS} + sC_{GD}(V_{GS} - V_{out})$

$$V_{in} = V_{GS} [1 + s(C_{GS} + C_{GD})R_S] - sC_{GD}R_S V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-(g_m R'_L) [1 - s(C_{GD} / g_m)]}{1 + sA + s^2 B}$$

Where,

$$A = [C_{GS} + C_{GD}(1 + g_m R'_L)]R_S + (C_L + C_{GD})R'_L$$

$$B = [(C_L + C_{GD})C_{GS} + C_L C_{GD}]R_S R'_L$$

## Common Source Amplifier (contd.)

### Observations

- There exists one zero  $\rightarrow$  not known through the approximate analysis
- 2<sup>nd</sup> order denominator  $[D(s)] \rightarrow$  presence of two poles
- There are three capacitances  $\rightarrow$  why only two poles and one zero

### Poles Determination

- As  $s \rightarrow 0$ , the transfer function approaches:

$$\Rightarrow \frac{V_{out}}{V_{in}} = -\left(g_m R'_L\right) \text{ DC Gain}$$

- Let  $\omega_{p1}$  and  $\omega_{p2}$  be the two poles then:

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) = 1 + s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1}\omega_{p2}}$$

- If  $\omega_{p1}$  is dominant then:  $D(s) \cong 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$

## Common Source Amplifier (contd.)

- Now, equating the coefficients:

$$\omega_{p1} = \frac{1}{\left[ C_{GS} + C_{GD} (1 + g_m R'_L) \right] R_S + (C_L + C_{GD}) R'_L}$$

$$\omega_{p1} \omega_{p2} = \frac{1}{\left[ (C_L + C_{GD}) C_{GS} + C_L C_{GD} \right] R_S R'_L}$$

$$\Rightarrow \omega_{p2} = \frac{\left[ C_{GS} + C_{GD} (1 + g_m R'_L) \right] R_S + (C_L + C_{GD}) R'_L}{\left[ (C_L + C_{GD}) C_{GS} + C_L C_{GD} \right] R_S R'_L}$$

**Very similar to the pole determined using OCTC method with the only addition being  $R'_L (C_{GD} + C_L)$**

## Common Source Amplifier (contd.)

### Example:


$$R_S = 50 \text{ Ohms}$$

$$L = 2.0 \text{ } \mu\text{m}$$

$$A_V = 15$$

$$f_{in} = 4.65 \text{ GHz}$$

$$f_{out} = 69.9 \text{ MHz}$$

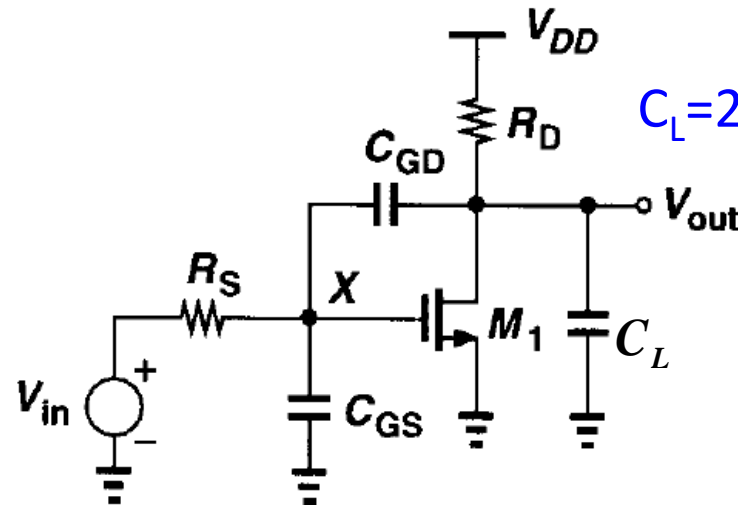


$$C_L = 27.51 \text{ fF}, R_L' = 60 \text{ KOhm}$$

$$\omega_{in} = \frac{1}{R_S (C_{GS} + (1 + g_m R_L') C_{GD})}$$


$$\omega_{out} = \frac{1}{R_L' (C_L + C_{GD})}$$

# Transfer Function

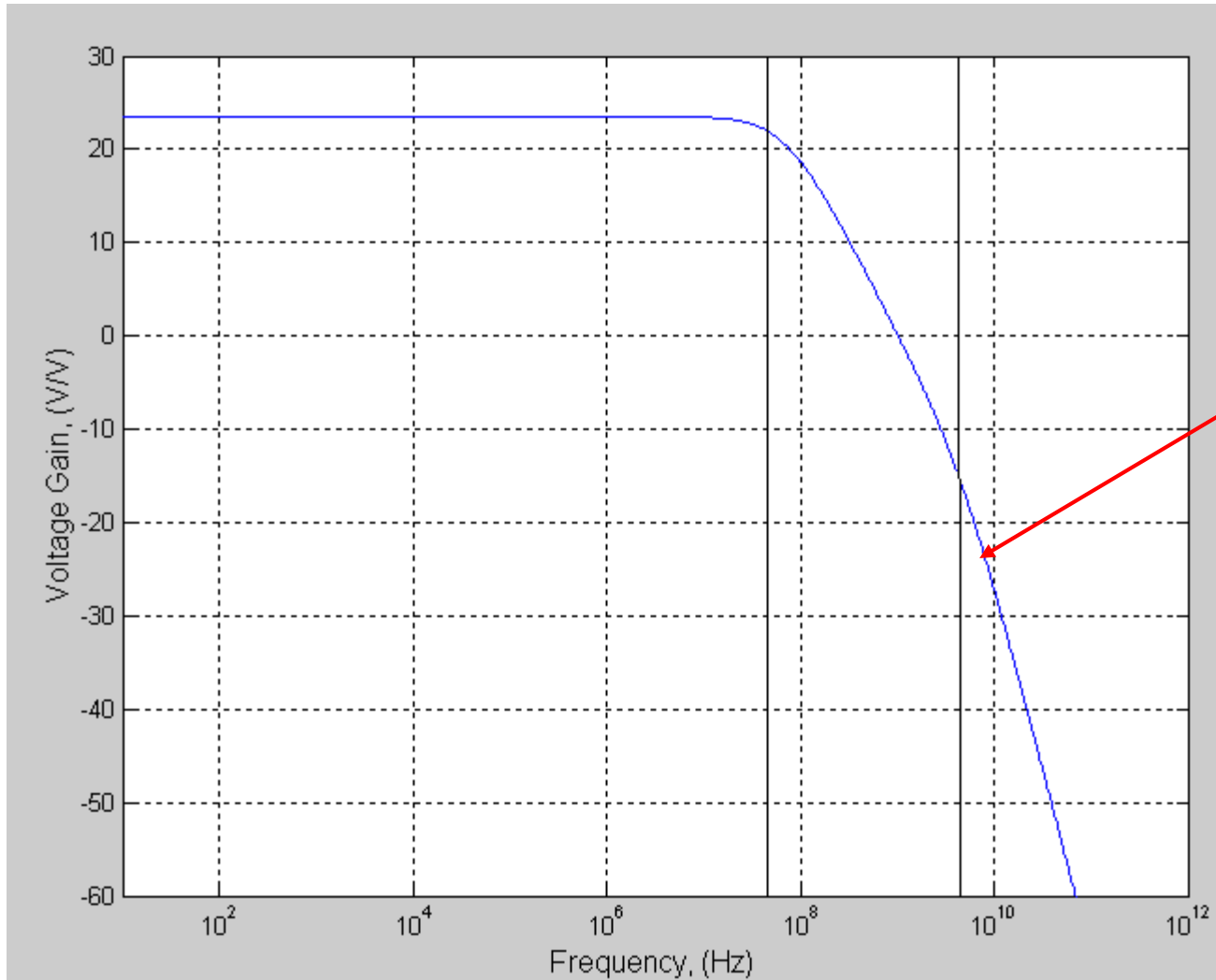

**Miller  
Approximation**

# Transfer Function

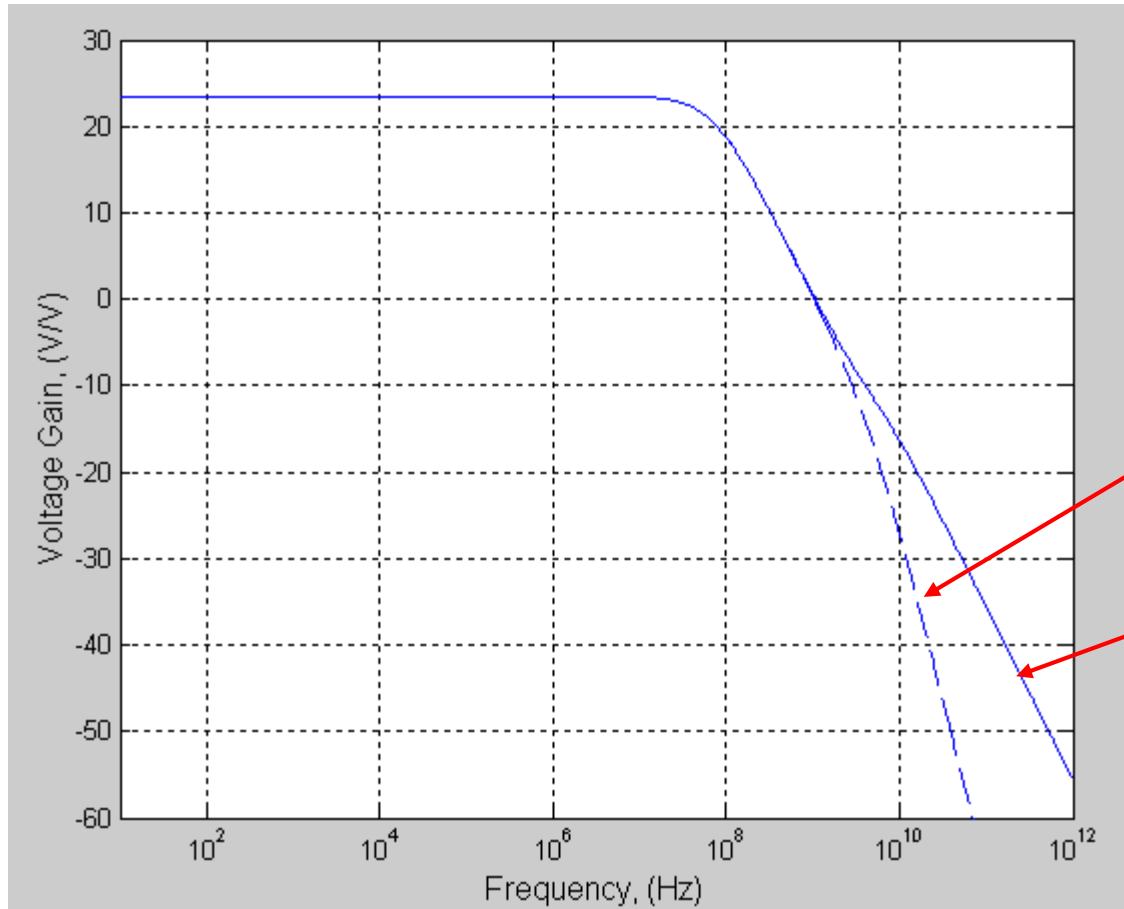

**Miller  
Approximation**



**Exact Analysis**

## Common Source Amplifier (contd.)

- There exists one zero given by:

$$\omega_{z1} = \frac{g_m}{C_{GD}}$$

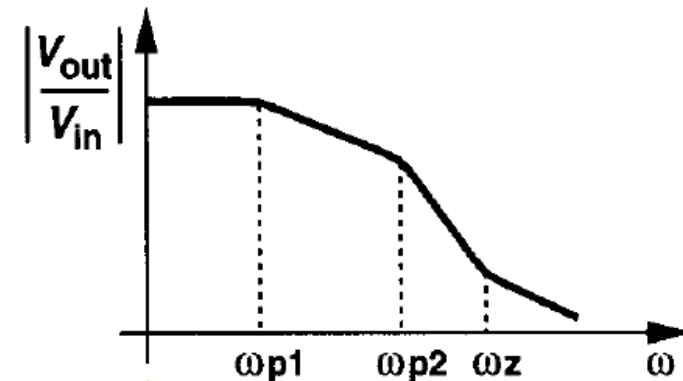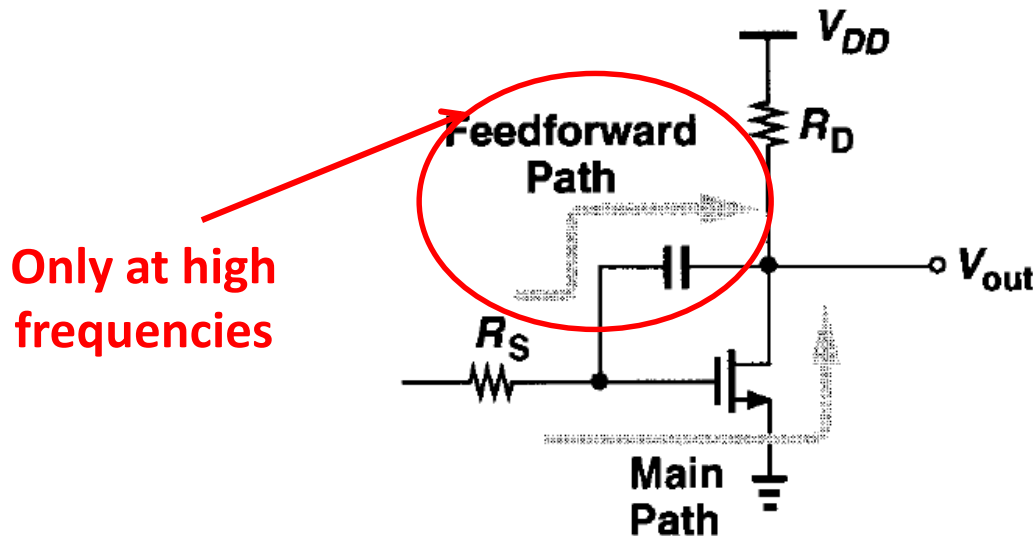
- This zero results from the direct coupling of the input and output through  $C_{GD}$  at high frequencies
- the capacitor provides a feed-forward path



It results in a slope in the frequency response that is less negative than -20dB/dec
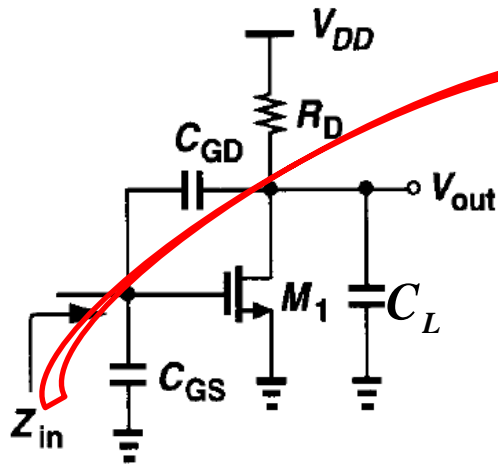
## Common Source Amplifier (contd.)

- In high speed applications, the input impedance of the common source stage is extremely important




At high enough frequency, we can derive

$$Z_{in} = \frac{1}{[C_{GS} + (1 + g_m R_D) C_{GD}] s}$$

**But at extremely high frequencies where Miller's approximation doesn't give appropriate performance, it's a must to take into account the contribution of output node**



## Common Source Amplifier (contd.)

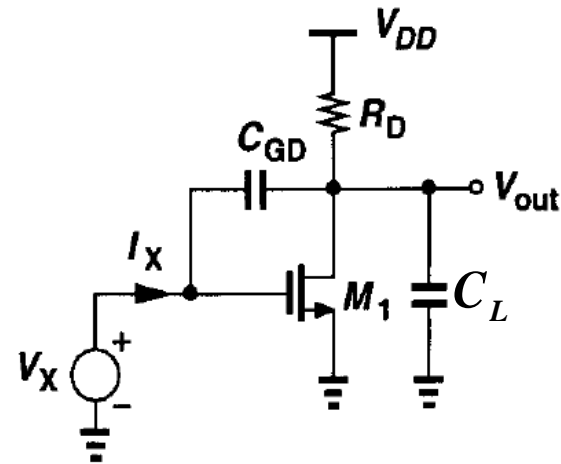

For simplification,  $C_{GS}$  has  
been ignored


Using small signal model:

$$\frac{V_X}{I_X} = \frac{1 + R_D (C_{GD} + C_{DB})s}{C_{GD}s \left[ (1 + g_m R_D + R_D C_L s) \right]}$$

Therefore:


$$Z_{in} = X_{C_{GS}} \parallel \frac{V_X}{I_X}$$

At extremely high frequency

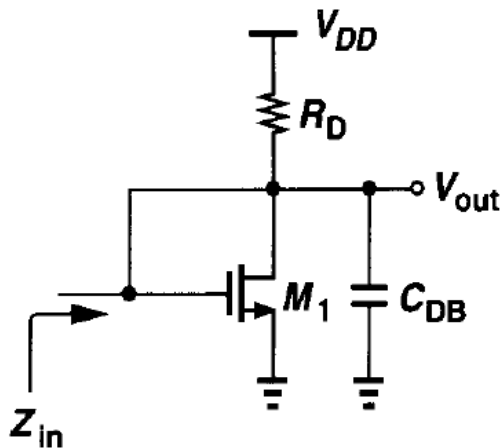

This is the case when  $C_{GD}$  is very high  
→ provides a low impedance path  
between G and D

## CS Amplifier with Source Degeneration

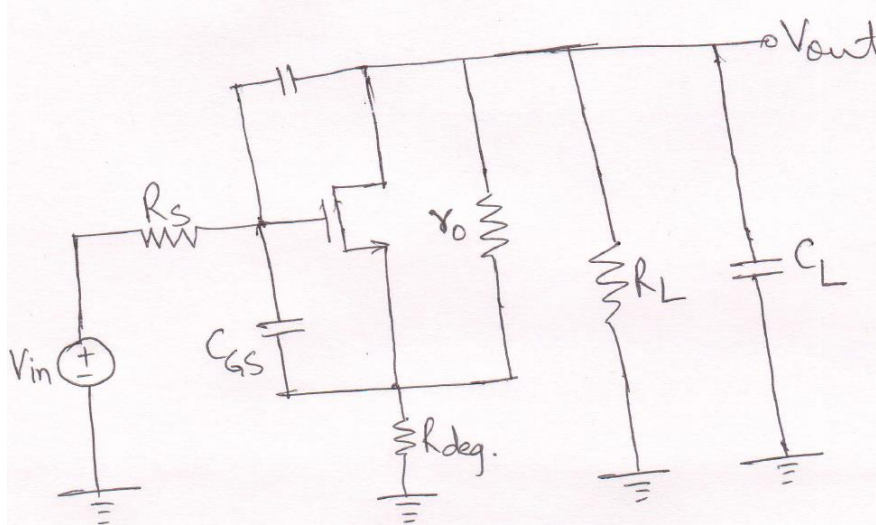

We know,

$$R_{out} = r_o \left[ 1 + (g_m + g_{mb}) R_{deg} \right]$$

$$G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_{deg}}$$

- To determine the effective time constant, use OCTC by considering one capacitor at a time.
- Consider  $C_{GD}$  first:  $R_{GD} = R_S \left( 1 + G_m R_L' \right) + R_L'$       Where,       $R_L' = R_L \parallel R_{out}$
- Then Consider  $C_L$ :  $R_{C_L} = R_L \parallel R_{out} = R_L'$

## CS Amplifier with Source Degeneration (contd.)

- **Finally Consider  $C_{GS}$ :** 
$$R_{GS} = \frac{R_S + R_{deg}}{1 + (g_m + g_{mb})R_{deg} \left( \frac{r_o}{r_o + R_L} \right)}$$
- **Now, the effective time constant:** 
$$\tau_H = C_{GS}R_{GS} + C_{GD}R_{GD} + C_L R_{C_L}$$
- **For relatively large  $R_S$  the contribution of  $C_{GD}R_{GD}$  in open circuit time constants ( $\tau_H$ ) will be largest.**

$$\Rightarrow \tau_H = C_{GD}R_{GD} \qquad \therefore f_H \cong \frac{1}{2\pi C_{GD}R_{GD}}$$

### Comment

- **If  $R_{deg}$  is increased  $\rightarrow$  the mid-band gain  $A_M$  will decrease  $\rightarrow$  this causes reduction in  $R_{GD} \rightarrow$  as a result  $f_H$  increases**
- **As  $G_m R_L' \gg 1$  and  $G_m R_S \gg 1$  the term  $R_{GD}$  can be approximated as:**



$$R_{GD} \cong G_m R_L' R_S = |A_M| R_S$$

## CS Amplifier with Source Degeneration (contd.)

$$\Rightarrow f_H = \frac{1}{2\pi C_{GD} |A_M| R_S}$$

Gain bandwidth product ( $f_H \cdot |A_M|$ ) remains constant for fixed  $R_S \rightarrow$  however other capacitances make it variable

## Common Drain

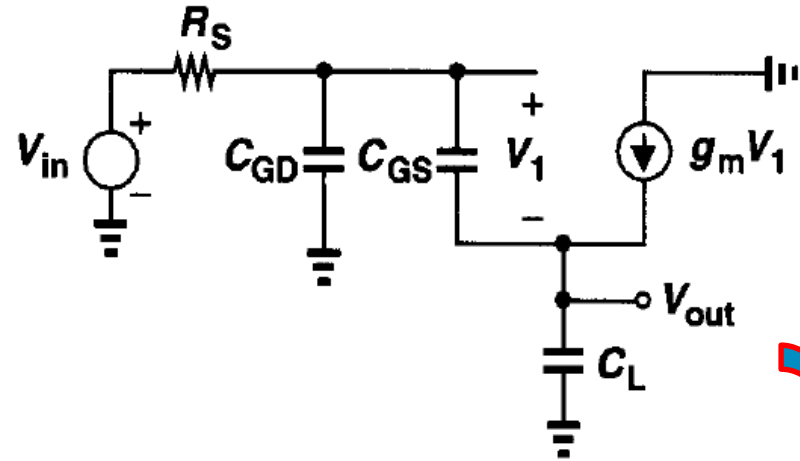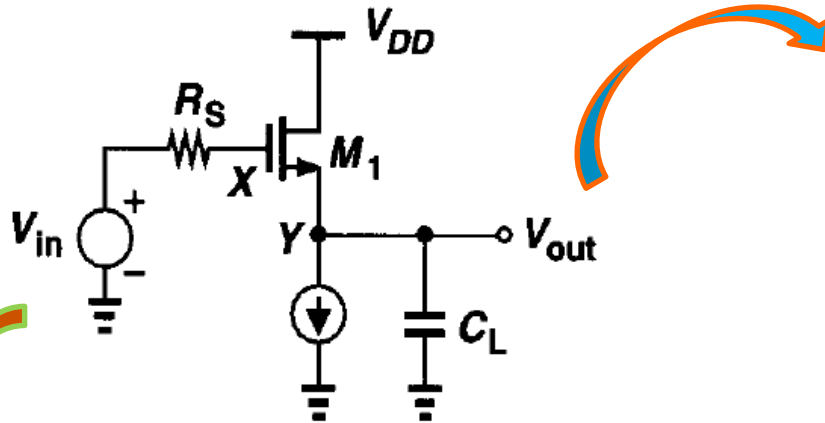

**Strong interaction between XY,  
making it difficult to associate  
each pole with each node**

$$H(s) = \frac{g_m + C_{GS}s}{R_S (C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

## Common Drain

$$H(s) = \frac{g_m + C_{GS}s}{R_S (C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

$$D = \left( \frac{s}{\omega_{p1}} + 1 \right) \left( \frac{s}{\omega_{p2}} + 1 \right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1$$



**Dominant Pole**


$$\omega_{p1} \approx \frac{g_m}{g_m R_S C_{GD} + C_L + C_{GS}} = \frac{1}{R_S C_{GD} + \frac{C_L + C_{GS}}{g_m}}$$

**If,  $R_S = 0$ : then**

$$\omega_{p1} = \frac{g_m}{C_L + C_{GS}}$$

## Common Drain Amplifier (contd.)

### Input Impedance

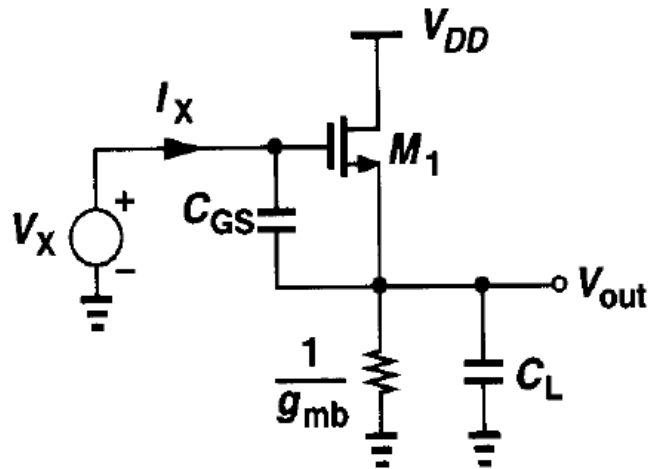

$$V_X = \frac{I_X}{C_{GS}s} + \left( I_X + \frac{g_m I_X}{C_{GS}s} \right) \left( \frac{1}{g_{mb}} \parallel \frac{1}{C_L s} \right)$$

$$Z_{in} = \frac{V_X}{I_X} = \frac{1}{C_{GS}s} + \left( 1 + \frac{g_m}{C_{GS}s} \right) \frac{1}{g_{mb} + C_L s}$$

At relatively low frequencies:

$$Z_{in} \approx \frac{V_X}{I_X} = \frac{1}{C_{GS}s} \left( 1 + \frac{g_m}{g_{mb}} \right) + \frac{1}{g_{mb}}$$

**Equivalent Input  
Capacitance :**

$$C_{in\_eq} = \frac{g_{mb} C_{GS}}{g_m + g_{mb}}$$

$$g_{mb} \gg |C_L s|$$

**Can also be obtained  
using Miller's Theorem**

## Common Drain Amplifier (contd.)

At high frequencies:

$$Z_{in} \approx \frac{1}{C_{GS}s} + \frac{1}{C_Ls} + \frac{g_m}{C_{GS}C_Ls^2}$$

$$g_{mb} \ll |C_Ls|$$

For a given,  $s=j\omega$

$$Z_{in} = \frac{1}{j\omega C_{GS}} + \frac{1}{j\omega C_L} - \frac{g_m}{\omega^2 C_{GS} C_L}$$

**Negative  
Resistance**

**must be some positive  
feedback at the input node**


**could be useful in  
oscillator design**



## Common Drain Amplifier (contd.)
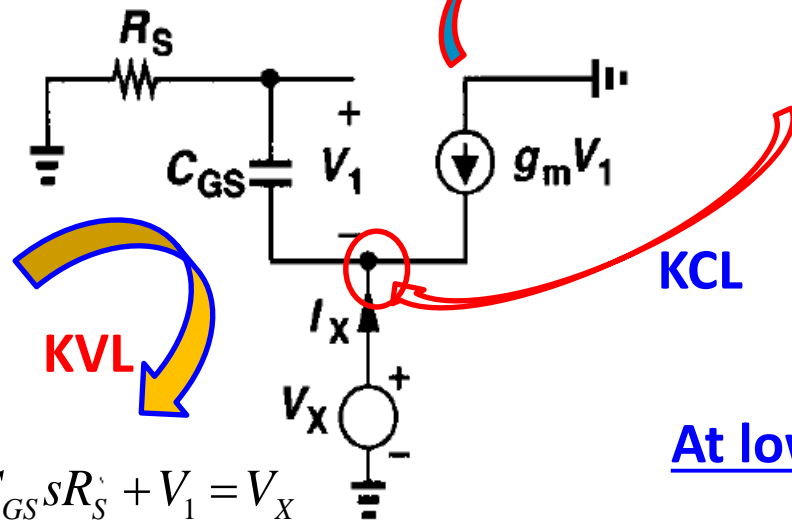
### Output Impedance

The body effect and  $C_{SB}$  yields an impedance in parallel to the output  $\rightarrow$  lets ignore this for now



$$-I_X = V_1 C_{GS} s + g_m V_1$$

$$\therefore Z_{out} = \frac{Z_X}{I_X} = \frac{R_S C_{GS} s + 1}{g_m + C_{GS} s}$$

At low frequencies:

$$Z_{out} = \frac{1}{g_m}$$

**Expected**



At very high frequencies:

$$Z_{out} = R_S$$



**Due to the fact that  $C_{GS}$  shorts the G and S**

## Common Drain Amplifier (contd.)

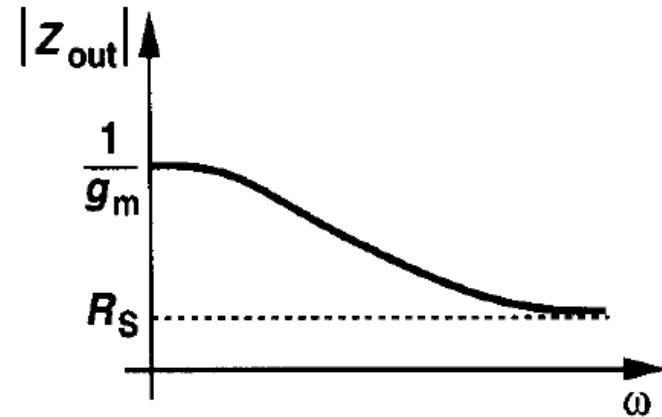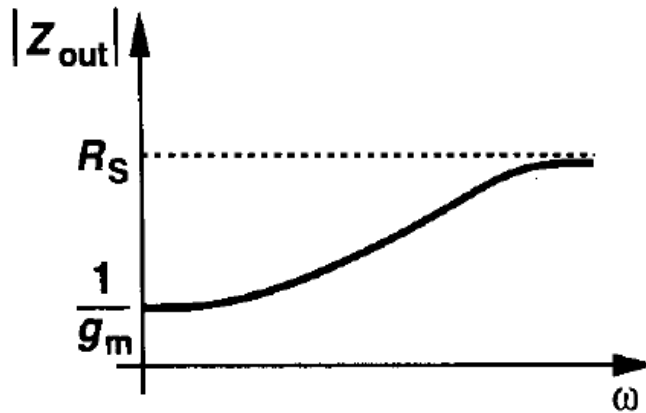


This is required considering that CD works as buffer and its purpose is to lower the output impedance i.e.,  $(1/g_m) < R_S$

The output impedance increases with frequency  $\leftrightarrow$  clear indication of the presence of inductive element

## Common Drain Amplifier (contd.)

### Output Network – first order model

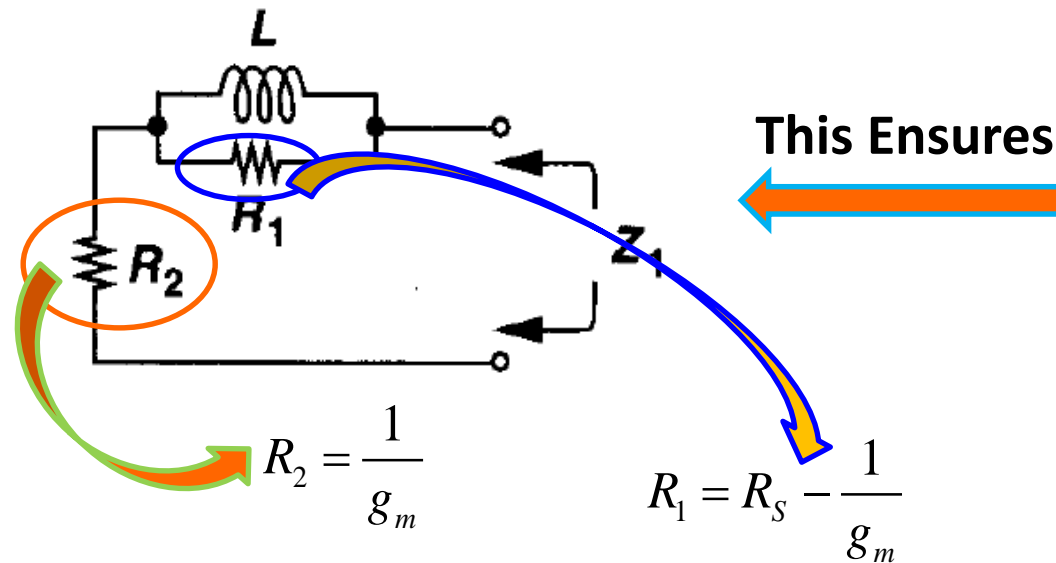

$$Z_1 = \frac{1}{g_m}$$

**At low  
frequencies**

$$Z_1 = R_S$$

**At very high  
frequencies**

- For the determination of  $L$ , equate the  $Z_1$  expression to that of  $Z_{out}$


$$L = \frac{C_{GS}}{g_m} \left( R_S - \frac{1}{g_m} \right)$$

## Common Drain Amplifier (contd.)

$$L = \frac{C_{GS}}{g_m} \left( R_S - \frac{1}{g_m} \right)$$

Its apparent that if a CD stage is driven by a  $R_S$ , then it exhibits inductive behavior at the output

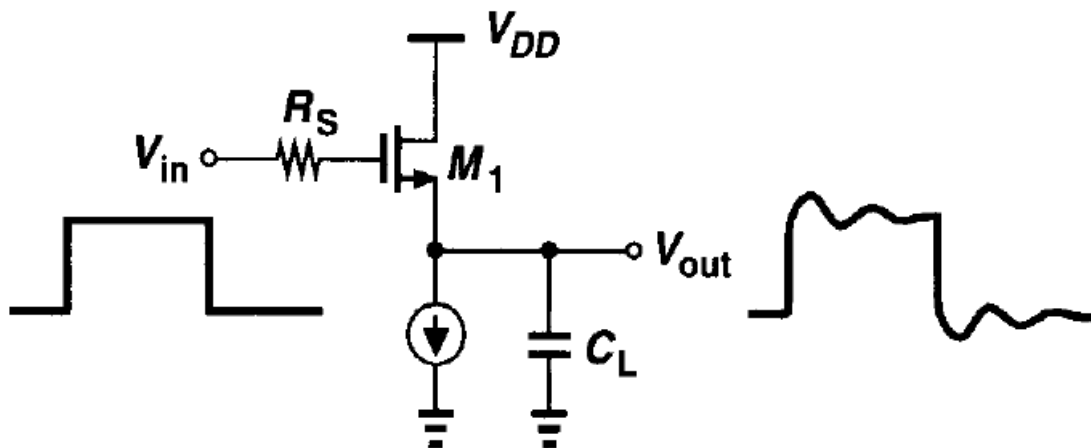It has detrimental effect on the output characteristics




For example, the ringing problem in step response

## Common Gate Amplifier

**Very important: no Miller multiplication of capacitances**



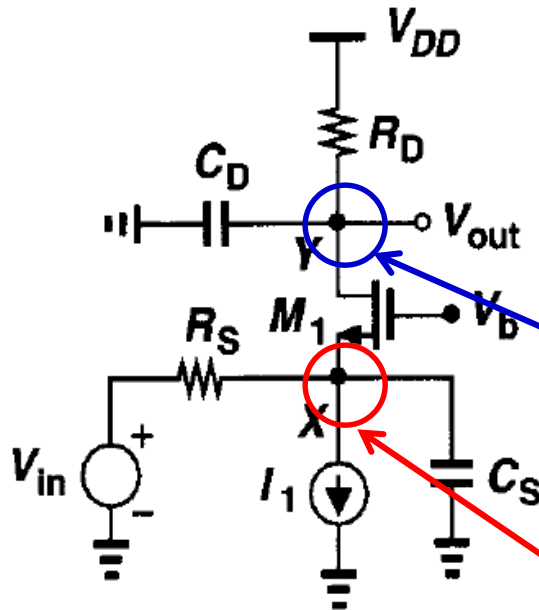**Primary factor for providing wide-band performance**



$$\omega_{out} = [C_D R_D]^{-1} \quad \leftarrow C_D = C_{GD} \parallel C_{DB}$$

$$\omega_{in} = \left[ C_S \left( R_S \parallel \frac{1}{g_m + g_{mb}} \right) \right]^{-1} \quad \leftarrow C_S = C_{GS} \parallel C_{SB}$$

Therefore the transfer function:

$$A_v = \frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \frac{1}{\left( 1 + \frac{C_S}{g_m + g_{mb} + R_S^{-1}} s \right) (1 + R_D C_D s)}$$

## Common Gate Amplifier (contd.)


- If we consider channel length modulation  $\rightarrow$  not easy to associate a pole to the input node  $\rightarrow$  direct analysis of the network is needed to determine the transfer function
- The low input impedance of may load the preceding stage
- The voltage drop across  $R_D$  is typically maximized to obtain a reasonable gain, therefore the dc level of input signal must be low
- CG stage with relatively large capacitance at the input  $\rightarrow$  possesses low output impedance  $\rightarrow$  good for cascode configuration

# Cascode Stage

## Why do we need cascode stage?

- High input impedance – good in a sense that it doesn't disturb the previous stage and doesn't get affected by the previous stage
- **High gain – important any way!**
- Relatively higher output impedance – doesn't disturb the succeeding stages
- **How about freq response?**
  - Provides a broader bandwidth of operation → due to CG stage (no Miller approximation of intrinsic capacitor) → it was the initial motivating factor for cascode stage!!!

## Cascode Stage (contd.)

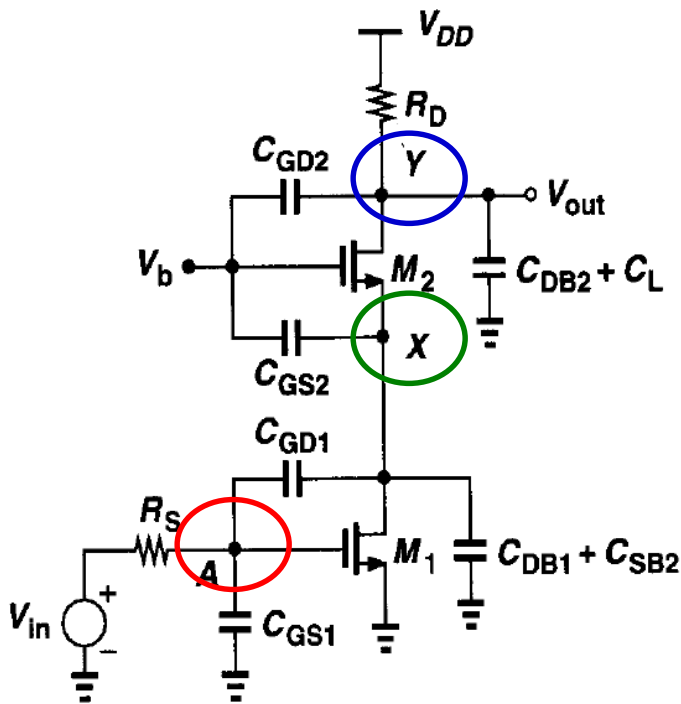

Capacitance at node A:

$C_{GS1}$  in parallel with  $(1-A_M)C_{GD1}$

Where  $A_M$  is given by: 
$$-\frac{g_{m1}}{g_{m2} + g_{mb2}}$$

With assumption that  $R_D$  is small  
and the channel length  
modulation is negligible

For equal dimensions of  $M_1$  and  $M_2$ :  $A_M$  approximately equals 1  $\rightarrow$   
therefore  $C_{GD}$  gets multiplied by a factor of roughly 2 both at node A  
as well as at node X  $\rightarrow$  much smaller multiplication factor as  
compared to a single CS stage



## Cascode Stage (contd.)

Therefore the pole associated with node A is:

$$\omega_{p,A} = \frac{1}{R_S \left[ C_{GS1} + \left( 1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]}$$

Capacitance at node X:

$$2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}$$

Therefore the pole associated with node X is:

$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}}$$

Capacitance at node Y:

$$C_{DB2} + C_L + C_{GD2}$$

Therefore the pole associated with node Y is:

$$\omega_{p,Y} = \frac{1}{R_D (C_{DB2} + C_L + C_{GD2})}$$


- Do you have any control on the choice of poles?
- **Yes** → through selection of appropriate devices
- Usually  $\omega_{p,X}$  is chosen very high → to obtain better stability

## Cascode Stage (contd.)

- Instead of  $R_D \rightarrow$  if a constant current source is used  $\rightarrow$  what happens?  $\rightarrow$  do the designer have control on the choice of poles?
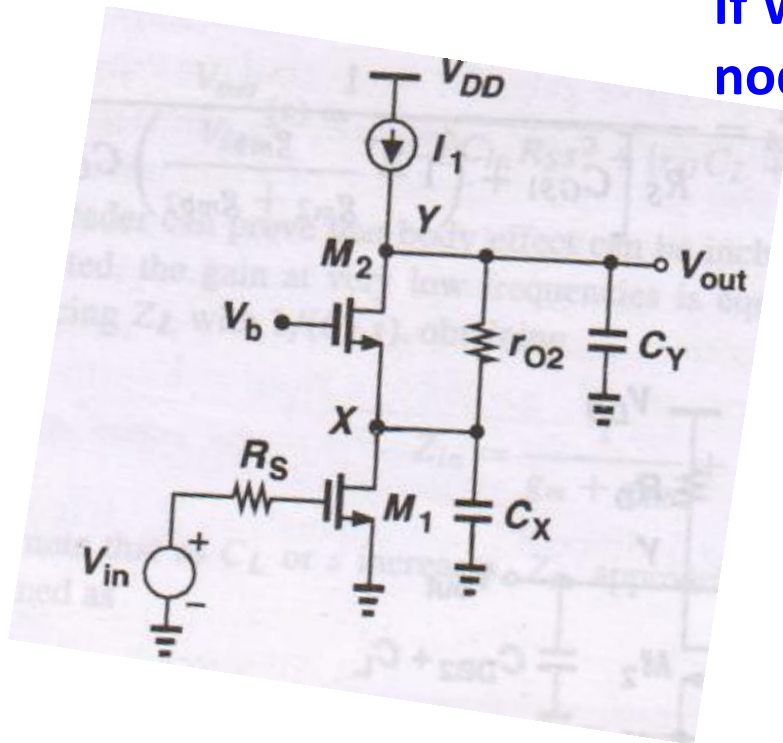
### How about output impedance?

If we ignore  $C_{GD1}$  and the capacitance at the node Y then:




$$Z_{out} = (1 + g_{m2}r_{o2})Z_X + r_{o2}$$

$$= r_{o1} \parallel (C_X s)^{-1}$$


$Z_{out}$  contains a pole at  $(r_{o1}C_X)^{-1}$

$Z_{out}$  falls above this frequency


## Differential Pair

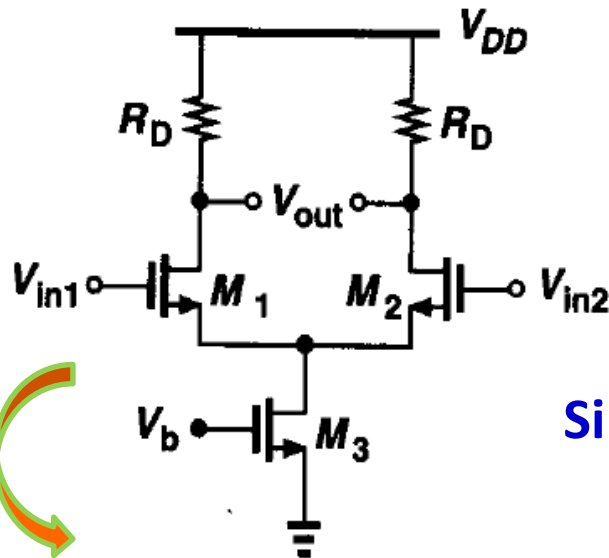

**Equivalent Half  
Circuit**

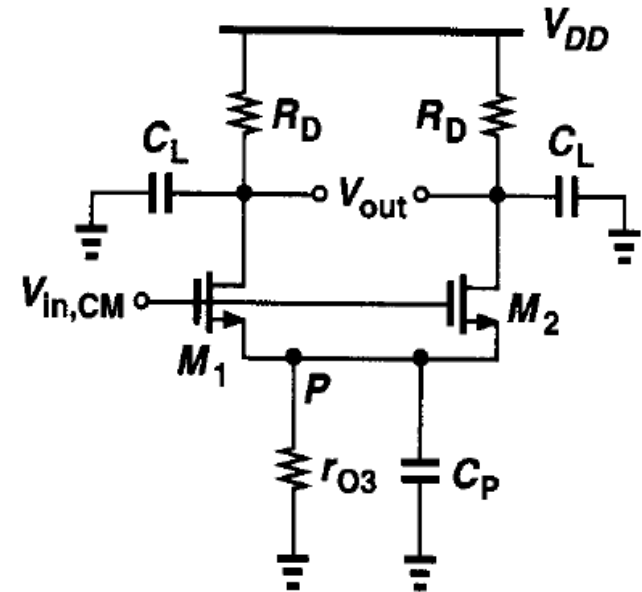

**Similar to CS  
Stage**

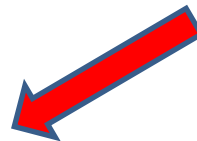

**Problem with CMRR**



To minimize voltage headroom consumed by  $M_3$  → its width is maximized → increases the capacitance contribution by  $M_3$  → higher capacitance at the source of  $M_1$  and  $M_2$  → degrades the differential gain of  $M_1$  and  $M_2$  at high frequencies → reduces the CMRR at high frequencies