



## Lecture-3

Date: 10.08.2015

- MOSFET – Second Order Effect (contd.)
- Steps for DC Analysis of MOSFET Circuits

## Second Order Effect – Body Effect


- In discrete circuit usually there is no body effect as the body is connected to the source terminal.
- In integrated circuit, there are thousands or millions of MOSFET **source terminals** and there is only one Body (B) – the silicon Substrate.
- Thus, if we were to tie (connect) **all** the MOSFET source terminals to the single body terminal, we would be connecting **all** the MOSFET source terminals to each other!
  - This would almost certainly result in a **useless** circuit!

Therefore, for integrated circuits, the MOSFET source terminals are **not** connected to the substrate body.

- Actually, the substrate is connected to the most negative power supply for NMOS circuit for achieving the desired functionality from the device.
- In such a scenario, what happens if the bulk voltage drops below the source voltage?
 
## Second Order Effect – Body Effect

- Now the voltage  $V_{SB}$  (voltage source-to-body) is **not** necessarily equal to zero (i.e.,  $V_{SB} \neq 0$ ). Thus, we are back to a **four-terminal** MOSFET device.
- There are **many** ramifications of this body effect; perhaps the most significant is with regard to the **threshold voltage**  $V_T$ .
- To understand, let us assume  $V_S = V_D = V_B = 0$ , and  $V_G$  is somewhat less than  $V_T$ . A depletion region forms but no inversion layer exists.
- As  $V_B$  becomes negative, more holes get attracted to the substrate which leaves a larger negative charge behind and as a result the depletion region becomes wider.



Wider depletion region

## Second Order Effect – Body Effect

- The wider depletion region leads to increase in threshold voltage given by:

$$V_T = V_{T0} + \gamma \left( \sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|} \right)$$


where  $\gamma$  and  $\Phi_F$  are MOSFET **device parameters** and are essentially process dependent.

- Note the value  $V_{T0}$  is the value of the threshold voltage **when**  $V_{SB} = 0$   $\leftrightarrow$  the value  $V_{T0}$  is simply the value of the device parameter  $V_T$  that we have been calling the threshold voltage up till now, i.e., without body effect.
- It is thus evident that the term  $\gamma \left( \sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|} \right)$  simply expresses an **extra** value added to the “ideal” threshold voltage  $V_{T0}$  when  $V_{SB} \neq 0$ .

### Questions

- Can a circuit designer control threshold voltage?**
- Body effect is desirable or undesirable?**

## Second Order Effect – Body Effect

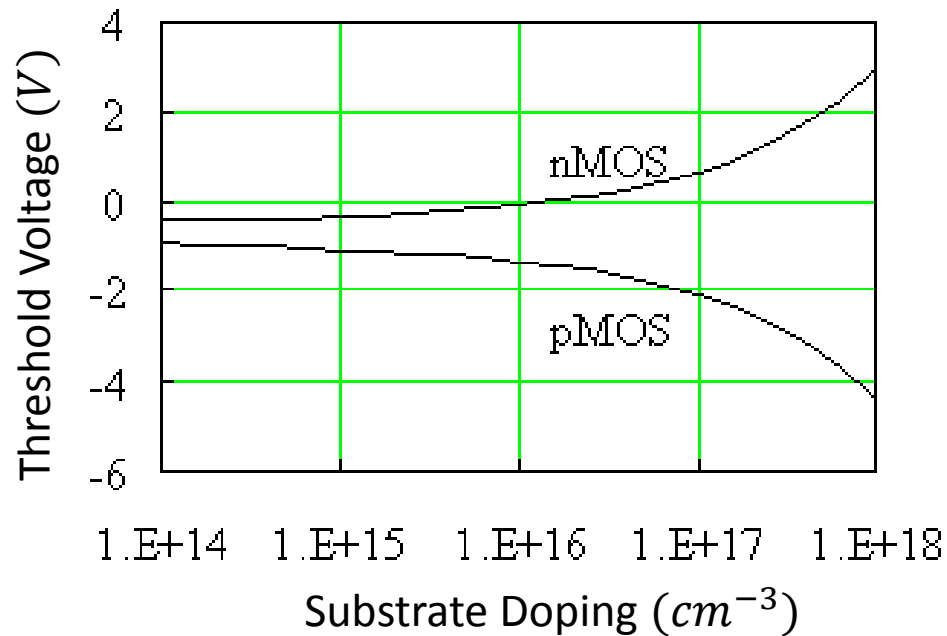

## Second Order Effect – Body Effect (contd.)

- Effect of body effect on Transconductance ( $g_m$ ).
- Let us check the sensitivity of  $I_{DS}$  to  $V_{SB}$

$g_m$

Simplification Yields:

$$g_{mb} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{T0}) \left( -\frac{\partial V_T}{\partial V_{BS}} \right)$$

$$\left( \frac{\partial V_T}{\partial V_{BS}} \right) = - \left( \frac{\partial V_T}{\partial V_{SB}} \right) = -\frac{\gamma}{2} (2\Phi_F + V_{SB})^{-\frac{1}{2}}$$

$$\Rightarrow g_{mb} = g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} = \eta g_m$$

$$\eta = g_{mb}/g_m$$

$\eta = 1/3$  to  $1/4$ , bias dependent

Thus, body effect has potential to alter (reduce) transconductance and therefore can impact device performance adversely



## Second Order Effect – Body Effect

For many cases, we find that this Body Effect is relatively insignificant, so we will (unless **otherwise** stated) **ignore the Body Effect**.

However, do **not** conclude that the Body Effect is **always** insignificant—it can in some cases have a tremendous impact on MOSFET circuit performance!

## Second Order Effect – Subthreshold Conduction

- For  $V_{GS} \approx V_T$ , a “weak” inversion layer still exists and some current flows from D to S.
- Even for  $V_{GS} < V_T$ ,  $I_D$  is finite  $\rightarrow$  subthreshold conduction
- For  $V_{DS}$  greater than roughly 200 mV:

$$I_D = I_0 \exp \frac{V_{GS}}{\zeta V_{TM}}$$

$$V_{TM} = kT/q$$

**Nonideality Factor**

- When  $V_{GS}$  is brought to zero, there will be some drain current in the channel. This is clearly unwanted situation as this small current will cause significant power consumption in large circuits



## Second Order Effect – Voltage Limitations

- Various breakdown occurs if their terminal voltage differences exceed certain limits
- At high  $V_{GS}$ , the gate oxide breaks down irreversibly
- In short-channel devices, an excessively large  $V_{DS}$  can widen the depletion region around the drain so much that it touches that around the source, creating a very large drain current → punch through

### Question

- Can channel length modulation affect NMOS/PMOS performance in linear/triode operation mode?

## DC Analysis of MOSFET Circuits

- To analyze MOSFET circuit with D.C. sources, we **must** follow these **five** steps:
  1. **ASSUME** an operating mode
  2. **ENFORCE** the equality conditions of that mode.
  3. **ANALYZE** the circuit with the enforced conditions.
  4. **CHECK** the inequality conditions of the mode for consistency with original assumption. If consistent, the analysis is complete; if inconsistent, go to step 5.
  5. **MODIFY** your original assumption and repeat all steps

## 1. ASSUME

Here we have **three** choices—cutoff, triode, or saturation. You can make an “**educated guess**” here, but remember, until you CHECK, it’s just a guess!

## 2. ENFORCE

For all three operating regions, we must ENFORCE just **one equality**.

- **Cutoff:** Since **no** channel is induced, we **ENFORCE**:  $I_D = 0$
- **Triode:** Since the conducting channel **is** induced but **not** in pinch-off, we **ENFORCE**: 
$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) \left[ 2(V_{GS} - V_T)V_{DS} - V_{DS}^2 \right]$$
- **Saturation:** Since the conducting channel **is** induced but **is** in pinch-off, we **ENFORCE**: 
$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_T)^2$$

## 3. ANALYZE

The task in D.C. analysis of a MOSFET circuit is to find **one current** and **two voltages**!

- a) Since the gate current  $I_G$  is zero ( $I_G = 0$ ) for all MOSFETS in all modes, we need **only** to find the **drain current**  $I_D$  - this current value must be **positive** (or zero).
- b) We also need to find **two** of the three **voltages** associated with the MOSFET. Typically, these two voltages are  $V_{GS}$  and  $V_{DS}$ , but given any two voltages, we can find the third using KVL:

$$V_{DS} = V_{DG} + V_{GS}$$

### Some hints for MOSFET DC analysis:

1. Gate current  $I_G = 0$  **always** !!!
2. Equations sometimes have **two** solutions! Choose solution that is **consistent** with the original ASSUMPTION.

## 4. CHECK

You do not know if your D.C. analysis is correct unless you CHECK to see if it is consistent with your original assumption!

**Q:** What exactly do we CHECK?

**A:** We ENFORCED the mode **equalities**, we CHECK the mode **inequalities**.

We must CHECK **two** separate inequalities after analyzing a MOSFET circuit. Essentially, we check if we have/have not induced a conducting channel, and then we check if we have/have not pinched-off the channel (if it is conducting).

### Cutoff

We must only CHECK to see if the MOSFET has a **conducting channel**. If **not**, the MOSFET is indeed in **cutoff**. We therefore CHECK to see if:

$$V_{GS} < V_T \quad (\text{NMOS})$$

$$V_{GS} > V_T \quad (\text{PMOS})$$

## Triode

- Here we must first CHECK to see **if** a channel has been induced:

$$V_{GS} > V_T \quad (\text{NMOS}) \qquad V_{GS} < V_T \quad (\text{PMOS})$$

- Likewise, we must CHECK to see if the channel has reached **pinch off**. If **not**, the MOSFET is indeed in the **triode** region. We therefore CHECK to see if:

$$V_{DS} < V_{GS} - V_T \quad (\text{NMOS}) \qquad V_{DS} > V_{GS} - V_T \quad (\text{PMOS})$$

## Saturation

- Here we must first CHECK to see **if** a channel has been induced:

$$V_{GS} > V_T \quad (\text{NMOS}) \qquad V_{GS} < V_T \quad (\text{PMOS})$$

- Likewise, we must CHECK to see if the channel has reached **pinch off**. If it **has**, the MOSFET is indeed in the **saturation** region and we need to CHECK:

$$V_{DS} > V_{GS} - V_T \quad (\text{NMOS}) \qquad V_{DS} < V_{GS} - V_T \quad (\text{PMOS})$$




- If the results of our analysis are consistent with **each** of these inequalities, then we have made the **correct** assumption! The **numeric** results of our analysis are then likewise **correct**. We can **stop** working!
- However, if **even one** of the results of our analysis is **inconsistent** with our ASSUMPTION, then we have made the **wrong** assumption → Time to move to step 5.

## 5. MODIFY

If **one or more** of the circuit MOSFETs are **not** in their ASSUMED mode, we must change our assumptions and start **completely** over!

In general, **all** of the results of our previous analysis are incorrect, and thus must be **completely** scraped!

## Example – 1

 

$$\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) = K = 0.4 \text{ mA} / \text{V}^2$$

$$V_T = 2.0 \text{ V}$$

**ASSUME:** the NMOS device is in saturation.

- Thus, we must ENFORCE the condition that:


$$I_D = K (V_{GS} - V_T)^2$$

- Now we must **ANALYZE** the circuit.

**Q:** What now? How do we proceed with this analysis?



## Example – 1 (contd.)

 

**A:** It's certainly not clear. Let's write the circuit equations and see what happens.

- **From the Gate-Source loop KVL:**

$$0 - V_{GS} - 1 \times 10^3(I_D) = -5.0$$

- **Therefore, rearranging:**

$$I_D = (5.0 - V_{GS})/10^3$$

- **And from the Drain-Source loop KVL:**

$$5 - 1 \times 10^3(I_D) - V_{DS} - 1 \times 10^3(I_D) = -5.0$$

- **Therefore, rearranging:**

$$V_{DS} = 10.0 - 2 \times 10^3(I_D)$$

## Example – 1 (contd.)

$$I_D = (5.0 - V_{GS})/10^3 = K(V_{GS} - V_T)^2$$

$$\longrightarrow 0.4 \text{ mA/V}^2 [V_{GS} - 2]^2 = \frac{5 - V_{GS}}{10^3}$$

$$V_{GS} = 3.76 \text{ V}$$

$$V_{GS} = -2.26 \text{ V}$$

- We **assumed** saturation. If the NMOS is in saturation, we know that:

$$V_{GS} > V_T = 2.0 \text{ V}$$

$$\therefore V_{GS} = 3.76 \text{ V}$$

- Inserting this voltage into the Gate-Source KVL equation, we find that the drain current is:

$$I_D = (5.0 - 3.76)/10^3 \longrightarrow \therefore I_D = 1.24 \text{ mA}$$

- And using the Drain-Source KVL, we find the remaining voltage:

$$V_{DS} = 10.0 - 2 \times 10^3 \times 1.24 \times 10^{-3} \longrightarrow \therefore V_{DS} = 7.52 \text{ V}$$

## Example – 1 (contd.)


- Even though we have answers (one current and two voltages), we still are not finished, as we now must **CHECK** our solution to see if it is consistent with the saturation mode inequalities.

$$3.76 = V_{GS} > V_T = 2.0$$

$$7.52 = V_{DS} > V_{GS} - V_T = 1.76$$

Both answers are consistent! Our solutions are correct!

## Example – 2

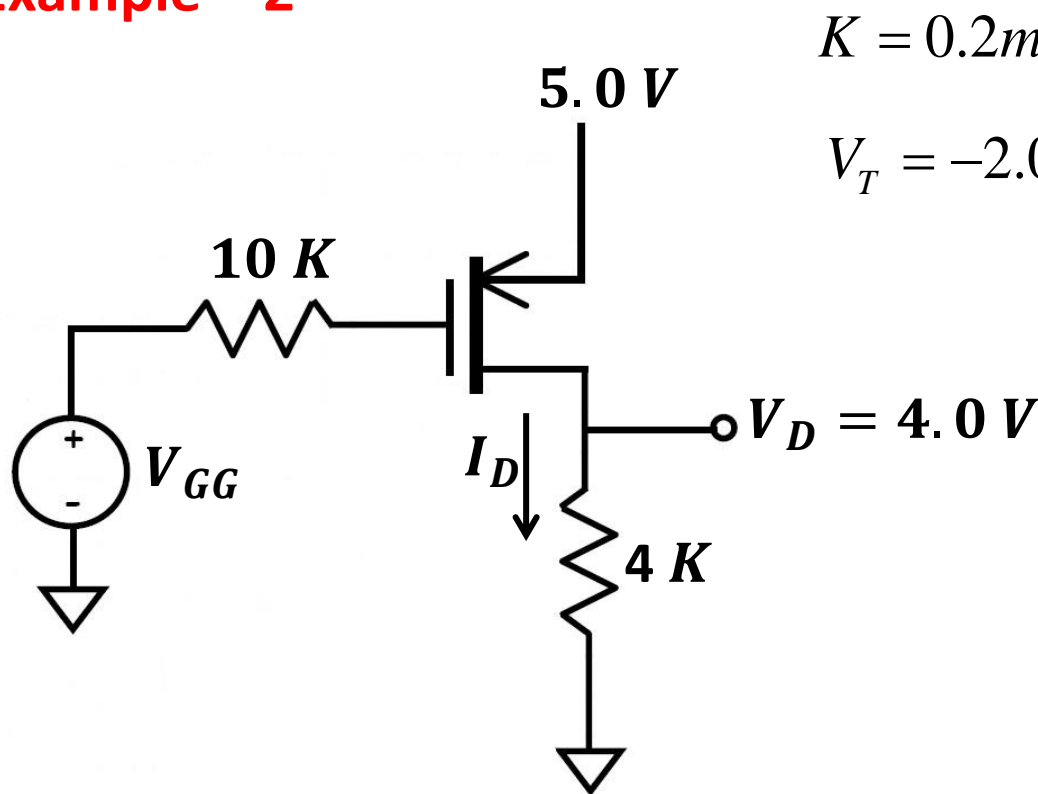

$$K = 0.2\text{ mA/V}^2$$

$$V_T = -2.0\text{ V}$$

Find  $V_{GG}$

- let's ASSUME that the PMOS is in **saturation** mode.

- Therefore, we ENFORCE the **saturation** drain current equation:

$$I_D = K (V_{GS} - V_T)^2$$

## Example – 2 (contd.)


**Q:** Yikes! Where do we start ?

**A:** The best way to start is by “picking the low-hanging fruit”. In other words, determine the **obvious** and easy values. **Don't** ask, “What is  $V_{GG}$ ?”, but **instead** ask, “What **do** I know?” !

$$I_G = 0.0 \text{ mA} \quad V_S = 5.0 \text{ V}$$

$$I_D = \frac{V_D - 0.0}{4 \times 10^3} = \frac{4}{4 \times 10^3} = 1 \text{ mA}$$
 
$$V_{DS} = V_D - V_S = 4 - 5 = -1 \text{ V}$$



$$V_G = V_{GG} - 10 \times 10^3 \times I_G = V_{GG}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5 \text{ V}$$

## Example – 2 (contd.)

- We can now relate these values using PMOS **drain current equation**.

$$I_D = K (V_{GS} - V_T)^2 \quad \longrightarrow \quad 1 \times 10^{-3} = 0.2 \times 10^{-3} \times (V_{GS} - (-2.0))^2$$

$$V_{GS} = 0.24 \text{ V} \quad V_{GS} = -4.23 \text{ V}$$

- For this example, we have ASSUMED that the PMOS device is in **saturation**. Therefore, the gate-to-source voltage must be **less** (remember, it's a **PMOS** device!) than the **threshold voltage**:

$$V_{GS} < V_T$$

$$\therefore V_{GS} = -4.23 \text{ V}$$

**Q:** Does this mean our saturation ASSUMPTION is **correct**?

**A: NO!** It merely means that our saturation ASSUMPTION **might** be correct! We need to CHECK the other inequalities to know for **sure**.


## Example – 2 (contd.)

- Now, returning to our circuit **analysis**, we can quickly determine the **unknown** value of  $V_{GG}$ . Recall that we **earlier** determined that:

$$V_{GS} = V_G - V_S = V_{GG} - 5 \text{ V} \quad \rightarrow \quad -4.23 = V_{GG} - 5 \text{ V} \quad \rightarrow \quad \therefore V_{GG} = 0.77 \text{ V}$$

This solution ( $V_{GG} = 0.77\text{V}$ ) is of course true **only if** our original ASSUMPTION was correct. Thus, we must **CHECK** to see if our **inequalities** are valid.

- We of course already know that the **first** inequality is true—a p-type channel is induced:

$$V_{GS} = -4.23\text{V} < V_T = -2.0\text{V}$$


- However:

$$V_{DS} = -1.0\text{V} \not< V_{GS} - V_T = -2.23\text{V}$$


shows us that our ASSUMPTION was **incorrect!**

## Example – 2 (contd.)

→ Time to make a **new** ASSUMPTION and **start over!**

- So, let's **now** ASSUME the PMOS device is in **triode** region. Therefore ENFORCE the drain current equation:

$$I_D = K \left[ 2(V_{GS} - V_T)V_{DS} - V_{DS}^2 \right]$$

- Note that most of our **original** analysis was **independent** of our PMOS mode ASSUMPTION. Thus, we **again** conclude that:

$$I_G = 0.0 \text{ mA} \quad V_S = 5.0 \text{ V} \quad I_D = \frac{V_D - 0.0}{4 \times 10^3} = \frac{4}{4 \times 10^3} = 1 \text{ mA}$$

$$I_D = \frac{V_D - 0.0}{4 \times 10^3} = \frac{4}{4 \times 10^3} = 1 \text{ mA} \quad V_G = V_{GG} - 10 \times 10^3 \times I_G = V_{GG}$$

$$V_{DS} = V_D - V_S = 4 - 5 = -1 \text{ V} \quad V_{GS} = V_G - V_S = V_{GG} - 5 \text{ V}$$



## Example – 2 (contd.)

- Now, inserting these values in the **triode drain current equation**:

$$1 \times 10^{-3} = 0.2 \times 10^{-3} \times \left[ 2(V_{GS} - (-2.0))(-1.0) - (-1.0)^2 \right]$$

- Solving for  $V_{GS}$  we find:  $V_{GS} = -5.0V$

- Therefore:  $V_{GG} = V_{GS} + 5.0 = -5.0 + 5.0 = 0$

The voltage source  $V_{GG}$  is equal to **zero**—provided that our triode ASSUMPTION was **correct**.

- First, we CHECK to see if a channel has indeed been **induced**.

$$V_{GS} = -5.0V < V_T = -2.0V$$



## Example – 2 (contd.)

- Next, we CHECK to make sure that our channel is **not** in pinch off.

$$V_{DS} = -1.0V > V_{GS} - V_T = -3.0V \quad \checkmark$$

Our **triode** ASSUMPTION is **correct!** Thus, the voltage source  $V_{GG} = 0.0 V$ .

## Example – 3

- Consider the **PMOS** circuit below, find the value of unknown of resistor R.

