




## Lecture – 4

Date: 13.08.2015

- The MOSFET as a Switch and Amplifier
- MOSFET Small Signal Operation, Models, Analysis

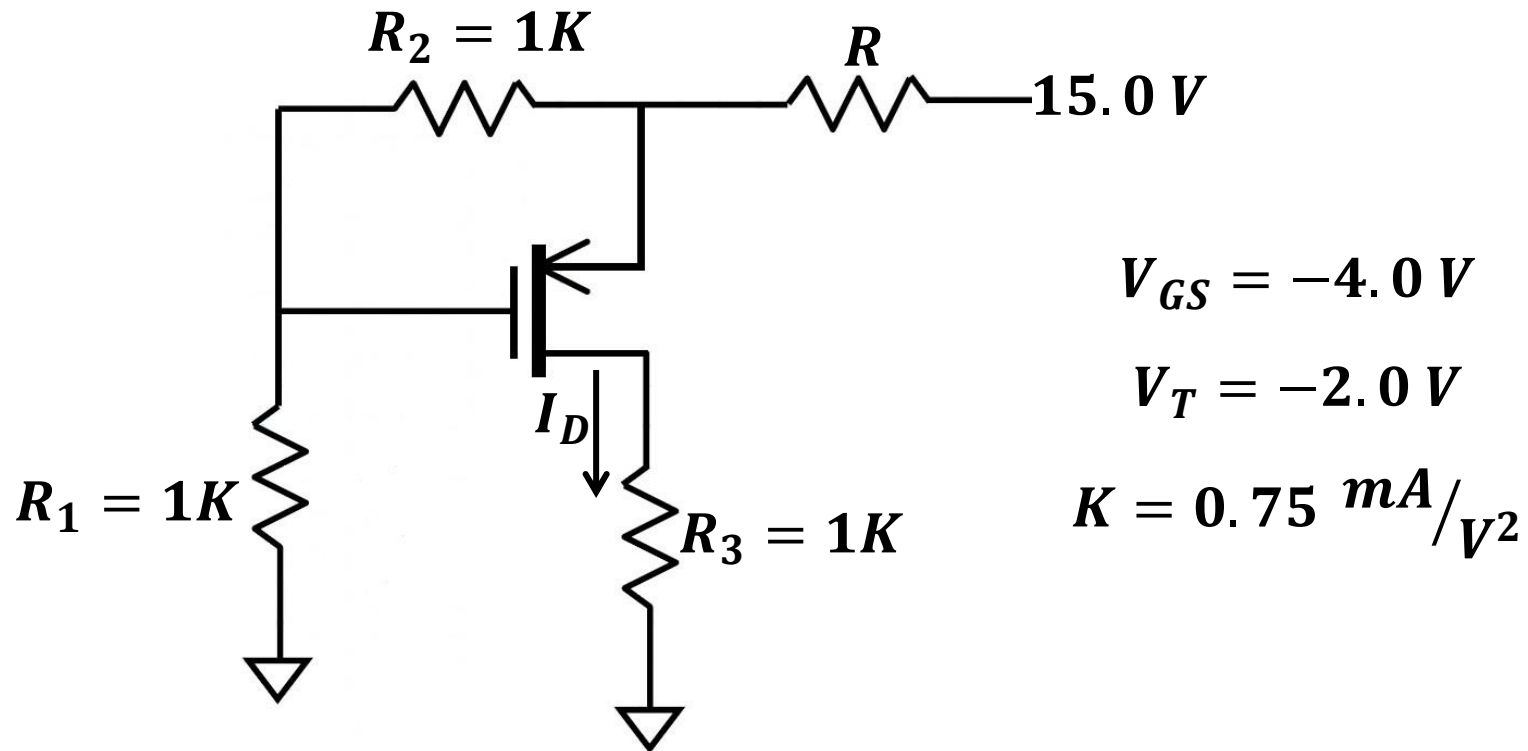
## Example – 3

- Consider the **PMOS** circuit below, find the value of unknown of resistor R.


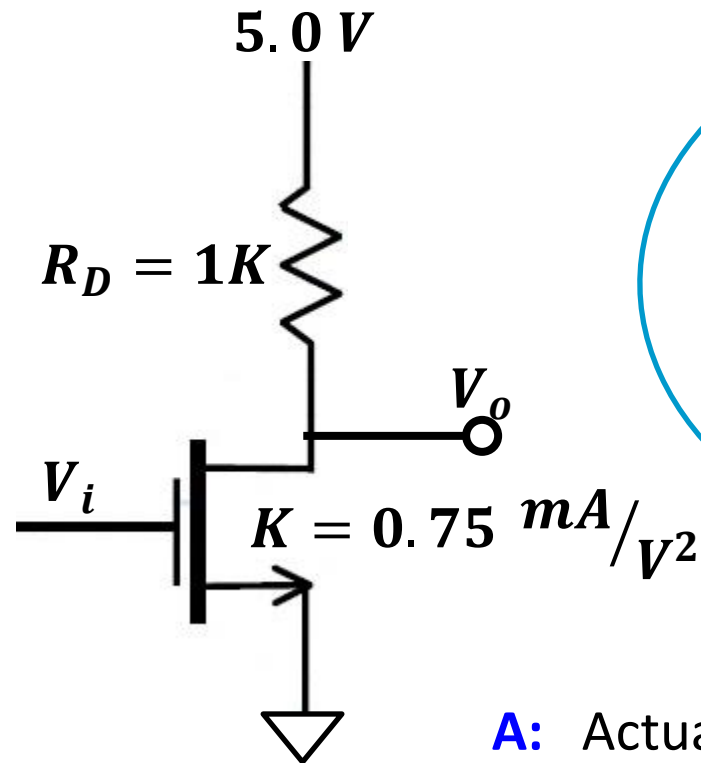
## The MOSFET as a Switch and an Amplifier

- Consider this **simple** MOSFET circuit:



**Q:** Oh, goody—you're going to **waste** my time with another of these **pointless** academic problems. Why can't you discuss a circuit that actually **does** something?



**A:** Actually, this circuit is a fundamental electronic device! To see what this circuit does, we need to determine its **transfer function**  $V_o = f(V_i)$ .

## The MOSFET as a Switch and an Amplifier (contd.)

**Q: Transfer function!** How can we determine the transfer function of a MOSFET circuit!?



**A: Same** as with junction diodes—we determine the output  $V_o$  for each device mode, and then determine **when** (i.e., for what values of  $V_i$ ) the device is in that mode!


- First, note that **regardless** of the MOSFET mode:

$$V_{GS} = V_i - 0.0 = V_i$$

$$V_{DS} = V_o - 0.0 = V_o$$

- From KVL, we can likewise conclude that:

$$V_{DS} = V_o = 5.0 - I_D R_D$$

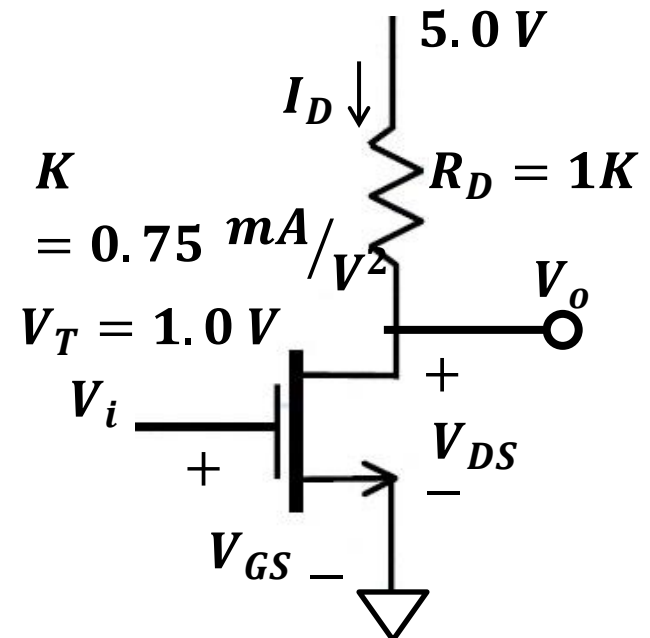

## The MOSFET as a Switch and an Amplifier (contd.)

- Now let's ASSUME that the MOSFET is in **cutoff**, thus ENFORCING  $I_D = 0$ .

$$V_{DS} = V_o = 5.0 - I_D R_D \quad \Rightarrow \quad V_o = 5.0 - 0 \times (1 \times 10^3)$$

$$\Rightarrow \therefore V_o = 5.0 \text{ V}$$

- Now, we know that MOSFET is in cutoff **when**:  $V_{GS} = V_i < V_T = 1.0 \text{ V}$

- Thus, we conclude that:

$$V_o = 5.0 \text{ V} \quad \underline{\text{when}} \quad V_i < 1.0 \text{ V}$$

## The MOSFET as a Switch and an Amplifier (contd.)

- Now, let's ASSUME that the MOSFET is in **saturation**, thus ENFORCE:

$$I_D = K(V_{GS} - V_T)^2 \quad \longrightarrow \quad I_D = K(V_i - 1.0)^2$$

- And thus the output voltage is:

$$V_o = 5.0 - I_D R_D = 5.0 - 0.75 \times 10^{-3} \times (V_i - 1.0)^2 \times 1 \times 10^3$$

$$\therefore V_o = 5.0 - 0.75 \times (V_i - 1.0)^2$$

- We know that MOSFET is in saturation **when**:

$$V_{GS} = V_i > V_T = 1.0 \text{ V} \quad \underline{\text{and}} \quad V_{DS} = V_o > V_{GS} - V_T = V_i - 1.0$$

- The second inequality means:

$$V_o > V_i - 1.0 \quad \longrightarrow \quad 5.0 - 0.75 \times (V_i - 1.0)^2 > V_i - 1.0$$

## The MOSFET as a Switch and an Amplifier (contd.)

$$0 > 0.75 \times (V_i - 1.0)^2 + (V_i - 1.0) - 5.0$$

- Solving this quadratic, we find that the **only** consistent solution is:

$$V_i - 1.0 < 2.0 \quad \longrightarrow \quad V_i < 3.0$$

- Thus we conclude that the MOSFET is in saturation:

$$V_o = 5.0 - 0.75 \times (V_i - 1.0)^2 \quad \text{when} \quad 1.0 < V_i < 3.0 \text{ V}$$

- Finally, let's ASSUME that the MOSFET is in **triode** mode, thus we ENFORCE:

$$I_D = K[2(V_{GS} - V_T)V_{DS} - (V_{DS})^2]$$

- And thus the output voltage is:

$$V_o = 5.0 - I_D R_D = 5.0 - 0.75 \times [2(V_i - 1.0)V_o - (V_o)^2]$$

## The MOSFET as a Switch and an Amplifier (contd.)

- Rearranging the equation, we get the quadratic form:

$$0.75(V_o)^2 - (1.5V_i - 0.5)V_o + 5.0 = 0$$

- The solutions of which are:

$$V_o = \frac{(1.5V_i - 0.5) \pm \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$

- Note because of the  $\pm$ , there are **two** possible solutions. However, to be in triode region, the MOSFET must not be in pinchoff, i.e.:

$$V_{DS} = V_o < V_{GS} - V_T = V_i - 1.0$$

- This condition is satisfied with the **smaller** of the two solutions (i.e., the solution with the minus sign!):

$$V_o = \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$



## The MOSFET as a Switch and an Amplifier (contd.)

$$V_o = \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$

This expression provides us with the output voltage **if** the MOSFET is in triode mode. The question remaining is thus **when** (i.e., for what values of  $V_i$ ) is the MOSFET in triode mode?

We could do a lot more math to find this answer, but this answer is actually quite **obvious!**

- Recall that we have already determined that:
  - The MOSFET is in cutoff **when**  $V_i < 1.0V$ .
  - The MOSFET is in saturation **when**  $1.0V < V_i < 3.0V$ .

## The MOSFET as a Switch and an Amplifier (contd.)

- Since there are only **three** modes of a MOSFET device, and since the transfer **function** must—well—be a **function**, we can conclude (correctly) that the MOSFET will be in triode region when  $V_i$  is the value of the **only region that is left**:  $V_i > 3.0 V$ .
- Thus we can conclude that:

$$V_o = \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$


when  $V_i > 3.0 V$

## The MOSFET as a Switch and an Amplifier (contd.)


- We now have determined the complete, continuous **transfer function** of this circuit!

$$V_o = \begin{cases} 5.0 \text{ V} & \text{when } V_i < 1.0 \text{ V} \\ 5.0 - 0.75 \times (V_i - 1.0)^2 & \text{when } 1.0 < V_i < 3.0 \text{ V} \\ \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5} & \text{when } V_i > 3.0 \text{ V} \end{cases}$$

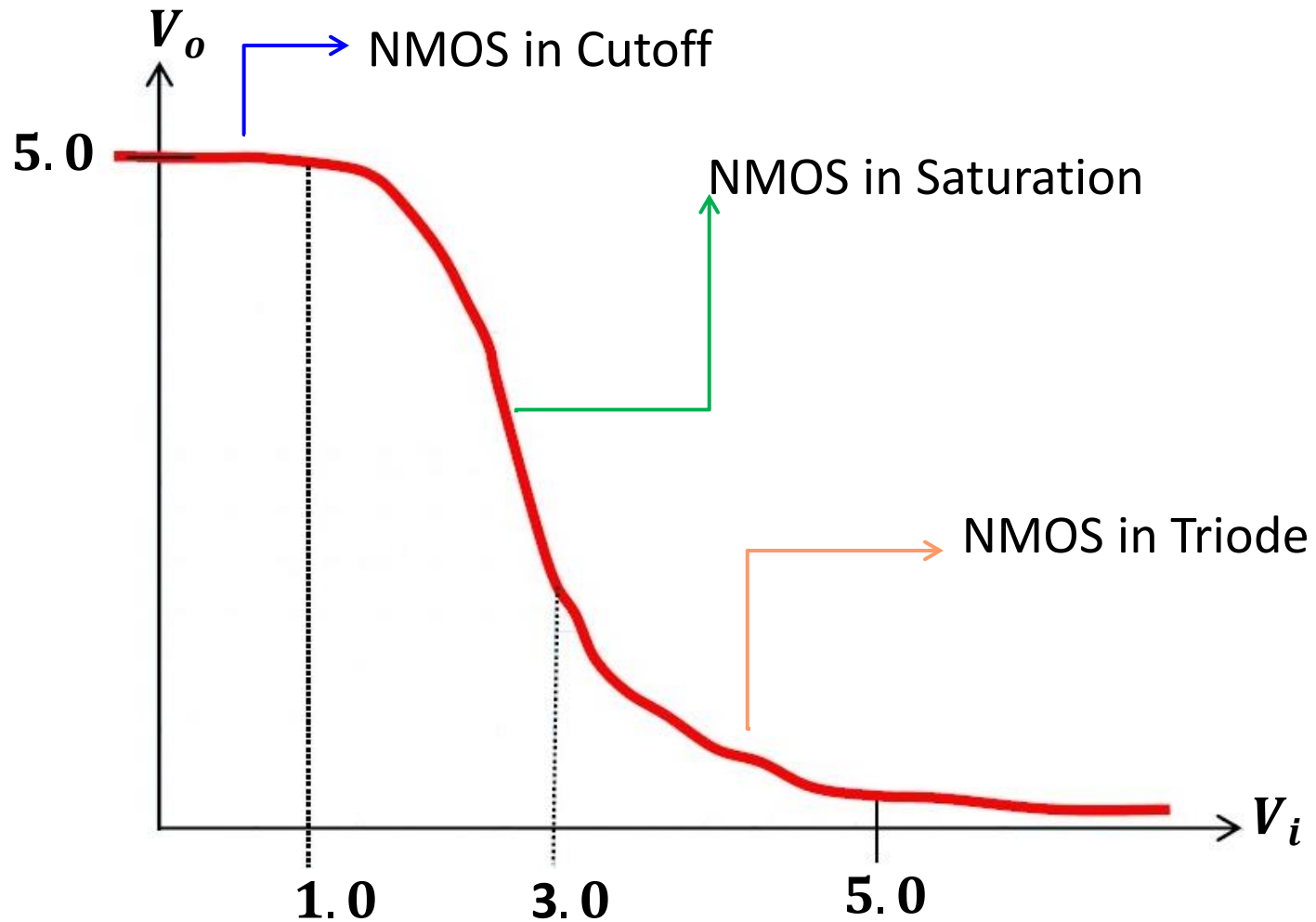
## The MOSFET as a Switch and an Amplifier (contd.)


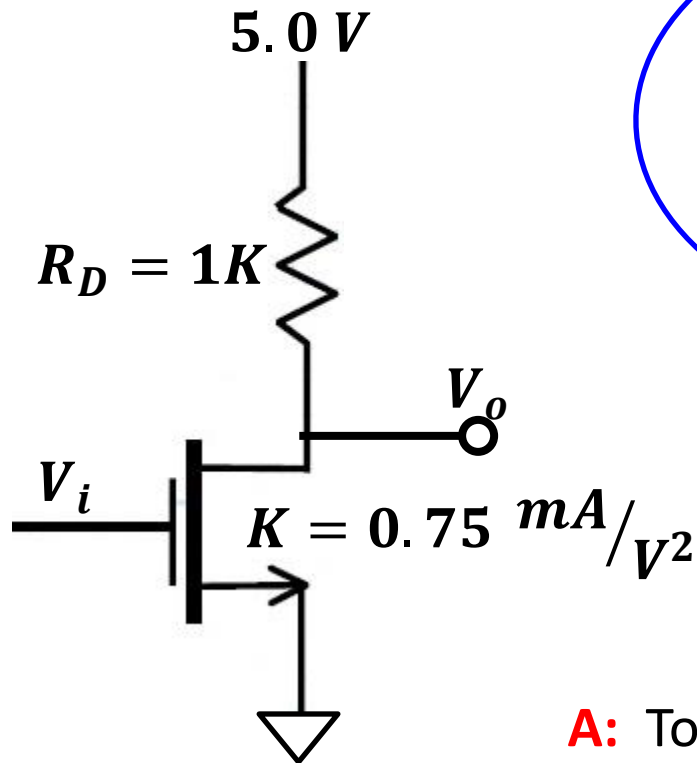
## The MOSFET as a Switch and an Amplifier (contd.)



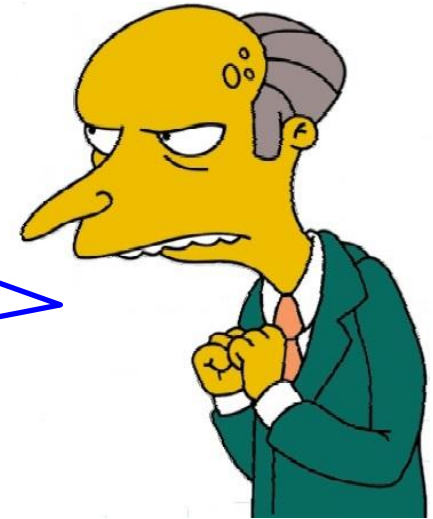**Q:** I thought you said this circuit **did** something. It appears to be just as **pointless** as all the others!




**A:** To see how this circuit is **useful**, consider what happens when the **input** voltage  $V_i$  is 0 V and 5V.

## The MOSFET as a Switch and an Amplifier (contd.)

- From the transfer function, we find that if  $V_i = 0V$ , the output voltage will be  $V_o = 5V$ . Likewise, if the input voltage is  $V_i = 5V$ , the output voltage will be small.

- Let's summarize these results in a table:

$V_i$	$V_o$	Mode
0.0	5.0	Cutoff
5.0	Small ( $\sim 0.5$ )	Triode

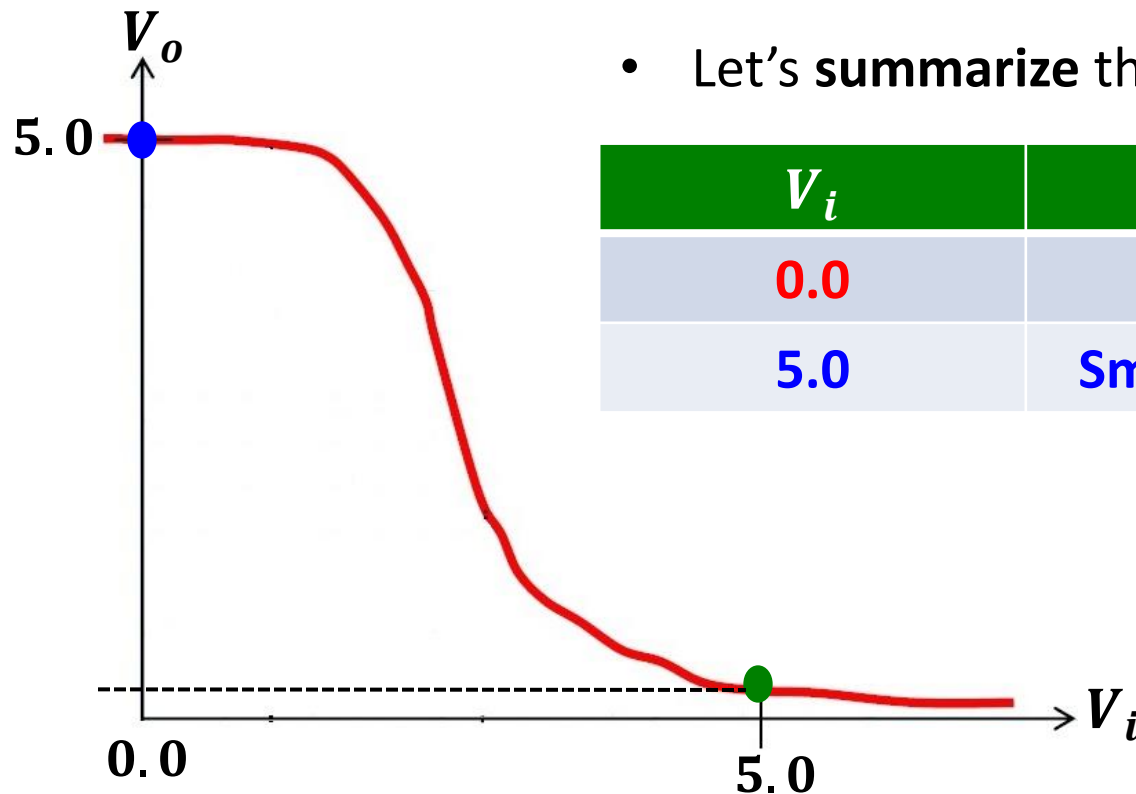

## The MOSFET as a Switch and an Amplifier (contd.)


Why, this device is not useless at all! It is **clearly** a:

**Switch**



- This circuit provides a **simple** example of **one** of the primary **applications** of MOSFET devices—**digital circuit design**. We can use MOSFETs to make digital devices such as **logic gates** (AND, OR, NOR, etc.), **flip-flops**, and digital **memory**.
  - We typically find that, just like this circuit, when a MOSFET digital circuit is in **either** of its **two** binary states (i.e., “0” or “1”), the MOSFETs in the circuit will either be in **cutoff** ( $I_D = 0$ ) or in **triode** ( $V_{DS}$  small) modes.
- **Cutoff** and **Triode** are the MOSFET modes associated with **digital** circuits and applications!
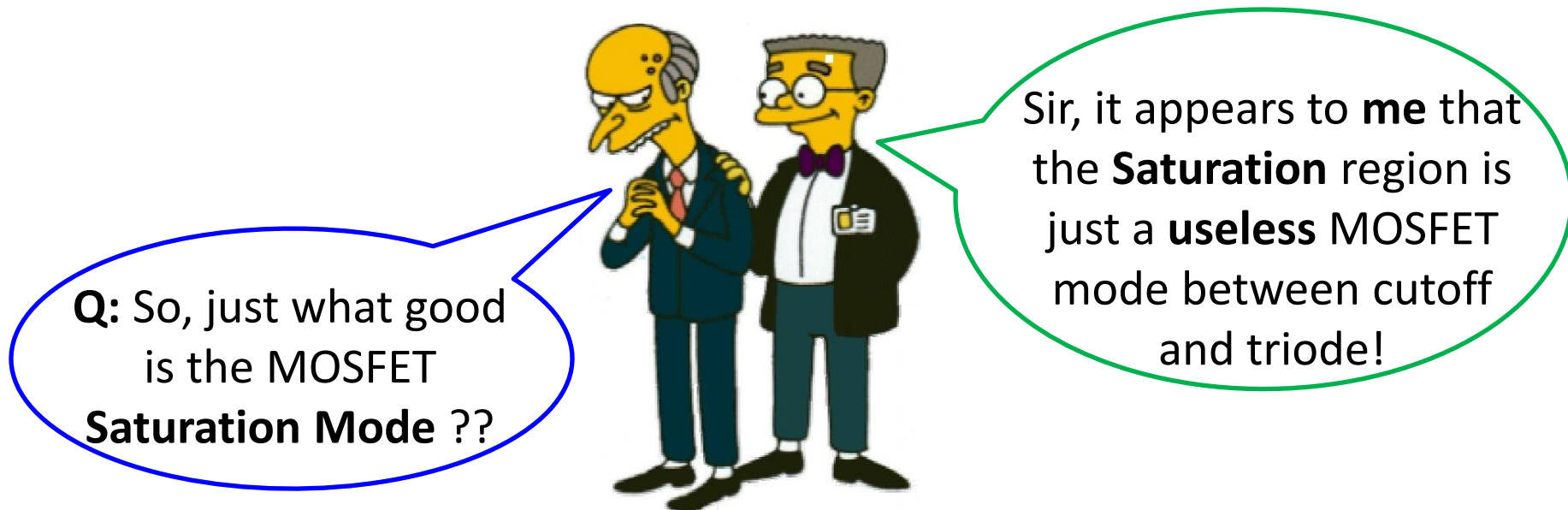
## The MOSFET as a Switch and an Amplifier (contd.)




**A:** Actually, we will find the MOSFET **saturation** mode to be **extremely useful!**


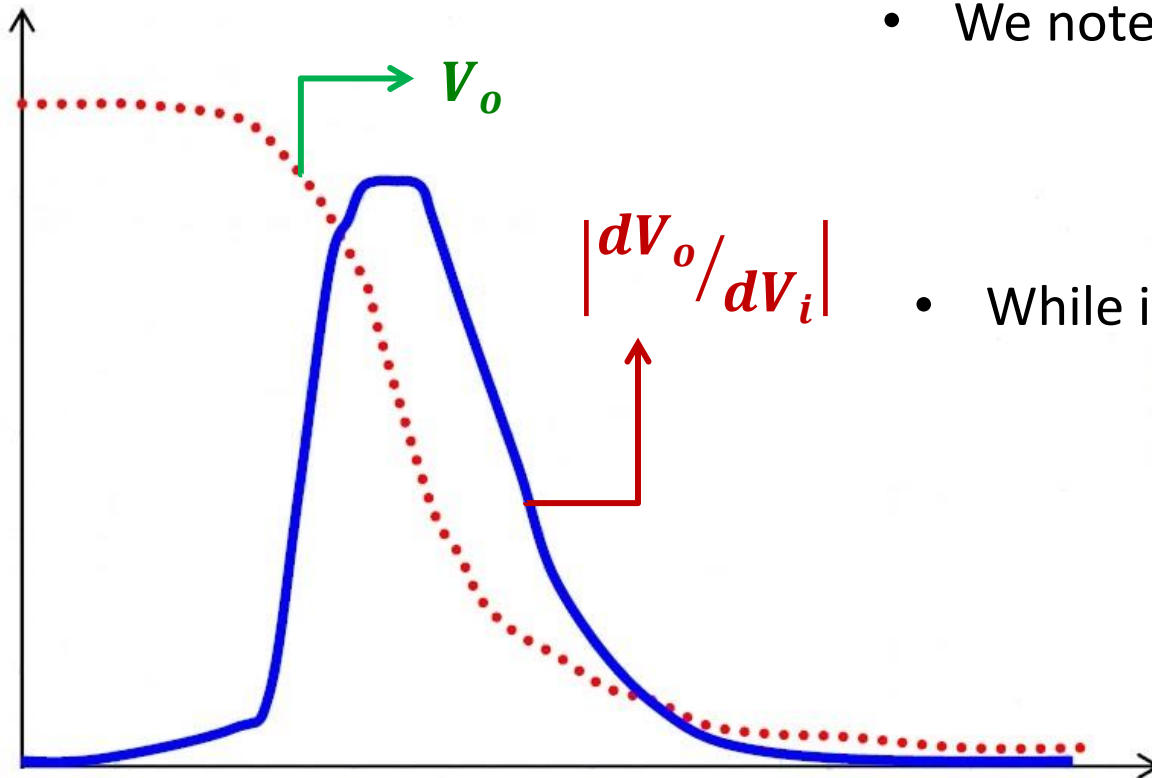
## The MOSFET as a Switch and an Amplifier (contd.)

- To see why, let us take the **derivative** of the above circuit's transfer function (i.e.,  $dV_o/dV_i$ ).



- We note that in **cutoff** and **triode**:

$$\left| \frac{dV_o}{dV_i} \right| \approx 0$$

- While in the **saturation** mode:

$$\left| \frac{dV_o}{dV_i} \right| \gg 1$$

## The MOSFET as a Switch and an Amplifier (contd.)

**Q:** Oh goody. The **slope** of the transfer function is **large** when the MOSFET is in **saturation**. Am I supposed to be impressed by that?! How are these results even **remotely** important!?



**A:** Since in **cutoff** and **triode**  $\left| \frac{dV_o}{dV_i} \right| \approx 0$ , a **small change** in input voltage  $V_i$  will result in almost **no change** in output voltage  $V_o$ .

Contrast this with the **saturation** region, where  $\left| \frac{dV_o}{dV_i} \right| \gg 1$ . This means that a **small change** in input voltage  $V_i$  results in a **large change** in the **output** voltage  $V_o$ !

## The MOSFET as a Switch and an Amplifier (contd.)

- To see how this is important, consider the case where the input signal has both a **DC** and a **small-signal** (AC) component:

$$v_I(t) = V_i + v_i(t)$$



- As a result, the **output** voltage likewise has both a DC and small signal component:

$$v_O(t) = V_o + v_o(t)$$

Now, let's consider **only** the **DC** components. We can select the DC input  $V_i$  such that the MOSFET is placed in **saturation**. The value  $V_i$ , along with the resulting DC output  $V_o$ , sets a **DC bias point** for this circuit.

By selecting the right value of  $V_i$  we **could** set this DC bias point to where the transfer function **slope** is the greatest.
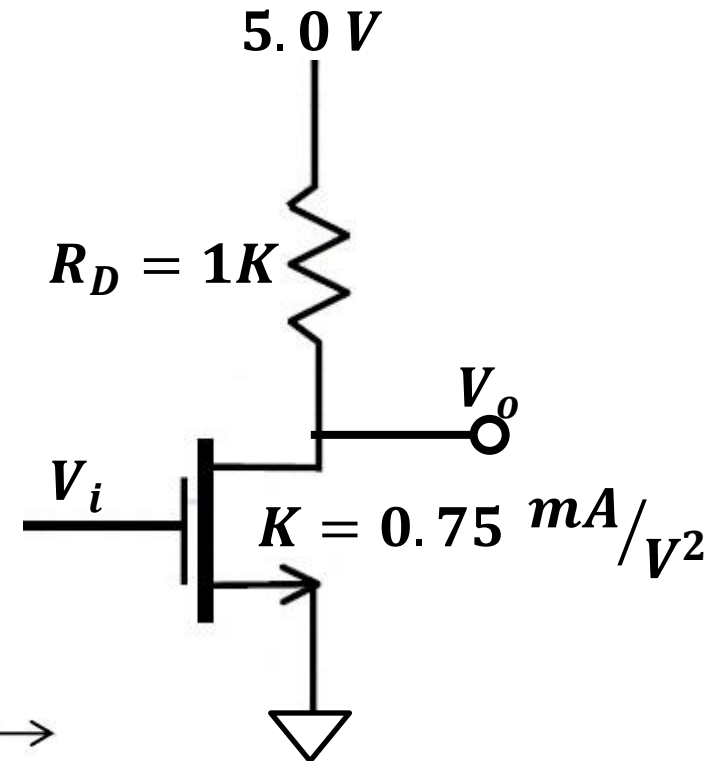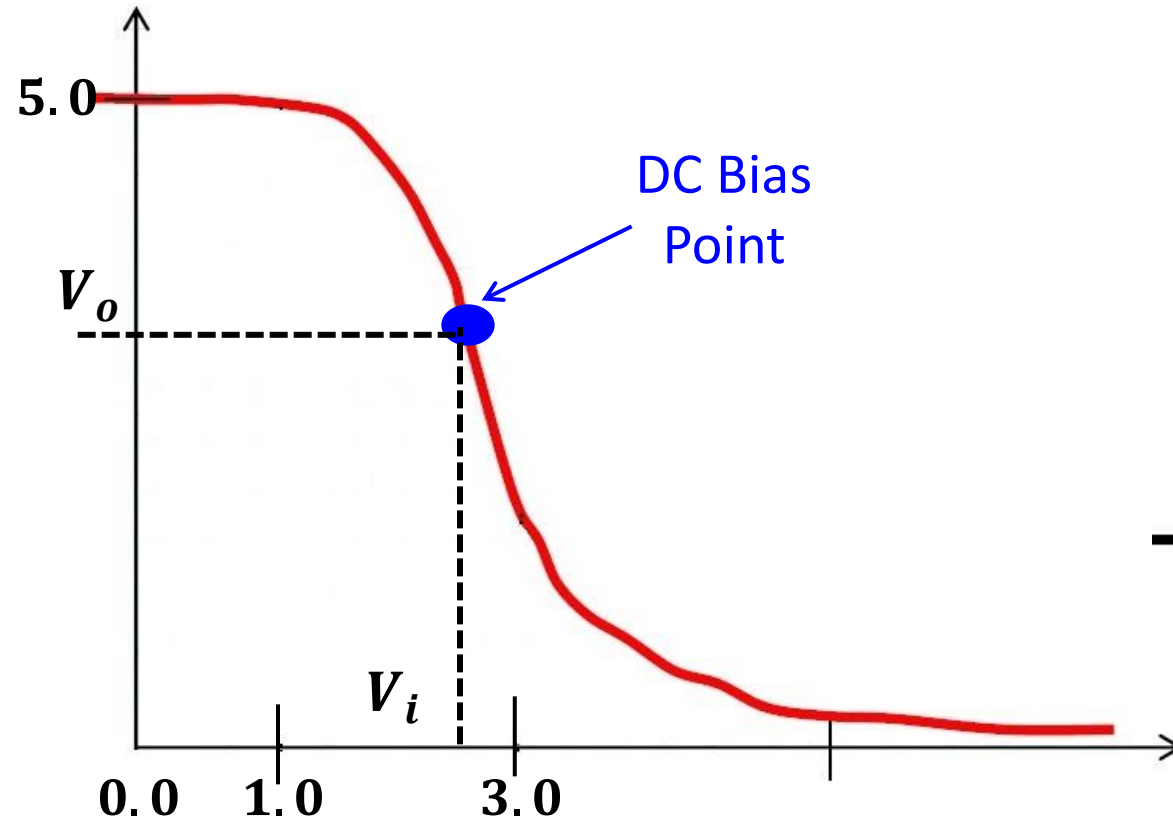
## The MOSFET as a Switch and an Amplifier (contd.)



Now, say we **add a small-signal**  $v_i$  to this input DC voltage (i.e.,  $v_I(t) = V_i + v_i(t)$ ). This small signal simply represents a small change in the input voltage from its **average** (i.e., DC) value. The result is of course as **small change** in the **output** voltage— the **small-signal output voltage**  $v_o(t)$ !

## The MOSFET as a Switch and an Amplifier (contd.)

- Now for the **interesting** part (I bet you were wondering when I would get around to it)! The small change in the output voltage will have a much **larger** magnitude than the small change in the input!

For example, if the input voltage changes by **1 mV** (i.e.,  $v_i = 1\text{mV}$ ), the output **might** change by, say, **5 mV** (i.e.,  $v_o = 5\text{mV}$ ).

**Q:** Goodness! By how much would the **output** change in our example circuit? How can we **determine** the small signal **output**  $v_o$  ??



## The MOSFET as a Switch and an Amplifier (contd.)

- Determining how much the output voltage of our circuit will change when we change the input voltage by a small amount is very **straightforward**— we simply take the **derivative** of the output voltage  $v_O$  with respect to input voltage  $v_I$ .
- By taking the **derivative** of  $v_O$  with respect to  $v_I$  (when the MOSFET is in saturation, we find:

$$\frac{dv_O}{dv_I} = \frac{d(5.0 - 0.75(v_I - 1.0)^2)}{dv_I} \quad \longrightarrow \quad = -1.50(v_I - 1.0)$$

when  $1.0 < v_I < 3.0 V$

The expression describes the **slope** of our circuit's transfer function (for  $1.0 < v_I < 3.0 V$ ). Note the slope with the **largest magnitude** occurs when  $v_I = 3.0V$ , providing a **slope** of  $-3.0 \text{ mV/mV}$ .

## The MOSFET as a Switch and an Amplifier (contd.)

- Thus, if we DC bias this circuit with  $V_i = 3.0$  V (resulting in  $V_o = 2.0$  V), we find that the small signal output will be **3 times** the small signal input!
- For example, say that the **input** to our circuit is:

$$v_I(t) = 3.0 + 0.01 \cos(\omega t) \text{ V} \quad \text{Here: } V_i = 3.0 \text{ V} \quad v_i = 0.01 \cos(\omega t)$$

- We would find that the **output voltage** would approximately be:

$$v_O(t) = 2.0 - 0.03 \cos(\omega t) \text{ V} \quad \text{Here: } V_o = 2.0 \text{ V} \quad v_o = -0.03 \cos(\omega t)$$


In other words, the magnitude of the small-signal output has a magnitude **three times larger** than the input magnitude.

We say then that our signal provides **small-signal gain**—our circuit is also a **small-signal amplifier**!
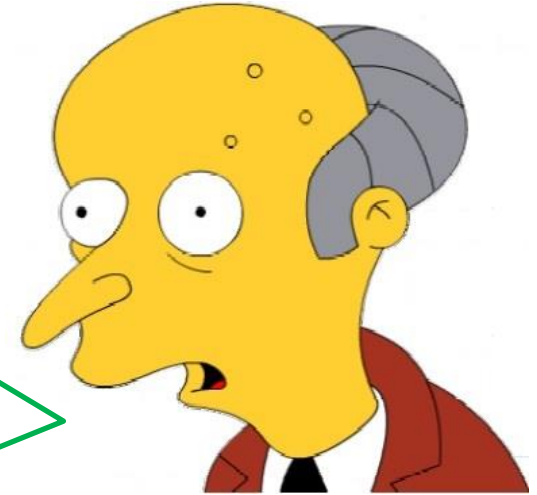
## The MOSFET as a Switch and an Amplifier (contd.)

I see. A **small** voltage change results in a **big** voltage change—it's **voltage gain!**

The **MOSFET saturation** mode turns out to be—**excellent.**




- Even the simple circuit of this example is sufficient to demonstrate the **two primary applications** of MOSFET transistors--**digital** circuits and signal **amplification**.
- Whereas the important MOSFET regions for **digital** devices are **triode** and **cutoff**, MOSFETs in amplifier circuits are typically biased into the **saturation** mode!


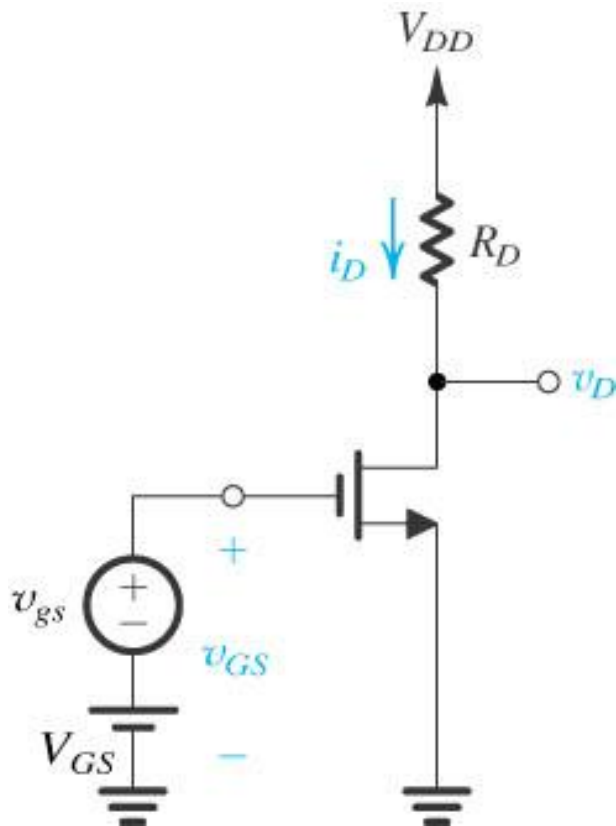
## MOSFET – Small Signal Operation

- Consider this circuit, which has both a **DC** and an AC **small signal** source. As a result, each voltage and current in the circuit has **both** a DC and small-signal component.



- If the MOSFET is in **saturation**, then the **total** drain current is:

$$i_D = K [V_{GS} + v_{gs} - V_T]^2$$

$$\Rightarrow i_D = \underbrace{K [V_{GS} - V_T]^2}_{I_D} + \underbrace{2K [V_{GS} - V_T] v_{gs}}_{i_d} + \underbrace{K v_{gs}^2}_{\text{small}} \quad \leftarrow \text{Very Small If: } v_{gs} \ll 2[V_{GS} - V_T]$$

**Very Small If:**  $v_{gs} \ll 2[V_{GS} - V_T]$

We call this equation the **small-signal** condition.

## MOSFET – Small Signal Operation (contd.)

Now,  $i_d = 2K[V_{GS} - V_T]v_{gs}$   $\Rightarrow \frac{i_d}{v_{gs}} = 2K[V_{GS} - V_T]$   $\leftarrow g_m$


Alternatively,  $\Rightarrow g_m = 2KV_{OV}$

- The small-signal parameter  $g_m$  can likewise be **derived** from a small-signal analysis of the drain current:

$$i_d = \left. \frac{di_D}{dV_{GS}} \right|_{v_{GS}=V_{GS}} (v_{gs}) = 2K[v_{GS} - V_T]_{v_{GS}=V_{GS}} (v_{gs})$$

$$i_d = 2K[V_{GS} - V_T](v_{gs}) \quad i_d = g_m(v_{gs})$$

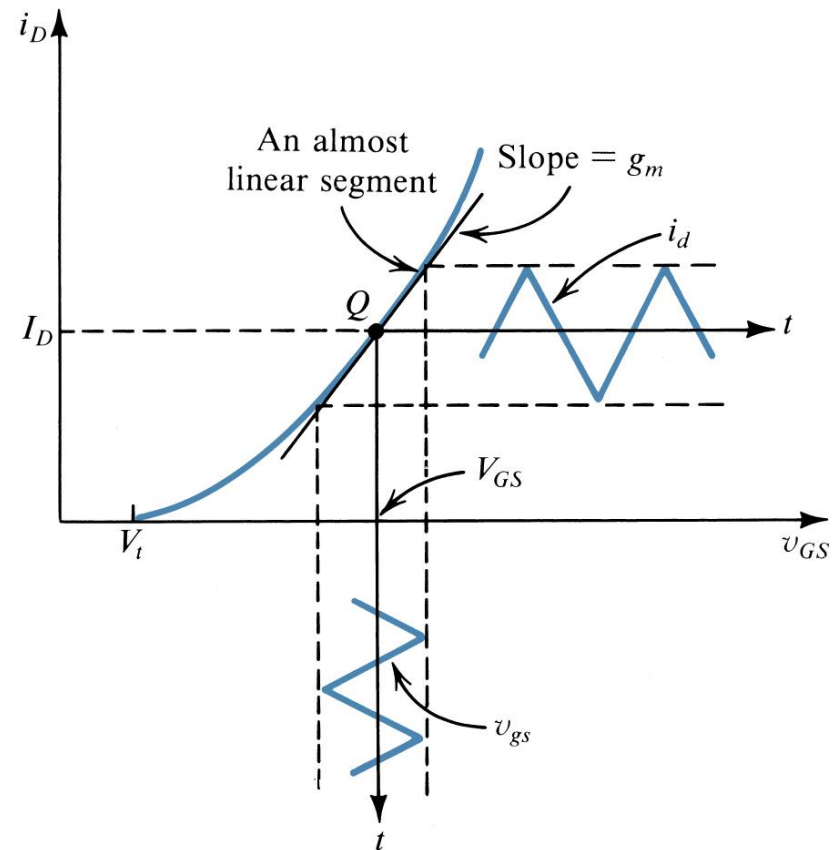Physical meaning of the  $g_m$   
 $\rightarrow$  formal definition






## MOSFET – Small Signal Operation (contd.)

The MOSFET transconductance relates a small **change** in  $v_{GS}$  to a small **change** in drain current  $i_D$ . This change is completely dependent on the **DC bias** point of the MOSFET,  $V_{GS}$  and  $I_D$ .
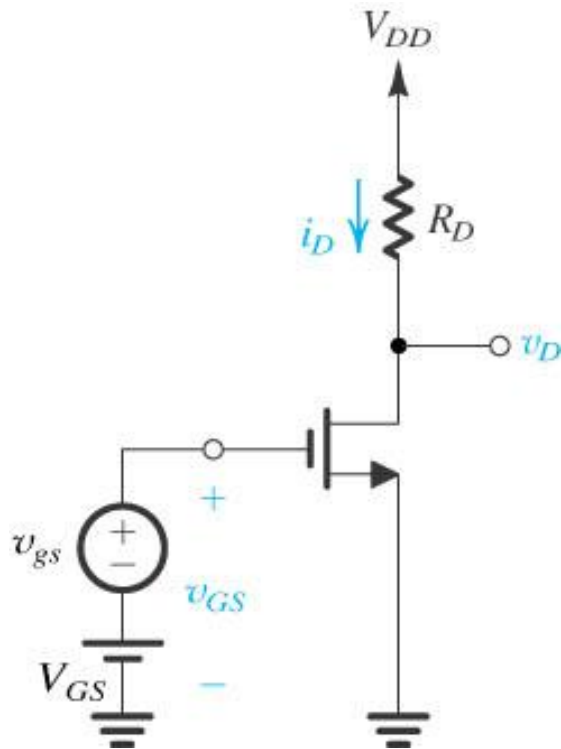
## MOSFET – Small Signal Operation (contd.)



- The total instantaneous drain voltage  $v_D$  is given by:

$$v_{DS} = v_D = V_{DD} - i_D R_D$$

- Under small signal condition it changes to:

$$v_D = V_{DD} - R_D (I_D + i_d)$$



$$\Rightarrow V_D + v_d = V_{DD} - I_D R_D - i_d R_D$$

**Signal component of drain voltage ( $v_d$ )**

$$v_d = -i_d R_D = -g_m v_{gs} R_D \quad \Rightarrow A_v = \frac{v_d}{v_{gs}} = -g_m R_D$$

Thus, if  $g_m R_D \gg 1$ , we have small-signal **voltage gain**.
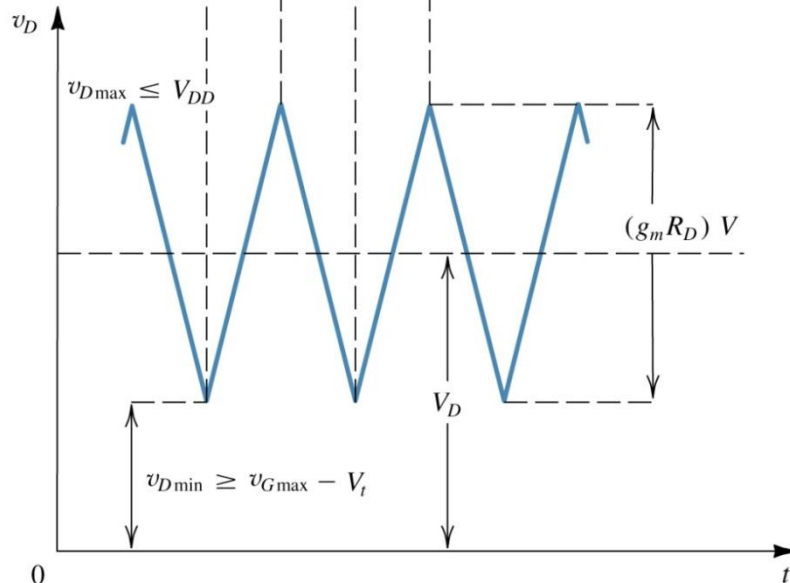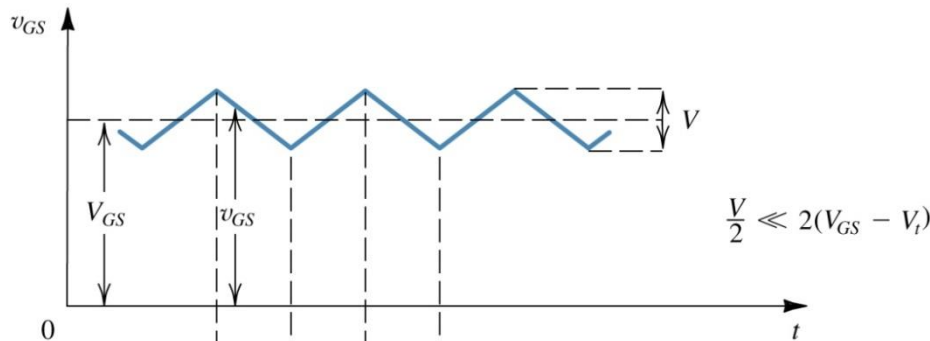
## MOSFET – Small Signal Operation (contd.)



$$A_v = \frac{v_d}{v_{gs}} = -g_m R_D$$

It indicates that  $v_d$  is  $180^\circ$  out of phase with respect to  $v_{gs}$

The input has been assumed very small as compared to overdrive voltage [ $v_{gs} \ll 2(V_{GS} - V_T)$ ]

For saturation:  $v_{Dmin} \geq v_{Gmax} - V_T$

$$v_{Dmax} \leq V_{DD}$$