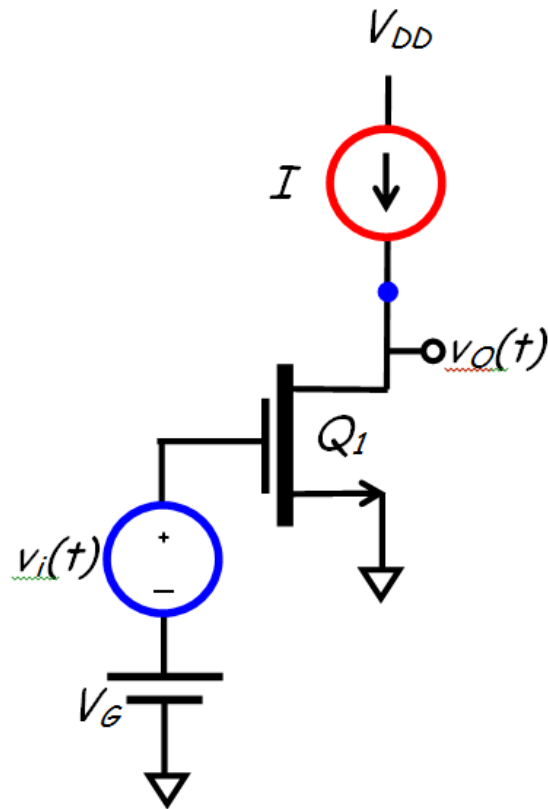


Lecture – 7

Date: 27.08.2015

- Common Source Amplifier with Constant Current Source, Triode Load, Source Degenerated Resistor
- Examples


CS Amplifier with Constant Current Source




- Now consider this NMOS amplifier using a **current source**.
- Note **no** resistors or capacitors are present!
- This is a **common source** amplifier.
- I_D stability is **not** a problem!

CS Amplifier with Constant Current Source (contd.)

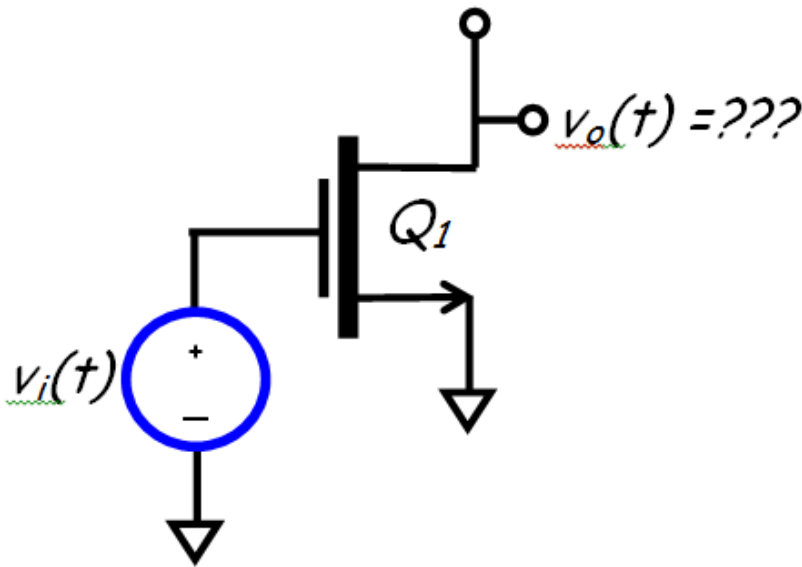Q: I don't understand! Wouldn't the small-signal circuit be:



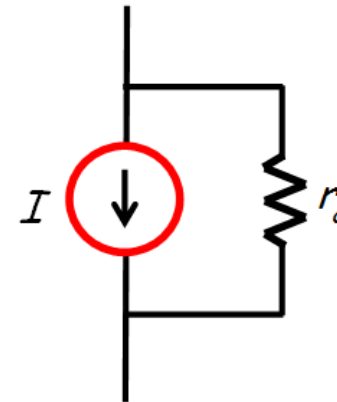
A: Remember, every **real** current source (as with every voltage source) has a **source resistance** r_o . A more **accurate** current source model is therefore:




Ideally, $r_o = \infty$. However, for good current sources, this output resistance is large (e.g., $r_o = 100 \text{ k}\Omega$). Thus, we mostly **ignore** this value (i.e., approximate it as $r_o = \infty$), but there are some circuits where this resistance makes quite a **difference**. \rightarrow **This** is one of those circuits!

CS Amplifier with Constant Current Source (contd.)

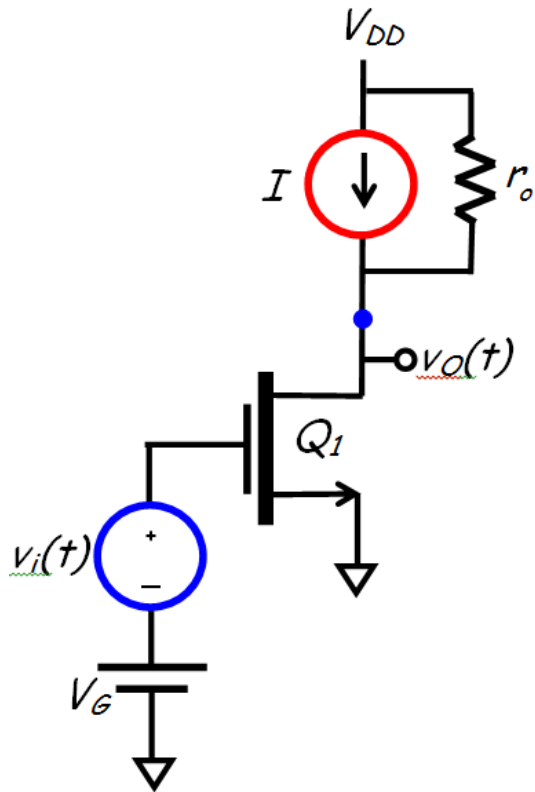- Therefore, a more **accurate** amplifier circuit schematic is:




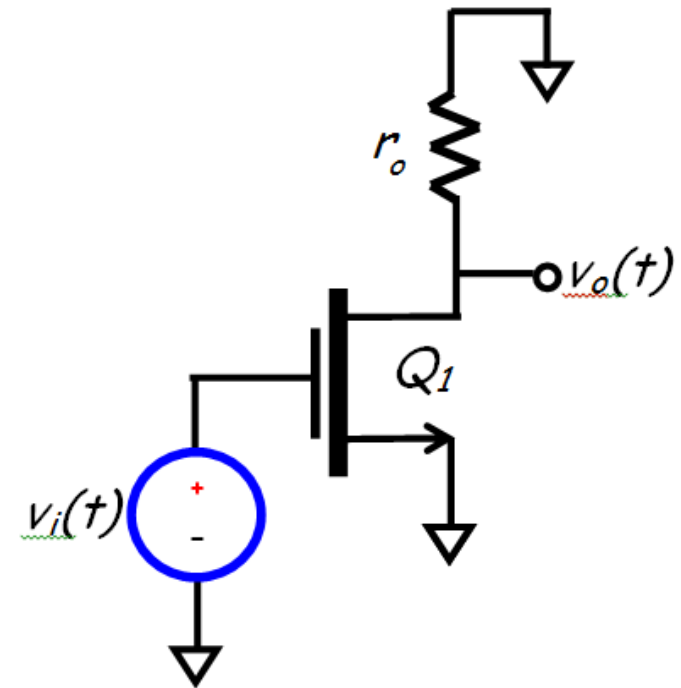- And so the **small-signal circuit** becomes the familiar:




CS Amplifier with Constant Current Source (contd.)

- Therefore, the small signal model is:

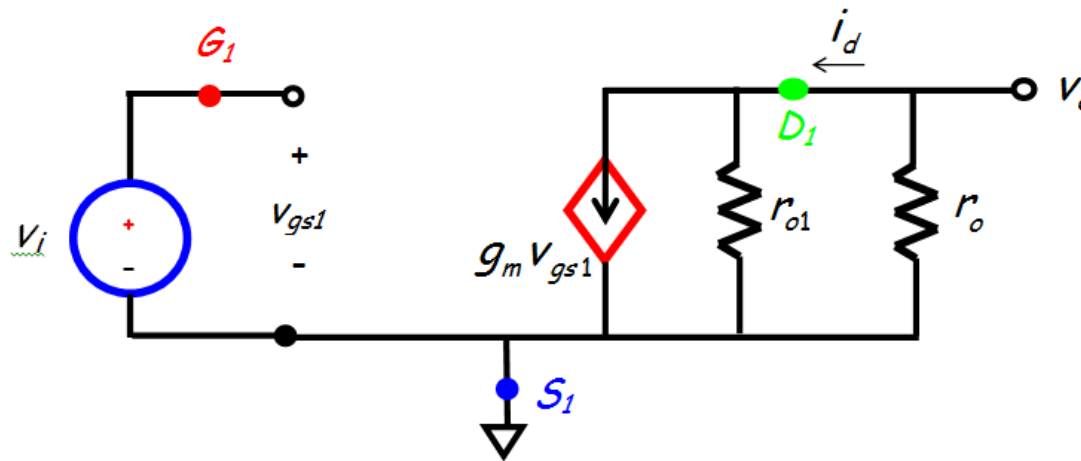


Now go ahead and do the analysis

Constant Current Source

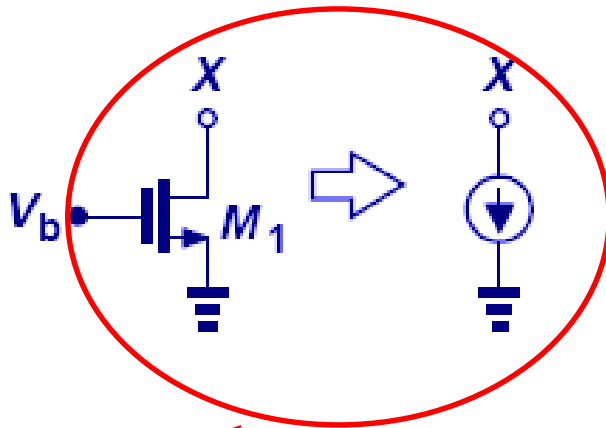

NFET ideal current source

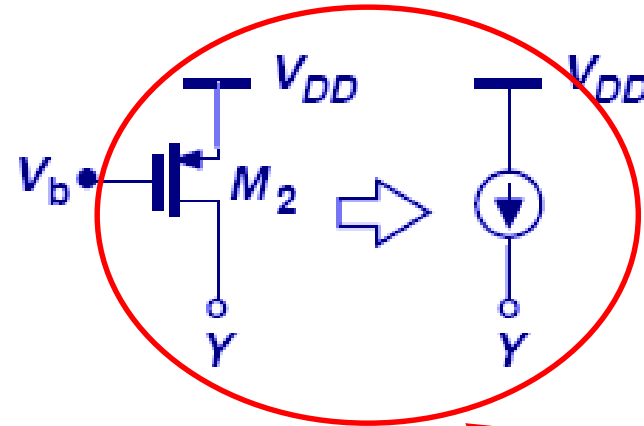


PFET ideal current source

- As long as a MOS transistor is in saturation region and $\lambda=0$, the current is independent of the drain voltage and it behaves as an ideal current source seen from the drain terminal.





Constant Current Source (contd.)

Example of poor current source

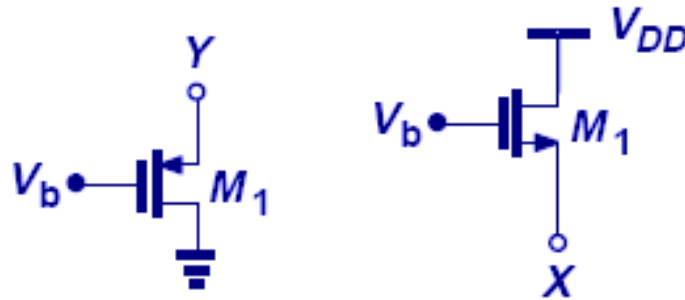

- Since the variation of the source voltage directly affects the current of a MOS transistor, it does not operate as a good current source if seen from the source terminal

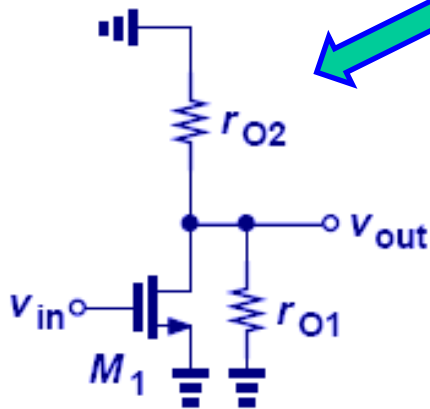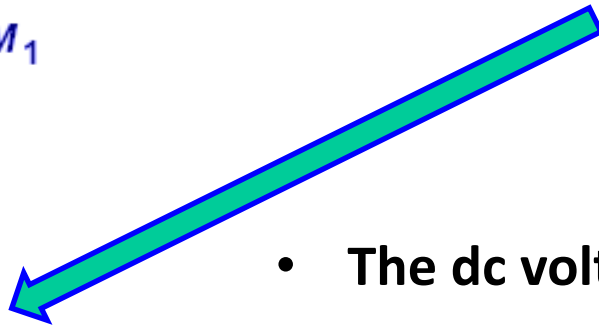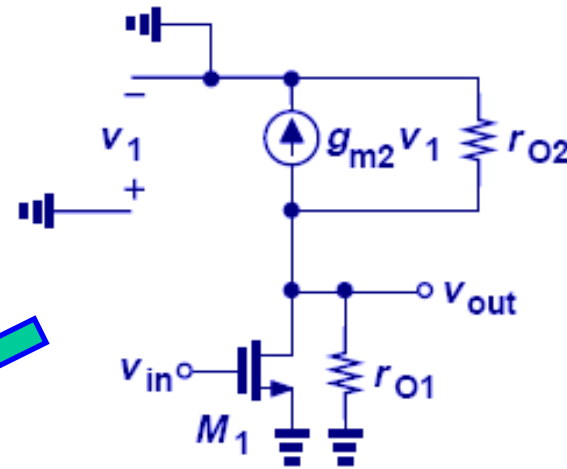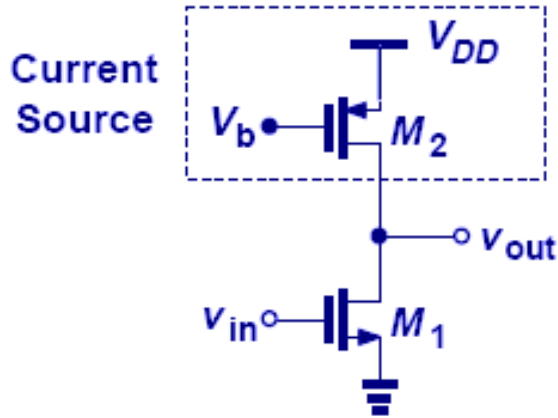CS Amplifier with Constant Current Source (contd.)



- The dc voltage V_{GS2} is constant and therefore $v_1 = 0 \rightarrow$ leads to $g_{m2}v_1 = 0$

CS Amplifier with Constant Current Source (contd.)

$$A_v = -g_{m1}(r_{o1} \parallel r_{o2})$$

- Both the load and the device operates in saturation
- The gain is loosely dependent on $|V_{DS}|$ of $M_2 \rightarrow$ as it regulates the r_{o2}
- The voltage $|V_{DS2,\min}| = |V_{GS2} - V_{T2}|$ can be reduced \rightarrow by increasing $(W/L)_2 \rightarrow$ increases $V_{D1} \rightarrow$ in essence the output voltage swing
- r_{o2} can be increased \rightarrow by reducing the channel length modulation effect \rightarrow through increasing the length and width of $M_2 \rightarrow$ while keeping $|V_{GS2} - V_{T2}|$ constant \rightarrow However, this also brings large capacitance at the output of M_2 .
- At a given drain current, W has to increase with the increasing L ($r_o \propto L/I_D$) for obtaining higher gain
- If length of M_1 is increased by a factor \rightarrow then the width has to be increased proportionally \rightarrow for a given I_{D1} , $V_{GS1} - V_{T1}$ is directly proportional to $(W/L)_1 \rightarrow$ if W_1 is not scaled properly then it will reduce $V_{GS1} - V_{T1} \rightarrow$ will effectively lead to reduced voltage swing


CS Amplifier with Constant Current-Source Load (contd.)

- Furthermore, just scaling of L_1 leads to reduced g_{m1} → in essence possibility of reduced gain

- However,
$$g_{m1}r_{o1} = \sqrt{2\left(\frac{W}{L}\right)_1 \mu_n C_{ox} I_D} \frac{1}{\lambda I_D}$$

- The gain will increase with increasing L_1 considering that λ depends more strongly on L than g_m does
- for M_2 , increase in L_2 while keeping W_2 constant → increases r_{o2} → increases gain of the CS amplifier → but decreases $|V_{DS2}|$ → reduces the output voltage swing

CS Amplifier with Triode Load

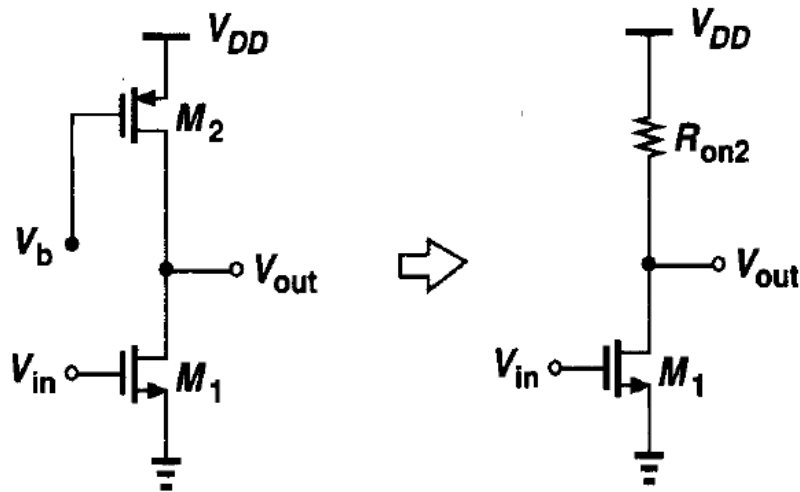


$$R_{on2} = \frac{1}{\mu_p C_{ox} (W/L)_2 (V_{DD} - V_b - |V_{TP}|)}$$


$$A_v = -g_{m1} R_{on2} \quad A_v = -g_{m1} (r_{o1} \parallel R_{on2})$$

- The main limitation of this technique is the dependence of gain on the process parameters → because R_{on} is dependent on these parameters
- Process parameters are temperature dependent → makes gain dependent on temperature
- Triode loads consume less voltage headroom as compared to diode-connected load → Here, $V_{out,max} = V_{DD}$

CS Amplifier with Source Degeneration

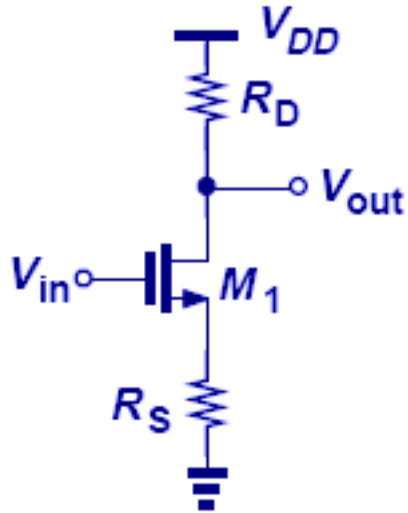

small signal
model

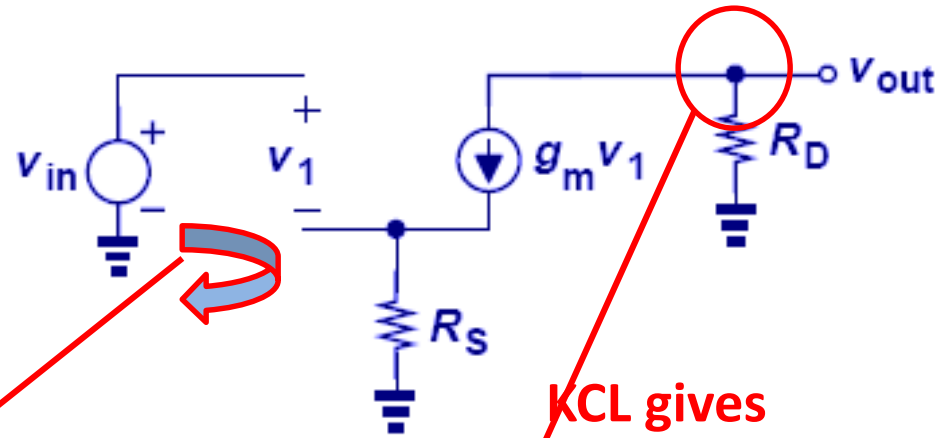

KVL gives

$$v_{in} = v_1 + g_m v_1 R_S$$

KCL gives

$$g_m v_1 = -\frac{v_{out}}{R_D} \Rightarrow v_1 = -\frac{v_{out}}{g_m R_D}$$


$$\therefore v_{in} = -\frac{v_{out}}{g_m R_D} (1 + g_m R_S)$$

CS Amplifier with Source Degeneration (contd.)


- Therefore the voltage gain: $A_v = \frac{v_{out}}{v_{in}} = -\frac{g_m R_D}{(1 + g_m R_S)}$

- The input resistance: $R_{in} = \infty$


- The output resistance: $R_{out} = R_D$

- For large R_S : $A_v = -\frac{R_D}{R_S}$  **Linear**

$$V_{DD} - V_{in} + V_T > I_D R_D \quad \leftarrow \quad V_{DD} - I_D R_D > V_{in} - V_T$$

- A_v drops when: $V_{DD} - V_{in} + V_T < I_D R_D$  **M_1 goes in triode**

Valid as long as M_1 is in saturation



Even with all the supposed benefits of this configuration, the major drawback is the reduced small-signal gain

CS Amplifier with Source Degeneration (contd.)

$$A_v = \frac{v_{out}}{v_{in}} = - \frac{g_m}{(1 + g_m R_S)} R_D$$

G_m

Equivalent Circuit Transconductance

$$G_m = \frac{g_m}{1 + g_m R_S} = \frac{1}{(1/g_m) + R_S}$$

For large V_{in} (while M_1 still in saturation) $\rightarrow g_m$ is high $\rightarrow G_m$ approaches $1/R_S$

$$\Rightarrow A_v = - \frac{R_D}{R_S}$$


Linear

Reduced Gain


CS Amplifier with Source Degeneration (contd.)

$$A_v = -\frac{g_m R_D}{(1 + g_m R_S)} = -\frac{R_D}{\left(\frac{1}{g_m} + R_S\right)}$$

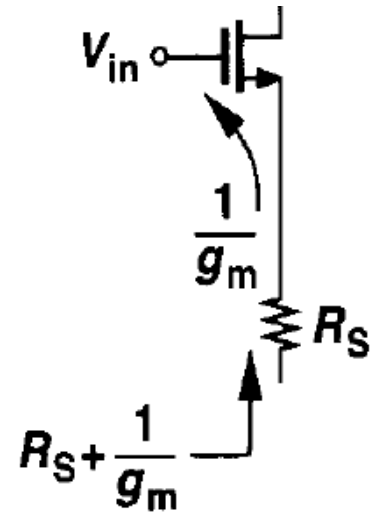Ratio of impedances in the drain and source path



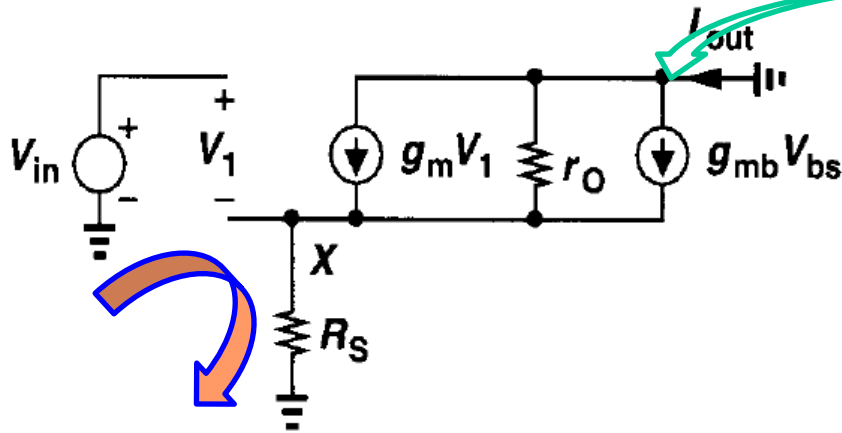With channel length modulation and body effect



KCL at output:

$$I_{out} = g_m V_1 - g_{mb} V_x - \frac{I_{out} R_S}{r_o}$$

$$\Rightarrow I_{out} = g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_o}$$


KVL at input:

$$V_{in} = V_1 + I_{out} R_S$$

$$\therefore G_m = \frac{I_{out}}{V_{in}} = \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}$$

CS Amplifier with Source Degeneration (contd.)

Output Resistance

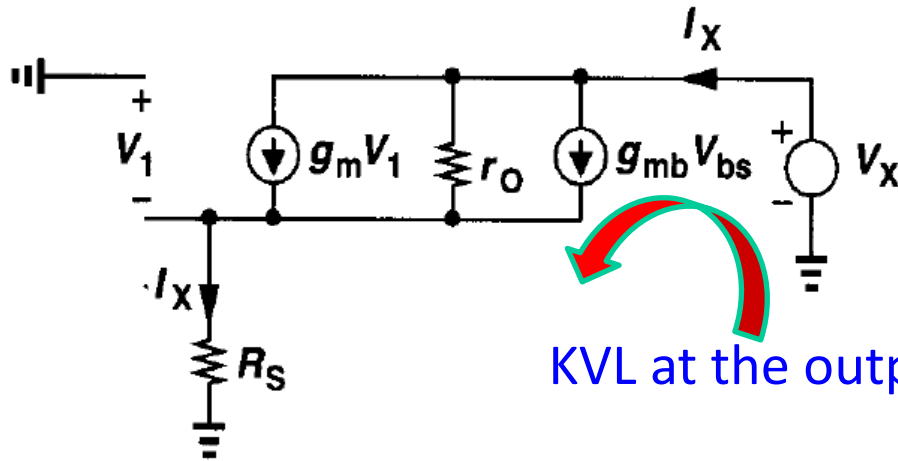

Current through R_S is I_X

$$\Rightarrow V_1 = -I_X R_S$$

Current through r_o is:

$$\Rightarrow I_{r_o} = I_X - (g_m + g_{mb})V_1$$

KVL at the output: $V_X = r_o [I_X + (g_m + g_{mb})R_S I_X] + I_X R_S$

$$\Rightarrow R_{out} = \frac{V_X}{I_X} = r_o [1 + (g_m + g_{mb})R_S] + R_S = [1 + (g_m + g_{mb})r_o]R_S + r_o$$

Usually, $(g_m + g_{mb})r_o \gg 1$

$$\therefore R_{out} \approx (g_m + g_{mb})r_o R_S + r_o$$

Output impedance has increased by this factor


$$\Rightarrow R_{out} \approx [1 + (g_m + g_{mb})R_S]r_o$$

Definitely a good prospect for applications requiring higher output impedance

Yes! It comes with a price
→ reduced gain

CS Amplifier with Source Degeneration (contd.)

Small-signal gain

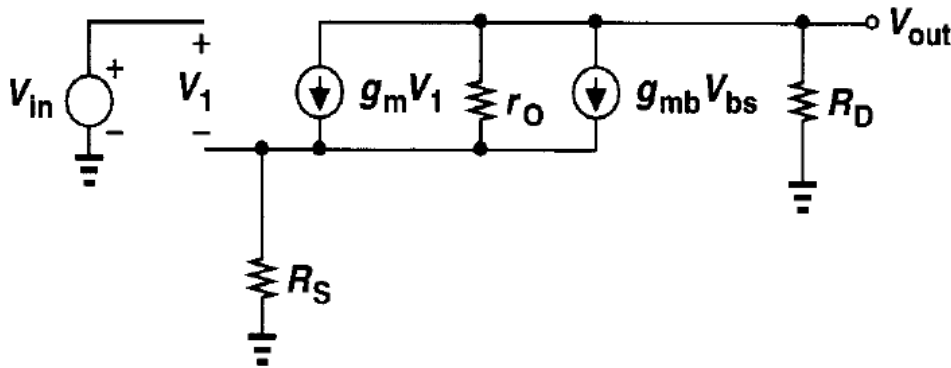

$$A_v = -\frac{V_{out}}{V_{in}}$$

$$= -\frac{g_m r_o R_D}{R_D + R_S + [1 + (g_m + g_{mb})R_S]r_o}$$

R_{out}

$$A_v = -\frac{g_m r_o R_D}{R_D + R_S + [1 + (g_m + g_{mb})R_S]r_o} \cdot \frac{R_S + [1 + (g_m + g_{mb})R_S]r_o}{R_S + [1 + (g_m + g_{mb})R_S]r_o}$$


For Simplification

$$A_v = \underbrace{\frac{g_m r_o}{R_S + [1 + (g_m + g_{mb})R_S]r_o}}_{G_m} \cdot \frac{[R_S + [1 + (g_m + g_{mb})R_S]r_o]R_D}{R_D + R_S + [1 + (g_m + g_{mb})R_S]r_o}$$

$R_D || R_{out}$

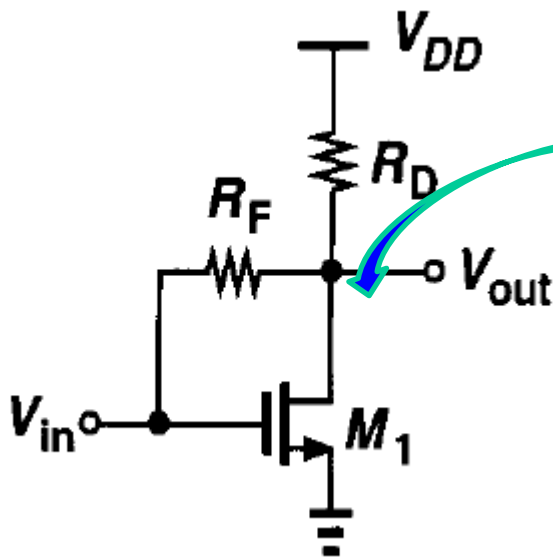Example – 1

- Assuming M_1 in saturation, calculate the small signal voltage gain of the following:




KCL at the output node:

$$\frac{v_{out} - v_{in}}{R_F} + g_{m1}v_{in} + \frac{v_{out}}{r_{o1}} + \frac{v_{out}}{R_D} = 0$$

$$A_v = \frac{v_{out}}{v_{in}} = -\frac{g_{m1} - \frac{1}{R_F}}{\frac{1}{R_F} + \frac{1}{r_{o1}} + \frac{1}{R_D}}$$

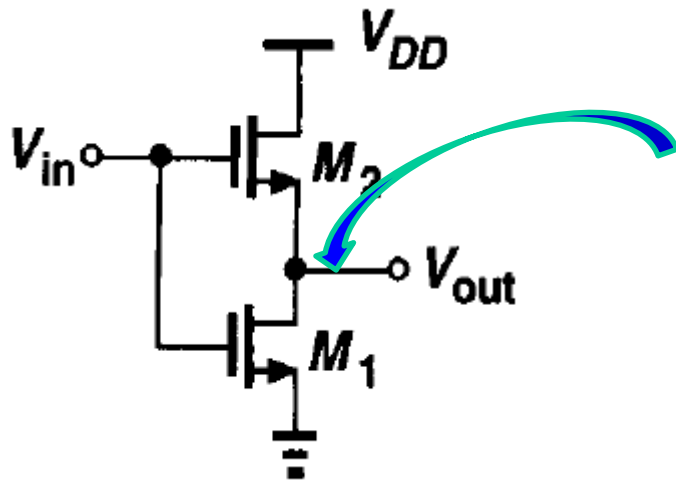Example – 2

- Assuming both M_1 and M_2 in saturation, calculate the small signal voltage gain of the following:




KCL at the output node:

$$g_{m2}(v_{in} - v_{out}) + \left(\frac{-v_{out}}{r_{o2}} \right) = g_{m1}v_{in} + \frac{v_{out}}{r_{o1}}$$

$$A_v = \frac{v_{out}}{v_{in}} = - \frac{g_{m1} - g_{m2}}{g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}}}$$

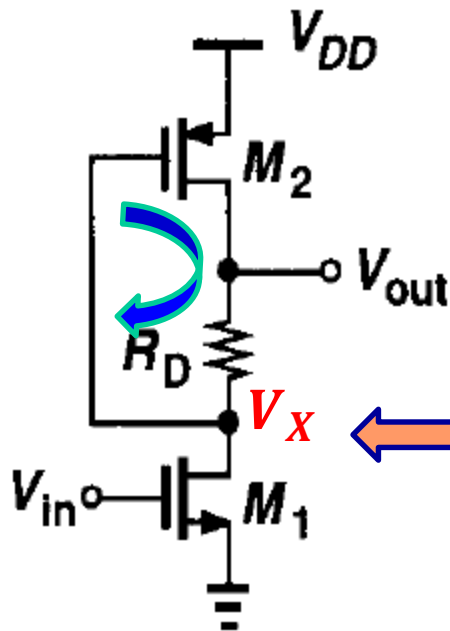Example – 3

- Assuming both M_1 and M_2 in saturation, calculate the small signal voltage gain of the following:



KVL in the mesh created by M_2 :

$$\left(g_{m1}v_{in} + \frac{v_x}{r_{o1}} \right) R_D + v_x = v_{out}$$

KCL at this node:

$$-\left(g_{m2}v_x + \frac{v_{out}}{r_{o2}} \right) = g_{m1}v_{in} + \frac{v_x}{r_{o1}}$$

$$v_x \left(-g_{m2} - \frac{1}{r_{o1}} \right) = g_{m1}v_{in} + \frac{v_{out}}{r_{o2}}$$

$$\therefore v_x = -\frac{g_{m1}v_{in} + \frac{v_{out}}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}}$$

Example – 3 (contd.)

$$\left(g_{m1} v_{in} + \frac{v_x}{r_{o1}} \right) R_D + v_x = v_{out} \quad \longrightarrow \quad g_{m1} R_D v_{in} + \left(1 + \frac{R_D}{r_{o1}} \right) v_x = v_{out}$$

- Simplification of the expressions gives:

$$g_{m1} R_D v_{in} - \frac{\left(1 + \frac{R_D}{r_{o1}} \right) \left(g_{m1} v_{in} + \frac{v_{out}}{r_{o2}} \right)}{g_{m2} + \frac{1}{r_{o1}}} = v_{out}$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{g_{m1} (g_{m2} R_D - 1)}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \left(1 + \frac{R_D}{r_{o1}} \right)}$$