




## Lecture – 8

Date: 31.08.2015

- Common Drain Amplifier
- Common Gate Amplifier
- Examples


## CD Amplifier (Source Follower)

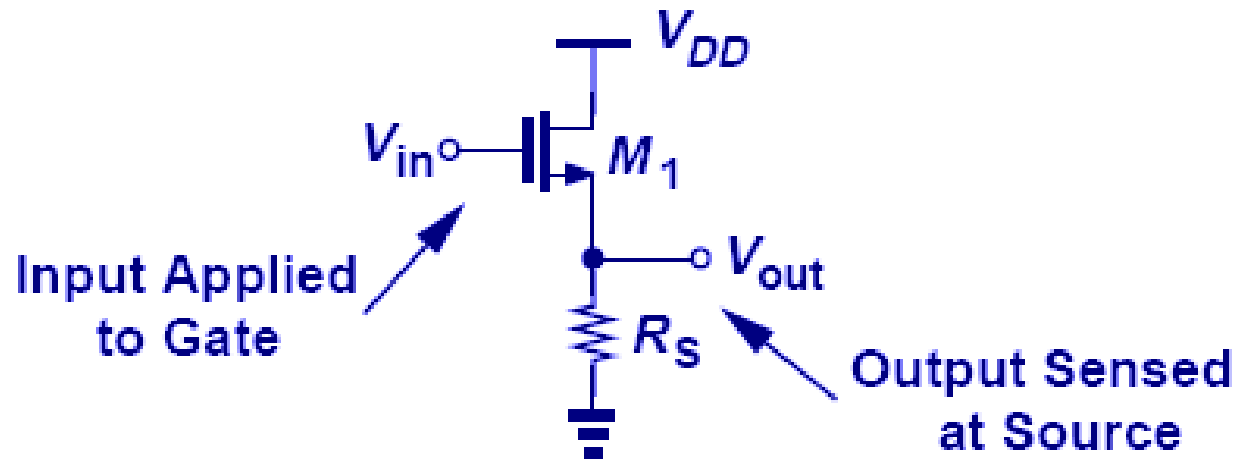

- It senses the input at the gate and produces the output at the source
- **CS-stage identifies that for achieving high voltage gain, the load impedance must be large** → if CS-stage is to be succeeded by a low impedance circuitry → a buffer is needed as a low impedance can't be driven by a CS-stage amplifier → **CD-stage works as a buffer**
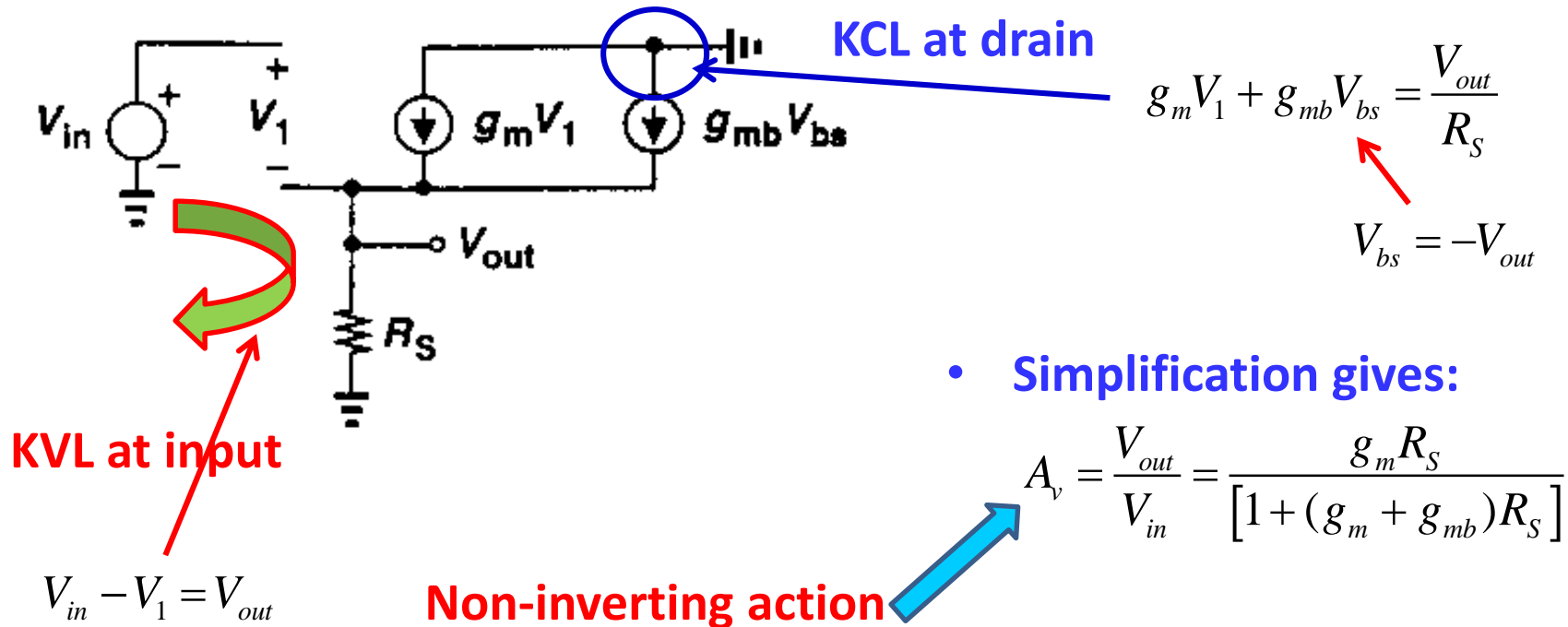
## CD Amplifier (Source Follower) – contd.

Let us look at the small-signal voltage gain of CD-stage:



Can you derive  $A_v$  without explicitly using the small signal model ?

## CD Amplifier (Source Follower) – contd.

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_S}{[1 + (g_m + g_{mb})R_S]}$$

### Observations

- For  $V_{in} = V_T$ , the transconductance  $g_m = 0$  and therefore  $A_v = 0$
- $V_{in}$  increases  $\rightarrow I_D$  increases  $\rightarrow$  leads to increase in  $g_m \rightarrow A_v$  increases and approaches:

$$A_v = \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}$$

$\eta$  decreases with increase in  $V_{out} \rightarrow$  leads to increase in  $A_v \rightarrow \eta$  is typically 0.2 and therefore  $A_v < 1$

Even for  $R_S = \infty$ , the small signal voltage gain  $A_v < 1$

## CD Amplifier (Source Follower) – contd.

### Example:


$$g_m = 2 \text{ mS}$$

$$g_{mb} = 0.328 \text{ mS}$$

$$R_S = 6 \text{ k}\Omega$$




Calculated  $A_v = 0.801$

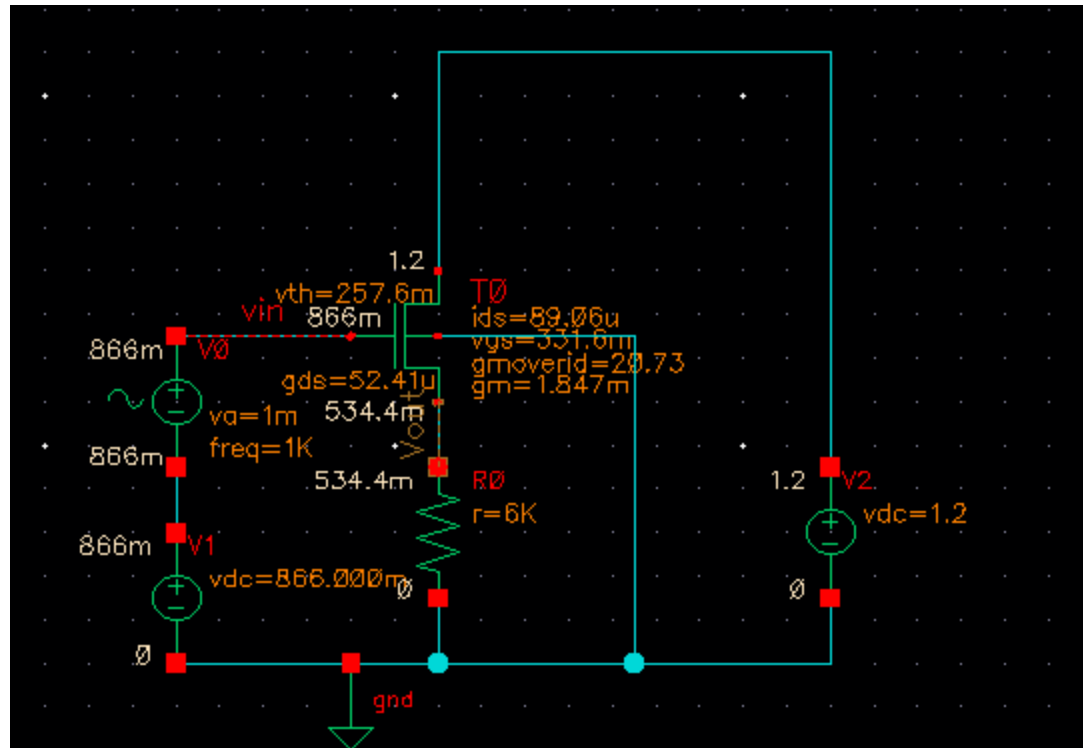

## CD Amplifier (Source Follower) – contd.

### Example (contd.):

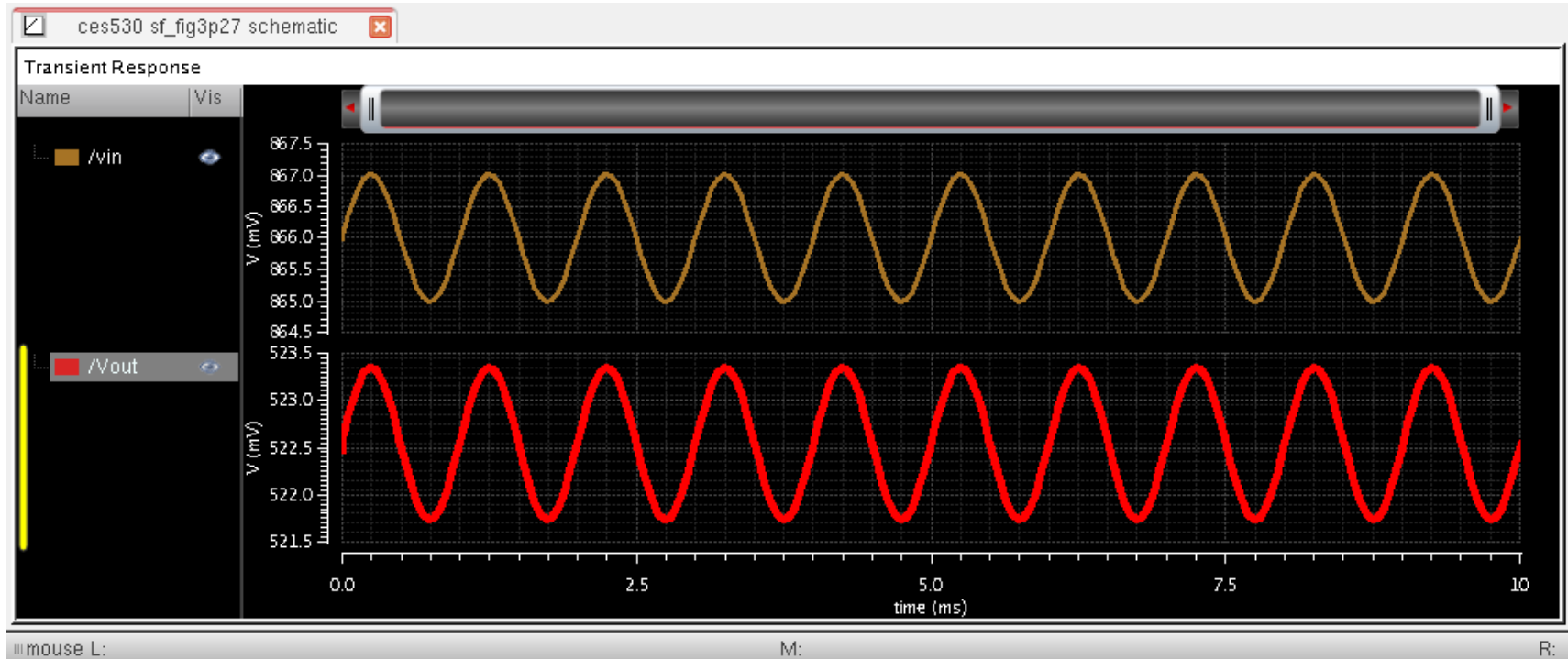

$$V_{in, pp} = 2 \text{ mV}$$

$$V_{out, pp} = 1.596 \text{ mV}$$

**Simulated:**  $A_v = 0.798$

## CD Amplifier (Source Follower) – contd.

$A_v < 1$  ← Definitely not an amplifier

- In the best case scenario when  $R_S$  is extremely high and body effect is ignored then:

$A_v = 1$  ← Usefulness as buffer

- How can you ignore body effect?


**Definitely not for NMOS**

**By employing a PMOS and with appropriate biasing**

## CD Amplifier (Source Follower) – contd.

- Furthermore, the strong dependence of  $A_v$  on the input voltage makes it a nonlinear configuration → Its due to strong dependence of  $I_D$  and therefore  $g_m$  on the input voltage  $V_{in}$


$$V_{in} = 1mV$$

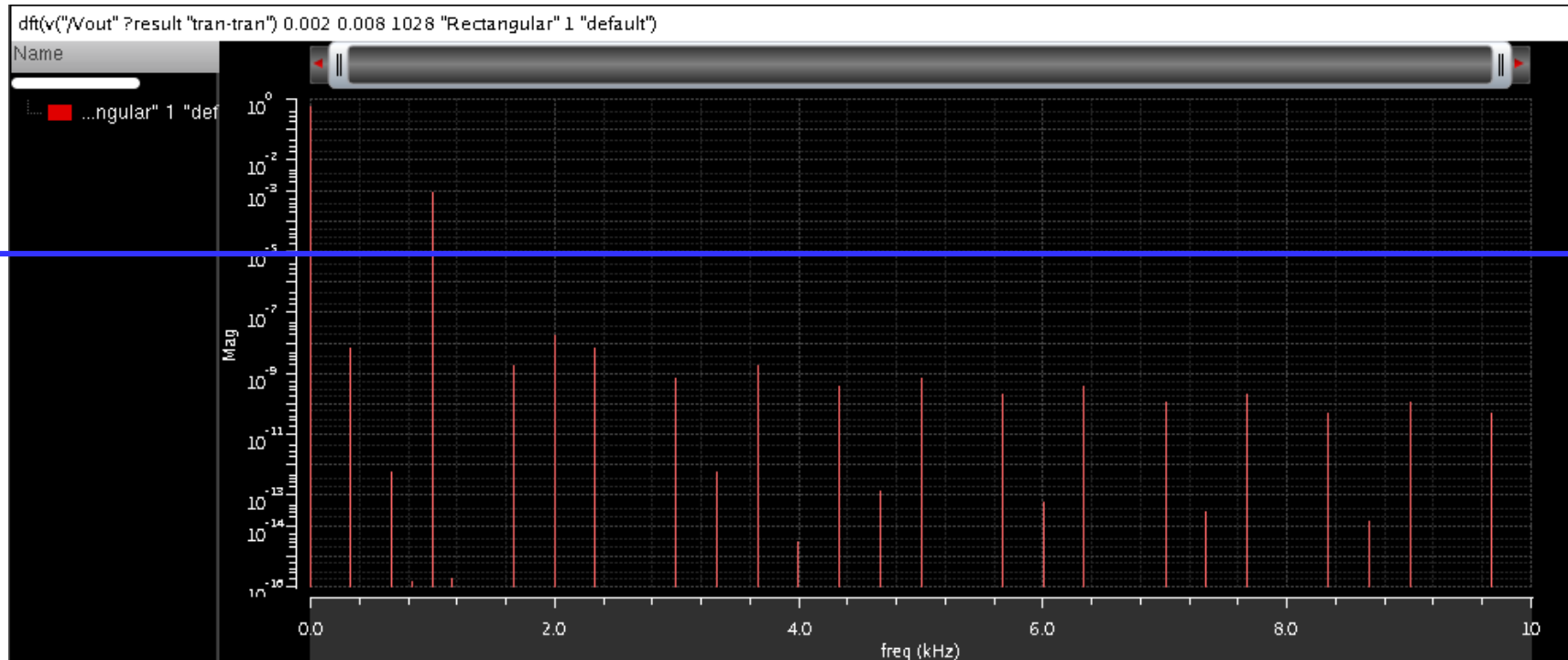




## CD Amplifier (Source Follower) – contd.

$$V_{in} = 330\text{mV}$$

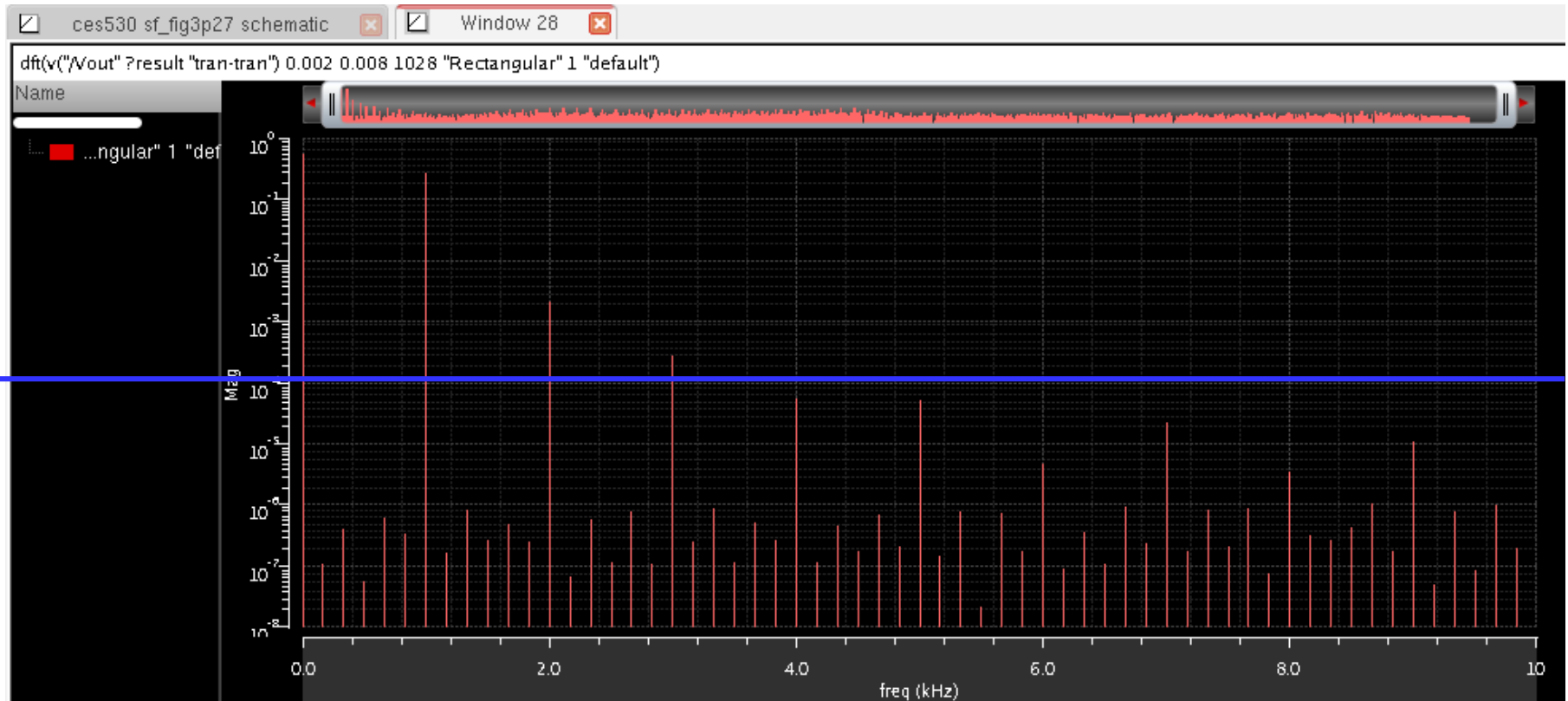

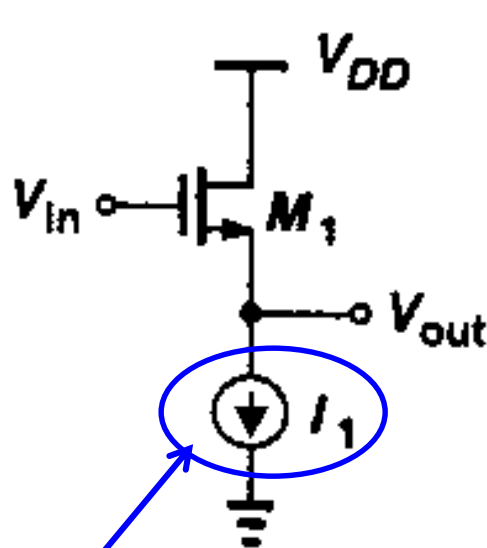
## CD Amplifier (Source Follower) – contd.

- To mitigate this dependence → resistor  $R_s$  is replaced by a current source → the current source is realized using an NMOS operating in saturation mode



Current source providing high  $R_s$

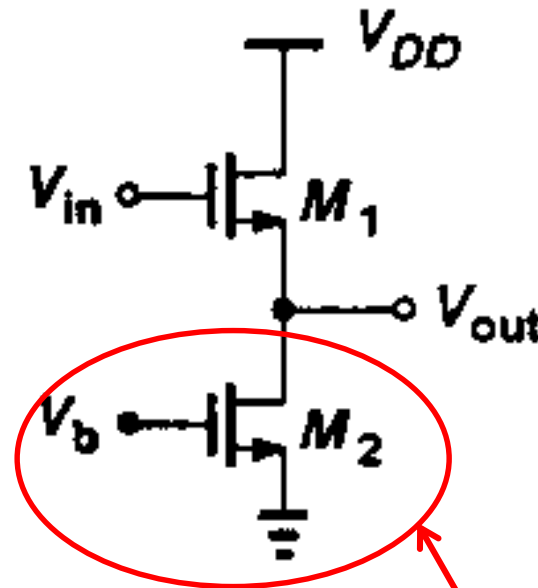


NMOS Operating in Saturation


$$A_v = \frac{\frac{1}{g_{mb}} \parallel r_{o1} \parallel r_{o2}}{\frac{1}{g_{mb}} \parallel r_{o1} \parallel r_{o2} + \frac{1}{g_m}}$$

## CD Amplifier (Source Follower) – contd.

- Let us get back to that example

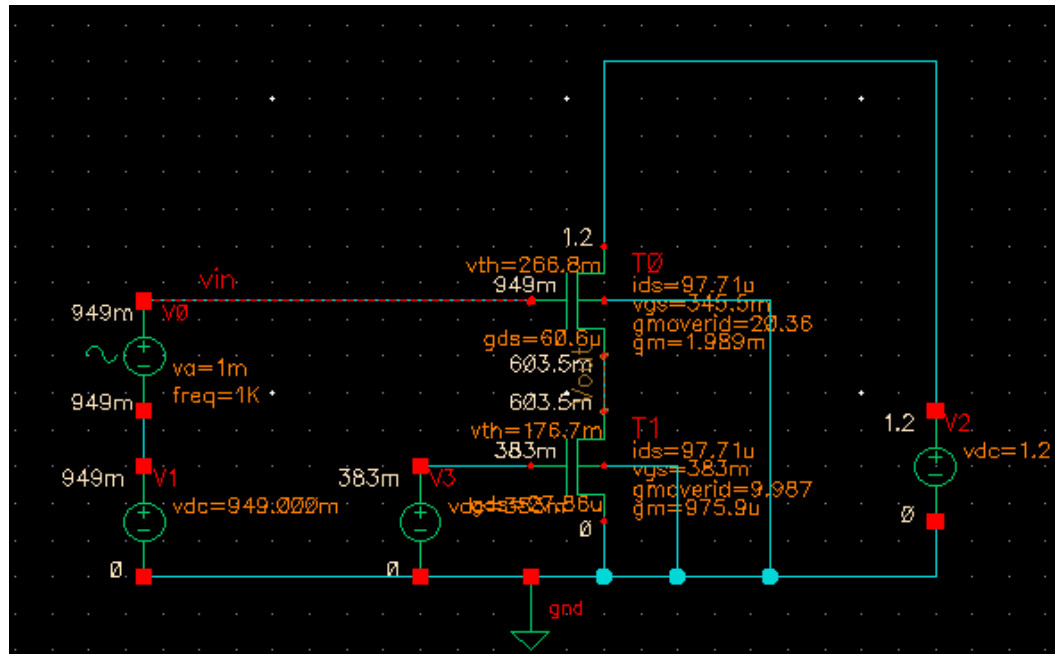
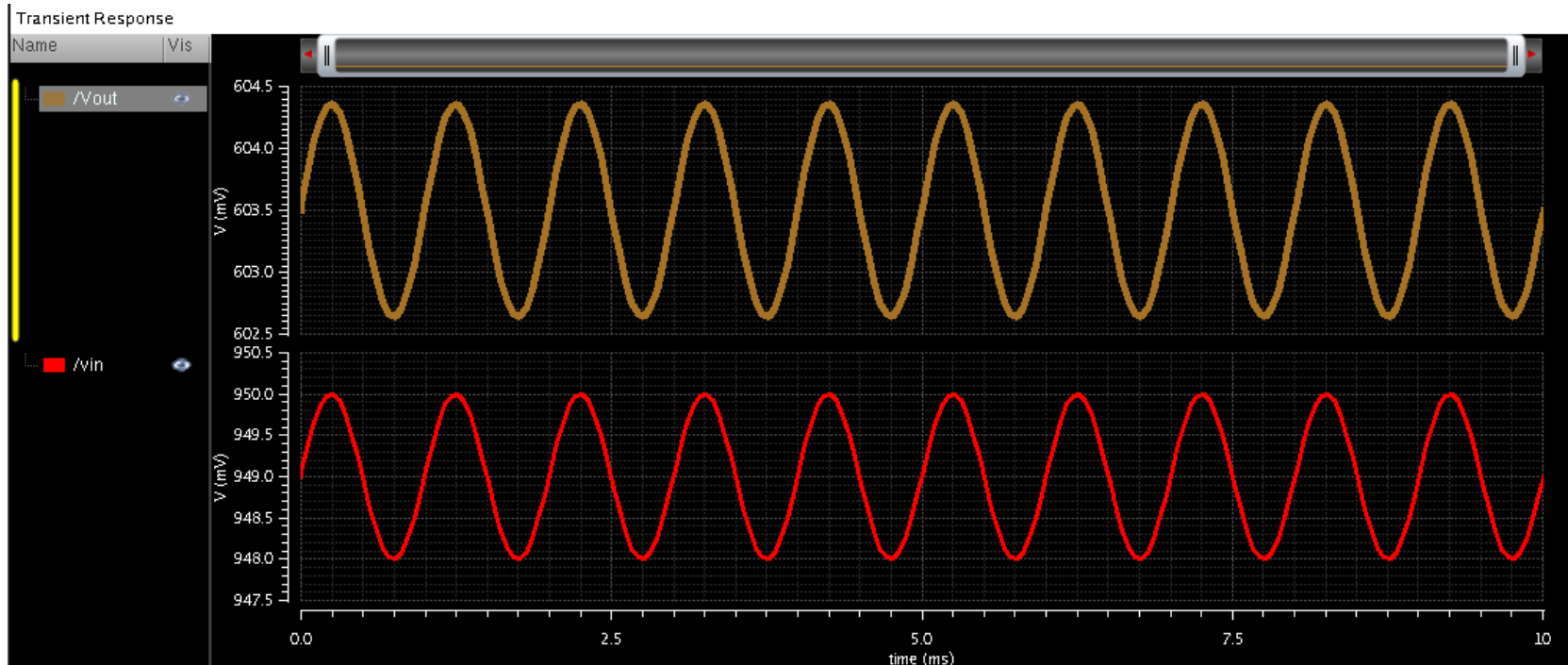
## CD Amplifier (Source Follower) – contd.



$$V_{in, pp} = 2 \text{ mV}$$

$$V_{out, pp} = 1.705 \text{ mV}$$


$$\text{Simulated: } A_v = 0.8525$$

## CD Amplifier (Source Follower) – contd.

$$V_{in} = 330\text{mV}$$


$$R_S = 6\text{k}\Omega$$

$$R_S = \text{CS}$$

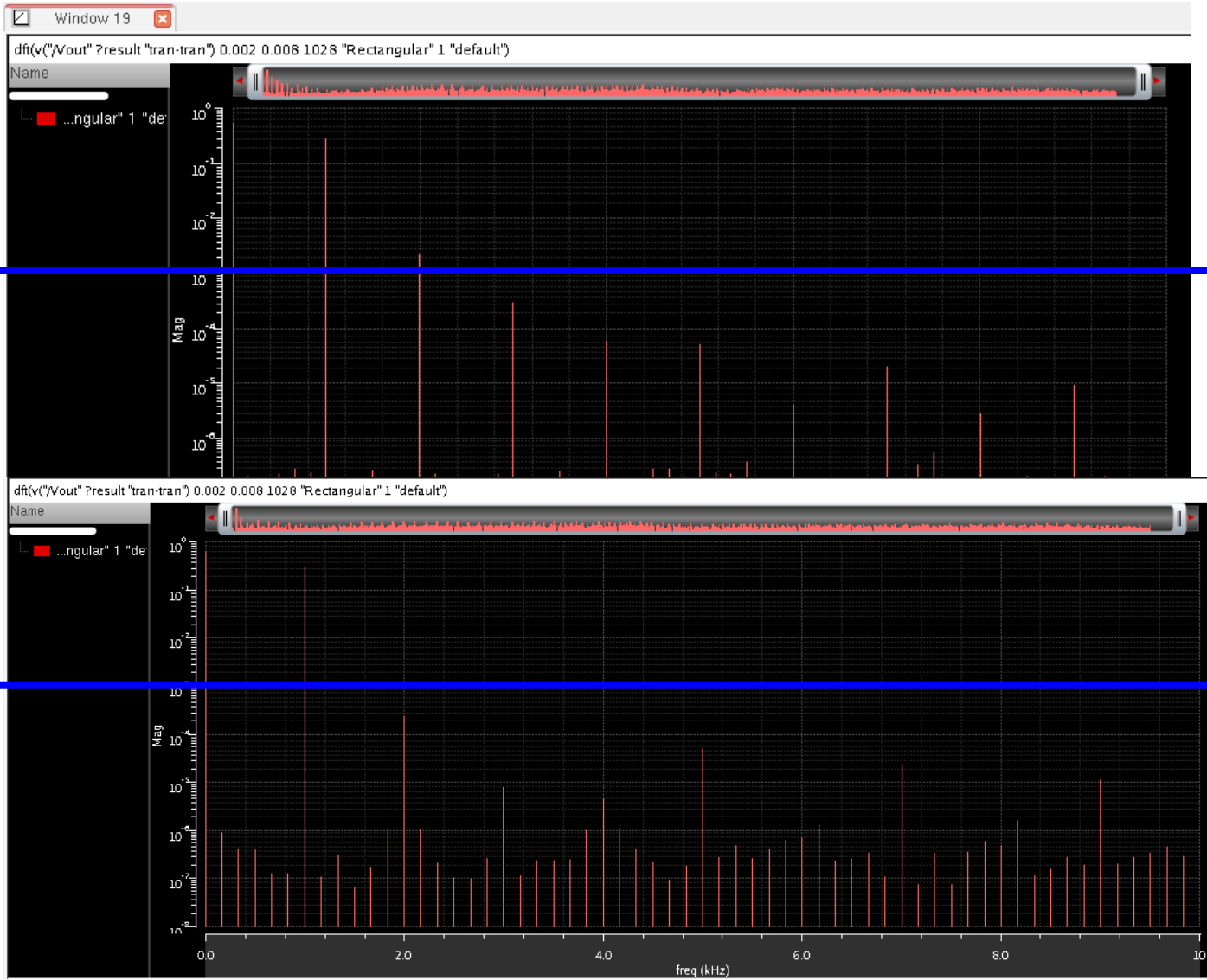
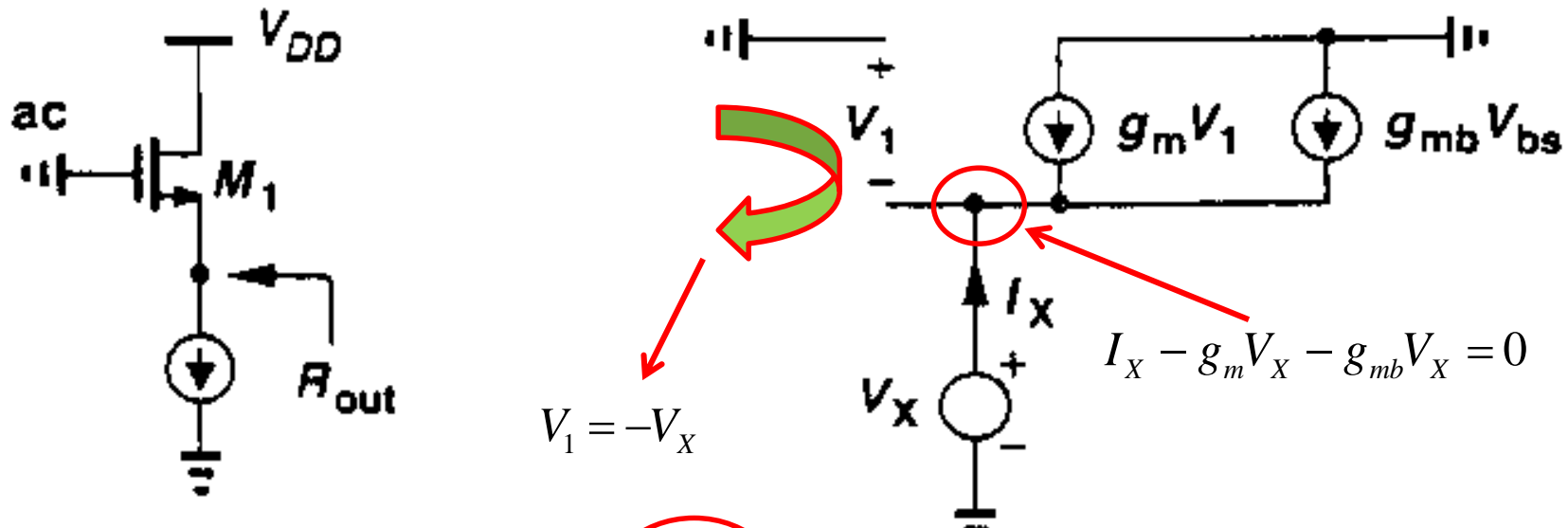
## CD Amplifier (Source Follower) – contd.

- Let us look into the small-signal output resistance:



$$R_{out} = \frac{1}{g_m + g_{mb}}$$

Body effect reduces the output impedance

- If channel length modulation is taken into account then:


$$\therefore R_{out} = \frac{1}{g_m + g_{mb}} \parallel r_o$$

Further Reduction in output impedance


## CD Amplifier (Source Follower) – contd.

- High input impedance and low output impedance with near unity gain enables CD stage to work as buffer (not always!) → useful for CS stage specially when the load impedance is raised very high to enhance the gain
- Reduced output voltage swing when used as buffer for a CS stage
- CD topology is nonlinear → due to body effect and channel length modulation → also the gain is dependent on  $g_m$
- CD topology generates substantial noise → hence not suitable for low noise applications (beyond this course!!)

## Comparison of CD and CS Stages

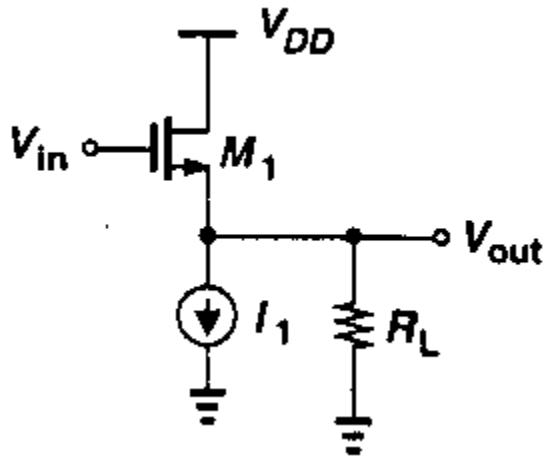

$$A_v |_{CD} \approx \frac{R_L}{R_L + \frac{1}{g_{m1}}}$$


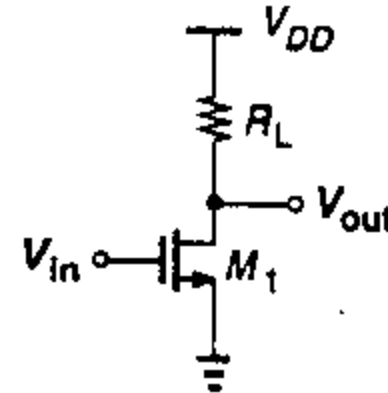


$$A_v |_{CS} \approx -g_{m1} R_L$$

- CD is non-inverting whereas CS is inverting
- CS provides higher gain
- For example, if  $1/g_{m1} = R_L$  then the gain provided by the CS stage equals 1 whereas the output of CD stage is 0.5 of the input



## Common Gate (CG) Amplifier

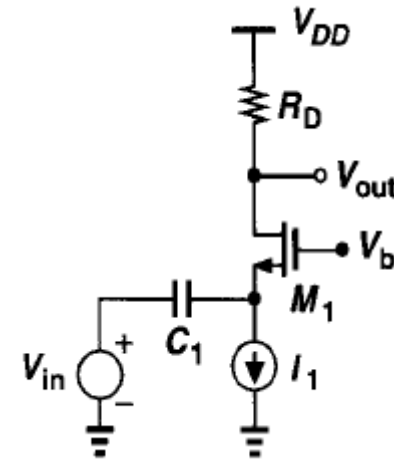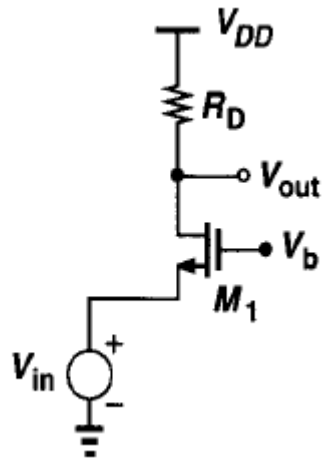

- CG Amplifier- Input is applied at the Source and the output is sensed at the Drain. The Gate terminal is used for establishing appropriate bias conditions for the transistor.
- Its characteristic can be studied through large-signal behavior as well.
- For large  $V_{in}$  i.e. for  $V_{in} > V_b - V_T$ :  $M_1$  is off and therefore:  $V_{out} = V_{DD}$
- For lower  $V_{in}$ : 
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T)^2$$

## Common Gate (CG) Amplifier (contd.)



- For saturated  $M_1$ :  $V_{out} = V_{DD} - I_D R_D = V_{DD} - \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T)^2 \right) R_D$
- Then small signal gain is:  $\frac{\partial V_{out}}{\partial V_{in}} = - \left( \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T) \left( -1 - \frac{\partial V_T}{\partial V_{in}} \right) \right) R_D$
- Since,  $\frac{\partial V_T}{\partial V_{in}} = \frac{\partial V_T}{\partial V_{SB}} = \eta$ :  $\frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T) (1 + \eta) R_D$

$$A_v = g_m (1 + \eta) R_D$$

Non-inverting Amplifier

Higher as compared to CS gain

## Common Gate (CG) Amplifier (contd.)

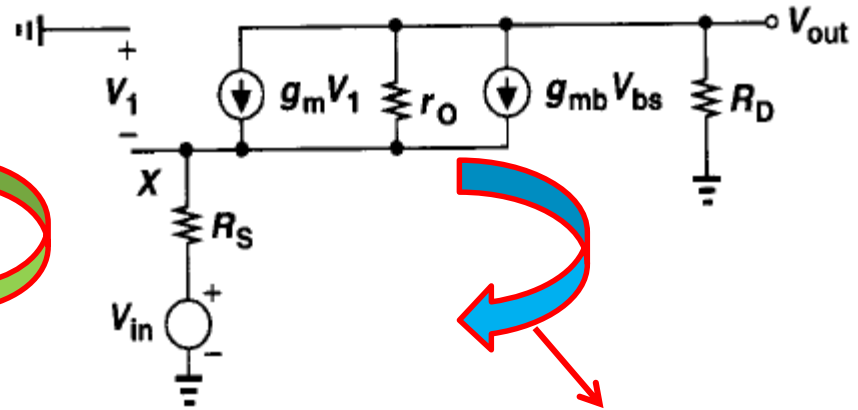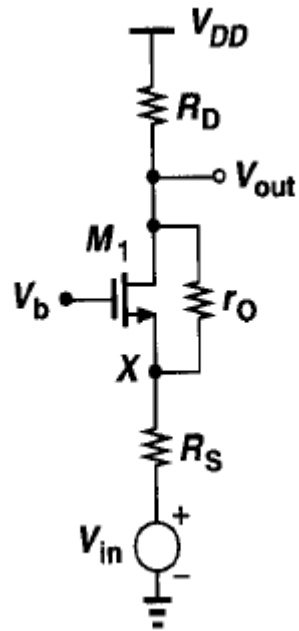

**KVL in loop-1:**

$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$$

**KVL in loop-2:**

$$V_{out} = r_o \left( \frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in}$$

- Simplification gives:** 
$$\frac{V_{out}}{V_{in}} = A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} R_D$$

## CG Amplifier (contd.)

$$\frac{V_{out}}{V_{in}} = A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} R_D$$

**Non-inverting with slightly higher value as compared to the CS stage → body effect is useful in this scenario**


- If the resistor  $R_D$  is replaced by a current source then:

$$\frac{V_{out}}{V_{in}} = A_v = (g_m + g_{mb})r_o + 1$$

$R_D \rightarrow \infty$  for an ideal current source

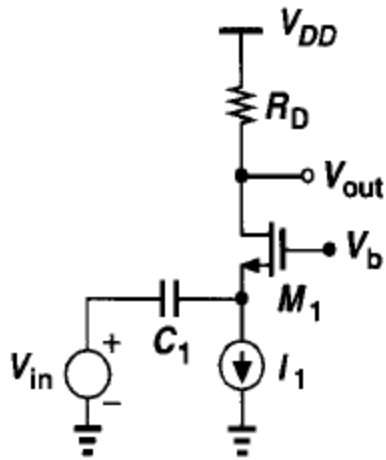
## CG Amplifier (contd.)

- Let us look at small-signal model – without channel length modulation and biased with a constant current source



KVL in  
loop-1

$$v_1 + v_{in} = 0$$

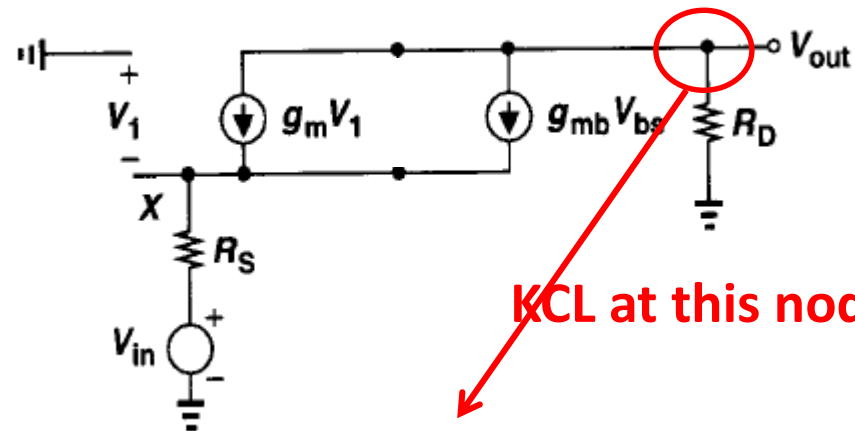


KCL at this node

$$(g_m + g_{mb})V_1 + \frac{V_{out}}{R_D} = 0$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = (g_m + g_{mb})R_D = g_m(1 + \eta)R_D$$

## CG Amplifier (contd.)

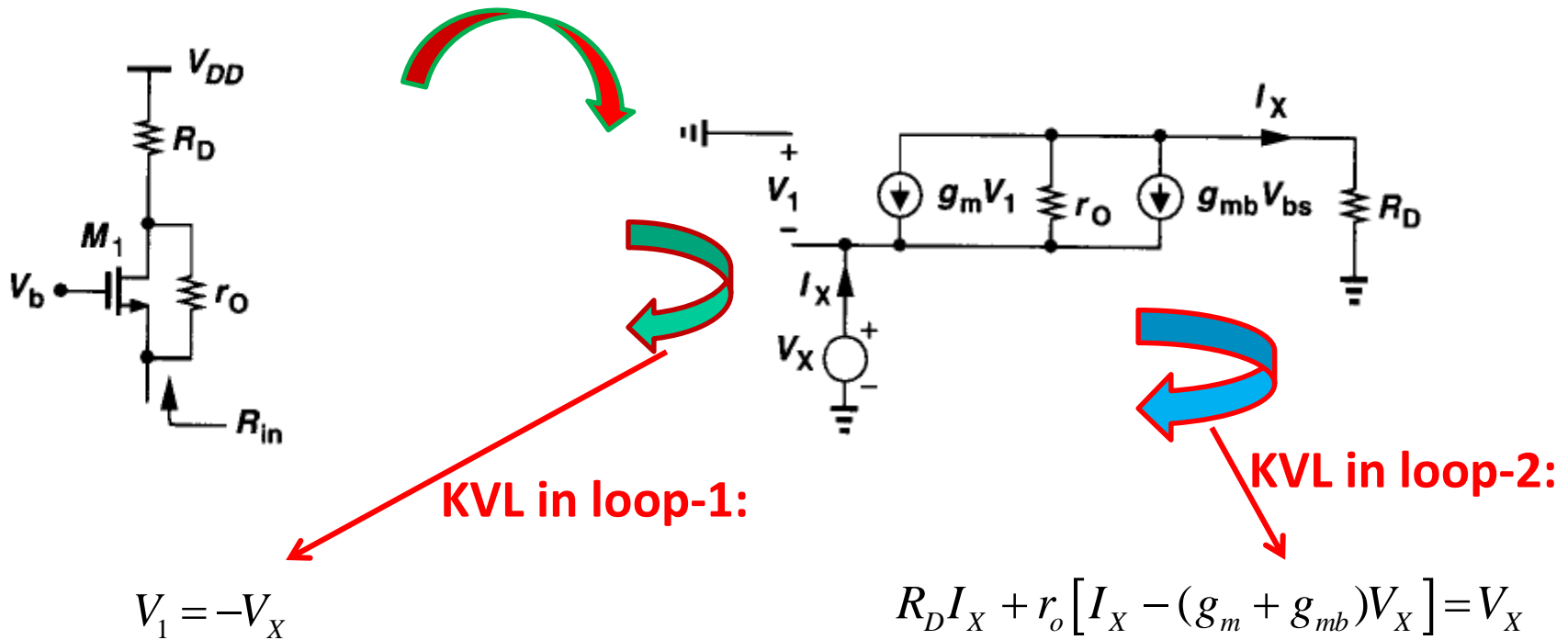

- Input Impedance



$$R_{in} = \frac{V_X}{I_X} = \frac{R_D + r_o}{1 + (g_m + g_{mb}) r_o} \approx \frac{R_D}{(g_m + g_{mb}) r_o} + \frac{1}{(g_m + g_{mb})}$$

## CG Amplifier (contd.)


$$R_{in} = \frac{V_X}{I_X} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \approx \frac{R_D}{(g_m + g_{mb})r_o} + \frac{1}{(g_m + g_{mb})}$$

- **Case-I:**  $R_D = 0$    $R_{in} = \frac{V_X}{I_X} = \frac{r_o}{1 + (g_m + g_{mb})r_o}$
- **Case-II:**  $R_D$  is an ideal current source ie,  $R_D \rightarrow \infty$    $R_{in} \rightarrow \infty$

It is apparent that the input impedance of common-gate stage is low only if the load impedance connected to the drain is low

## CG Amplifier (contd.)

- Output Impedance

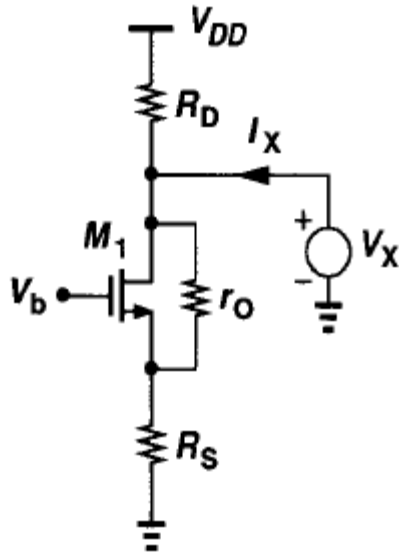


$$R_{out} = \left\{ \left[ 1 + (g_m + g_{mb})r_o \right] R_S + r_o \right\} \parallel R_D$$



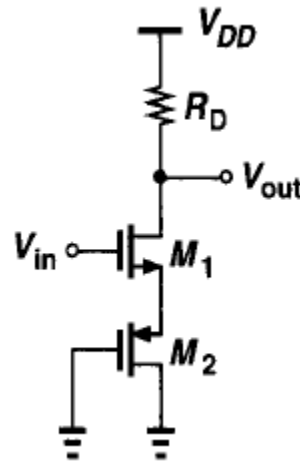
## Example – 1

- Derive the small-signal voltage gain expression for the following amplifier. Consider the cases when channel length modulation are absent and present.


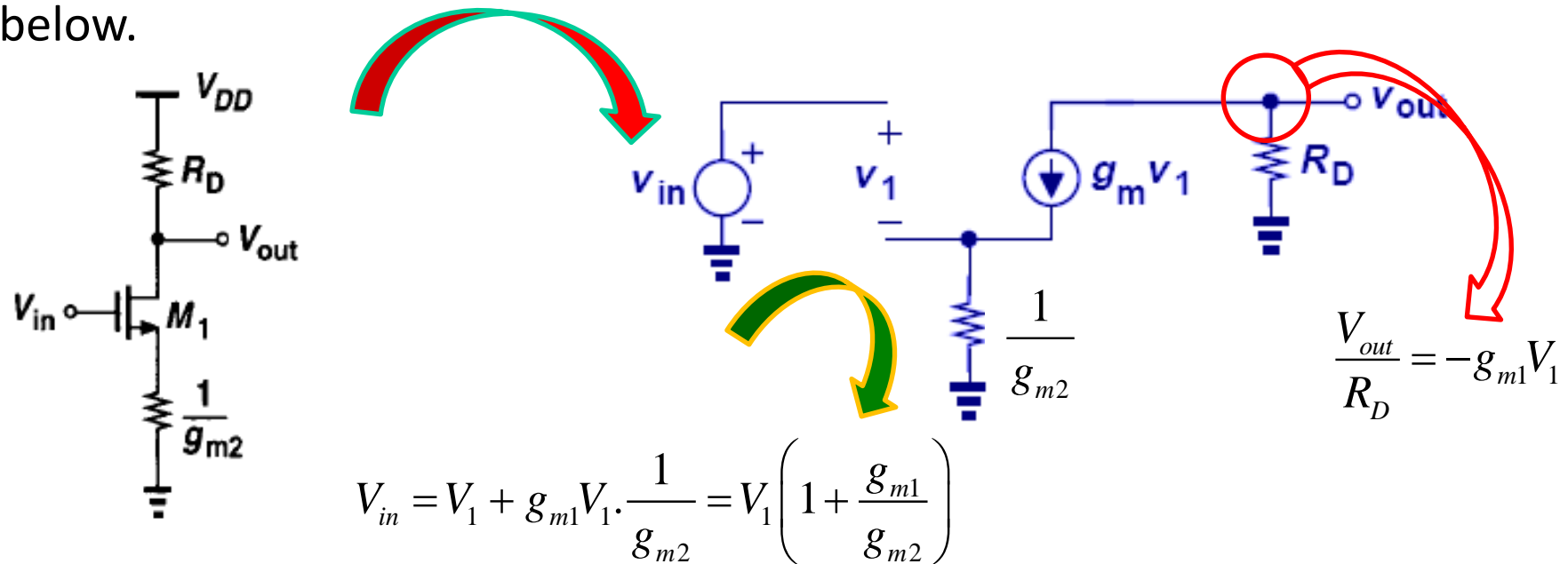
## Example – 1 (contd.)

- **Case-I:**  $\lambda = 0$  both for  $M_1$  and  $M_2 \rightarrow$  In such a case  $M_2$  presents a degenerating impedance of  $1/g_{m2}$  to a single stage CS amplifier as shown below.




**Simplification gives:**  $V_{out} = -g_{m1} V_1 R_D$

$$\Rightarrow V_{out} = -g_{m1} R_D \cdot \frac{g_{m2} \cdot V_{in}}{g_{m2} + g_{m1}}$$

$$\therefore A_v = -\frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$
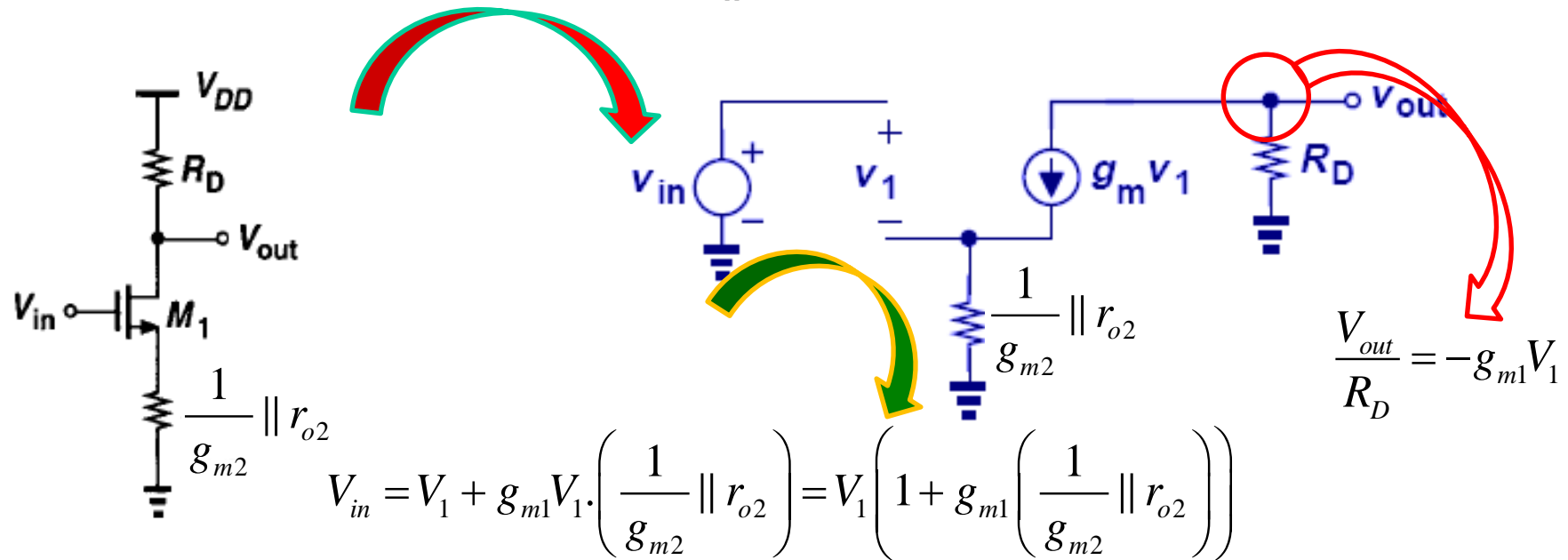
## Example – 1 (contd.)

- **Case-II:**  $\lambda = 0$  for  $M_1$  and  $\lambda \neq 0$  for  $M_2 \rightarrow$  In such a case  $M_2$  presents a degenerating impedance of  $(1/g_{m2} \parallel r_{o2})$  as shown below.




Simplification gives:

$$\therefore A_v = - \frac{R_D}{\frac{1}{g_{m1}} + \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

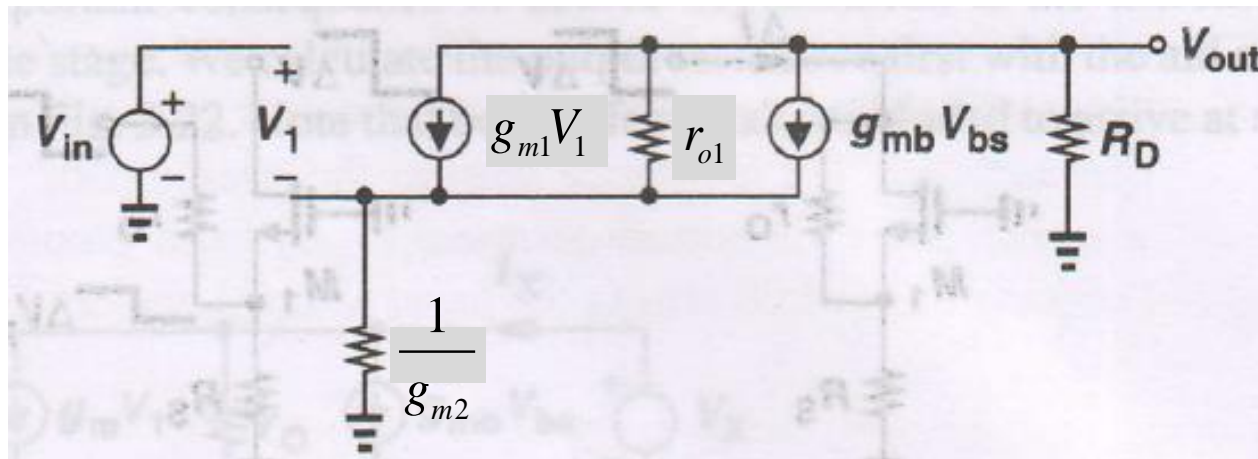
## Example – 1 (contd.)

- **Case-III:**  $\lambda = 0$  for  $M_2$  and  $\lambda \neq 0$  for  $M_1 \rightarrow$  In such a case the small signal model looks like:



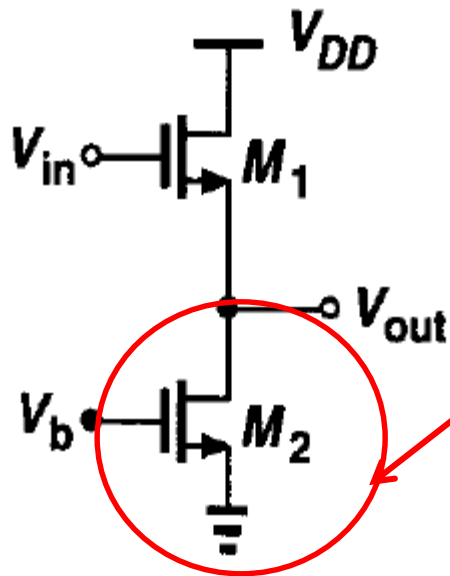
## Example – 2


- Derive expression for the small-signal voltage gain of the following circuit. (Assume:  $\lambda \neq 0$  for both  $M_1$  and  $M_2$ . Neglect body effect)



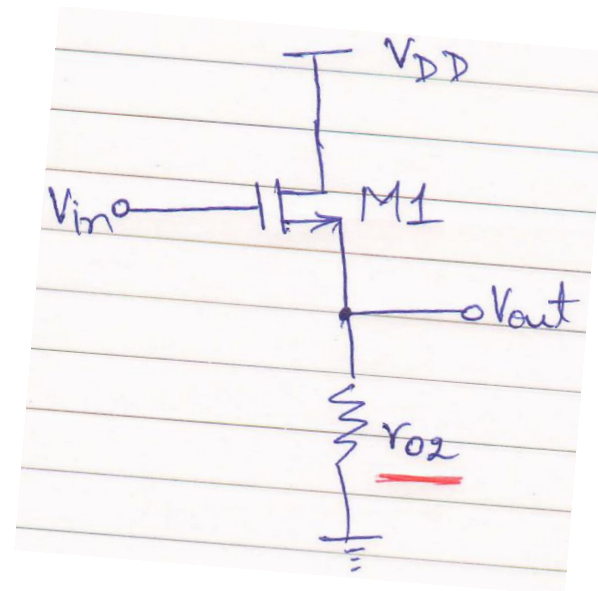**Gate and Source are fixed.**  
 Therefore this NMOS works as  
 a constant current source with  
 an impedance  $r_{o2}$  across its  
 drain and source



## Example – 2 (contd.)

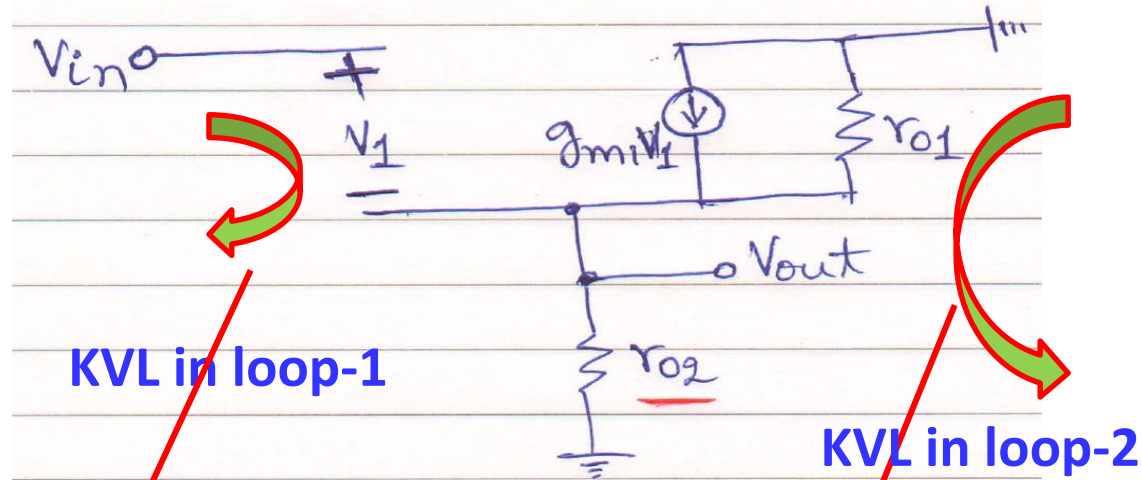

KVL in loop-1

KVL in loop-2

$$V_{in} = V_1 + V_{out}$$


$$g_{m1}V_1(r_{o1} \parallel r_{o2}) = V_{out}$$

$$g_{m1}(V_{in} - V_{out})(r_{o1} \parallel r_{o2}) = V_{out}$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = \frac{(r_{o1} \parallel r_{o2})}{\left[ \frac{1}{g_{m1}} + (r_{o1} \parallel r_{o2}) \right]}$$

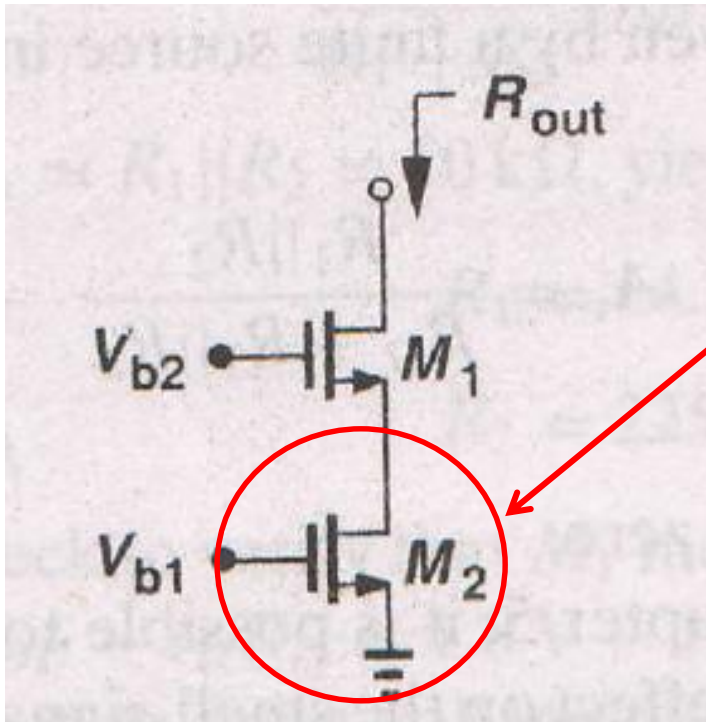
## Example – 3

- What is  $R_{out}$  in the following circuit. (Assume:  $\lambda \neq 0$  for both  $M_1$  and  $M_2$  and both are in saturation.)



**Gate and Source are fixed.**  
 Therefore this NFET works as  
 a constant current source with  
 an impedance  $r_{o2}$  across its  
 drain and source

## Example – 3 (contd.)

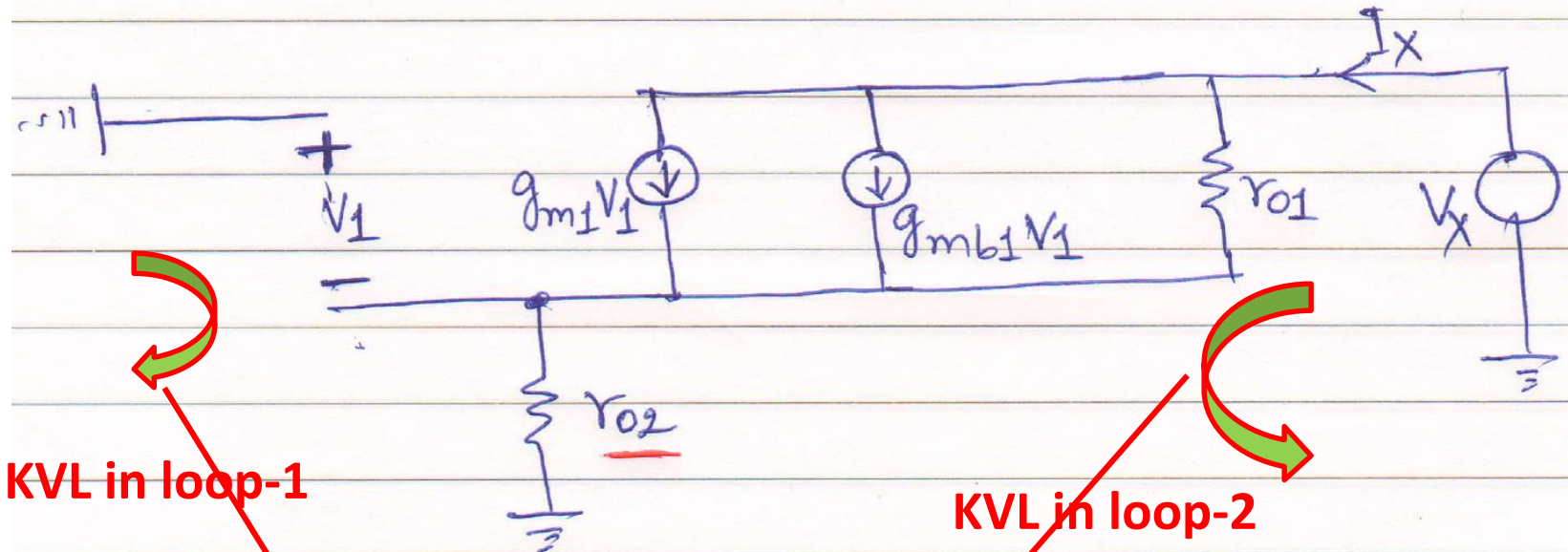

KVL in loop-1

$$V_1 = -I_X r_{o2}$$

KVL in loop-2

$$V_X = I_X r_{o2} + (I_X - g_{m1} V_1 - g_{mb1} V_1) r_{o1}$$

$$\Rightarrow \frac{V_X}{I_X} = r_{o2} + r_{o1} + r_{o1} (g_{m1} r_{o2} + g_{mb1} r_{o2}) = R_{out}$$



## Example – 3 (contd.)

$$R_{out} = r_{o2} + r_{o1} + r_{o1}(g_{m1}r_{o2} + g_{mb1}r_{o2})$$

$$\Rightarrow R_{out} = r_{o2} + r_{o1}[1 + r_{o2}(g_{m1} + g_{mb1})]$$

$$\therefore R_{out} = r_{o1} + r_{o2}[1 + r_{o1}(g_{m1} + g_{mb1})]$$

**However:**  $r_{o1}(g_{m1}r_{o2} + g_{mb1}r_{o2}) \gg r_{o1}$

$$\Rightarrow r_{o1}(g_{m1}r_{o2} + g_{mb1}r_{o2}) \gg r_{o2}$$

$$\therefore R_{out} \approx (g_{m1} + g_{mb1})r_{o1}r_{o2}$$