




Lecture – 9

Date: 03.09.2015

- Biasing in MOS Amplifier Circuits

Biasing using Single Power Supply

 - The general form of a **single-supply** MOSFET amplifier biasing circuit is:



- We typically attempt to satisfy three main bias design goals:

1) Maximize Gain

Typically, the small-signal **voltage gain** of a MOSFET amplifier will be proportional to transconductance g_m .

$$A_v \propto g_m$$

Thus, to maximize the amplifier voltage gain, we must **maximize** the MOSFET transconductance.

Biasing using Single Power Supply (contd.)

Q: What does this have to do with **D.C. biasing**?

A: Recall that the transconductance depends on the **DC excess gate voltage**:

$$g_m = 2K(V_{GS} - V_T)$$

- Another way to consider transconductance is to express it in terms of DC drain current I_D .
- Recall this DC current is related to the DC excess gate voltage (in saturation!) as:

$$I_D = K(V_{GS} - V_T)^2 \quad \Rightarrow \quad (V_{GS} - V_T) = \sqrt{\frac{I_D}{K}}$$

- And so transconductance can be alternatively expressed as:

$$g_m = 2K(V_{GS} - V_T) = 2K\sqrt{\frac{I_D}{K}} = 2\sqrt{KI_D}$$

Biasing using Single Power Supply (contd.)

- Therefore, the amplifier voltage gain is typically **proportional** to the square-root of the DC drain current:

$$A_v \propto \sqrt{I_D}$$

To maximize A_v , maximize I_D

2) Maximize Voltage Swing

Recall that if the DC drain voltage V_D is biased too close to V_{DD} , then even a small **small-signal** drain voltage $v_d(t)$ can result in a **total** drain voltage that is too **large**, i.e.:

$$v_D(t) = V_D + v_d(t) \geq V_{DD}$$

In other words, the MOSFET enters **cutoff**, and the result is a **distorted** signal!

Biasing using Single Power Supply (contd.)

- To avoid this (to allow $v_d(t)$ to be as large as possible without MOSFET entering cutoff), we need to bias our MOSFET such that the DC drain voltage V_D is as **small** as possible.
- Note that the drain voltage is: $V_D = V_{DD} - R_D I_D$
- Therefore V_D is minimized by designing the bias circuit such that the DC drain current I_D is as **large** as possible.
- However, we must **also** consider the signal distortion that occurs when the MOSFET enters **triode**. This of course is avoided if the total drain-to-source voltage remains greater than the excess gate voltage, i.e.:

$$v_{DS}(t) = V_{DS} + v_{ds}(t) > (V_{GS} - V_T)$$

- Thus, to avoid the MOSFET triode mode—and the resulting signal distortion—we need to bias our MOSFET such that the DC voltage is as **large** as possible.

To minimize signal distortion, maximize V_{DS}

Biasing using Single Power Supply (contd.)

3) Minimize Sensitivity to changes in K, V_T

- We find that MOSFETs are **sensitive** to temperature—specifically, the value of K is a function of temperature.
- Likewise, the values of K and V_T are not particularly constant with regard to the manufacturing process.
- Both of these facts lead to the requirement that our bias design be **insensitive** to the values of K and V_T . Specifically, we want to design the bias network such that the DC bias current does **not** change values when K and/or V_T does.
- **Mathematically**, we can express this requirement as minimizing the value: $\frac{dI_D}{dK}$ and $\frac{dI_D}{dV_T}$
- These derivatives can be minimized by maximizing the value of **source resistor R_S** .


Biassing using Single Power Supply (contd.)

- So, let's **recap** what we have learned about designing our bias network:

 1. Make I_D as large as possible.
2. Make V_{DS} as large as possible.
3. Make R_S as large as possible.

Actually these three goals are conflicting, as they are constrained by the KVL equation of the bias circuit.

Biasing using Single Power Supply (contd.)



$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

or

$$I_D R_D + V_{DS} + I_D R_S = V_{DD}$$


Maximize A_v by **maximizing** this term.

Minimize distortion by **maximizing** this term.

Minimize sensitivity by **maximizing** this term.

But the **total** of the three terms must equal this!


Example – 1

 

- If the MOSFET has device values $K = 1.0 \text{ mA/V}^2$ and $V_T = 1.0\text{V}$, determine the resistor values to bias this MOSFET with a DC drain current of $I_D = 4.0\text{mA}$.

The MOSFET Current Mirror

- Consider the following MOSFET circuit:

 

- Note $V_D = V_G$, therefore: $V_{DS} = V_{GS}$
- and thus: $V_{DS} = V_{GS}$
- The MOSFET is in saturation if $V_G > V_T$.**
- We know that for a MOSFET in saturation, the drain current is:

$$I_D = K (V_{GS} - V_T)^2$$

Say we want this current I_D to be a **specific** value—call it I_{ref} .

- Since $V_S = 0$, we find that from the above equation, the drain voltage must be:

$$V_D = \sqrt{\frac{I_{ref}}{K}} + V_T$$

The MOSFET Current Mirror (contd.)

- Likewise, from KVL we find that:

$$I_{ref} = \frac{V_{DD} - V_D}{R}$$


- And thus the **resistor** value to achieve the desired drain current I_{ref} is:

$$R = \frac{V_{DD} - V_D}{I_{ref}}$$

where: $V_D = \sqrt{\frac{I_{ref}}{K}} + V_T$

Q: Why are we doing this?

 A: Say we now add another component to the circuit, with a second MOSFET that is **identical** to the first :



The MOSFET Current Mirror (contd.)

Q: So what is current I_L ?

A: Note that the gate voltage of each MOSFET is the **same** (i.e., $V_{GS1} = V_{GS2}$), and if the MOSFETS are the **same** (i.e., $K_1 = K_2, V_{T1} = V_{T2}$), and if the second MOSFET is likewise in **saturation**.

- The drain current I_L is:

$$I_L = K_2 (V_{GS2} - V_{T2})^2$$

$$= K_1 (V_{GS1} - V_{T1})^2 = I_{ref}$$

Therefore, the drain current of the **second** MOSFET is **equal** to the current of the **first**!




$$I_{ref} = I_L$$

Q: Wait a minute! You mean to say that the current through the resistor R_L is **independent** of the value of resistor R_L ?


A: Absolutely! As long as the second MOSFET is in **saturation**, the current through R_L is equal to I_{ref} —**period**.

The MOSFET Current Mirror (contd.)

 - The current through R_L is independent of the value of R_L (provided that the MOSFET remains in saturation). Think about what this means—this device is a **current source** !



The MOSFET Current Mirror (contd.)

 

- Remember, the second MOSFET **must** be in saturation for the current through R_L to be a constant value I_{ref} . As a result, we find that:

$$V_{DS2} > V_{GS2} - V_{T2}$$


- For this example: $V_{D2} > V_{G2} - V_{T2}$

- Since $V_{D2} = V_{DD} - R_L I_{ref}$, we find that the MOSFET will be in saturation if: $V_{DD} - R_L I_{ref} > V_{G2} - V_{T2} = V_{G1} - V_{T1}$

- Alternatively, we find the limitation on the load resistor R_L :

$$V_{DS2} > V_{GS2} - V_{T2}$$

The MOSFET Current Mirror (contd.)

 

$$R_L < \frac{V_{DD} - V_{G1} + V_{T1}}{I_{ref}}$$


- We know that: $V_{G1} = V_{DD} - R I_{ref}$
- Thus we can alternatively write the above equation as:

$$R_L < R + \frac{V_{T1}}{I_{ref}}$$

- If the **load** resistor becomes **larger** than $R + \frac{V_{T1}}{I_{ref}}$, the voltage V_{DS2} will drop **below** the excess gate voltage $V_{GS2} - V_{T2}$, and thus the second MOSFET will enter the **triode** region. As a result, the drain current will **not** equal I_{ref} —the current source will **stop working!**
- Although the circuit presented here is sometimes referred to as a current **sink**, understand that the circuit is clearly a way of designing a **current source**.


The MOSFET Current Mirror (contd.)

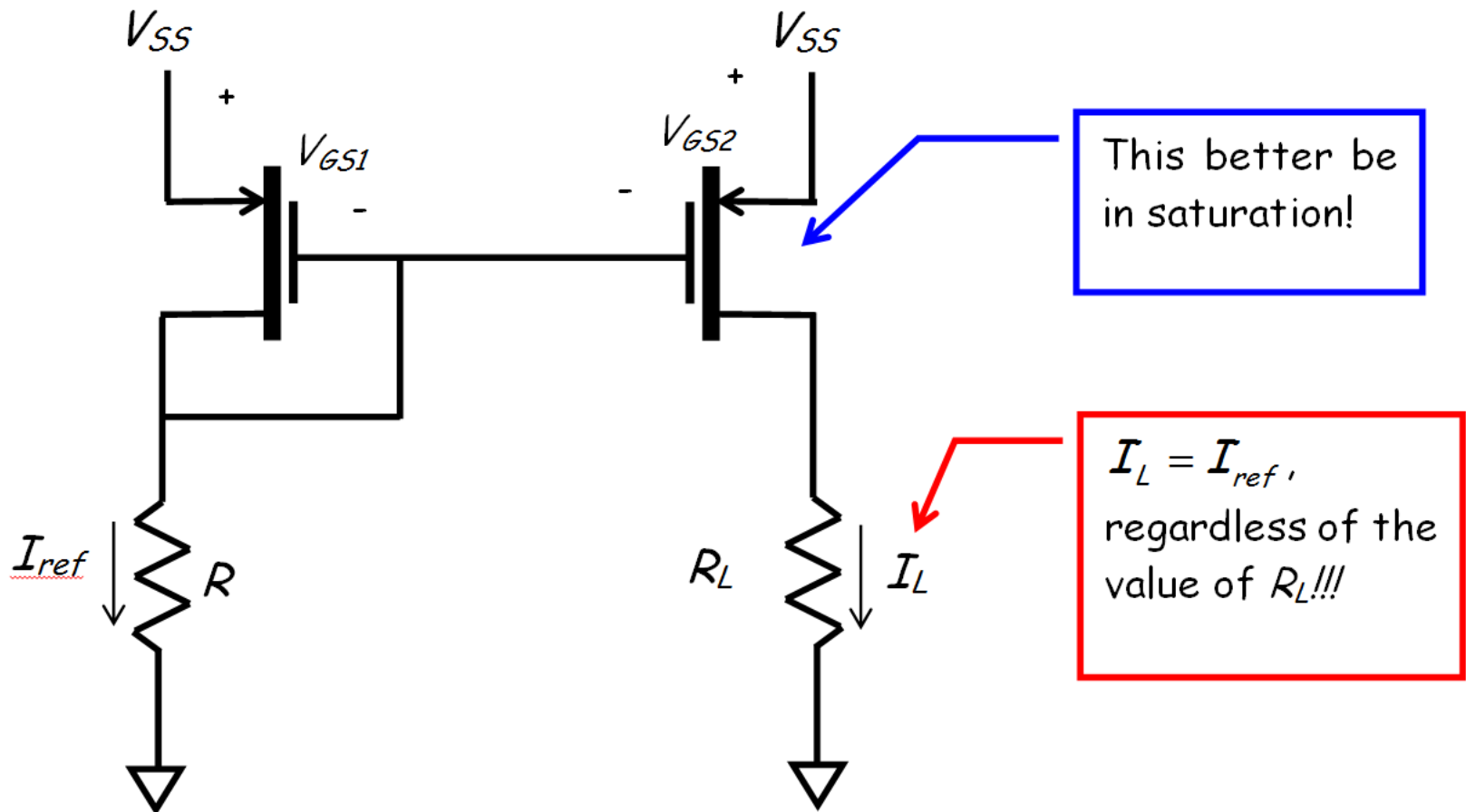- We can also use **PMOS** devices to construct a current mirror!



MOSFET Biasing using Current Mirror

 - We can bias a MOSFET amplifier using a **current source** as:




It is evident that the DC drain current I_D , is equal to the current source I , **regardless** of the MOSFET values K or V_T !

Thus, this bias design maximizes drain current **stability**!

MOSFET Biasing using Current Mirror (contd.)

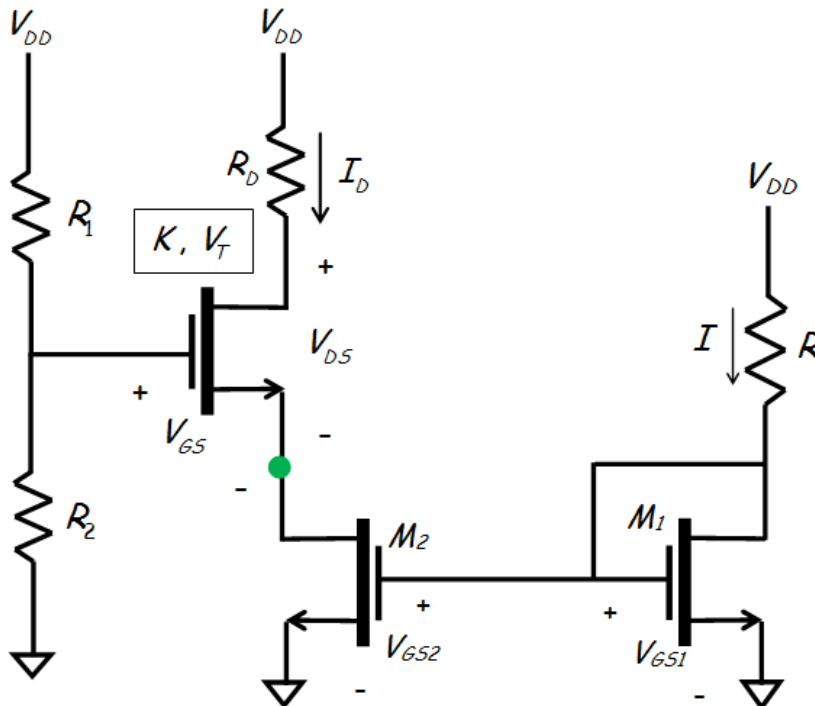- We now know how to implement this bias design with MOSFETs—we use the **current mirror** to construct the current source!



- Since $I_D = I$, it is evident that V_{GS} **must** be equal to:

$$V_{GS} = \sqrt{\frac{I}{K}} + V_T$$

- Since the DC **gate** voltage is:

$$V_G = V_{DD} \left(\frac{R_2}{R_1 + R_2} \right)$$

- Therefore:

$$\begin{aligned} V_S &= V_G - V_{GS} \\ &= V_{DD} \left(\frac{R_2}{R_1 + R_2} \right) - \left(\sqrt{\frac{I}{K}} + V_T \right) \end{aligned}$$

MOSFET Biasing using Current Mirror (contd.)

- Since we are biasing with a current source, we do **not** need to worry about drain current **stability**—the current source will determine the DC drain current for **all** conditions (i.e., $I_D = I$).
- We might conclude, therefore, that we should make DC source voltage V_S as **small** as possible. After all, this would allow us to **maximize** the output voltage swing (i.e., maximize $I_D R_D$ and V_{DS}).
- Note however, that the **source** voltage V_S of the MOSFET is numerically equal to the **drain** voltage V_{D2} (and thus V_{DS2}) of the second MOSFET of the **current mirror**.

Q: So what?!


A: The voltage must be **greater** than:

$$\begin{aligned} V_{GS2} - V_{T2} &= V_{GS1} - V_{T1} \\ &= (V_{DD} - I_{ref} R) - V_{T1} \end{aligned}$$

in order for the **second** MOSFET to remain in **saturation**.

MOSFET Biasing using Current Mirror (contd.)

 There is a **minimum voltage** across the current source in order for the current source to properly operate!



- Thus, to maximize output swing, we **might** wish to set:

$$V_S = V_{GS1} - V_{T1}$$

(although to be practical, we should make V_S **slightly greater** than this to allow for some design **margin**).

Q: How do we “set” the DC **source** voltage V_S ??

A: By setting the DC **gate** voltage V_G !!

MOSFET Biasing using Current Mirror (contd.)

- Recall that the DC voltage V_{GS} is determined by the DC current source value I :

$$V_{GS} = \sqrt{\frac{I}{K}} + V_T$$

- and the DC gate voltage is determined by the **two** resistors R_1 and R_2 :

$$V_G = V_{DD} \left(\frac{R_2}{R_1 + R_2} \right)$$

- Thus, we should **select** these resistors such that:

$$\begin{aligned} V_G &= V_{GS} + V_S \\ &= \left(\sqrt{\frac{I}{K}} + V_T \right) + (V_{GS1} - V_{T1}) \end{aligned}$$

Q: So what should the value of resistor R_D be?

A: Recall that we should set the DC **drain** voltage V_D :

- much **less** than V_{DD} to avoid **cutoff**.
- much **greater** than $V_G - V_T$ to avoid **triode**.

MOSFET Biasing using Current Mirror (contd.)

- Thus, we **compromise** by setting the DC drain voltage to a point **halfway** in between!


$$V_D = \frac{V_{DD} + (V_G - V_T)}{2}$$

- To achieve this, we must select the drain **resistor** R_D so that:

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{V_{DD} - (V_G - V_T)}{I_D}$$

 Example – 2

Let's determine the proper resistor values to DC bias this MOSFET. The current source is 5.0 mA and has a minimum voltage of 2.0 Volts in order to operate properly



- Since $I = I_D = 5 \text{ mA}$, we know that the value of V_{GS} should be:

$$\begin{aligned}
 V_{GS} &= \sqrt{\frac{I}{K}} + V_T \\
 &= \sqrt{\frac{5.0}{0.2}} + 1.0 \\
 &= 6.0 \text{ V}
 \end{aligned}$$

- Assuming that we want the DC source voltage to be the minimum value of $V_S = 2.0 \text{ V}$, we need for the DC gate voltage to be:

$$\begin{aligned}
 V_G &= V_{GS} + V_S \\
 &= 6.0 + 2.0 \\
 &= 8.0 \text{ V}
 \end{aligned}$$

Example – 2 (contd.)

- Thus, we need to select resistors R_1 and R_2 so that: $V_G = 8.0 = V_{DD} \left(\frac{R_2}{R_1 + R_2} \right)$
- or in other words, we want: $\left(\frac{R_2}{R_1 + R_2} \right) = \frac{8.0}{15.0}$
- Since we can make R_1 and R_2 large, let's assume that we want: $R_1 + R_2 = 300K$

So that $R_1 = 140 k\Omega$ and $R_2 = 160 k\Omega$.

- Finally, we want the DC drain voltage to be: $V_D = \frac{V_{DD} + (V_G - V_T)}{2}$
 $= \frac{15.0 + (8.0 - 1.0)}{2}$
 $= 11.0 V$
- So that the resistor is: $R_D = \frac{V_{DD} - V_D}{I_D}$
 $= \frac{15.0 - 11.0}{5.0}$
 $= 0.8 K\Omega$

Example – 2 (contd.)

