

Solution Test - 1

Here we assume that both the current and voltage have both a **DC** and **small-signal** component:

$$i = I_{DC} + i_{ss} \quad \text{and} \quad v = V_{DC} + v_{ss}$$

Now, since the DC voltage across the device is $V_{DC} = 3.0$, we get:

$$i = I_{DC} + i_{ss} \quad \text{and} \quad v = 3.0 + v_{ss}$$

In other words, the device voltage v is always **very close** to 3.0 volts!

Applying a **Taylor's series** expansion around $V_{DC} = 3.0$, we find:

$$\begin{aligned} i &\cong (4v + v^2) \Big|_{v=3} + \frac{\partial(4v + v^2)}{\partial v} \Big|_{v=3} v_{ss} \\ &= (4(3) + 3^2) + (4 + 2v) \Big|_{v=3} v_{ss} \\ &= 21 + (4 + (2)3)v_{ss} \\ &= 21 + 10v_{ss} \end{aligned}$$

Since $i = I_{DC} + i_{ss}$, we can equate terms (DC and small-signal) and conclude:

$$I_{DC} = 21 \text{ mA} \quad \text{and} \quad i_{ss} = 10 v_{ss} \text{ mA}$$

a) Thus, the **small-signal** resistance r_{ss} of this device is:

$$r_{ss} = \frac{v_{ss}}{i_{ss}} = \frac{v_{ss}}{10v_{ss}} = \frac{1}{10} = 0.1K = \underline{\underline{100\Omega}}$$

b) If:

$$i_{ss}(t) = 0.2 \cos \omega t \text{ mA}$$

Then:

$$v_{ss}(t) = r_{ss} i_{ss}(t) = (0.1) 0.2 \cos \omega t = \underline{\underline{0.02 \cos \omega t \text{ V}}}$$