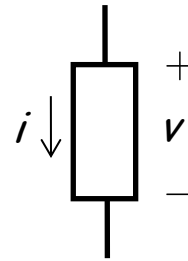


Class Test – 1
Date: 17.08.2015
Time: 20 minutes

A **strange**, two-terminal device has the following relationship between the current through it (i) and the voltage across it (v):

$$i = 4v + v^2$$

where v is in **volts** and i in **mA**.



We can define the **small-signal resistance** r_{ss} of this device as:

$$r_{ss} = \frac{V_{ss}}{i_{ss}}$$

where V_{ss} is the **small-signal voltage** across the device and i_{ss} is the **small-signal current** through it.

- a) Determine the **value** of this small-signal resistance r_{ss} if the **DC voltage** across the device is $V = 3.0 \text{ V}$
- b) Determine the **small-signal voltage** $v_{ss}(t)$ across this device if the **DC voltage** across it is 3.0 V, and the **small-signal current** i_{ss} through it is:

$$i_{ss}(t) = 0.2 \cos \omega t \text{ mA}$$