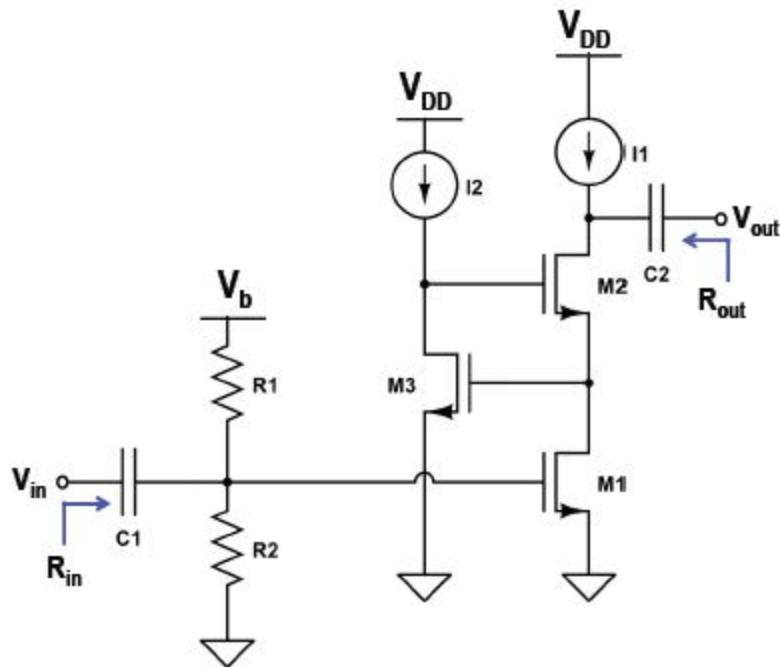


# Home Assignment #3

Deadline : 15/09/2016

1. Design an amplifier of **gain >6dB**.  
(Do any one design on ELDO and two on Cadence)
  - a) Using Current source as load
  - b) Using Current Mirror Application
  - c) Using Diode Connected Load
2. Consider the following questions using the parameter value listed below. Assume all MOSFET share the same parameters except for the one specified. Ignore body-effect. Provide expressions for the input resistance  $R_{in}$ , output resistance  $R_{out}$ , and gain  $v_{out}/v_{in}$  for the amplifier in Fig. 1. Assume  $V_b$  biases all the transistors properly in saturation region. (Only theoretical Analysis needed )



## Parameters :

$L=0.8 \text{ um}$   
 $M_1 (W) = 16 \text{ um}$   
 $M_2(W) = 8 \text{ um}$   
 $M_3(W) = 8 \text{ um}$   
 $t_{ox}=60e-10 \text{ m}$   
 $V_{th}=0.6 \text{ Volt}$   
 Mobility of electrons =  $1400 \text{ cm}^2/\text{v.s}$

$R_1=10K$   
 $R_2=20K$   
 $I_1=1\text{mA}$   
 $I_2=0.1 \text{ mA}$   
 $V_{dd}=3.3 \text{ V}$   
 Oxide Relative Permittivity = 3.9  
 $\lambda=0.2/\text{volt}$