



Lecture – 3

Date: 08.08.2016

- Steps for DC Analysis of MOSFET Circuits
- MOSFET as a Switch and Amplifier

DC Analysis of MOSFET Circuits

- To analyze MOSFET circuit with D.C. sources, we **must** follow these **five steps**:
 1. **ASSUME** an operating mode
 2. **ENFORCE** the equality conditions of that mode.
 3. **ANALYZE** the circuit with the enforced conditions.
 4. **CHECK** the inequality conditions of the mode for consistency with original assumption. If consistent, the analysis is complete; if inconsistent, go to step 5.
 5. **MODIFY** your original assumption and repeat all steps

1. ASSUME

Here we have **three** choices—cutoff, triode, or saturation. You can make an “**educated guess**” here, but remember, until you CHECK, it’s just a guess!

2. ENFORCE

For all three operating regions, we must ENFORCE just **one equality**.

- **Cutoff:** Since **no** channel is induced, we **ENFORCE:** $I_D = 0$
- **Triode:** Since the conducting channel **is** induced but **not** in pinch-off, we **ENFORCE:**

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[2(V_{GS} - V_T) V_{DS} - V_{DS}^2 \right]$$
- **Saturation:** Since the conducting channel **is** induced but **is** in pinch-off, we **ENFORCE:**

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$

3. ANALYZE

The task in D.C. analysis of a MOSFET circuit is to find **one current** and **two voltages!**

- The gate current I_G is zero ($I_G = 0$) for MOSFETS in all modes, we need **only** to find the **drain current** I_D - this current value must be **positive** (or zero).
- We also need to find **two** of the three **voltages** associated with the MOSFET. Typically, these two voltages are V_{GS} and V_{DS} , but given any two voltages, we can find the third using KVL:

$$V_{DS} = V_{DG} + V_{GS}$$

Some hints for MOSFET DC analysis:

1. Gate current $I_G = 0$ **always** !!!
2. Equations sometimes have **two** solutions! Choose solution that is **consistent** with the original ASSUMPTION.

4. CHECK

You do not know if your D.C. analysis is correct unless you CHECK to see if it is consistent with your original assumption!

Q: What exactly do we CHECK?

A: We ENFORCED the mode **equalities**, we CHECK the mode **inequalities**.

We must CHECK **two** separate inequalities after analyzing a MOSFET circuit. Essentially, we check if we have/have not induced a conducting channel, and then we check if we have/have not pinched-off the channel (if it is conducting).

Cutoff

We must only CHECK to see if the MOSFET has a **conducting channel**. If **not**, the MOSFET is indeed in **cutoff**. We therefore CHECK to see if:

$$V_{GS} < V_T \quad (\text{NMOS})$$

$$V_{GS} > V_T \quad (\text{PMOS})$$

Triode

- Here we must first CHECK to see **if** a channel has been induced:

$$V_{GS} > V_T \quad (\text{NMOS}) \qquad V_{GS} < V_T \quad (\text{PMOS})$$

- Likewise, we must CHECK to see if the channel has reached **pinch off**. If **not**, the MOSFET is indeed in the **triode** region. We therefore CHECK to see if:

$$V_{DS} < V_{GS} - V_T \quad (\text{NMOS}) \qquad V_{DS} > V_{GS} - V_T \quad (\text{PMOS})$$

Saturation

- Here we must first CHECK to see **if** a channel has been induced:

$$V_{GS} > V_T \quad (\text{NMOS}) \qquad V_{GS} < V_T \quad (\text{PMOS})$$

- Likewise, we must CHECK to see if the channel has reached **pinch off**. If it **has**, the MOSFET is indeed in the **saturation** region and we need to CHECK:


$$V_{DS} > V_{GS} - V_T \quad (\text{NMOS}) \qquad V_{DS} < V_{GS} - V_T \quad (\text{PMOS})$$

- If the results of our analysis are consistent with **each** of these inequalities, then we have made the **correct** assumption! The **numeric** results of our analysis are then likewise **correct**. We can **stop** working!
- However, if **even one** of the results of our analysis is **inconsistent** with our ASSUMPTION, then we have made the **wrong** assumption → move to step 5.

5. MODIFY

- If **one or more** of the circuit MOSFETs are **not** in their ASSUMED mode, we must change our assumptions and start **completely** over!
- In general, **all** of the results of our previous analysis are incorrect, and thus must be **completely** scraped!

Example – 1

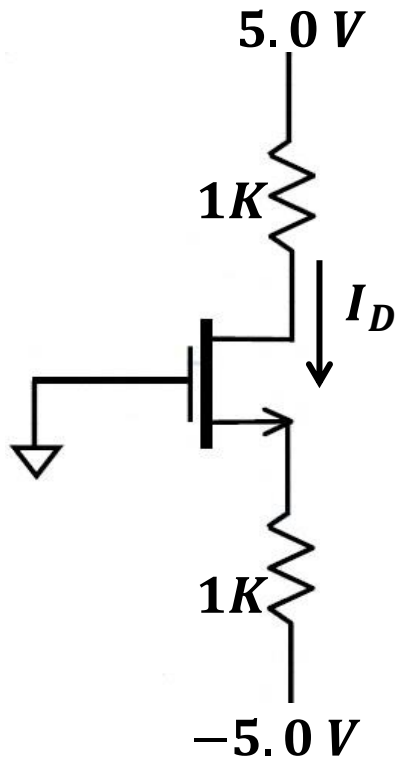

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) = K = 0.4 \text{ mA/V}^2 \quad V_T = 2.0 \text{ V}$$


ASSUME: the NMOS device is in saturation.

- Thus, we must **ENFORCE** the condition that:
$$I_D = K (V_{GS} - V_T)^2$$
- Now we must **ANALYZE** the circuit.

Q: What now? How do we proceed with this analysis?

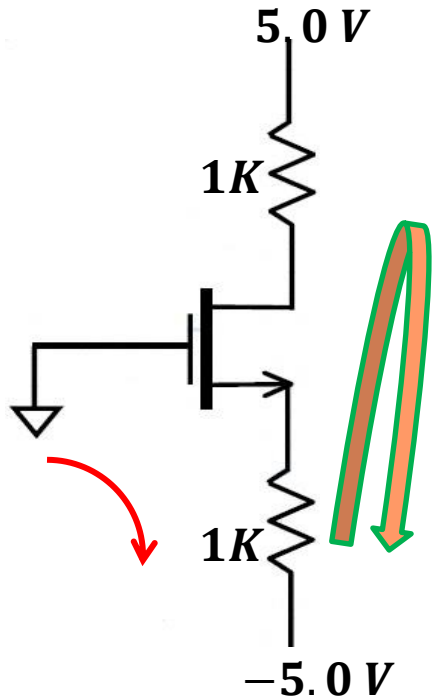Example – 1 (contd.)

A: It's certainly not clear. Let's write the circuit equations and see what happens.



- **From the Gate-Source loop KVL:** $0 - V_{GS} - 1 \times 10^3(I_D) = -5.0$
- **Therefore, rearranging:** $I_D = (5.0 - V_{GS})/10^3$
- **And from the Drain-Source loop KVL:** $5 - 1 \times 10^3(I_D) - V_{DS} - 1 \times 10^3(I_D) = -5.0$
- **Therefore, rearranging:** $V_{DS} = 10.0 - 2 \times 10^3(I_D)$

$$I_D = (5.0 - V_{GS})/10^3 = K(V_{GS} - V_T)^2$$

$$0.4mA/V^2 [V_{GS} - 2]^2 = \frac{5 - V_{GS}}{10^3}$$

$$V_{GS} = 3.76V$$

$$V_{GS} = -2.26V$$

Example – 1 (contd.)

- We **assumed** saturation. If the NMOS is in saturation, we know that:

$$V_{GS} > V_T = 2.0V$$

$$\therefore V_{GS} = 3.76V$$

- Inserting this voltage into the Gate-Source KVL equation, we find that the drain current is:

$$I_D = (5.0 - 3.76)/10^3$$

$$\therefore I_D = 1.24 \text{ mA}$$

- And using the Drain-Source KVL, we find the remaining voltage:

$$V_{DS} = 10.0 - 2 \times 10^3 \times 1.24 \times 10^{-3}$$

$$\therefore V_{DS} = 7.52 V$$


- Even though we have answers (one current and two voltages), we still are not finished, as we now must **CHECK** our solution to see if it is consistent with the saturation mode inequalities.

$$3.76 = V_{GS} > V_T = 2.0$$

$$7.52 = V_{DS} > V_{GS} - V_T = 1.76$$

Both answers are consistent! Our solutions are correct!

Example – 2

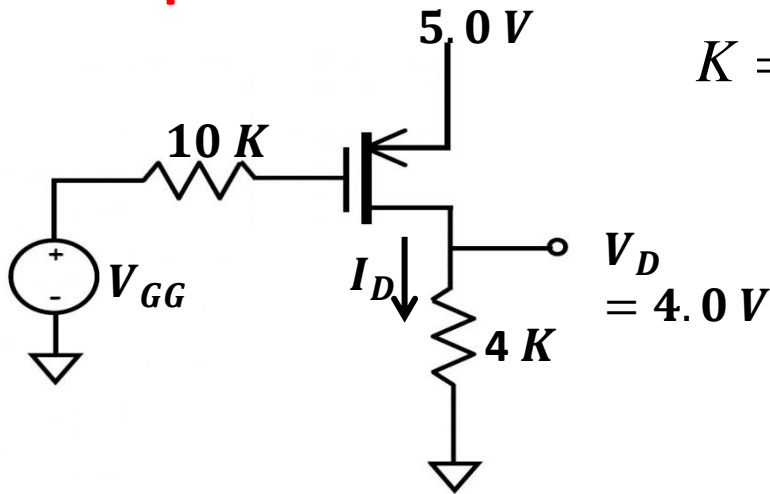

$$K = 0.2 \text{ mA} / \text{V}^2 \quad V_T = -2.0 \text{ V} \quad \text{Find } V_{GG}$$

- let's **ASSUME** that the PMOS is in **saturation** mode.
- Therefore, we **ENFORCE** the **saturation** drain $I_D = K (V_{GS} - V_T)^2$ current equation:

Q: Yikes! Where do we start ?

A: The best way to start is by “**picking the low-hanging fruit**”. In other words, determine the **obvious** and easy values. **Don't** ask, “What is V_{GG} ?”, but **instead** ask, “What **do** I know?” !

$$I_G = 0.0 \text{ mA} \quad V_S = 5.0 \text{ V}$$

$$I_D = \frac{V_D - 0.0}{4 \times 10^3} = \frac{4}{4 \times 10^3} = 1 \text{ mA}$$

$$V_G = V_{GG} - 10 \times 10^3 \times I_G = V_{GG}$$

$$V_{DS} = V_D - V_S = 4 - 5 = -1 \text{ V}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5 \quad \text{V}$$

Example – 2 (contd.)

- We can now relate these values using PMOS **drain current equation**.

$$I_D = K (V_{GS} - V_T)^2 \quad \longrightarrow \quad 1 \times 10^{-3} = 0.2 \times 10^{-3} \times (V_{GS} - (-2.0))^2$$

$$V_{GS} = 0.24 \text{ V} \quad V_{GS} = -4.23 \text{ V}$$

- For this example, we have **ASSUMED** that the PMOS device is in **saturation**. Therefore, the gate-to-source voltage must be **less** (remember, it's a **PMOS** device!) than the **threshold voltage**: $V_{GS} < V_T$
 $\therefore V_{GS} = -4.23 \text{ V}$

Q: Does this mean our saturation **ASSUMPTION** is **correct**?

A: NO! It merely means that our saturation ASSUMPTION **might** be correct! We need to CHECK the other inequalities to know for **sure**.


- Now, returning to our circuit **analysis**, we can quickly determine the **unknown** value of V_{GG} . Recall that we **earlier** determined that:

$$V_{GS} = V_G - V_S = V_{GG} - 5 \quad \longrightarrow \quad -4.23 = V_{GG} - 5 \quad \longrightarrow \quad \therefore V_{GG} = 0.77 \text{ V}$$

Example – 2 (contd.)

This solution ($V_{GG} = 0.77V$) is of course true **only if** our original ASSUMPTION was correct. Thus, we must CHECK to see if our **inequalities** are valid.

- We of course already know that the **first** inequality is true—a p-type channel is induced:

$$V_{GS} = -4.23V < V_T = -2.0V$$


- However:

$$V_{DS} = -1.0V < V_{GS} - V_T = -2.23V$$


shows us that our ASSUMPTION was **incorrect!**

→ Time to make a **new ASSUMPTION** and **start over!**

- let's **now** ASSUME the PMOS device is in **triode** region. Then ENFORCE: $I_D = K \left[2(V_{GS} - V_T)V_{DS} - V_{DS}^2 \right]$

- Note that most of our **original** analysis was **independent** of our PMOS mode ASSUMPTION. Thus, we **again** conclude that:

$$I_G = 0.0 \text{ mA} \quad V_S = 5.0 \text{ V} \quad I_D = \frac{V_D - 0.0}{4 \times 10^3} = \frac{4}{4 \times 10^3} = 1 \text{ mA}$$

Example – 2 (contd.)

$$I_D = \frac{V_D - 0.0}{4 \times 10^3} = \frac{4}{4 \times 10^3} = 1 \text{mA}$$

$$V_G = V_{GG} - 10 \times 10^3 \times I_G = V_{GG}$$

$$V_{DS} = V_D - V_S = 4 - 5 = -1 \text{ V}$$

$$V_{GS} = V_G - V_S = V_{GG} - 5 \text{ V}$$

- Now, inserting these values in the **triode drain current equation**:

$$1 \times 10^{-3} = 0.2 \times 10^{-3} \times \left[2(V_{GS} - (-2.0))(-1.0) - (-1.0)^2 \right]$$

- Solving for V_{GS} we find:

$$V_{GS} = -5.0 \text{V}$$

- Therefore:

$$V_{GG} = V_{GS} + 5.0 = -5.0 + 5.0 = 0$$

The voltage source V_{GG} is equal to **zero**—provided that our triode ASSUMPTION is **correct**.

Example – 2 (contd.)

- First, we CHECK to see if a channel has indeed been **induced**.

$$V_{GS} = -5.0V < V_T = -2.0V$$



- Next, we CHECK to make sure that our channel is **not** in pinch off.


$$V_{DS} = -1.0V > V_{GS} - V_T = -3.0V$$



Our **triode** ASSUMPTION is **correct!** Thus, the voltage source $V_{GG} = 0.0V$.

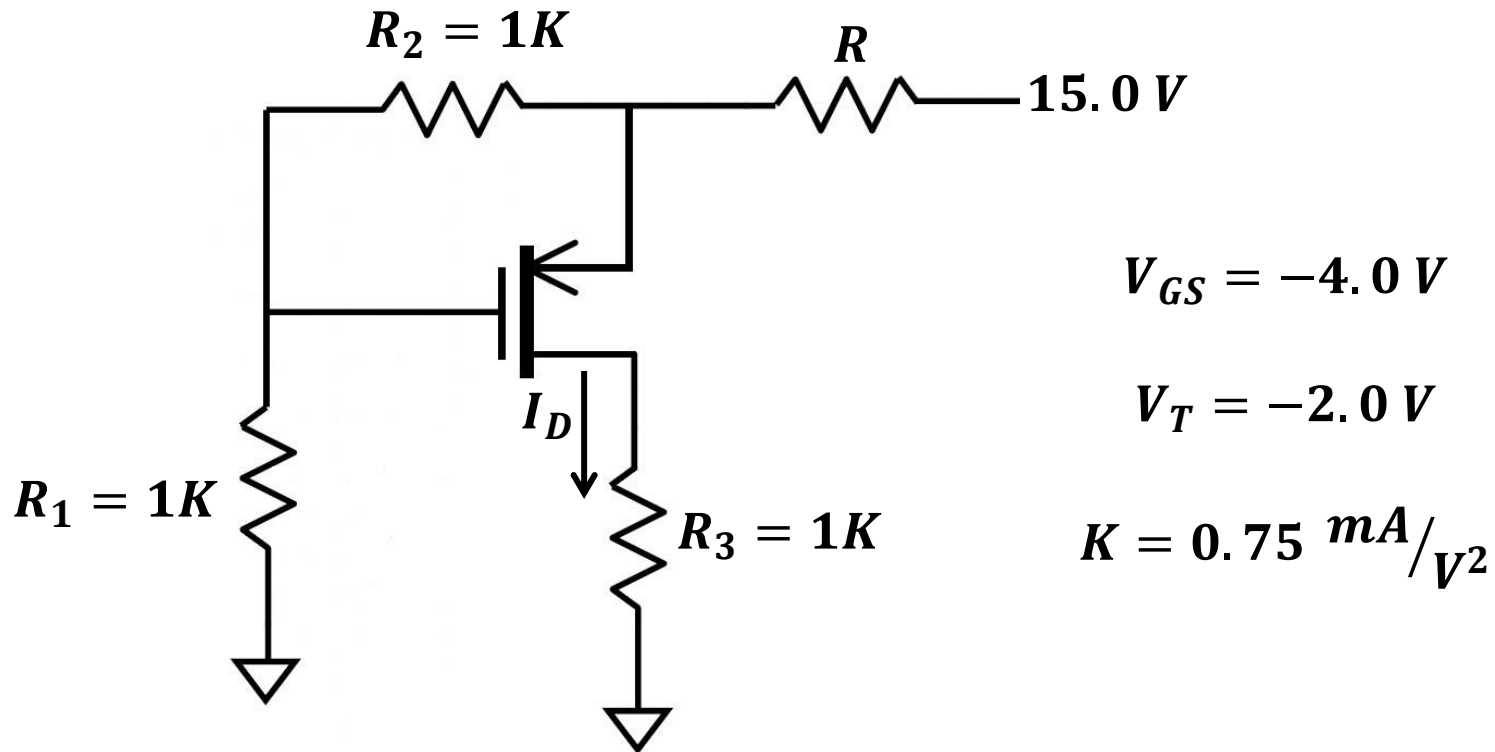
Example – 3

- Consider the **PMOS** circuit below, find the value of unknown of resistor R .



The MOSFET as a Switch and an Amplifier

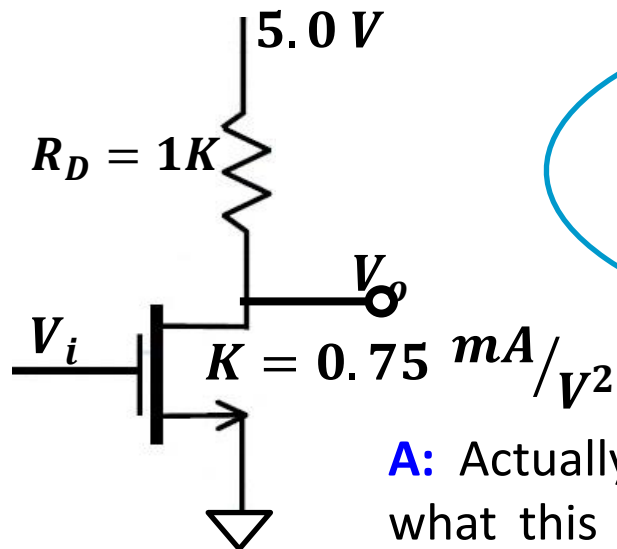- Consider this **simple** MOSFET circuit:



Q: Oh, goody—you're going to **waste** my time with another of these **pointless** academic problems. Why can't you discuss a circuit that actually **does** something?



A: Actually, this circuit **is** a fundamental electronic device! To see what this circuit does, we need to determine its **transfer function** $V_o = f(V_i)$.

Q: **Transfer function!** How can we determine the transfer function of a MOSFET circuit!?



A: **Same** as junction diodes—determine the output V_o for each device mode, and then determine **when** (i.e., for what values of V_i) the device is in that mode!

The MOSFET as a Switch and an Amplifier (contd.)

- First, note that **regardless** of the MOSFET mode:


$$V_{GS} = V_i - 0.0 = V_i \quad V_{DS} = V_o - 0.0 = V_o$$

- From KVL, we can likewise conclude that:

$$V_{DS} = V_o = 5.0 - I_D R_D$$

$$K = 0.75 \text{ mA/V}^2$$

$$V_T = 1.0 \text{ V}$$

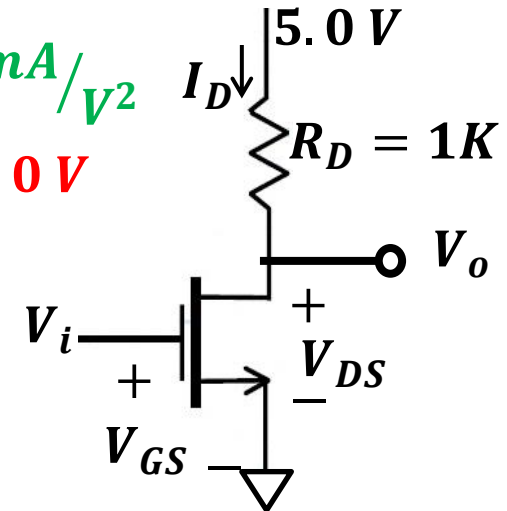

- Now let's ASSUME that the MOSFET is in **cutoff**, thus ENFORCING $I_D = 0$.

$$V_{DS} = V_o = 5.0 - I_D R_D \Rightarrow V_o = 5.0 - 0 \times (1 \times 10^3) \Rightarrow \therefore V_o = 5.0 \text{ V}$$

- Now, we know that MOSFET is in cutoff **when**: $V_{GS} = V_i < V_T = 1.0 \text{ V}$

- Thus, we conclude that: $V_o = 5.0 \text{ V}$ when $V_i < 1.0 \text{ V}$

The MOSFET as a Switch and an Amplifier (contd.)

- Now, let's ASSUME that the MOSFET is in **saturation**, thus ENFORCE:

$$I_D = K(V_{GS} - V_T)^2 \quad \longrightarrow \quad I_D = K(V_i - 1.0)^2$$

- And thus the output voltage is:

$$V_o = 5.0 - I_D R_D = 5.0 - 0.75 \times 10^{-3} \times (V_i - 1.0)^2 \times 1 \times 10^3$$

$$\therefore V_o = 5.0 - 0.75 \times (V_i - 1.0)^2$$

- We know that MOSFET is in saturation **when**:

$$V_{GS} = V_i > V_T = 1.0 \text{ V} \quad \text{and} \quad V_{DS} = V_o > V_{GS} - V_T = V_i - 1.0$$

- The second inequality means:

$$V_o > V_i - 1.0 \quad \longrightarrow \quad 5.0 - 0.75 \times (V_i - 1.0)^2 > V_i - 1.0$$

- Solving this quadratic, we find that the **only** consistent solution is:

$$V_i - 1.0 < 2.0 \quad \longrightarrow \quad V_i < 3.0$$

- Thus we conclude that the MOSFET in saturation:

$$V_o = 5.0 - 0.75 \times (V_i - 1.0)^2 \quad \text{when} \quad 1.0 < V_i < 3.0 \text{ V}$$

The MOSFET as a Switch and an Amplifier (contd.)

- Finally, let's ASSUME that the MOSFET is in **triode** mode, thus we ENFORCE:

$$I_D = K[2(V_{GS} - V_T)V_{DS} - (V_{DS})^2]$$

- And thus the output voltage is:

$$V_o = 5.0 - I_D R_D = 5.0 - 0.75 \times [2(V_i - 1.0)V_o - (V_o)^2]$$

- Rearranging the equation, we get the quadratic form:

$$0.75(V_o)^2 - (1.5V_i - 0.5)V_o + 5.0 = 0$$

- The solutions of which are:

$$V_o = \frac{(1.5V_i - 0.5) \pm \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$

- Note due to \pm , there are **two** possible solutions. However, for triode region, the $V_{DS} = V_o < V_{GS} - V_T = V_i - 1.0$ MOSFET must not be in pinchoff, i.e.:

- This is satisfied with the **smaller** of the two solutions (i.e., the solution with the minus sign!):

$$V_o = \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$

The MOSFET as a Switch and an Amplifier (contd.)

$$V_o = \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$

This provides us with the output voltage **if** the MOSFET is in triode. The question remaining is thus **when** (i.e., for what values of V_i) is the MOSFET in triode mode?

We could do a lot more math to find this answer, but this answer is actually quite obvious!

- Recall that we have already determined that:
 - The MOSFET is in cutoff **when** $V_i < 1.0V$.
 - The MOSFET is in saturation **when** $1.0V < V_i < 3.0V$.
- Since there are only **three** modes of a MOSFET device, and since the transfer **function** must—well—be a **function**, we can conclude (correctly) that the MOSFET will be in triode region when V_i is the value of the **only region that is left: $V_i > 3.0V$.**

The MOSFET as a Switch and an Amplifier (contd.)

- Thus we can conclude that:

$$V_o = \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5}$$



when

$$V_i > 3.0 V$$

- We now have determined the complete, continuous **transfer function** of this circuit!

$$V_o = \begin{cases} 5.0 V & \text{when } V_i < 1.0 V \\ 5.0 - 0.75 \times (V_i - 1.0)^2 & \text{when } 1.0 < V_i < 3.0 V \\ \frac{(1.5V_i - 0.5) - \sqrt{(1.5V_i - 0.5)^2 - 15.0}}{1.5} & \text{when } V_i > 3.0 V \end{cases}$$

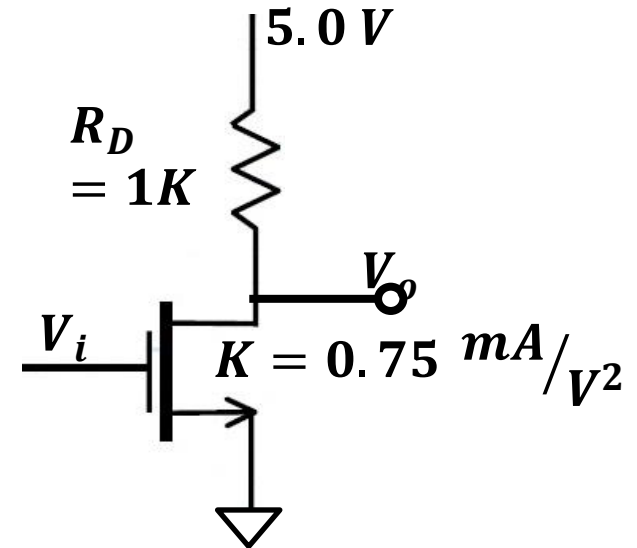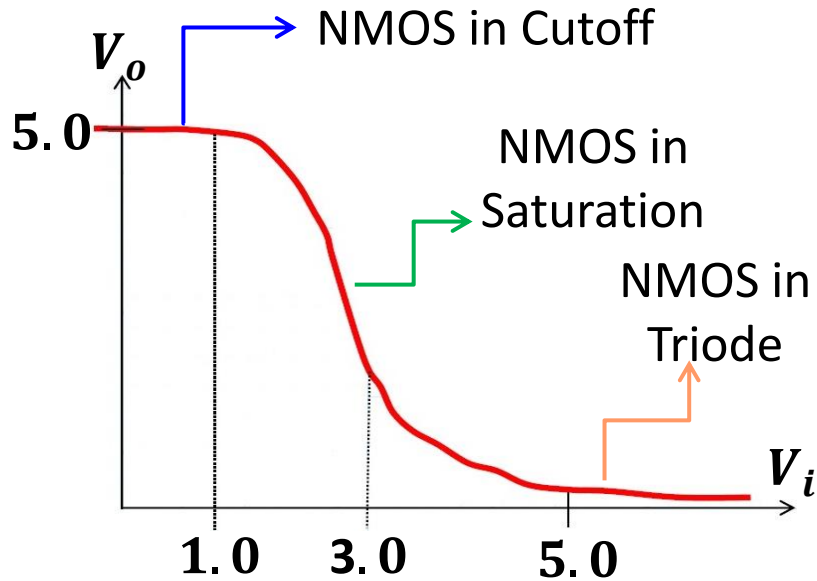The MOSFET as a Switch and an Amplifier (contd.)




Q: I thought you said this circuit **did** something. It appears to be just as **pointless** as all the others!

A: To see how this circuit is **useful**, consider what happens when the **input** voltage V_i is 0 V and 5V.

The MOSFET as a Switch and an Amplifier (contd.)

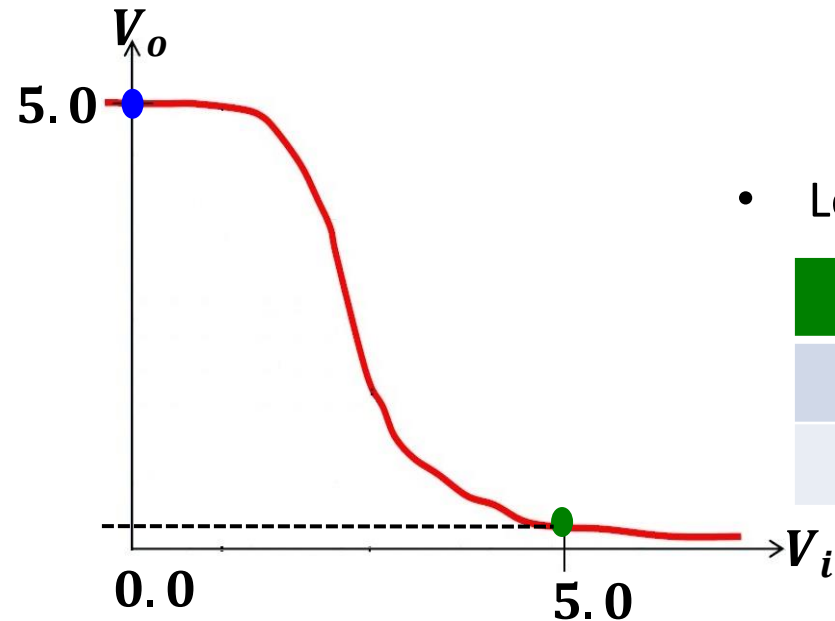- From the transfer function, we find if $V_i = 0V$, the output voltage will be $V_o = 5V$. Likewise, if the input voltage is $V_i = 5V$, the output voltage will be **small**.



- Let's summarize these results in a table:

V_i	V_o	Mode
0.0	5.0	Cutoff
5.0	Small (~ 0.5)	Triode


This device is not useless at all! It is **clearly** a: **Switch**



The MOSFET as a Switch and an Amplifier (contd.)

- This circuit provides a **simple** example of **one** of the primary **applications** of MOSFET devices—**digital circuit design**. We can use MOSFETs to make digital devices such as **logic gates** (AND, OR, NOR, etc.), **flip-flops**, and digital **memory**.
- We typically find that, just like this circuit, when a MOSFET digital circuit is in **either** of its **two** binary states (i.e., “0” or “1”), the MOSFETs in the circuit will either be in **cutoff** ($I_D = 0$) or in **triode** (V_{DS} small) modes.

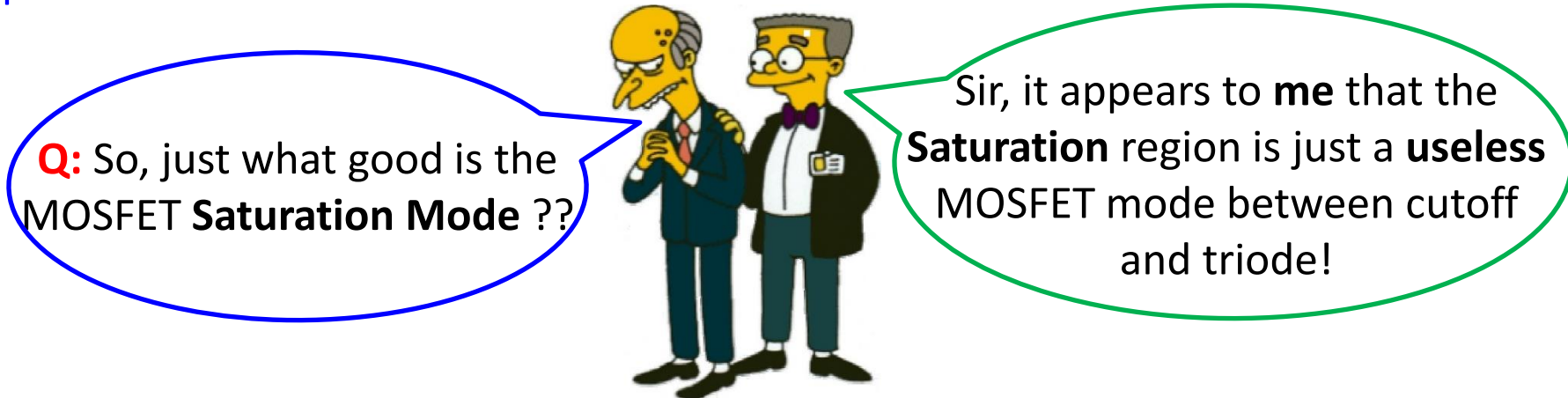
→ **Cutoff** and **Triode** are the MOSFET modes associated with **digital** circuits and applications!



A: Actually, we will find the MOSFET **saturation** mode to be **extremely useful!**

The MOSFET as a Switch and an Amplifier (contd.)

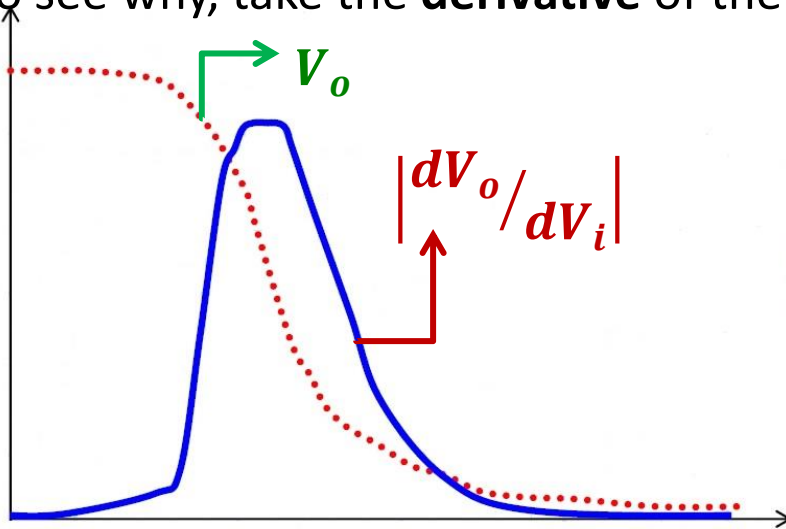- To see why, take the **derivative** of the above circuit's transfer function (dV_o/dV_i).



- We note that in **cutoff** and **triode**: $|dV_o/dV_i| \approx 0$
- While in the **saturation** mode: $|dV_o/dV_i| \gg 1$

Q: Oh goody. The **slope** of the transfer function is **large** when the MOSFET is in **saturation**. Am I supposed to be impressed by that?! How are these results even **remotely** important!?



A: Since in **cutoff** and **triode** $|dV_o/dV_i| \approx 0$, a **small change** in input voltage V_i will result in almost **no change** in output voltage V_o .

Contrast this with the **saturation** region, where $|dV_o/dV_i| \gg 1$. This means that a **small change** in input voltage V_i results in a **large change** in the **output** voltage V_o !



The MOSFET as a Switch and an Amplifier (contd.)

- To see how this is important, consider the case where the input signal has both a **DC** and a **small-signal** (AC) component: $v_I(t) = V_i + v_i(t)$
- As a result, the **output** voltage likewise has both a DC and small signal component: $v_O(t) = V_o + v_o(t)$

Now, let's consider **only** the **DC** components. We can select the DC input V_i such that the MOSFET is placed in **saturation**. The value V_i , along with the resulting DC output V_o , sets a **DC bias point** for this circuit.

By selecting the right value of V_i we **could** set this DC bias point to where the transfer function **slope** is the greatest.

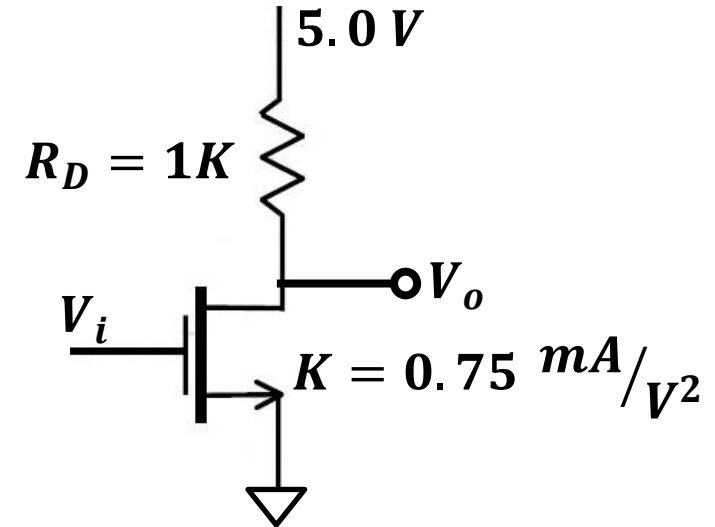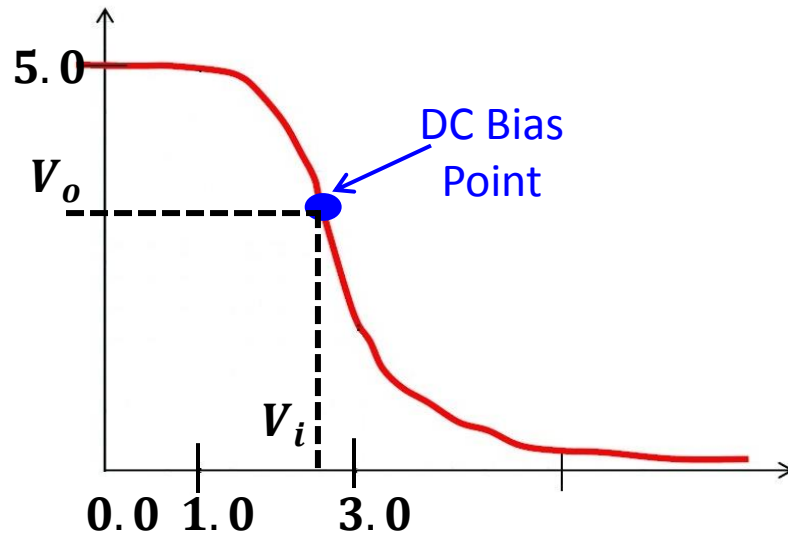The MOSFET as a Switch and an Amplifier (contd.)



Now, say we **add** a **small-signal** v_i to this input DC voltage (i.e., $v_I(t) = V_i + v_i(t)$). This small signal simply represents a small change in the input voltage from its **average** (i.e., DC) value. The result is of course a **small change** in the **output** voltage—the **small-signal output voltage** $v_o(t)$!

- Now for the **interesting** part (I bet you were wondering when I would get around to it)! The small change in the output voltage will have a much **larger** magnitude than the small change in the input!

For example, if the input voltage changes by **1 mV** (i.e., $v_i = 1\text{mV}$), the output **might** change by, say, **5 mV** (i.e., $v_o = 5\text{mV}$).

The MOSFET as a Switch and an Amplifier (contd.)



Q: Goodness! By how much would the **output** change in our example circuit? How can we **determine** the small signal **output** v_o ??

- Determining how much the output voltage of our circuit will change when we change the input voltage by a small amount is very **straightforward**—we simply take the **derivative** of the output voltage v_o with respect to input voltage v_I .
- By taking the **derivative** of v_o with respect to v_I (when the MOSFET is in saturation, we find:

$$\frac{dv_o}{dv_I} = \frac{d(5.0 - 0.75(v_I - 1.0)^2)}{dv_I} \quad \Rightarrow \quad = -1.50(v_I - 1.0) \quad \text{when } 1.0 < v_I < 3.0 \text{ V}$$

The expression describes the **slope** of our circuit's transfer function (for $1.0 < v_I < 3.0 \text{ V}$). Note the slope with the **largest magnitude** occurs when $v_I = 3.0 \text{ V}$, providing a **slope** of -3.0 mV/mV .

The MOSFET as a Switch and an Amplifier (contd.)

- Thus, **if** we DC bias this circuit with $V_i = 3.0$ V (resulting in $V_o = 2.0$ V), we find that the small signal output will be **3 times** the small signal input!
- **For example**, say that the **input** to our circuit is:

$$v_i(t) = 3.0 + 0.01 \cos(\omega t) \text{ V} \quad \text{Here: } V_i = 3.0 \text{ V} \quad v_i = 0.01 \cos(\omega t)$$

- We would find that the **output voltage** would approximately be:

$$v_o(t) = 2.0 - 0.03 \cos(\omega t) \text{ V} \quad \text{Here: } V_o = 2.0 \text{ V} \quad v_o = -0.03 \cos(\omega t)$$

In other words, the magnitude of the small-signal output has a magnitude **three times larger** than the input magnitude.

We say then that our signal provides **small-signal gain**—our circuit is also a **small-signal amplifier**!

The MOSFET as a Switch and an Amplifier (contd.)

I see. A **small** voltage change results in a **big** voltage change—it's **voltage gain!**

The **MOSFET saturation** mode turns out to be—**excellent.**



- Even the simple circuit of this example is sufficient to demonstrate the **two primary applications** of MOSFET transistors--**digital** circuits and signal **amplification**.
- The important MOSFET regions for **digital** devices are **triode** and **cutoff**, MOSFETs in amplifier circuits are typically biased into the **saturation** mode!