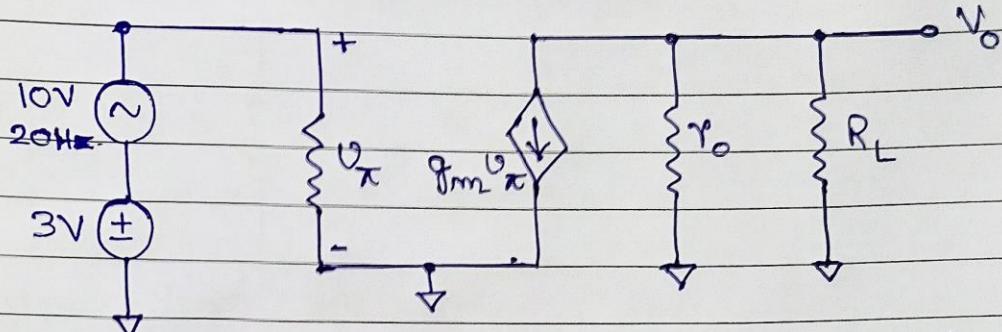



## Problem set



The given circuit represents a very basic model of a FET. It operates on the principle of voltage dependent current sources where the drain current is directly dependent on the gate-source voltage. Transconductance ( $g_m$ ) is a parameter that defines the current dependency on the voltage. It has an unit of  $(\frac{A}{V})$ . Here, if  $g_m = 10 \text{ mS}$ ,  $r_\pi = 100 \text{ k}\Omega$ ,  $r_o = 200 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ , find the output voltage  $V_o$  manually as well as in SPICE.


If there is a capacitive load  $C_L = 100 \mu\text{F}$  in parallel with  $R_L$ , find the time required to charge it to maximum (in SPICE, as well as manually).

$$[5+5=10]$$

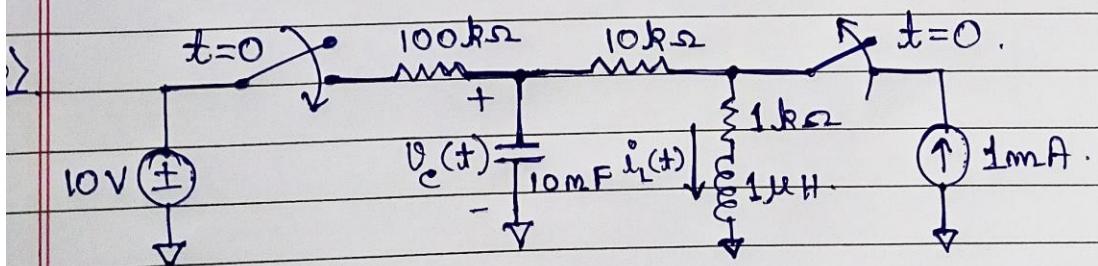


Determine the value of  $V_c(t)$  and  $i_L(t)$  long time after the event of switching [in SPICE as well as manually].  $[5+5=10]$

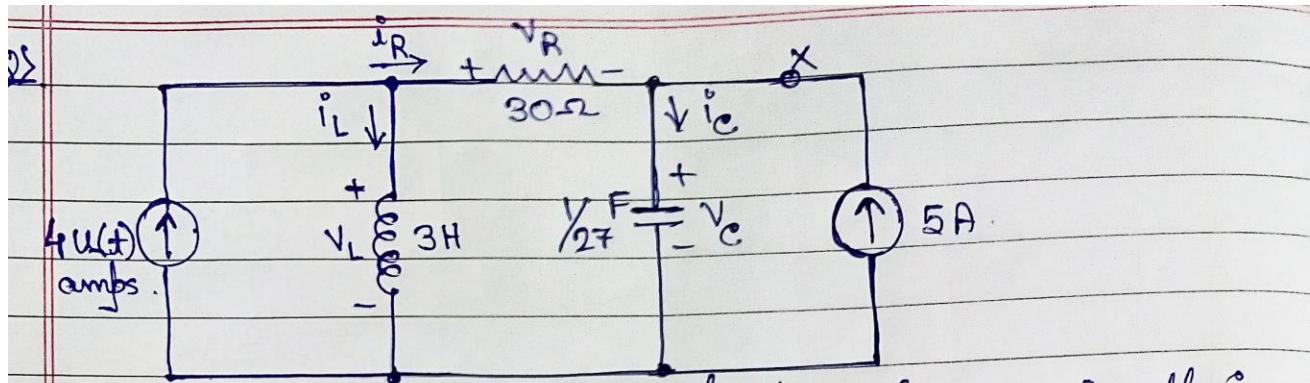→ BONUS: In practical circuits where high voltage switching occurs, why is it always advisable to place a capacitor across a switch.



Assume that the circuit has been in this situation for a long time. Find  $\frac{dv_c}{dt}|_{t=0^+}$   
[in SPICE and manually].

$$[5+5=10]$$

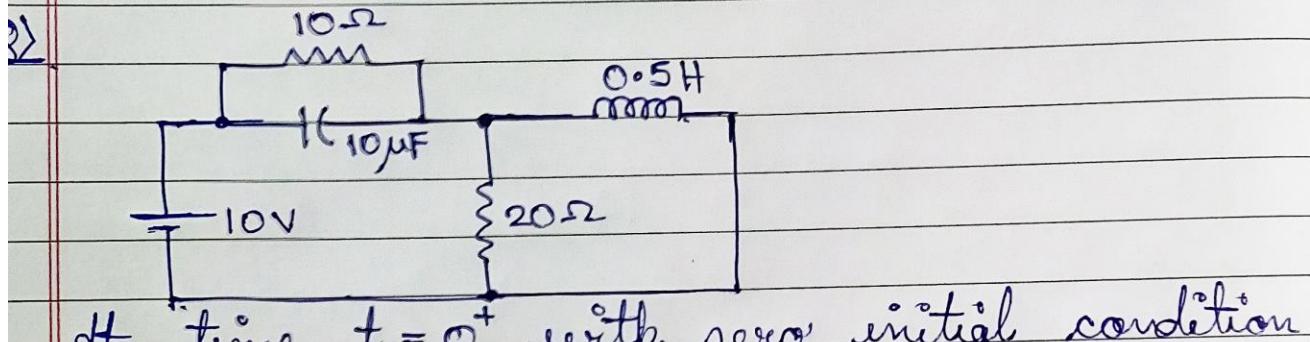

At time  $t = 0^+$  with zero initial condition voltage across the  $20\Omega$  resistor is ?  
[in SPICE and manually].

$$[5+5=10]$$