
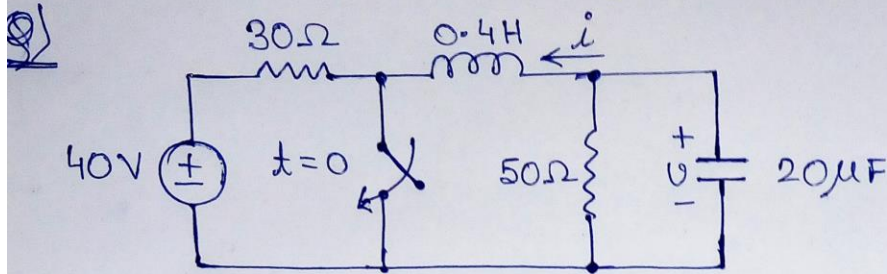



Assignment.

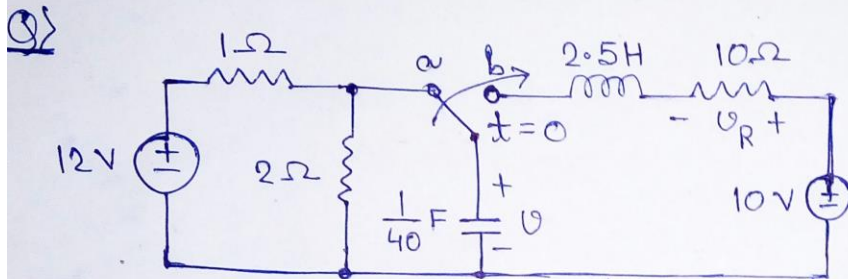


Find $v(t)$ for $t > 0$ in the RLC circuit shown above. [SPICE + manually]



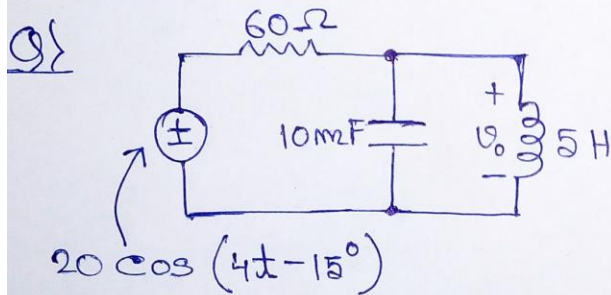Having been in position 'a' for a long time the switch in Fig. it is moved to position 'b' at $t = 0$. Find $v(t)$ and $v_R(t)$ for $t > 0$. [SPICE + manually]



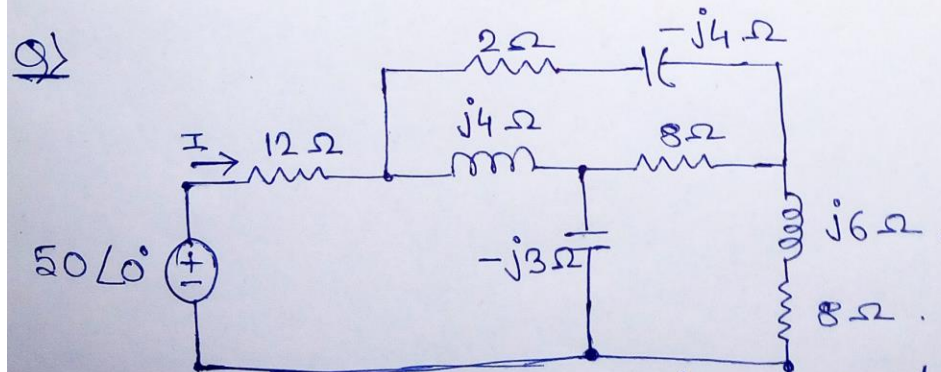Determine $v_o(t)$ in the circuit. [SPICE + manually]



Find current I in the circuit [SPICE + manually]

Q5) A capacitance bridge balances when $R_1 = 100\Omega$