

Lecture – 14


Date: 29.09.2016

- Transformer

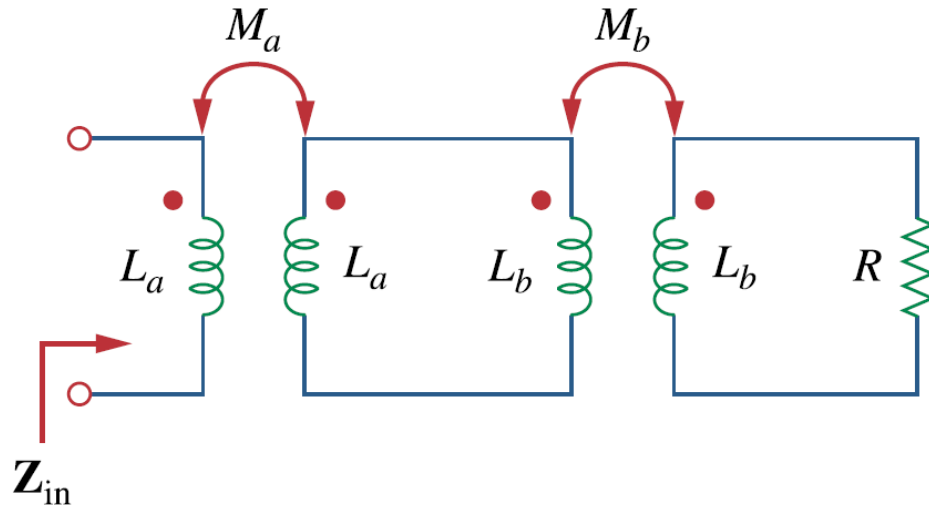Example – 1


Two linear transformers are cascaded as shown below. Show:

$$\mathbf{Z}_{in} = \frac{\omega^2 R(L_a^2 + L_a L_b - M_a^2 + j\omega^3(L_a^2 L_b + L_a L_b^2 - L_a M_b^2 - L_b M_a^2))}{\omega^2(L_a L_b + L_b^2 - M_b^2) - j\omega R(L_a + L_b)}$$



Ideal Transformers

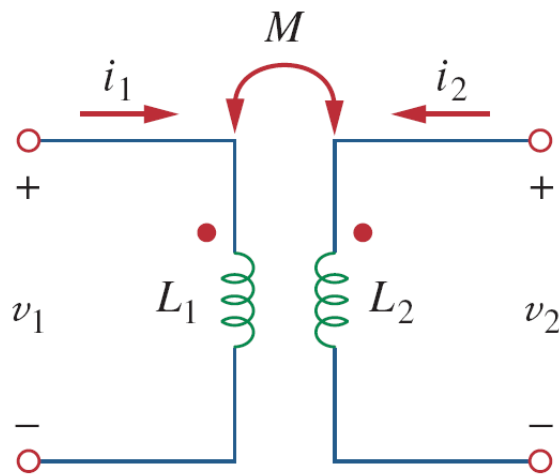- An ideal transformer exhibits perfect coupling i.e., $k = 1$.
- It consists of two (or more) coils with a large number of turns wound on a common core of high permeability. Because of this high permeability of the core, the flux links all the turns of both coils, thereby resulting in a perfect coupling.



- In the frequency domain:

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2$$

$$\mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2$$

$$\mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 + \frac{M \mathbf{V}_1}{L_1} - \frac{j\omega M^2 \mathbf{I}_2}{L_1}$$

Ideal Transformers (contd.)

- We know for ideal transformer $k = 1$ and therefore $M = \sqrt{L_1 L_2}$

$$V_2 = j\omega L_2 I_2 + \frac{\sqrt{L_1 L_2} V_1}{L_1} - \frac{j\omega L_1 L_2 I_2}{L_1} = \sqrt{\frac{L_2}{L_1}} V_1 = n V_1$$



For $L_1, L_2, M \rightarrow \infty$, the turn ratio n remains the same and in such a scenario the coupled coils become an ideal transformer.

$$n = \sqrt{L_2 / L_1}$$

- A transformer is said to be ideal if:**
 - Coils have very large reactances ($L_1, L_2, M \rightarrow \infty$)
 - Coupling coefficient is equal to unity ($k=1$)
 - Primary and secondary coils are lossless ($R_1 = 0 = R_2$).

Iron-core transformers are close approximations to ideal transformers.

Ideal Transformers (contd.)

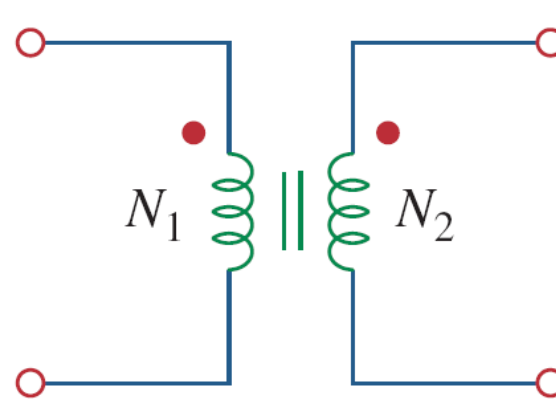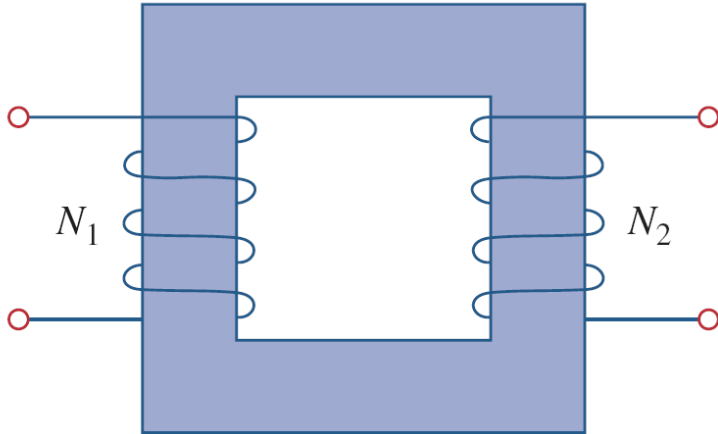

$$v_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n \quad \rightarrow \quad \frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

- For power conservation, the energy supplied to the primary must equal the energy absorbed by the secondary (there are no losses in an ideal transformer).

$$v_1 i_1 = v_2 i_2$$

$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = n$$

the primary and secondary currents are related to the turns ratio in the inverse manner as the voltages.

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$





Ideal Transformers (contd.)

- For $n > 1$, we have a ***step-up transformer***, as the voltage is increased from primary to secondary ($V_2 > V_1$).
- For $n < 1$, the transformer is a ***step-down transformer***, as the voltage is decreased from primary to secondary ($V_2 < V_1$).

The ratings of transformers are usually specified as V_1 / V_2 . A transformer with rating 2400/120 V should have 2400 V on the primary and 120 in the secondary (i.e., a step-down transformer). Keep in mind that the voltage ratings are in rms.

- It is important to get the proper polarity of the voltages and the direction of the currents for the transformer. The two simple rules to follow are:
 - If V_1 and V_2 are *both* positive or both negative at the dotted terminals, use $+n$ in the equations. Otherwise, use $-n$.
 - If I_1 and I_2 are *both* enter into or both leave the dotted terminals, use $+n$. Otherwise use $-n$.

Ideal Transformers (contd.)

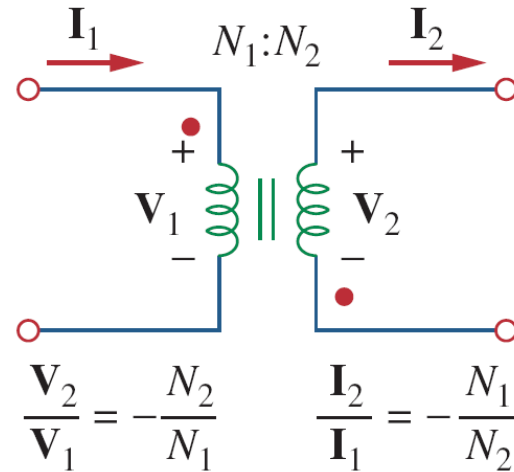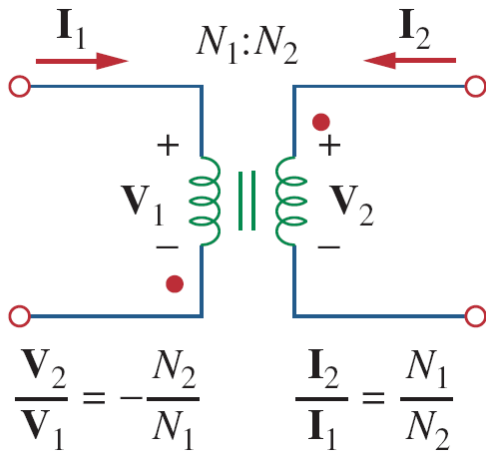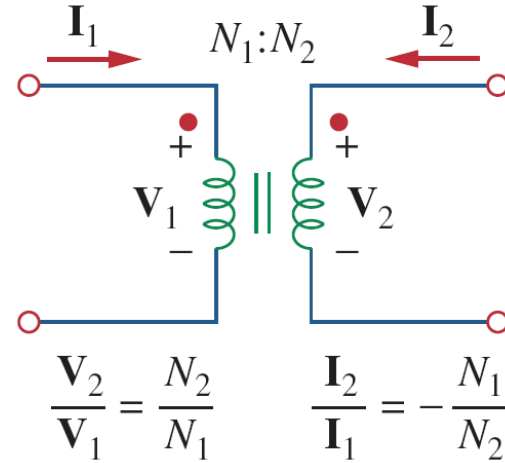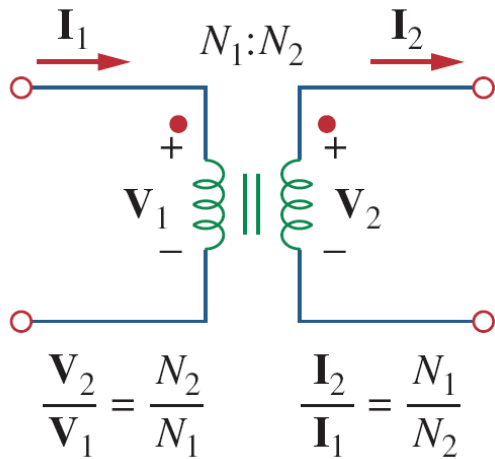

Ideal Transformers (contd.)

$$V_1 = \frac{V_2}{n} \quad \text{or} \quad V_2 = nV_1$$

- we can always express:

$$I_1 = nI_2 \quad \text{or} \quad I_2 = \frac{I_1}{n}$$

- The complex power in the primary winding is:

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (nI_2)^* = V_2 I_2^* = S_2$$

the complex power supplied to the primary is delivered to the secondary without loss. The transformer absorbs no power. It is expected as the ideal transformer is lossless.



- The input impedance seen by the source:

$$Z_{in} = \frac{V_1}{I_1} = \frac{1}{n^2} \frac{V_2}{I_2} \quad \rightarrow \quad Z_{in} = \frac{Z_L}{n^2}$$

- The input impedance is also called the *reflected impedance*. The ability of the transformer to transform a given impedance into another impedance provides us a means of *impedance matching* to ensure maximum power transfer.

Ideal Transformers (contd.)

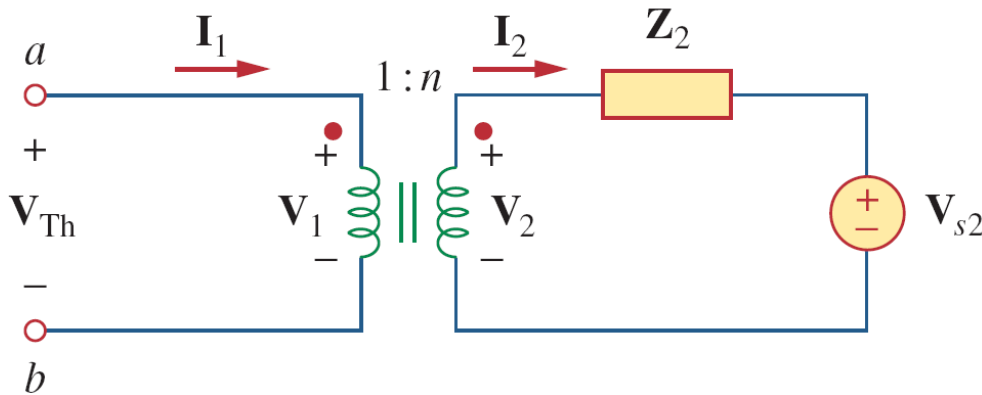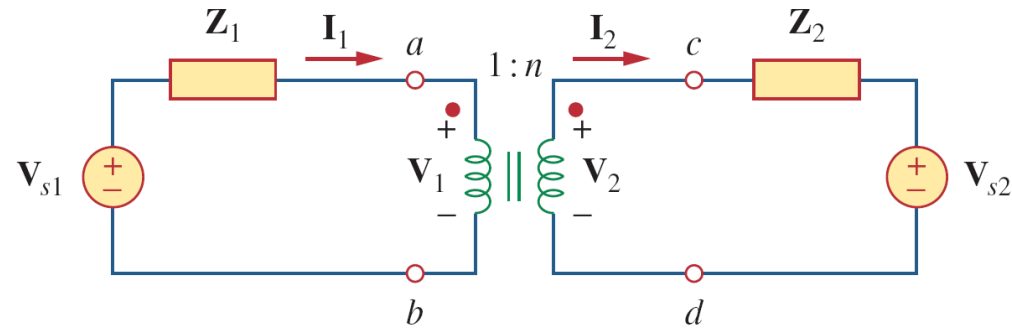- In analyzing a circuit containing an ideal transformer, it is common practice to eliminate the transformer by reflecting impedances and sources from one side of the transformer to the other.
- suppose we want to reflect the secondary side of the circuit to the primary side i.e, *a-b*.




- First, obtain V_{TH} as the open-circuit voltage at terminals *a-b*.


• **Now, a-b is open: so $V_2 = V_{s2}$:**
$$V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n}$$

Ideal Transformers (contd.)

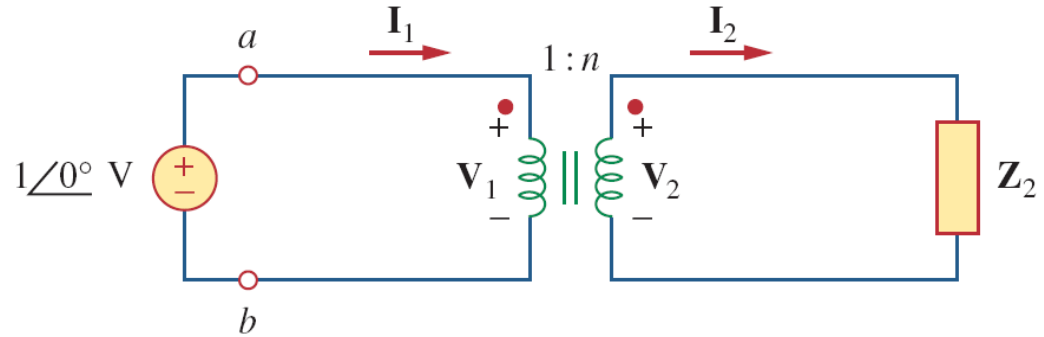- For Z_{TH} , remove voltage source in secondary and excite the primary with a unit source.
- Now, $I_1 = nI_2$ and $V_1 = \frac{V_2}{n}$ and therefore:
- Once we have Z_{TH} and V_{TH} , we get the equivalent circuit as:



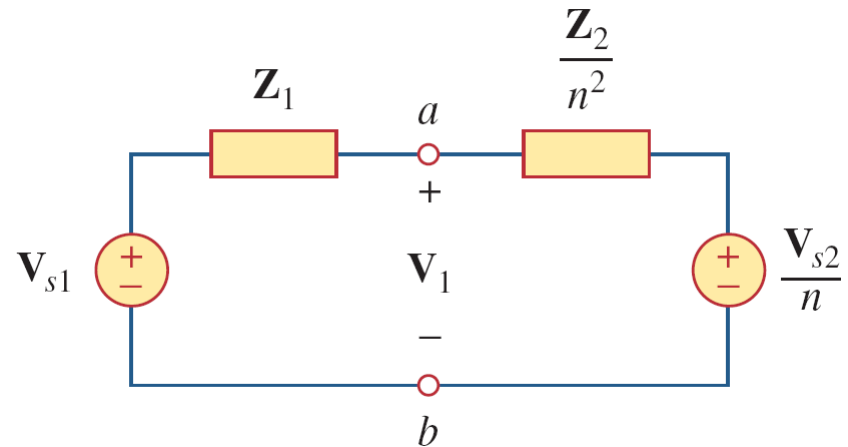
$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2/n}{nI_2} = \frac{Z_2}{n^2}, \quad V_2 = Z_2 I_2$$



Ideal Transformers (contd.)




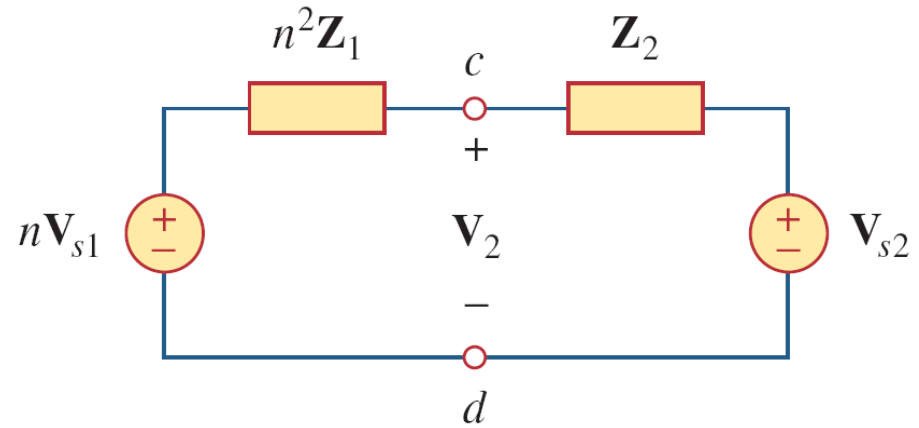
- We can also reflect the primary side of the circuit as:



- the power remains the same, whether calculated on the primary or the secondary side.
- However, this reflection approach only applies if there are no external connections between the primary and secondary windings.
- When we have external connections between the primary and secondary windings, we simply use regular mesh and nodal analysis.

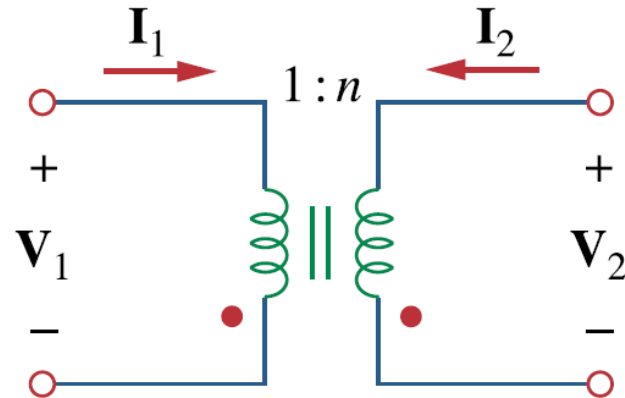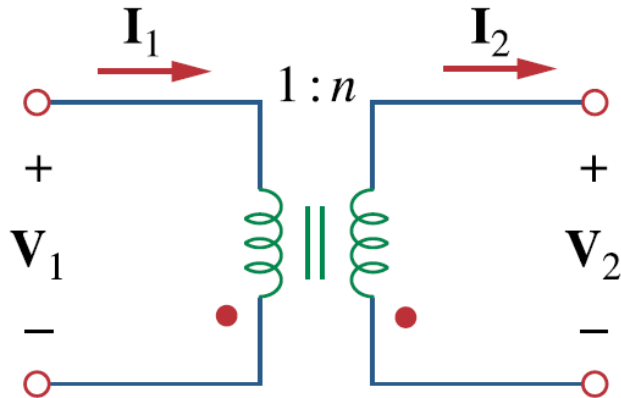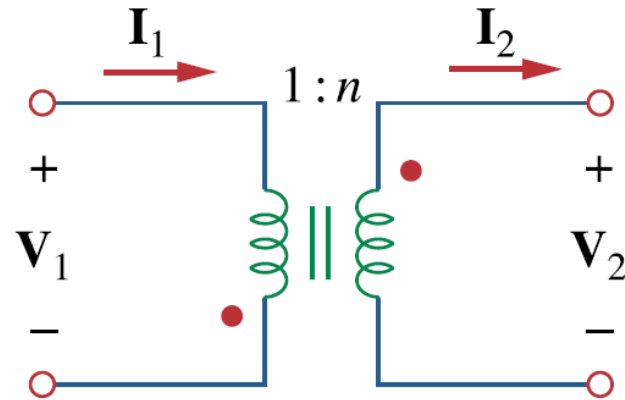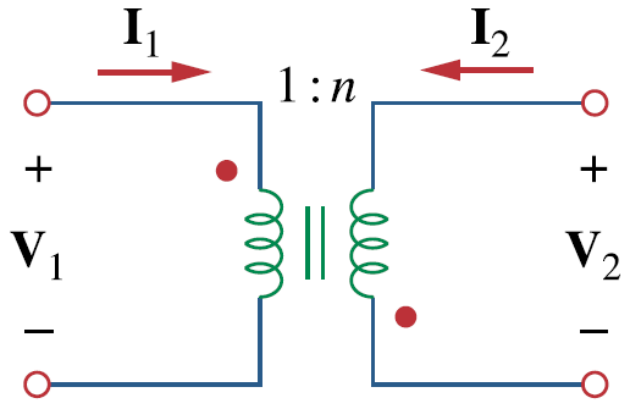Example – 2

- obtain the relationships between terminal voltages and currents for each of the ideal transformers given below




Example – 3

The primary of an ideal transformer with a turns ratio of 5 is connected to a voltage source with Thevenin parameters $v_{TH} = 10\cos 2000t$ V and $R_{TH} = 100\Omega$. Determine the average power delivered to a 200Ω load connected across the secondary winding.

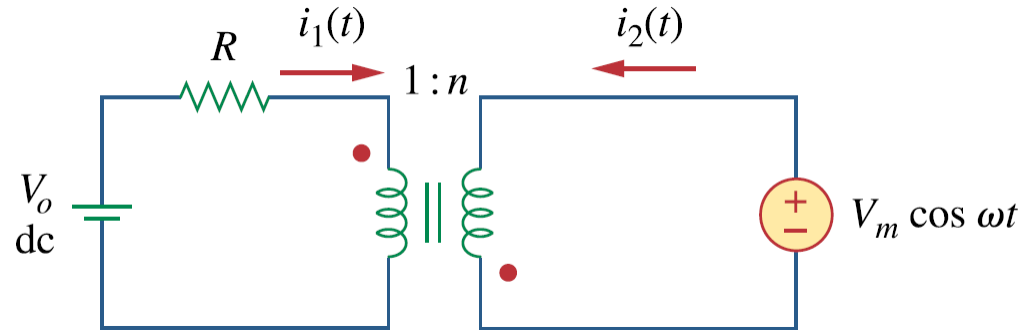
Example – 4

- In this ideal transformer circuit, find $i_1(t)$ and $i_2(t)$.




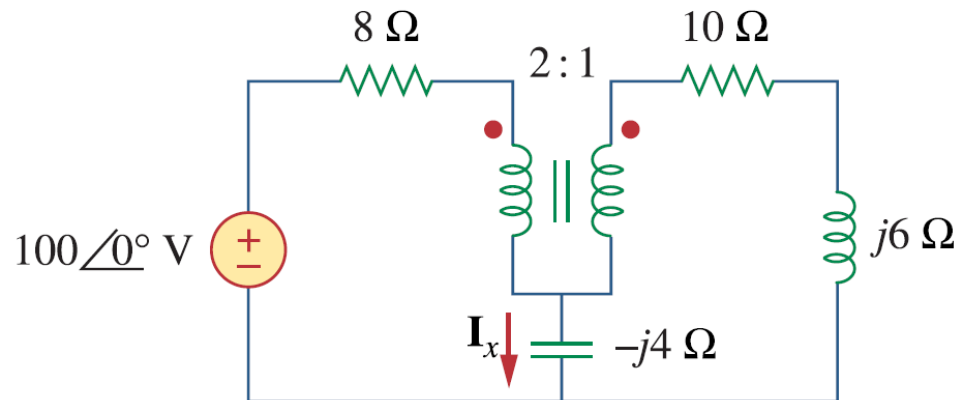
Example – 5

Find I_x in this ideal transformer circuit



Ideal Autotransformers

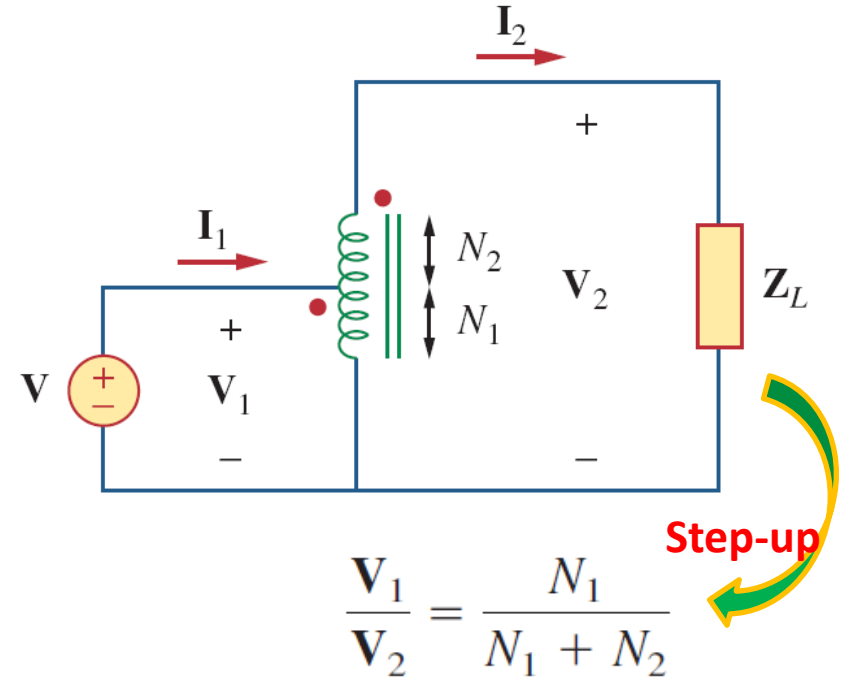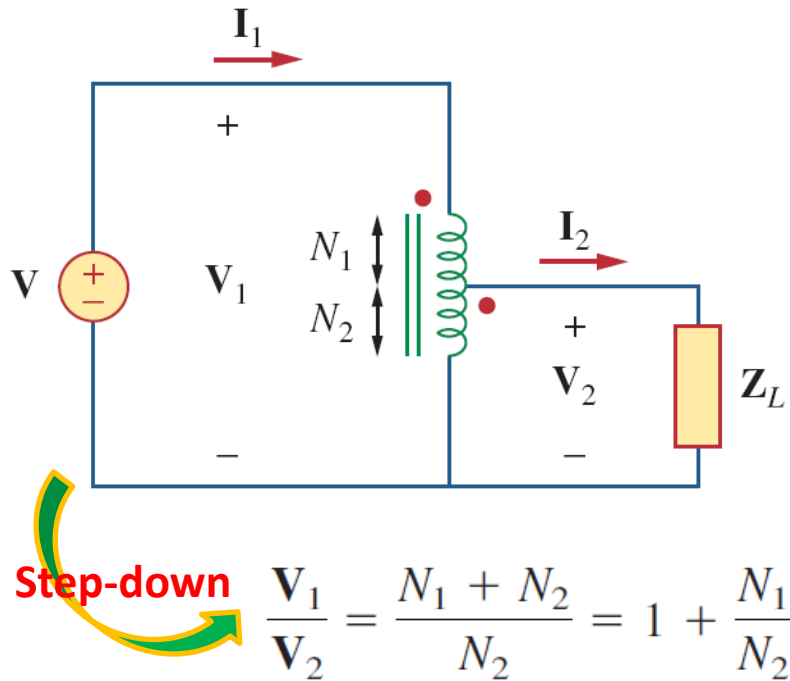- An *autotransformer* has a single continuous winding with a connection point called a *tap* between the primary and secondary sides.
- The tap is often adjustable so as to provide the desired turns ratio for stepping up or stepping down the voltage. This way, a variable voltage can be provided to the load connected to the autotransformer.



Ideal Autotransformers

- an ideal autotransformer, there are no losses, so the complex power remains the same in the primary and secondary:

$$S_1 = V_1 I_1^* = S_2 = V_2 I_2^*$$

→ $V_1 I_1 = V_2 I_2$

→ $\frac{V_2}{V_1} = \frac{I_1}{I_2}$

Step-down

$$\frac{I_1}{I_2} = \frac{N_2}{N_1 + N_2}$$

Step-up

$$\frac{I_1}{I_2} = \frac{N_1 + N_2}{N_1} = 1 + \frac{N_2}{N_1}$$

- A major difference between conventional transformers and autotransformers is that the primary and secondary sides of the autotransformer are not only coupled magnetically but also coupled conductively.
- The autotransformer can be used in place of a conventional transformer when electrical isolation is not required.

Example – 6

