

# Magnitude/Frequency/Magnitude-Frequency Scaling

## **Circuit Theory and Devices**



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY **DELHI**

# Magnitude Scaling

- **Magnitude scaling is the process of increasing all impedance in a network by a factor, such that the frequency response remaining unchanged**
- **Multiply impedances of each circuit elements by a constant  $k_m$**
- **Before scaling,  $Z_R = R, Z_L = j\omega L, Z_C = 1/j\omega C$**
- **After scaling the impedances**

$$Z_R' = k_m Z_R, Z_L' = k_m Z_L, Z_C' = k_m Z_C$$

- **Scaled component values  $R' = k_m R, L' = k_m L, C' = C/k_m$**
- **What would be the effect of magnitude scaling on Q-factor and resonant frequency for series RLC circuit?**

# Frequency Scaling


- Frequency scaling is the process of shifting the frequency response of a network up or down the frequency axis while leaving the impedance the same
- Multiply frequency by a constant  $k_f$  keeping the impedance same i.e.  $\omega' = k_f \omega$
- Before scaling,  $Z_R = R, Z_L = j\omega L, Z_C = 1/j\omega C$
- After frequency scaling,  $Z_L = j(\omega k_f)L', Z_C = 1/j(\omega k_f)C'$
- Scaled component values  $R' = R, L' = L/k_f, C' = C/k_f$
- What would be the effect of magnitude scaling on Q-factor and resonant frequency for series RLC circuit?

# Magnitude/Frequency Scaling

- **Scaling in magnitude and frequency results in**

$$R' = k_m R, L' = (k_m L)/k_f, C' = C/(k_m k_f)$$

**Example 1:**

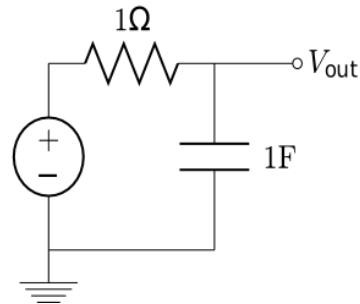

$$\text{3-dB cut-off frequency: } f = \frac{1}{2\pi} \text{ Hz}$$

Requirement: 3-dB cut-off frequency = 1 kHz and  $C' = 1 \text{ nF}$

Step 1: Frequency scaling factor =  $1000 / \frac{1}{2\pi} = 2000\pi$

Step 2: Magnitude scaling factor,  $k_m = C / (C' k_f) = 1.59 * 10^5$

Step 3: Scaled resistor value,


$$R' = k_m R = 1.59 * 10^5 * 1 = 1.59 * 10^5 \Omega$$

# Magnitude/Frequency Scaling
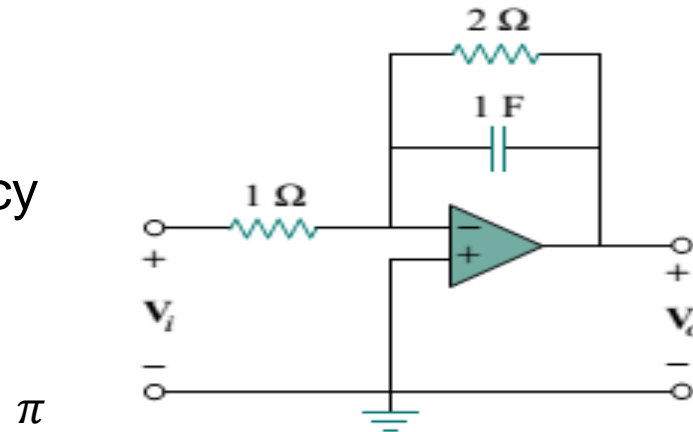
## Example 2:

3-dB cut-off frequency:  $\omega = 1$  rad/s

Requirement: 3-dB cut-off frequency  
= 200 rad/s and  $C' = 1 \mu\text{F}$



Solution

Step 1: Frequency scaling factor =  $200/1 = 200$

Step 2: Magnitude scaling factor,  $k_m = C/(C'k_f) = 5000$

Step 3: Scaled resistor value,

$$R' = k_m R = 5000 * 1 = 5000 \Omega$$

$$R'_2 = 2R' = 10000 \Omega$$