
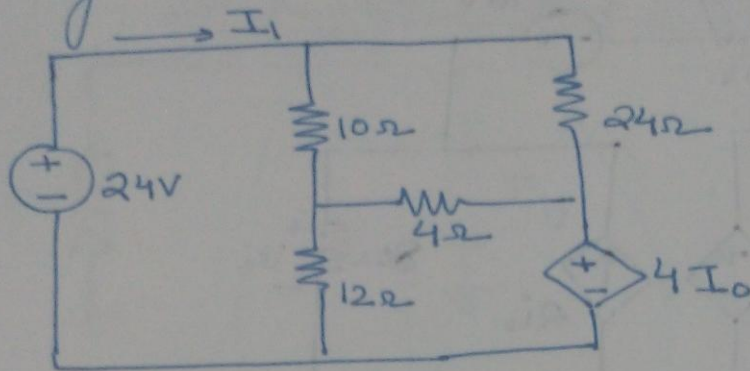


Assignment-1

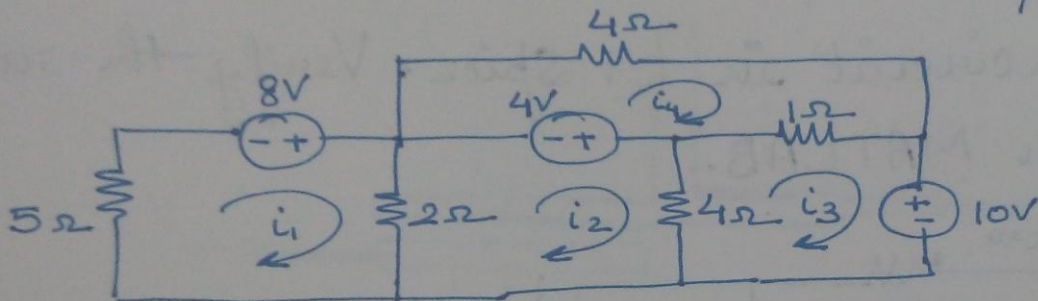
1. Simulate the circuit in LT spice and verify manually.



2. Simulate the circuit in LT spice.



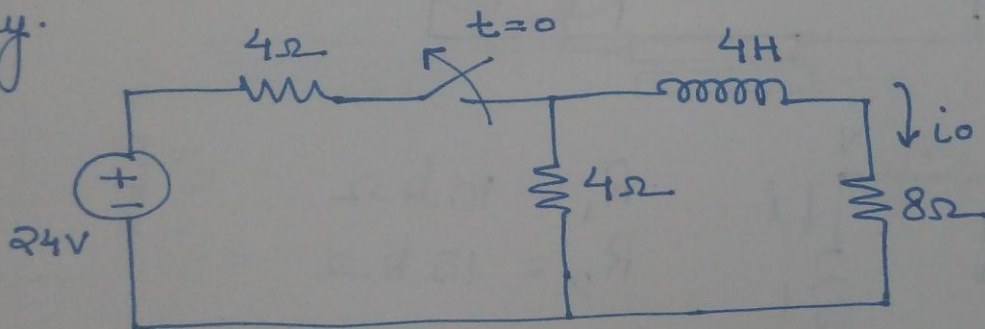3. Simulate the circuit in LT spice and verify manually.



Determine $i(t)$.

