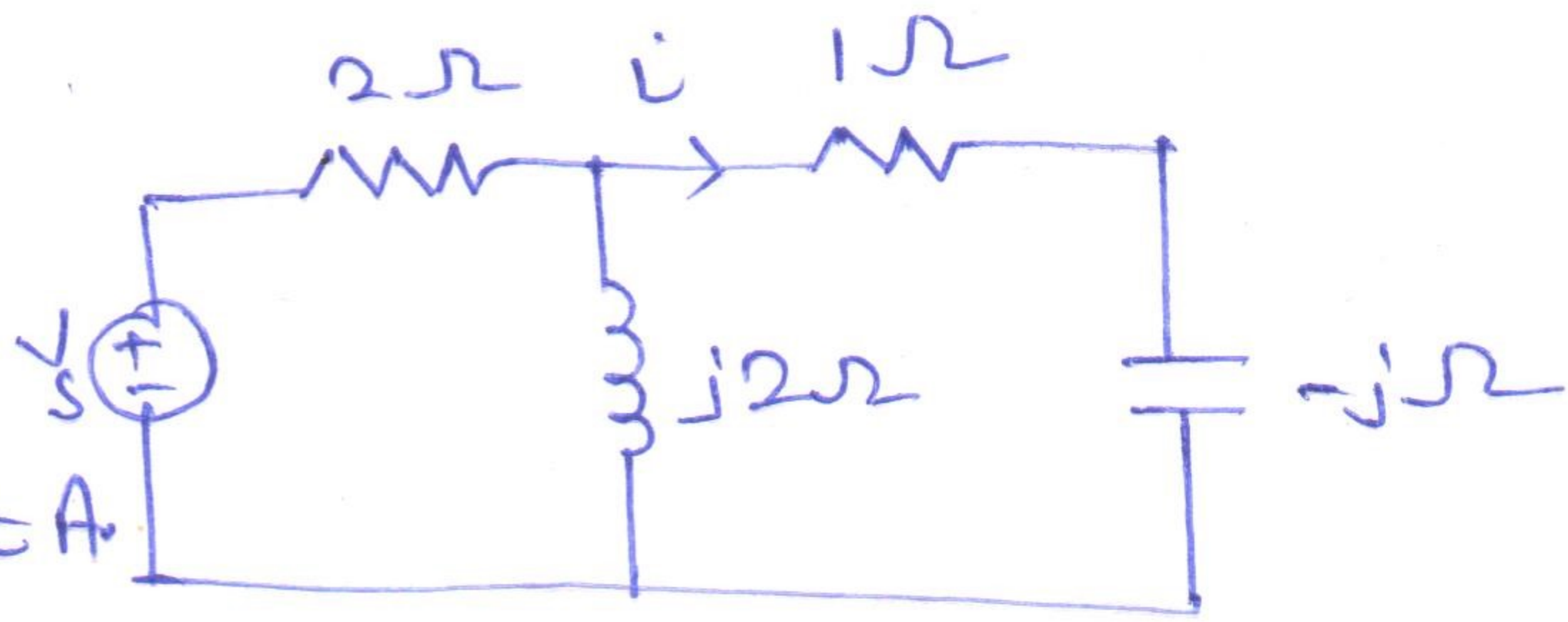


HA# 4

Q:- For this ckt. find

Plot V_s when

'i' is given as $0.5 \sin 200t$ A.



Indicate the phase lag/lead of voltage source w.r.t current, i. Also give reasoning. (10)

Q:-



For both the ckt's. plot

i & V . Also indicate

the phase lag/lead.

What inferences you conclude from the results? (10)

$10 \cos(3t + 10^\circ)$ A

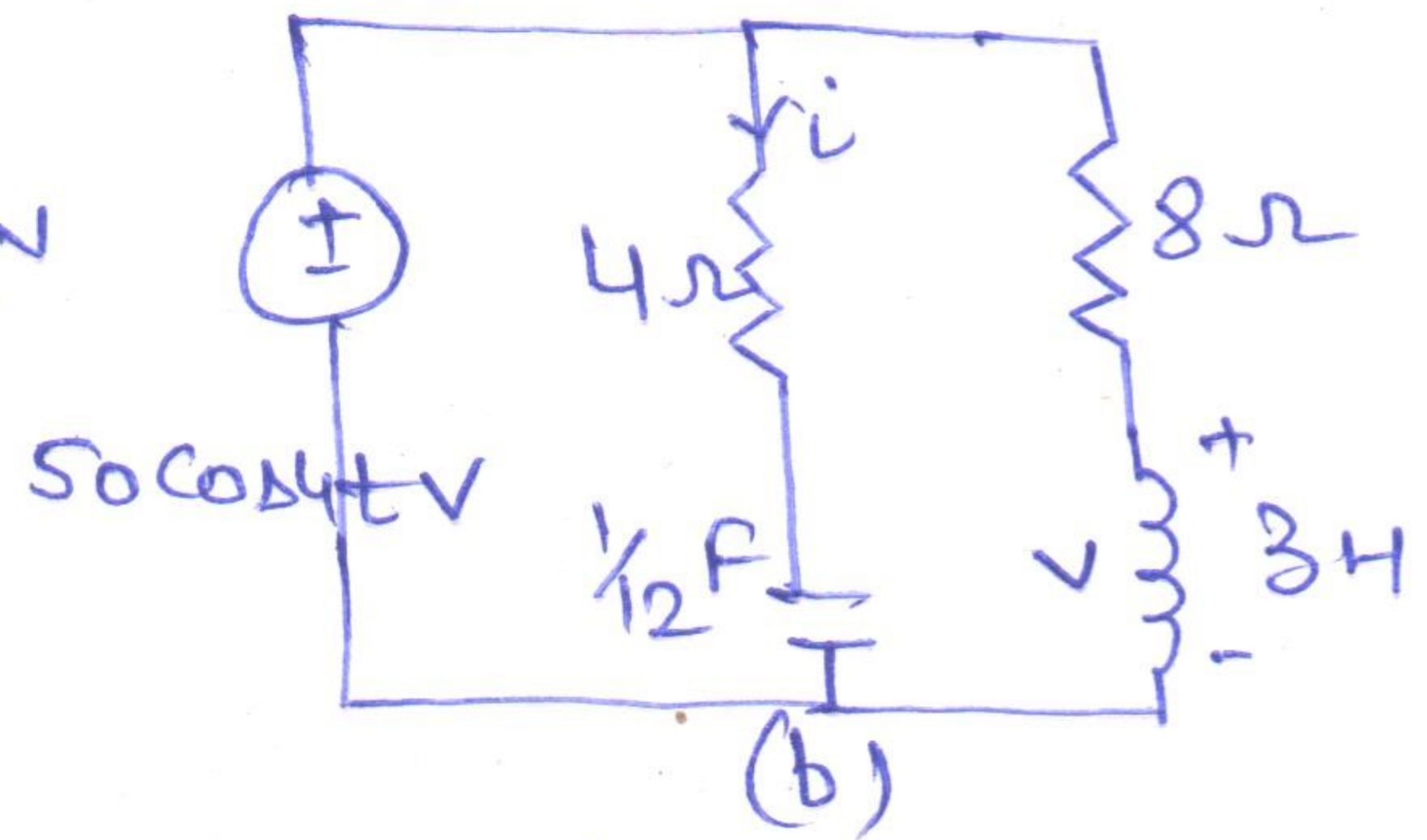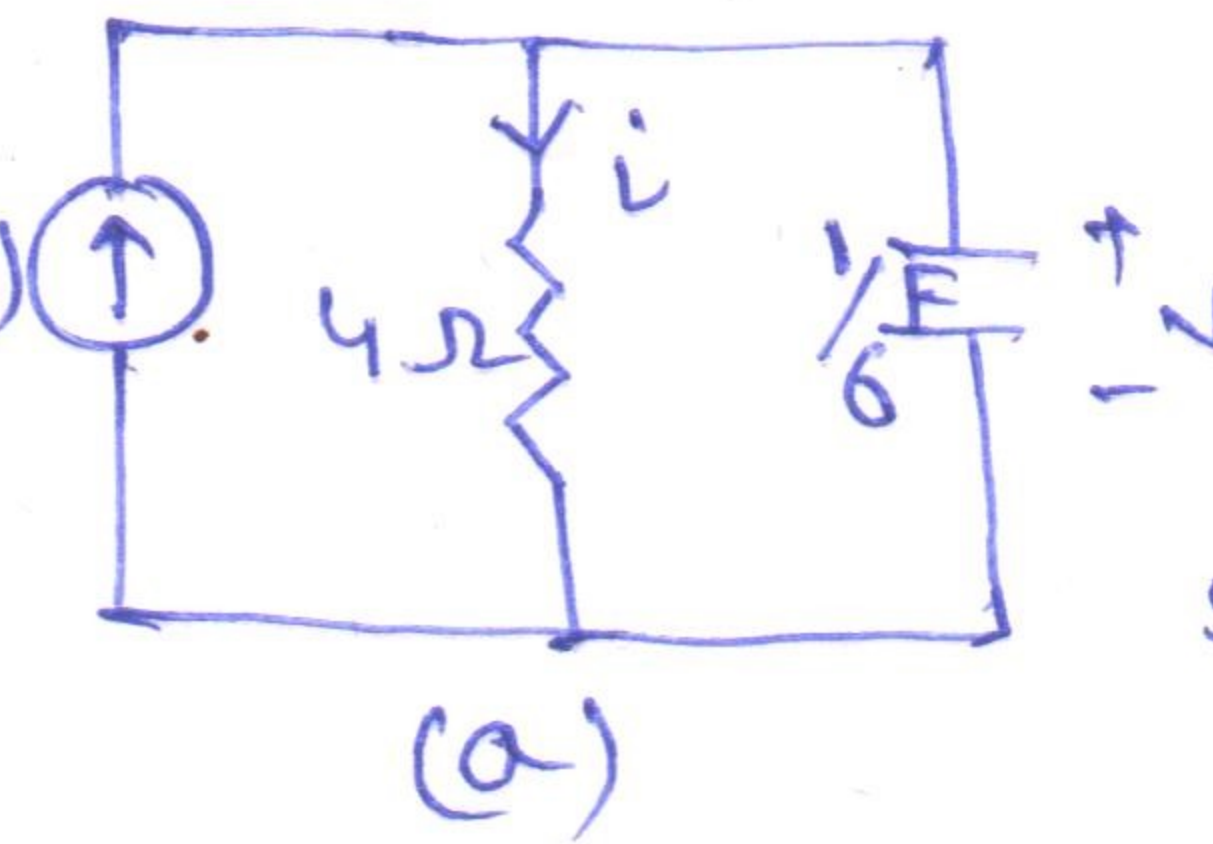

Q:- For the ckt.

deduce the

net impedance, Z_{eq} .

Now, suppose a pseudo


voltage source

drives the ckt. The

angular frequency

of the voltage source

is 100 rad/s .

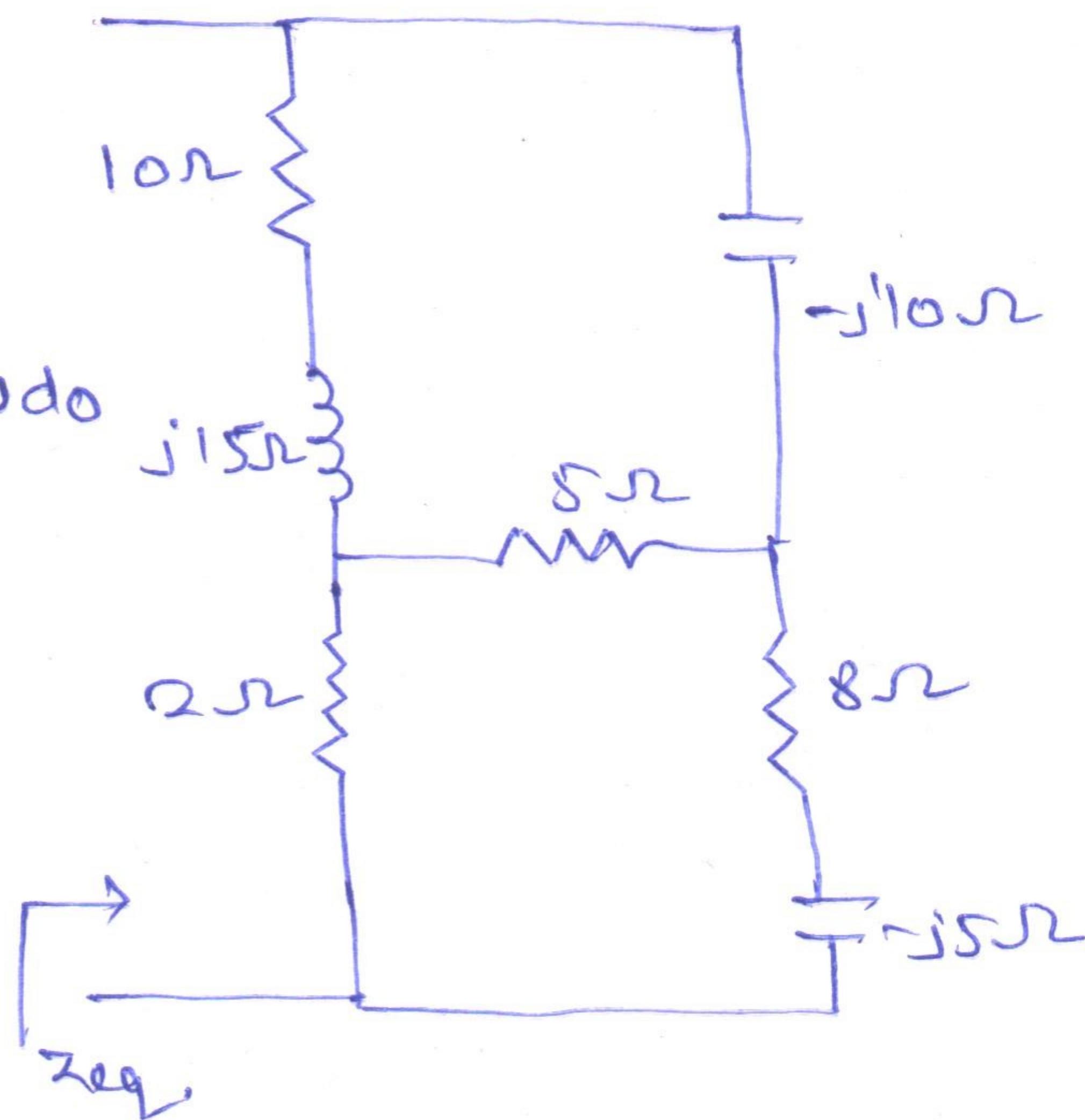

Plot current through $-j10 \Omega$, $j15 \Omega$ and voltage across $-j15 \Omega$. Indicate the phase lag/lead.