
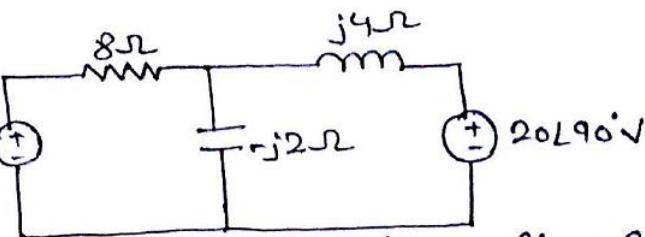


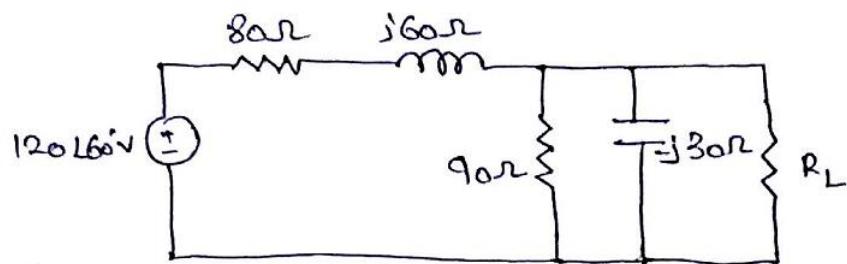Q1:- Calculate the average power absorbed by each of the five elements in the circuit. (Manually + SPICE)




Q2:-



Calculate  $R_L$  and the maximum power absorbed by it, when resistor ' $R_L$ ' is adjusted until it absorbs the maximum average power. (LTSPICE).

Q3:- Compute the average power absorbed by the  $2\Omega$  &  $4\Omega$  resistor in the circuit. (Manually)

Plot the average powers in LTSPICE-

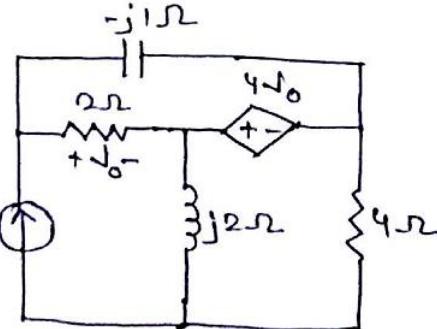

a) For  $2\Omega$  &  $4\Omega$

b) Sweep the values of resistors from 1 to  $10\Omega$ .

Q4:- Find the complex power absorbed in each of the elements.

plot the complex powers in LTSPICE.

