

## Assignment-6

Note:- There will be one surferize question.

1. Find the steady state current  $i$  flowing through circuit when (a)  $f = 60\text{Hz}$  and (b)  $f = 400\text{Hz}$ , where  $V_s = 160 \cos \omega t \text{ V}$ .

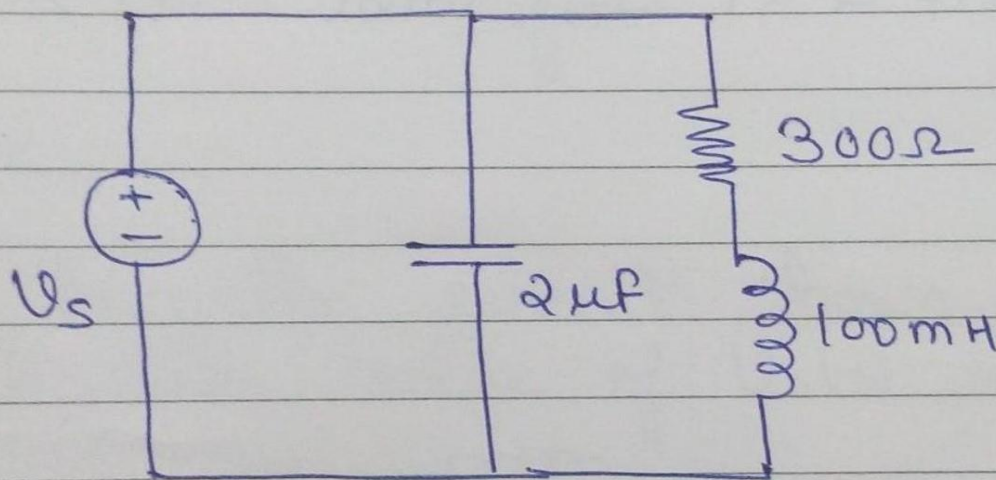


Fig: 1

2. For the circuit shown in fig 2, determine phasor currents  $I_s$ ,  $I_C$ ,  $I_L$  and  $I_R$  if  $\omega = 1000 \text{ rad/sec}$ .

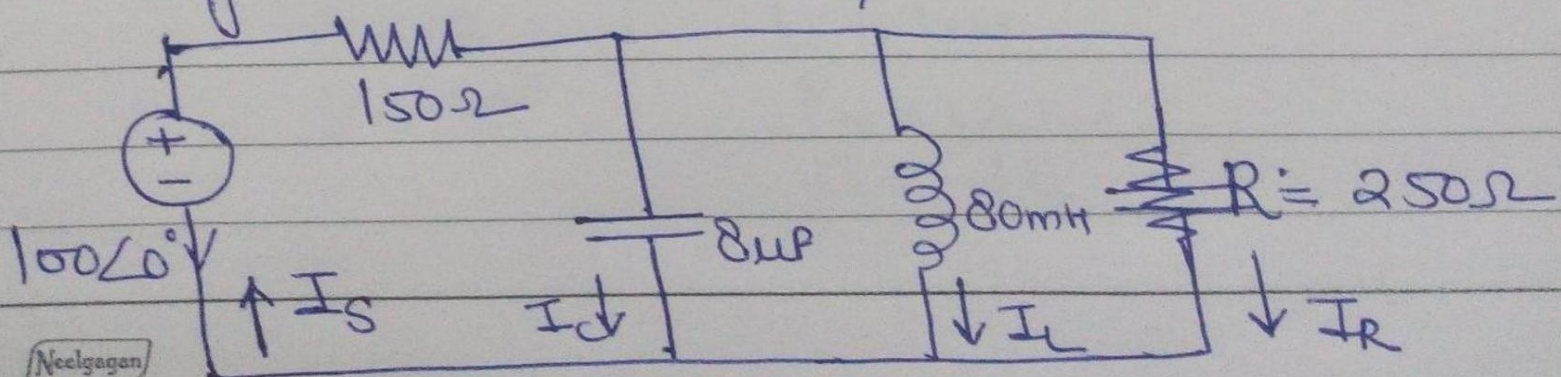


Fig: 2.



3. Find the two node voltages  $V_a(t)$  and  $V_b(t)$  for the circuit shown in fig 3 when  $V_s(t) = 1.2 \cos 4000t$ .


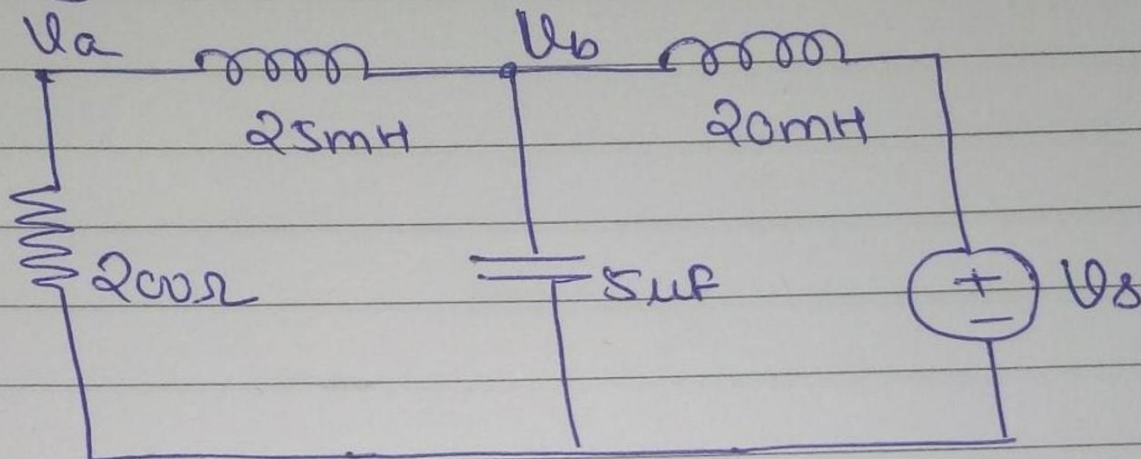


Fig 3

~~Ans~~

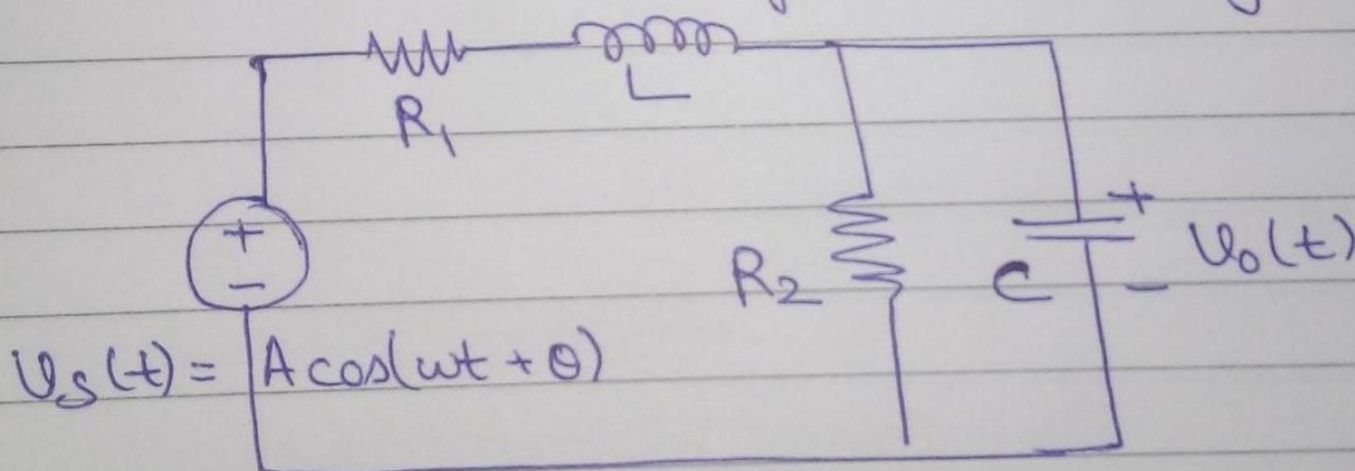4. For the circuit shown in fig 4, Calculate value of  $V_o(t)$  using MATLAB



where,  $\omega = 2$   
 $A = 12$   
 $\theta = 30^\circ$

$R_1 = 6\Omega$   
 $L = 4H$   
 $R_2 = 12\Omega$   
 $C = 1/24 F$