

## **Lecture – 14**

**Date: 25.09.2017**

- Frequency Response

## Introduction

- In sinusoidal circuit analysis, we learnt how to find voltages and currents in a circuit with a constant frequency source.
- However, if the amplitude of the sinusoidal source remain constant and the frequency is varied then one can obtain the circuit's *frequency response*.
- The frequency response may be regarded as a complete description of the sinusoidal steady-state behavior of a circuit as a function of frequency.
- The sinusoidal steady-state frequency responses of circuits are of significance in many applications, especially in communications and control systems.
- A specific application is in electric filters that block out or eliminate signals with unwanted frequencies and pass signals of the desired frequencies.
- Filters are used in radio, TV, and telephone systems to separate one broadcast frequency from another.

## Transfer Function

- The transfer function (also called the *network function*) is a useful analytical tool for finding the frequency response of a circuit.
- It is represented by  $H(\omega)$ .
- Circuit's frequency response is essentially the plot of  $H(\omega)$  when  $\omega$  varies between 0 and  $\infty$ .

$$\mathbf{H}(\omega) = \frac{\mathbf{Y}(\omega)}{\mathbf{X}(\omega)}$$



It is the frequency-dependent ratio of a phasor output  $\mathbf{Y}(\omega)$  to a phasor input  $\mathbf{X}(\omega)$ .

- Since the input and output can be either voltage or current at any place in the circuit, there are four possible transfer functions:

$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

Being a complex quantity,  $\mathbf{H}(\omega)$  has a magnitude  $H(\omega)$  and a phase  $\varphi$ .

## Transfer Function (contd.)

- The transfer function of a circuit can be obtained by first converting it to frequency-domain equivalent by replacing resistors, inductors, and capacitors with their impedances  $R$ ,  $j\omega L$  and  $1/j\omega C$ .
- One can then use any circuit technique(s) to obtain the appropriate expressions.
- Can be simplified to:

$$\mathbf{H}(\omega) = \frac{\mathbf{N}(\omega)}{\mathbf{D}(\omega)}$$




The roots of  $\mathbf{N}(\omega)$  are called the *zeros* and are usually represented as  $j\omega = z_1, z_2, \dots$ . Similarly, the roots of  $\mathbf{D}(\omega)$  are the *poles* and are represented as  $j\omega = p_1, p_2, \dots$ .

A zero is a value that results in a zero value of the function. A pole is a value for which the function is infinite.


To avoid complex algebra, it is expedient to replace temporarily  $j\omega$  with  $s$  when working with  $\mathbf{H}(\omega)$  and replace  $s$  with  $j\omega$  at the end.
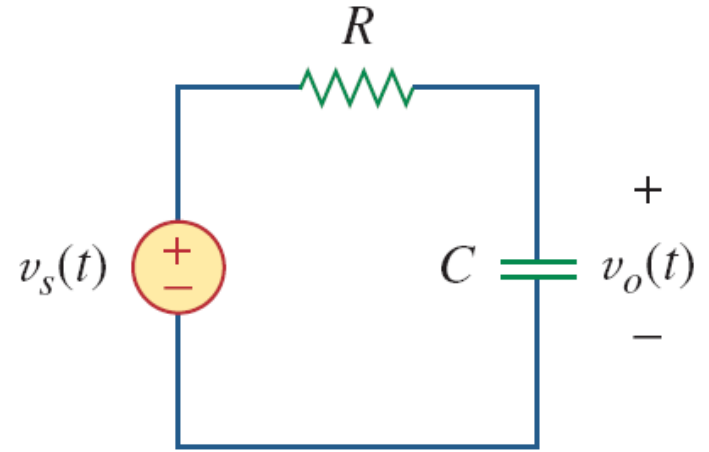
## Example – 1

Find the transfer function  $\frac{V_o}{V_s}$  and the corresponding frequency response of this  $RC$  circuit. Assume,  $v_s = V_m \cos \omega t$ .



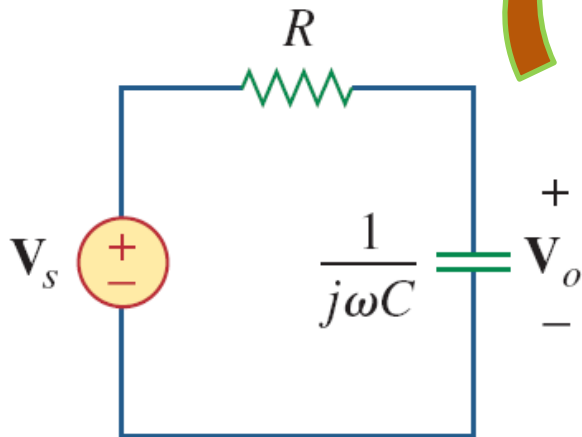The frequency-domain equivalent of the circuit:



the transfer function



$$H(\omega) = \frac{V_o}{V_s} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

$$H = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}, \quad \phi = -\tan^{-1} \frac{\omega}{\omega_0}$$

where  $\omega_0 = \frac{1}{RC}$ . For plotting  $H$  and  $\phi$  for  $0 < \omega < \infty$ , we need values at some critical points.




## Example – 1 (contd.)

$\omega/\omega_0$	$H$	$\phi$	$\omega/\omega_0$	$H$	$\phi$
0	1	0	10	0.1	$-84^\circ$
1	0.71	$-45^\circ$	20	0.05	$-87^\circ$
2	0.45	$-63^\circ$	100	0.01	$-89^\circ$
3	0.32	$-72^\circ$	$\infty$	0	$-90^\circ$

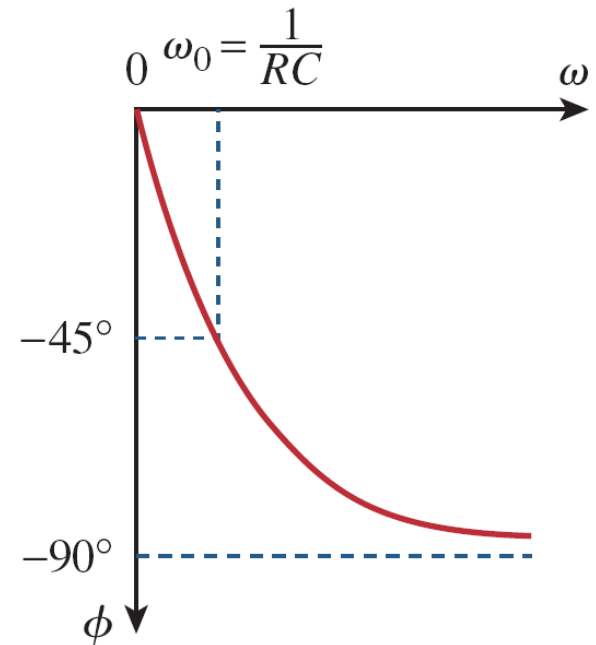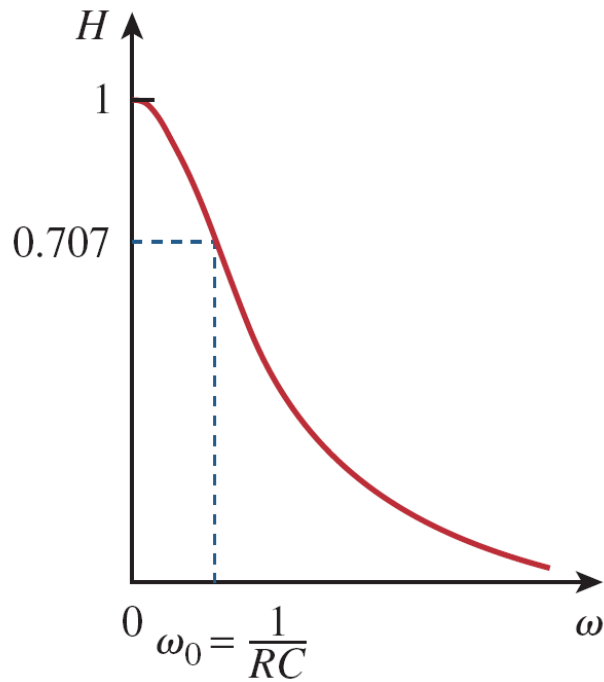
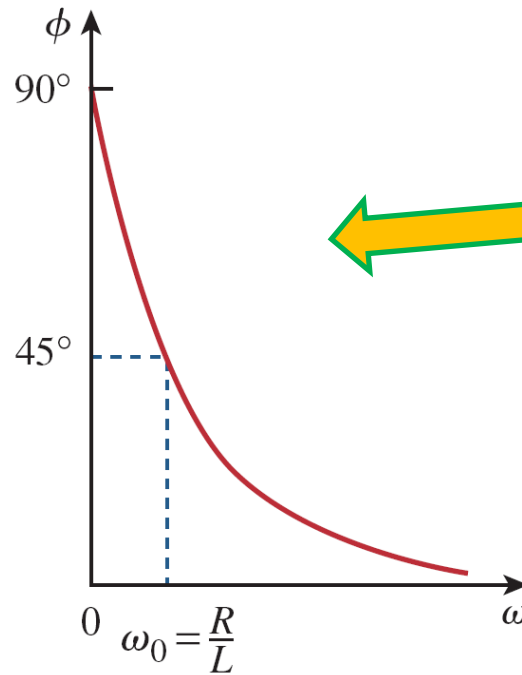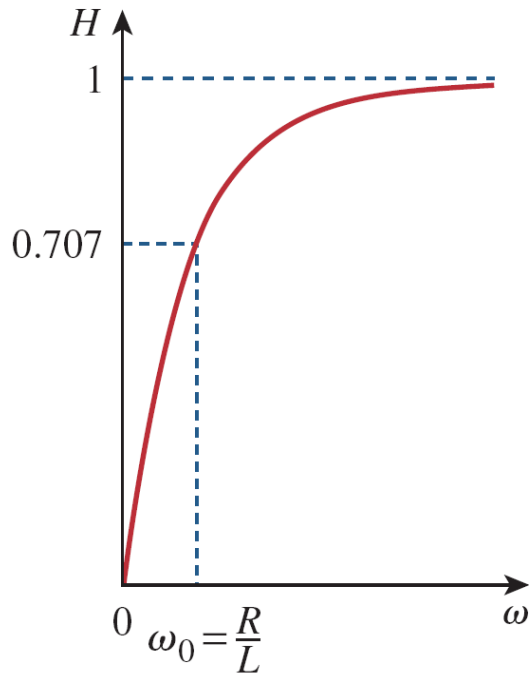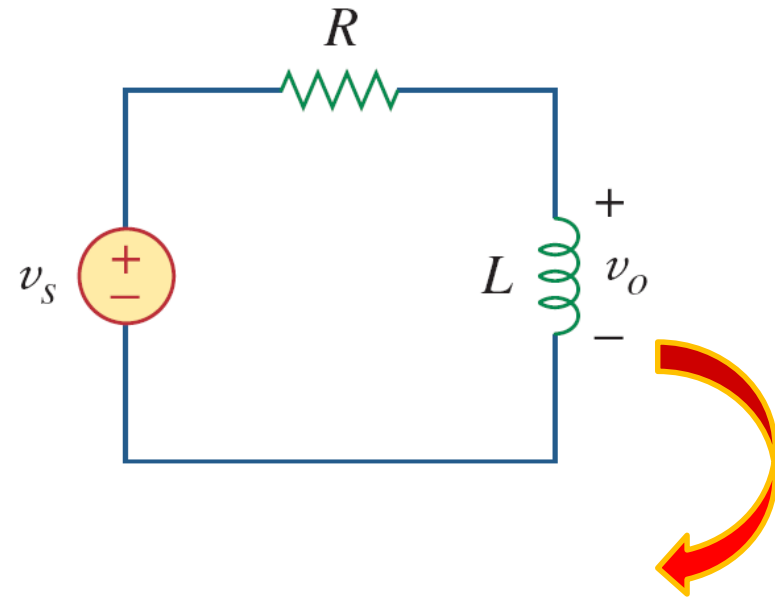
## Example – 2


Find the transfer function  $\frac{V_0}{V_S}$  and the corresponding frequency response of this  $RL$  circuit. Assume,  $v_s = V_m \cos \omega t$ .



$$H(\omega) = \frac{V_0}{V_S} = \frac{j\omega L}{R + j\omega L}$$

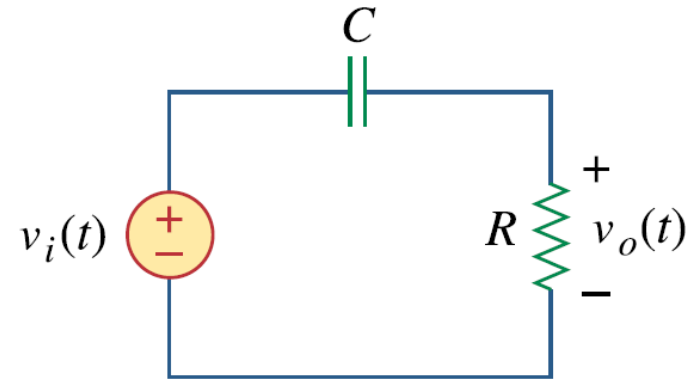
### Example – 3

Find the transfer function  $\frac{V_o}{V_s}$  and the corresponding frequency response of this  $RC$  circuit. Assume,  $\omega_0 = \frac{1}{RC}$ .



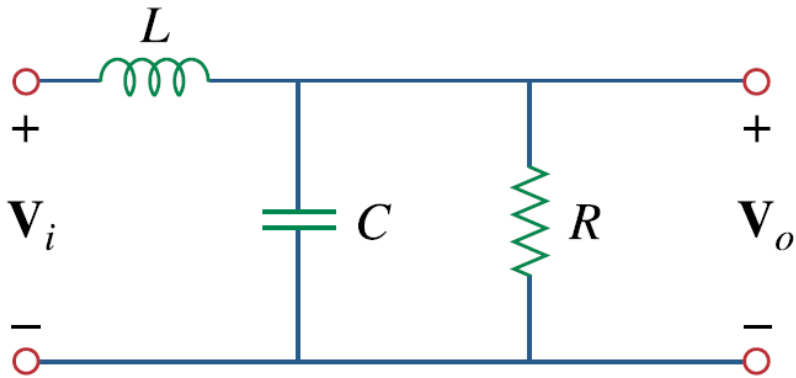
### Example – 4

Find the transfer function  $\frac{V_o}{V_i}$  of the following circuits.



(a)

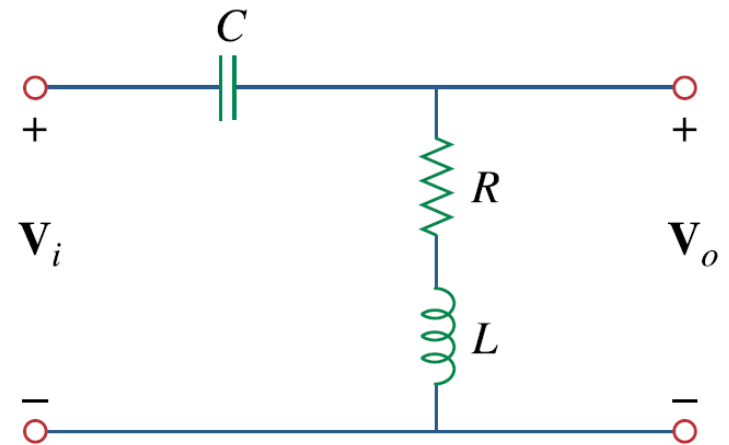


(b)


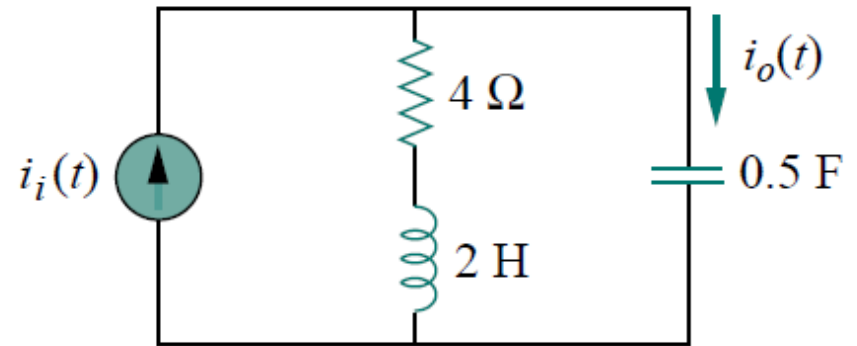
## Example – 5

For this circuit, calculate the gain  $\frac{I_o(\omega)}{I_i(\omega)}$  and its poles and zeros.



## Example – 6

For this circuit, calculate the gain  $\frac{V_o(\omega)}{I_i(\omega)}$  and its poles and zeros.

