

## **Lecture – 18**

**Date: 10.10.2017**

- Examples
- Active Filters
- Scaling

## Passive Filter – Summary


- the maximum gain of a passive filter is unity. To generate a gain greater than unity, one should use an active filter.
- There are other ways to get the types of filters.
- The filters discussed here are the simple types. Many other filters have sharper and complex frequency responses.

### Example – 4

Show that a series  $LR$  circuit is a lowpass filter if the output is taken across the resistor. Calculate the corner frequency  $f_c$  if  $L = 2$  mH and  $R = 10$  k $\Omega$ .
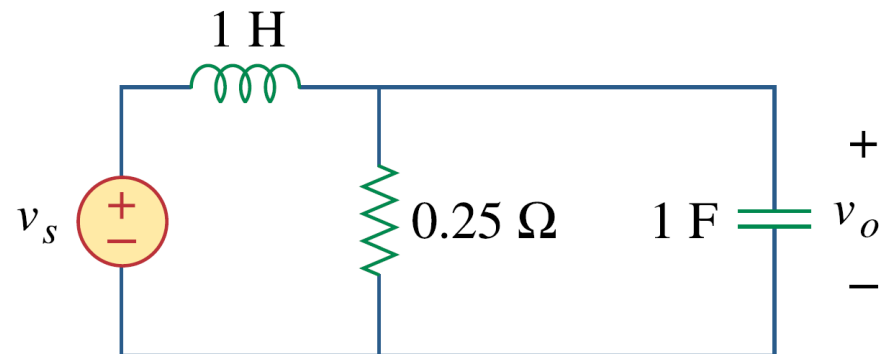
### Example – 5

Find the transfer function  $V_o/V_s$  of the circuit. Show that the circuit is a lowpass filter.



### Example – 6

In a highpass  $RL$  filter with a cutoff frequency of 100 kHz,  $L = 40$  mH. Find  $R$ .

### Example – 7


Design a series  $RLC$  type bandpass filter with cutoff frequencies of 10 kHz and 11 kHz. Assuming  $C = 80$  pF, find  $R$ ,  $L$ , and  $Q$ .

### Example – 8

Determine the range of frequencies that will be passed by a series  $RLC$  bandpass filter with  $R = 10 \Omega$ ,  $L = 25$  mH, and  $C = 0.4 \mu\text{F}$ . Find the quality factor.
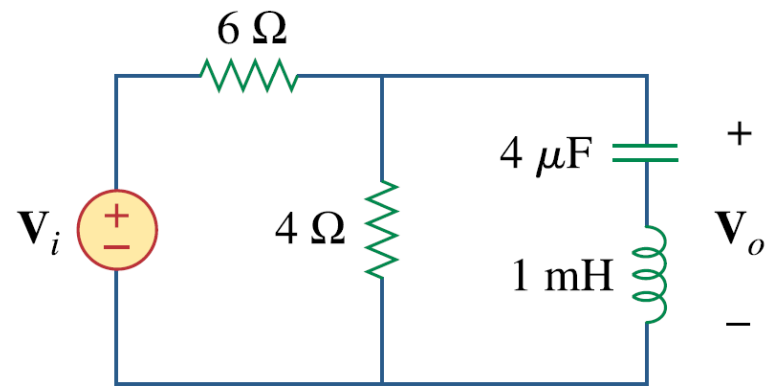
### Example – 9

Find the bandwidth and center frequency of the bandstop filter



## Active Filter

- There are three major limitations to the passive filters:
  - cannot generate gain greater than 1 → passive elements cannot add energy to the network.
  - may require bulky and expensive inductors.
  - perform poorly at freqs below the audio frequency range ( $300\text{Hz} < f < 3000\text{Hz}$ ) → passive filters are useful at high freqs.


### Active filters:

- consist of combinations of resistors, capacitors, and op amps.
- are often smaller and less expensive, because they do not require inductors → This enables realizations of filters ICs
- can provide gain in addition to providing the same frequency response as *RLC* filters.
- can be combined with buffer amplifiers (voltage followers) to isolate each stage of the filter from source and load impedance effects → allows designing the stages independently and then cascading them to realize the desired transfer function.

## Active Filter

- Active filters are less reliable and less stable.
- The practical limit of most active filters is about 100 kHz → most active filters operate well below that frequency.
- These filters are often classified according to their order (or number of poles) or their specific design type.

## First Order Low Pass Filter

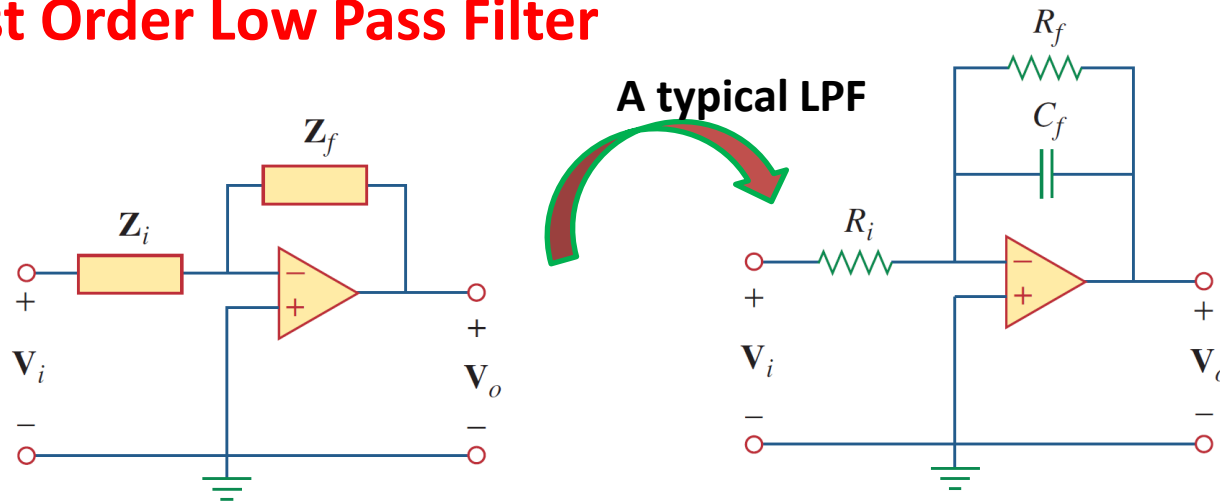

$$H(\omega) = \frac{V_o}{V_i} = - \frac{Z_f}{Z_i}$$

$$Z_i = R_i$$


$$Z_f = R_f \parallel \frac{1}{j\omega C_f} \\ = \frac{R_f}{1 + j\omega C_f R_f}$$

- The components selected for  $Z_f$  and  $Z_i$  determine if its a lowpass or highpass
- but one of the components must be reactive.


## First Order Low Pass Filter

$$\mathbf{H}(\omega) = -\frac{R_f}{R_i} \frac{1}{1 + j\omega C_f R_f}$$

Similar to passive LPF expression  $\rightarrow$  except that there is a low frequency ( $\omega \rightarrow 0$ ) gain or dc gain of  $-\frac{R_f}{R_i}$ .

the corner frequency is:  $\omega_c = \frac{1}{R_f C_f}$   Independent of  $R_i$

## First Order High Pass Filter

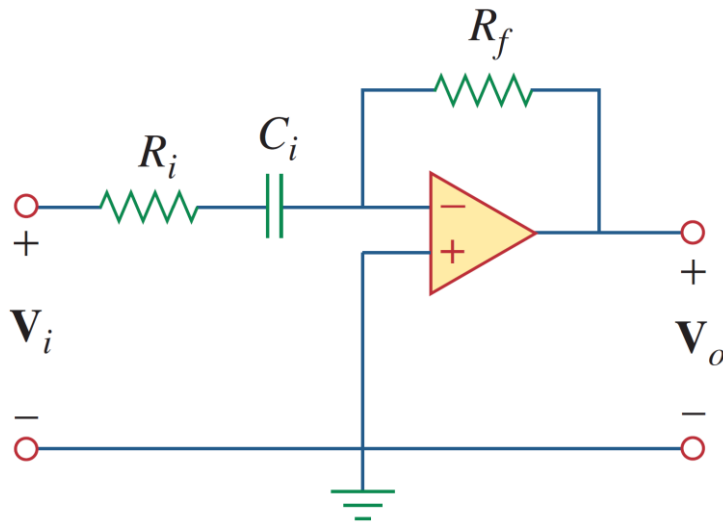

$$\mathbf{H}(\omega) = \frac{V_o}{V_i} = -\frac{Z_f}{Z_i}$$




$$\mathbf{H}(\omega) = -\frac{R_f}{R_i + 1/j\omega C_i} = -\frac{j\omega C_i R_f}{1 + j\omega C_i R_i}$$

At high frequency ( $\omega \rightarrow \infty$ ), the gain tends to  $-\frac{R_f}{R_i}$ .

the corner frequency is:  $\omega_c = \frac{1}{R_i C_i}$
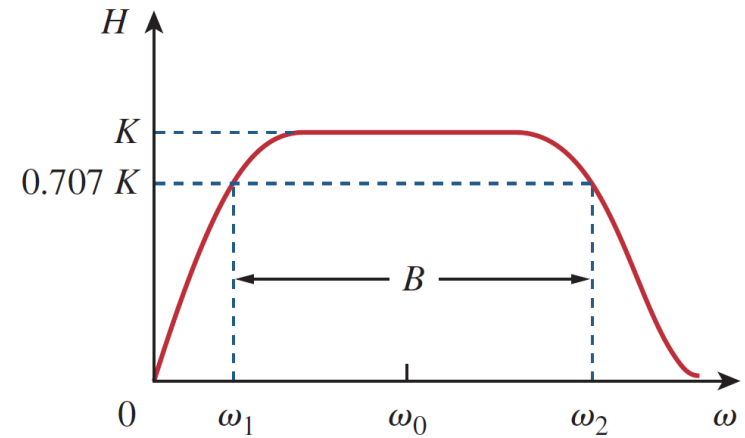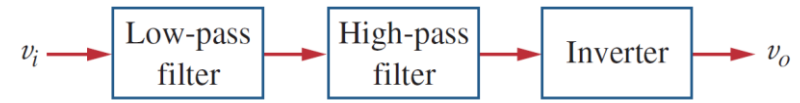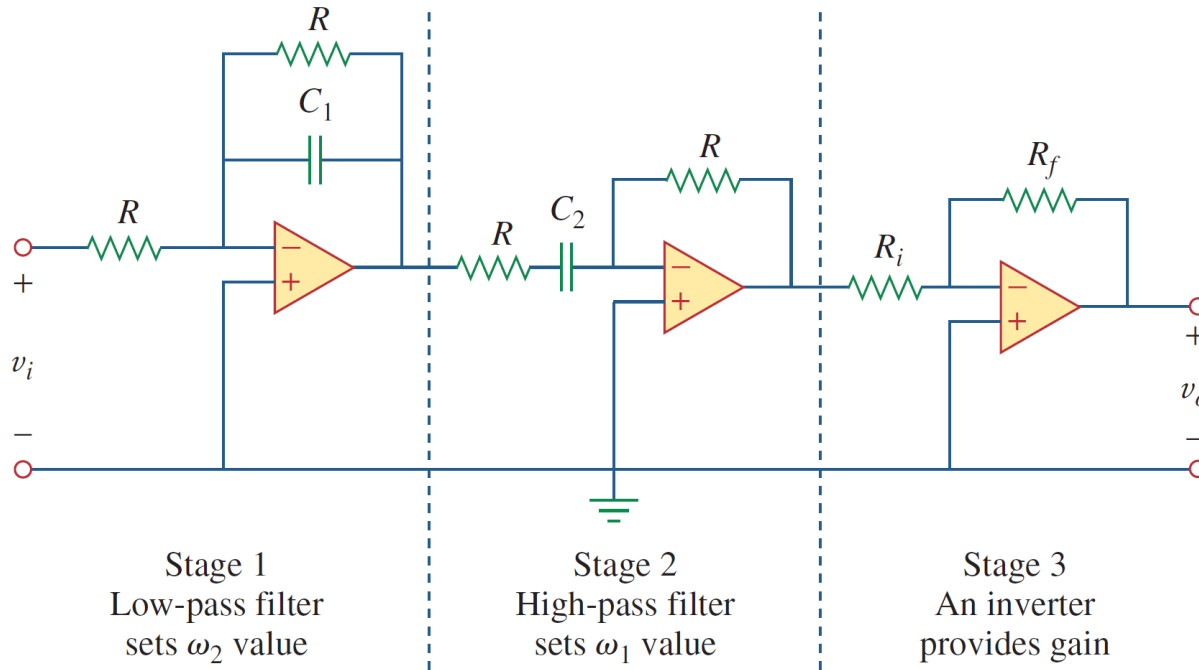
# Band Pass Filter

- LPF and HPF can be combined to form a BPF
- By cascading a unity-gain LPF, a unity-gain HPF, and an inverter with gain  $-\frac{R_f}{R_i}$



$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}$$

$$= \left( -\frac{1}{1 + j\omega C_1 R} \right) \left( -\frac{j\omega C_2 R}{1 + j\omega C_2 R} \right) \left( -\frac{R_f}{R_i} \right)$$

## Band Pass Filter

$$\mathbf{H}(\omega) = -\frac{R_f}{R_i} \frac{1}{1 + j\omega C_1 R} \frac{j\omega C_2 R}{1 + j\omega C_2 R}$$

- the high pass section sets the lower corner frequency:

- Once the values of  $\omega_1$  and  $\omega_2$  are known, the center frequency, bandwidth, and quality factor are:

- The low pass section sets the upper corner frequency:

$$\omega_2 = \frac{1}{RC_1}$$

$$\omega_1 = \frac{1}{RC_2}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2} \quad B = \omega_2 - \omega_1 \quad Q = \frac{\omega_0}{B}$$

- Passband gain  $K$ : 
$$\mathbf{H}(\omega) = \frac{-K j\omega/\omega_1}{(1 + j\omega/\omega_1)(1 + j\omega/\omega_2)} = \frac{-K j\omega\omega_2}{(\omega_1 + j\omega)(\omega_2 + j\omega)}$$

- At  $\omega_0$ : 
$$H(\omega_0) = \left| \frac{-K j\omega_0\omega_2}{(\omega_1 + j\omega_0)(\omega_2 + j\omega_0)} \right| = \frac{K\omega_2}{\omega_1 + \omega_2} \quad \overset{\text{green arrow}}{\Rightarrow} \quad \frac{K\omega_2}{\omega_1 + \omega_2} = \frac{R_f}{R_i}$$




then gain  $K$  can be determined


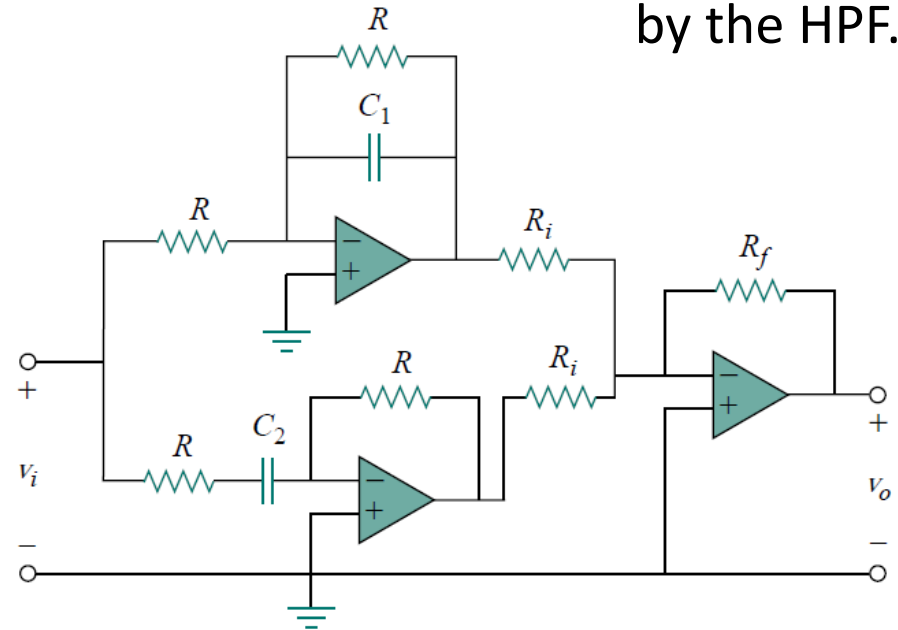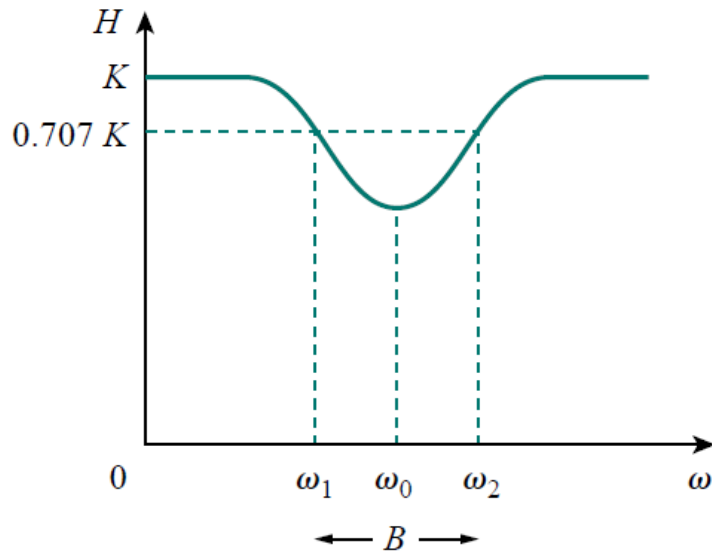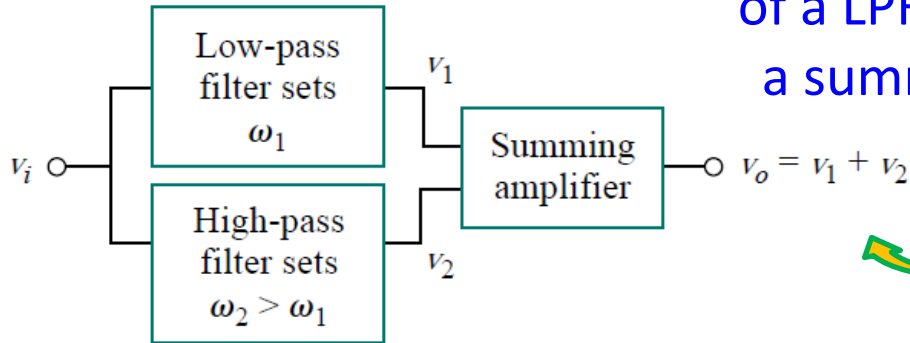
# Band Reject Filter

parallel combination  
of a LPF and a BPF and  
a summing amplifier

You design it so that  
the lower cutoff  
frequency  $\omega_1$  is set  
by the LPF while the  
upper cutoff  
frequency  $\omega_2$  is set  
by the HPF.



$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = -\frac{R_f}{R_i} \left( -\frac{1}{1 + j\omega C_1 R} - \frac{j\omega C_2 R}{1 + j\omega C_2 R} \right)$$

## Band Reject Filter

The formulas for calculating the values of  $\omega_1$ ,  $\omega_2$ , the center frequency, bandwidth, and quality factor are similar to the BPF

- To determine the pass band gain  $K$  of the filter:

$$\mathbf{H}(\omega) = \frac{R_f}{R_i} \left( \frac{1}{1 + j\omega/\omega_2} + \frac{j\omega/\omega_1}{1 + j\omega/\omega_1} \right) = \frac{R_f}{R_i} \frac{(1 + j2\omega/\omega_1 + (j\omega)^2/\omega_1\omega_1)}{(1 + j\omega/\omega_2)(1 + j\omega/\omega_1)}$$

- For the two pass bands ( $\omega \rightarrow 0$  and  $\omega \rightarrow \infty$ ) the gain is:  $K = \frac{R_f}{R_i}$



- We can also find the gain at the  $\omega_0$  by finding the magnitude:

$$H(\omega_0) = \left| \frac{R_f}{R_i} \frac{(1 + j2\omega_0/\omega_1 + (j\omega_0)^2/\omega_1\omega_1)}{(1 + j\omega_0/\omega_2)(1 + j\omega_0/\omega_1)} \right|$$
$$= \frac{R_f}{R_i} \frac{2\omega_1}{\omega_1 + \omega_2}$$

Again, the filters treated in this section are only typical. There are many other active filters that are more complex.
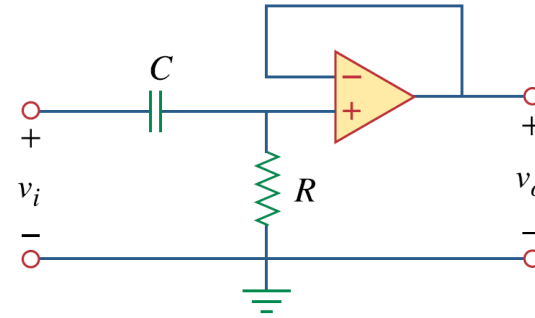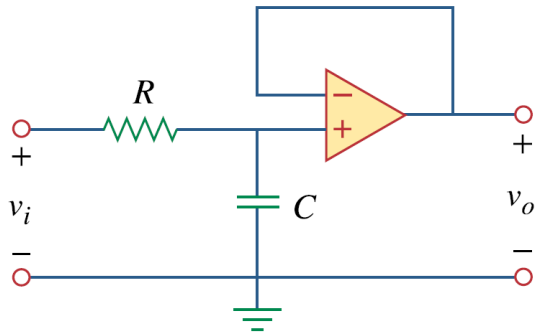
## Example – 10

Find the transfer function for each of the following active filters



## Example – 11

Design an active first-order high pass filter with:

$$\mathbf{H}(s) = -\frac{100s}{s + 10},$$

$$s = j\omega$$

Use a 1- $\mu\text{F}$  capacitor.


## Example – 12

A filter is given.

Show that the transfer function is:

$$\mathbf{H}(\omega) = \left(1 + \frac{R_f}{R_i}\right) \frac{j\omega RC}{1 + j\omega RC}$$

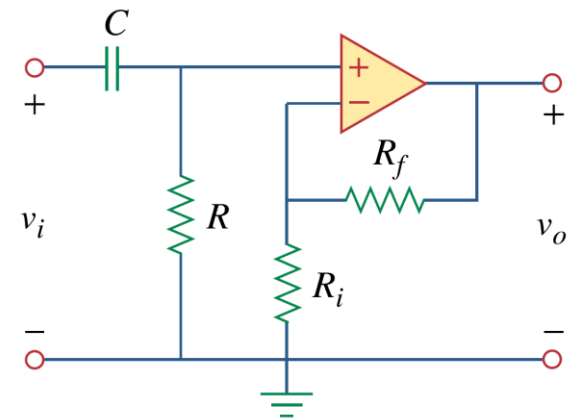What type of filter is this? What is the corner frequency



## Example – 13


A “general” first-order filter is shown.

(a) Show that the transfer function is:

$$\mathbf{H}(s) = \frac{R_4}{R_3 + R_4} \times \frac{s + (1/R_1 C)[R_1/R_2 - R_3/R_4]}{s + 1/R_2 C}$$

(b) What condition must be satisfied for the circuit to operate as a highpass filter?

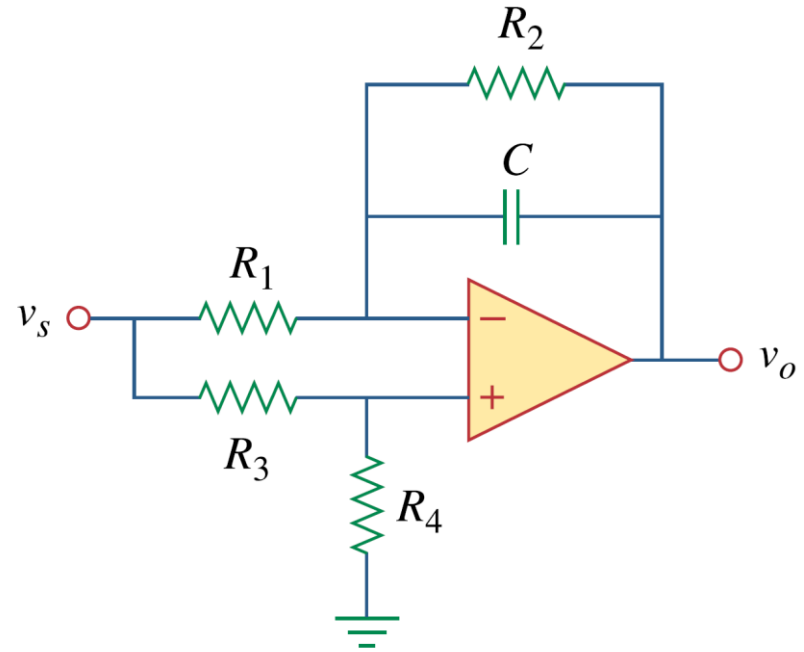(c) What condition must be satisfied for the circuit to operate as a lowpass filter?




## Example – 14

A second-order active filter is given.

(a) Find the transfer function.

(b) Show that it is a lowpass filter.

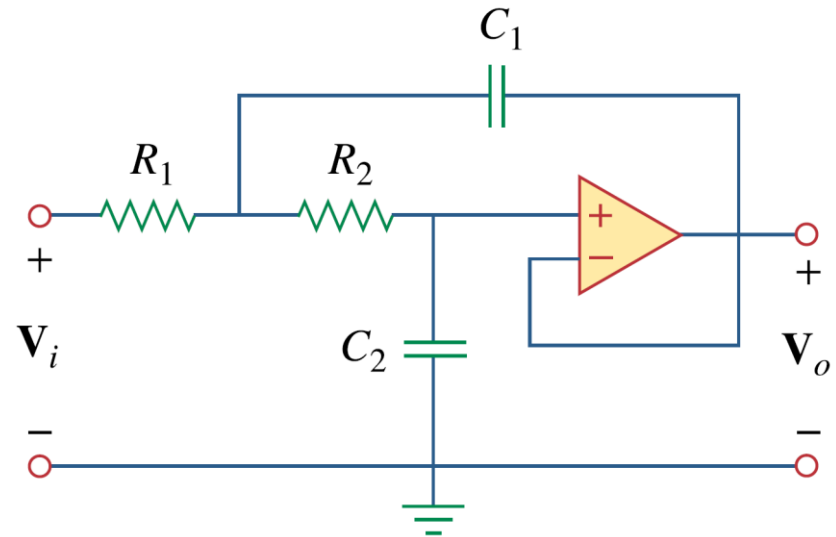

## Scaling

- In the design and analysis of filters and resonant circuits, it is often convenient to work with element values of  $1\Omega$ ,  $1H$ , or  $1F$ , and then transform the values to realistic values by **scaling**.
- There are two ways of scaling a circuit: *magnitude* or *impedance scaling*, and *frequency scaling*.
- Magnitude scaling leaves the frequency response of a circuit unaltered, while frequency scaling shifts the frequency response up or down the frequency spectrum.

## Magnitude Scaling

- **Magnitude scaling** is the process of increasing all impedances in a network by a factor, the frequency response remaining unchanged.

- The impedances of individual elements  $R$ ,  $L$ , and  $C$  are:

$$\mathbf{Z}_R = R, \quad \mathbf{Z}_L = j\omega L, \quad \mathbf{Z}_C = \frac{1}{j\omega C}$$

- Then impedance of each circuit element is multiplied by a factor  $K_m$  and while the frequency remain constant.

$$\mathbf{Z}'_R = K_m \mathbf{Z}_R = K_m R,$$

$$\mathbf{Z}'_L = K_m \mathbf{Z}_L = j\omega K_m L$$

$$\mathbf{Z}'_C = K_m \mathbf{Z}_C = \frac{1}{j\omega C / K_m}$$

## Magnitude Scaling

- In magnitude scaling, the new values of the elements and frequency are:

$$\begin{aligned} R' &= K_m R, & L' &= K_m L \\ C' &= \frac{C}{K_m}, & \omega' &= \omega \end{aligned}$$

**primed variables: new values**

- For the series or parallel *RLC* circuit:

$$\omega'_0 = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{K_m LC / K_m}} = \frac{1}{\sqrt{LC}} = \omega_0$$

Similarly, it can be shown that the quality factor and the bandwidth are not affected by magnitude scaling.

## Frequency Scaling

It is the process of shifting the frequency response of a network up or down the frequency axis while leaving the impedance the same.

**It is achieved by multiplying the frequency by a factor  $K_f$  while keeping the impedance the same.**

## Frequency Scaling

Application of frequency scaling to  $Z_L(\omega)$  and  $Z_C(\omega)$  leads to:

$$\mathbf{Z}_L = j(\omega K_f)L' = j\omega L \quad \Rightarrow \quad L' = \frac{L}{K_f}$$
$$\mathbf{Z}_C = \frac{1}{j(\omega K_f)C'} = \frac{1}{j\omega C} \quad \Rightarrow \quad C' = \frac{C}{K_f}$$

- In frequency scaling, the new values of the elements and frequency are

$$R' = R, \quad L' = \frac{L}{K_f}$$
$$C' = \frac{C}{K_f}, \quad \omega' = K_f \omega$$

- For the series or parallel *RLC* circuit:

$$\omega'_0 = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{(L/K_f)(C/K_f)}} = \frac{K_f}{\sqrt{LC}} = K_f \omega_0 \quad B' = K_f B$$

**the quality factor remains**

## Frequency and Magnitude Scaling

$$R' = K_m R, \quad L' = \frac{K_m}{K_f} L$$
$$C' = \frac{1}{K_m K_f} C, \quad \omega' = K_f \omega$$

We set  $K_m = 1$  when there is no magnitude scaling or  $K_f = 1$  when there is no frequency scaling.

### Example – 15

What values of  $K_m$  and  $K_f$  will scale a 4-mH inductor and a 20- $\mu$ F capacitor to 1H and 2F respectively?

### Example – 16

- (a) Find  $\mathbf{Z}_{in}(s)$ .
- (b) Scale the elements by  $K_m = 10$  and  $K_f = 100$ . Find  $\mathbf{Z}_{in}(s)$  and  $\omega_0$ .

