

## **Lecture – 24**

**Date: 31.10.2017**


- Multi-port networks (Contd.), Scattering Matrix
- Matched, Lossless, and Reciprocal Networks

# Scattering Matrix

- At “**low**” frequencies, a **linear** device or network can be fully characterized using an **impedance or admittance** matrix, which relates the currents and voltages at **each** device terminal to the currents and voltages at **all** other terminals.
- But, at high frequencies, it is **not feasible** to measure total currents and voltages!
- Instead, we can measure the **magnitude** and **phase** of each of the two transmission line **waves**  $V^+(z)$  and  $V^-(z)$  → enables determination of relationship between the incident and reflected waves at **each** device terminal to the incident and reflected waves at **all** other terminals
- These relationships are completely represented by the **scattering matrix** that **completely** describes the behavior of a linear, multi-port device at a **given frequency**  $\omega$ , and a given line impedance  $Z_0$
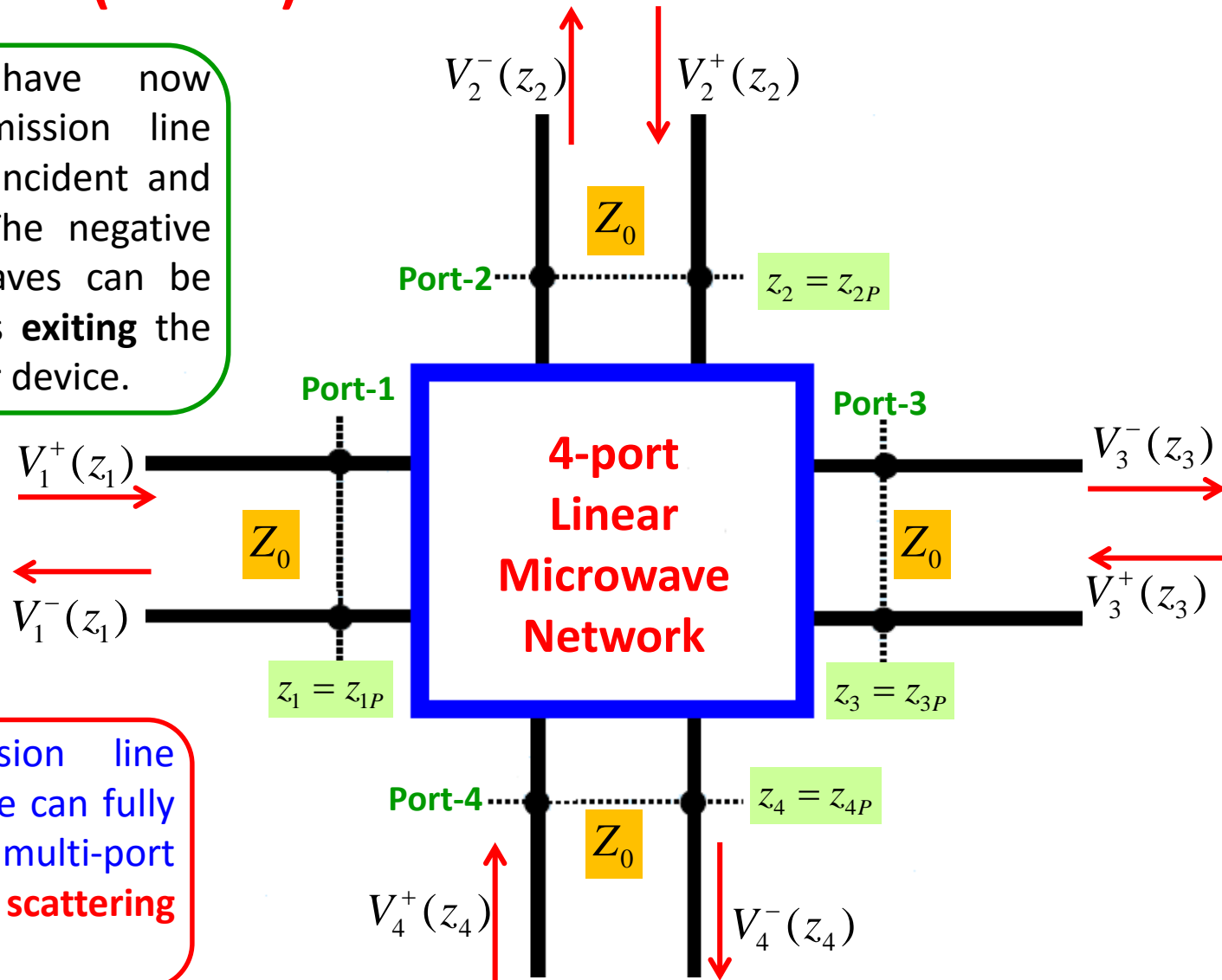
# Scattering Matrix (contd.)


Note that we have now characterized transmission line activity in terms of incident and “reflected” waves. The negative going “reflected” waves can be viewed as the waves **exiting** the multi-port network or device.



Viewing transmission line activity this way, we can fully characterize a multi-port device by its **scattering parameters!**

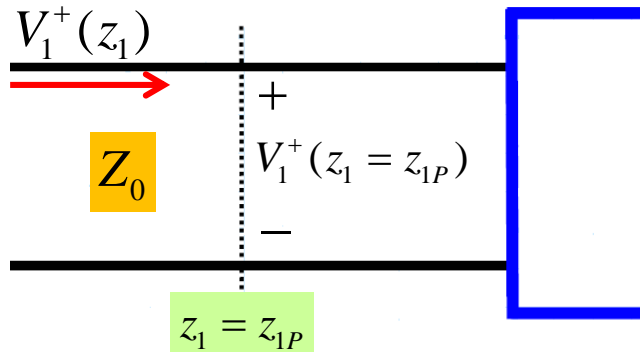
## Scattering Matrix (contd.)

- Say there exists an **incident** wave on **port 1** (i.e.,  $V_1^+(z_1) \neq 0$ ), while the incident waves on all other ports are known to be **zero** (i.e.,  $V_2^+(z_2) = V_3^+(z_3) = V_4^+(z_4) = 0$ ).



Say we measure/determine the voltage of the wave flowing **into port 1**, at the port 1 plane (i.e., determine  $V_1^+(z_1 = z_{1P})$ ).

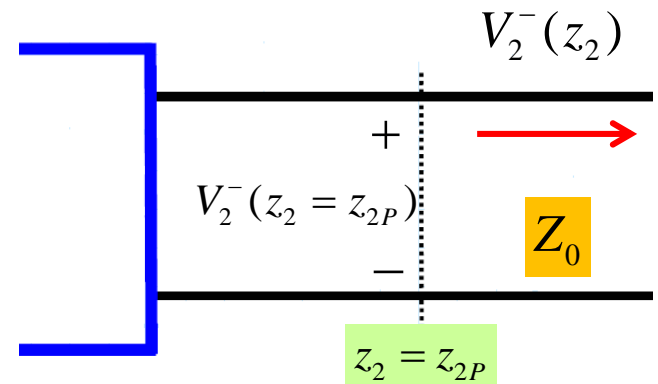Say we then measure/determine the voltage of the wave flowing **out of port 2**, at the port 2 plane (i.e., determine  $V_2^-(z_2 = z_{2P})$ ).



The complex ratio between  $V_1^+(z_1 = z_{1P})$  and  $V_2^-(z_2 = z_{2P})$  is known as the **scattering parameter**  $S_{21}$

## Scattering Matrix (contd.)

Therefore:

$$S_{21} = \frac{V_2^-(z_2 = z_{2P})}{V_1^+(z_1 = z_{1P})} = \frac{V_2^- e^{+j\beta z_{2P}}}{V_1^+ e^{-j\beta z_{1P}}} = \frac{V_2^-}{V_1^+} e^{+j\beta(z_{2P} + z_{1P})}$$

Similarly:

$$S_{31} = \frac{V_3^-(z_3 = z_{3P})}{V_1^+(z_1 = z_{1P})}$$

$$S_{41} = \frac{V_4^-(z_4 = z_{4P})}{V_1^+(z_1 = z_{1P})}$$

- We of course could **also** define, say, scattering parameter  $S_{34}$  as the ratio between the complex values  $V_3^-(z_3 = z_{3P})$  (the wave **out of** port 3) and  $V_4^+(z_4 = z_{4P})$  (the wave **into** port 4), given that the input to all other ports (1, 2, and 3) are zero
- Thus, more **generally**, the ratio of the wave incident on port **n** to the wave emerging from port **m** is:

$$S_{mn} = \frac{V_m^-(z_m = z_{mP})}{V_n^+(z_n = z_{nP})}$$


$$V_k^+(z_k) = 0 \quad \text{for all } k \neq n$$

## Scattering Matrix (contd.)

- Note that, frequently the port positions are assigned a **zero** value (e.g.,  $z_{1P}=0$ ,  $z_{2P}=0$ ). This of course **simplifies** the scattering parameter calculation:

$$S_{mn} = \frac{V_m^-(z_m = 0)}{V_n^+(z_n = 0)} = \frac{V_m^+ e^{+j\beta 0}}{V_n^- e^{-j\beta 0}} = \frac{V_m^+}{V_n^-}$$

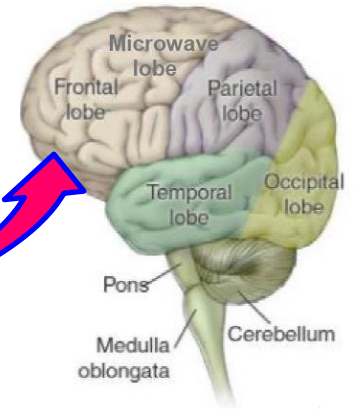
- We will **generally assume** that the port locations are defined as  $z_{nP}=0$ , and thus use the **above** notation. But **remember** where this expression came from!



**Q:** How do we ensure that **only one** incident wave is non-zero ?

**A:** **Terminate** all other ports with a **matched load!**

# Scattering Matrix (contd.)

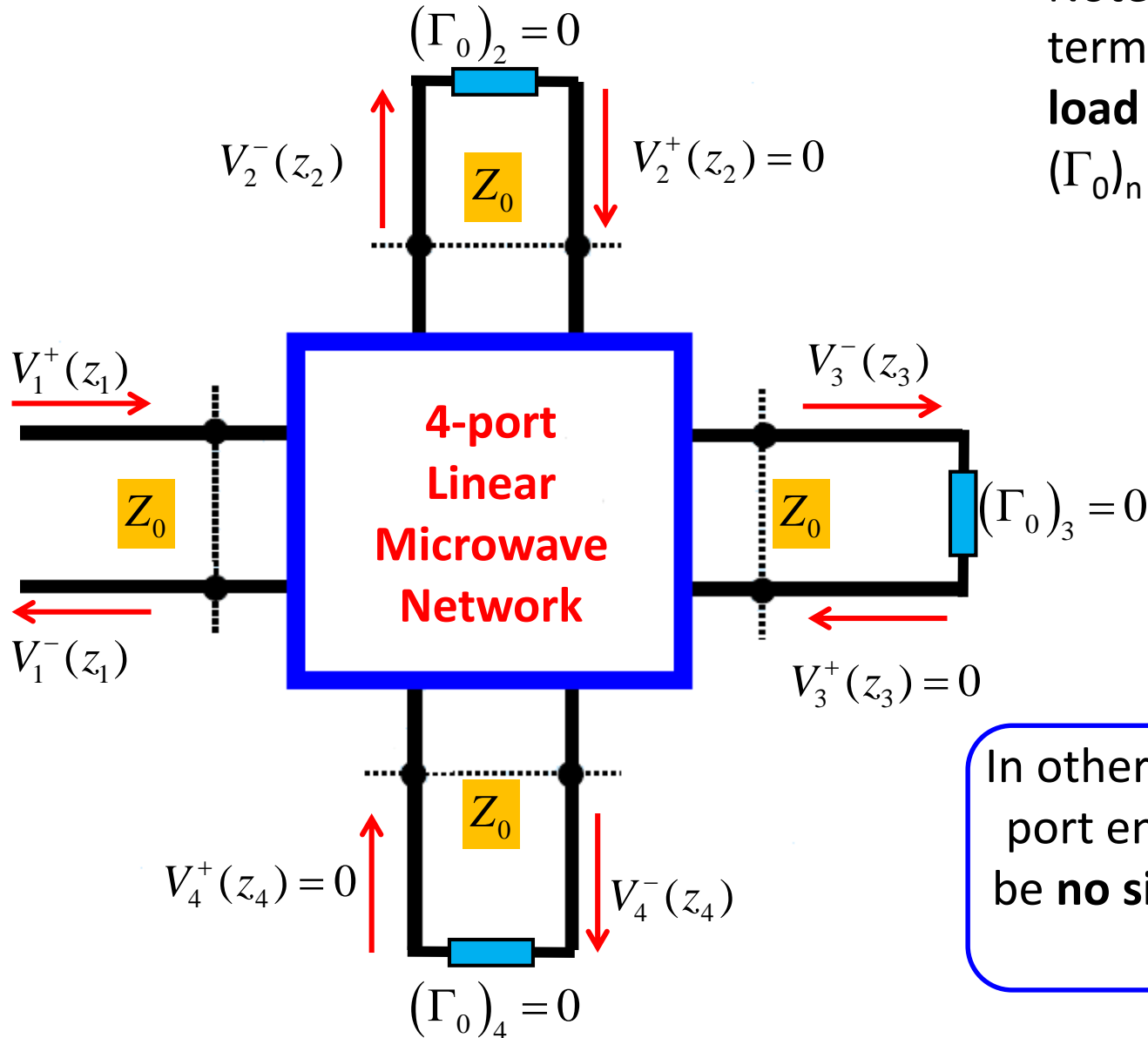

- Note that if the ports are terminated in a **matched load** (i.e.,  $Z_L = Z_0$ ), then  $(\Gamma_0)_n = 0$  and therefore:

$$V_n^+(z_n) = 0$$

In other words, terminating a port ensures that there will be **no signal** incident on that port!

## Scattering Matrix (contd.)



Just between you and me, I think you've messed this up! **In all** previous slides you said that if  $\Gamma_0 = 0$ , the wave in the **minus** direction would be zero:

$$V^-(z) = 0 \quad \text{if} \quad \Gamma_0 = 0$$

but just **now** you said that the wave in the **positive** direction would be zero:

$$V^+(z) = 0 \quad \text{if} \quad \Gamma_0 = 0$$


Obviously, there is **no way** that **both** statements can be correct!


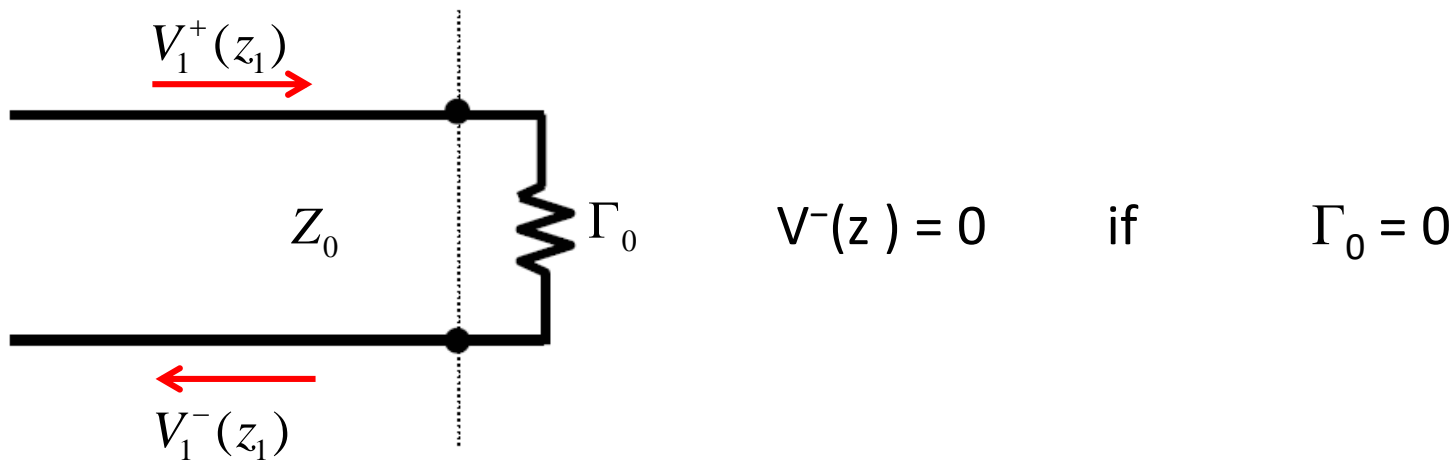
## Scattering Matrix (contd.)

Actually, **both** statements are correct! You must be careful to understand the **physical definitions** of the plus and minus directions—in other words, the propagation directions of waves  $V_n^+(z_n)$  and  $V_n^-(z_n)$ !


For example, we **originally** analyzed this case:



In this original case, the wave **incident** on the load is  $V^+(z)$  (**plus** direction), while the **reflected** wave is  $V^-(z)$  (**minus** direction).
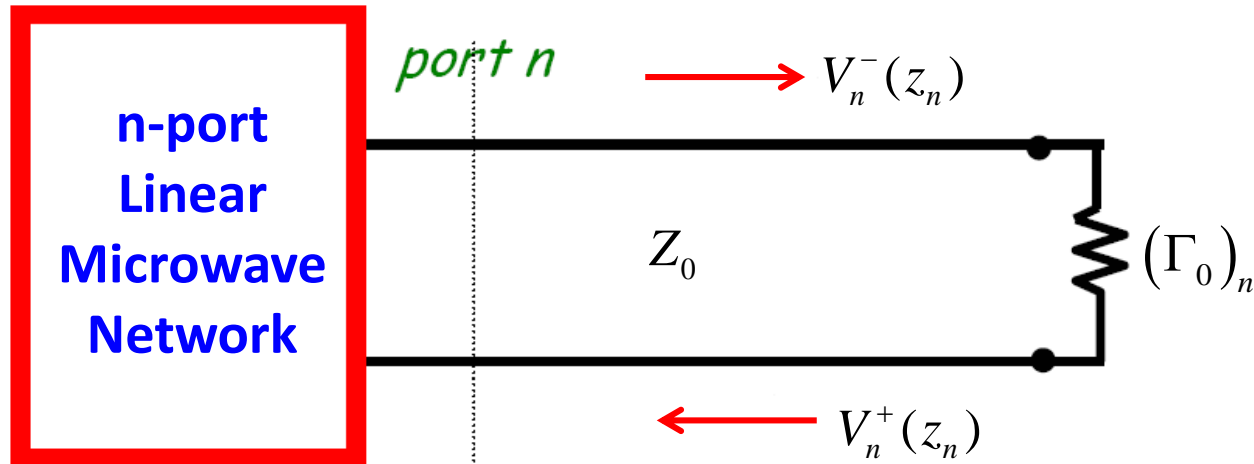
## Scattering Matrix (contd.)

Contrast this with the case we are **now** considering:



- For this current case, the situation is **reversed**. The wave incident on the load is **now** denoted as  $V_n^-(z_n)$  (coming **out** of port n), while the wave reflected off the load is **now** denoted as  $V_n^+(z_n)$  (going **into** port n).

## Scattering Matrix (contd.)

- **back** to our discussion of **S-parameters**. We found that **if**  $z_{nP} = 0$  for all ports  $n$ , the scattering parameters could be directly written in terms of wave **amplitudes**  $V_n^+$  and  $V_m^-$

$$S_{mn} = \frac{V_m^-}{V_n^+} \quad V_k^+(z_k) = 0$$


**for all  $k \neq n$**

- Which we can now **equivalently** state as:

$$S_{mn} = \frac{V_m^-}{V_n^+} \quad (\text{for all ports, except port } n, \text{ are terminated in matched loads})$$

- One more **important** note—notice that for the ports terminated in matched loads (i.e., those ports with **no** incident wave), the voltage of the exiting **wave** is also the **total** voltage!
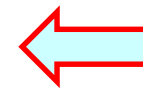
$$V_m(z_m) = V_m^+ e^{-j\beta z_m} + V_m^- e^{+j\beta z_m} = 0 + V_m^- e^{+j\beta z_m} = V_m^- e^{+j\beta z_m}$$



For all  
terminated  
ports!

## Scattering Matrix (contd.)

- We can use the scattering matrix to determine the solution for a more **general** circuit—one where the ports are **not** terminated in matched loads!
- Since the device is **linear**, we can apply **superposition**. The output at any port due to **all** the incident waves is simply the coherent **sum** of the output at that port due to **each** wave!
- For example, the **output** wave at port 3 can be determined by (assuming  $z_{nP} = 0$ ):
- More **generally**, the output at port  $m$  of an N-port device is:

$$V_3^- = S_{34}V_4^+ + S_{33}V_3^+ + S_{32}V_2^+ + S_{31}V_1^+$$

$$V_m^- = \sum_{n=1}^N S_{mn} V_n^+ \quad z_{nP} = 0$$

- This expression of Scattering parameter can be written in **matrix** form as:

$$\mathbf{V}^- = \mathbf{S}\mathbf{V}^+$$

## Scattering Matrix (contd.)

$$V^- = SV^+$$

Scattering Matrix

$$S = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1n} \\ S_{21} & & & \vdots \\ \vdots & & & \\ S_{m1} & S_{m2} & \dots & S_{mn} \end{bmatrix}$$

- The scattering matrix is N by N matrix that **completely characterizes** a linear, N-port device. Effectively, the scattering matrix describes a multi-port device the way that  $\Gamma_0$  describes a single-port device (e.g., a load)!
- The values of the scattering matrix for a particular device or network, like  $\Gamma_0$ , are **frequency dependent!** Thus, it may be more instructive to **explicitly** write:
$$S(\omega) = \begin{bmatrix} S_{11}(\omega) & S_{12}(\omega) & \dots & S_{1n}(\omega) \\ S_{21}(\omega) & & & \vdots \\ \vdots & & & \\ S_{m1}(\omega) & S_{m2}(\omega) & \dots & S_{mn}(\omega) \end{bmatrix}$$
- Also realize that—also just like  $\Gamma_0$ —the scattering matrix is dependent on **both** the **device/network** and the  $Z_0$  value of the **cable connected** to it.
- Thus, a device connected to cables with  $Z_0 = 50\Omega$  will have a **completely different scattering matrix** than that same device connected to transmission lines with  $Z_0 = 100\Omega$

# Matched, Lossless, Reciprocal Devices

- A device can be **lossless** or **reciprocal**. In addition, we can also classify it as being **matched**.
- Let's examine **each** of these three characteristics, and how they relate to the **scattering matrix**.

## Matched Device

A matched device is another way of saying that the **input impedance** at each port is **equal to  $Z_0$**  when **all other** ports are terminated in matched loads. As a result, the **reflection coefficient** of each port is **zero**—no signal will come out from a port if a signal is incident on that port (**but only that port!**).

- **In other words:**  $V_m^- = S_{mm} V_m^+ = 0$  For all  $m$   $\longrightarrow$  **When all the ports 'm' are matched**

- It is apparent that a matched device will exhibit a scattering matrix where all **diagonal elements are zero**.

$$\mathbf{S} = \begin{bmatrix} 0 & 0.1 & j0.2 \\ 0.1 & 0 & 0.3 \\ j0.2 & 0.3 & 0 \end{bmatrix}$$

# Matched, Lossless, Reciprocal Devices (contd.)


## Lossless Device

- For a lossless device, all of the power that is delivered to each device port must eventually find its way **out!**
- In other words, power is not **absorbed** by the network—no power to be **converted to heat!**
- The **power incident** on some port  $m$  is related to the amplitude of the **incident wave** ( $V_m^+$ ) as:  
$$P_m^+ = \frac{|V_m^+|^2}{2Z_0}$$
- The power of the **wave exiting** the port is:  
$$P_m^- = \frac{|V_m^-|^2}{2Z_0}$$
- power absorbed by that port is the **difference** of the incident power and reflected power:  
$$\Delta P_m = P_m^+ - P_m^- = \frac{|V_m^+|^2}{2Z_0} - \frac{|V_m^-|^2}{2Z_0}$$

# Matched, Lossless, Reciprocal Devices (contd.)

- For an N-port device, the total incident power is:

$$P^+ = \sum_{m=1}^N P_m^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_m^+|^2$$

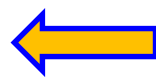

$$|V_m^+|^2 = (\mathbf{V}^+)^H \mathbf{V}^+$$



$(\mathbf{V}^+)^H$  is the conjugate transpose of the row vector  $\mathbf{V}^+$

$$P^+ = \sum_{m=1}^N P_m^+ = \frac{(\mathbf{V}^+)^H \mathbf{V}^+}{2Z_0}$$

Similarly, the total reflected power



$$P^- = \sum_{m=1}^N P_m^- = \frac{(\mathbf{V}^-)^H \mathbf{V}^-}{2Z_0}$$

- Recall that the incident and reflected wave amplitudes are **related** by the **scattering matrix** of the device as:

$$\mathbf{V}^- = \mathbf{S} \mathbf{V}^+$$

- Therefore:

$$P^- = \frac{(\mathbf{V}^-)^H \mathbf{V}^-}{2Z_0} = \frac{(\mathbf{V}^+)^H \mathbf{S}^H \mathbf{S} \mathbf{V}^+}{2Z_0}$$

- Therefore the **total power delivered** to the N-port device is:

$$\Delta P = P^+ - P^- = \frac{(\mathbf{V}^+)^H \mathbf{V}^+}{2Z_0} - \frac{(\mathbf{V}^+)^H \mathbf{S}^H \mathbf{S} \mathbf{V}^+}{2Z_0}$$

$$\Rightarrow \Delta P = \frac{(\mathbf{V}^+)^H}{2Z_0} (\mathbf{I} - \mathbf{S}^H \mathbf{S}) \mathbf{V}^+$$



# Matched, Lossless, Reciprocal Devices (contd.)

- For a lossless device:  $\Delta P = 0 \Rightarrow \frac{(V^+)^H}{2Z_0} (I - S^H S) V^+ = 0$  ← For all  $V^+$

- Therefore:  $I - S^H S = 0 \Rightarrow S^H S = I$   
 a special kind of matrix known as a **unitary matrix**

If a network is **lossless**, then its scattering matrix **S** is **unitary**

## How to recognize a unitary matrix?

The **columns** of a unitary matrix form an **orthonormal set!**

**Example:**

$$S = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

each **column** of the scattering matrix will have a **magnitude equal to one**

$$\sum_{m=1}^N |S_{mn}|^2 = 1 \quad \text{For all } n$$

inner product (i.e., dot product) of **dissimilar columns** must be **zero**

dissimilar columns are orthogonal

$$\sum_{m=1}^N S_{mi} S_{mj}^* = S_{1i} S_{1j}^* + S_{2i} S_{2j}^* + \dots + S_{Ni} S_{Nj}^* = 0 \quad \text{For all } i \neq j$$

## Matched, Lossless, Reciprocal Devices (contd.)

- For example, for a lossless **three-port** device: say a signal is incident on port 1, and that **all** other ports are **terminated**. The power **incident** on port 1 is therefore:

$$P_1^+ = \frac{|V_1^+|^2}{2Z_0}$$

- and the power **exiting** the device at each port is:

$$P_m^- = \frac{|V_m^-|^2}{2Z_0} = \frac{|S_{m1}V_1^+|^2}{2Z_0} = |S_{m1}|^2 P_1^+$$

- The **total** power exiting the device is therefore:

$$P^- = P_1^- + P_2^- + P_3^- = |S_{11}|^2 P_1^+ + |S_{21}|^2 P_1^+ + |S_{31}|^2 P_1^+$$

$$\Rightarrow P^- = (|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2) P_1^+$$

- Since this device is **lossless**, the incident power (**only on port 1**) is **equal** to exiting power (i.e.,  $P^- = P_1^+$ ). This is true **only if**:

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$$

- Of course, this will be true if the incident wave is placed on **any** of the **other** ports of this lossless device:

$$|S_{12}|^2 + |S_{22}|^2 + |S_{32}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1$$

## Matched, Lossless, Reciprocal Devices (contd.)

- We can state in general then that:  $\sum_{m=1}^N |S_{mn}|^2 = 1$  For all  $n$
- In other words, the columns of the scattering matrix must have **unit magnitude** (a requirement of all **unitary** matrices). It is apparent that this must be true for energy to be conserved.

- An **example** of a (unitary) scattering matrix for a 4-port **lossless** device is:

$$S = \begin{bmatrix} 0 & 1/2 & j\sqrt{3}/2 & 0 \\ 1/2 & 0 & 0 & j\sqrt{3}/2 \\ j\sqrt{3}/2 & 0 & 0 & 1/2 \\ 0 & j\sqrt{3}/2 & 1/2 & 0 \end{bmatrix}$$

### Reciprocal Device

- Recall **reciprocity** results when we build a **passive** (i.e., unpowered) device with **simple** materials.
- For a reciprocal network, we find that the elements of the scattering matrix are **related** as:

$$S_{mn} = S_{nm}$$

## Matched, Lossless, Reciprocal Devices (contd.)

- For example, a **reciprocal** device will have  $S_{21} = S_{12}$  or  $S_{32} = S_{23}$ . We can write reciprocity in matrix form as:

$$\boxed{S^T = S} \quad \text{where T indicates transpose.}$$

- An **example** of a scattering matrix describing a **reciprocal**, but **lossy** and **non-matched** device is:

$$S = \begin{bmatrix} 0.10 & -0.40 & -j0.20 & 0.05 \\ -0.40 & j0.20 & 0 & j0.10 \\ -j0.20 & 0 & 0.10 - j0.30 & -0.12 \\ 0.05 & j0.10 & -0.12 & 0 \end{bmatrix}$$

## Example – 3

- A **lossless, reciprocal** 3-port device has S-parameters of  $S_{11} = 1/2$ ,  $S_{31} = 1/\sqrt{2}$ , and  $S_{33} = 0$ . It is likewise known that all scattering parameters are **real**.

→ Find the remaining **6** scattering parameters.



**Q:** This problem is clearly **impossible**—you have not provided us with sufficient **information!**

**A:** Yes I have! Note I said the device was **lossless** and **reciprocal!**

## Example – 3 (contd.)

- Start with what we **currently** know:

$$\mathbf{S} = \begin{bmatrix} 1/2 & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ 1/\sqrt{2} & S_{32} & 0 \end{bmatrix}$$

- As the device is **reciprocal**, we then also know:

$$S_{12} = S_{21}$$

$$S_{13} = S_{31} = 1/\sqrt{2}$$

$$S_{32} = S_{23}$$

- And therefore:


$$\mathbf{S} = \begin{bmatrix} 1/2 & S_{21} & 1/\sqrt{2} \\ S_{21} & S_{22} & S_{32} \\ 1/\sqrt{2} & S_{32} & 0 \end{bmatrix}$$

- Now, since the device is **lossless**, we know that:

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1 \quad \longrightarrow \quad (1/2)^2 + |S_{21}|^2 + (1/\sqrt{2})^2 = 1$$

$$|S_{12}|^2 + |S_{22}|^2 + |S_{32}|^2 = 1 \quad \longrightarrow \quad |S_{21}|^2 + |S_{22}|^2 + |S_{32}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1 \quad \longrightarrow \quad (1/2)^2 + |S_{32}|^2 + (1/\sqrt{2})^2 = 1$$

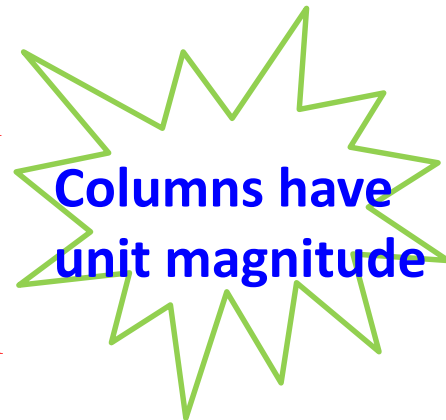

## Example – 3 (contd.)

$$0 = S_{11}S_{12}^* + S_{21}S_{22}^* + S_{31}S_{32}^* = \frac{1}{2}S_{12}^* + S_{21}S_{22}^* + \frac{1}{\sqrt{2}}S_{32}^*$$

$$0 = S_{11}S_{13}^* + S_{21}S_{23}^* + S_{31}S_{33}^* = \frac{1}{2}\frac{1}{\sqrt{2}} + S_{21}S_{32}^* + \frac{1}{\sqrt{2}}(0)$$

$$0 = S_{12}S_{13}^* + S_{22}S_{23}^* + S_{32}S_{33}^* = S_{21}\left(\frac{1}{\sqrt{2}}\right) + S_{22}S_{32}^* + S_{32}(0)$$



We can simplify these expressions and can further simplify them by using the fact that the elements are all **real**, and therefore  $S_{21} = S_{21}^*$  (etc.).



**Q:** I count the simplified expressions and find 6 equations yet only a paltry 3 unknowns. Your typical buffoonery appears to have led to an over-constrained condition for which there is **no** solution!

## Example – 3 (contd.)

**A:** Actually, we have **six** real equations and **six** real unknowns, since scattering element has a magnitude and phase. In this case we know the values are **real**, and thus the phase is either  $0^\circ$  or  $180^\circ$  (i.e.,  $e^{j0} = 1$  or  $e^{j\pi} = -1$ ); however, we do not know which one!

- the scattering matrix for the given **lossless, reciprocal** device is:

$$\mathbf{S} = \begin{bmatrix} 1/2 & 1/2 & 1/\sqrt{2} \\ 1/2 & 1/2 & -1/\sqrt{2} \\ 1/\sqrt{2} & -1/\sqrt{2} & 0 \end{bmatrix}$$