

# ECE 215

## Lecture – 5

Date: 14.08.2017

- Second-Order Circuit (contd.)

## Step Response of a Series RLC Circuit


- Apply KVL around the loop for  $t > 0$ :

$$L \frac{di}{dt} + Ri + v = V_s \quad \leftarrow \quad i = C \frac{dv}{dt}$$



$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

solution has two components

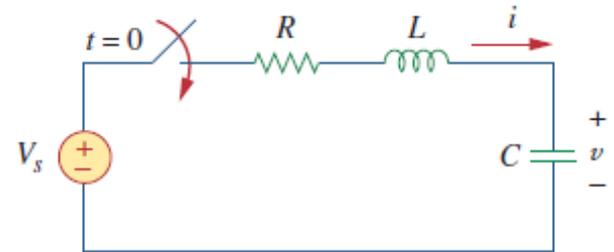

$$v(t) = v_t(t) + v_{ss}(t)$$

- $v_t(t)$  dies out with time and is of the form:

$$v_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v_t(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

- $v_{ss}(t)$  is the final value of the capacitor voltage.  $v_{ss}(t) = v(\infty) = V_s$

## Step Response of a Series RLC Circuit (contd.)

- the complete solutions are:

$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$


$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$


- The values of  $A_1$  and  $A_2$  are obtained from the initial conditions:  $v(0)$  and  $dv(0)/dt$
- Just to reiterate:  $v$  and  $i$  are the voltage across the capacitor and the current through the inductor respectively.
- Above expressions help in finding  $v$ .
- once the capacitor voltage is  $v_c = v$  is known, we can determine  $i = C \, dv/dt$  which is the same current through the capacitor, inductor, and resistor.
- the voltage across the resistor is  $v_R = iR$  while the inductor voltage is  $L \, di/dt$ .
- Alternatively, the complete response for any variable  $x(t)$  can be found directly, because it has the general form:  $x(t) = x_{ss}(t) + x_t(t)$
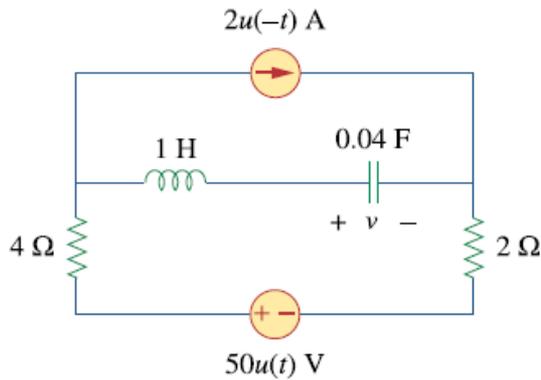
## Example – 1

For this circuit, find  $v(t)$  for  $t > 0$ .



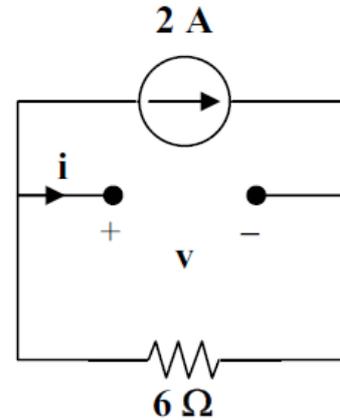- For  $t = 0^-$ , the equivalent circuit is:



$$i(0^-) = 0, \quad v(0^-) = -2 \times 6 = -12\text{V}$$

- For  $t > 0$ , we have a series RLC circuit with a step input.

$$\alpha = R/(2L) = 6/2 = 3$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{0.04}$$

Underdamped

$$s = -3 \pm \sqrt{9 - 25} = -3 \pm j4$$


$$v(t) = V_f + [(A \cos 4t + B \sin 4t)e^{-3t}]$$

## Example – 1 (contd.)

$V_f = \text{final capacitor voltage} = 50 \text{ V}$    $v(t) = 50 + [(A\cos 4t + B\sin 4t)e^{-3t}]$

$v(0) = -12 = 50 + A$    $A = -62$

$i(0) = 0 = Cdv(0)/dt$

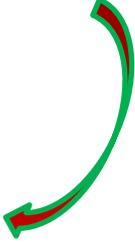$dv/dt = [-3(A\cos 4t + B\sin 4t)e^{-3t}] + [4(-A\sin 4t + B\cos 4t)e^{-3t}]$  

$0 = dv(0)/dt = -3A + 4B$  or  $B = (3/4)A = -46.5$

$v(t) = \underline{\{50 + [(-62\cos 4t - 46.5\sin 4t)e^{-3t}]\}} \text{ V}$


## Practice Example

A series *RLC* circuit is described by:  $L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 2$

Find the response when  $L=0.5\text{H}$ ,  $R=4\Omega$ , and  $C=0.2\text{F}$ . Let  $i(0) = 1$ ,  $di(0)/dt=0$ .
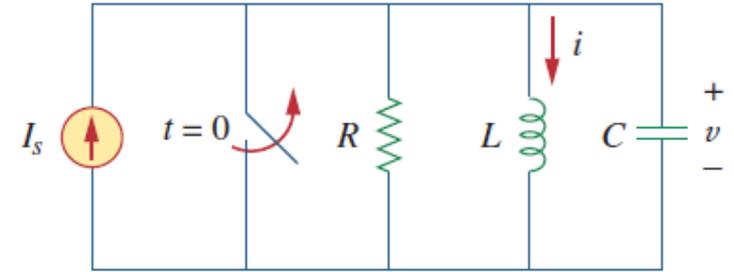
# Step Response of a Parallel RLC Circuit

- Apply KCL at the top node for  $t > 0$ :



$$\frac{v}{R} + i + C \frac{dv}{dt} = I_s \quad \leftarrow \quad v = L \frac{di}{dt}$$

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC} \quad \longrightarrow \quad i(t) = i_t(t) + i_{ss}(t)$$

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$i(t) = I_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

$A_1$  and  $A_2$  to be determined from  $i(0)$  and  $\frac{di(0)}{dt}$ .

$$i = i_L \quad \longrightarrow \quad v = L \frac{di}{dt}$$

$$i_R = v/R,$$


$$i_C = C \frac{dv}{dt}$$

- Alternatively, the complete response for any variable  $x(t)$  can be found directly, because it has the general form:

$$x(t) = x_{ss}(t) + x_t(t)$$
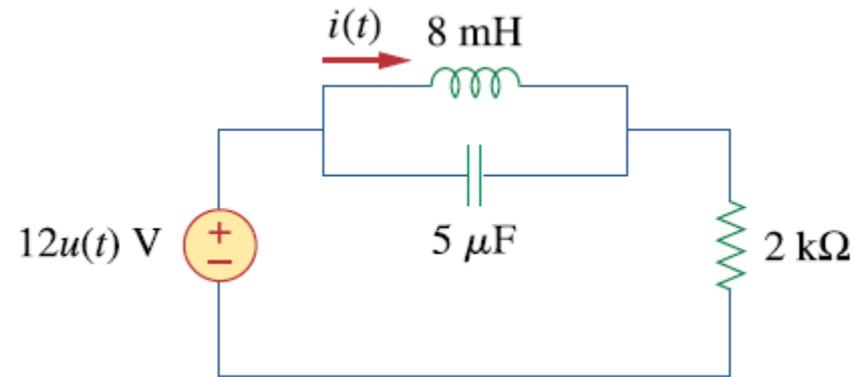
## Example – 2

find  $i(t)$  for  $t > 0$  in this circuit:




## General Second-Order Circuits

- the series and parallel  $RLC$  circuits are the second-order circuits of greatest interest, other second-order circuits including op amps are also useful.
- for a second-order circuit, we determine its step response  $x(t)$  (which may be voltage or current) by taking the following four steps:
  1. We first determine the initial conditions  $x(0)$  and  $\frac{dx(0)}{dt}$  and the final value  $x(\infty)$ .
  2. We turn off the independent sources and find the form of the transient response  $x_t(t)$  by applying KCL and KVL.
  3. We obtain the steady-state response as:  $x_{SS}(t) = x(\infty)$ .
  4. The total response is then found as the sum of the transient response and steady-state response.

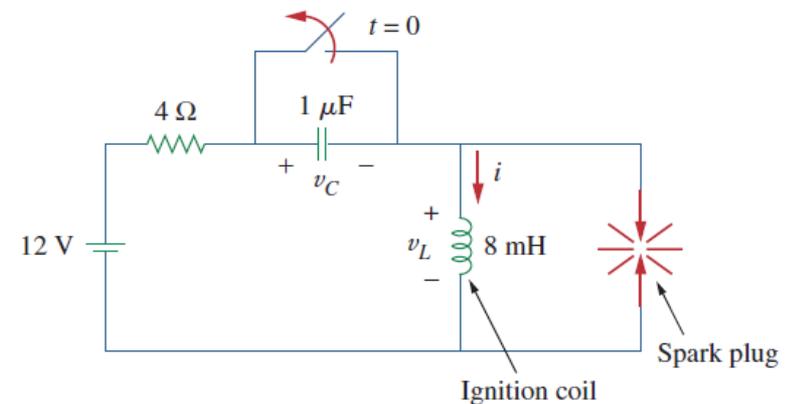
# Automobile Ignition System

- Earlier, considered the automobile ignition system as a charging system. That was only a part of the system.
- another part—the voltage generating system.
- The 12-V source is due to the battery and alternator.
- The  $4\Omega$  resistor represents the resistance of the wiring.
- The ignition coil is modeled by the 8-mH inductor.
- The  $1\mu F$  capacitor (known as the *condenser* to auto mechanics) is in parallel with the switch (known as the *breaking points* or *electronic ignition*).


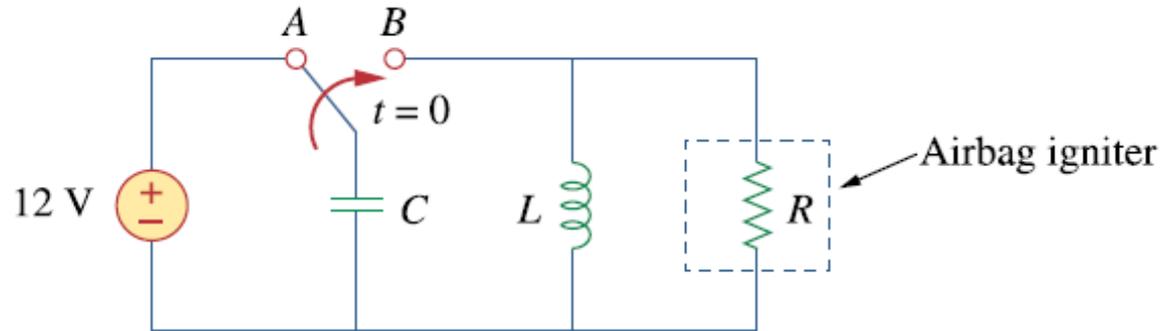
### Example – 3

An automobile airbag igniter is modeled by the following circuit. Determine the time it takes the voltage across the igniter to reach its first peak after switching from A to B. Let  $R = 3\Omega$ ,  $C = 1/30\text{pF}$ , and  $L = 60\text{mH}$ .



### Example – 4

A load is modeled as a 250-mH inductor in parallel with a  $12\Omega$  resistor. A capacitor is needed to be connected to the load so that the network is critically damped at 60 Hz. Calculate the size of the capacitor.