

ECE 215

Lecture – 7

Date: 22.08.2017

- Phasors
- AC Circuits: Impedance and Admittance, Kirchoff's Laws, Phase Shifter

Example – 8: If $f(\phi) = \cos \phi + j \sin \phi$, show that $f(\phi) = e^{j\phi}$.

Example – 9: Find the phasors corresponding to the following signals:

(a) $v(t) = 21 \cos(4t - 15^\circ)$ V

(b) $i(t) = -8 \sin(10t + 70^\circ)$ mA

(c) $v(t) = 120 \sin(10t - 50^\circ)$ V

(d) $i(t) = -60 \cos(30t + 10^\circ)$ mA

Example – 10: Obtain the sinusoids corresponding to each of the following phasors:

(a) $\mathbf{V}_1 = 60 \angle 15^\circ$ V, $\omega = 1$

(b) $\mathbf{V}_2 = 6 + j8$ V, $\omega = 40$

(c) $\mathbf{I}_1 = 2.8e^{-j\pi/3}$ A, $\omega = 377$

(d) $\mathbf{I}_2 = -0.5 - j1.2$ A, $\omega = 10^3$

Example – 11: Simplify the following:

(a) $f(t) = 5 \cos(2t + 15^\circ) - 4 \sin(2t - 30^\circ)$

(b) $g(t) = 8 \sin t + 4 \cos(t + 50^\circ)$



(c) $h(t) = \int_0^t (10 \cos 40t + 50 \sin 40t) dt$

Example – 12: Using phasors, determine $i(t)$ in the following equations:

(a) $2 \frac{di}{dt} + 3i(t) = 4 \cos(2t - 45^\circ)$

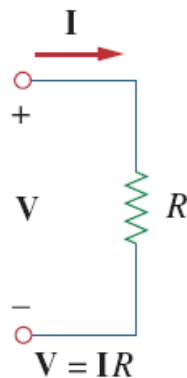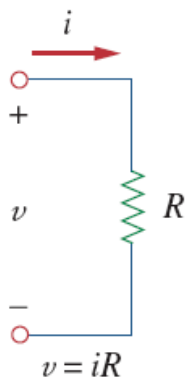(b) $10 \int i dt + \frac{di}{dt} + 6i(t) = 5 \cos(5t + 22^\circ)$



Phasor Relationships for Circuit Elements



If the current through a resistor R is $i = I_m(\cos\omega t + \phi)$, then the voltage across it is given by Ohm's law as:

$$v = iR = RI_m \cos(\omega t + \phi) \quad \mathbf{V = RI_m \angle \phi} \quad \boxed{V = RI}$$

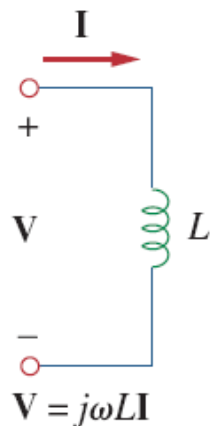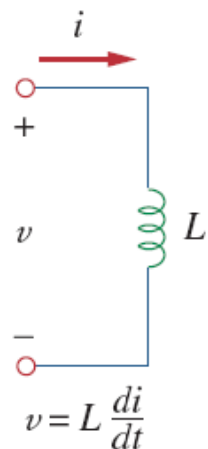\therefore voltage-current relation for the resistor in the phasor domain continues to be Ohm's law



For the inductor L , assume current $i = I_m(\cos\omega t + \phi)$, then the voltage across it is:

$$v = L \frac{di}{dt} = -\omega LI_m \sin(\omega t + \phi)$$

$$v = \omega LI_m \cos(\omega t + \phi + 90^\circ)$$




Phasor Relationships for Circuit Elements

$$v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

$$\mathbf{V} = \omega L I_m e^{j(\phi+90^\circ)} = \omega L I_m e^{j\phi} e^{j90^\circ} = \omega L I_m \angle \phi + 90^\circ$$


$$\mathbf{V} = j\omega L \mathbf{I}$$

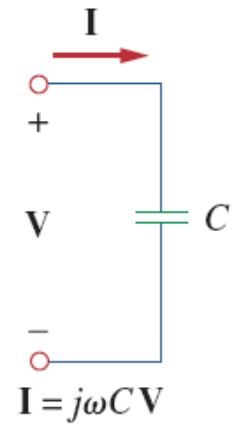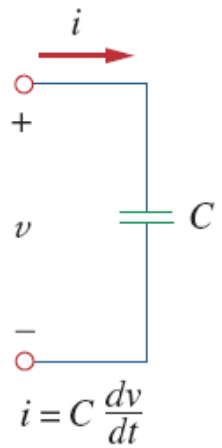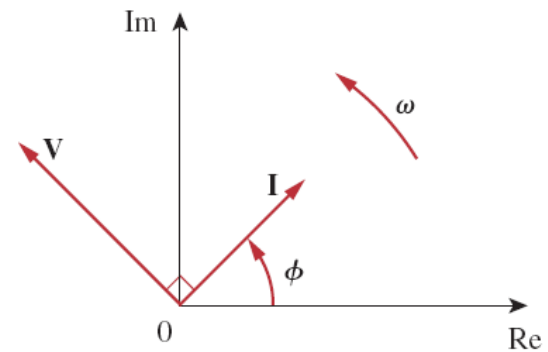the voltage has a magnitude of $\omega L I_m$ and a phase of ϕ . The voltage and current are 90° out of phase. Specifically, the current lags the voltage by 90° .



$$\mathbf{I} = j\omega C \mathbf{V} \Rightarrow \mathbf{V} = \frac{\mathbf{I}}{j\omega C}$$

the current leads the voltage by 90° .

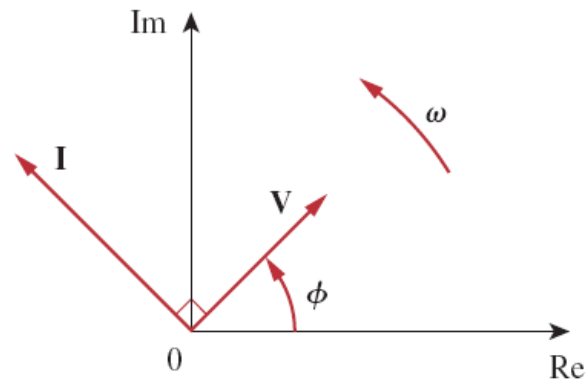

Example – 13

What is the instantaneous voltage across a $2\mu\text{F}$ capacitor when the current through it is $i = 4 \sin(10^6 t + 25^\circ) \text{ A}$?

Example – 14

A voltage $v(t) = 100 \cos(60t + 20^\circ) \text{ V}$ is applied to a parallel combination of a $40\text{k}\Omega$ resistor and a $50\mu\text{F}$ capacitor. Find the steady-state currents through the resistor and the capacitor.

Example – 15

A series RLC circuit has $R = 80 \Omega$, $L = 240\text{mH}$, and $C = 5\text{mF}$. If the input voltage is $v(t) = 100 \cos(2t)$, find the current flowing through the circuit.

Impedance and Admittance

- we know: $V = RI$, $V = j\omega LI$, $V = \frac{I}{j\omega C}$ $\frac{V}{I} = R$, $\frac{V}{I} = j\omega L$, $\frac{V}{I} = \frac{1}{j\omega C}$
- we express Ohm's law in phasor form: $Z = \frac{V}{I}$ or $V = ZI$

where Z is a frequency-dependent quantity known as *impedance*, measured in ohms. It is the ratio of the phasor voltage V to the phasor current I , measured in Ω .

$$Z_L = j\omega L \text{ and } Z_C = -j/\omega C$$

- For $\omega = 0$ (i.e., dc sources): $Z_L = 0$ and $Z_C \rightarrow \infty$.
- the inductor acts like a short circuit, while the capacitor acts like an open circuit.
- For $\omega \rightarrow \infty$ (i.e., high frequencies): $Z_L \rightarrow \infty$ and $Z_C = 0$.
- the inductor acts like an open circuit, while the capacitor acts like a short circuit.

- complex quantity

$$Z = R + jX \longrightarrow Z = |Z| \angle \theta$$

$$R = |Z| \cos \theta,$$

$$X = |Z| \sin \theta$$

$$|Z| = \sqrt{R^2 + X^2},$$

$$\theta = \tan^{-1} \frac{X}{R}$$

Impedance and Admittance

- It is sometimes (parallel circuits) convenient to work with the reciprocal of impedance, known as *admittance (Y)*.


$$Y = \frac{1}{Z} = \frac{I}{V} \quad \longrightarrow \quad Y = G + jB$$
$$G = \frac{R}{R^2 + X^2}$$
$$B = -\frac{X}{R^2 + X^2}$$

Example – 1

A linear network has a current input $4\cos(\omega t + 20^\circ)\text{A}$ and a voltage output $10\cos(\omega t + 110^\circ)\text{V}$. Determine the associated impedance.

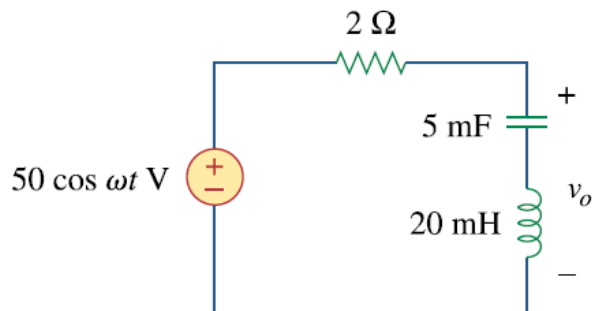
Example – 2

What value of ω will cause the forced response v_o in this circuit to be zero?



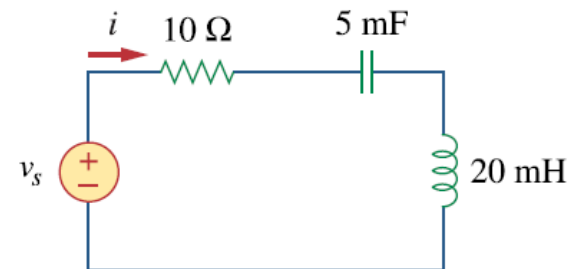
Example – 3

Find current i in this circuit, when $v_s(t) = 50\cos 200t \text{ V}$.



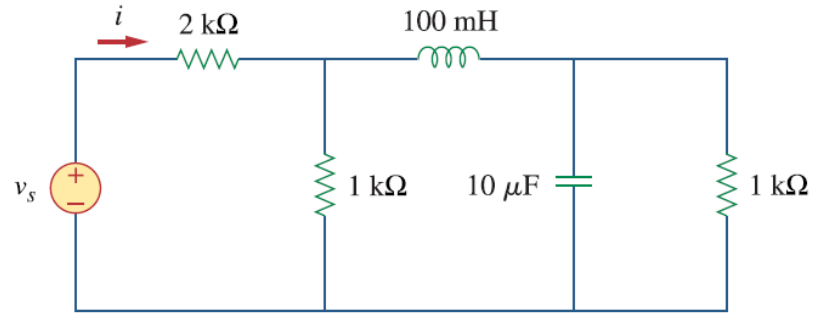
Example – 4

Find current i in this circuit, when $v_s(t) = 60\cos(200t - 10^\circ)$ V.



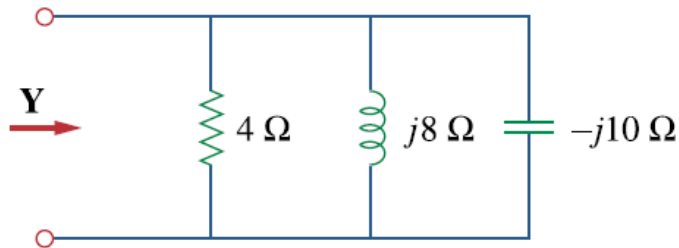
Example – 5

Determine the admittance \mathbf{Y} for this circuit.



Example – 6

Find current i in this circuit.

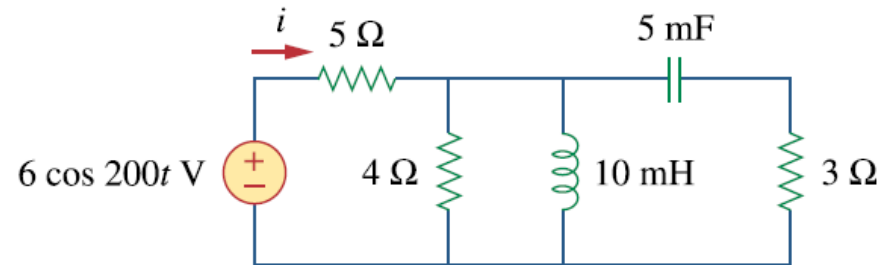

Kirchoff's Laws

- cannot do circuit analysis in the frequency domain without Kirchoff's current and voltage laws.
- Therefore, need to express them in the frequency domain.

Kirchoff's Laws

For KVL, let v_1, v_2, \dots, v_n are the voltages around a closed loop.

$$v_1 + v_2 + \dots + v_n = 0 \quad \Rightarrow \quad V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n) = 0$$

$$\text{Re}(V_{m1}e^{j\theta_1}e^{j\omega t}) + \text{Re}(V_{m2}e^{j\theta_2}e^{j\omega t}) + \dots + \text{Re}(V_{mn}e^{j\theta_n}e^{j\omega t}) = 0$$


$$\text{Re}[(V_{m1}e^{j\theta_1} + V_{m2}e^{j\theta_2} + \dots + V_{mn}e^{j\theta_n})e^{j\omega t}] = 0$$

$$\Rightarrow \text{Re}[(V_1 + V_2 + \dots + V_n)e^{j\omega t}] = 0 \quad \Rightarrow \quad V_1 + V_2 + \dots + V_n = 0$$

Kirchoff's voltage law holds for phasors.

Similarly, one can prove that Kirchoff's current law holds in the frequency domain

Impedance Combinations

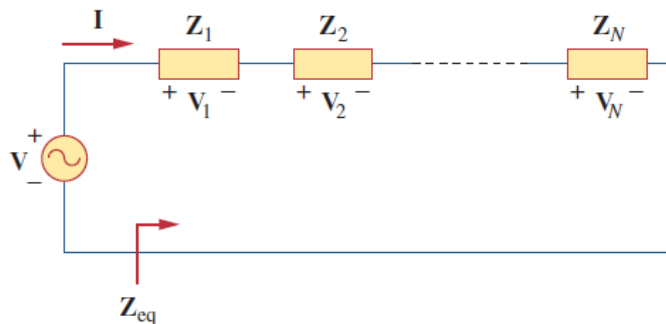


$$V = V_1 + V_2 + \dots + V_N = I(Z_1 + Z_2 + \dots + Z_N)$$

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N$$

This is similar to the series connection of resistances.

Impedance Combinations

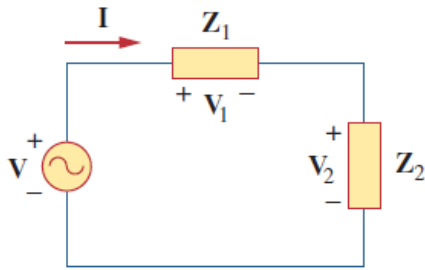


$$I = \frac{V}{Z_1 + Z_2}$$

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V$$

$$V_2 = \frac{Z_2}{Z_1 + Z_2} V$$


voltage-division relationship

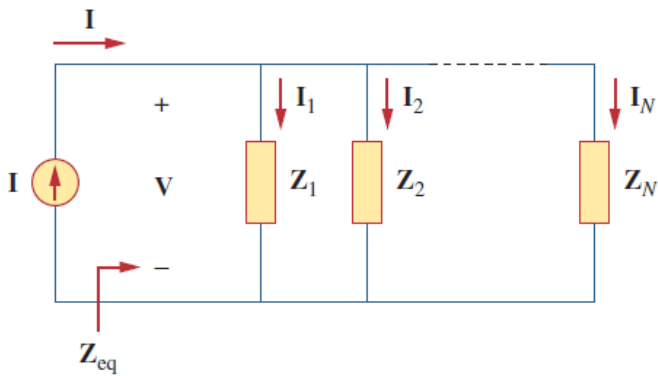

$$I = I_1 + I_2 + \dots + I_N = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

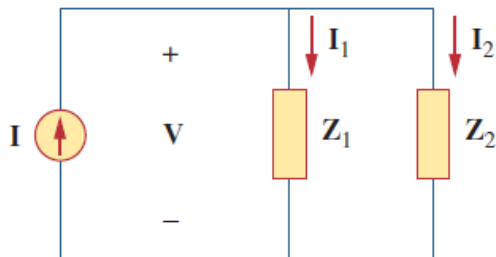

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{Y_1 + Y_2} = \frac{1}{1/Z_1 + 1/Z_2} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$V = I Z_{eq} = I_1 Z_1 = I_2 Z_2$$


$$I_1 = \frac{Z_2}{Z_1 + Z_2} I$$

$$I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

the *current-division* principle.

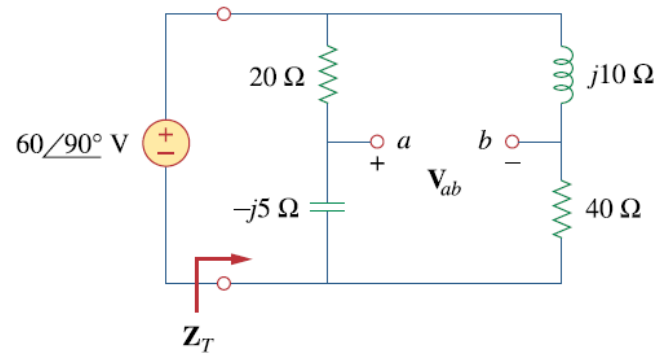
Example – 7

For this circuit, calculate Z_T and V_{ab} .



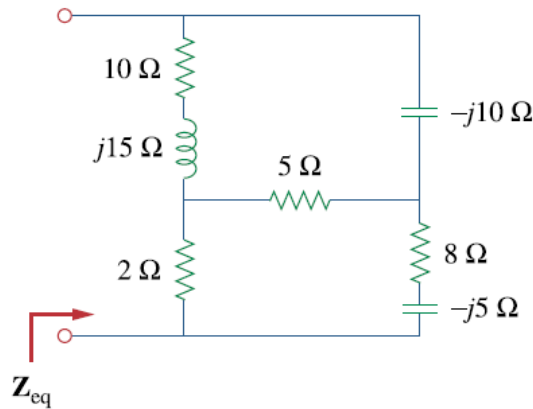
Example – 9

Find the equivalent impedance of this circuit.



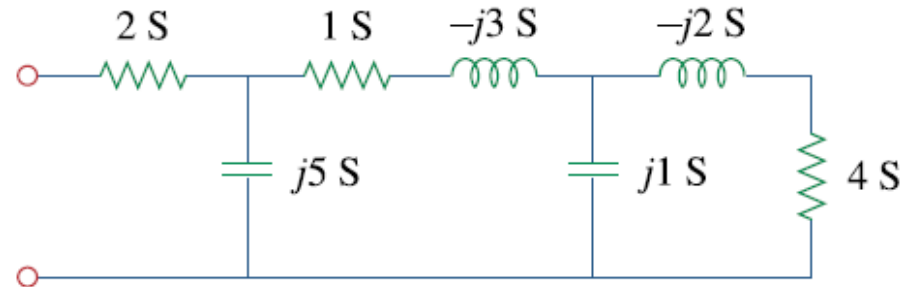Example – 8



Find the equivalent admittance Y_{eq} of this circuit.



Phase Shifter

- A phase-shifting circuit is used for correcting undesirable phase shift present in a circuit.
- It is also used for the creation of desired phase shifts.
- *RC and RL circuits are extremely useful for this purpose.*

Phase Shifter

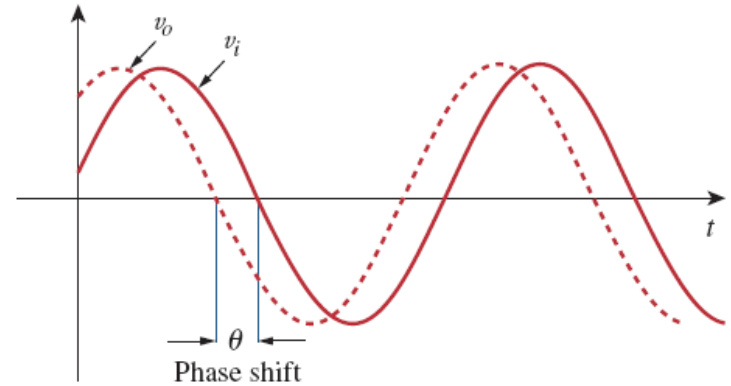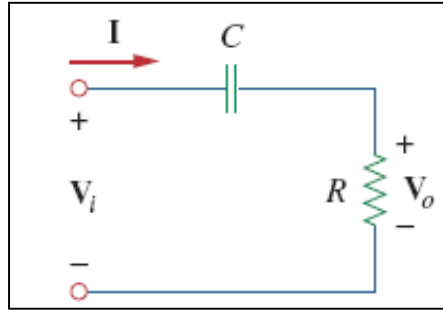

the circuit current I leads the applied voltage by some phase angle θ , where $0 < \theta < 90^\circ$ depending on the values of R and C .

$$Z = R + jX_C \quad \longrightarrow \quad \theta = \tan^{-1} \frac{X_C}{R}$$


the amount of phase shift depends on the values of R , C , and the operating frequency.

- These simple single stage RC circuits are generally not used in practice.
- These RC circuits also work as voltage dividers. Therefore, as the phase shift approaches 90° the output voltage approaches zero. For this reason, these simple RC circuits are used only when small amounts of phase shift are required.
- For large phase shifts, the RC networks are cascaded. This provides a total phase shift equal to the sum of the individual phase shifts.

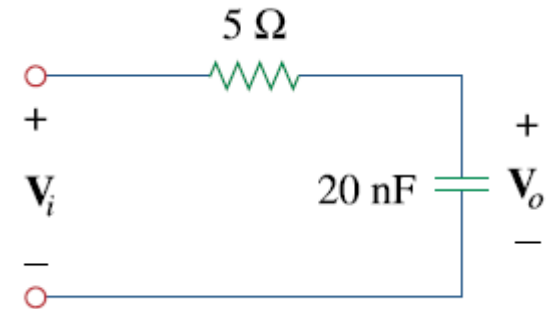Example – 10

For this RC circuit:

- Calculate the phase shift at 2 MHz.
- Find the frequency where the phase shift is 45° .



Example – 11

A coil with impedance $8 + j6\ \Omega$ is connected in series with a capacitive reactance X . The series combination is connected in parallel with a resistor R . Given that the equivalent impedance of the resulting circuit is $5\angle 0^\circ\ \Omega$, find the value of R and X .

Example – 12

Consider this phase-shifting circuit.

- V_o when R is maximum
- V_o when R is minimum
- the value of R that will produce a phase shift of 45° .

