


Lecture – 5

Date: 18.01.2016

- Voltage Reflection Coefficient
- Examples
- Standing Waves

Voltage Reflection Coefficient

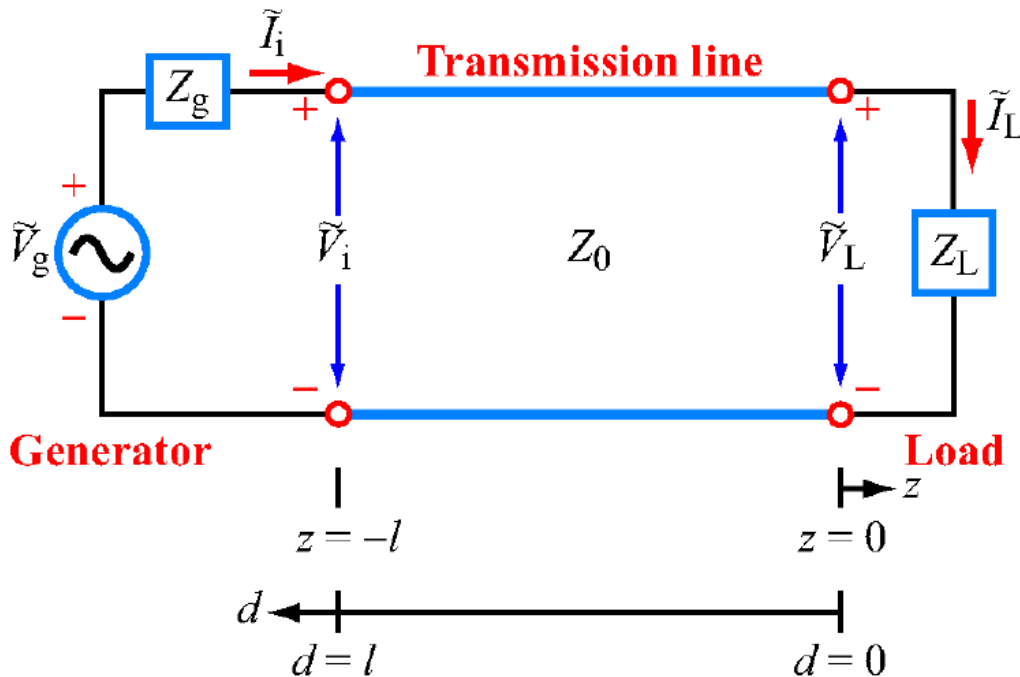- To determine the unknowns V_0^+ and V_0^- , we need to consider the lossless transmission line in the context of complete circuit including a generator circuit at its input terminals and a load at its output terminals.



At the load side:

$$Z_L = \frac{\tilde{V}_L}{\tilde{I}_L}$$

- Where, \tilde{V}_L and \tilde{I}_L are the total voltage and current at the load.

$$\tilde{V}_L = \tilde{V}(z = 0) = V_0^+ + V_0^-$$


$$\tilde{I}_L = \tilde{I}(z = 0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

Voltage Reflection Coefficient (contd.)

$$\tilde{V}_L = \tilde{V}(z=0) = V_0^+ + V_0^- \qquad \tilde{I}_L = \tilde{I}(z=0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} = \frac{V_0^+ - V_0^-}{Z_0}$$

$$Z_L = \frac{\tilde{V}_L}{\tilde{I}_L} \quad \longrightarrow \quad Z_L = \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0$$


- Solving for V_0^- gives: $V_0^- = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) V_0^+ \quad \longrightarrow \quad \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$

$\frac{V_0^-}{V_0^+}$  The ratio of the amplitudes of the reflected and the incident voltage waves at the load is called voltage reflection coefficient Γ

$$\therefore \Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

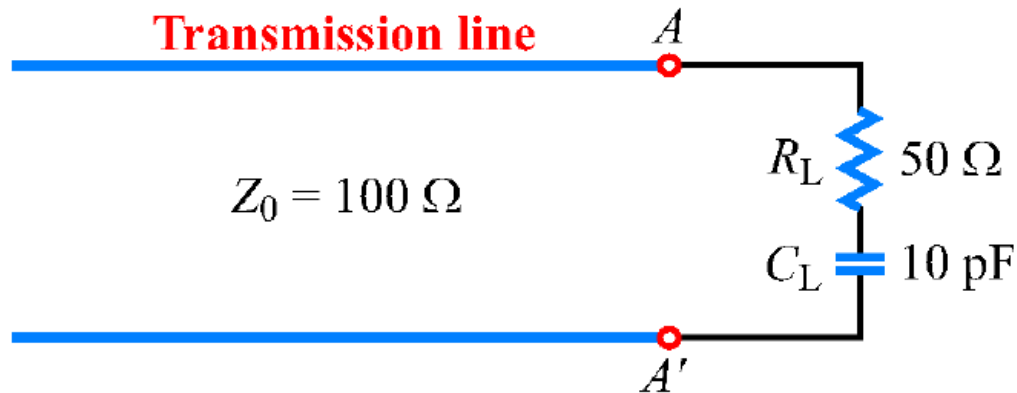Example – 1

- A 100Ω transmission line is connected to a load consisting of a 50Ω resistor in series with a 10pF capacitor. Find the reflection coefficient at the load for a 100MHz wave.



Example – 2


- A 150Ω lossless transmission line is terminated in a capacitor with impedance $Z_L = -j30\Omega$. Calculate Γ .

Example – 3

- Show that $|\Gamma| = 1$ for a lossless line connected to a purely reactive load.

Standing Wave and Standing Wave Ratio

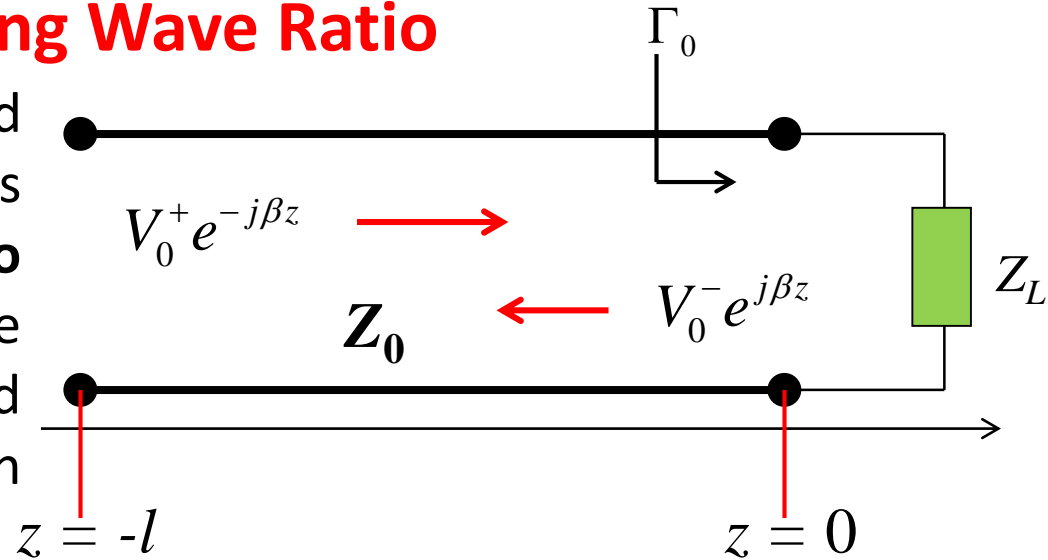- Another traditional real-valued measure of load match is **Voltage Standing Wave Ratio (VSWR)**. Consider again the **voltage** along a terminated transmission line, as a function of **position** z .



$$\tilde{V}(z) = V_0^+ \left[e^{-j\beta z} + \Gamma_0 e^{+j\beta z} \right]$$



$$\tilde{V}(-l) = V_0^+ \left[e^{j\beta l} + \Gamma_0 e^{-j\beta l} \right]$$

- For a short circuited line: $\Gamma_0 = -1$ $\Rightarrow \tilde{V}(-l) = V_0^+ \left(e^{+j\beta l} - e^{-j\beta l} \right)$
 $2j\sin(\beta l)$

$$\therefore \tilde{V}(-l) = 2jV_0^+ \sin \beta l$$

Standing Wave and Standing Wave Ratio (contd.)

$$v(-l, t) = \text{Re}(\tilde{V}(-l)e^{j\omega t}) = \text{Re}(2jV_0^+ \sin(\beta l)e^{j\omega t})$$

$$\therefore v(-l, t) = 2V_0^+ \sin(\beta l) \cos(\omega t + (\pi / 2))$$

Definitely not a traveling wave!!

Always zero for $-l=0$ i.e., the point of short-circuit

Where has the traveling wave $V(z)$ gone?


- As the time and space are decoupled \rightarrow No wave propagation takes place**
- The incident wave is 180° out of phase with the reflected wave \rightarrow gives rise to zero crossings of the wave at $0, \lambda/2, \lambda, 3\lambda/2$, and so on \rightarrow standing wave pattern!!!**

Standing Wave and Standing Wave Ratio (contd.)

Corresponding βl : $0, \pi, 2\pi, 3\pi$



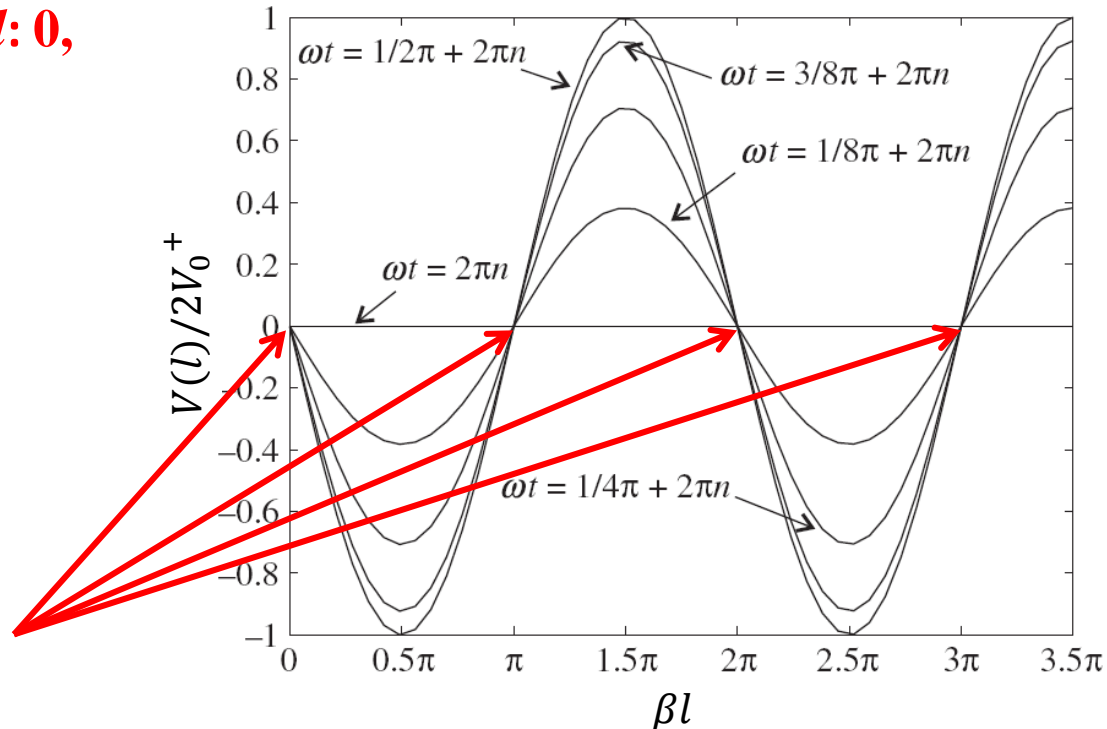Spatial Location:
 $0, \lambda/2, \lambda, 3\lambda/2$



Standing Wave Pattern for Various Instances of Time

- for arbitrarily terminated line:

$$\tilde{V}(-l) = V_0^+ \left(e^{+j\beta l} + \Gamma_0 e^{-j\beta l} \right) = V_0^+ e^{+j\beta l} \left(1 + \Gamma_0 e^{-j2\beta l} \right)$$

$$\Rightarrow \tilde{V}(-l) = A(-l) (1 + \Gamma(-l))$$



Valid anywhere
on the line

Standing Wave and Standing Wave Ratio (contd.)

$$\Rightarrow \tilde{V}(-l) = A(-l)(1 + \Gamma(-l)) \leftarrow \text{Valid anywhere on the line}$$

- Under the matched condition, $\Gamma_0 = 0$ and therefore $\Gamma(-l) = 0 \rightarrow$ as expected, only positive traveling wave exists.
- For other arbitrary impedance loads: Standing Wave Ratio (SWR) or Voltage Standing Wave Ratio (VSWR) is the measure of mismatch.
- SWR is defined as the ratio of maximum voltage (or current) amplitude and the minimum voltage (or current) amplitude along a line \rightarrow therefore, for an arbitrarily terminated line:

$$VSWR = \left| \frac{\tilde{V}(-l)_{\max}}{\tilde{V}(-l)_{\min}} \right|$$

We have: $\tilde{V}(-l) = V_0^+ e^{+j\beta l} (1 + \Gamma_0 e^{-j2\beta l})$


- Two possibilities for extreme values: $\Gamma_0 e^{-j\beta l} = 1$ $\Gamma_0 e^{-j\beta l} = -1$

Standing Wave and Standing Wave Ratio (contd.)

Max. voltage: $|\tilde{V}(-l)|_{\max} = |V_0^+|(1 + |\Gamma_0|)$ Min. voltage: $|\tilde{V}(-l)|_{\min} = |V_0^+|(1 - |\Gamma_0|)$

$$\therefore VSWR = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|}$$

Apparently: $0 \leq \Gamma_0 \leq 1$

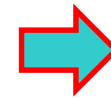

$$\therefore 1 \leq VSWR < \infty$$

- Note if $|\Gamma_0| = 0$ (i.e., $Z_L = Z_0$), then $VSWR = 1$. We find for this case:

$$|\tilde{V}(z)|_{\max} = |\tilde{V}(z)|_{\min} = |V_0^+|$$

In other words, the voltage magnitude is a **constant** with respect to position z .

- Conversely, if $|\Gamma_0| = 1$ (i.e., $Z_L = Z_0$), then $VSWR = \infty$. We find for **this** case:

$$|\tilde{V}(z)|_{\max} = 2|V_0^+|$$

$$|\tilde{V}(z)|_{\min} = 0$$

In other words, the voltage magnitude varies **greatly** with respect to position z .

In practice, SWR can only be defined for lossless line as the SWR equation is not valid for attenuating voltage and current

Example – 4

- A 50Ω lossless transmission line is terminated in a load with impedance $Z_L = (100 + j30)\Omega$. Calculate voltage reflection coefficient and the voltage standing wave ratio.