

**Fields and Waves**  
**Tutorial-2 19<sup>th</sup> January, 2016**

Ques1: A Telephone line has  $R = 30 \Omega/km$ ,  $L = 100 \text{ mH}/km$ ,  $G=0$  and  $C = 20 \mu\text{F}/km$ . Obtain characteristic impedance of the line, propagation constant and phase velocity at 1MHz.

Ques2: A transmission line of characteristic impedance of  $600\Omega$  is terminated by a reactance of  $j150\Omega$ , find the input impedances of sections 25cm long and 50 cm long at angular frequency 1884 M radians/sec.

Ques3: The following characteristics have been measured on a lossy transmission line at 100MHz:

$$\begin{aligned}Z_0 &= 50 + j0 \\ \alpha &= 0.01 \frac{\text{dB}}{\text{m}} \\ \beta &= 0.8\pi \text{ rad/m}\end{aligned}$$

Determine R,L,G and C.

**Home Assignment to be submitted and discussed during tutorial session.**

Ques1: A transmission line has  $R = 10.4 \Omega/km$ ,  $L = 3.666 \text{ mH}/km$ ,  $G = 0.08 \mu\text{mho}/km$  and  $C = 0.00835 \mu\text{F}/km$  at an angular frequency of 5000 radians/sec. Calculate attenuation constant, phase constant, phase velocity and characteristic impedance of the transmission line.

Ques2: A signal generator having an internal resistance  $1 \Omega$  and an open circuit voltage  $v_g(t) = 0.3 \cos(2\pi 10^8 t)$  (V) is connected to a  $50 \Omega$  lossless transmission line. The line is 4m long and velocity of wave propagation is  $2.5 \cdot 10^8$  m/s. For a matched load, find (a) instantaneous expressions for current and voltages at arbitrary positions on line (b) instantaneous expressions for current and voltages at load (c) average power transmitted.