

# Analog Circuit Design (ACD) – ECE520

## Home Assignment - 2


Total Marks: 10

Submission Deadline: 16.09.2013


### Instructions:

- Answer all the questions.
- Please adhere to institute's plagiarism policy.
- Submit before 5:00pm on the submission day. No late submission allowed.

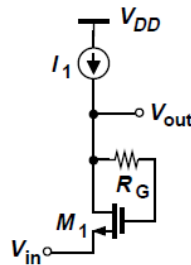
**Q1. [2.5 marks]** Calculate the voltage gain of the circuit shown below and comment on the type of configuration of the circuit



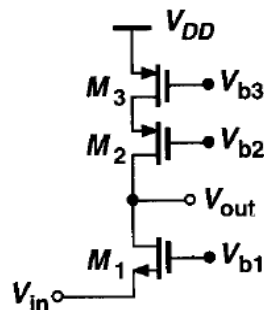**Q2. [2.5 marks]** Calculate the voltage gain of the circuits shown below:



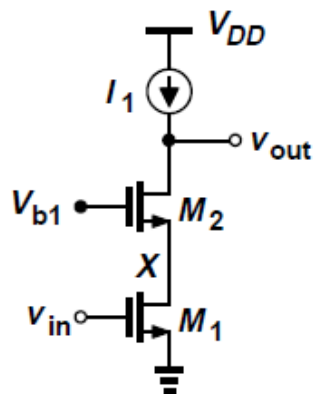**Q3. [2 marks]** The MOS cascode shown below must provide a voltage gain of 200. If  $\mu_n c_{ox} = 100 \mu\text{A}/\text{V}^2$  and  $\lambda = 0.1$  for both transistors, determine the required value of  $(W/L)_1 = (W/L)_2$



**Q4. [3 marks]** The MOS cascode of the circuit below must provide a bias current of 0.5 mA with an output impedance of at least 50k. If  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$  and  $(W/L) = 20/0.18$  for both transistors, compute the maximum tolerable value of  $\lambda$ .

