

Analog Circuit Design (ACD) – ECE520

Home Assignment - 2


Total Marks: 10

Submission Deadline: 23.09.2013


Instructions:

- Answer all the questions.
- Please adhere to institute's plagiarism policy.
- Submit before 5:00pm on the submission day. No late submission allowed.

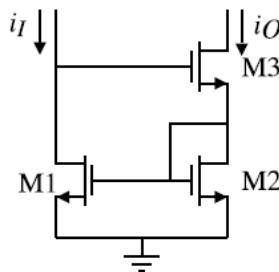
Q1. [3 marks] Determine the expression for input impedance (R_{in}) for the following circuit.



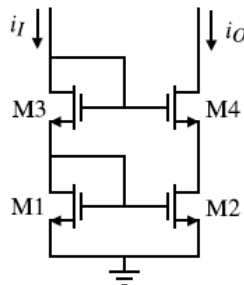Q2. [2 marks] Determine the expression for input impedance (R_{in}) for the following circuit.




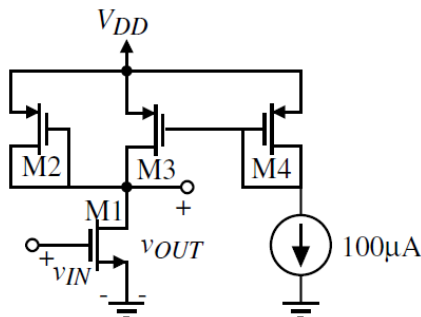Q3. [2.5 marks] Assume that W/L ratios in the following circuit are: $(W/L)_1=2\mu\text{m}/1\mu\text{m}$; $(W/L)_2=(W/L)_3=(W/L)_4= 1\mu\text{m}/1\mu\text{m}$. Find the dc value of V_{in} that will give a dc current in M1 of $110\mu\text{A}$. Calculate the small-signal voltage gain and output resistance.



Please use $\mu_n C_{ox} = 110\mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 36\mu\text{A}/\text{V}^2$, $V_{TN} = 0.73\text{V}$, $V_{TP} = -0.88\text{V}$, $V_{DD} = 5\text{V}$, $C_{ox} = 2.5 \times 10^{-15}\text{F}$

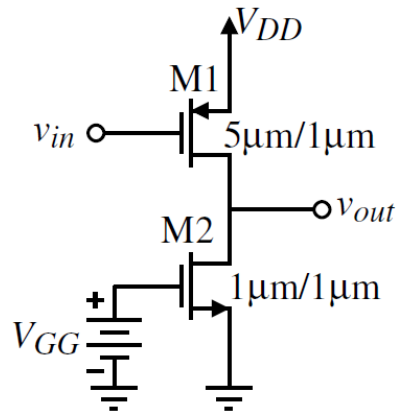Q4. [2.5 marks] A CMOS amplifier is shown below. Assume M1 and M2 operate in saturation. (a) what value of V_{GG} gives $100 \mu\text{A}$ through M1 and M2, (b) what is the dc value of V_{in} , (c) what is the small signal voltage gain (v_{in}/v_{out}) for this amplifier.



Please use $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 36 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.73\text{V}$, $V_{TP} = -0.88\text{V}$, $V_{DD} = 5\text{V}$, $C_{ox} = 2.5 \times 10^{-15}\text{F}$