

Analog Circuit Design (ACD) – ECE520

Home Assignment - 5

Total Marks: 10


Submission Deadline: 01.11.2013

Instructions:

- Answer all the questions.
 - Please adhere to institute's plagiarism policy.
 - Submit before 5:00pm on the submission day. No late submission allowed.
-

 Q1. [3 marks] In the following circuit assume that the bulk of the two NFETs are connected to the ground, $\lambda = 0$, and $\Upsilon \neq 0$.


- What is the region of operation of transistor M_1 ?
- Does the region of operation of M_1 depend on the relative sizing of the transistors?
- Assume that the I_{bias} and the transistor sizes are chosen such that the drain voltage of M_1 is very close to zero. Give an expression for the output resistance of the circuit seen at the drain of M_2 in terms of circuit parameters.



 Q2. [3 marks] Assuming that the following circuit is symmetrical and $\Upsilon = 0$: and $\lambda \neq 0$:

- Find the expression for the small-signal differential voltage gain $[V_{\text{out}} / (V_{\text{in1}} - V_{\text{in2}})]$ of the circuit at very low frequencies.
- What is the gain of the circuit at very high frequencies?


Note: In this question neglect all other capacitances that are not shown in the circuit



 Q3. [4 marks] Design a symmetric differential amplifier based on the topology shown below with the following design specifications:

- $V_{DD} = 1.8V$
- Total power consumption of 1.8mW
- Output DC level of 0.9V
- Total gain of 5
- $L = 0.4\mu m$ for all devices

Assume that the minimum required voltage at the drain of M_0 to keep it in saturation is 0.2V.



The technology parameters are:

$$\lambda(\text{NMOS}) = 0, \lambda(\text{PMOS}) = 0, \gamma = 0, V_{DD} = 1.8V, V_{TN} = |V_{TP}| = 0.4V, \\ \mu_n C_{ox} = 1\text{mA/V}^2, \mu_p C_{ox} = 0.5\text{mA/V}^2$$

- Find V_{bias1} , and all the transistor widths
- Find the minimum and maximum allowable input common-mode (input DC) levels.