

## HA # 2

1. Write MATLAB code to determine the input impedance of a transmission line that is terminated in a **short circuit**, and whose length is:

a) 
$$l = \frac{\lambda}{8} = 0.125\lambda$$
  $\Rightarrow$   $2\beta l = 90^{\circ}$   
b)  $l = \frac{3\lambda}{8} = 0.375\lambda$   $\Rightarrow$   $2\beta l = 270^{\circ}$ 



Indraprastha Institute of Information Technology Delhi

- 2. A load **terminating** at transmission line has a normalized impedance  $z_L' = 2.0 + j2.0$ . What should the **length** l of transmission line be in order for its input impedance to be:
  - a) Purely **real** (i.e.,  $X_{in} = 0$ )
  - b) Have a real (resistive) part equal to **one** (i.e.,  $r_{in} = 1.0$ )
  - Write MATLAB code to demonstrate the achieved solutions on Smith Chart.
  - Demonstrate this using ADS Design Guide.
- 3. A load impedance  $Z_{\rm L} = (20 + j40)\Omega$  is connected to a 50 $\Omega$  TL of 1cm length and operated at 2 GHz. Use the reflection coefficient concept to find the input impedance  $Z_{\rm in}$  under the assumption that the phase velocity is 100% of the speed of light. Compare the obtained results using Analytical Technique and ADS Design Guide.



- For an open-circuited 50Ω TL operated at 3GHz and with a phase velocity of 77% of speed of light, find the line lengths to create a 2pF capacitor and 5.3nH inductor. Demonstrate this using ADS Design Guide.
  - 5. Using MATLAB, convert and demonstrate the following normalized input impedance  $z_{in}'$  into normalized input admittance  $y_{in}'$  on the Z-Smith chart:

$$z_{in} = 0.5 + j0.5$$

6. Given:  $z_{in} = 1 + j2$ 

Use ADS Design Guide to demonstrate the normalized admittance  $\lambda/8$  away from the load