

## **Lecture – 10**

**Date: 04.02.2016**


- The Signal Flow Graph

## Signal Flow Graph

**Q:** Using individual device scattering parameters to analyze a complex microwave network results in a lot of **messy** math! Isn't there an **easier** way?

**A:** Yes! We can represent a microwave network with its **signal flow graph (SFG)** and then decompose this graph using a standard set of rules → results into simpler analysis.

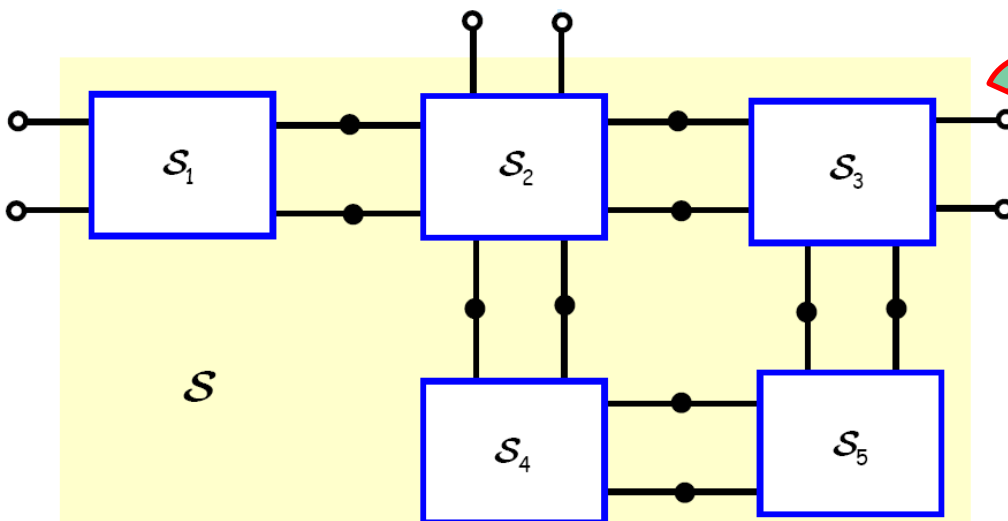- To understand the significance of SFG, let us consider a complex **3-port** microwave network constructed of **5** simpler microwave devices



It provides a sort of a **graphical** way to do algebra!

$S_n$  is the **scattering matrix** of each device, and  $S$  is the **overall** scattering matrix of the **entire 3-port network**

## Signal Flow Graph (contd.)

The S-parameter ( $S$ ) of the whole network can be obtained from the knowledge of S-parameter of individual devices

**Tedious Algebra!**

**Alternative is SFG based solution!**

### Signal flow graphs are helpful in three ways!

**Way 1** – It provide us with a **graphical** means of **solving** large systems of simultaneous equations.

**Way 2** – We'll see that it can provide us with a **road map** of the wave **propagation paths** throughout a HF device or network. If we're paying attention, we can glean great **physical insight** as to the inner working of the device represented by the graph.


**Way 3** – It provide us with a quick and accurate method for **approximating** a network or device. We will find that we can often replace a rather complex graph with a much **simpler** one that is **almost** equivalent.

## Signal Flow Graph (contd.)

We find this to be very helpful when **designing** microwave components. From the analysis of these approximate graphs, we can often determine **design rules** or equations that are tractable, and allow us to design components with (near) optimal performance.
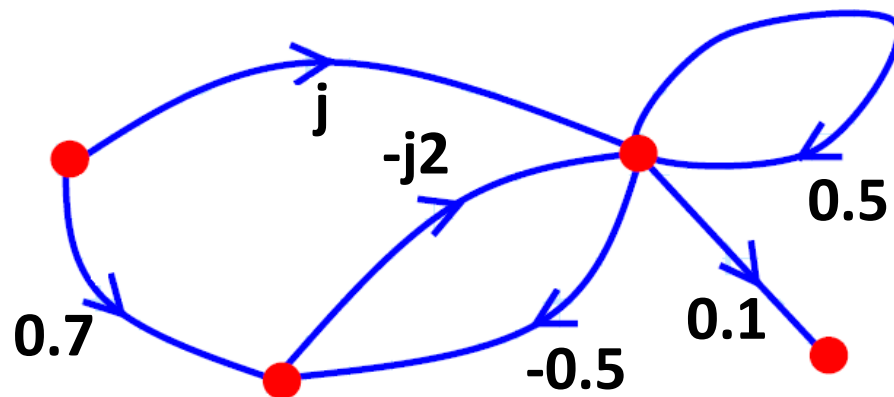
### Some definitions!

Every SFG consists of a set of **nodes**. These nodes are connected by **branches**, which are simply contours with a specified **direction**. Similarly, each branch has an associated complex **value**.



**Q:** What could this possibly have to do with **RF/microwave engineering**?

## Signal Flow Graph (contd.)

- In high frequency applications, each **port** of a device is represented by **two nodes**—the “a” node and the “b” node. The “a” node simply represents the value of the **normalized amplitude** of the wave incident on that port, evaluated **at** the plane of that port:

$$a_n = \frac{V_n^+ (z_n = z_{nP})}{\sqrt{Z_{0n}}}$$


- Similarly, the “b” node simply represents the **normalized amplitude** of the wave **exiting** that port, evaluated **at** the plane of that port:

$$b_n = \frac{V_n^- (z_n = z_{nP})}{\sqrt{Z_{0n}}}$$

- Then the **total voltage** at a port is simply:


$$V_n (z_n = z_{nP}) = (a_n + b_n) \sqrt{Z_{0n}}$$

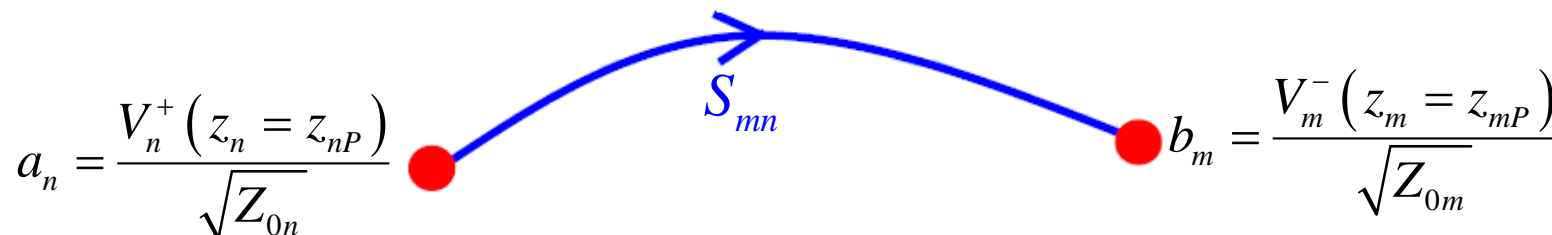- The value of the **branch** connecting two nodes is simply the value of the **scattering parameter** relating these two voltage values.


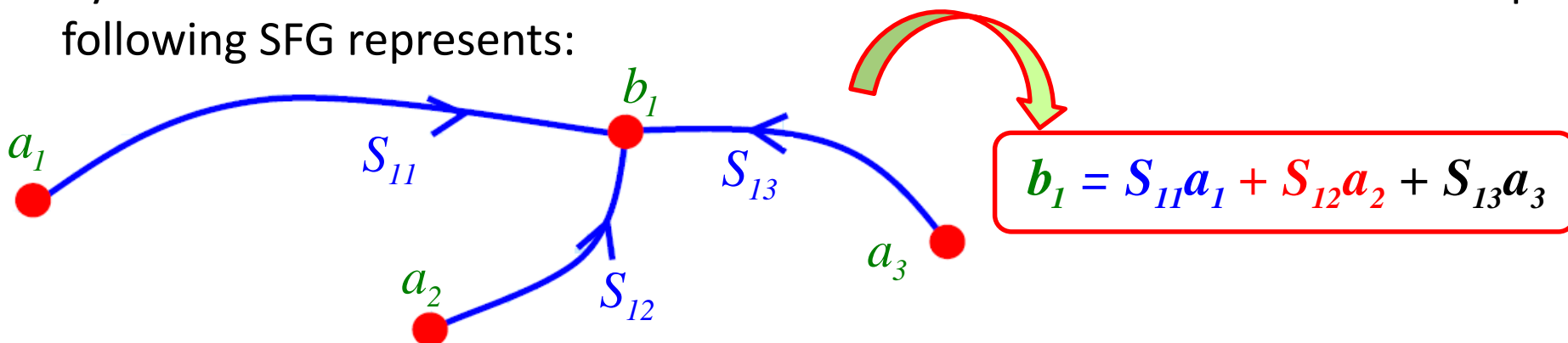
## Signal Flow Graph (contd.)

- The signal flow graph is simply **graphical** representation of the equation:
- Moreover, if **multiple** branches enter a node, then the voltage represented by that node is the **sum** of the values from each branch. For example, following SFG represents:




- Now, consider a **two-port device** with a scattering matrix  $\mathbf{S}$ :

$$\mathbf{S} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$


So that:  $b_1 = S_{11}a_1 + S_{12}a_2$      $b_2 = S_{21}a_1 + S_{22}a_2$

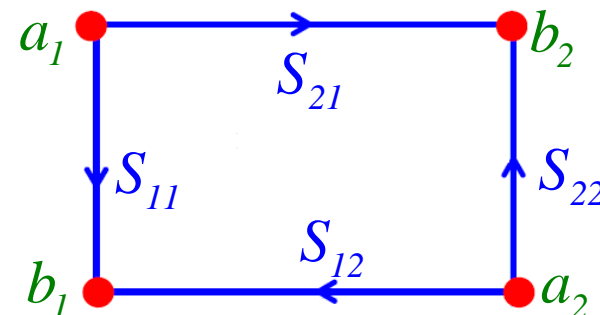- We can then **graphically** represent a **two-port device** as:


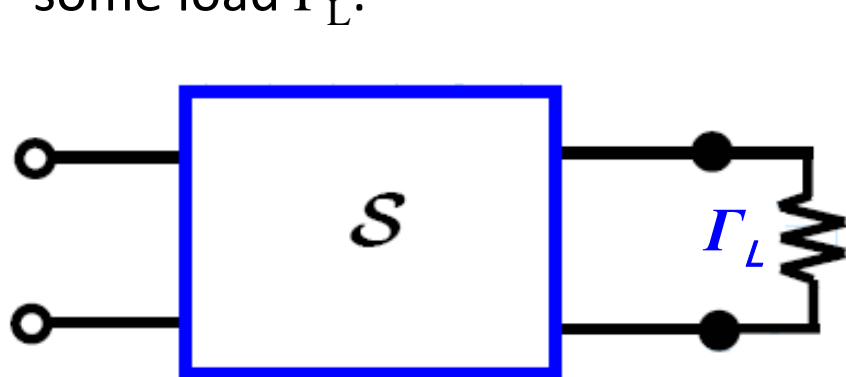
## Signal Flow Graph (contd.)

- Now, consider a two-port device where the second port is **terminated** by some load  $\Gamma_L$ :




**Additional  
Equation**

$$V_2^+(z_2 = z_{2P}) = \Gamma_L V_2^-(z_2 = z_{2P})$$


$$\Rightarrow a_2 = \Gamma_L b_2$$

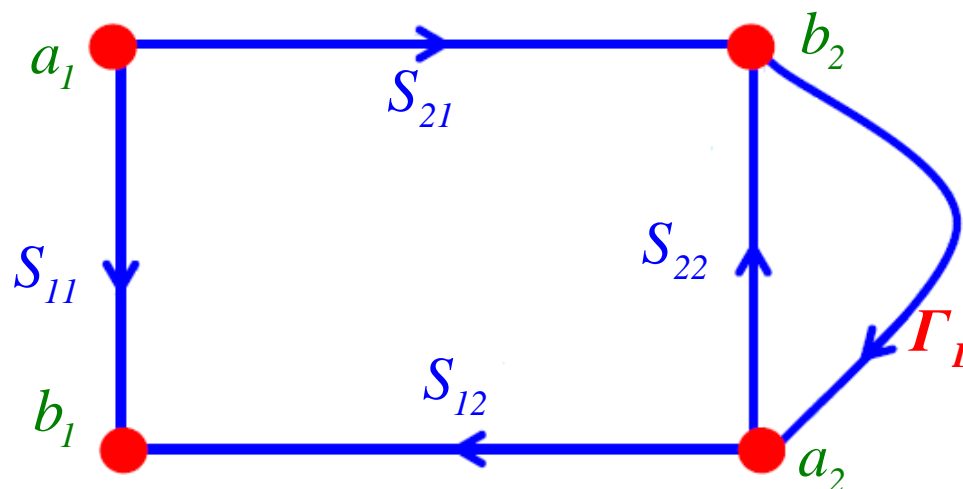- Therefore, the signal flow graph of this **terminated** network is:


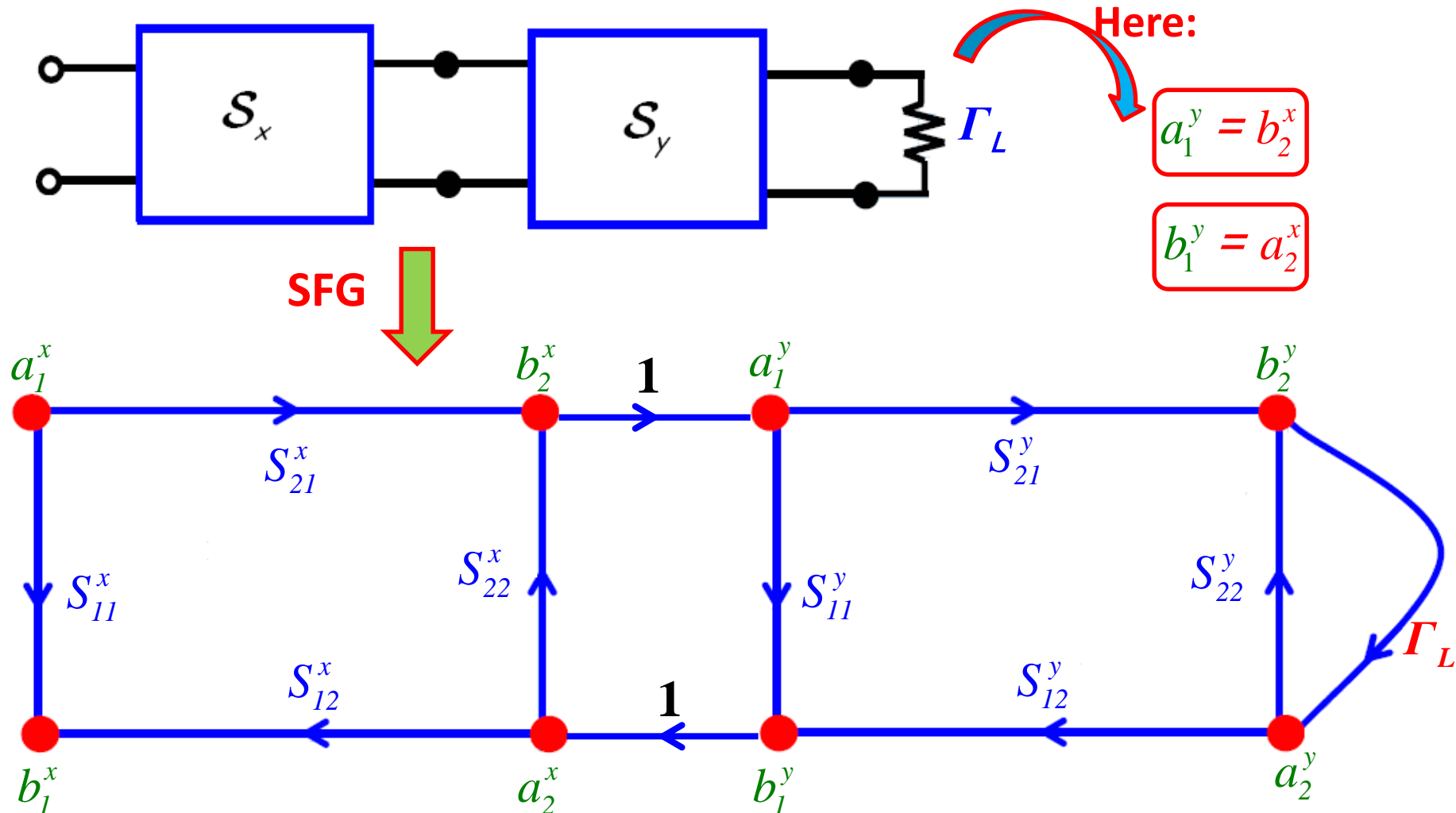
## Signal Flow Graph (contd.)


- Now consider cascading of **two different** two-port networks





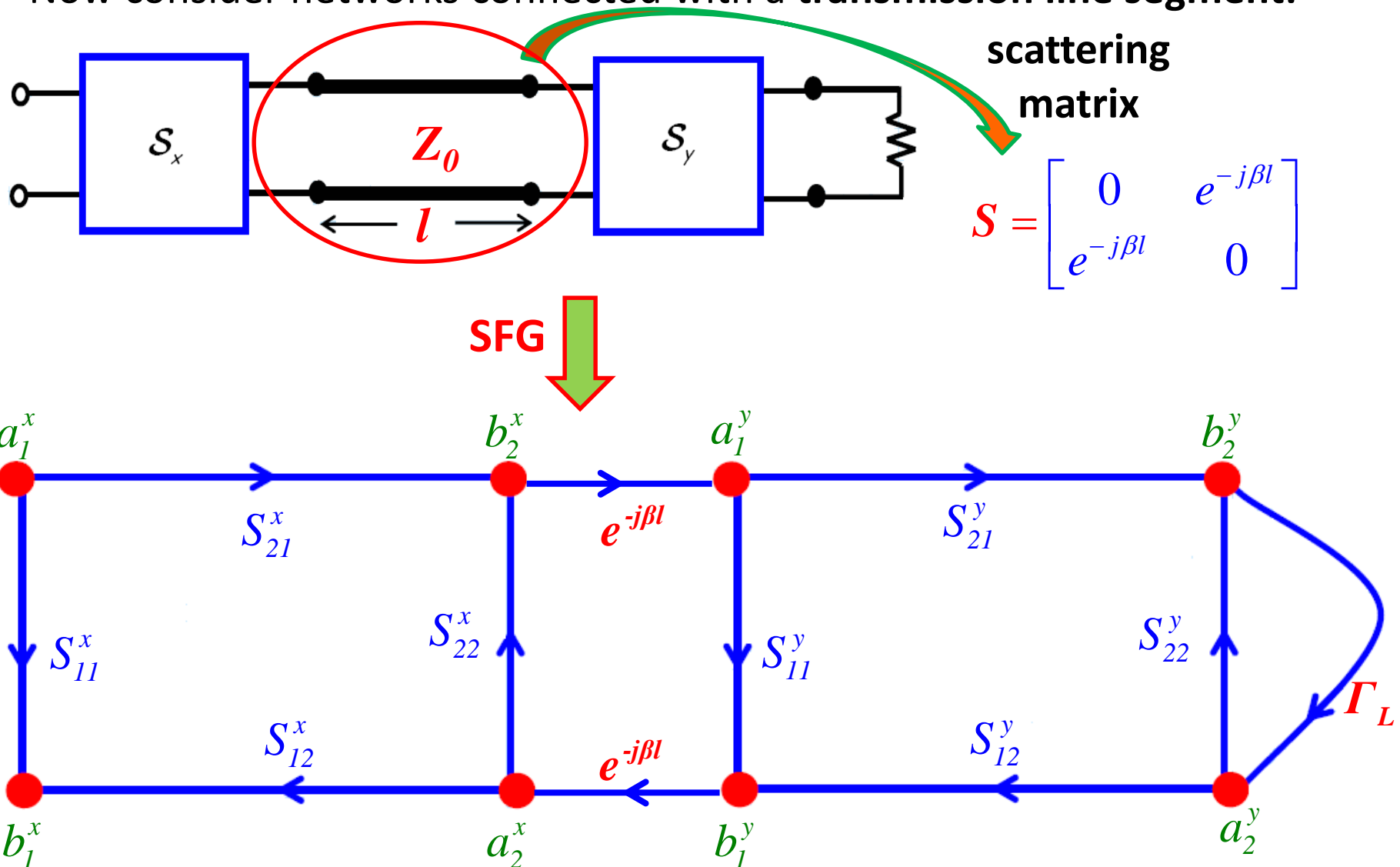
## Signal Flow Graph (contd.)

- Now consider networks connected with a **transmission line segment**:



## Signal Flow Graph (contd.)

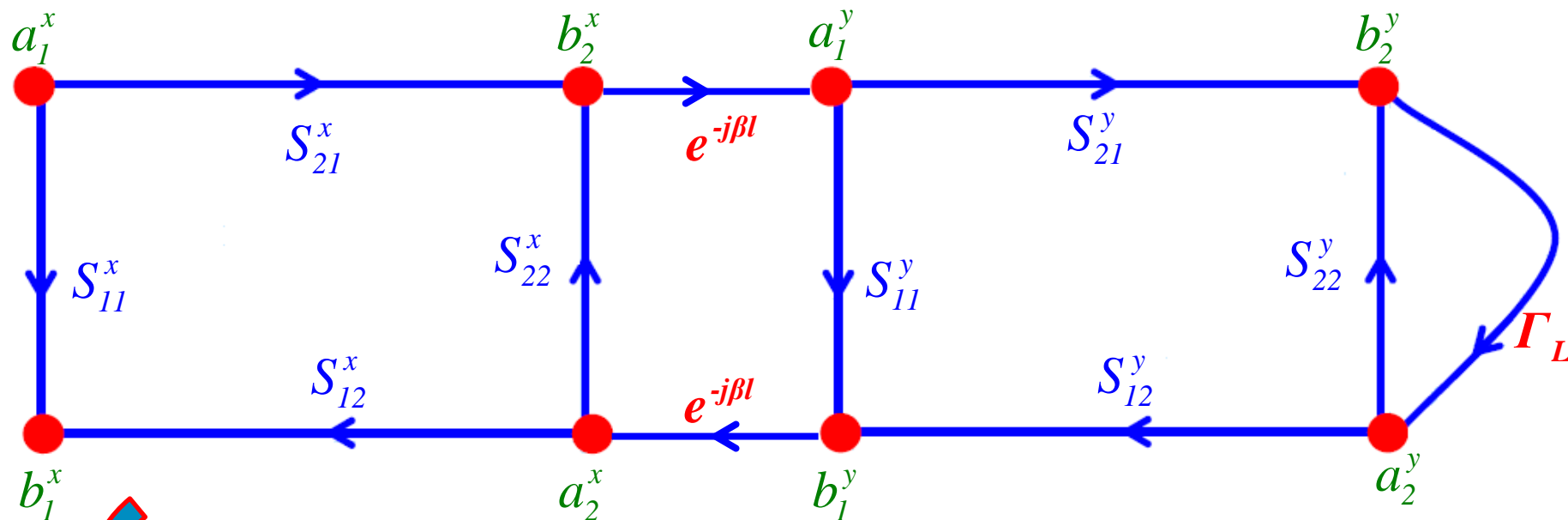

Note that there is **one** (and only one!) independent variable in this graphical representation (i.e., SFG)  $\rightarrow a_1^x$

This is the only node of the SFG that does **not** have any **incoming** branches. As a result, its value depends on **no other** node values in the SFG

**Independent nodes in the SFG are called sources!**

## Signal Flow Graph (contd.)



Independent nodes in the SFG are called sources!

- This makes sense physically (do **you** see why?)
- The node value  $a_1^x$  represents the complex amplitude of the wave **incident** on the one-port network. If this value is **zero**, then **no power** is incident on the network—the rest of the nodes (i.e., wave amplitudes) will be **zero**!

Now, say we wish to determine, for example:

1. The **reflection coefficient**  $\Gamma_{in}$  of the one-port device
2. The **total current** at port 1 of second network (i.e., network y)
3. The **power absorbed** by the load at port 2 of the **second (y) network**.

## Signal Flow Graph (contd.)

- In the first case, we need to determine the value of dependent node  $b_1^x$ :

$$\Gamma_{in} = \frac{b_1^x}{a_1^x}$$

- For the third and final case, the values of nodes  $a_2^y$  and  $b_2^y$  are required:

- For the second case, we must determine the value of wave amplitudes  $a_1^y$  and  $b_1^y$ :

$$I_1^y = \frac{a_1^y - b_1^y}{\sqrt{Z_0}}$$

$$P_{abs} = \frac{|b_2^y|^2 - |a_2^y|^2}{2}$$

solve the **simultaneous equations** that describe this network.

How do we **determine** the values of these wave amplitude “nodes”?

**Decompose (reduce)** the SFG!

## Signal Flow Graph (contd.)

- SFG **reduction** is a method for **simplifying** the **complex** paths of that SFG into a more **direct (but equivalent!)** form.
  - Reduction is really just a **graphical** method of **decoupling** the simultaneous equations that are **described** by the SFG.
- SFGs can be reduced by applying one of **four simple rules**.

**Q:** Can these rules be applied in **any order**?

**A: YES!** The rules can only be applied when/where the structure of the SFG allows. You must **search** the SFG for structures that allow a rule to be applied, and the SFG will then be (a little bit) reduced. You then search for the **next** valid structure where a rule can be applied. Eventually, the SFG will be **completely reduced!**

It's a bit like solving a **puzzle**. Every SFG is different, and so each requires a different reduction procedure. It requires a little **thought**, but with a little practice, the reduction procedure can be **easily** mastered → **You may find its kind of a fun! (TRUST ME)**

## Signal Flow Graph (contd.)


### Series Rule

- Consider these two complex equations:  $b_1 = \alpha a_1$        $a_2 = \beta b_1$
- These two equations can be combined to form an **equivalent set** of equations:

$$b_1 = \alpha a_1$$

$$a_2 = \beta b_1 = \beta(\alpha a_1) = \alpha\beta a_1$$

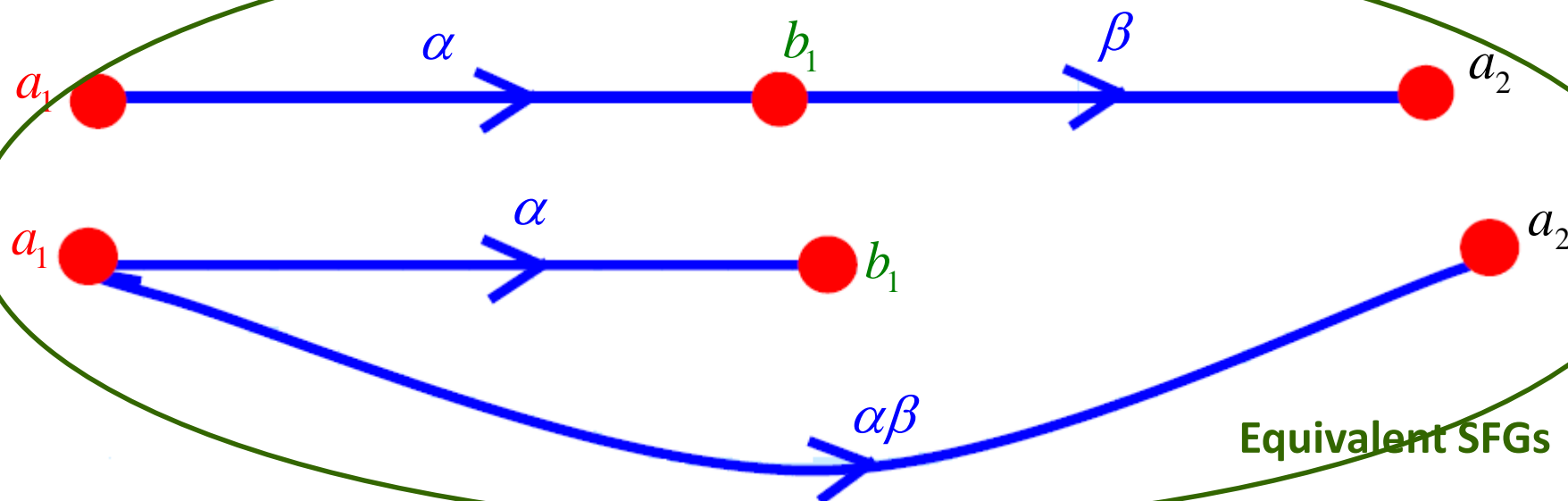- Graphically they can be represented as:




## Signal Flow Graph (contd.)

This leads us to our **first SFG reduction rule**:

### Rule 1 - Series Rule

If a node has **one** (and only one!) incoming branch, and **one** (and only one!) outgoing branch, the node can be eliminated and the two branches can be combined, with the new branch having a value equal to the product of the original two.


### Example:

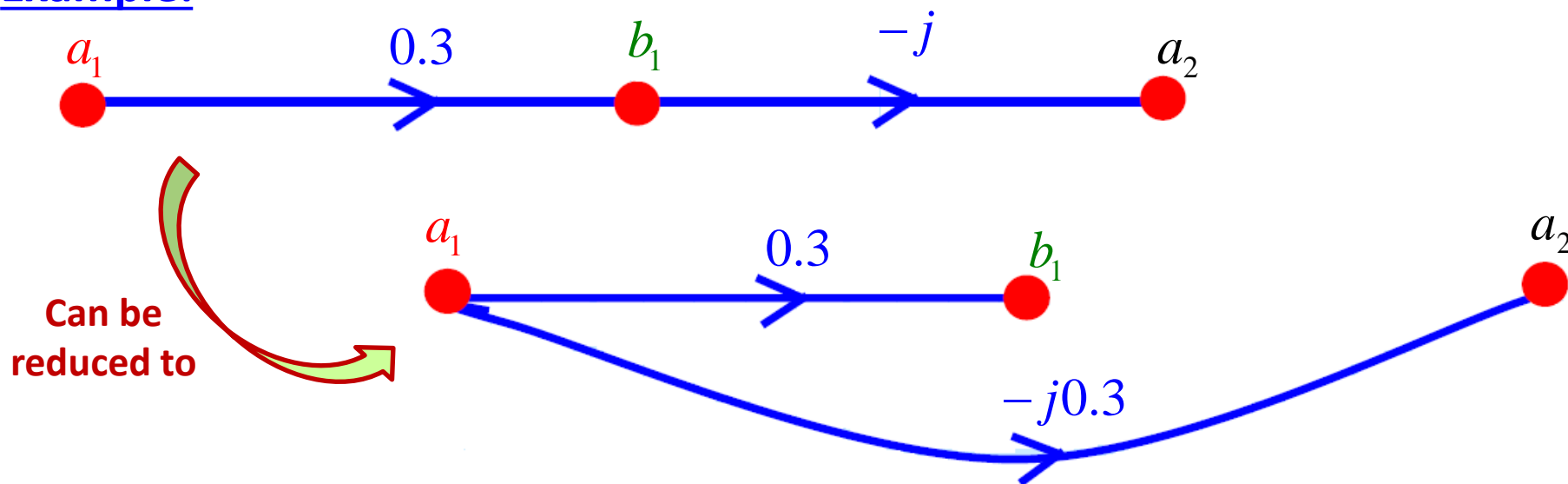

## Signal Flow Graph (contd.)
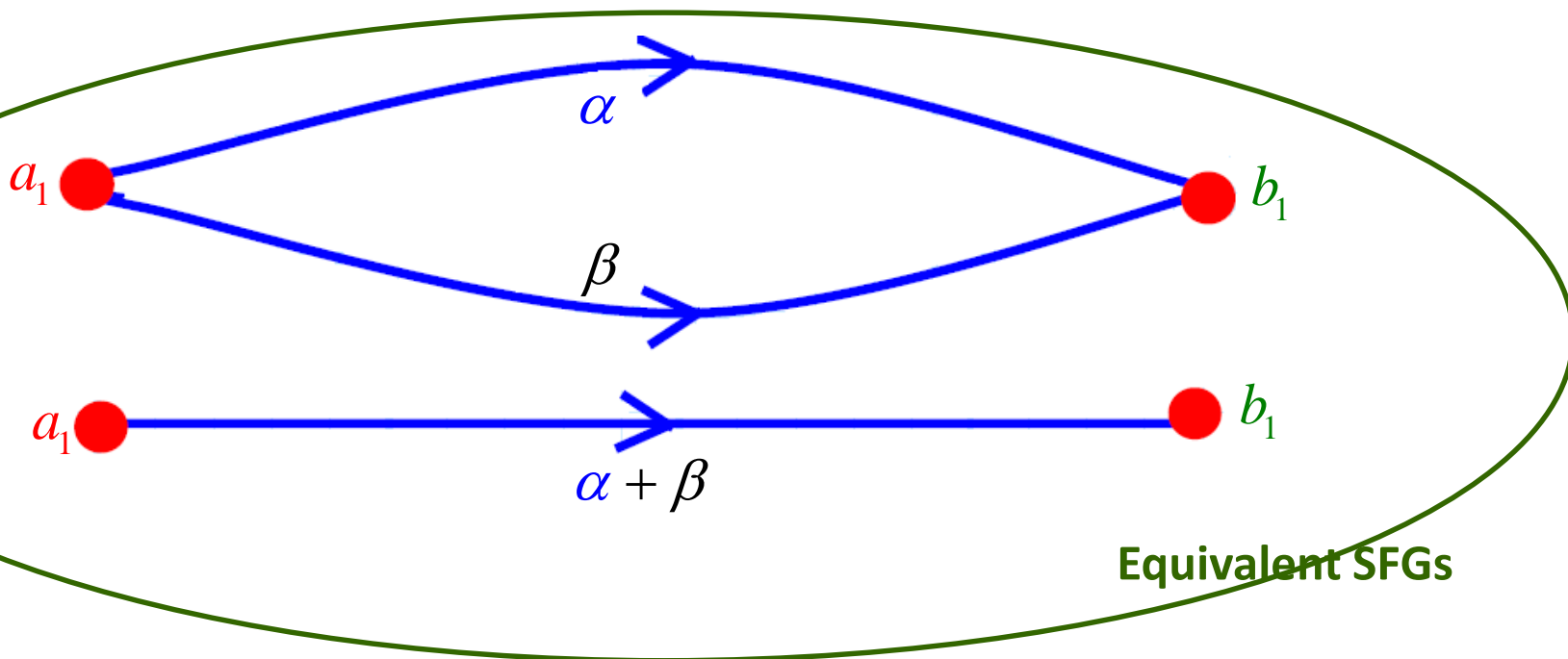
### Parallel Rule

- Consider these two complex equations:  $b_1 = \alpha a_1 + \beta a_1$
- The equation can also be expressed as:  $b_1 = (\alpha + \beta) a_1$
- These equations can be expressed in terms of SFG as:






## Signal Flow Graph (contd.)

This leads us to our **second SFG reduction rule**:

### Rule 2 - Parallel Rule



If two nodes are connected by parallel branches—and the branches have the **same direction**—the branches can be combined into a single branch, with a value equal to the **sum** of each two original branches.

### Example:

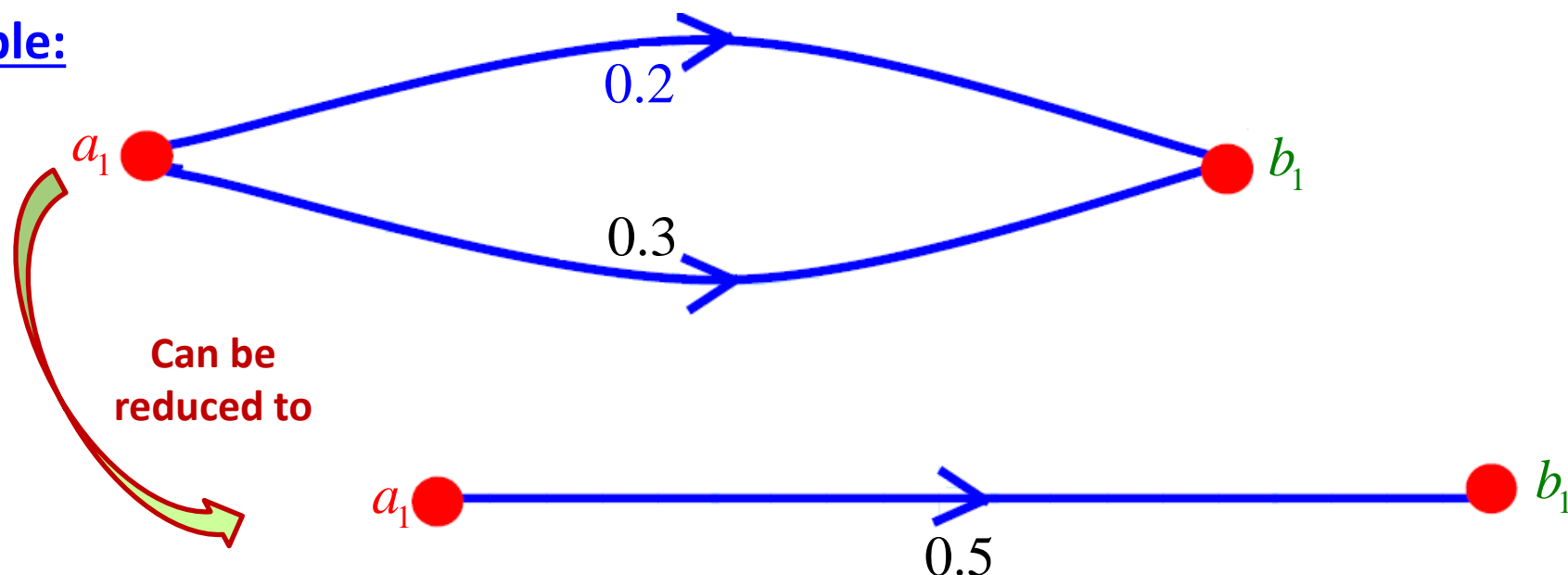


## Signal Flow Graph (contd.)

What about **this** signal flow graph?

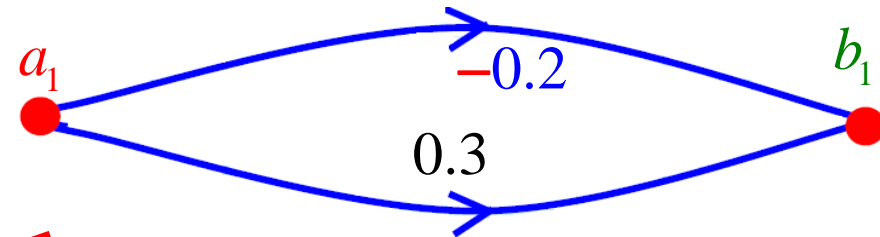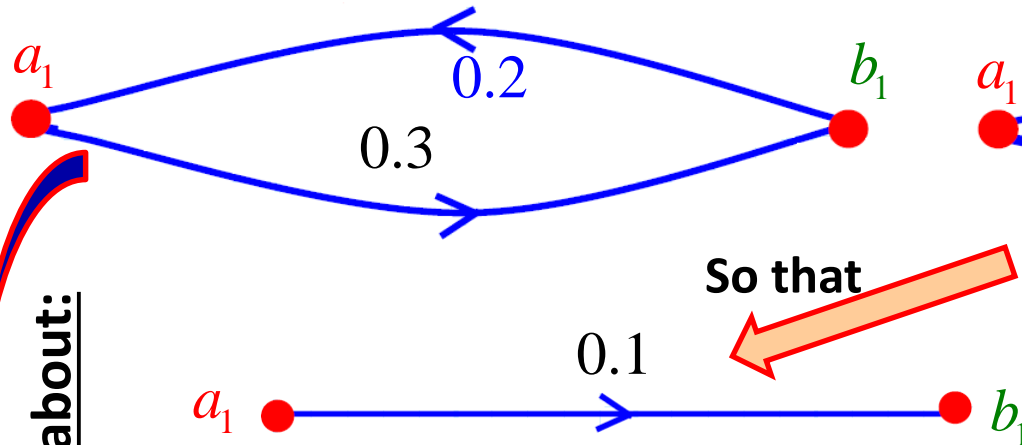


Absolutely not!  
**NEVER DO THIS!!**

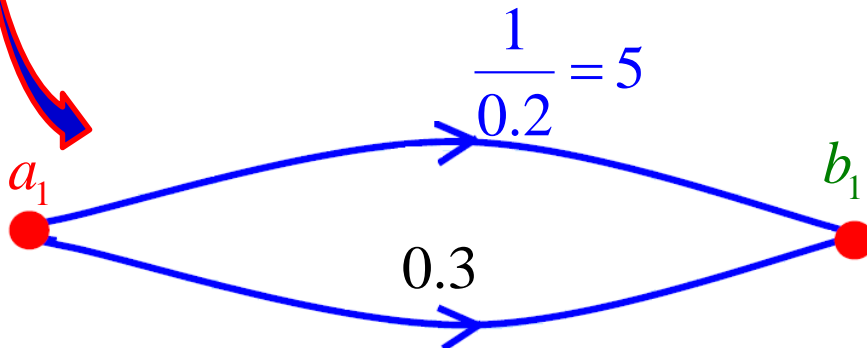

Absolutely not! **NEVER DO THIS EITHER!!**

## Signal Flow Graph (contd.)

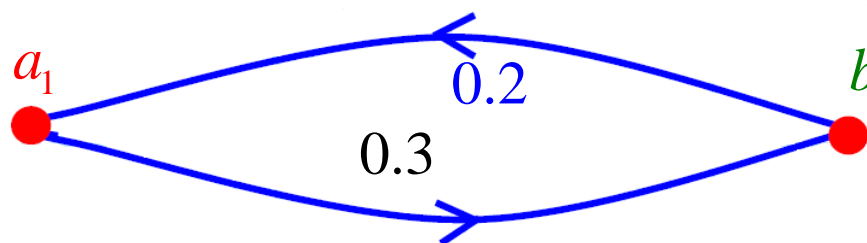

Actually from this SFG we can only conclude that


$$b_1 = 0.3a_1$$

$$a_1 = 0.2b_1$$

$$a_1 = 0.06a_1$$

$$b_1 = 0.3a_1$$

SFG can be of the form

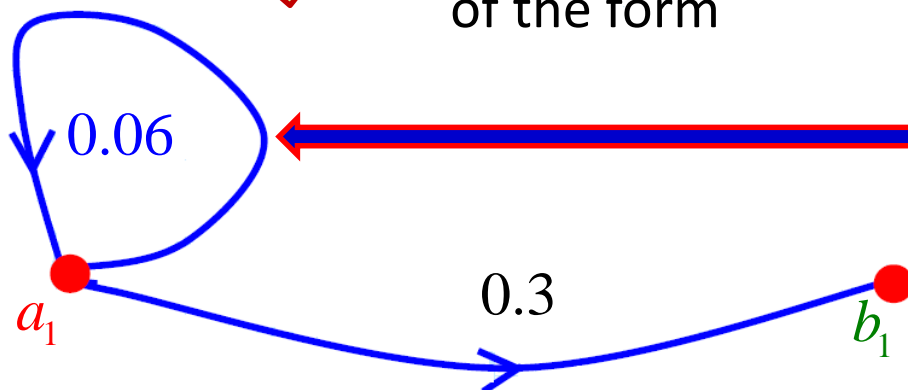


Branches that begin and end at the same node are called self-loops

In practical situations, self-loop node will **always** have at least **one other incoming branch**

## Signal Flow Graph (contd.)
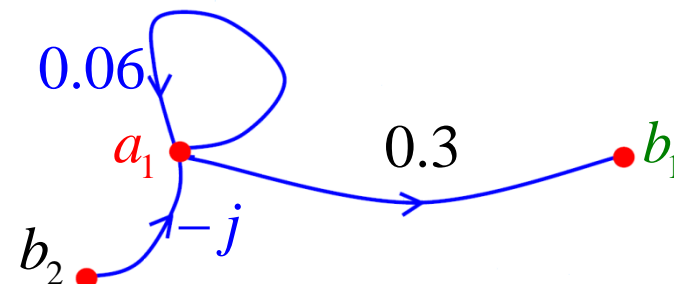
### Practical example of node with self-loop:




### Self-Loop Rule

- Consider the complex equation:


$$b_1 = \alpha a_1 + \beta a_2 + \gamma b_1$$

- A little bit of **algebra** allows us to determine the value of node  $b_1$ :
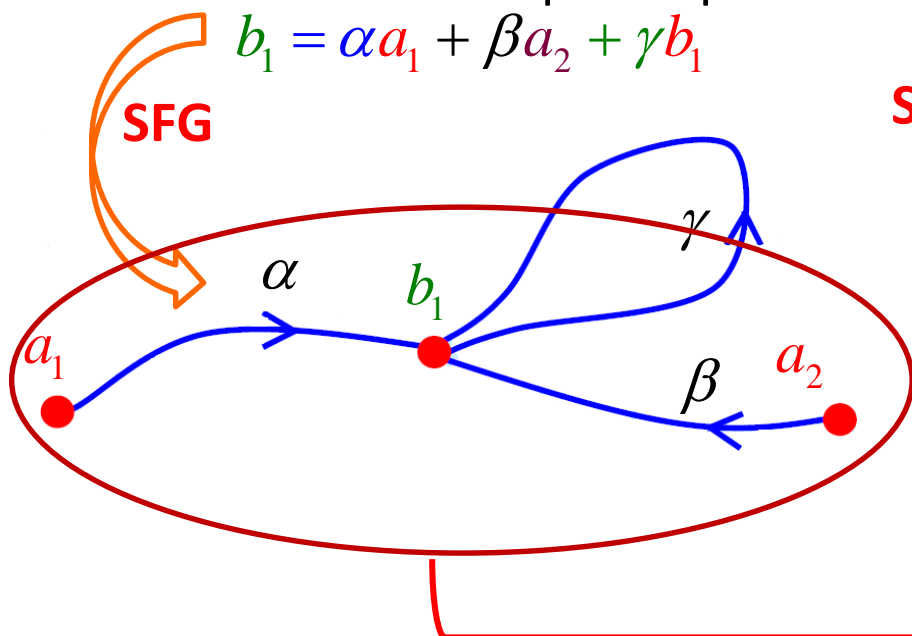
$$b_1 = \frac{\alpha}{1-\gamma} a_1 + \frac{\beta}{1-\gamma} a_2$$



**SFG**

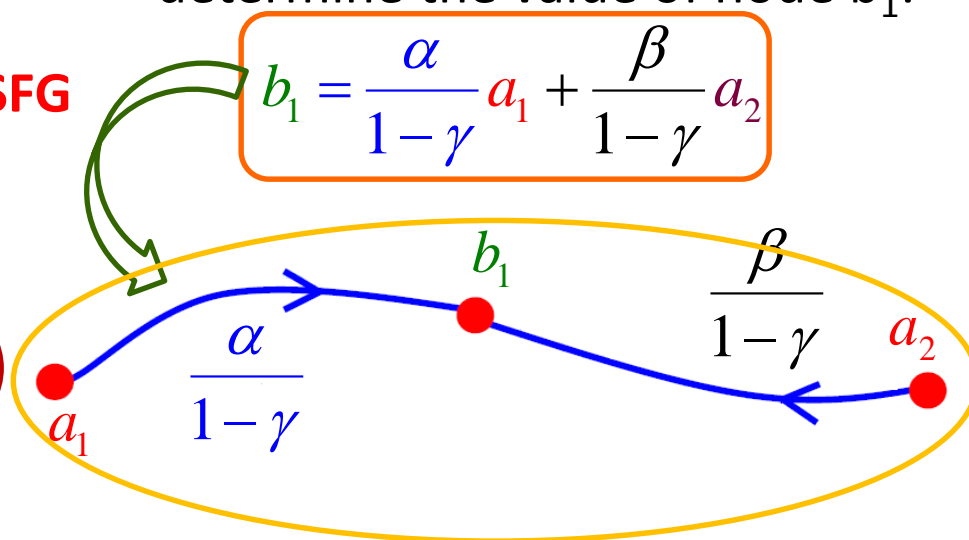

**Equivalent**


## Signal Flow Graph (contd.)

This leads us to our **third SFG reduction rule**:

### Rule 3 – Self-Loop Rule

A self-loop can be eliminated by multiplying **all** of the branches “**feeding**” the self-loop node by  $1(1-S_{sl})$ , where  $S_{sl}$  is the value of the self loop branch.


### Example

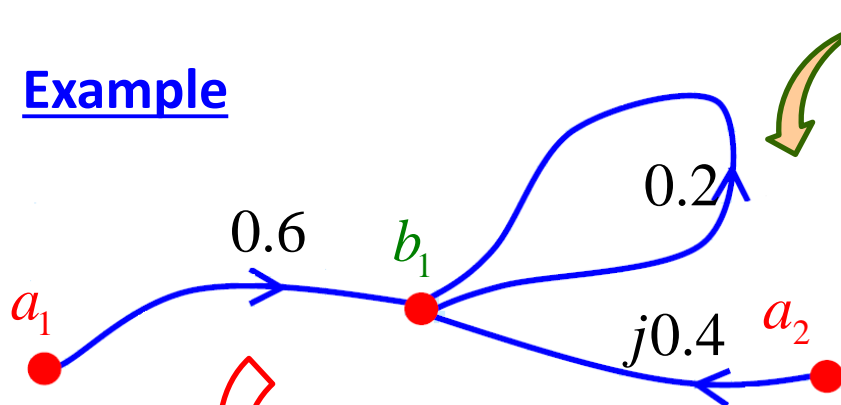

can be simplified by **eliminating the self-loop** → multiply **both** of the two branches **feeding** the self-loop node by:


$$\frac{1}{1-S_{sl}} = \frac{1}{1-0.2} = 1.25$$

Simplified and Reduced

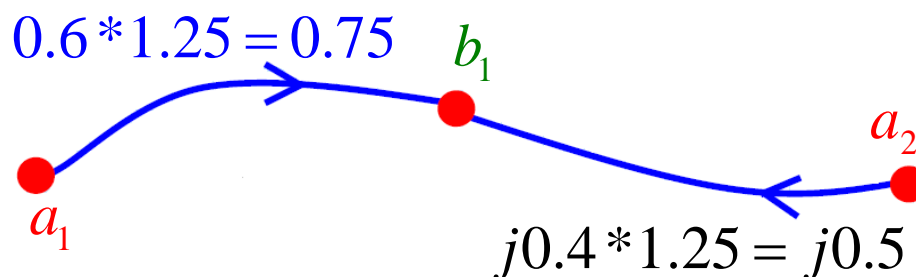

## Signal Flow Graph (contd.)

### Example

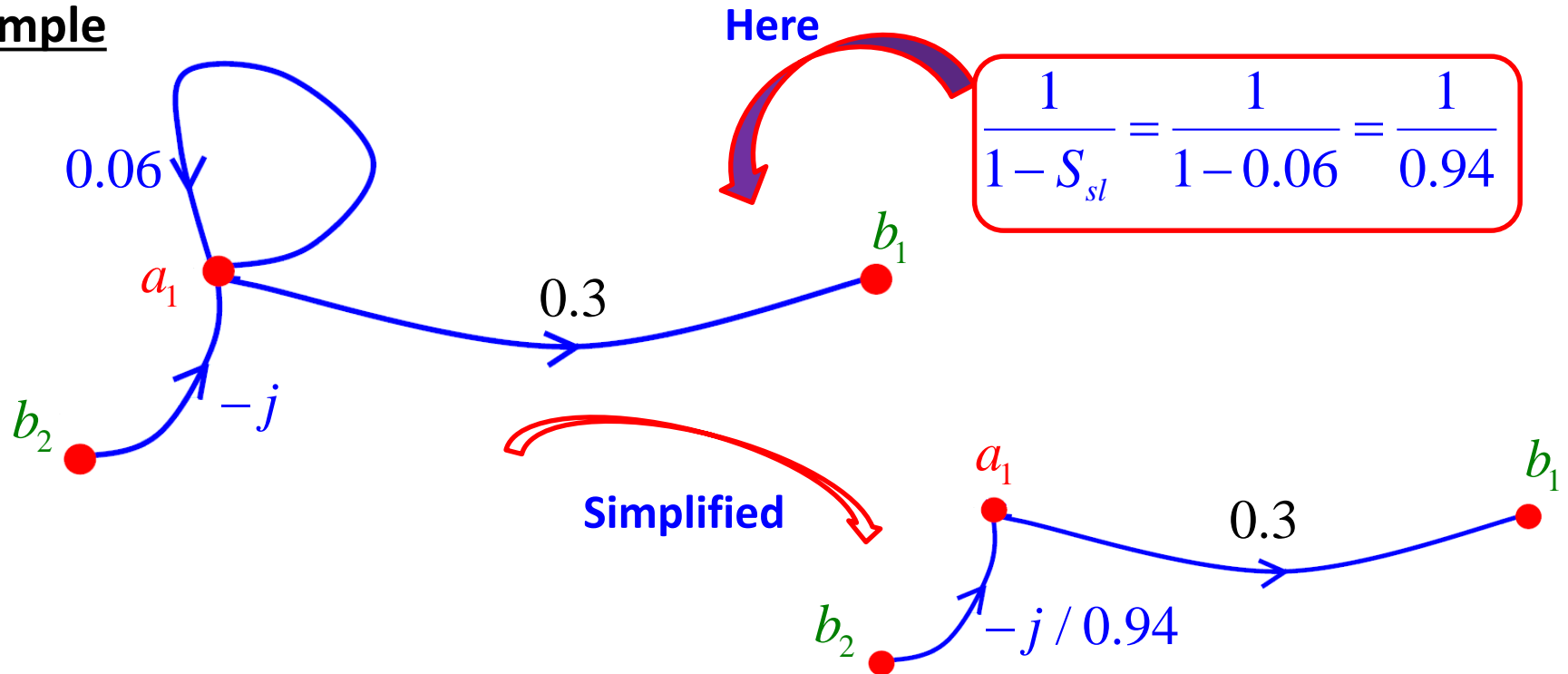

Only the incoming branches are modified by the self-loop rule! Here, the  $0.3$  branch is **exiting** the self-loop node  $a_1$  and therefore doesn't get modified. **Only** the  $-j$  branch (incoming at node  $a_1$ ) to the self-loop node are modified by the self-loop rule!

## Signal Flow Graph (contd.)


### Splitting Rule

- Now consider the three equations

$$b_1 = \alpha a_1$$

$$a_2 = \beta b_1$$

$$a_3 = \gamma b_1$$

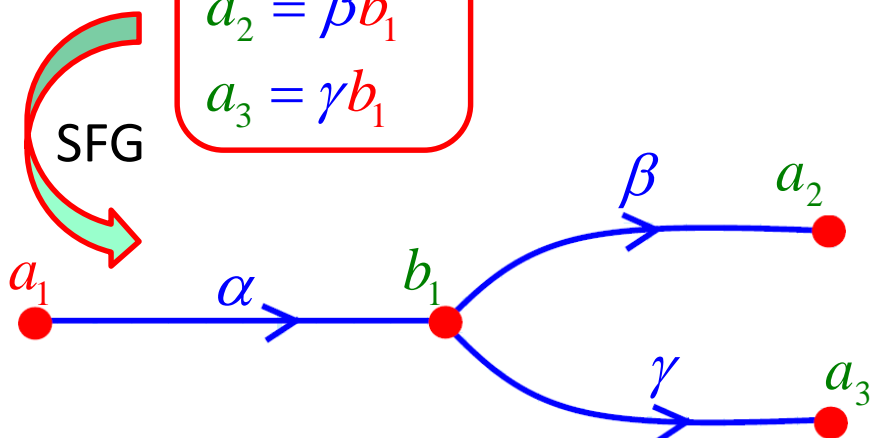


- These equations can be equivalently written as

$$b_1 = \alpha a_1$$

$$a_2 = \alpha \beta a_1$$

$$a_3 = \gamma b_1$$

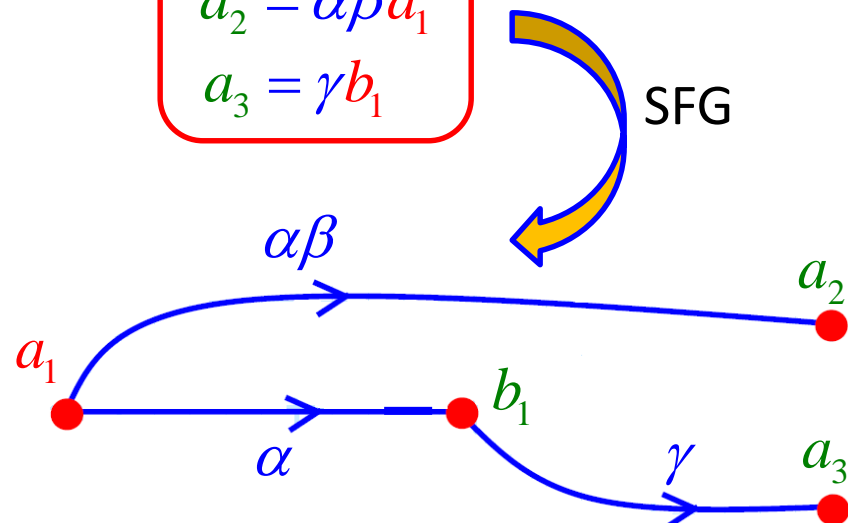


### Rule 4 – Splitting Rule

If a node has one (and only one!) incoming branch, and one (or more) exiting branches, the incoming branch can be “split”, and directly combined with each of the exiting branches.

## Signal Flow Graph (contd.)



### Example

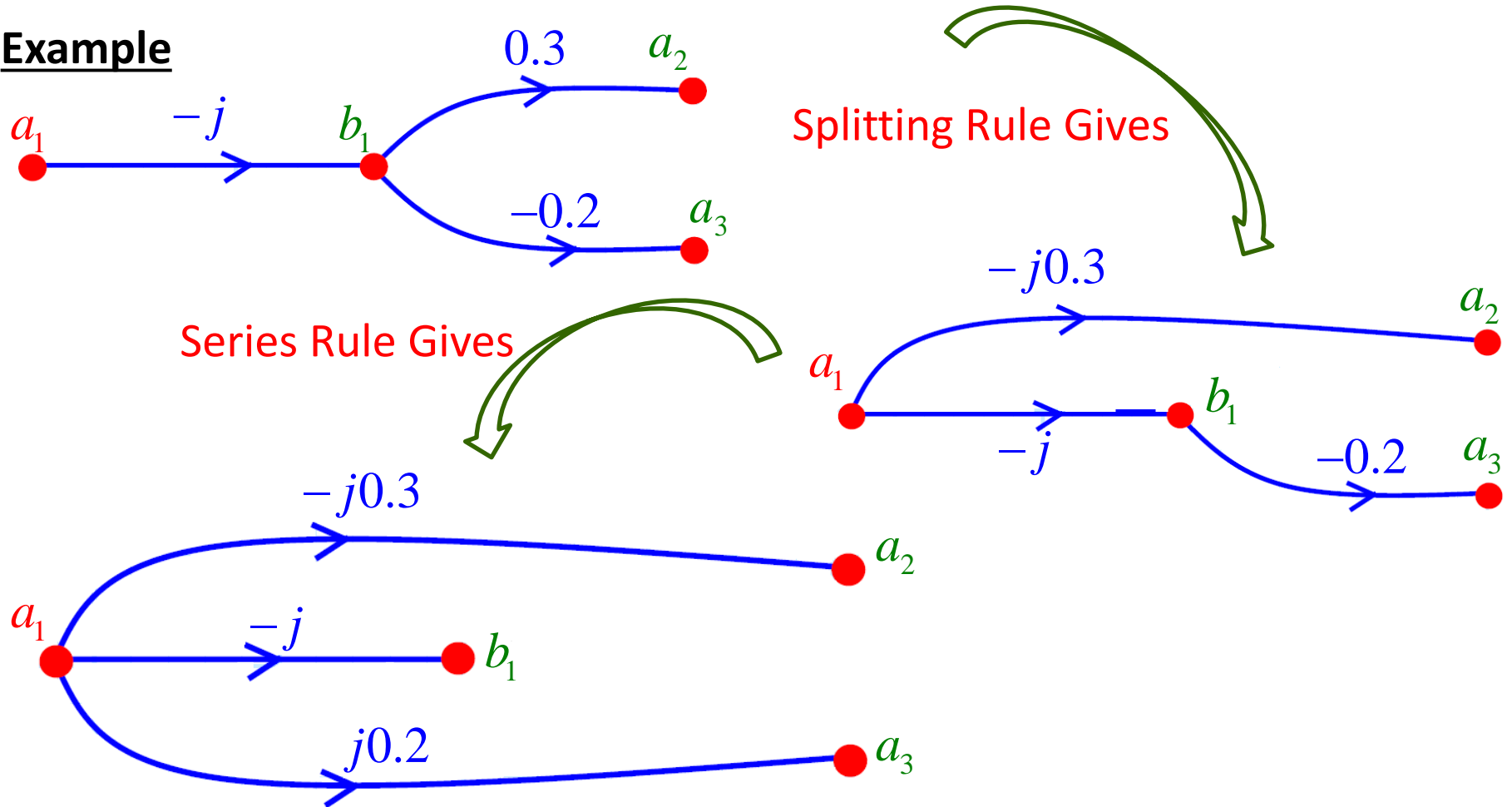


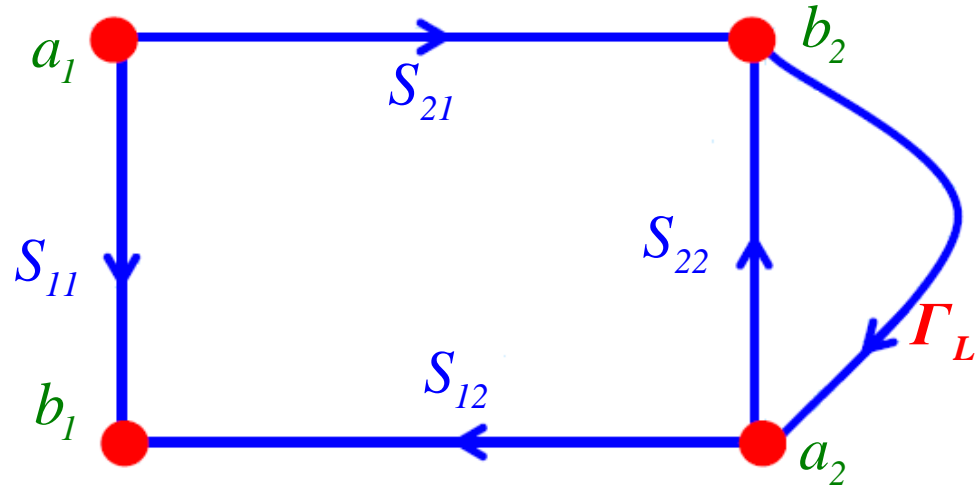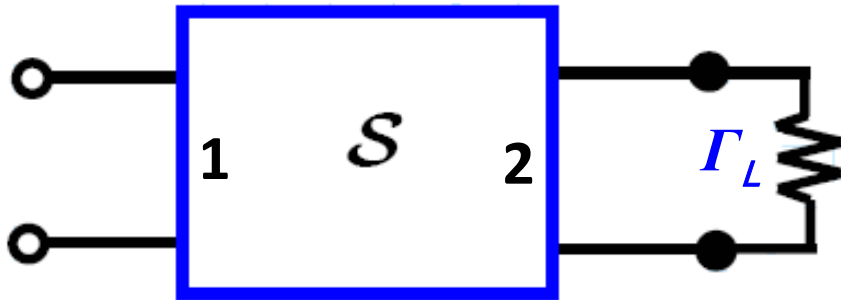
## Example-1

Consider the basic 2-port network, terminated with load  $\Gamma_L$ :



determine the value:  $\Gamma_1 = \frac{b_1}{a_1}$


### Solution:

- Isn't this simply  $S_{11}$  ?
- Only if  $\Gamma_L = 0$  (and in this situation it is not!)

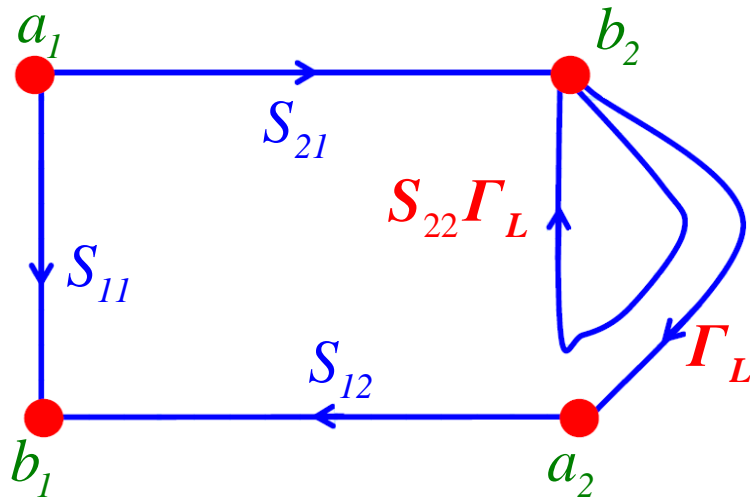
## Example-1 (contd.)

- let's decompose (simplify) the signal flow graph and find out!


**Step-1: splitting rule** on node  $a_2$



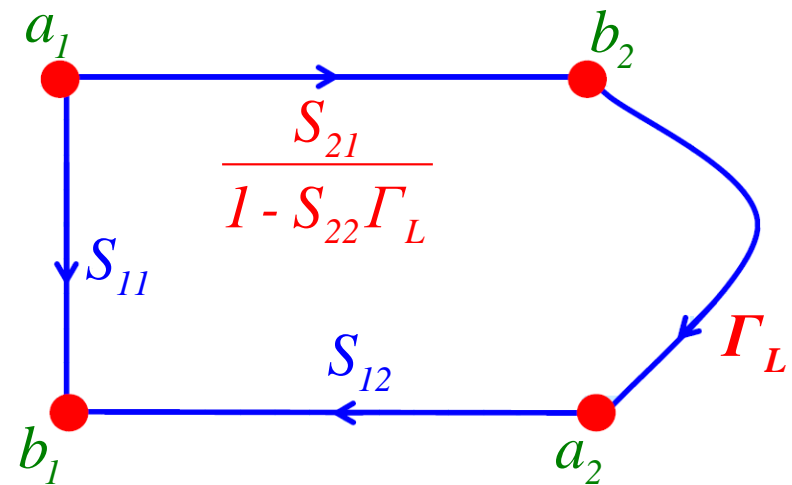
**Step-2: self-loop rule** on node  $b_2$



**Step-3: series rule** gives

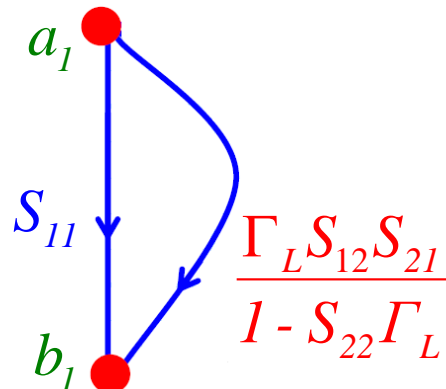


**Step-4: parallel rule** gives

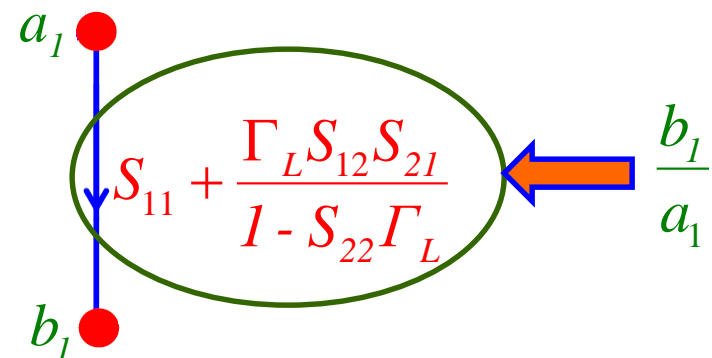
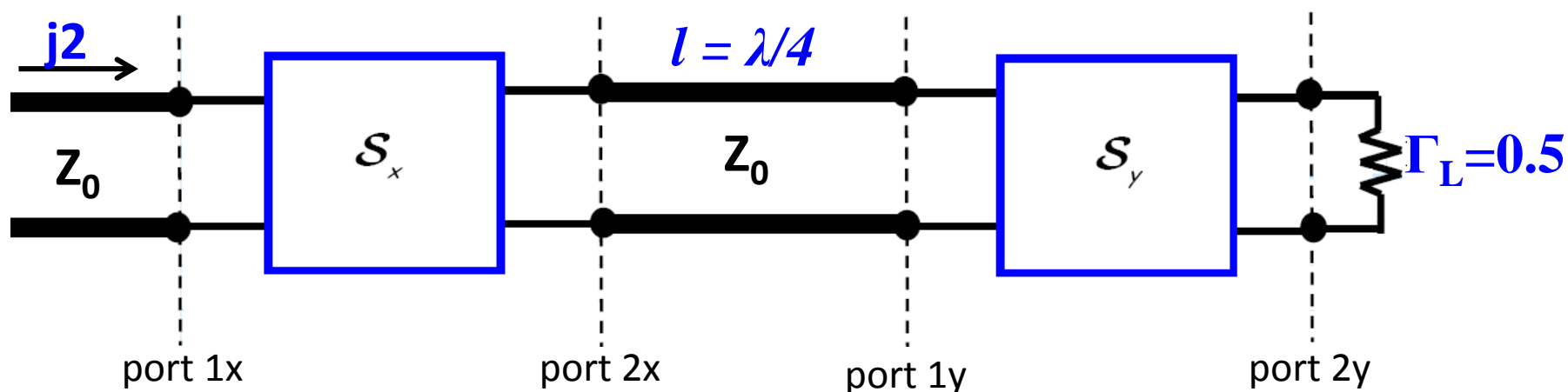
## Example – 2

Below is a **single-port** device (with **input** at port 1x) constructed with two two-port devices ( $S_x$  and  $S_y$ ), a quarter wavelength transmission line, and a load impedance.



### Given

$$Z_0 = 50\Omega$$


$$S_x = \begin{bmatrix} 0.35 & 0.5 \\ 0.5 & 0 \end{bmatrix}$$

$$S_y = \begin{bmatrix} 0 & 0.8 \\ 0.8 & 0.4 \end{bmatrix}$$

Draw the complete **signal flow graph** of this circuit, and then reduce the graph to determine: **a)** The total current through load  $\Gamma_L$ ; **b)** The power delivered to (i.e., absorbed by) port 1x.
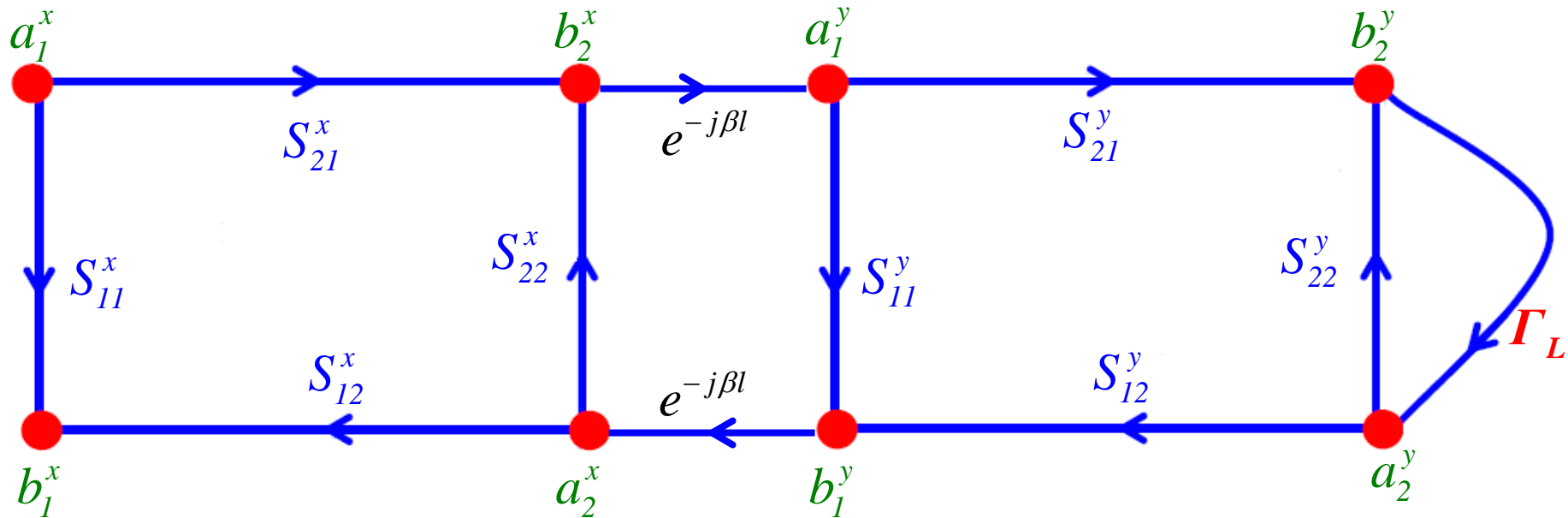
## Example – 2 (contd.)

The signal flow graph describing this network is:




We know that the value of the wave **incident** on port 1 of device  $S_x$  is:

$$a_1^x = \frac{V_{1x}^+(z_{1x} = z_{1xP})}{\sqrt{Z_0}} = \frac{j2}{\sqrt{50}} = \frac{j\sqrt{2}}{5}$$

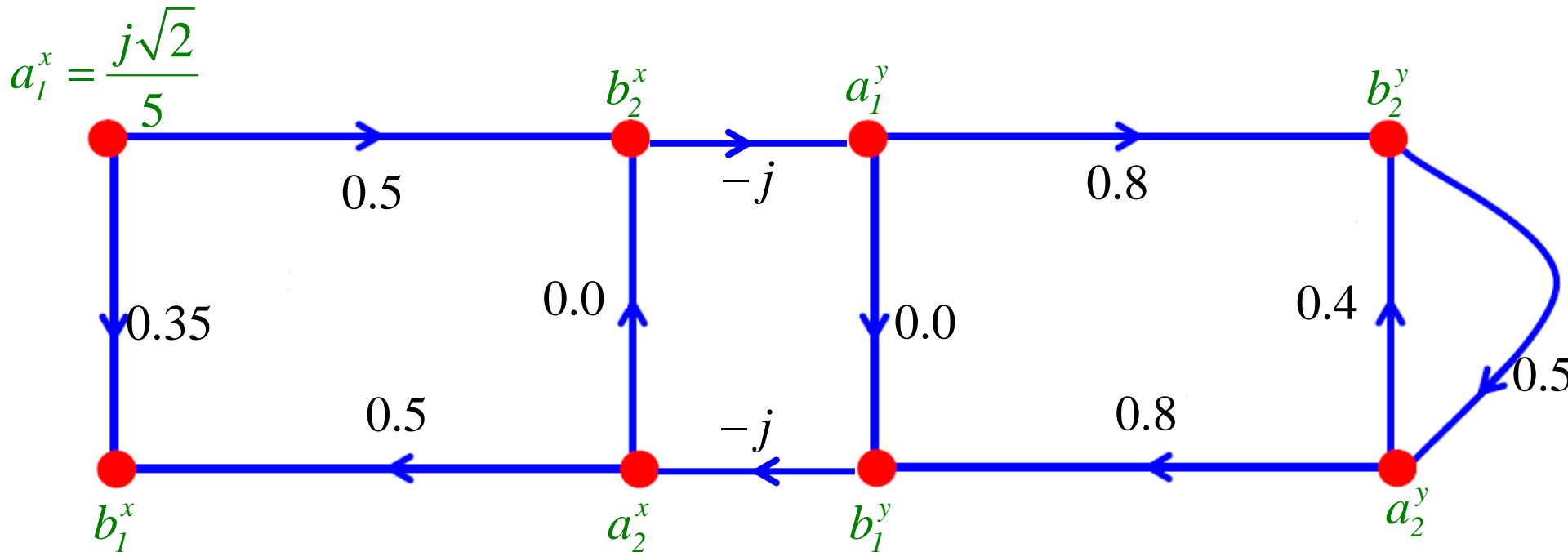
## Example – 2 (contd.)

Let us place the given numeric values of branches on this SFG:




## Example – 2 (contd.)

- Remove the zero valued branches:

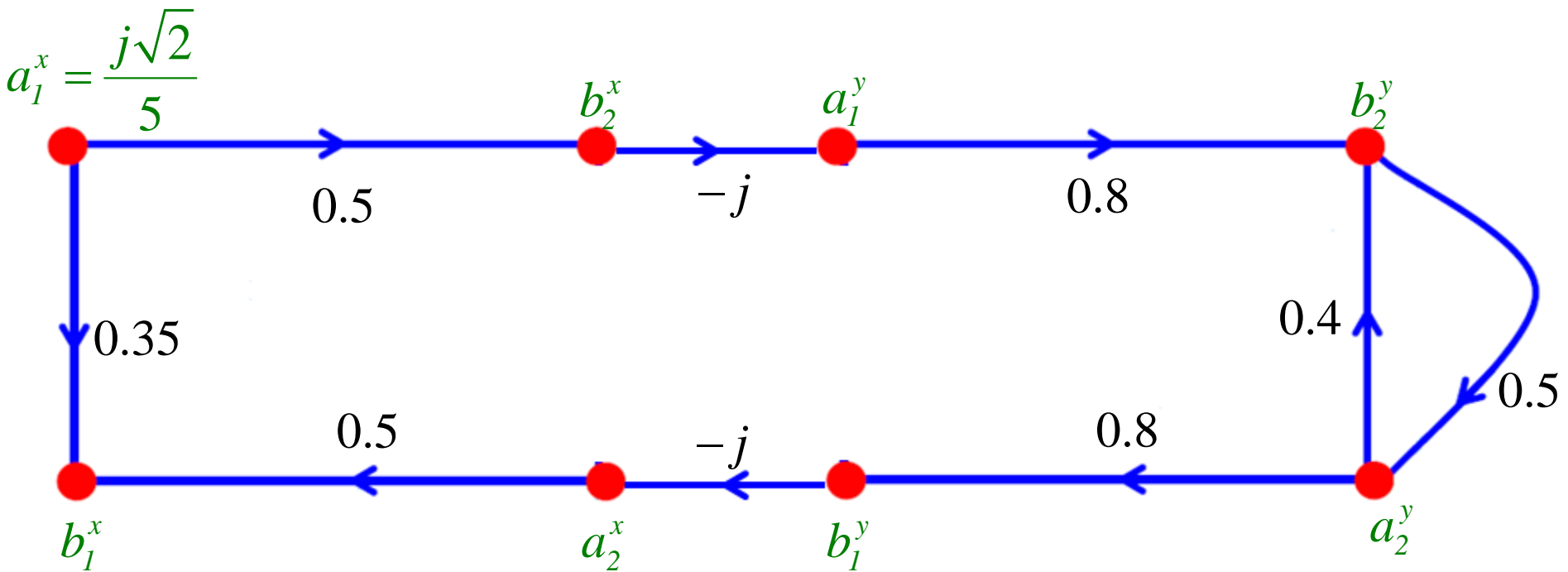

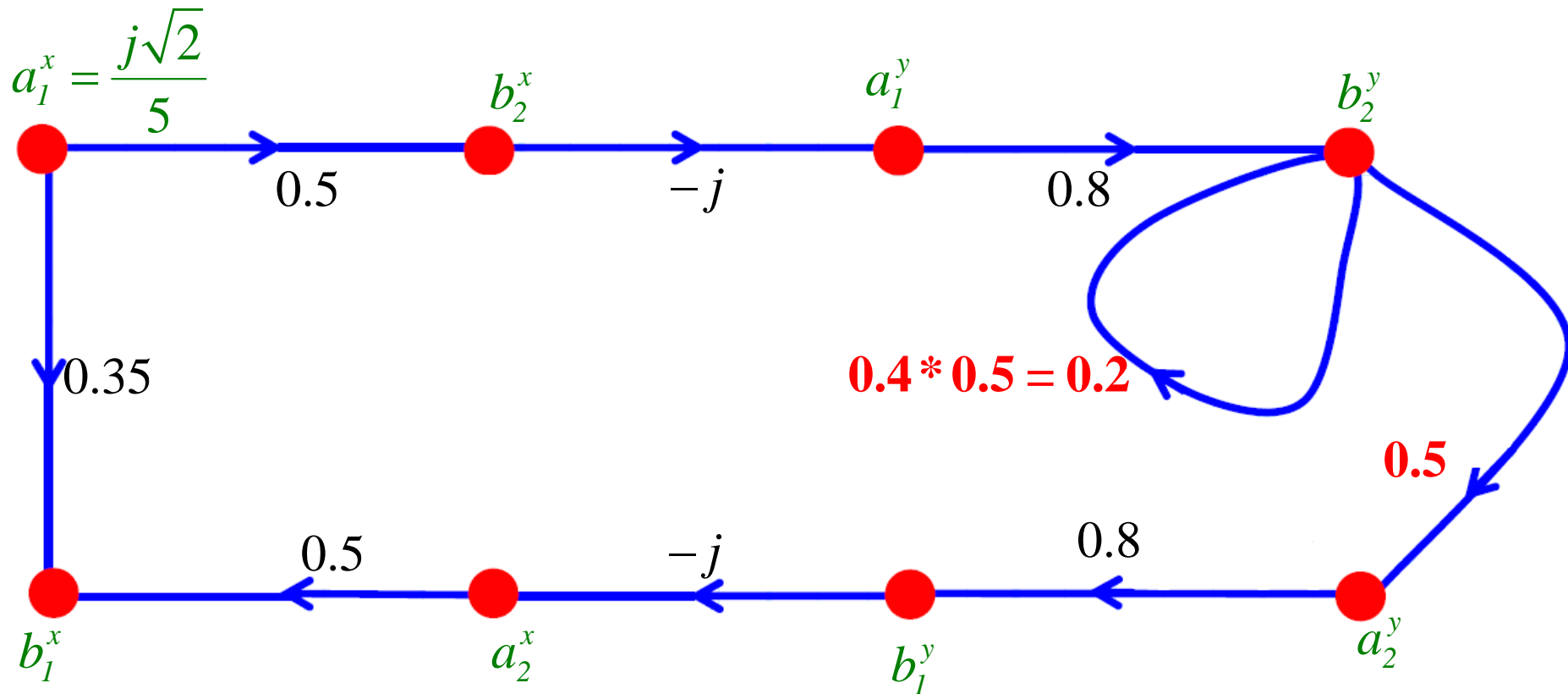
## Example – 2 (contd.)

Now apply “splitting” rule at node  $a_{2y}$


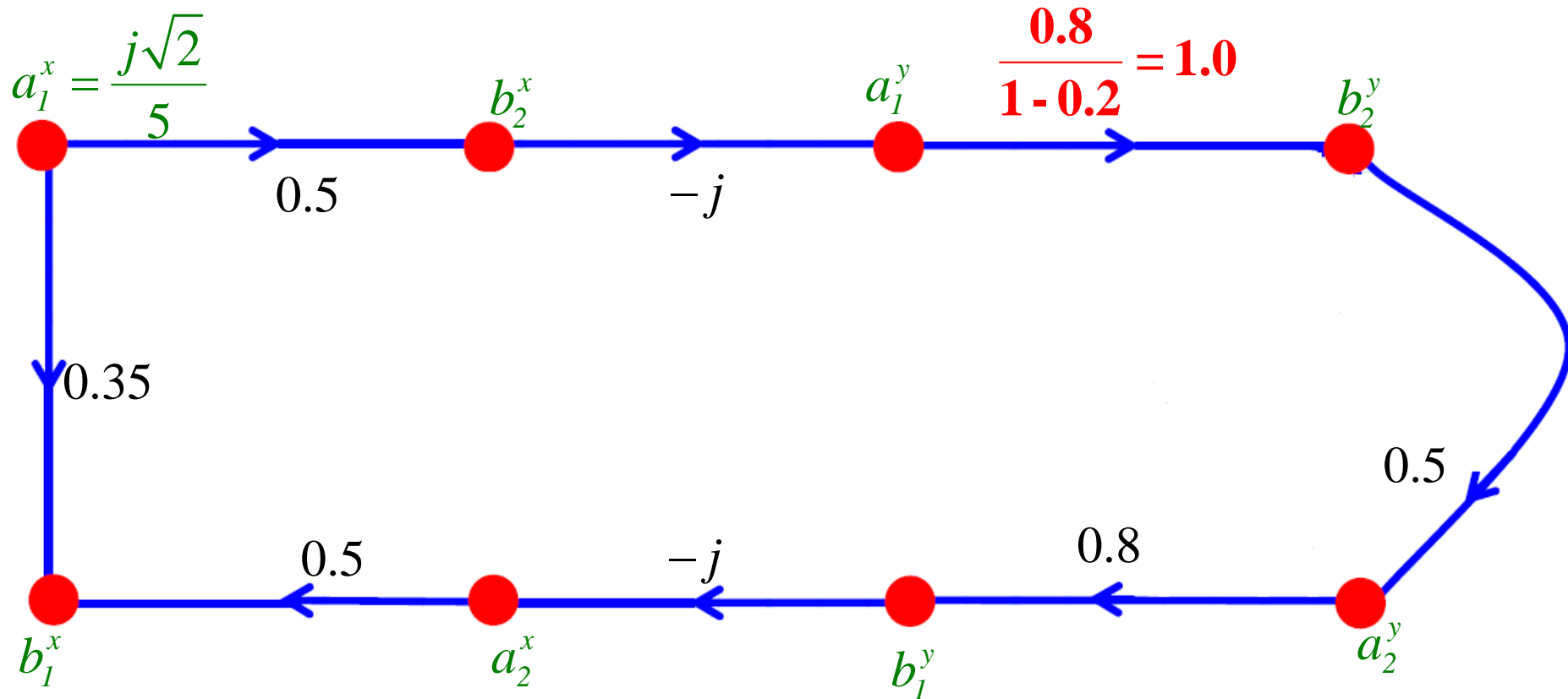
## Example – 2 (contd.)

Then apply “self-loop” rule at node  $b_{2y}$





## Example – 2 (contd.)

let's use this simplified signal flow graph to find the solutions to our questions!


a) The total current through load  $\Gamma_L$

$$I_L = -I(z_{2y} = z_{2yP}) = -\frac{V_{2y}^+(z_{2y} = z_{2yP}) - V_{2y}^-(z_{2y} = z_{2yP})}{Z_0}$$

$$\Rightarrow I_L = -\frac{a_{2y} - b_{2y}}{\sqrt{Z_0}} = \frac{b_{2y} - a_{2y}}{\sqrt{50}}$$

Thus, we need to determine the value of nodes  $a_{2y}$  and  $b_{2y}$

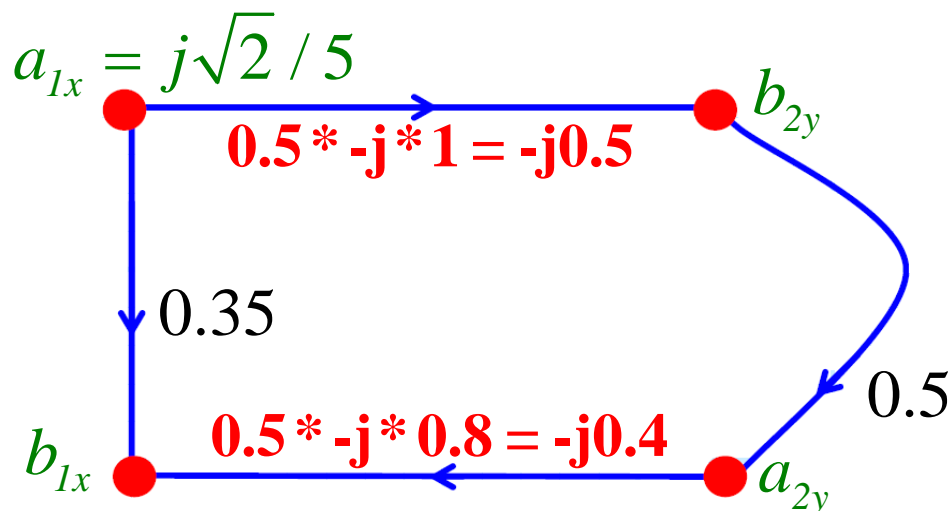• Using the “series” rule on the SFG gives



Therefore,

$$b_{2y} = -j0.5 * a_{1x} = -j0.5 * \frac{j\sqrt{2}}{5} = 0.1\sqrt{2}$$

$$a_{2y} = 0.5 * b_{2y} = 0.05\sqrt{2}$$

## Example – 2 (contd.)

Thus the total current through  $\Gamma_L$  is:

$$I_L = \frac{b_{2y} - a_{2y}}{\sqrt{50}} = \frac{(0.1 - 0.05)\sqrt{2}}{\sqrt{50}} = \frac{0.05}{5} = 10mA$$

**b)** The power delivered to (i.e., absorbed by) port 1x is:


$$P_{abs} = P^+ - P^- = \frac{|V_{1x}^+(z_{1x} = z_{1xP})|^2}{2Z_0} - \frac{|V_{1x}^-(z_{1x} = z_{1xP})|^2}{2Z_0}$$

$$\Rightarrow P_{abs} = \frac{|a_{1x}|^2 - |b_{1x}|^2}{2}$$

Requires knowledge of  
nodes  $a_{1x}$  and  $b_{1x}$

## Example – 2 (contd.)

We have:

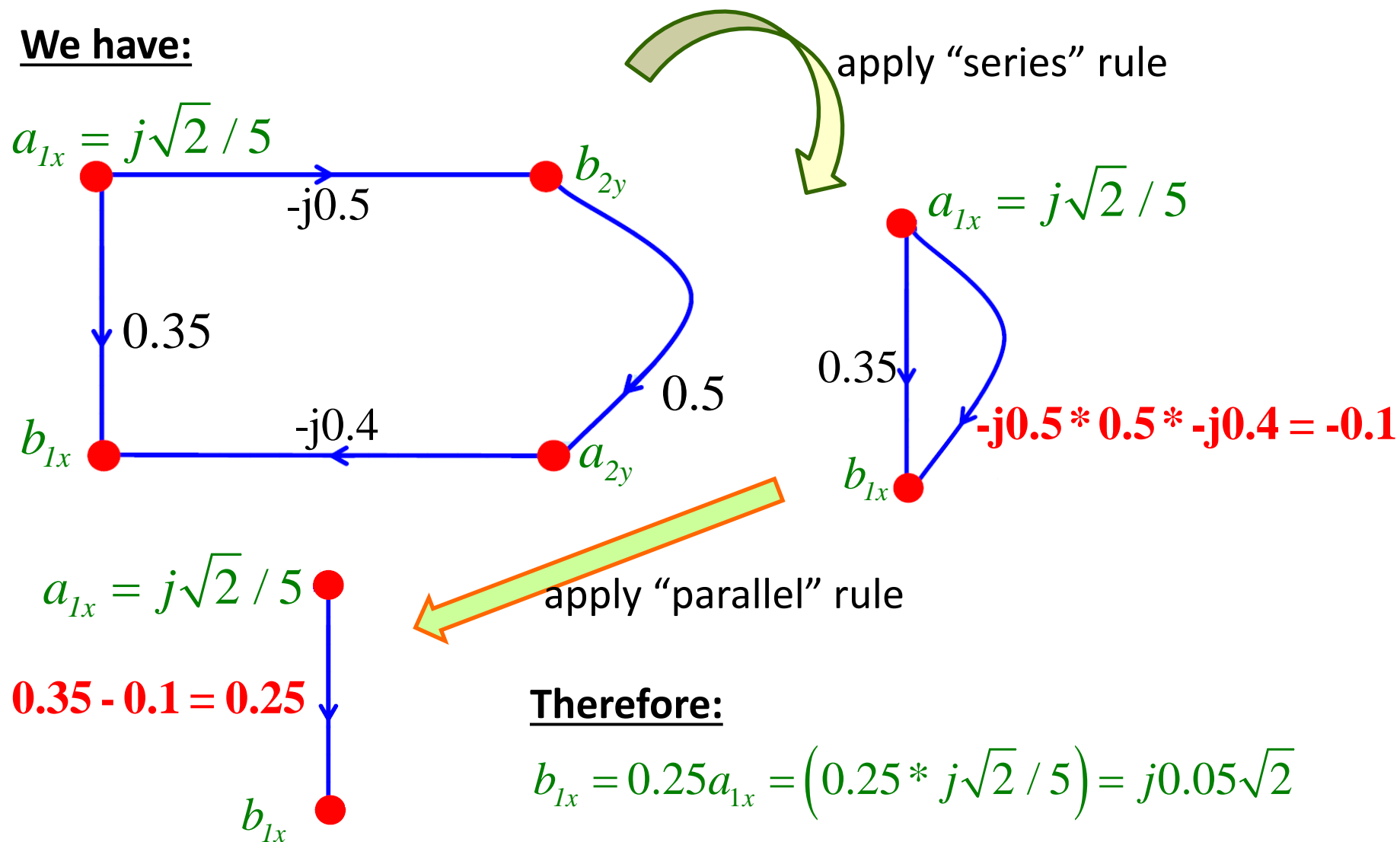

Therefore:

$$b_{1x} = 0.25a_{1x} = \left(0.25 * j\sqrt{2}/5\right) = j0.05\sqrt{2}$$

## Example – 2 (contd.)

Therefore, the power delivered to (i.e., absorbed by ) port 1x is:

$$\Rightarrow P_{abs} = \frac{|j\sqrt{2} / 5|^2 - |j0.05\sqrt{2}|^2}{2} = \frac{0.08 - 0.005}{2} = 37.5mW$$