

Lecture – 18

Date: 28.03.2016

- High Frequency Filter
- Filter Phase Function
- The Linear Phase Filter
- The Insertion Loss Method
- Filter Realization using Lumped Components



## **Filters**

- Microwave filter → A two-port microwave network that allows source power to be transferred to a load as an explicit <u>function of frequency</u>.
- RF/microwave **filter** is (typically) a passive, reciprocal, 2-port linear device.





# Filters (contd.)

- **Q:** What happens to the "missing" power  $P_{inc} P_{out}$ ?
- **A: Two** possibilities: the power is either **absorbed** ( $P_{abs}$ ) by the filter (converted to heat), or is **reflected** ( $P_r$ ) at the input port.
- Thus, by conservation of energy:
- Now ideally, a microwave filter is lossless, therefore P<sub>abs</sub> = 0 and:
- Alternatively we can write:

$$\frac{P_{inc}}{P_{inc}} = \frac{P_r + P_{out}}{P_{inc}}$$

power 
$$P_{inc} - P_{out}$$
?  
 $P_{inc}$   
 $P_r \leftarrow$   
 $P_{inc} = P_r + P_{abs} + P_{out}$   
 $P_{inc} = P_r + P_{out}$   
 $P_{inc} = P_r + P_{out}$   
 $I = \frac{P_r}{P_{inc}} + \frac{P_{out}}{P_{inc}}$   
 $I = \Gamma + T$ 

ECE321/521



# Filters (contd.)

In the last expression:

t  $T = \frac{P_{out}}{P_{inc}}$  Transmission Coefficient  $\Gamma \doteq \frac{P_r}{P_{inc}} = |S_{11}|^2$  Power Reflection Coefficient

Therefore, another way of saying a 2-port lossless device can be:



Now, here's the important part! → For a microwave filter, the coefficients
 Γ and T are functions of frequency! i.e.,:



The **behavior** of a microwave filter is described by these **functions**!

• We find that for most signal frequencies  $\omega_s$ , these functions will have a value equal to one of **two** different **approximate** values.



 $\Gamma(\omega = \omega_s) \approx 1$ 

### ECE321/521

# Filters (contd.)

• Either:

<u>or</u>

$$\Gamma(\omega = \omega_s) \approx 0$$
In this case, the signal frequency  $\omega_s$  is said to lie in the pass-band of the filter. Almost all of the incident signal power will pass through the filter.

In this case, the signal frequency  $\omega_s$  is said to lie in the stop-band of the filter. Almost all of the incident signal power will be reflected at the input—almost no power will appear at the filter output.

 $T(\omega = \omega_s) \approx 0$ 



ECE321/521

# Filters (contd.)

• Consider then these **four types** of functions of  $\Gamma(\omega)$  and  $T(\omega)$ :



This filter is a **low-pass** type, as it **"passes"** signals with frequencies **less** than  $\omega_c$ , while **"rejecting"** signals at frequencies **greater** than  $\omega_c$ .



A: Frequency  $\omega_c$  is a filter parameter known as the **cutoff frequency**; a value that **approximately** defines the frequency region where the filter pass-band **transitions** into the filter stop band.

 Accordingly, this frequency is defined as the frequency where the power transmission coefficient is equal to 1/2:

$$T\left(\omega=\omega_{c}\right)=0.5$$

 Note for a lossless filter, the cutoff frequency is likewise the value where the power reflection coefficient is 1/2:

$$\Gamma(\omega = \omega_c) = 0.5$$



ECE321/521



This filter is a **high-pass** type, as it **"passes"** signals with frequencies **greater** than  $\omega_c$ , while **"rejecting"** signals at frequencies **less** than  $\omega_c$ .



#### ECE321/521



- This filter is a **band-pass** type, as it **"passes"** signals within a frequency bandwidth  $\Delta \omega$ , while **"rejecting"** signals at all frequencies **outside this bandwidth**.
- In addition to filter bandwidth  $\Delta \omega$ , a fundamental parameter of bandpass filters is  $\omega_0$ , which defines the **center frequency** of the filter bandwidth.

#### ECE321/521



This filter is a band-stop type as it **"rejects"** signals within a frequency bandwidth Δω, while **"passing"** signals at all frequencies **outside this bandwidth.** 



#### **The Filter Phase Function**

• Recall that the power transmission coefficient  $T(\omega)$  can be determined from the scattering parameter  $S_{21}(\omega)$ :

$$T(\omega) = \left|S_{21}(\omega)\right|^2$$

**Q:** I see, we only care about the **magnitude** of complex function  $S_{21}(\omega)$  when using microwave filters !?

A: Hardly! Since  $S_{21}(\omega)$  is complex, it can be expressed in terms of its magnitude and **phase**:

$$S_{21}(\omega) = \operatorname{Re}\{S_{21}(\omega)\} + j\operatorname{Im}\{S_{21}(\omega)\}$$

<u>where</u> the phase is denoted as  $\angle S_{21}(\omega)$  :

$$\angle S_{21}(\omega) = \tan^{-1} \left[ \frac{\operatorname{Im} \{ S_{21}(\omega) \}}{\operatorname{Re} \{ S_{21}(\omega) \}} \right]$$

We therefore care **very** much about this phase function!



**Q:** Just what does this phase tell us?

A: It describes the relative phase **between** the wave incident on the input to the filter, and the wave exiting the output of the filter (given the output port is matched).

• In other words, if the **incident** wave is:

$$V_1^+(z_1) = V_{01}^+ e^{-j\beta z}$$

• Then the exiting (output) wave will be:

$$V_2^{-}(z_1) = V_{02}^{-} e^{+j\beta z_2}$$

$$S_{21}V_{01}^+e^{+j\beta z_2} = |S_{21}|V_{01}^+e^{+j(\beta z + \angle S_{21})}$$

We say that there has been a "**phase shift**" of  $\angle S_{21}(\omega)$  between the input and output waves.

Q: What causes this phase shift?

A: Propagation **delay.** It takes some non-zero amount of **time** for signal energy to propagate from the input of the filter to the output.

**Q**: Can we tell from  $\angle S_{21}(\omega)$  how **long** this delay is?

A: Yes!

#### The Filter Phase Function (contd.)

- To see how, consider an **example** two-port network (filter) with the impulse response:  $h(t) = \delta(t \tau)$
- We just identified that this device would merely delay an input signal (say by some amount *t*):

$$v_{out}(t) = \int_{-\infty}^{\infty} h(t-t')v_{in}(t')dt' = \int_{-\infty}^{\infty} \delta(t-t'-\tau)v_{in}(t')dt' = v_{in}(t-\tau)$$

$$v(t) = v_{in}(t)$$

$$v_{in}(t) = v_{in}(t-\tau)$$



 Now if we take the Fourier transform of this impulse response, then frequency response of this two-port network is:

The interesting result here is the **phase** ∠H(ω). The result means that a delay of **τ** seconds results in an output "phase shift" of –ω**τ** radians!

Note that although the **delay** of device is a **constant**  $\tau$ , the **phase shift** is a **function** of  $\omega \rightarrow$  in fact, it is directly proportional to frequency  $\omega$ .

- Note if the **input** signal for this device was of the form:  $v_{in}(t) = \cos \omega t$
- Then the output would be:

$$v_{out}(t) = \cos \omega (t - \tau)$$



Thus, we could **either** view the signal  $v_{in}(t) = \cos\omega t$  as being **delayed** by an amount  $\tau$  seconds, **or phase shifted** by an amount  $-\omega \tau$  radians.

**Q:** Then by **measuring** the output signal phase shift  $\angle H(\omega)$ , we could determine the delay  $\tau$  through the device with the equation:

$$\tau = -\frac{\angle H(\omega)}{\omega}$$

right?

A: Not exactly. The problem is that we cannot **unambiguously** determine the phase shift  $\angle H(\omega) = -\omega\tau$  by **looking** at the output signal!

• The reason is that  $\cos(\omega t + \angle H(\omega)) = \cos(\omega t + \angle H(\omega) + 2\pi) = \cos(\omega t + \angle H(\omega) - 4\pi)$ , etc. More specifically:

 $\cos(\omega t + \angle H(\omega)) = \cos(\omega t + \angle H(\omega) + n2\pi)$ 

where n is any integer — positive or negative. We can't tell which of these output signal we are looking at!



 Thus, any phase shift measurement has an inherent ambiguity. Typically, we interpret a phase measurement (in radians) such that:

 $-\pi < \angle H(\omega) \le \pi$  or  $0 \le \angle H(\omega) < 2\pi$ But almost certainly the actual value of  $\angle H(\omega) = -\omega\tau$  is nowhere near these interpretations!



#### The Filter Phase Function (contd.)



**Clearly using the equation:** 



would **not** get us the correct result in this case—after all, there will be **several** frequencies  $\omega$  with exactly the **same measured** phase  $\angle H(\omega)!$ 

**Q:** So determining the delay τ is **impossible**? **A:** NO! It is **entirely** possible—we simply must find the correct **method**.

Looking at the plot, this method should become **apparent**. Note that although the measured phase (blue curve) is definitely **not** equal to the phase function –ωτ (red curve), the **slope** of the two are **identical** at every point!

- **Q:** What good is knowing the **slope** of these functions?
- A: Just look! Recall that we can determine the slope by taking the first **derivative**:



The slope directly tells us the **propagation delay**!

Thus, we can determine the propagation delay of this device by:

 $\tau = -\frac{\partial \angle H(\omega)}{\partial \omega}$ 

where ∠H(ω) can be the **measured** phase. Of course, the method requires us to **measure** ∠H(ω) as a **function** of frequency (i.e., to make measurements at **many** signal frequencies).

**Q:** Now I see! If we wish to **determine** the propagation delay  $\tau$  through some **filter**, we simply need to take the derivative of  $\angle S_{21}(\omega)$  with respect to frequency. **Right**?

A: Well, sort of!

- Recall for the example case that h(t) = δ(t −τ) and ∠H(ω) = −ωτ, where τ is a constant. For a microwave filter, neither of these conditions are true.
- Specifically, the phase function  $\angle S_{21}(\omega)$  will typically be some arbitrary function of frequency ( $\angle S_{21}(\omega) \neq -\omega\tau$ ).

**Q:** How could this be true? I thought you said that phase shift was **due** to filter delay  $\tau$ !

A: Phase shift is due to device delay, it's just that the propagation delay of most devices (such as filters) is **not a constant**, but instead depends on the **frequency** of the signal propagating through it!

In other words, the propagation delay of a filter is typically some arbitrary **function** of frequency (i.e.,  $\tau(\omega)$ ). That's why the phase  $\angle S_{21}(\omega)$  is **likewise** an arbitrary function of frequency.



**Q:** Yikes! Is there **any** way to determine the relationship between these two arbitrary functions?

A: Yes there is! Just as before, the two can be related by:



This result τ(ω) is also known as **phase delay**, and is **very** important function to consider when designing/specifying/selecting a **microwave filter** 

**Q:** Why; what might happen if we don`t consider?

A: If you get a filter with wrong  $\tau(\omega)$ , your **output signal** could be **horribly distorted** – distorted by the evil effects of signal dispersion.



### **Filter Dispersion**

Any signal that carries significant **information** must have some nonzero **bandwidth**. In other words, the signal energy (as well as the information it carries) is **spread** across many frequencies.

If the different frequencies that comprise a signal propagate at different velocities through a microwave filter (i.e., each signal frequency has a different delay  $\tau$  ), the output signal will be **distorted**. We call this phenomenon signal **dispersion**.

**Q:** I see! The phase delay  $\tau(\omega)$  of a filter **must** be a constant with respect to frequency—otherwise signal dispersion (and thus signal distortion) will result. Right?

A: Not necessarily! Although a constant phase delay will **insure** that the output signal is not distorted, it is **not** strictly a requirement for that happy event to occur.

This is a **good** thing, for as we shall latter see, building a good filter with a constant phase delay is **very** difficult!



ECE321/521



ECE321/521

### Filter Dispersion (contd.)

Now, let's likewise For example, consider a modulated plot the **phase delay** function  $\tau(\omega)$  of signal with the following frequency some filter: spectrum, exhibiting a bandwidth of B<sub>c</sub> Hertz.  $|V(\omega)|^2$  $1/\tau(\omega)$  $|V(\omega)|^2$ In this case the filter phase delay is **nowhere** near a  $2\pi B$  $2\pi B$ constant with respect to frequency. ω ω  $\omega_{s}$  $\omega_{s}$ 

However, this fact alone does **not** necessarily mean that our signal would suffer from **dispersion** if it is passed through this filter. Indeed, the signal in this case **would** be distorted, but **only** because the phase delay  $\tau(\omega)$  changes significantly across the **bandwidth** B<sub>s</sub> of the signal.



## Filter Dispersion (contd.)

• Conversely, consider this **phase delay**:



As with the previous case, the phase delay of the filter is **not** a constant. Yet, if this signal were to pass through this filter, it would **not** be distorted!

The reason for this is that the phase delay across the **signal bandwidth** is approximately constant—each frequency component of the **signal** will be delayed by the **same** amount.



### Filter Dispersion (contd.)

• Compare this to the **previous** case, where the phase delay changes by a precipitous value  $\Delta \tau$  across signal bandwidth B<sub>s</sub>:



**Q**: So does  $\Delta \tau$  need to be **precisely** zero for no signal distortion to occur, or is there some **minimum** amount  $\Delta \tau$  that is acceptable?

A: Mathematically, we find that dispersion will be **insignificant** if:

$$\omega_s \Delta \tau \leq 1$$



# Filter Dispersion (contd.)

- A more specific (but **subjective**) "rule of thumb" is:
- Or, using  $\omega_s = 2\pi f_s$ :



$$\omega_s \Delta \tau \leq \frac{\pi}{5}$$

**Generally** speaking, we find for **wideband** filters—where filter bandwidth B is much greater than the signal bandwidth (i.e., B >>B<sub>s</sub>)—the above criteria is **easily** satisfied. In other words, signal dispersion is **not** typically a problem for wide band filters (e.g., pre-select filters).

This is **not** to say that τ(ω) is a constant for wide band filters. Instead, the phase delay can change **significantly** across the wide **filter** bandwidth.

# ECE321/521

# Filter Dispersion (contd.)

- What we typically find however, is that the function τ(ω) does not change very rapidly across the wide filter bandwidth. As a result, the phase delay will be approximately constant across the relatively narrow signal bandwidth Bs.
- Conversely, a **narrowband** filter where filter bandwidth B is approximately **equal** to the signal bandwidth (i.e.,  $B_s = B$ ) – can (if we are not careful!) exhibit a phase delay which changes **significantly** over **filter** bandwidth B. This means that the delay also changes significantly over the **signal** bandwidth  $B_s$ .



Thus, a **narrowband** filter (e.g., IF Filter) must exhibit a near constant phase delay  $\tau(\omega)$  in order to avoid distortion due to signal dispersion.



### The Linear Phase Filter

**Q:** So, narrowband filters should exhibit a **constant** phase delay  $\tau(\omega)$ . What should the phase function  $\angle S_{21}(\omega)$  be for this **dispersionless** case? **A:** We can express this problem mathematically as:

$$\tau(\omega) = \tau_c$$

where  $\tau_c$  is some **constant**.

• Recall that the definition of **phase delay** is:

$$\tau(\omega) = -\frac{\partial \angle S_{21}(\omega)}{\partial \omega}$$

Thus combining these two equations, we find ourselves with a differential equation:

$$-\frac{\partial \angle S_{21}(\omega)}{\partial \omega} = \tau_c$$

The **solution** to this differential equation provides us with the necessary phase function  $\angle S_{21}(\omega)$  for a **constant** phase delay  $\tau_c$ .

Fortunately, this differential equation can be **easily** solved!



The Linear Phase Filter (contd.)

The solution is:

 $\pi$ 

#### $\angle S_{21}(\omega) = -\omega \tau_c + \phi_c$ where $\phi_c$ is an arbitrary **constant**.

ECE321/521

• Plotting this phase function (with  $\phi_c = 0$ ):  $\bigwedge \angle H(\omega)$ 

As you rightly expected, this phase function is linear, such that it has constant slope  $(-\tau_c)$ 

Filters with such phase response are called linear phase filters, and have the desirable trait that cause no dispersion distortion.

# **The Insertion Loss Method**

- Recall that a **lossless** filter can be described in terms of either its power transmission coefficient  $T(\omega)$  or its power reflection coefficient  $\Gamma(\omega)$ , as the two values are completely **dependent**:
- Ideally, these functions would be quite simple:
- **1.**  $T(\omega) = 1$  and  $\Gamma(\omega) = 0$  for **all** frequencies within the **pass**band.
- **2.**  $T(\omega) = 0$  and  $T(\omega) = 1$  for **all** frequencies within the **stop**band.



- Add to this a **linear phase** response, and you have the **perfect** microwave filter!
- There's just one small problem with this **perfect** filter  $\rightarrow$  It's **impossible** to build!



# The Insertion Loss Method (contd.)

 Now, if we consider only possible (i.e., realizable) filters, we must limit ourselves to filter functions that can be expressed as finite polynomials of the form:

$$T(\omega) = \frac{a_{o} + a_{1}\omega + a_{2}\omega^{2} + \dots}{b_{o} + b_{1}\omega + b_{2}\omega^{2} + \dots + b_{N}\omega^{2N}}$$

The **order** N of the (denominator) polynomial is likewise the **order** of the filter.

 Instead of the power transmission coefficient, we often use an equivalent function (assuming lossless) called the **power loss ratio** P<sub>LR</sub>:

$$P_{LR} = \frac{P_1^+}{P_2^-} = \frac{1}{1 - \Gamma(\omega)}$$
Note,  $P_{LR} = \infty$  when  $\Gamma(\omega) = 1$ , and  
 $P_{LR} = 1$  when  $\Gamma(\omega) = 0$ .  
We likewise note that, for a lossless filter:  $P_{LR} = \frac{1}{T(\omega)}$   
Therefore  $P_{LR}(dB)$  is:  $P_{LR}(dB) = 10\log_{10} P_{LR} = -10\log_{10} T(\omega)$   
 $\rightarrow$  Insertion Loss



The power loss ratio in dB is simply the insertion loss of a lossless filter, and thus filter design using the power loss ratio is also called the Insertion Loss Method.

• We find that realizable filters will have a power loss ratio of the form:

 $P_{LR}(\omega) = 1 + \frac{M(\omega^2)}{N(\omega^2)}$  where  $M(\omega^2)$  and  $N(\omega^2)$  are polynomials with terms  $\omega^2, \omega^4, \omega^6$ , etc.

By specifying these polynomials, we specify the frequency behavior of a realizable filter. Our job is to first choose a desirable polynomial!

- There are many different types of polynomials that result in good filter responses, and each type has its own set of characteristics.
- The type of polynomial likewise describes the type of microwave filter.
   Let's consider three of the most popular types.



**1. Elliptical: These** filters have three primary characteristics:

a) They exhibit very steep "roll-off", meaning that the transition from pass-band to stop-band is very rapid.
b) They exhibit ripple in the pass-band, meaning that the value of T will vary slightly within the pass-band.

c) They exhibit ripple in the **stop**band, meaning that the value of **T** will vary slightly within the stopband.



We can make the roll-off **steeper** by accepting more **ripple**.

(J)

# The Insertion Loss Method (contd.)

**2. Chebychev: These** filters are also known as <u>equal-ripple</u> filters, and have two primary characteristics  ${}_{\Lambda}T(\omega)$ 

1

- a) Steep roll-off (but not as steep as Elliptical).
- b) Pass-band **ripple** (but not stop-band ripple).

We likewise find that the roll-off can be made steeper by **accepting** more ripple.

• The Chebychev **low-pass** filters have a power loss ratio equal to:



where *k* specifies the passband **ripple**,  $T_N(x)$  is a Chebychev polynomial of **order** N, and  $\omega_c$  is the low-pass **cutoff frequency**.



#### 3. Butterworth

Also known as **maximally flat** filters, they have two primary characteristics

- a) Gradual roll-off
- **b)** No ripple—not anywhere.



**Q:** So we always choose **elliptical** filters; since they have the steepest roll-off, they are **closest** to ideal—**right**?

A: Ooops! I forgot to talk about the **phase response**  $\angle S_{21}(\omega)$  of these filters. Let's examine  $\angle S_{21}(\omega)$  for each filter type **before** we pass judgment.

Butterworth ∠S <sub>21</sub> (ω)	$\rightarrow$	Close to linear phase
Chebyshev ∠S <sub>21</sub> (ω)	$\rightarrow$	Not very linear
Elliptical ∠S <sub>21</sub> (ω)	$\rightarrow$	A big non-linear mess!

• Thus, it is apparent that as the filter roll-off **improves**, the phase response gets **worse** (watch out for **dispersion!**).

→ There is **no** such thing as the "**best**" filter type!

Q: So, a filter with perfectly linear phase is impossible to construct?
A: No, it is possible to construct a filter with near perfect linear phase—but it will exhibit a horribly poor roll-off!



- Now, for any type of filter, we can improve roll-off (i.e., increase stop-band attenuation) by increasing the filter order N. However, be aware that increasing the filter order likewise has these deleterious effects:
  - 1. It makes **phase response**  $\angle S_{21}(\omega)$  worse (i.e., more nonlinear).
  - 2. It increases filter **cost**, **weight**, and **size**.
  - 3. It increases filter **insertion loss** (this is bad).
  - 4. It makes filter performance more **sensitive** to temperature, aging, etc.

From a **practical** viewpoint, the **order** of a filter should typically be kept to **N** < **10**.

- **Q:** So how do we take these polynomials and make real filters
- A: Similar to matching networks and couplers, we:
- 1. Form a general circuit structure with **several** degrees of design freedom.
- 2. Determine the **general form** of the power loss ratio for these circuits.
- 3. Use the degrees of design freedom to equate terms in the general form to the terms of the **desired** power loss ratio polynomial.

# Filter Realizations Using Lumped Elements

- Our **first** filter circuit will be "**realized**" with lumped elements.
- Lumped elements—we mean inductors L and capacitors C !
- Since each of these elements are (ideally) perfectly **reactive**, the resulting filter will be **lossless** (ideally).



#### ECE321/521

#### Filter Realizations Using Lumped Elements (contd.)

• Let us first consider two configurations of a ladder circuit:



Note that these two structures provide a **low-pass** filter response (evaluate the circuits at  $\omega = 0$  and  $\omega = \infty$ !).

Moreover, these structures have N different **reactive elements** (i.e., N degrees of design freedom) and thus can be used to realize an **N-order** power loss ratio.



#### ECE321/521

#### Filter Realizations Using Lumped Elements (contd.)

For example, consider the **Butterworth** power loss ratio function:

$$P_{LR}(\omega) = 1 + \left(\frac{\omega}{\omega_c}\right)^{2N}$$

Recall this is a low-pass function, as P<sub>LR</sub> = 1 at ω = 0, and P<sub>LR</sub> = ∞ at ω = ∞. Note also that at ω<sub>c</sub> = ω:

$$P_{LR}(\omega = \omega_c) = 1 + \left(\frac{\omega_c}{\omega_c}\right)^{2N} = 2$$
Thus
$$\Gamma(\omega = \omega_c) = T(\omega = \omega_c) = \frac{1}{2}$$

In other words,  $\omega_c$  defines the 3dB bandwidth of the low-pass filter.



#### Filter Realizations Using Lumped Elements (contd.)

• Likewise, we find that this Butterworth function is **maximally flat** at  $\omega = 0$ :

$$P_{LR}(\omega=0) = 1 + \left(\frac{0}{\omega_c}\right)^{2N} = 1 \qquad \text{and:} \quad \left(\frac{d^n P_{LR}(\omega)}{d\omega^n}\Big|_{\omega=0} = 0\right) \quad \text{For all } n$$

- Now, we can determine the function  $P_{LR}(\omega)$  for a lumped element ladder circuit of N elements using our knowledge of **complex circuit theory**.
- Then, we can equate the resulting polynomial to the maximally flat function above. In this manner, we can determine the appropriate values of all inductors L and capacitors C!
- Finding these L an C requires little bit of complex algebra.
- Pozar provides tables of complete Butterworth and Chebychev low-pass solutions.

#### Filter Realizations Using Lumped Elements (contd.)

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ , N = 1 to 10)

N	$g_1$	<i>g</i> <sub>2</sub>	83	<i>8</i> 4	85	<b>g</b> 6	<b>g</b> 7	<b>g</b> 8	<b>8</b> 9	$g_{10}$	$g_{11}$
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, Microwave Filters, Impedance-Matching Networks, and Coupling Structures, Artech House, Dedham, Mass., 1980, with permission.

#### Filter Realizations Using Lumped Elements (contd.)

TABLE 8.4 Element Values for Equal-Ripple Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ , N = 1 to 10, 0.5 dB and 3.0 dB ripple)

0.5 dB Ripple											
N	<i>g</i> 1	<i>g</i> 2	<b>g</b> 3	<i>g</i> 4	<i>8</i> 5	<b>g</b> 6	<b>g</b> 7	<i>g</i> 8	<i>8</i> 9	<b>g</b> 10	<b>g</b> 11
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
б	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841
	3.0 dB Ripple										
N	<i>g</i> 1	<i>g</i> 2	<b>g</b> 3	<i>g</i> 4	<i>g</i> 5	<b>g</b> 6	<b>g</b> 7	<i>g</i> 8	<b>g</b> 9	<b>g</b> 10	<b>g</b> 11
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
б	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	2 52 40	0 7760	4 6692	0 8118	4,7272	0.8118	4.6692	0.7760	3.5340	1.0000	
	5.5540	0.7700	1.0022	0.0110							
10	3.5340 3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095



#### ECE321/521

### **Insertion Loss Method**



Attenuation versus Normalized Frequency



#### Example – 1

A maximally flat low-pass filter is to be designed with a cut-off frequency of 8GHz and a minimum attenuation of 20dB at 11GHz. How many filter elements are required?

ECE321/521





#### Example – 2

Design a maximally flat low-pass filter with a cut-off frequency of 2GHz, impedance of  $50\Omega$  and at least 15dB insertion loss at 3GHz.

- First, find the required order of the maximally flat filter to satisfy the insertion loss specification at 3GHz.
- We have:

$$\frac{\frac{\omega}{2\pi}}{\omega_c/2\pi} - 1 = \frac{3}{2} - 1 = 0.5$$

- It is apparent that N =5 will be sufficient.
- From the table we get:  $g_1 = 0.618$ ,  $g_2 = 1.618$ ,  $g_3 = 2.000$ ,  $g_4 = 1.618$ ,  $g_5 = 0.618$ .

ECE321/521

 $C_n = g_n$ 

# Example – 2 (contd.)

- The Analysis of N-element filters give:
- The elements are therefore:

 $C_1 = 0.984 \, pF$   $L_2 = 6.438 nH$   $C_3 = 3.183 \, pF$   $L_4 = 6.438 nH$   $C_5 = 0.984 \, pF$ 

 $L_n = g_n \left( \frac{R_s}{\omega_c} \right)$ 



### Filter Realizations Using Lumped Elements (contd.)

**Q:** What?! What the heck do these values  $g_n$  mean? **A:** We can use the values  $g_n$  to find the values of inductors and capacitors required for a given **cutoff frequency**  $\omega_c$  and source resistance  $R_s$  ( $Z_0$ ).

 Specifically, we use the values of g<sub>n</sub> to find ladder circuit inductor and capacitor values as:

$$L_n = g_n \left(\frac{R_s}{\omega_c}\right)$$

$$C_n = g_n \left(\frac{1}{R_s \omega_c}\right)$$

where 
$$n = 1, 2, ..., N$$

- Likewise, the value g<sub>N+1</sub> describes the load impedance.
   Specifically, we find that if the last reactive element (i.e., g<sub>N</sub>) of the ladder circuit is a shunt capacitor, then:
- Whereas, if the last reactive element (i.e., g<sub>N</sub>) of the ladder circuit is a series inductor, then:



 $R_L = g_{N+1}R_s$ 

# Filter Realizations Using Lumped Elements (contd.)

Note, however, for the Butterworth solutions (in Table 8.3) we find that g<sub>N+1</sub>=1 always, and therefore:

 $R_L = R_s$  (Regardless of the last element)

- Moreover, we note (in Table 8.4) that this (i.e., g<sub>N+1</sub>=1) is likewise true for the Chebyshev solutions – provided that N is odd.
- Thus, we typically desire a filter where:

$$R_L = R_s = Z_0$$

We can use **any** order of **Butterworth** filter, or an **odd** order of **Chebyshev.** 

In other words, avoid even order Chebyshev filters!

Q: OK, so we now have the solutions for Chebychev and Butterworth **lowpass** filters. But what about high-pass, band-pass, or band-stop filters? A: Surprisingly, the low-pass filter solutions **likewise** provide us with the solutions for **any** and **all** high-pass, band-pass and band-stop filters! All we need to do is apply **filter transformations**.



#### **Filter Transformations**

We can use the concept of **filter transformations** to determine the **new** filter designs from a low-pass design. As a result, we can construct a 3rd-order Butterworth **high-pass** filter or a 5th-order Chebychev **bandpass** filter!

It will be apparent that the mathematics for each filter design will be very **similar**. For example, the difference between a low-pass and high-pass filter is essentially an **inverse**—the frequencies below  $\omega_c$  are mapped into frequencies above  $\omega_c$  —and vice versa.



ECE321/521

### Filter Transformations (contd.)

• However: 
$$T_{lp}(\omega = \omega_c) = T_{hp}(\omega = \omega_c) = 0.5$$

• Therefore, we can express:

$$T_{lp}(\omega = \alpha \omega_c) = T_{hp}(\omega = \frac{1}{\alpha} \omega_c)$$

where  $\alpha$  is some positive, real value (i.e.,  $0 \le \alpha < \infty$ ).

• For example, if  $\alpha = 0.5$ , then:

$$T_{lp}(\omega = 0.5\omega_c) = T_{hp}(\omega = 2\omega_c)$$

In other words, the transmission through a low-pass filter at one half the cut-off frequency will be equal to the transmission through a (mathematically similar) high-pass filter at twice the cut-off frequency.

# Filter Transformations (contd.)

 Now, recall the loss-ratio functions for Butterworth and Chebychev lowpass filters:



• Consider now this mapping:

$$\frac{\omega}{\omega_c} \Rightarrow -\frac{\omega_c}{\omega}$$

This mapping transforms the low-pass filter response into a corresponding high pass filter response! i.e.:

$$P_{LR}^{hp}(\omega) = 1 + \left(\frac{\omega_c}{\omega}\right)^{2N}$$

$$P_{LR}^{hp}(\omega) = 1 - k^2 T_N^2 \left(\frac{\omega_c}{\omega}\right)$$

# Filter Transformations (contd.)

**Q:** Yikes! Where did this mapping come from? Are sure this works?

Consider again the case where  $\omega = \alpha \omega_c$ ; the low pass responses are:

$$P_{LR}^{lp}(\omega) = 1 + (\alpha)^{2N} \qquad P_{LR}^{lp}(\omega) = 1 + k^2 T_N^2(\alpha)$$

Now consider the high-pass responses where  $\omega = -\omega_c/\alpha$ :

$$P_{LR}^{hp}(\omega) = 1 + (\alpha)^{2N}$$

$$P_{LR}^{hp}(\omega) = 1 - k^2 T_N^2(\alpha)$$

• Thus, we can conclude from this mapping that:

$$P_{LR}^{lp}(\omega = \alpha \omega_c) = P_{LR}^{hp}(\omega = -\omega_c / \alpha)$$

And since 
$$T = P_{LR}^{-1}$$
:  
 $T_{lp}(\omega = \alpha \omega_c) = T_{hp}(\omega = -\frac{1}{\alpha}\omega_c)$ 

Exactly the result that we expected! Our mapping provides a method for transforming a low-pass filter into a high-pass filter!

# Filter Transformations (contd.)

**Q:** OK Poindexter, you have succeeded in providing another one of your "fascinating" mathematical insights, but does this "mapping" provide anything useful for us engineers?

A: Absolutely! We can apply this mapping one component element (capacitor or inductor) at a time to our low-pass schematic design, and the result will be a direct transformation into a high-pass filter schematic.

Recall the reactance of an inductor element in a low-pass filter design is:

while that of a capacitor is: 
$$\int jX_n^{lp} = \frac{1}{i\omega C^{lp}} =$$

• Now apply the mapping:

$$jX_n^{lp} = j\omega L_n^{lp} = j\omega g_n \left(\frac{R_s}{\omega_c}\right) = jg_n R_s \left(\frac{\omega}{\omega_c}\right)$$

$$jX_n^{lp} = \frac{1}{j\omega C_n^{lp}} = -j\frac{R_s}{g_n}\left(\frac{\omega_c}{\omega}\right)$$

$$\frac{\omega}{\omega_c} \Rightarrow -\frac{\omega_c}{\omega}$$

#### ECE321/521

# Filter Transformations (contd.)

 The inductor becomes:

$$jX_n^{hp} = jg_n R_s \left(-\frac{\omega_c}{\omega}\right) = -j\frac{g_n R_s \omega_c}{\omega} = \frac{1}{j\left(g_n R_s \omega_c\right)^{-1} \omega}$$

• and the capacitor:

$$jX_n^{hp} = -j\frac{R_s}{g_n}\left(-\frac{\omega_c}{\omega}\right) = j\omega\left(\frac{R_s}{g_n\omega_c}\right)$$

It is clear (do you see why?) that the transformation has converted a positive (i.e., inductive) reactance into a negative (i.e., capacitive) reactance—and vice versa.

- As a result, to transform a low-pass filter schematic into a high-pass filter schematic, we:
  - 1. Replace each inductor with a capacitor of value:

$$C_n^{hp} = \frac{1}{g_n R_s \omega_c} = \frac{1}{\omega_c^2 L_n^{lp}}$$

2. Replace each capacitor with an inductor of value:

$$L_n^{hp} = \frac{R_s}{g_n \omega_c} = \frac{1}{\omega_c^2 C_n^{lp}}$$

### ECE321/521

#### Filter Transformations (contd.)

 Thus, a high-pass ladder circuit consists of series capacitors and shunt inductors (compare this to the low-pass) ladder circuit!).



 $\mathcal{O}_{c}$ 

Q: What about band-pass filters? A: The difference between a low-pass and band-pass filter is simply a **shift** in

the "center" frequency of the filter, where the center frequency of a low-pass filter is essentially  $\omega = 0$ .

• For this case, we find the **mapping**:

transforms a low-pass function into a **band-pass** function, where  $\Delta$  is the **normalized bandwidth**:

 $\omega_1$  and  $\omega_2$  define the two **3dB frequencies** of the bandpass filter.

Ŵ

## Filter Transformations (contd.)

 For example, the Butterworth low-pass function:

$$P_{LR}^{lp}(\omega) = 1 + \left(\frac{\omega}{\omega_c}\right)^{2N}$$

$$P_{LR}^{bp}(\omega) = 1 + \frac{1}{\Delta^{2N}} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^{2N}$$

• Applying this transform to the reactance of a low-pass inductive element:

$$jX_{n}^{bp} = jg_{n}R_{s}\frac{1}{\Delta}\left(\frac{\omega}{\omega_{0}} - \frac{\omega_{0}}{\omega}\right) = j\omega\left(\frac{g_{n}R_{s}}{\omega_{0}\Delta}\right) + \frac{1}{j\omega\left(\frac{\Delta}{g_{n}\omega_{0}R_{s}}\right)}$$

- Look what happened! The transformation turned the inductive reactance into an inductive reactance in series with a capacitive reactance.
- A similar analysis of the transformation of the low-pass capacitive reactance shows that it is transformed into an inductive reactance in parallel with an capacitive reactance.



### Filter Transformations (contd.)

- As a result, to transform a low-pass filter schematic into a band-pass filter schematic, we:
- Replace each series inductor with a capacitor and inductor in series, with values:
- 2. Replace each shunt capacitor with an inductor and capacitor in parallel, with values:
- Thus, the ladder circuit for band-pass circuit is simply a ladder network of LC resonators, both series and parallel:

$$L_{n}^{bp} = g_{n} \frac{R_{s}}{\omega_{0}\Delta}$$

$$C_{n}^{bp} = \frac{1}{g_{n}} \frac{\Delta}{\omega_{0}R_{s}}$$

$$L_{n}^{bp} = \frac{1}{g_{n}} \frac{\Delta R_{s}}{\omega_{0}}$$

$$C_{n}^{bp} = g_{n} \frac{1}{\omega_{0}\Delta R_{s}}$$





#### **Filter Implementations**

**Q:** So, we now know how to make any and all filters with **lumped** elements but this is a **RF/microwave** engineering course!

You said that lumped elements where difficult to make and implement at high frequencies. You said that distributed elements were used to make microwave components. So how do we make a filter with distributed elements!?!

A: There are many ways to make RF/microwave filters with distributed elements. Perhaps the most straightforward is to "realize" each individual lumped element with transmission line sections, and then insert these approximations in our lumped element solutions.

The **first** of these realizations is: Richard's Transformations

To easily **implement** Richard's Transforms in a microstrip or stripline circuit, we must apply one of **Kuroda's Identities**.