

ECE321/521

# <u>Lecture – 3</u>

# Date: 11.01.2016

- Transmission Lines (TL) Introduction
- TL Equivalent Circuit Representation
- Definition of Some TL Parameters
- Examples of Transmission Lines

Indraprastha Institute of Information Technology Delhi

### Line Impedance (Z) – contd.

It appears to me that Z<sub>0</sub> is a transmission line parameter, depending only on the transmission line values R, L, C and G.

Whereas, Z(z) depends on the magnitude and the phase of the two propagating waves  $V^+(z)$  and  $V^-(z) \rightarrow$ values that depend not only on the transmission line, but also on the two things attached to either end of the transmission line.



Exactly!!!

Right?

Indraprastha Institute of Information Technology Delhi



## **Example of Transmission Lines**

Two common examples:

coaxial cable



A transmission line is normally used in the balanced mode, meaning equal and opposite currents (and charges) on the two conductors.





Indraprastha Institute of Information Technology Delhi

## **Example of Transmission Lines (contd.)**

#### **Coaxial Cable**



$$C = \frac{2\pi\varepsilon_{0}\varepsilon_{r}}{\ln\left(\frac{b}{a}\right)} \quad [F/m] \qquad G = \frac{2\pi\sigma_{d}}{\ln\left(\frac{b}{a}\right)} \quad [S/m]$$
$$L = \frac{\mu_{0}}{2\pi}\ln\left(\frac{b}{a}\right) \quad [H/m] \qquad R = \frac{1}{\sigma_{m}\delta}\left(\frac{1}{2\pi a} + \frac{1}{2\pi b}\right) \quad [\Omega/m]$$
$$\delta = \sqrt{\frac{2}{\omega\mu\sigma_{m}}} \quad (skin \ depth \ of \ metal)}$$



## **Example of Transmission Lines (contd.)**

Another common example (for printed circuit boards):





## **Microstrip Line (contd.)**

• The severity of field leakage also depends on the relative dielectric constants ( $\varepsilon_r$ ).



Indraprastha Institute of Information Technology Delhi

# **Microstrip Line (contd.) microstrip** line **USB Hub Ports** Neo1973 **Debug Port** JTAG (Non-Neo1973) ÚART (Non-Neo1973)

Indraprastha Institute of Information Technology Delhi

## **Microstrip Transmission Lines Design**



- Simple parallel plate model can not accurately define this structure.
- Because, if the substrate thickness increases or the conductor width decreases then fringing field become more prominent (and therefore need to be incorporated in the model).

#### **<u>Case-I</u>:** thickness (t) of the line is negligible

For narrow microstrips  $\binom{w}{h} \leq 1$ : 2

$$Z_0 = \frac{Z_f}{2\pi\sqrt{\varepsilon_{eff}}} \ln\left(8\frac{h}{w} + \frac{w}{4h}\right)$$

Where, 
$$Z_f = \sqrt{\mu_0 / \varepsilon_0} = 377 \Omega$$
 wave impedance in free space

$$\varepsilon_{eff} = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \left[ \left( 1 + 12\frac{h}{w} \right)^{-1/2} + 0.004 \left( 1 - \frac{w}{h} \right)^2 \right] \xleftarrow{\text{Effective Dielectric}}_{\text{Constant}}$$



## **Microstrip Transmission Lines Design (contd.)**

• For wide microstrips  $({}^w/_h \ge 1)$ :

$$Z_0 = \frac{Z_f}{\sqrt{\varepsilon_{eff}} \left( 1.393 + \frac{w}{h} + \frac{2}{3} \ln\left(\frac{w}{h} + 1.444\right) \right)}$$

• Where the effective dielectric constant is expressed as:

$$\varepsilon_{eff} = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \left(1 + 12\frac{h}{w}\right)^{-1/2}$$

• The two distinct expressions give approximate values of characteristic impedance and effective dielectric constant for narrow and wide strip microstrip lines  $\rightarrow$  these can be used to plot  $Z_0$  and  $\varepsilon_{eff}$  as a function of  ${}^w/_h$ .



### **Microstrip Transmission Lines Design (contd.)**



Indraprastha Institute of Information Technology Delhi

## **Microstrip Transmission Lines Design (contd.)**



Indraprastha Institute of Information Technology Delhi

**Free Space** 

Wavelength

#### **Microstrip Transmission Lines Design (contd.)**

- The effective dielectric constant (*eff*) is viewed as the dielectric constant of a  $\lambda = \frac{v_p}{f} = \frac{c}{f \sqrt{\varepsilon_{eff}}}$ The effective dielectric constant ( $\varepsilon_{eff}$ ) is space around the line. Therefore:
- The wavelength in the microstrip line for  $W/_h \ge 0.6$  is:
- The wavelength in the microstrip line for  $W/_h \leq 0.6$  is:

$$\lambda = \frac{\lambda_0}{\sqrt{\varepsilon_r}} \left[ \frac{\varepsilon_r}{1 + 0.63(\varepsilon_r - 1)(W/h)^{0.1255}} \right]^{1/2}$$
$$\lambda = \frac{\lambda_0}{\sqrt{\varepsilon_r}} \left[ \frac{\varepsilon_r}{1 + 0.6(\varepsilon_r - 1)(W/h)^{0.0297}} \right]^{1/2}$$

Speed of Light



## **Microstrip Transmission Lines Design (contd.)**

 In some specifications, wavelength is known. In that case following curve can be used to identify the w/h ratio.



Indraprastha Institute of Information Technology Delhi

## **Microstrip Transmission Lines Design (contd.)**

• If  $Z_0$  and  $\varepsilon_r$  is specified or known, following expression can be used to determine w/h:

For w/h≤2: 
$$\frac{w}{h} = \frac{8e^{A}}{e^{2A} - 2}$$
 Where:  $A = 2\pi \frac{Z_0}{Z_f} \sqrt{\frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{\varepsilon_r + 1}} \left( 0.23 + \frac{0.11}{\varepsilon_r} \right)$   
For w/h≥2:  $\frac{w}{h} = \frac{2}{\pi} \left( B - 1 - \ln(2B - 1) + \frac{\varepsilon_r - 1}{2\varepsilon_r} \left[ \ln(B - 1) + 0.39 - \frac{0.61}{\varepsilon_r} \right] \right)$  Where:  $B = \frac{Z_f \pi}{2Z_0 \sqrt{\varepsilon_r}}$ 

<u>Case-II</u>: thickness (t) of the line is not negligible  $\rightarrow$  in this scenario all the formulas are valid with the assumption that the effective width of the line increases as:

$$w_{eff} = w + \frac{t}{\pi} \left( 1 + \ln \frac{2x}{t} \right)$$
  
Where  $x = h$  if  $w > \frac{h}{2\pi}$  or  $x = 2\pi w$  if  $\frac{h}{2\pi} > w > 2t$ 



# Example – 1

A microstrip material with  $\varepsilon_r = 10$  and h = 1.016 mm is used to build a narrow transmission line. Determine the width for the microstrip transmission line to have a characteristic impedance of 50 $\Omega$ . Also determine the wavelength and the effective relative dielectric constant of the microstrip line.

#### **Using the Formulas:**

Let us consider the first formula:  

$$\frac{w}{h} = \frac{8e^{A}}{e^{2A} - 2}$$

$$A = 2\pi \frac{Z_{0}}{Z_{f}} \sqrt{\frac{\varepsilon_{r} + 1}{2}} + \frac{\varepsilon_{r} - 1}{\varepsilon_{r} + 1} \left( 0.23 + \frac{0.11}{\varepsilon_{r}} \right) = 2\pi \frac{50}{377} \sqrt{\frac{10 + 1}{2}} + \frac{10 - 1}{10 + 1} \left( 0.23 + \frac{0.11}{10} \right)$$

$$\Rightarrow A = 2.1515$$
Therefore:  $\frac{w}{h} = \frac{8e^{2.1515}}{e^{2(2.1515)} - 2} = 0.9563$ 

Now: h = 1.016 mm = 0.1016 cm = 0.1016(1000/2.54) mils = 40 mils

$$\therefore w = 0.9563 * 40 mils = 38.2 mils$$

Indraprastha Institute of Information Technology Delhi

## Example – 1 (contd.)

ШГ

$$\lambda = \frac{\lambda_0}{\sqrt{\varepsilon_r}} \left[ \frac{\varepsilon_r}{1 + 0.63(\varepsilon_r - 1)(w/h)^{0.1255}} \right]^{1/2}$$

$$\therefore \lambda = \frac{\lambda_0}{\sqrt{10}} \left[ \frac{10}{1 + 0.63(10 - 1)(0.9563)^{0.1255}} \right]^{1/2} = 0.387 \lambda_0$$

$$\lambda = \frac{v_p}{f} = \frac{c}{f\sqrt{\varepsilon_{eff}}} = \frac{\lambda_0}{\sqrt{\varepsilon_{eff}}} \implies \varepsilon_{eff} = \left(\frac{\lambda_0}{\lambda}\right)^2$$

$$\therefore \varepsilon_{eff} = \left(\frac{1}{0.387}\right)^2 = 6.68$$



# Example – 1 (contd.)

#### **Using the Design Curves**



Indraprastha Institute of Information Technology Delhi

# Example – 1 (contd.)

#### **Using the Design Curves**





## Example – 2

- a. Using the design curves, calculate W,  $\lambda$ , and  $\varepsilon_{eff}$  for a characteristic impedance of 50 $\Omega$  using RT/Duroid with  $\varepsilon_r = 2.23$  and h = 0.7874 mm.
- b. Use design equations to show that for RT/Duroid with  $\varepsilon_r = 2.23$  and h = 0.7874 mm, a 50 $\Omega$ -characteristic impedance is obtained with  $W/_h = 3.073$ . Also show,  $\varepsilon_{eff} = 1.91$  and  $\lambda = 0.7236\lambda_0$ .





# Example – 2 (contd.)



For 
$$\frac{W}{h} \approx 3.1$$
 and  $\varepsilon_r = 2.23$   
 $\frac{\lambda}{\lambda_{TEM}} = 1.08 \longrightarrow \lambda = 1.08\lambda_{TEM}$   
We know:  $\lambda_{TEM} = \frac{\lambda_0}{\sqrt{\varepsilon_r}}$   
 $\therefore \lambda = 0.723\lambda_0$ 

Also: 
$$\lambda = \frac{\lambda_0}{\sqrt{\varepsilon_{eff}}} \qquad \Longrightarrow \varepsilon_{eff} = 1.91$$



## Example – 2 (contd.)

For w/h≥2: 
$$\frac{w}{h} = \frac{2}{\pi} \left( B - 1 - \ln(2B - 1) + \frac{\varepsilon_r - 1}{2\varepsilon_r} \left[ \ln(B - 1) + 0.39 - \frac{0.61}{\varepsilon_r} \right] \right)$$
 Where:  
 $B = \frac{Z_f \pi}{2Z_0 \sqrt{\varepsilon_r}}$ 

Therefore: 
$$\frac{w}{h} = \frac{2}{\pi} \left( B - 1 - \ln(2B - 1) + \frac{2.23 - 1}{2 \times 2.23} \left[ \ln(B - 1) + 0.39 - \frac{0.61}{2.23} \right] \right)$$

Where: 
$$B = \frac{377\pi}{2 \times 50 \times \sqrt{2.23}} = 7.931$$
  $\therefore \frac{w}{h} = 3.073$ 

• For 
$${}^{W}/_{h} \ge 0.6$$
:  $\lambda = \frac{\lambda_{0}}{\sqrt{\varepsilon_{r}}} \left[ \frac{\varepsilon_{r}}{1 + 0.63(\varepsilon_{r} - 1)(W/h)^{0.1255}} \right]^{1/2}$   
 $\therefore \lambda = \frac{\lambda_{0}}{\sqrt{2.23}} \left[ \frac{2.23}{1 + 0.63(2.23 - 1)(3.073)^{0.1255}} \right]^{1/2} = 0.724\lambda_{0}$ 



## **Lossless Transmission Line**

• For a lossless transmission line:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$
$$\beta = \omega \sqrt{LC}$$

• Similarly the current phasor for a lossless line can be described:

**Q**:  $Z_0$  and  $\beta$  are determined from L, C, and  $\omega$ . How do we find  $V_0^+$  and  $V_0^-$ ? **A**: Apply **Boundary Conditions**!

Every transmission line has **2** "boundaries":

- 1) At one end of the transmission line.
- 2) At the other end of the trans line!

Typically, there is a **source** at one end of the line, and a **load** at the other.



#### **Terminated Lossless Transmission Line**

 Now let's attach something to our transmission line. Consider a lossless line, length l, terminated with a load Z<sub>l</sub>.



**Q:** What is the **current** and **voltage** at each and **every** point on the transmission line (i.e., what is I(z) and V(z) for **all** points z where  $z_l - l < z < z_l$ .

A: To find out, we must apply **boundary conditions**!

Indraprastha Institute of ECE321/521 Information Technology Delhi **Terminated Lossless Transmission Line (contd.)**  $l(z) \longrightarrow$ The load is assumed at  $z = z_1$ The voltage wave couples + + $I_L$ into the line at  $z = z_l - l$ V(z) $Z_L$ *>∑*.  $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$  $z = z_l - l$  $z = z_1$ Incident Wave **Reflected Wave** At the load:  $V(z = z_1) = V^+(z = z_1) + V^-(z = z_1) = V_0^+ e^{-j\beta z_1} + V_0^- e^{j\beta z_1}$  $I(z=z_l) = \frac{V^+(z=z_l)}{Z_0} - \frac{V^-(z=z_l)}{Z_0} = \frac{V_0^+}{Z_0}e^{-j\beta z_l} - \frac{V_0^-}{Z_0}e^{j\beta z_l}$ 



So now we have the **boundary conditions** for **this** particular problem.



**Careful**! Different transmission line problems lead to **different** boundary conditions—**you** must assess each problem **individually** and **independently**!



## **Terminated Lossless Transmission Line (contd.)**

• **Combining** these equations and boundary conditions, we find that:

$$V(z=z_l) = V_L = Z_L I_L = Z_L I(z=z_l)$$

$$V^{+}(z=z_{l})+V^{-}(z=z_{l})=\frac{Z_{L}}{Z_{0}}\left(V^{+}(z=z_{l})-V^{-}(z=z_{l})\right)$$

• Rearranging, we can conclude:

$$\frac{V^{-}(z=z_{l})}{V^{+}(z=z_{l})} = \frac{Z_{L} - Z_{0}}{Z_{L} + Z_{0}}$$

Voltage Reflection Coefficient  $\Gamma(z = z_l)$ 

also holds true for current wave but with opposite sign

This value is of **fundamental** importance for the terminated transmission line problem, so we provide it with its **own** special symbol ( $\Gamma_0$ )!



• We can express the reflected voltage wave as:



#### **Terminated Lossless Transmission Line (contd.)**

• Therefore:

$$V^{-}(z) = \left(\Gamma_{0}V_{0}^{+}e^{-j2\beta z_{l}}\right)e^{+j\beta z}$$

$$V(z) = V^{+}(z) + V^{-}(z) = V_{0}^{+}\left[e^{-j\beta z} + \left(\Gamma_{0}e^{-j2\beta z_{l}}\right)e^{+j\beta z}\right]$$

$$I(z) = \frac{V^{+}(z) - V^{-}(z)}{Z_{0}} = \frac{V_{0}^{+}}{Z_{0}}\left[e^{-j\beta z} - \left(\Gamma_{0}e^{-j2\beta z_{l}}\right)e^{+j\beta z}\right]$$

• Simplify by arbitrarily assigning the end point a zero value (i.e.,  $z_l = 0$ )

$$V(z=0) = V^{+}(z=0) + V^{-}(z=0) = V_{0}^{+}e^{-j\beta(0)} + V_{0}^{-}e^{+j\beta(0)} = V_{0}^{+} + V_{0}^{-}$$
$$I(z=0) = \frac{V_{0}^{+} - V_{0}^{-}}{Z} \qquad Z(z=0) = \frac{V(z=0)}{Z} = Z_{0} \left[\frac{V_{0}^{+} + V_{0}^{-}}{Z}\right] = Z$$

$$D) = \frac{V_0 - V_0}{Z_0} \qquad Z(z=0) = \frac{V(z=0)}{I(z=0)} = Z_0 \left[ \frac{V_0 + V_0}{V_0^+ - V_0^-} \right] = Z_L$$

• The current and voltage along the line in this case are:

$$V(z) = V_0^+ \left[ e^{-j\beta z} + \Gamma_0 e^{+j\beta z} \right]$$

$$I(z) = \frac{V_0^+}{Z_0} \left[ e^{-j\beta z} - \Gamma_0 e^{+j\beta z} \right]$$
Q: But, how do we determine  $V_0^+$ ?

Indraprastha Institute of Information Technology Delhi

## ECE321/521

 $Z(z) = \frac{V(z)}{I(z)}$ 

## **Special Termination Conditions**

 Let us once again consider a generic TL terminated in arbitrary impedance Z<sub>L</sub>



It's interesting to note that Z<sub>L</sub> enforces a boundary condition that explicitly determines neither V(z) nor I(z)—but completely specifies line impedance Z(z)!





## **Special Termination Conditions (contd.)**

$$Z(z) = Z_0 \frac{e^{-j\beta z} + \Gamma_0 e^{+j\beta z}}{e^{-j\beta z} - \Gamma_0 e^{+j\beta z}} = Z_0 \frac{Z_L \cos(\beta z) - jZ_0 \sin(\beta z)}{Z_0 \cos(\beta z) - jZ_L \sin(\beta z)}$$

• Likewise, the load boundary condition leaves  $V^+(z)$  and  $V^-(z)$  undetermined, but completely determines reflection coefficient function  $\Gamma(z)$ !

$$\Gamma(z) = \frac{V^{-}(z)}{V^{+}(z)} = \Gamma_0 e^{+j2\beta z} = \frac{Z_L - Z_0}{Z_L - Z_0} e^{+j2\beta z}$$

Let's look at some **specific** values of load impedance  $Z_L = R_L + jX_L$ and see what functions Z(z) and  $\Gamma(z)$  result!



Indraprastha Institute of ECE321/521 Information Technology Delhi Special Termination Conditions (contd.) A device with no load is **Short-Circuited Line** •  $Z_L = 0$ called short circuit  $R_{I} = 0 \quad X_{I} = 0$  $\mathbf{I}_{0}$ Short-circuit entails setting this impedance to zero  $Z_L = 0$  $Z_0$  $\Gamma_0 = \frac{0 - Z_0}{0 + Z} =$  $z \equiv 0$ Alternatively  $Z(z) = -jZ_0 \tan(\beta z)$  $Z(z) = -jZ_0 \tan \left|$ 

Note that this impedance is **purely reactive**. This means that the current and voltage on the transmission line will be everywhere 90° **out of phase**.



# **Special Termination Conditions (contd.)**

- <u>Short-Circuited Line</u>
- The current and voltage along the TL is:

$$V(z) = V_0^+ \left[ e^{-j\beta z} - e^{+j\beta z} \right] = -j2V_0^+ \sin(\beta z)$$

$$I(z) = \frac{2V_0^+}{Z_0} \cos(\beta z)$$

• Finally, the reflection coefficient **function** is:

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

Short-Circuited Line:

$$Z(-l) = jZ_0 \tan(\beta l)$$

Indraprastha Institute of Information Technology Delhi

# **Special Termination Conditions (contd.)**

**Short-Circuited Line**  $Z_{in}$ inductive ßl  $\pi/2$  $3\pi/2$  $5\pi/2$ capacitive  $\frac{3\lambda}{4}$  $\frac{\lambda}{4} = \frac{\lambda}{2}$  $\frac{5\lambda}{4}$ d λ 0

$$Z(-l) = jZ_0 \tan(\beta l)$$

#### It can be observed:

- At -*l*=0, the impedance is zero (short-circuit condition)
- Increase in -l leads to inductive behavior
- At  $-l=\lambda/4$ , the impedance equals infinity (open-circuit condition)
- Further increase in -l leads to capacitive behavior
- At  $-l=\lambda/2$ , the impedance becomes zero (short-circuit condition)
- The entire periodic sequence repeats for  $-l > \lambda/2$  and so on...



## Example – 3

For a short-circuited TL of l = 10 cm, compute the magnitude of the input impedance when the frequency is swept from f = 1 GHz to 4 GHz. Assume the line parameters L = 209.4 nH/m and C = 119.5 pF/m.

#### Solution:

$$Z_{0} = \sqrt{L/C} = \sqrt{(209.4 * 0.1) / (119.5 * 0.5)} = 41.86\Omega$$

$$v_{p} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(209.4 * 0.1) * (119.5 * 0.5)}} = 41.86\Omega} = 1.99 * 10^{8} m / s$$

$$Z(z = -l) = jZ_{0} \tan(\beta l) = jZ_{0} \tan\left(\frac{2\pi f}{v_{p}}l\right)$$
Set  $l = 10$  cm and then write a MATLAB program to obtain the Z<sub>in</sub> curve

Compare the MATLAB results to that obtained from ADS simulation





Again note that this impedance is **purely reactive**. current and voltage on the transmission line are  $90^{\circ}$  **out of phase**.



# **Special Termination Conditions (contd.)**

- Open-Circuited Line
- The current and voltage along the TL is:

$$V(z) = V_0^+ \left[ e^{-j\beta z} + e^{+j\beta z} \right] = 2V_0^+ \cos(\beta z)$$

• At the load, 
$$z = 0$$
, therefore:  $V(0) = 2V_0^+$ 

$$I(z) = -j\frac{2V_0^+}{Z_0}\sin(\beta z)$$

$$I(0) = 0$$

As expected, the current is zero at the end of the transmission line (i.e. the current through the open). Likewise, the voltage at the end of the line (i.e., the voltage across the open) is at a maximum!

• Finally, the reflection coefficient **function** is:

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave! Indraprastha Institute of Information Technology Delhi

# **Special Termination Conditions (contd.)**

Open-Circuited Line



$$Z(-l) = -jZ_0 \cot(\beta l)$$

#### It can be observed:

- At -*l*=0, the impedance is infinite (open-circuit condition)
- Increase in -l leads to capacitive behavior
- At  $-l = \lambda/4$ , the impedance equals zero (short-circuit condition)
- Further increase in -*l* leads to inductive behavior
- At  $-l=\lambda/2$ , the impedance becomes infinite (open-circuit condition)
- The entire periodic sequence repeats for  $-l > \lambda/2$  and so on...



Indraprastha Institute of Information Technology Delhi

ECE321/521

#### **Transmission Line Input Impedance – Special Cases**

1. length of the line is  $l = m(\lambda/2)$ 

$$Z_{in} = Z(z = \lambda/2) = Z_0 \frac{Z_L + jZ_0 \tan\left(\frac{2\pi}{\lambda}, \frac{\lambda}{2}\right)}{Z_0 + jZ_L \tan\left(\frac{2\pi}{\lambda}, \frac{\lambda}{2}\right)} = Z_L$$

- For a transmission line of half wavelength long the input impedance equals the load impedance irrespective of the characteristic impedance of the line
- It means it is possible to design a circuit segment where the transmission line's characteristic impedance plays no role (obviously the length of line segment has to equal half wavelength at the operating frequency)





#### **Transmission Line Input Impedance – Special Cases (contd.)**

2. length of the line is  $l = \lambda/4$  or  $\lambda/4 + m(\lambda/2)$ 

$$Z_{in} = Z(l = \lambda / 4) = Z_0 \frac{Z_L + jZ_0 \tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}\right)}{Z_0 + jZ_L \tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}\right)} = \frac{Z_0^2}{Z_L}$$

 This result implies that a transmission line segment can be used to synthesize matching of any desired real input impedance (Z<sub>in</sub>) to the specified real load impedance (Z<sub>L</sub>)





#### Transmission Line Input Impedance – Special Cases (contd.)

2. length of the line is  $l = \lambda/4$  or  $\lambda/4 + m(\lambda/2)$ 



input impedance of a quarter-wave line is inversely proportional to the load impedance

→ Think about what this means! Say the load impedance is a short circuit then:

$$Z_{in} = \frac{Z_0^2}{Z_L} = \frac{Z_0^2}{0} = \infty$$

Z<sub>in</sub> = ∞ ! This is an open circuit ! The quarter wave TL transforms a short-circuit into open-circuit and vice-versa





## Example – 4

- Consider a load resistance  $R_L = 100\Omega$  to be matched to a 50 $\Omega$  line with a quarter-wave transformer. Find the characteristic impedance of the matching section and plot the magnitude of the reflection coefficient versus normalized frequency,  $f/f_0$ , where  $f_0$  is the frequency at which the line is  $\lambda/4$  long.
  - the necessary characteristic impedance is:

$$Z_0 = \sqrt{Z_L Z_{in}}$$
  $(\therefore Z_0 = \sqrt{Z_L Z_{in}} = \sqrt{50 \times 100} = 70.71\Omega)$ 

• The reflection coefficient magnitude is given as



Indraprastha Institute of Information Technology Delhi

ECE321/521

## Example – 4 (contd.)

