

Lecture – 7

Date: 25.01.2016

- Smith Chart – Examples
- Admittance Transformation

Example-1


Given:

$$\Gamma_0 = 0.5 \angle 45^\circ$$

$$Z_0 = 50\Omega$$

What is load
impedance, Z_L ?

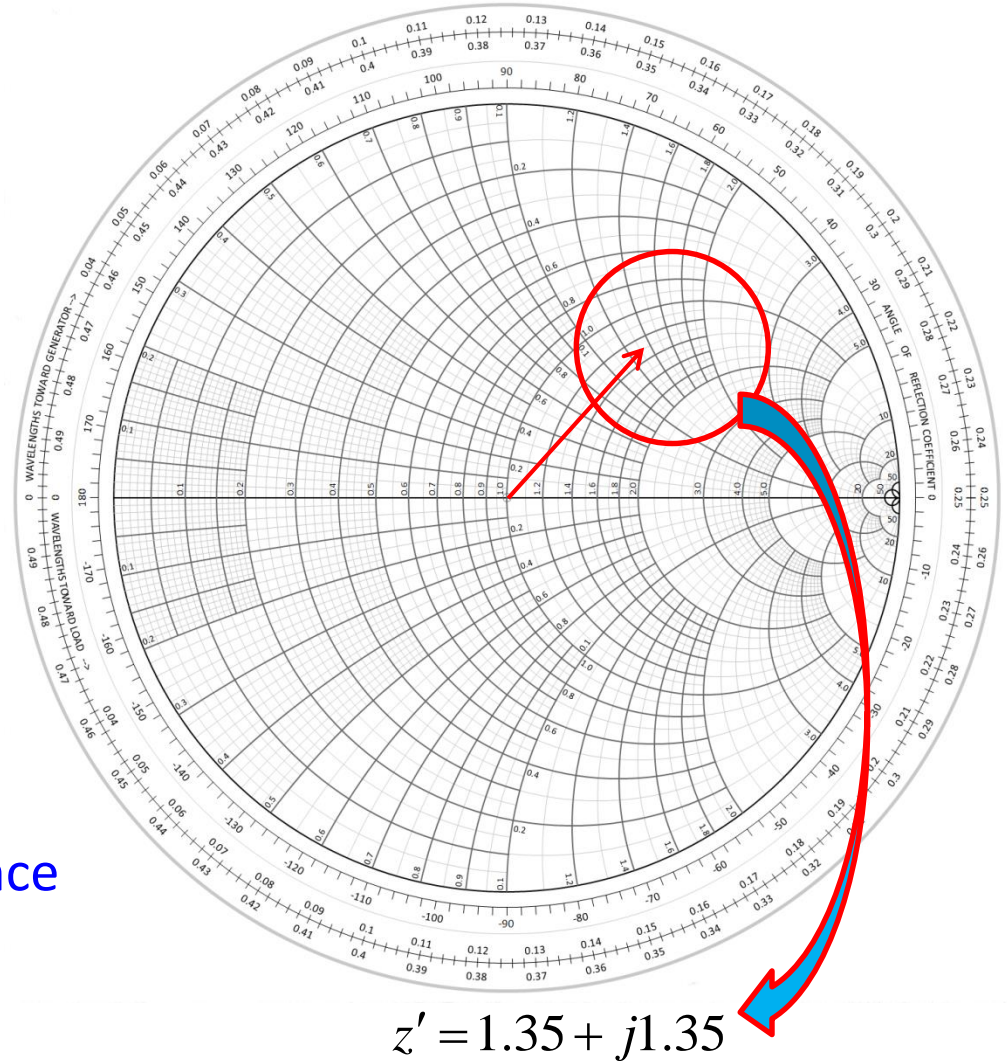- Locate Γ_0 on the smith chart
- Read the normalized impedance
- Then multiply the identified normalized impedance by Z_0



$$\therefore Z_L = 50\Omega * (1.35 + j1.35) = 67.5\Omega + j67.5\Omega$$

Example-2


Given:

$$Z_L = (15 - j25)\Omega$$

$$Z_0 = 50\Omega$$


What is load
impedance, Γ_0 ?

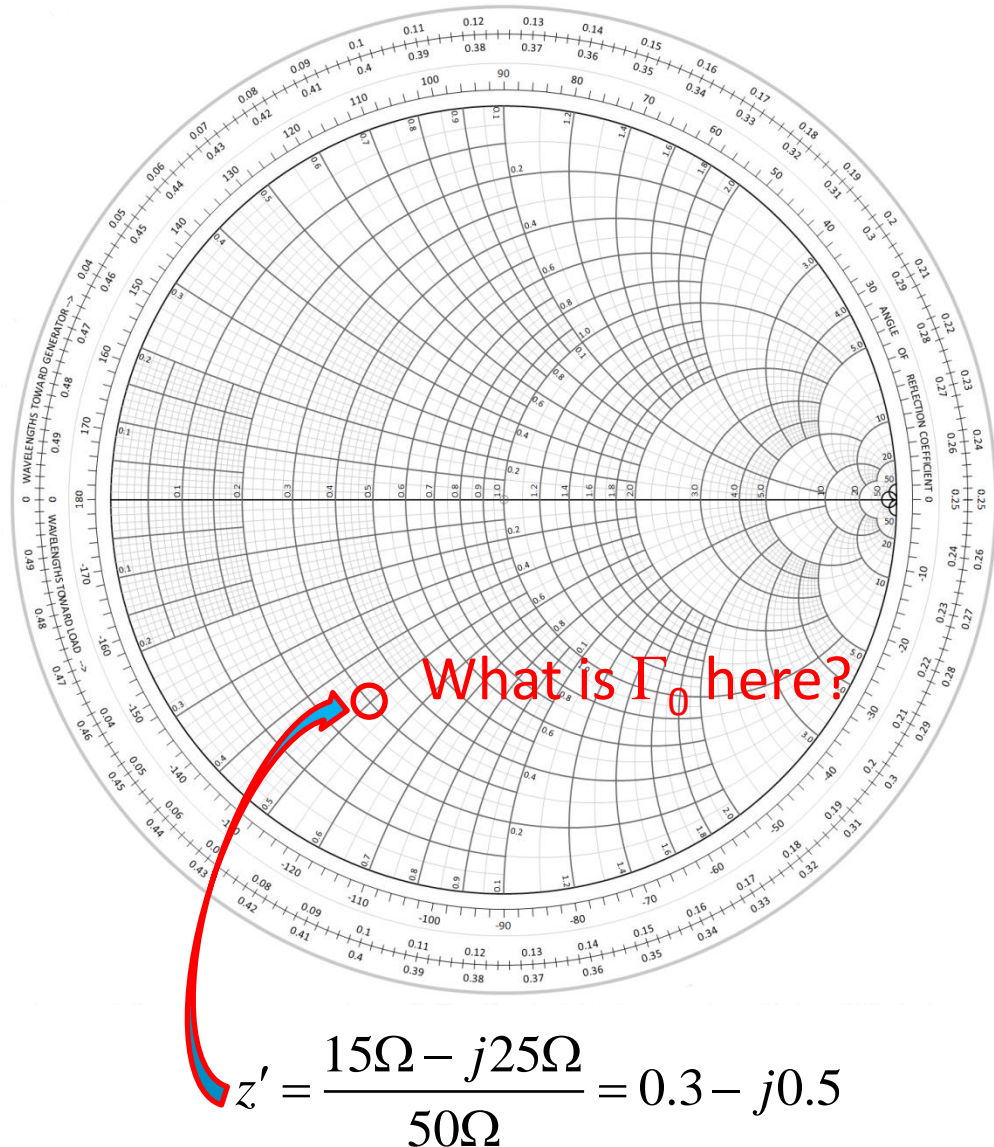- Normalize the given Z_L
- Mark the normalized impedance Smith chart
- Read the value of Γ_0 from Smith chart



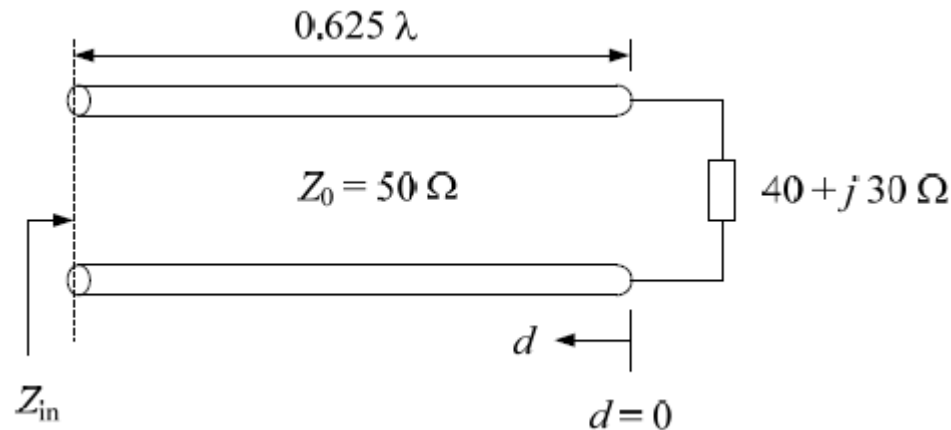Example-3

- Using Smith chart, determine the voltage reflection coefficient at the load and the input impedance of the following TL



$$1. \quad z_L'(d=0) = \frac{Z(d=0)}{Z_0} = \frac{Z_L}{Z_0} = 0.8 + j0.6 \quad \leftarrow \text{Mark this on Smith chart}$$

2. What is Γ_0 ? Read this directly from Smith chart.

$$|\Gamma_0| = 0.33 \quad \angle \Gamma_0 = 90^\circ$$


Example-3 (contd.)

3. For Z_{in}' , rotate the load reflection coefficient point clockwise (towards generator) by $d = 0.625\lambda$ (it is full rotation and then additional rotation of 0.125λ) \rightarrow Then read normalized input impedance from Smith chart

$$z'_{in} = 2 + j0$$

Therefore the
input
impedance of
the TL is:

$$Z_{in} = 50 * z'_{in} = 100\Omega$$

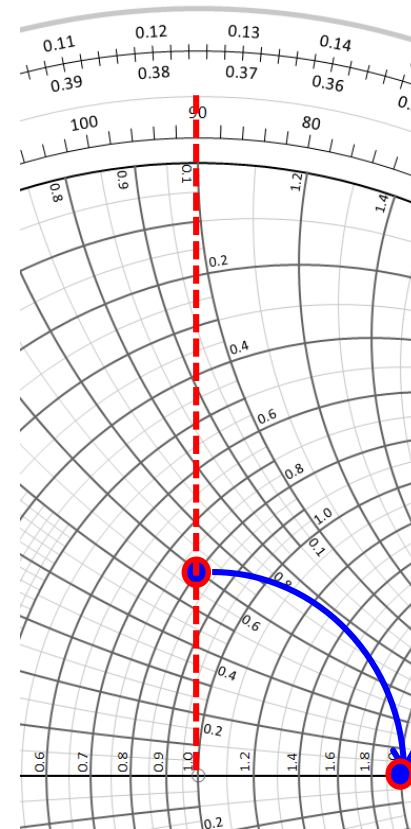

Example – 4

- A load impedance $Z_L = (30 + j60)\Omega$ is connected to a 50Ω TL of 2cm length and operated at 2 GHz. Use the reflection coefficient concept and find the input impedance Z_{in} under the assumption that the phase velocity is 50% of the speed of light

First Approach

- We first determine the load reflection coefficient:

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 + j60 - 50}{30 + j60 + 50} = 0.2 + j0.6 = \sqrt{.40}e^{j71.56^\circ}$$

- Next we compute Γ ($l = 2\text{cm}$) based on the fact that:

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{v_p} = \frac{2\pi f}{0.5c} = 83.77\text{m}^{-1}$$

$$\Rightarrow 2\beta l = 192^\circ \text{ How?}$$

Example – 4 (contd.)

- Therefore, reflection coefficient at the other end of the TL is:

$$\Gamma = \Gamma_0 e^{-j2\beta l} = \sqrt{.40} e^{-120.4^\circ} = -0.32 - j0.55$$

- The corresponding input impedance is:

$$Z_{in} = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = R + jX = (14.7 - j26.7)\Omega$$

Second Approach

Using Smith chart

Example – 4 (contd.)

Using Smith Chart

1. The normalized load impedance is:


$$z_L' = (30 + j60)\Omega / 50\Omega = 0.6 + j1.2$$

2. This point on the Smith chart can be identified as the intersection of the circle of constant resistance $r = 0.6$ with the circle of constant reactance $x = 1.2$
3. The straight line connecting the origin to *normalized load impedance* determines the load reflection coefficient Γ_o . The associated angle is recorded with respect to the positive real axis. From Smith chart we can find that $|\Gamma_o| = 0.6325$ and *phase of $\Gamma_o = 71.56^\circ$* .
4. Rotate clockwise this by $2\beta l = 192^\circ$ to obtain Γ_{in}


Example – 4 (contd.)

phase (Γ_0) = 71.56°

$|\Gamma_0| = 0.6325$

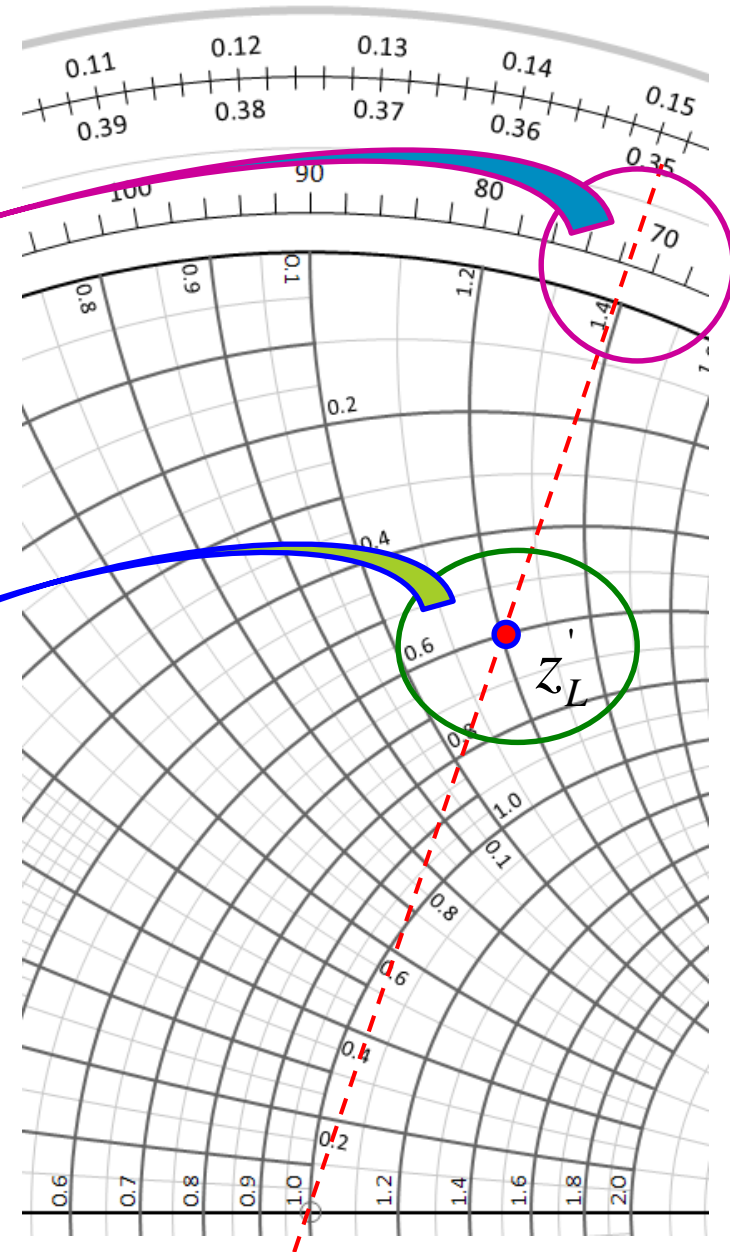

Example – 4 (contd.)

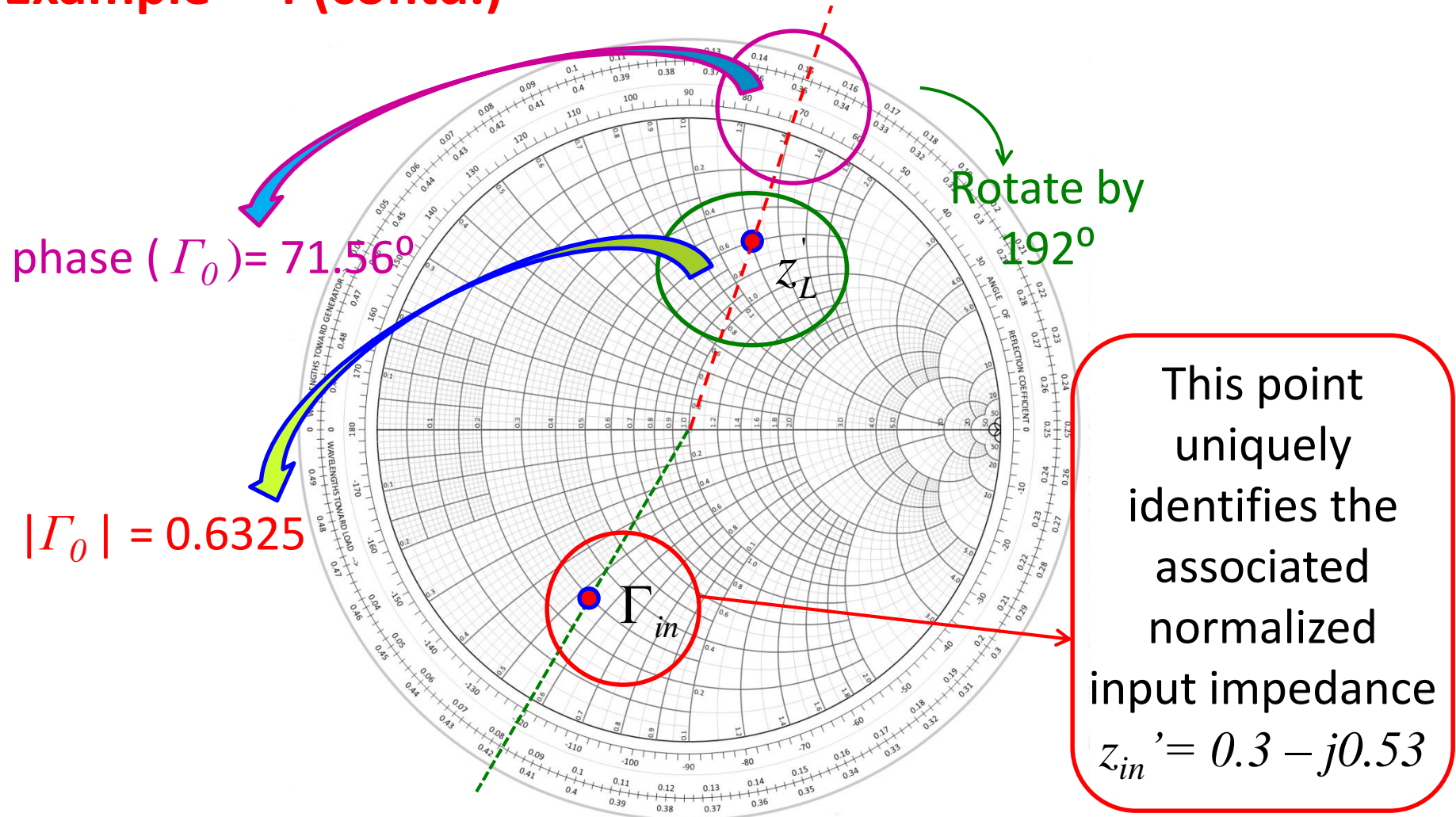

Example – 4 (contd.)

5. The Γ_{in} uniquely identifies the associated normalized input impedance $z_{in}' = 0.3 - j0.53$
6. The preceding normalized impedance can be converted back to actual input impedance values by multiplying it by $Z_0 = 50\Omega$, resulting in the final solution $Z_{in} = (15 - j26.5)\Omega$

The exact value of Z_{in} computed earlier was $(14.7 - j26.7)\Omega$. The small anomaly is expected considering the approximate processing of graphical data in Smith chart

Special Transformation Conditions in Smith Chart

- The rotation angle of the normalized TL impedance around the Smith chart is regulated by the length of TL or operating frequency
- Thus, both capacitive and inductive impedances can be generated based on the length of TL and the termination conditions at a given frequency
- The open- and short-circuit terminations are very popular in generating inductive and capacitive elements

Open Circuit Transformations

- **For an arbitrary terminated line the input impedance is:**

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta z)}{Z_0 + jZ_L \tan(\beta z)} \quad \xrightarrow{\text{For an open circuit}} \quad Z_{in}(z) = -jZ_0 \cot(\beta z)$$

- **For a capacitive impedance of $X_C = 1/j\omega C$ we get:**

$$\frac{1}{j\omega C} \cdot \frac{1}{Z_0} \equiv z_{in} = -j \cot(\beta z_1) \quad \xrightarrow{\quad} \quad z_1 = \frac{1}{\beta} \left[\cot^{-1} \left(\frac{1}{\omega C Z_0} \right) + n\pi \right]$$

Special Transformation Conditions in Smith Chart (contd.)

Open Circuit Transformations

- For an inductive impedance of $X_L = j\omega L$ we get:

$$j\omega L \frac{1}{Z_0} \equiv z'_{in} = -j \cot(\beta z_2) \quad \longrightarrow \quad z_2 = \frac{1}{\beta} \left[\pi - \cot^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$

Short Circuit Transformations

- For an arbitrary terminated line the input impedance is:

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta z)}{Z_0 + jZ_L \tan(\beta z)} \quad \xrightarrow{\text{For a short circuit}} \quad Z_{in}(z) = jZ_0 \tan(\beta z)$$

- For a capacitive impedance of $X_C = 1/j\omega C$ we get:

$$\frac{1}{j\omega C} \cdot \frac{1}{Z_0} \equiv z'_{in} = j \tan(\beta z_1) \quad \longrightarrow \quad z_1 = \frac{1}{\beta} \left[\pi - \tan^{-1} \left(\frac{1}{\omega C Z_0} \right) + n\pi \right]$$

- For an inductive impedance of $X_L = j\omega L$ we get:

$$j\omega L \frac{1}{Z_0} \equiv z'_{in} = j \tan(\beta z_2) \quad \longrightarrow \quad z_2 = \frac{1}{\beta} \left[\tan^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$

Example – 5

- For an open-circuited 50Ω TL operated at 3GHz and with a phase velocity of 77% of speed of light, find the line lengths to create a 2pF capacitor and 5.3nH inductor. Use Smith Chart for solving this problem.

- For the given phase velocity, the propagation constant is:

$$\beta = \frac{2\pi f}{v_p} = \frac{2\pi f}{0.77c} = 81.6m^{-1}$$

- We know that an open-circuit can create a capacitor as per following equation:

$$z_1 = \frac{1}{\beta} \left[\cot^{-1} \left(\frac{1}{\omega C Z_0} \right) + n\pi \right]$$

$$\beta = 81.6m^{-1}$$

$$C = 2pF$$

$$f = 3GHz$$

$$z_1 = 13.27 + n38.5$$

- We know that an open-circuit can create an inductor as per following equation:

$$z_2 = \frac{1}{\beta} \left[\pi - \cot^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$

$$\beta = 81.6m^{-1}$$

$$L = 5.3nH$$

$$f = 3GHz$$


$$z_2 = 32.81 + n38.5$$

Example – 5 (contd.)

Using Smith Chart

- At 3GHz, the reactance of a 2pF capacitor is: $X_C = \frac{1}{j\omega C} = -j26.5\Omega$
- Therefore, the normalized capacitive reactance is: $z'_c = \frac{X_C}{Z_0} = -j0.53$
- At 3GHz, the reactance of a 5.3nH inductor is: $X_L = j\omega L = j100\Omega$
- Therefore, the normalized inductive reactance is: $z'_L = \frac{X_L}{Z_0} = j2$
- The wavelength is: $\lambda = \frac{v_p}{f} = 77mm$

Example – 5 (contd.)

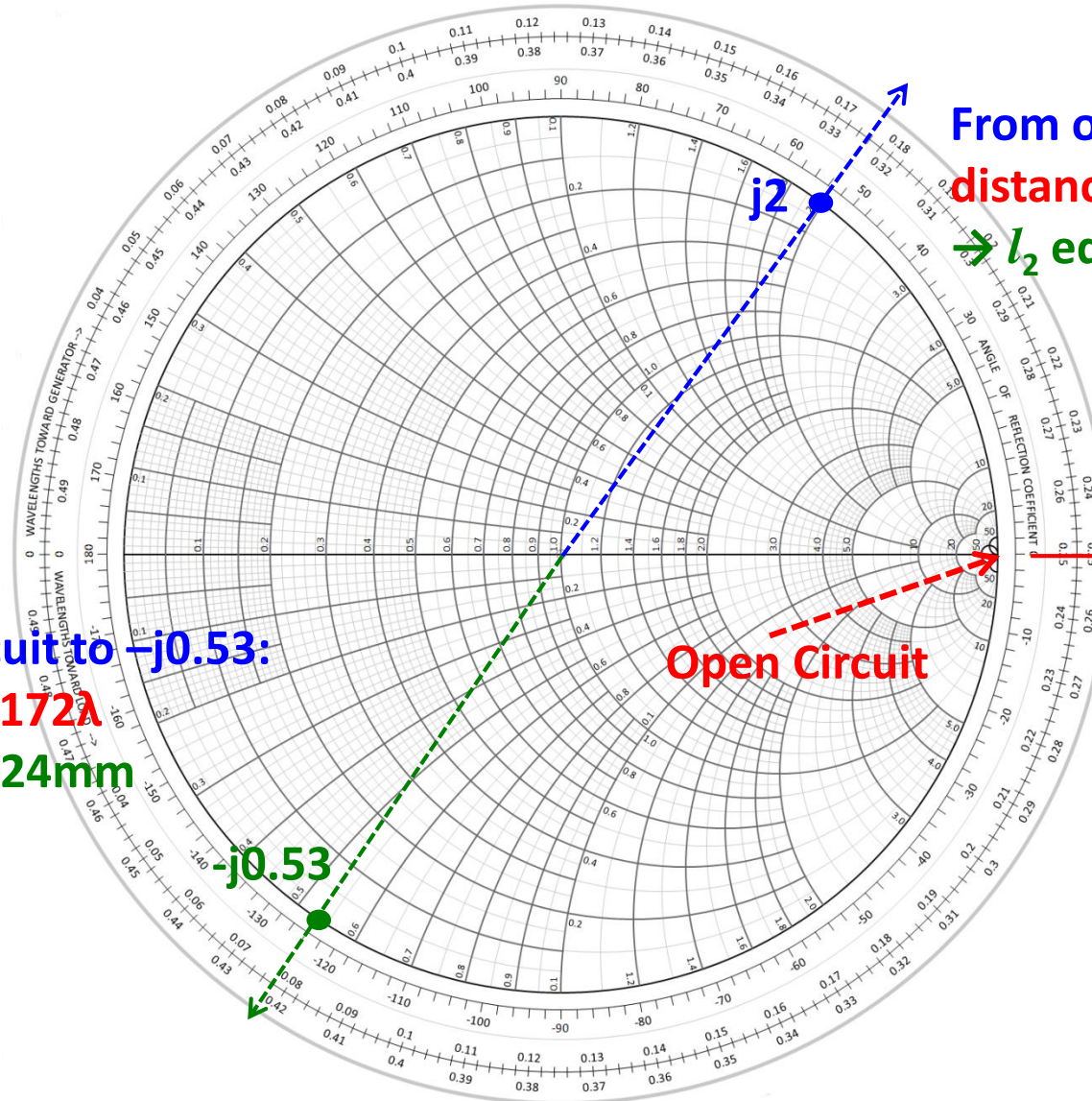

From open-circuit to $j2$:
distance l_2 is 0.426λ
→ l_2 equals 32.8mm


From open-circuit to $-j0.53$:
distance l_1 is 0.172λ
→ l_1 equals 13.24mm

Open Circuit

Towards
Generator

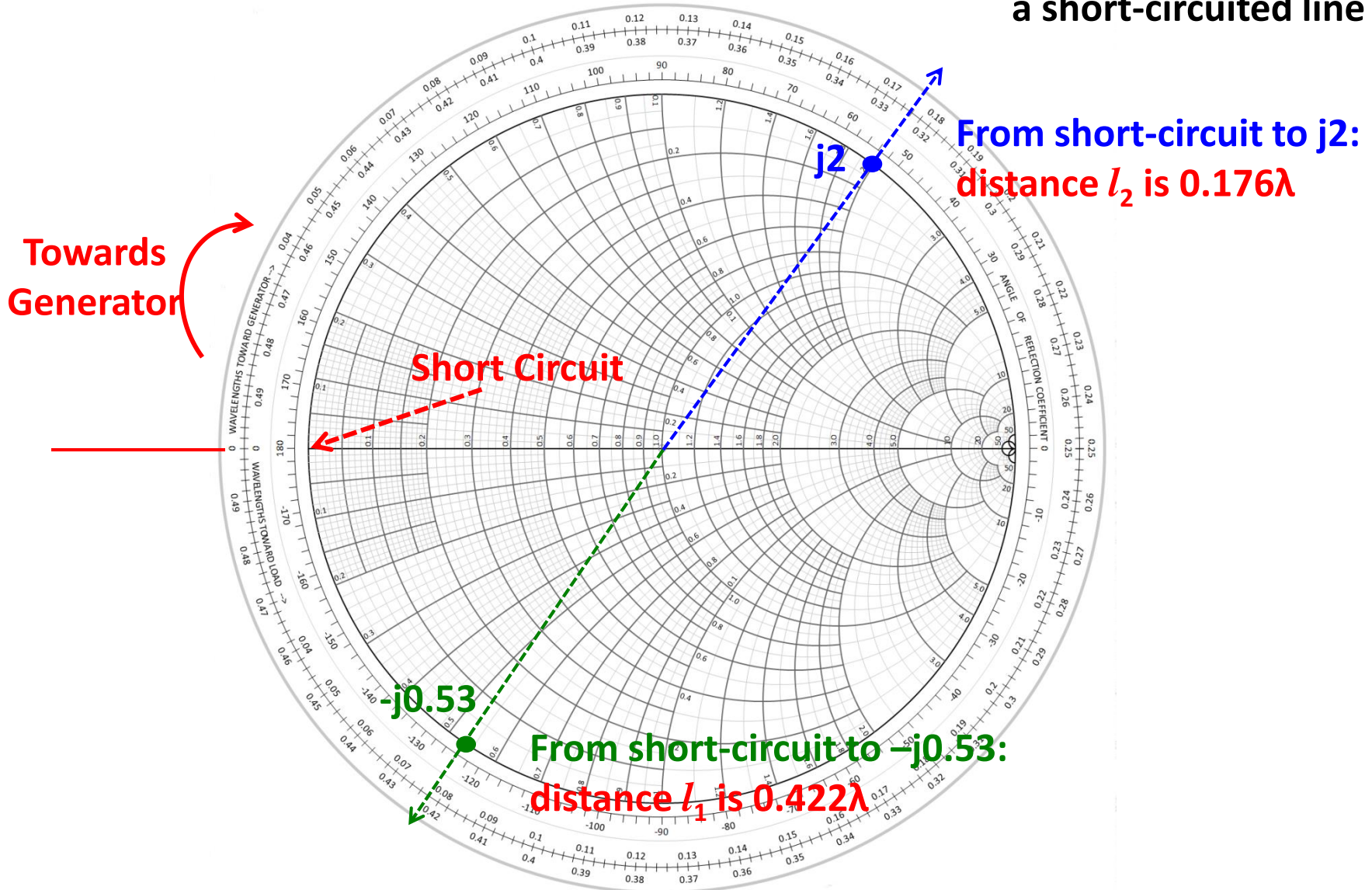Example – 6

- Same problem but for a short-circuited line




Special Transformation Conditions in Smith Chart (contd.)

Summary

- It is apparent that both open-circuit and short-circuit TLs can achieve desired capacitance or inductance. Which configuration is more useful?
- At high frequencies, it's difficult to maintain perfect open-circuit conditions → due to changing temperatures, humidity, and other parameters of the medium surrounding the open TL → short-circuit TLs are, therefore, more popular
- However, short-circuit TL is problematic at higher frequencies → through-hole short connections create parasitic inductances (why?)
- Sometimes board size regulates the choice of open or short TL → for example, an open-circuit TL will always require smaller TL segment for realizing any specified capacitance as compared to a short-circuit TL segment

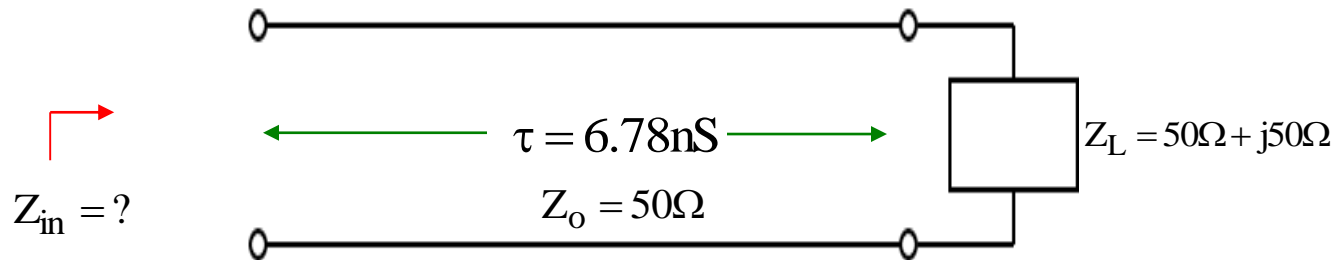Example – 7

What is Z_{in} at 50 MHz for the following circuit?



1. Normalized Impedance: $z_L' = \frac{50 \Omega + j50 \Omega}{50 \Omega} = 1.0 + j1.0$
2. Mark the normalized impedance on the Smith chart
3. Read reflection coefficient from Smith Chart: $\Rightarrow \Gamma_0 = 0.445 \angle 64^\circ$
4. Transform the load reflection coefficient to the input:

$$\Gamma_{in} = \Gamma_0 e^{-j2\beta l} = \Gamma_0 e^{-j2\omega\tau}$$

$2\omega\tau = 244^\circ$


Rotate clockwise (towards generator)

$$\Rightarrow \Gamma_{in} = 0.445 \angle 180^\circ$$

Read the normalized
input impedance in the
Smith chart

$$z_{in}' = 0.38 + j0.0$$


Example – 7 (contd.)

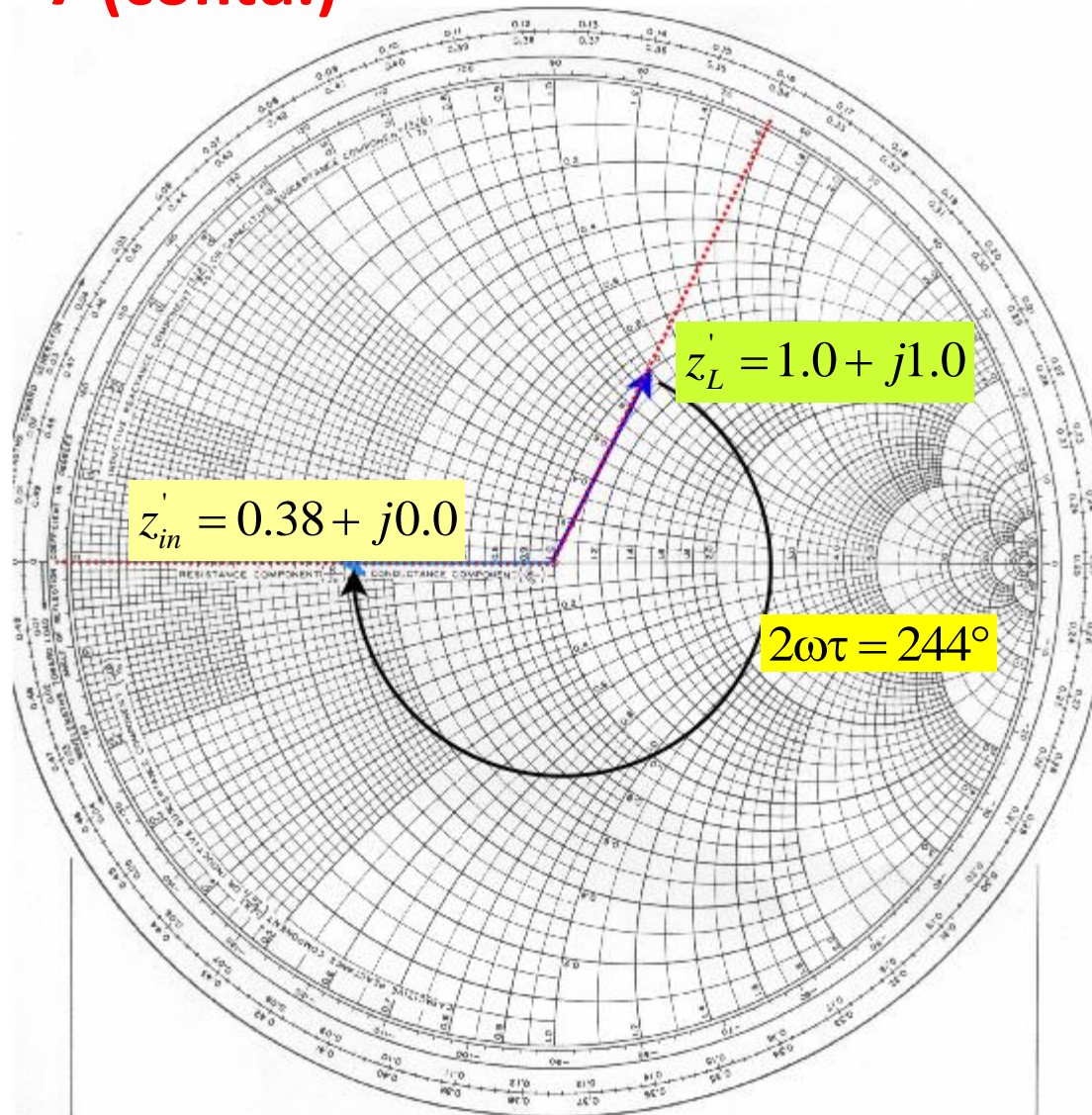

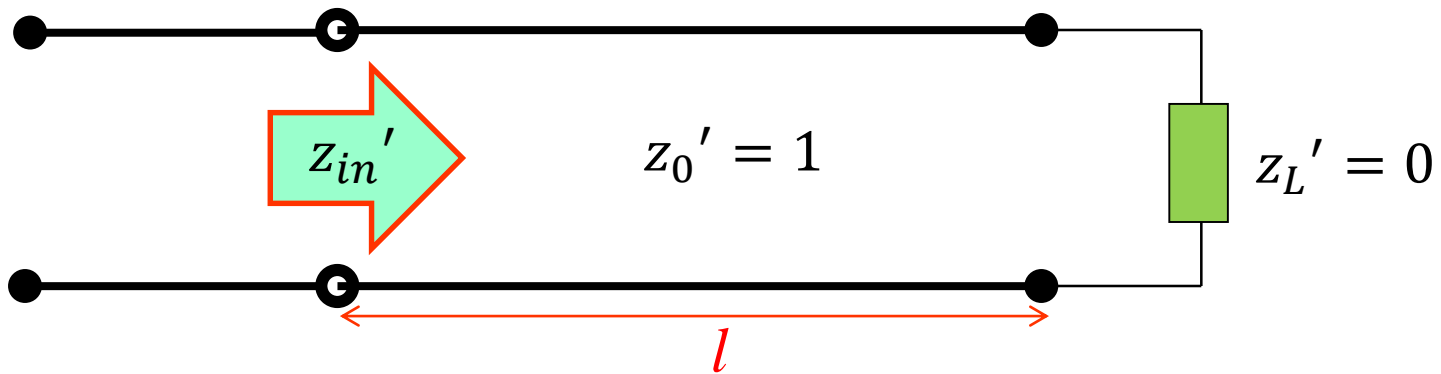Example – 8

- determine the input impedance of a transmission line that is terminated in a **short circuit**, and whose length is:

$$\begin{aligned} \text{a) } l &= \lambda/8 = 0.125\lambda & \Rightarrow & 2\beta l = 90^\circ \\ \text{b) } l &= 3\lambda/8 = 0.375\lambda & \Rightarrow & 2\beta l = 270^\circ \end{aligned}$$



- Solution:**

a) Rotate **clockwise** 90° from $\Gamma = -1.0 = e^{j180^\circ}$ and find Z_{in}' .

$$Z_{in}' = j$$


b) Rotate **clockwise** 270° from $\Gamma = -1.0 = e^{j180^\circ}$ and find Z_{in}' .

$$Z_{in}' = -j$$

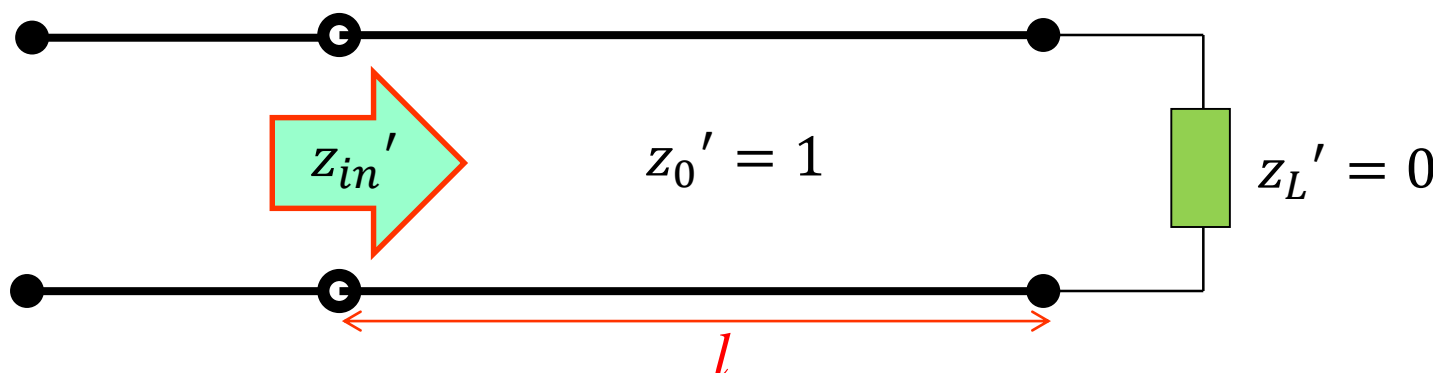Example – 9

- determine the input impedance of a transmission line that is terminated in a **short circuit**, and whose length is:

$$\begin{aligned} \text{a) } l &= \lambda/8 = 0.125\lambda & \Rightarrow & 2\beta l = 90^\circ \\ \text{b) } l &= 3\lambda/8 = 0.375\lambda & \Rightarrow & 2\beta l = 270^\circ \end{aligned}$$



Solution:

- a) Rotate **clockwise** 90° from $\Gamma = -1.0 = e^{j180^\circ}$ and find Z_{in}' .

$$Z_{in}' = j$$

- b) Rotate **clockwise** 270° from $\Gamma = -1.0 = e^{j180^\circ}$ and find Z_{in}' .

$$Z_{in}' = -j$$

Example – 10

- A load **terminating** at transmission line has a normalized impedance $z_L' = 2.0 + j2.0$. What should the **length** l of transmission line be in order for its input impedance to be:
 - a) Purely **real** (i.e., $X_{in} = 0$)
 - b) Have a real (resistive) part equal to **one** (i.e., $r_{in} = 1.0$)

- **Solution:**

- a) Find $z_L' = 2.0 + j2.0$ on your Smith Chart, and then rotate **clockwise** until you “bump into” the contour $x = 0$ (recall this contour lies on the Γ_r – **axis!**).
- When you reach the $x = 0$ contour—**stop!** Lift your pen and note that the impedance value of this location is **purely real** (after all, $x = 0$!).
- Now, measure the **rotation angle** that was required to move clockwise from $z_L' = 2.0 + j2.0$ to an impedance on the $x = 0$ contour—this **angle** is equal to $2\beta l$!

You can now **solve** for l , or alternatively use the **electrical length scale** surrounding the Smith Chart.

Example – 10 (contd.)

One more important point—there are **two** possible solutions!

$$z_{in}' = 4.2 + j0 \quad \xrightarrow{\text{yellow}} \quad 2\beta l = 30^\circ \quad \xrightarrow{\text{red}} \quad l = 0.042\lambda$$

$$z_{in}' = 0.24 + j0 \quad \xrightarrow{\text{red}} \quad 2\beta l = 210^\circ \quad \xrightarrow{\text{green}} \quad l = 0.292\lambda$$

b) Find $z_L' = 2.0 + j2.0$ on your Smith Chart, and then rotate **clockwise** until you “bump into” the **circle** $r = 1$ (recall this circle intersects the **center** point of the Smith Chart!).

- When you reach the $r = 1$ circle—**stop**! Lift your pencil and note that the impedance value of this location has a real value equal to **one** (after all, $r = 1$!).
- Now, measure the **rotation angle** that was required to move clockwise from $z_L' = 2.0 + j2.0$ to an impedance on the $r = 1$ circle—this **angle** is equal to $2\beta l$!

Example – 10 (contd.)

- Thus, for impedances where $r = 1$ (i.e., $z' = 1 + jx$):

$$\Gamma = \frac{z' - 1}{z' + 1} = \frac{(1 + jx) - 1}{(1 + jx) + 1} = \frac{jx}{2 + jx}$$

- and therefore:

$$|\Gamma|^2 = \frac{|jx|^2}{|2 + jx|^2} = \frac{x^2}{4 + x^2}$$

$$x^2 = \frac{4|\Gamma|^2}{1 - |\Gamma|^2}$$

there are **two** equal by
opposite solutions!

$$x = \pm \frac{2|\Gamma|}{\sqrt{1 - |\Gamma|^2}}$$

for **this** example gives us solutions $x = \pm 1.6$.

Admittance Transformation

- RF/Microwave network, similar to any electrical network, has impedance elements in series and parallel
- Impedance Smith chart is well suited while working with series configurations while admittance Smith chart is more useful for parallel configurations
- The impedance Smith chart can easily be used as an **admittance calculator**

$$z_{in}(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \quad \leftarrow \quad y_{in}(z) = \frac{Y_{in}(z)}{Y_0} = \frac{1/Z_{in}(z)}{1/Z_0} = \frac{1}{Z_{in}(z)/Z_0} = \frac{1}{z_{in}(z)}$$

Hence, $y_{in}(z) = \frac{1 - \Gamma(z)}{1 + \Gamma(z)}$ \rightarrow $y_{in}(z) = \frac{1 + e^{-j\pi}\Gamma(z)}{1 - e^{-j\pi}\Gamma(z)}$

It means, to obtain normalized admittance \rightarrow take the normalized impedance and multiply associated reflection coefficient by $-1 = e^{-j\pi} \rightarrow$ it is equivalent to a 180° rotation of the reflection coefficient in complex Γ -plane

Example – 11

- Convert the following **normalized input impedance z_{in}'** into **normalized input admittance y_{in}'** using the Smith chart:

$$z_{in}' = 1 + j1 = \sqrt{2}e^{j(\pi/4)}$$

First approach: The normalized admittance can be found by direct inversion as:

$$y_{in}' = \frac{1}{z_{in}'} = \frac{1}{1 + j1} = \frac{1}{\sqrt{2}}e^{-j(\pi/4)} = \frac{1}{2} - j\frac{1}{2}$$

Alternative approach:


- Mark the normalized impedance on Smith chart
- Identify phase angle and magnitude of the associated reflection coefficient
- Rotate the reflection coefficient by 180°
- Identify the **x-circle** and **r-circle** intersection of the rotated reflection coefficient

Example – 11 (contd.)

Quick investigation
show that the
normalized
impedance (y_{in}') is
the intersection of
r-circle of $1/2$ and
x-circle of $-1/2$

To denormalize, multiply
with the inverse of Z_0 .
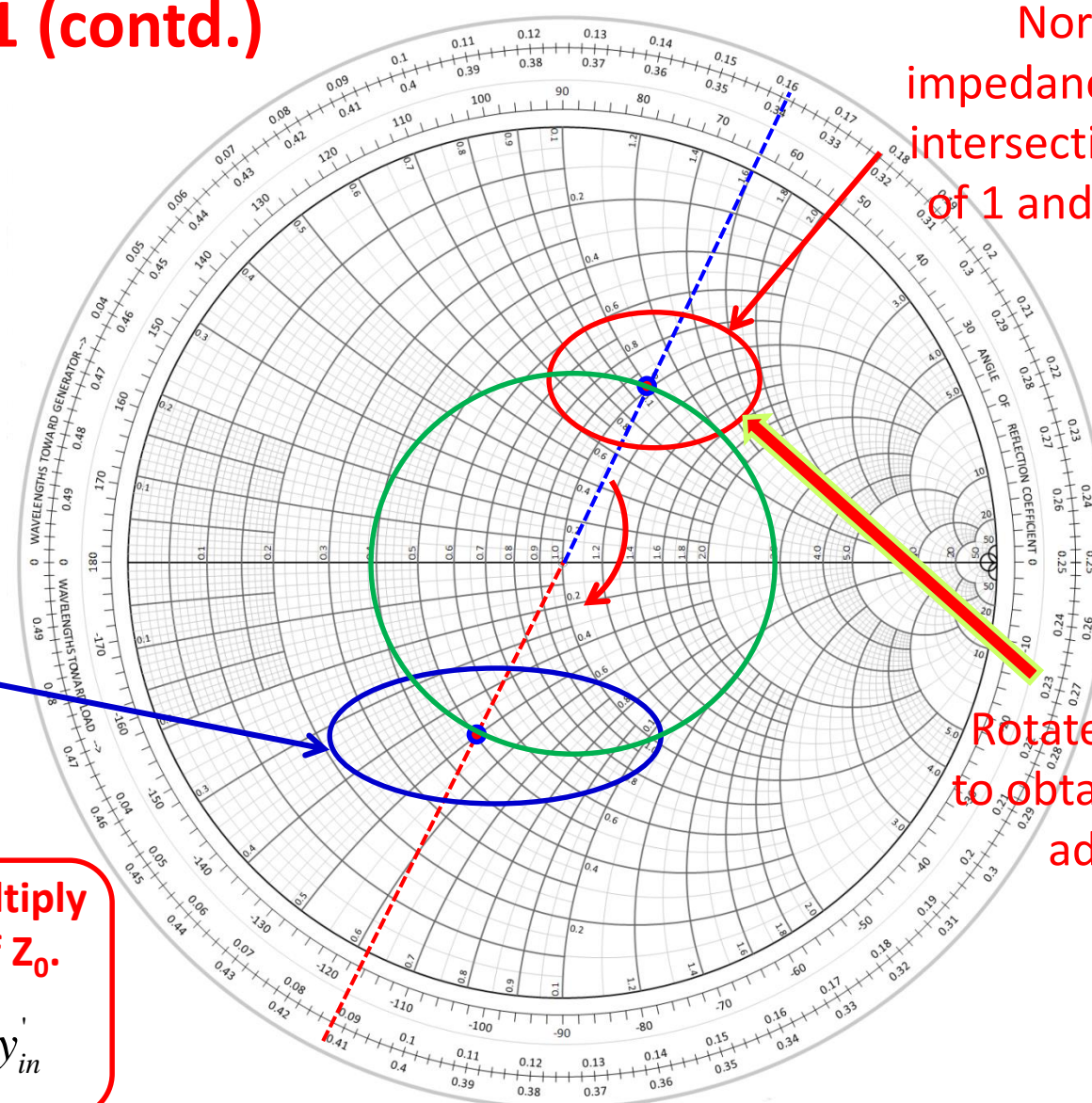
$$Y_{in} = y_{in}' \frac{1}{Z_0} = Y_0 y_{in}'$$



Example – 12


Given: $z'_{in} = 1 + j2$

- Find the normalized admittance $\lambda/8$ away from the load

Steps:

1. Mark the normalized impedance on Smith Chart
2. Clockwise rotate it by 180°
3. Identify the normalized impedance and the phase angle of the associated reflection coefficient
4. Clockwise rotate the reflection coefficient (associated with the normalized admittance) by $2\beta l$ (here $l = \lambda/8$)
5. The new location gives the required normalized admittance

Example – 12 (contd.)

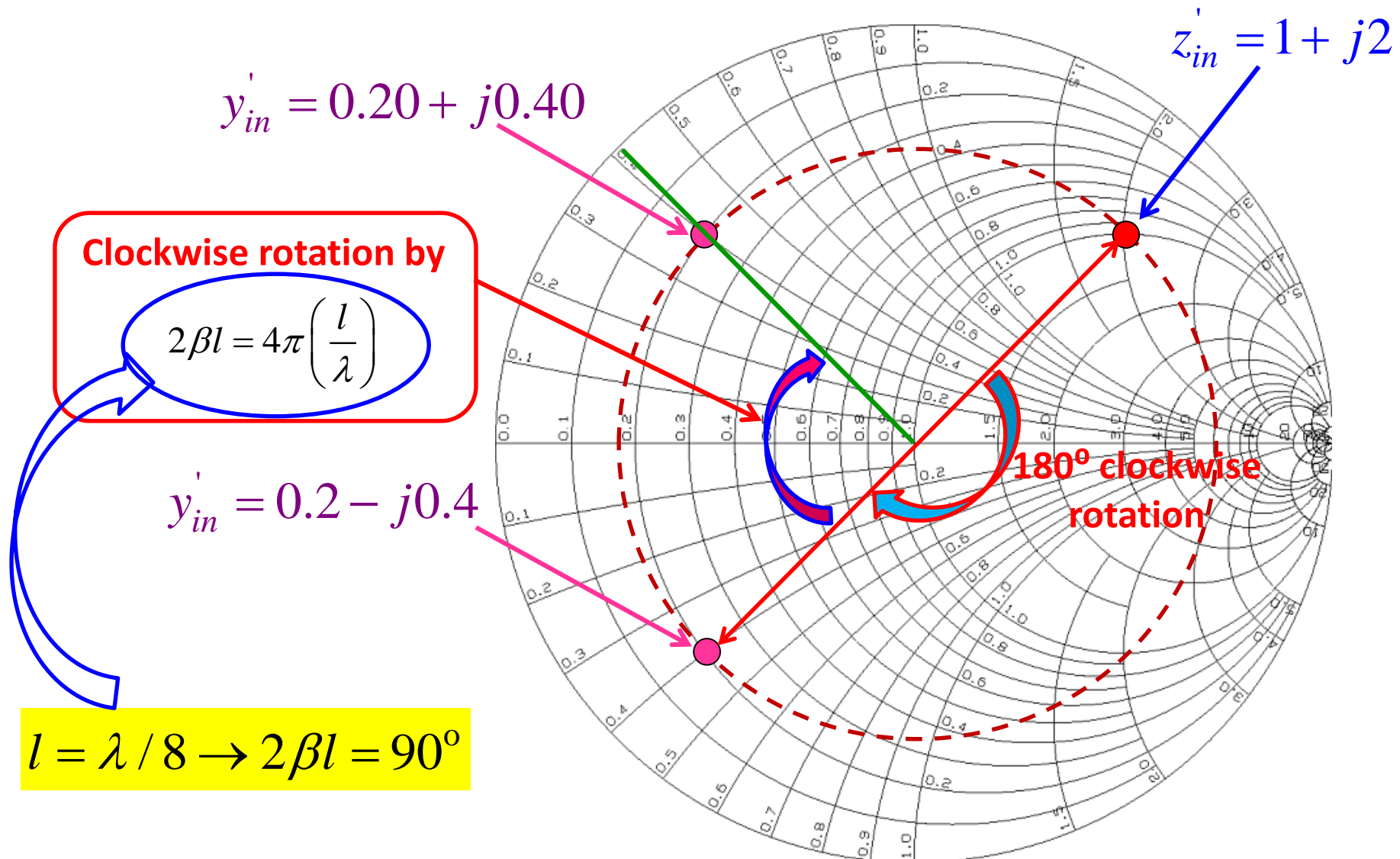

Admittance Smith chart


- Alternative approach to solve parallel network elements is through 180° rotated Smith chart
- This rotated Smith chart is called **admittance Smith chart** or **Y-Smith chart**
- The corresponding **normalized resistances** become **normalized conductances** & **normalized reactances** become **normalized susceptances**

$$r = \frac{R}{Z_0} \Rightarrow g = \frac{G}{Y_0} = Z_0 G$$

$$x = \frac{X}{Z_0} \Rightarrow b = \frac{b}{Y_0} = Z_0 B$$

- **The Y-Smith chart preserves:**
 - The direction in which the angle of the reflection coefficient is measured
 - The direction of rotation (either toward or away from the generator)


Admittance Smith chart (contd.)

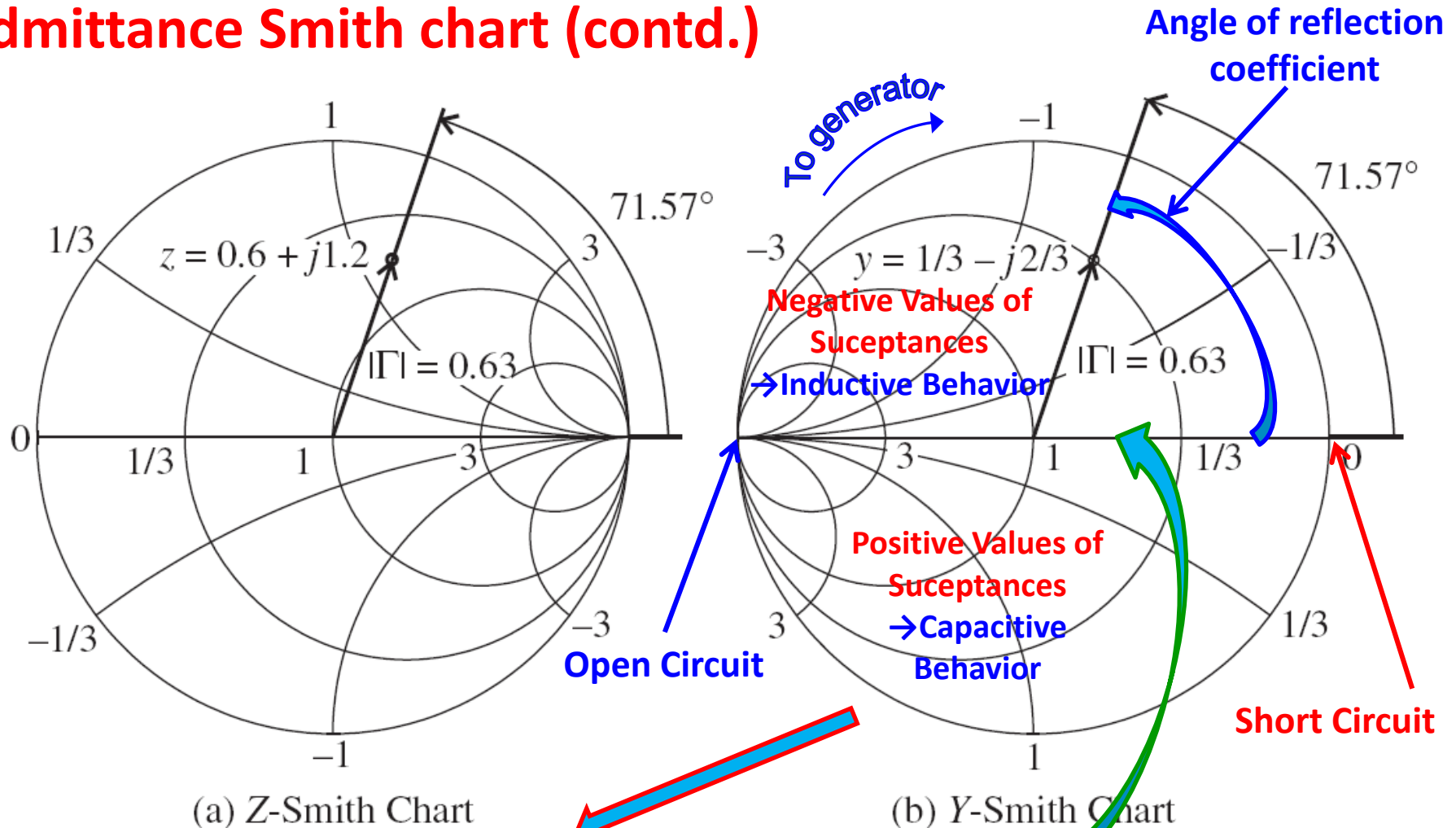

In this chart, admittance is represented in exactly the same manner as the impedance in the Z-smith Chart
→ without 180° rotation

Combined Z- and Y- Smith Charts

Red: Z – Smith Chart

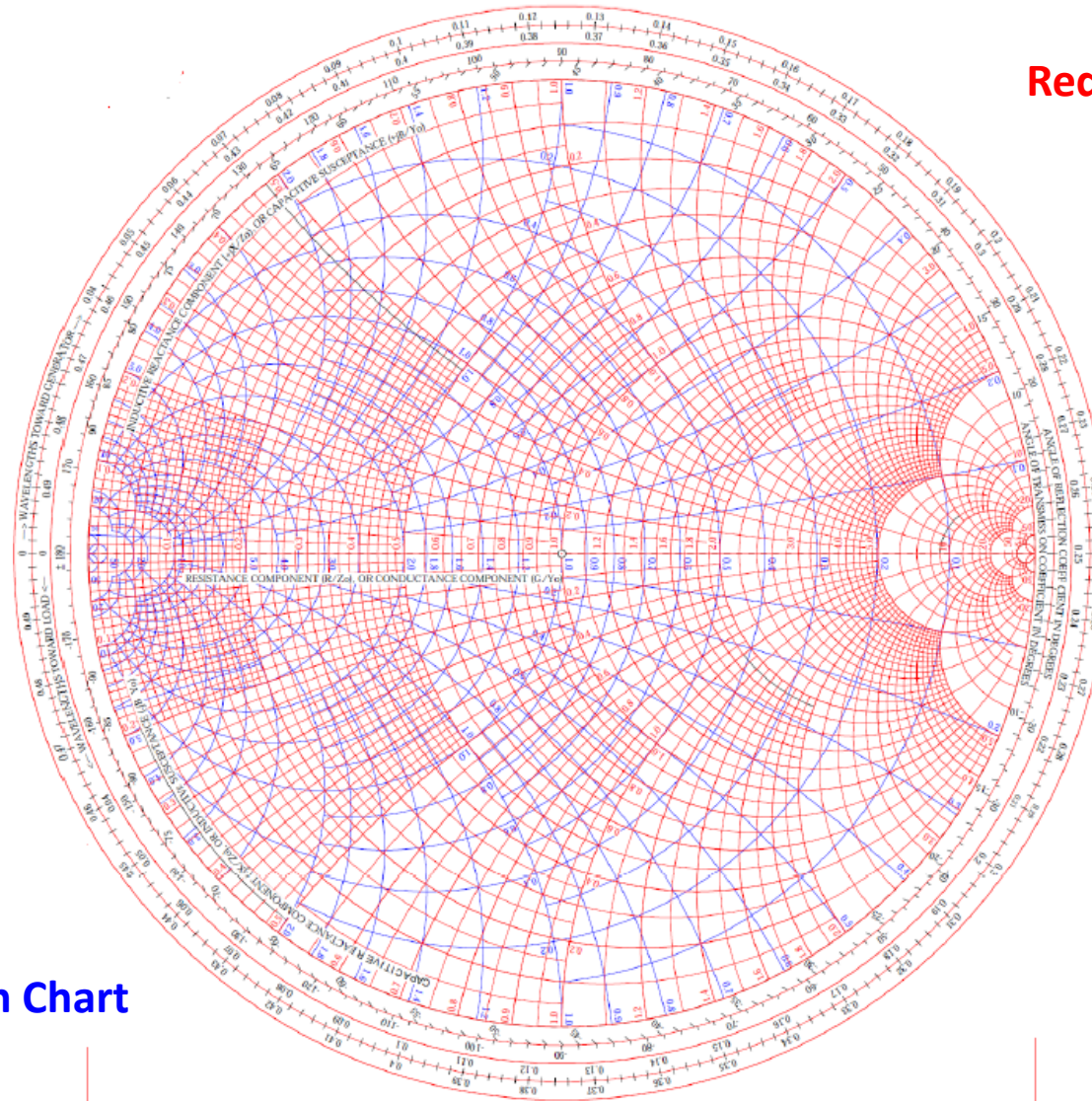

Blue: Y – Smith Chart

Example – 13

- Identify (a) the normalized impedance $z' = 0.5 + j0.5$, and (b) the normalized admittance value $y' = 1 + j2$ in the combined ZY-Smith Chart and find the corresponding values of normalized admittance and impedance

Example – 13 (contd.)

