


## **Lecture – 12**

**Date: 09.02.2017**

- Microstrip Matching Networks
- Series- and Shunt-stub Matching
- Quarter Wave Impedance Transformer
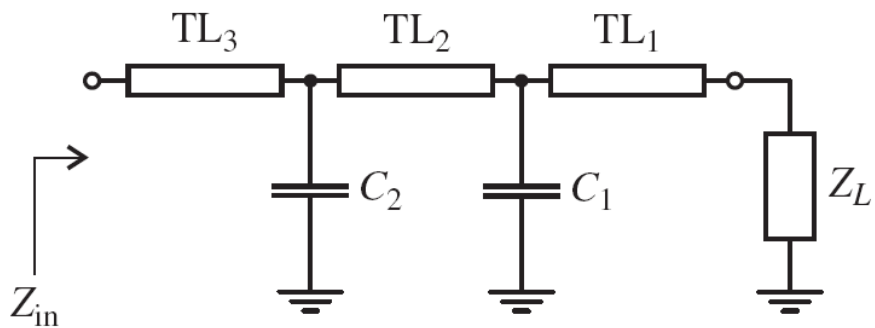
## Microstrip Line Matching Networks

- In the lower RF region, it's often a standard practice to use a hybrid approach that combines lumped and distributed elements → These types of matching circuits usually contain TL segments in series and capacitors in shunt.



- Inductors are avoided in these designs as they tend to have higher resistive losses as compared to capacitors.
- In principle, only one shunt capacitor with two TL segments connected in series on both sides is sufficient to transform any given load impedance to any input impedance.
- Similar to the L-type matching network, these configurations may also involve the additional requirement of a fixed  $Q_n$ , necessitating additional components to control the bandwidth of the circuit.

## Microstrip Line Matching Networks (contd.)

- In practice, these configurations are extremely useful as they permit tuning of the circuits even after manufacturing → changing the values of capacitors as well as placing them at different locations along the TL offers a wide range of flexibility → In general, all the TL segments have the same width to simplify the actual tuning → the tuning ability makes these circuits very appropriate for prototyping.

### Example – 1


Design a hybrid matching network that transforms the load  $Z_L = (30 + j10)\Omega$  to an input impedance  $Z_{in} = (60 + j80)\Omega$ . The matching network should contain only two series TL segments and one shunt capacitor. Both TLs have a  $50\Omega$  characteristic impedance, and the frequency at which the matching is required is  $f = 1.5$  GHz

#### Solution

- Mark the normalized load impedance  $(0.6 + j0.2)$  on the Smith chart.
- Draw the corresponding SWR circle.
- Mark the normalized input impedance  $(1.2 + j1.6)$  on the Smith chart.
- Draw the corresponding SWR circle.
- The choice of the point from which we transition from the load SWR circle to the input SWR circle can be made arbitrarily.
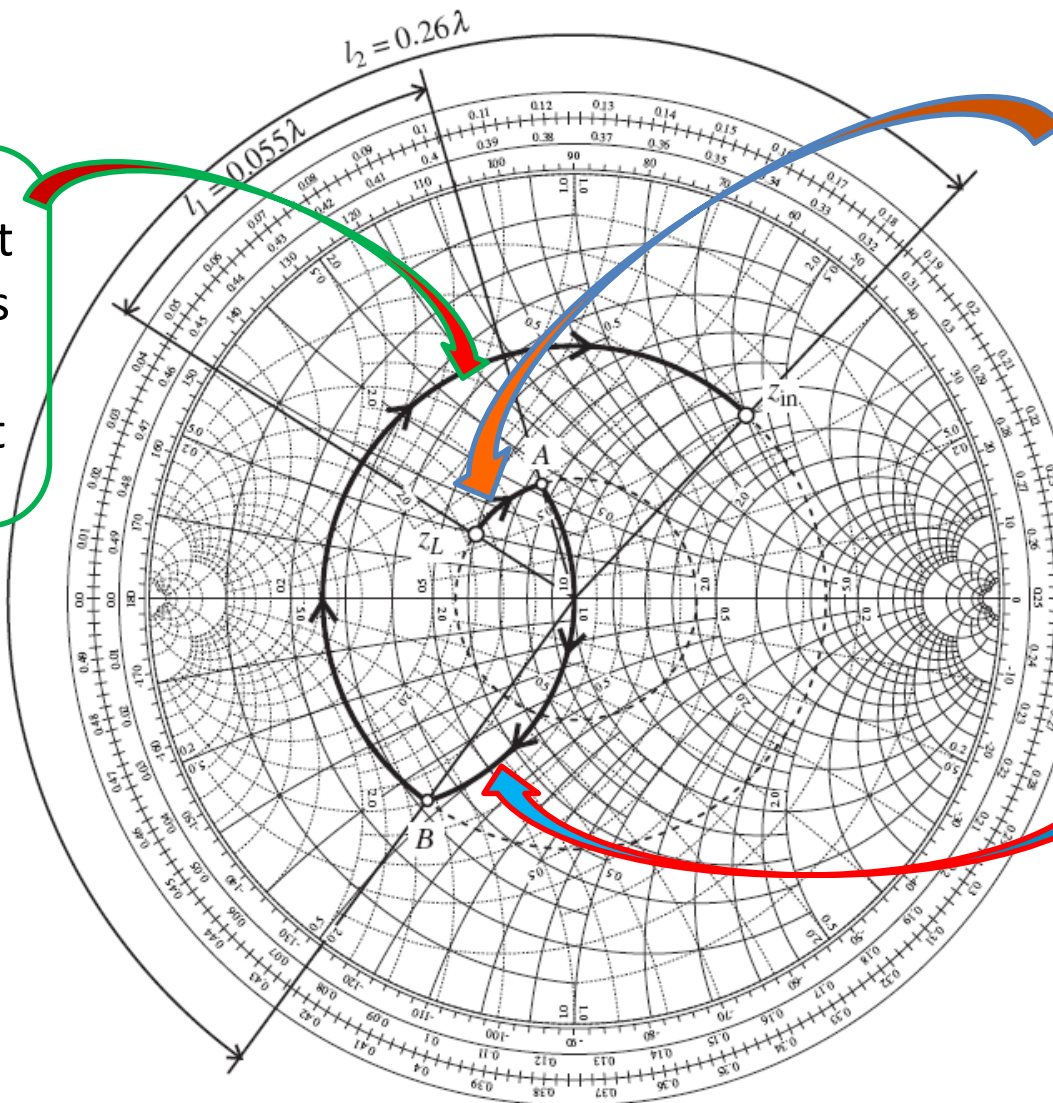
## Example – 1 (contd.)

point B to  
normalized input  
impedance gives  
length of the  
second segment  
of TL





Normalized load  
to the point A  
gives length of  
the first segment  
of TL

A to B provides  
the necessary  
susceptance  
value for the  
shunt capacitor

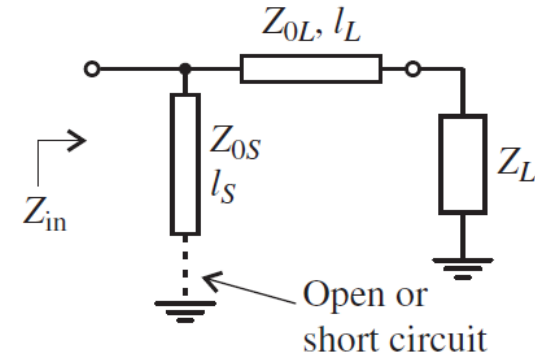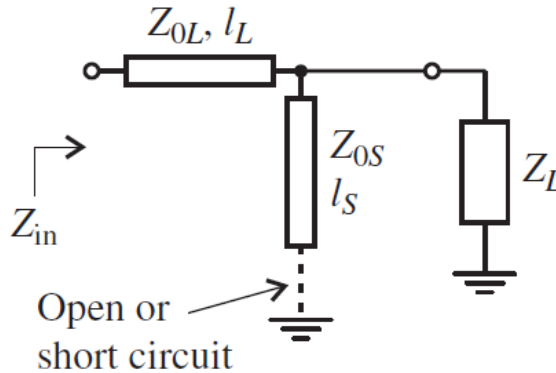
## Stub Matching Networks

- The next logical step is the complete elimination of all lumped components  $\rightarrow$  this can be achieved by employing open – and/or short – circuited stub lines


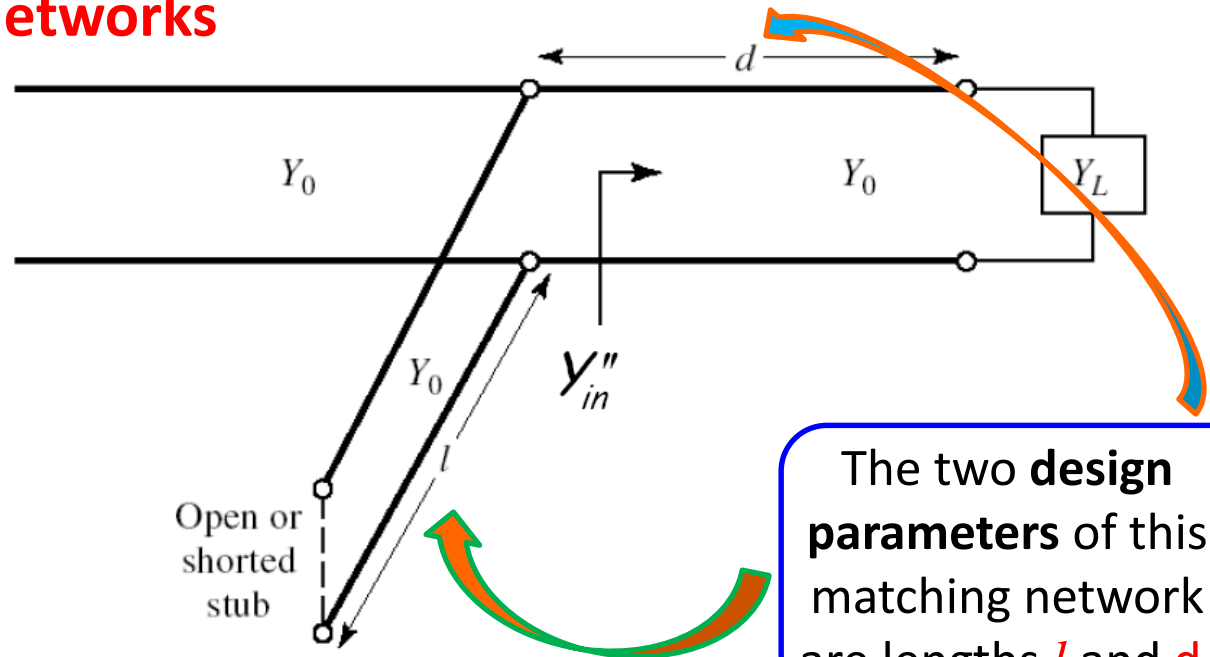
## Shunt-stub Matching Networks


- Let us consider this configuration with shunt stub.



The two **design parameters** of this matching network are lengths  $l$  and  $d$ .
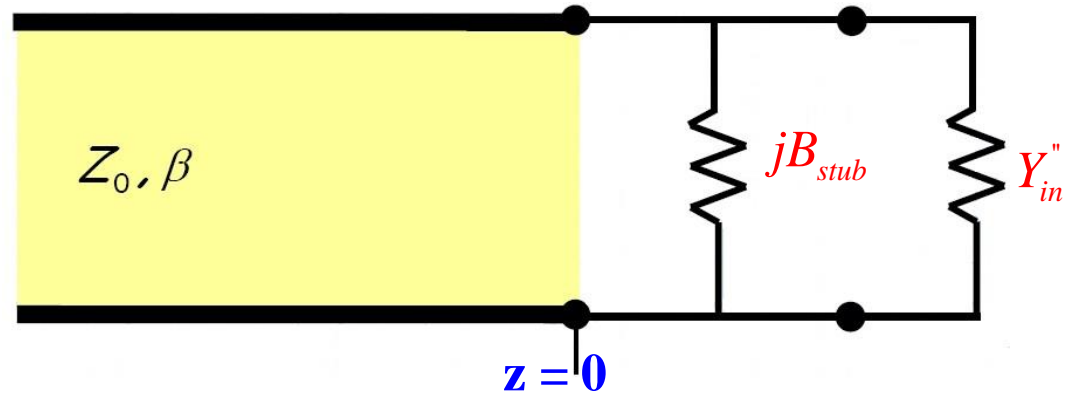
## Shunt-stub Matching Networks (contd.)

- An equivalent circuit for the shunt-tub TL can be:



Where:

$$Y_{in}'' = Y_0 \left( \frac{Y_L + jY_0 \tan(\beta d)}{Y_0 + jY_L \tan(\beta d)} \right)$$

$$jB_{stub} = \begin{cases} jY_0 \tan(\beta l) & \text{For open-stub} \\ -jY_0 \cot(\beta l) & \text{For short-stub} \end{cases}$$

- Therefore, for a matched circuit, we require:  $jB_{stub} + Y_{in}'' = Y_0$
- Note this complex equation is actually **two real equations!**

$$\text{Re}\{Y_{in}''\} = Y_0$$

$$\text{Im}\{jB_{stub} + Y_{in}''\} = 0 \Rightarrow B_{stub} = -B_{in}''$$

Where:  $B_{in}'' = \text{Im}\{Y_{in}''\}$

## Shunt-stub Matching Networks (contd.)

- Since  $Y_{in}''$  is dependent on  $d$  only, our **design procedure** is:

1) Set  $d$  such that  $\text{Re}\{Y_{in}''\} = Y_0$ .

2) Then set  $\ell$  such that  $B_{stub} = -B_{in}''$ .

We have two choice, either **Analytical** or **Smith** chart for finding out the lengths  $d$  and  $\ell$

### Use of the Smith Chart to determine the lengths!

- Rotate **clockwise** around the Smith Chart from  $y_L$  until you intersect the  $g_s=1$  **circle**. The “length” of this rotation determines the value  $d$ . Recall there are **two** possible solutions!
- Rotate **clockwise** from the short/open circuit point around the  $g = 0$  **circle**, until  $b_{stub}$  equals  $-b_{in}''$ . The “length” of this rotation determines the stub length  $\ell$ .

### Example – 2


Let us take the case where we want to match a load of  $Z_L = (60-j80)\Omega$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .



## Example – 2 (contd.)
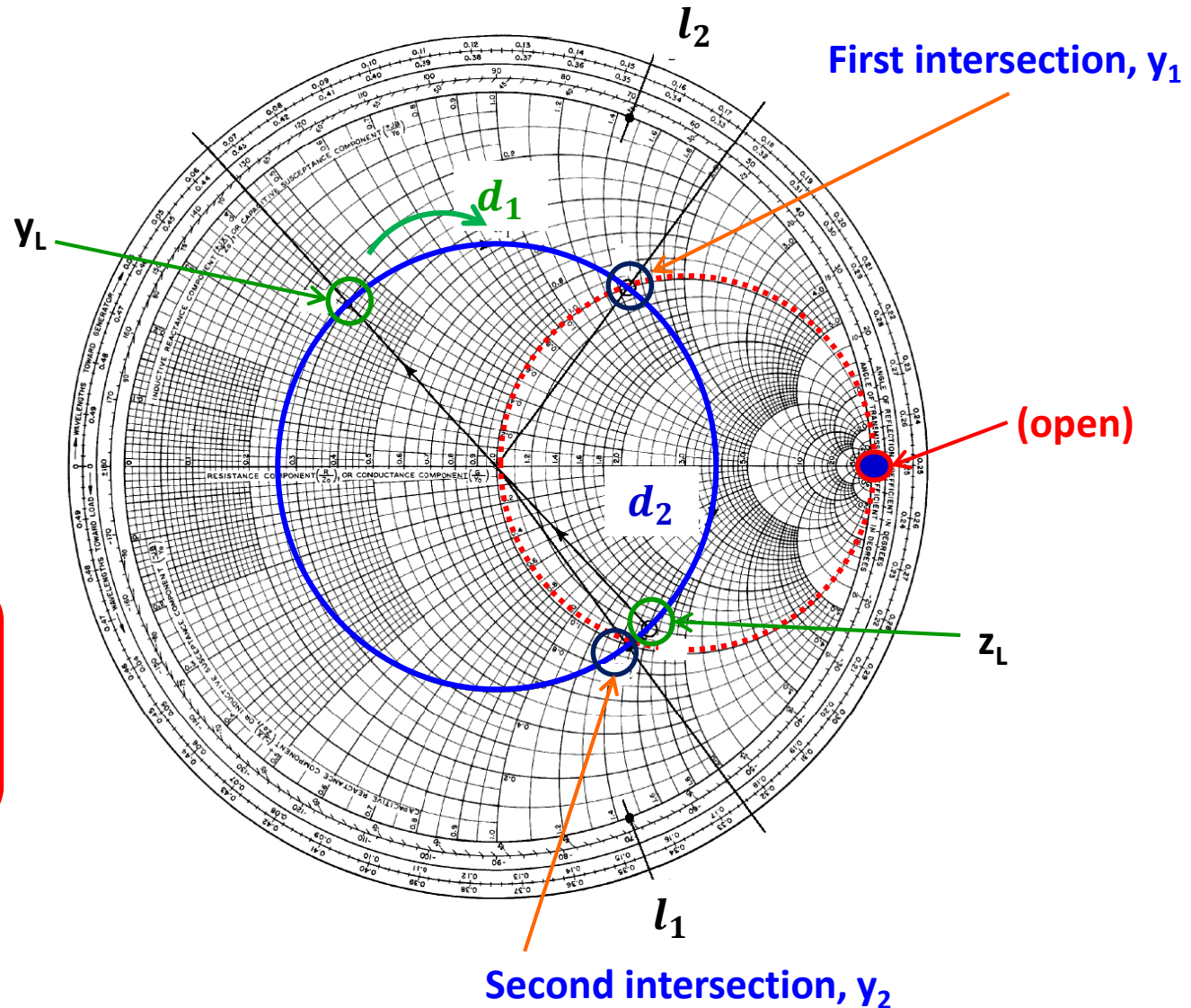
### Solution

$y_L$  to  $y_1$  towards  
generator  
(clockwise) gives  
length  $d_1$  (first  
solution)




$y_L$  to  $y_2$  towards  
generator (clockwise)  
gives length  $d_2$   
(second solution)



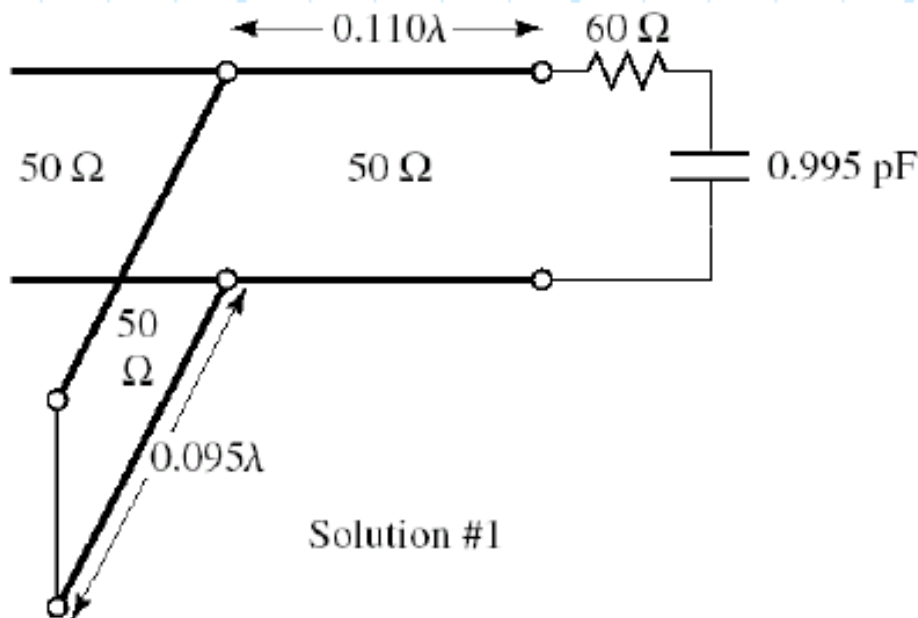
## Example – 2 (contd.)

- Determine the respective admittances at the two intersection points
- These are of the form  $1 + jx$  and  $1 - jx$
- Cancel these imaginary part of the admittances by introducing shunt-stubs of length  $l_1$  and  $l_2$  respectively
- $l_1$  and  $l_2$  are the lengths from open circuit point in the Smith chart (if open stub is used) along the  $g = 0$  circle until the achieved admittances are of opposite signs to those at the intersection points in the earlier step



Solution #1

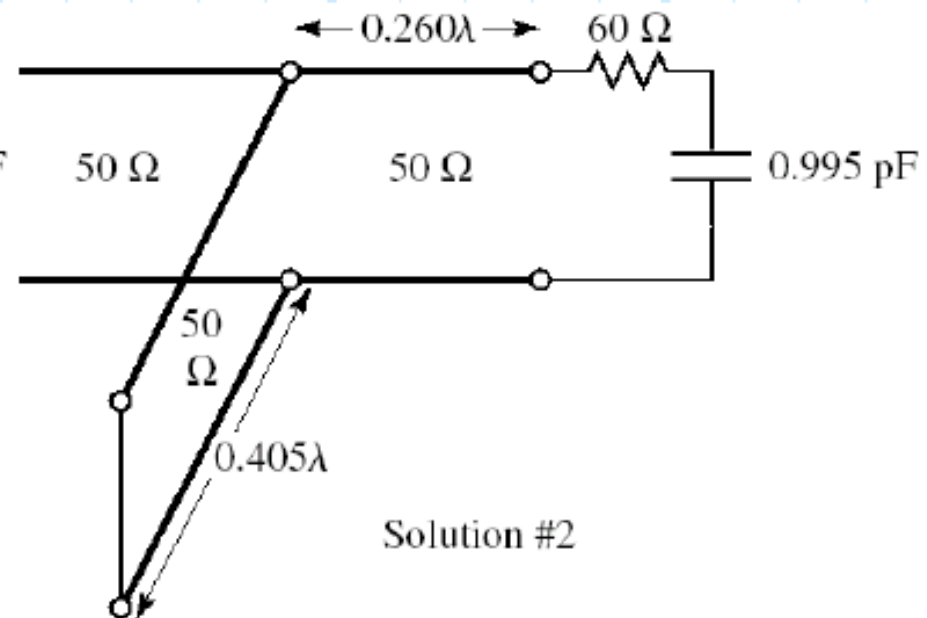

Solution #2

## Example – 2 (contd.)


**Q:** Two solutions! Which one do we use?

**A:** The one with the **shortest** lengths of transmission line!

**Q:** Oh, I see! Shorter transmission lines provide **smaller** and (slightly) cheaper matching networks.

**A:** True! But there is a more **fundamental** reason why we select the solution with the **shortest** lines—the matching **bandwidth** is **larger**!

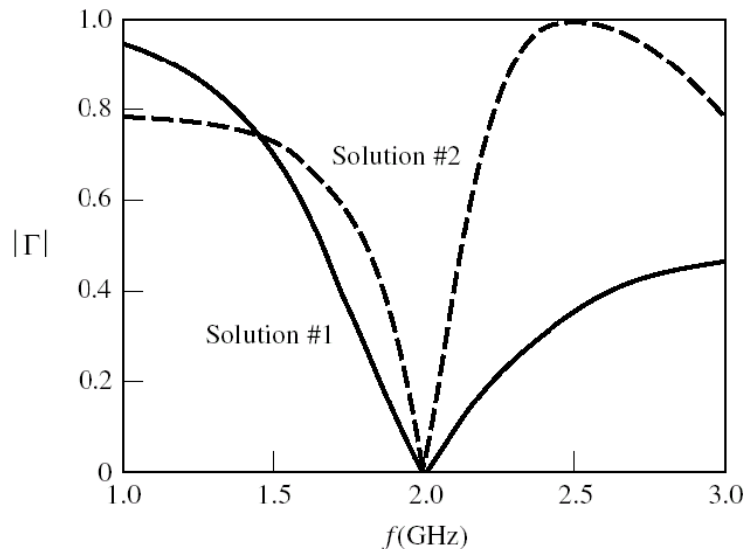
- For example, consider the **frequency response** of the two solutions:



Clearly, solution 1 provides a **wider** bandwidth!
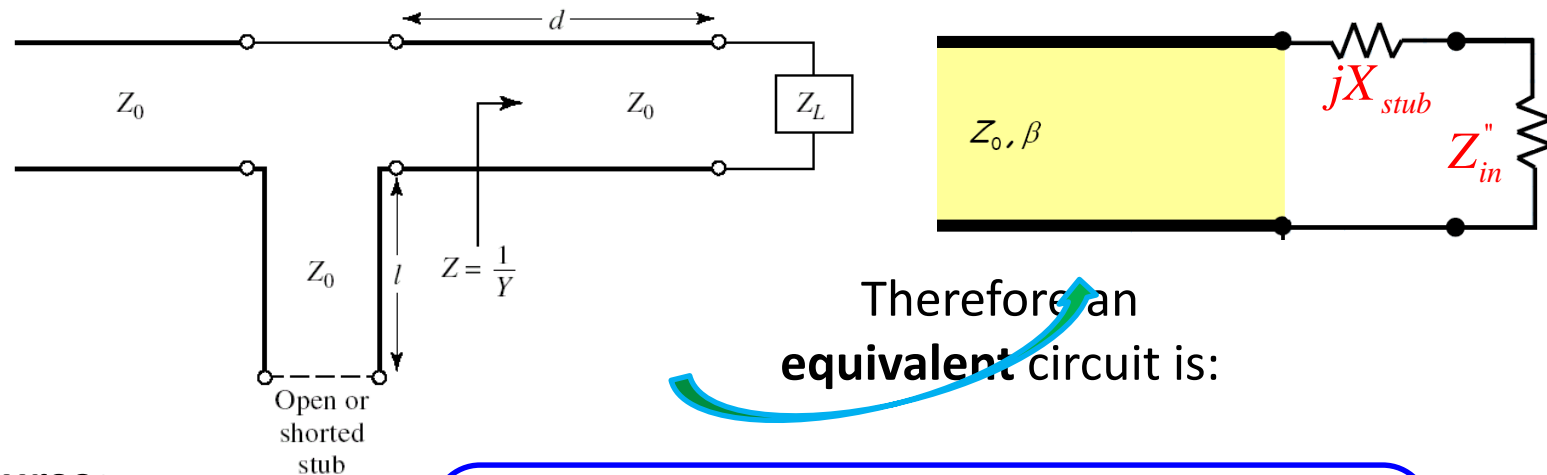
## Series-stub Matching Networks

- Consider the following transmission line structure, with a **series** stub:



Therefore an  
**equivalent** circuit is:

where of course:

$$Z_{in}'' = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right)$$

$$jX_{stub} = \begin{cases} -jZ_0 \cot(\beta l) & \text{For open-stub} \\ jZ_0 \tan(\beta l) & \text{For short-stub} \end{cases}$$

### Example – 3

Let us take the case where we want to match a load of  $Z_L = (100 + j80)\Omega$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .


**Example – 3 (contd.)**

$z_l$  to  $z_1$  towards generator (clockwise) gives length  $d_1$  (first solution)

$z_l$  to  $z_2$  towards generator (clockwise) gives length  $d_2$  (second solution)



Determine the respective impedances at the two intersection points and these are of the form  $1 + jx$  and  $1 - jx$

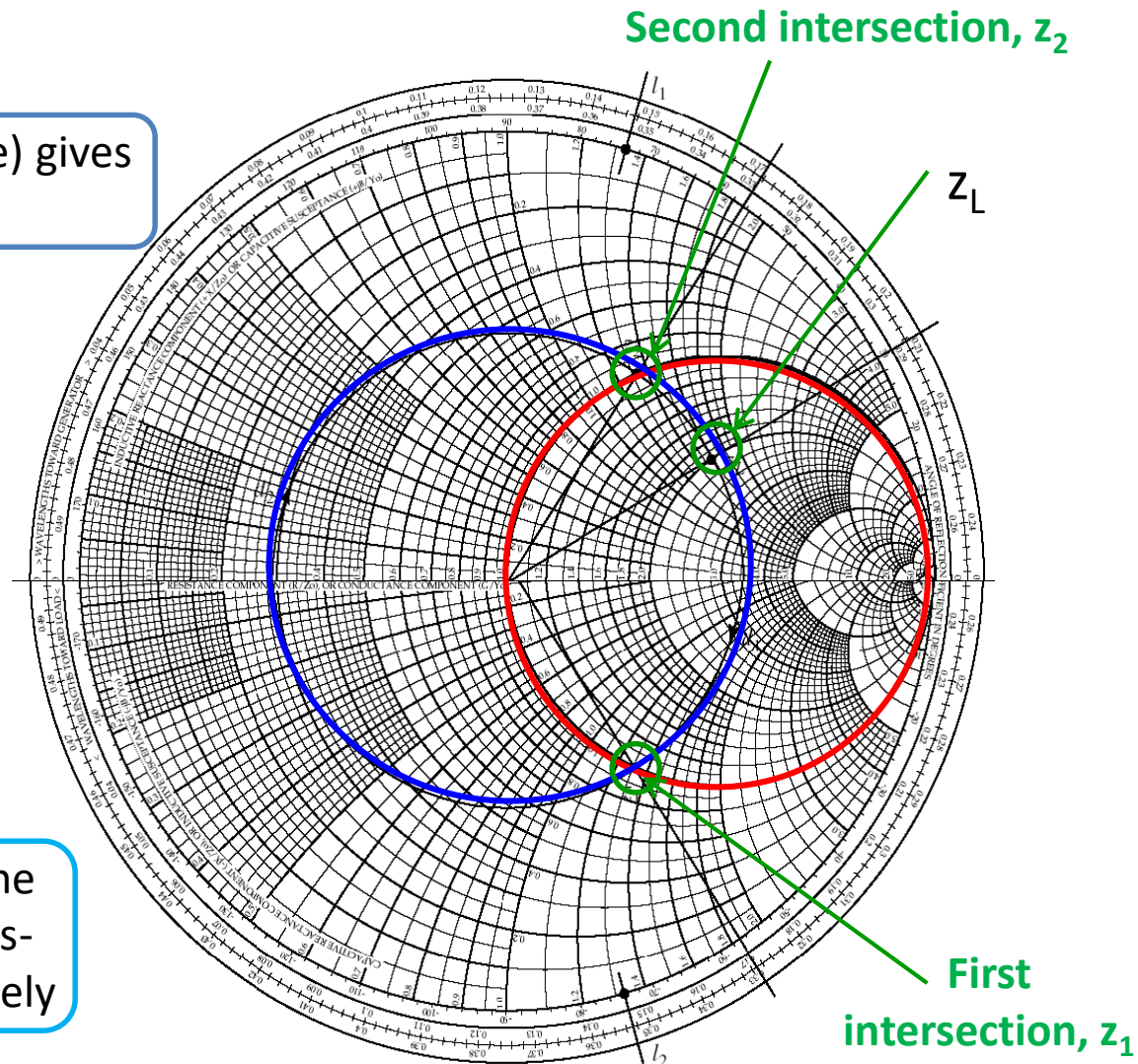Cancel these imaginary part of the impedances by introducing series-stubs of length  $l_1$  and  $l_2$  respectively





- $l_1$  and  $l_2$  are the lengths from open circuit point in the Smith chart (if open stub is used) along the  $r = 0$  circle until the achieved impedances are of opposite signs to those at the intersection points in the earlier step

## Example – 3 (contd.)

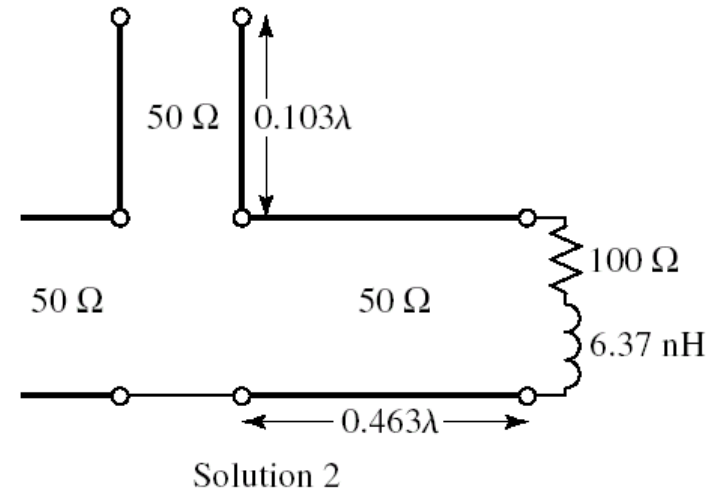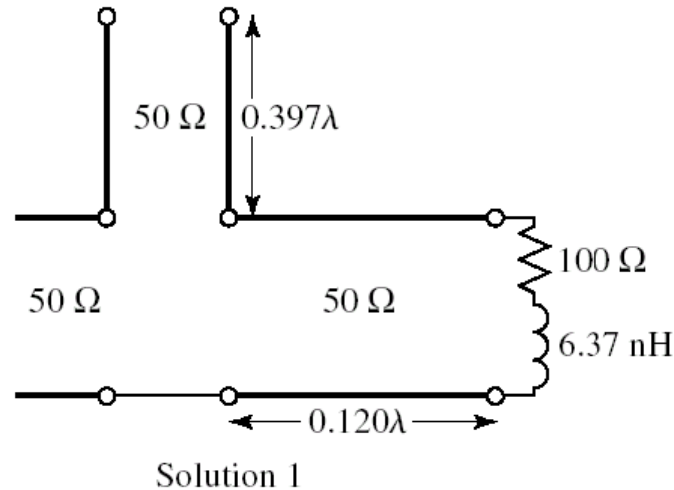

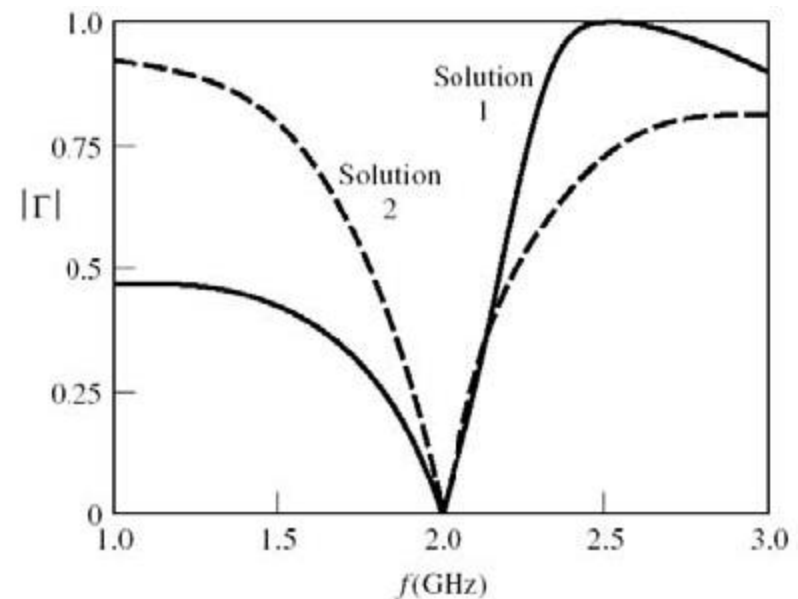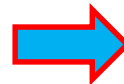Again, we should use the solution with the **shortest** transmission lines, although in **this** case that distinction is a bit **ambiguous**. As a result, the bandwidth of each design is about the same (depending on how **you** define **bandwidth!**).



## Example – 4

For a load impedance of  $Z_L = (60 - j45)\Omega$ , design single-stub (shunt) matching networks that transform the load to a  $Z_{in} = (75 + j90)\Omega$  input impedance. Assume both the stub and transmission line have a characteristic impedance of  $Z_0 = 75\Omega$

### Solution

- Normalize the  $Z_L$  and  $Z_{in}$  with  $75\Omega$
- Mark these normalized impedances on the Z-Smith chart
- Move to Y-Smith chart or better use ZY-Smith chart
- Plot constant conductance ( $g_L$ ) circle
- Plot SWR circle for normalized input impedance ( $z_{in}$ )
- Two intersection points between constant conductance circle and SWR circle can be observed
- Rotation from intersection points to  $z_{in}$  give the lengths  $d_1$  and  $d_2$  and corresponding changes in admittance
- Look for cancelling the additional admittances using shunt stub by equating corresponding stub lengths from 'open' in Smith chart


## Example – 4 (contd.)

Here:

$$z_L = 0.8 - j0.6$$

$y_{in}$  to A towards  
generator  
(clockwise) gives  
length  $d_1$  (first  
solution)

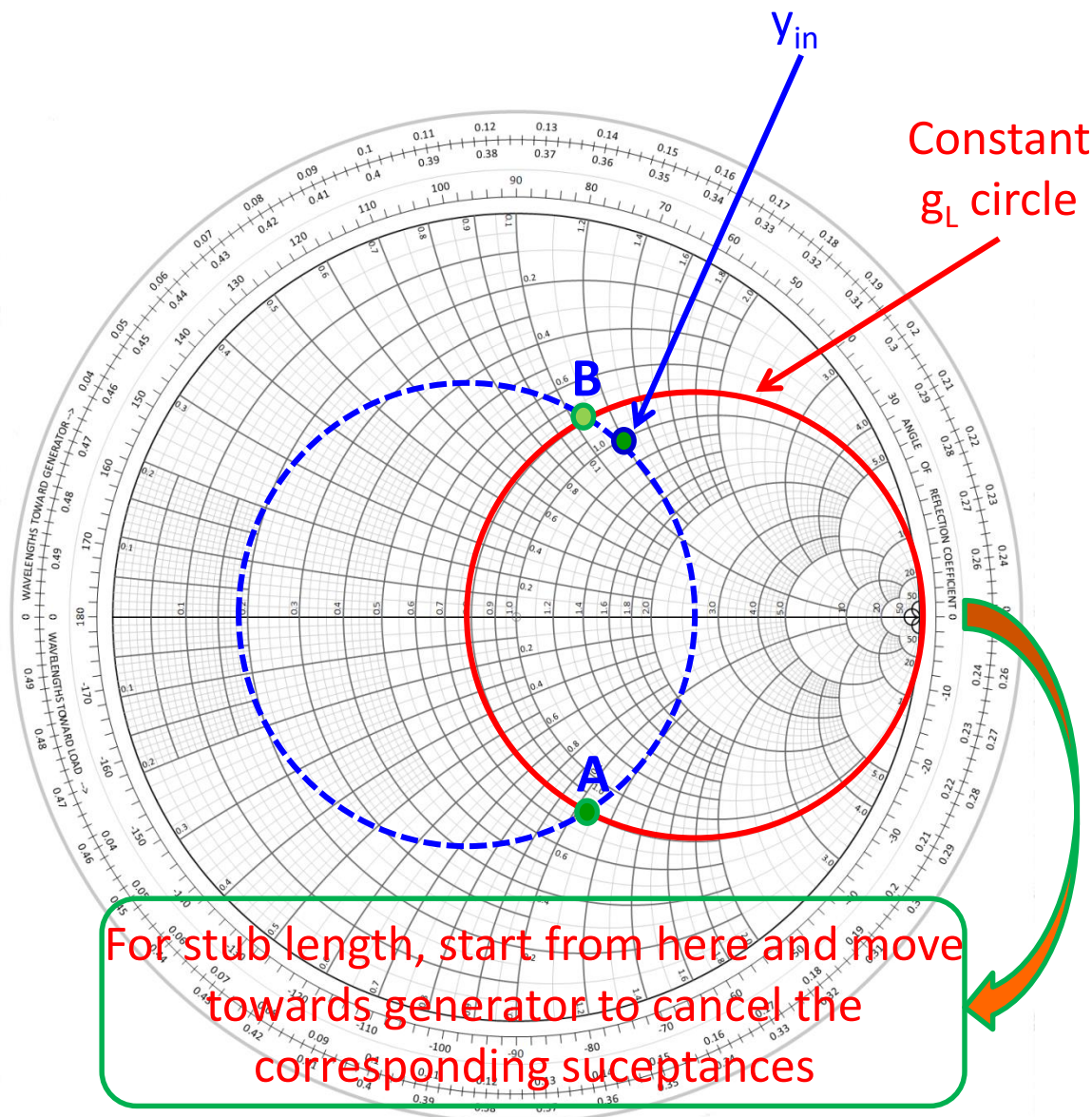
$y_{in}$  to B towards  
generator  
(clockwise) gives  
length  $d_2$  (second  
solution)




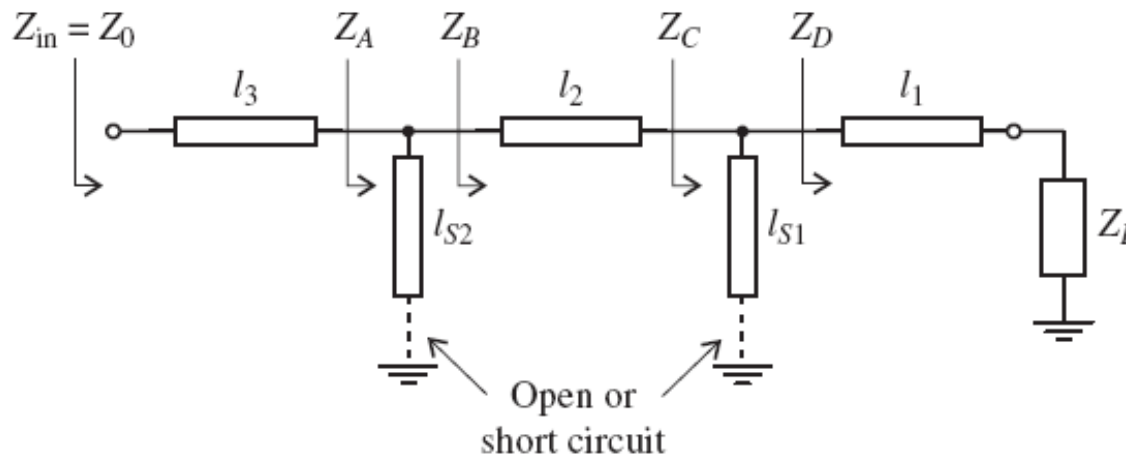
## Double-stub Matching Networks

- The single-stub matching networks are quite versatile → allows matching between any input and load impedances, so long as they have a non-zero real part.
- Main drawback is the requirement of variable length TL between the stub and the input port or the stub and the stub and the load impedance → many a times problematic when variable impedance tuner is needed.
- In a double-stub matching networks, **two short- or open-circuited stubs are connected in shunt with a fixed-length TL separating them** → the usual separation is  $\lambda/8$ ,  $3\lambda/8$  or  $5\lambda/8$ .



Self Study