

## **Lecture – 13**

**Date: 13.02.2017**


- Quarter Wave Impedance Transformer
- Multiple Reflection Viewpoints
- Theory of Small Reflections

## The Quarter Wave Transformer

- By now you must have noticed that a **quarter-wave length** of transmission line ( $l = \lambda/4$ ,  $2\beta l = \pi$ ) appears **often** in RF/microwave engineering problems.
- Another application of the  $l = \lambda/4$  transmission line is as an **impedance matching network**.

**Q:** Why does the quarter-wave matching network work — after all, the quarter-wave line is **mismatched** at both ends?

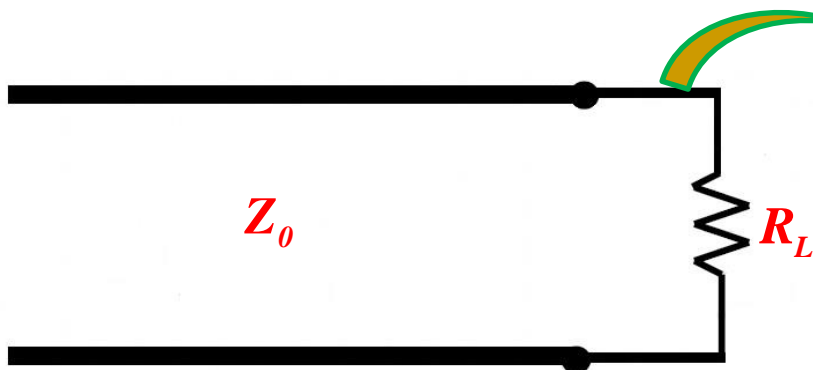
- Let us consider a TL (with characteristic impedance  $Z_0$ ) where the end is terminated with a **resistive** (i.e., real) load:



Unless  $R_L = Z_0$ , the resistor is **mismatched** to the line, and thus some of the incident power will be **reflected**.

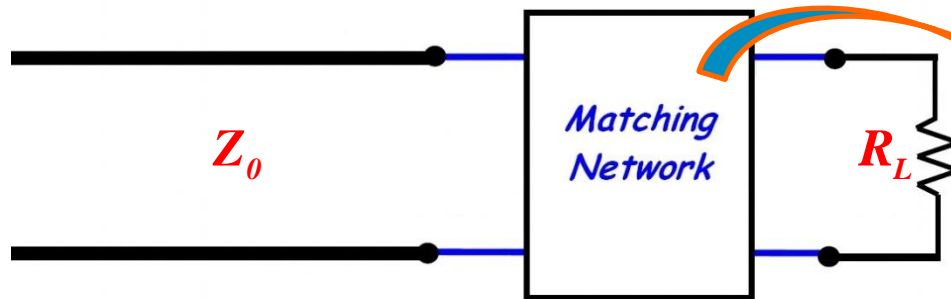
## The Quarter Wave Transformer (contd.)

- We can correct this situation by placing a matching network between the line and the load:



In addition to the designs we have just studied (e.g., L-networks, stub tuners), one of the simplest matching network designs is the **quarter-wave transformer**.

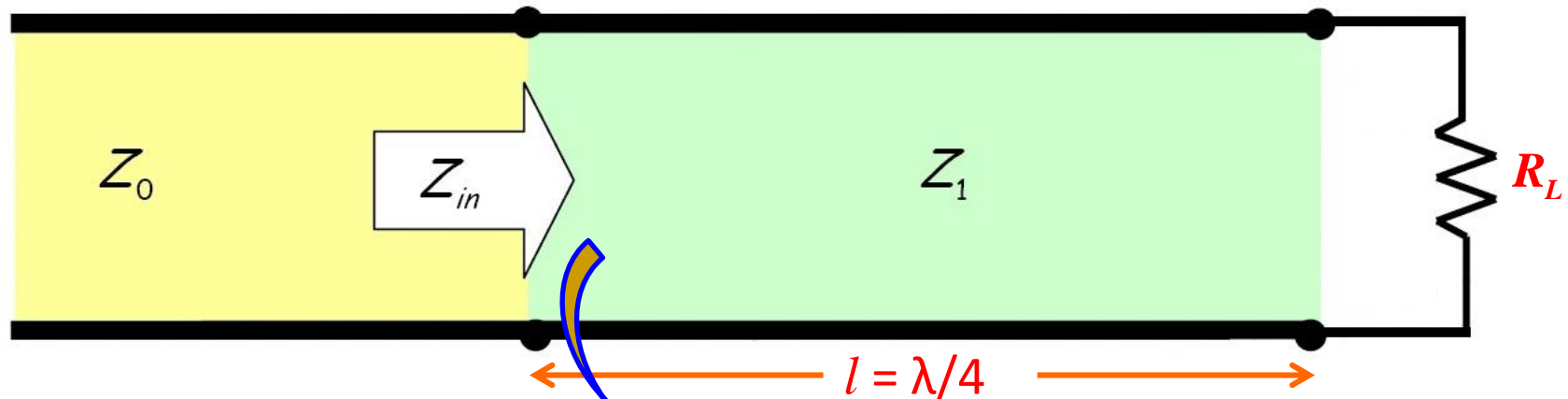- The quarter-wave transformer is simply a transmission line with characteristic impedance  $Z_1$  and length  $l = \lambda/4$  (i.e., a quarter-wave line).



This  $\lambda/4$  line is the **matching network**!

**Q:** But what about the characteristic impedance  $Z_1$ ; what **should** its value be??

## The Quarter Wave Transformer (contd.)

**A:** Remember, the  $\lambda/4$  case is one of the **special** cases that we studied. In such a situation the **input** impedance of the line is:

$$Z_{in} = \frac{(Z_1)^2}{Z_L} = \frac{(Z_1)^2}{R_L}$$

- Thus, if we wish for  $Z_{in}$  to be numerically equal to  $Z_0$ , we find:


$$Z_{in} = \frac{(Z_1)^2}{R_L} = Z_0$$

- we find the **required** value of  $Z_1$  be:

$$Z_1 = \sqrt{Z_0 R_L}$$

In other words, the characteristic impedance of the quarter wave line is the **geometric average** of  $Z_0$  and  $R_L$ !

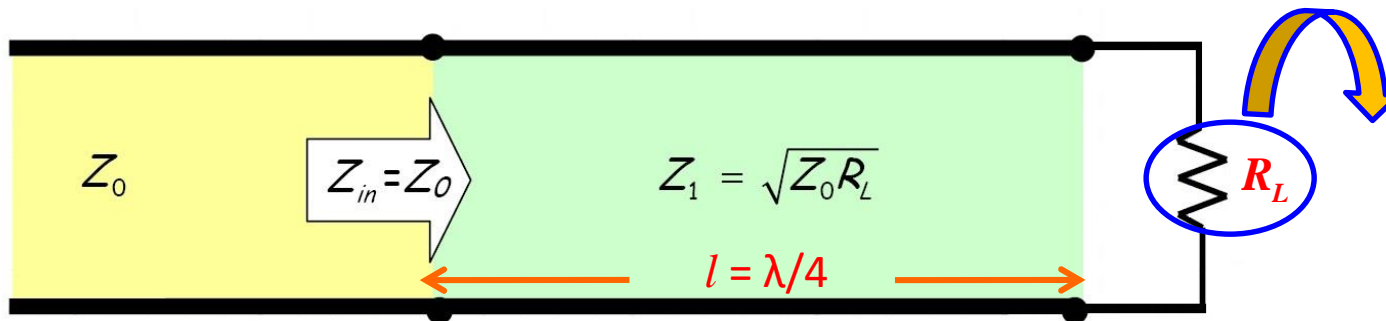Therefore, a  $\lambda/4$  line with characteristic impedance  $Z_1 = \sqrt{Z_0 R_L}$  will **match** a transmission line with characteristic impedance  $Z_0$  **to** a resistive load  $R_L$



This ensures that **all power** is delivered to load  $R_L$ !

Alas, the quarter-wave transformer (like all our designs) have a few problems!

## The Quarter Wave Transformer (contd.)

### Problem #1

- The matching **bandwidth** is **narrow** !
- In other words, we obtain a **perfect** match at precisely the frequency where the length of the matching transmission line is a **quarter**-wavelength.

remember, this length can be a quarter-wavelength at just **one** frequency!

- **Wavelength** is related to **frequency** as:

$$\lambda = \frac{v_p}{f} = \frac{1}{f\sqrt{LC}}$$



$v_p$  is propagation  
velocity of wave


- For **example**, assuming that  $v_p = c$  (the speed of light in vacuum), one wavelength at 1 GHz is 30 cm ( $\lambda = 0.3\text{m}$ ), while one wavelength at 3 GHz is 10 cm ( $\lambda = 0.1\text{m}$ ). As a result, a TL length  $l = 7.5\text{cm}$  is a quarter wavelength for a signal at 1GHz **only**.

**Thus, a quarter-wave transformer provides a perfect match ( $\Gamma_{in} = 0$ ) at one and only one signal frequency!**

In other words, as the signal frequency (i.e., wavelength) changes, the **electrical** length of the matching TL segment changes. It will **no longer** be a **quarter** wavelength, and thus we **no longer** will have a **perfect** match
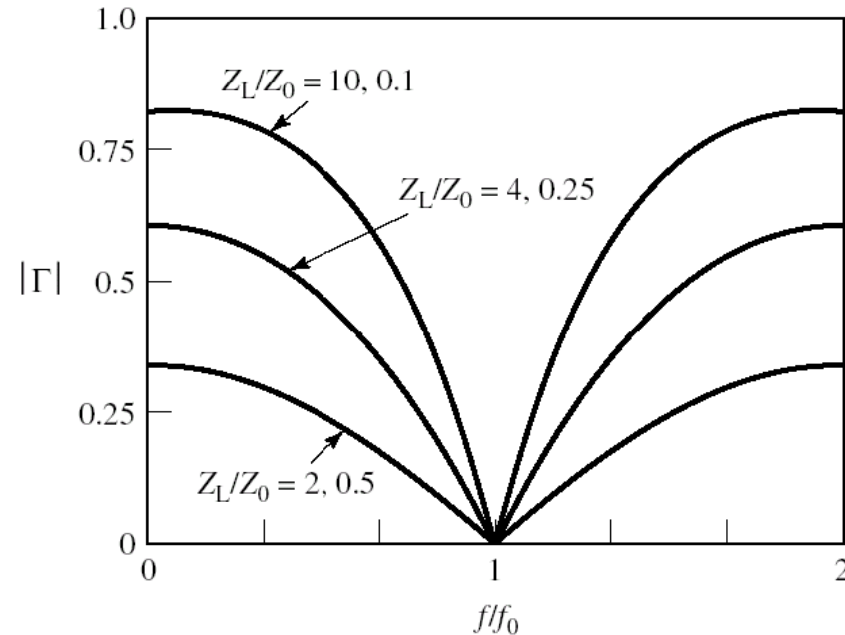
## The Quarter Wave Transformer (contd.)

It can be observed that the **closer**  $R_L$  (or  $R_{in}$ ) is to characteristic impedance  $Z_0$ , the **wider** the bandwidth of the quarter wavelength transformer



In principle, the bandwidth can be **increased** by adding **multiple**  $\lambda/4$  sections!

### Problem #2


Recall the matching solution was limited to loads that were **purely real!** i.e.:

$$Z_L = R_L + j0$$

Obviously, this is a BIG problem, as most loads will have a **reactive** component!
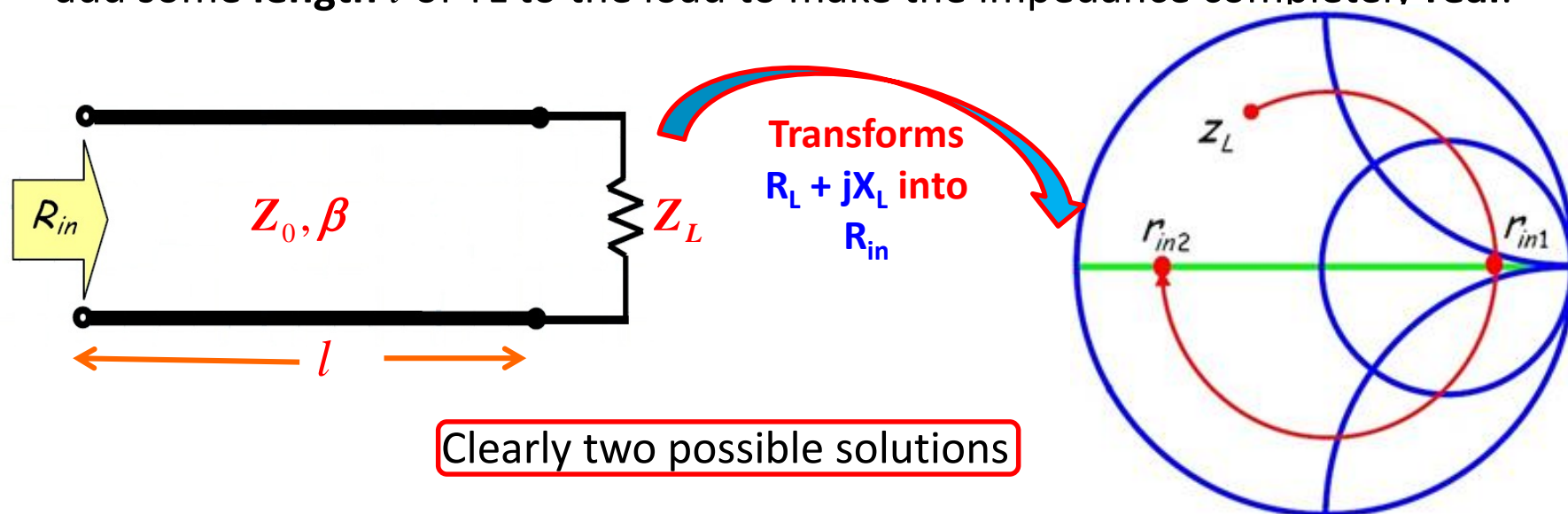
## The Quarter Wave Transformer (contd.)


- Fortunately, we have a relatively easy **solution** to this problem, as we can always add some **length**  $l$  of TL to the load to make the impedance completely **real**:



However, it should be understood that the input impedance will be purely real at only **one** frequency!


Once the output impedance has been converted to purely real, one can then build a quarter-wave transformer to **match** the line  $Z_0$  to resistance  $R_{in}$

## The Quarter Wave Transformer (contd.)

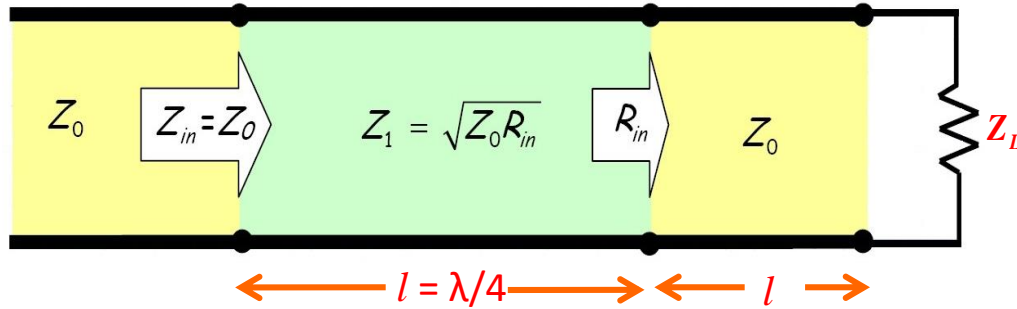

Again, since the transmission lines are lossless, **all** of the incident power is delivered to the **load**  $Z_L$ .

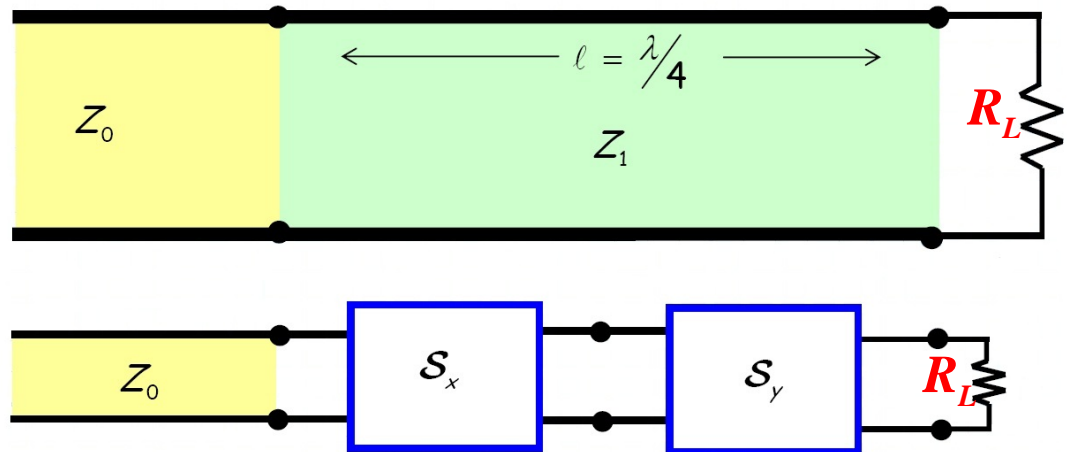- A quarter wave transformer can be thought of as a cascaded series of **two** two-port devices, terminated with a load  $R_L$ :




**Q:** **Two** two-port devices? It appears to me that a quarter-wave transformer is **not** that complex. What **are** the **two** two-port devices?

**A:** The **first** is a “**connector**”. Note a connector is the interface between one transmission line (characteristic impedance  $Z_0$ ) to a second transmission line (characteristic impedance  $Z_1$ ).



## The Quarter Wave Transformer (contd.)

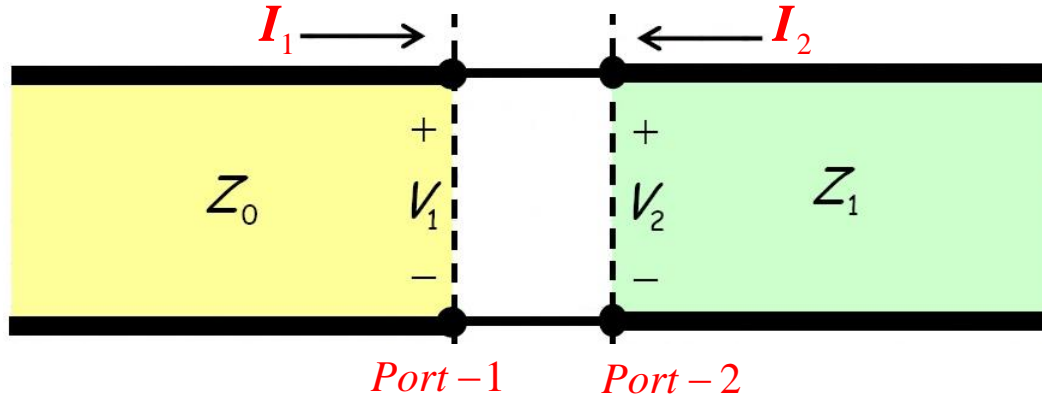


- we **earlier** determined the scattering matrix of this two-port device as:


$$S_x = \begin{bmatrix} \frac{Z_1 - Z_0}{Z_1 + Z_0} & \frac{2\sqrt{Z_0 Z_1}}{Z_1 + Z_0} \\ \frac{2\sqrt{Z_0 Z_1}}{Z_1 + Z_0} & \frac{Z_0 - Z_1}{Z_1 + Z_0} \end{bmatrix}$$

$$S_x = \begin{bmatrix} \Gamma & T \\ T & -\Gamma \end{bmatrix} \xrightarrow{\text{Compact Form}}$$

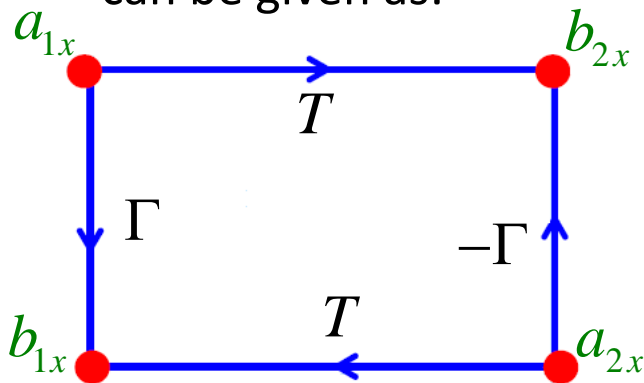- Therefore signal flow graph of the connector can be given as:



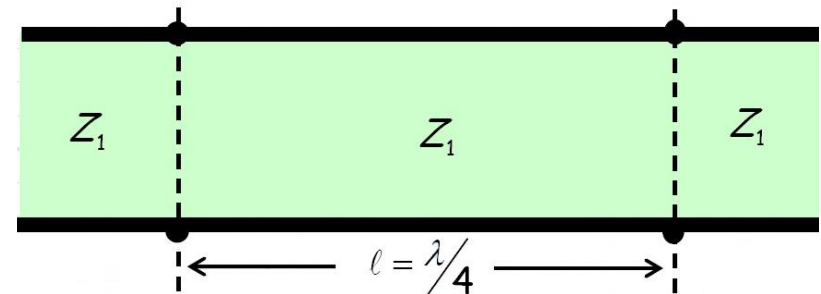
- Now, the **second** two-port device is a quarter wavelength of TL:


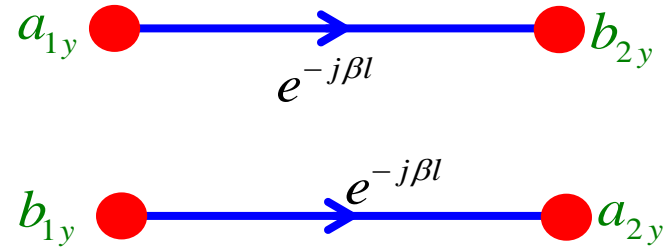
## The Quarter Wave Transformer (contd.)

- The second device has the scattering matrix and SFG as:


$$S_y = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$




- Finally, a **load** has a “scattering matrix” and SFG as:


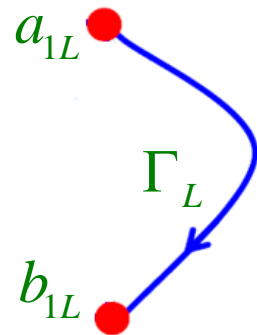
$$S = \left[ \frac{R_L - Z_1}{R_L + Z_1} \right] = \Gamma_L$$



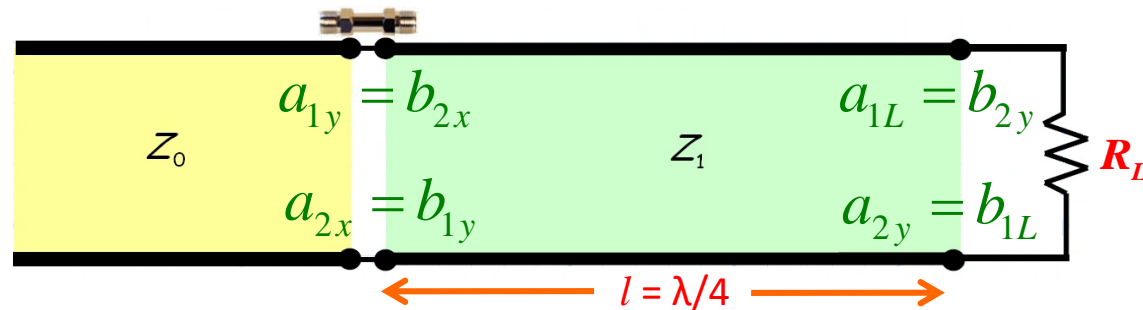- if we connect the ideal connector to a  $\lambda/4$  of transmission line, and terminate the whole thing with load  $R_L$ , we have formed a  **$\lambda/4$  matching network!**




- The boundary conditions associated with these connections are likewise:


$$a_{1y} = b_{2x} \quad a_{2x} = b_{1y} \quad a_{1L} = b_{2y} \quad a_{2y} = b_{1L}$$
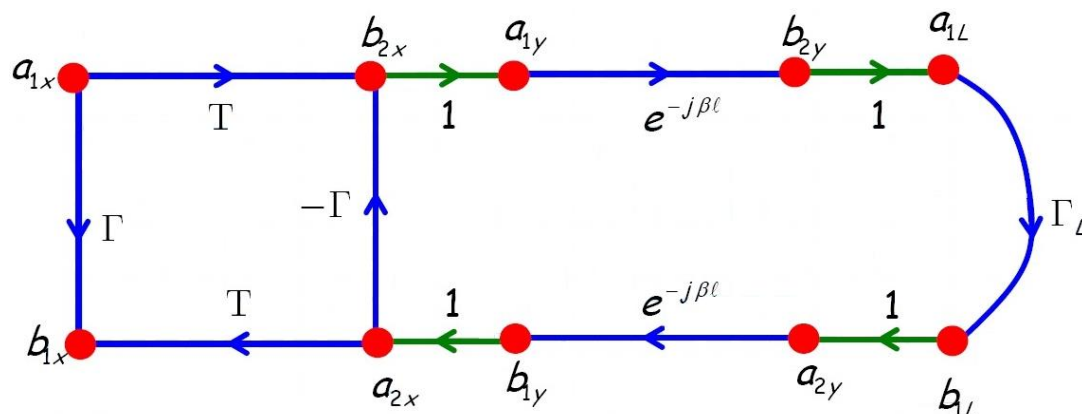
## The Quarter Wave Transformer (contd.)


- Therefore, we can put the signal-flow graph pieces together to form the **signal-flow graph** of the quarter wave network:




- Simplification gives:**

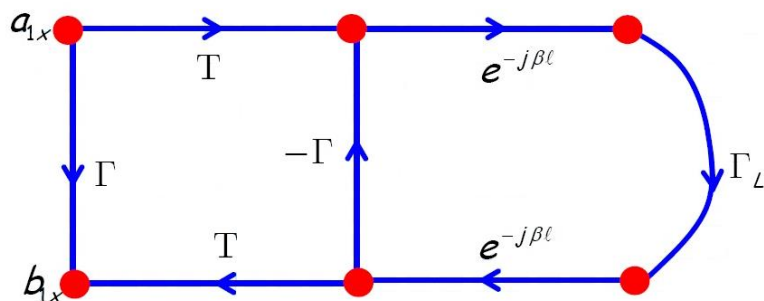

Simplification:

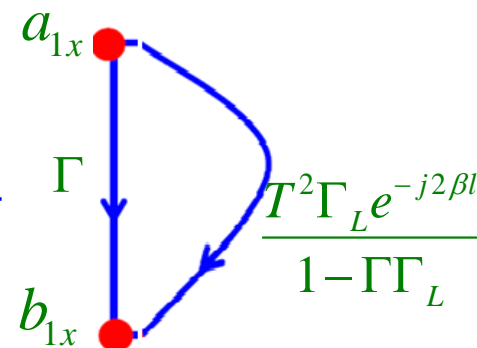

**Final  
Simplification**

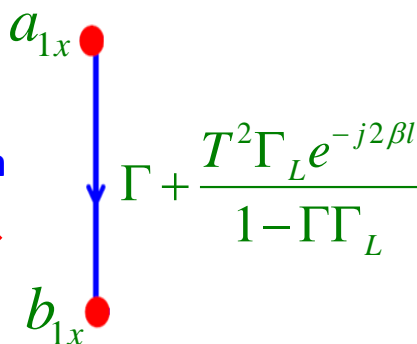

## The Quarter Wave Transformer (contd.)

Therefore:

$$\Gamma_{in} \doteq \frac{b_{1x}}{a_{1x}} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta l}}{1 - \Gamma \Gamma_L}$$

**Q:** Hey wait! If the quarter-wave transformer is a **matching network**, shouldn't  $\Gamma_{in} = 0$ ??

**A:** Who says it isn't! Consider now **three important facts**.

- For a **quarter wave transformer**, we set  $Z_1$  such that:

$$Z_1^2 = Z_0 R_L \quad \Rightarrow \quad Z_0 = \frac{Z_1^2}{R_L}$$

- Inserting** this into the scattering parameter  $S_{11}$  of the connector, we find:

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{Z_1 - Z_1^2 / R_L}{Z_1 + Z_1^2 / R_L} = \frac{R_L - Z_1}{R_L + Z_1}$$

- For the quarter-wave transformer, the **connector**  $S_{11}$  value (i.e.,  $\Gamma$ ) is the **same** as the **load** reflection coefficient  $\Gamma_L$ :

$$\Gamma = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L$$

 **Fact 1**

- Since the connector is **lossless** (unitary scattering matrix!), we can conclude (and likewise show) that:

$$1 = |S_{11}|^2 + |S_{21}|^2 = |\Gamma|^2 + |T|^2$$

## The Quarter Wave Transformer (contd.)

- Since  $Z_0$ ,  $Z_1$ , and  $R_L$  are all real, the values  $\Gamma$  and  $T$  are also **real valued**. As a result,  $|\Gamma|^2 = \Gamma^2$  and  $|T|^2 = T^2$ , and we can likewise conclude:

$$|\Gamma|^2 + |T|^2 = \Gamma^2 + T^2 = 1 \quad \leftarrow \text{Fact 2}$$

- Likewise, the  $Z_1$  transmission line has  $l = \lambda/4$ , so that:

$$2\beta l = 2\left(\frac{2\pi}{\lambda}\right)\frac{\lambda}{4} = \pi \quad \Rightarrow \quad e^{-j\beta l} = e^{-j\pi} = -1 \quad \leftarrow \text{Fact 3}$$

- As a result:

$$\Gamma_{in} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta l}}{1 - \Gamma \Gamma_L} = \Gamma - \frac{T^2 \Gamma_L}{1 - \Gamma \Gamma_L}$$

- And using the **newly discovered** fact that (for a correctly designed transformer)  $\Gamma_L = \Gamma$ :

$$\Gamma_{in} = \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2}$$


- We also have a **recent** discovery that says  $T^2 = 1 - \Gamma^2$ , therefore:

$$\Gamma_{in} = \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2} = \Gamma - \frac{T^2 \Gamma}{T^2} = 0$$

**A perfect match!** The quarter-wave transformer does indeed work!
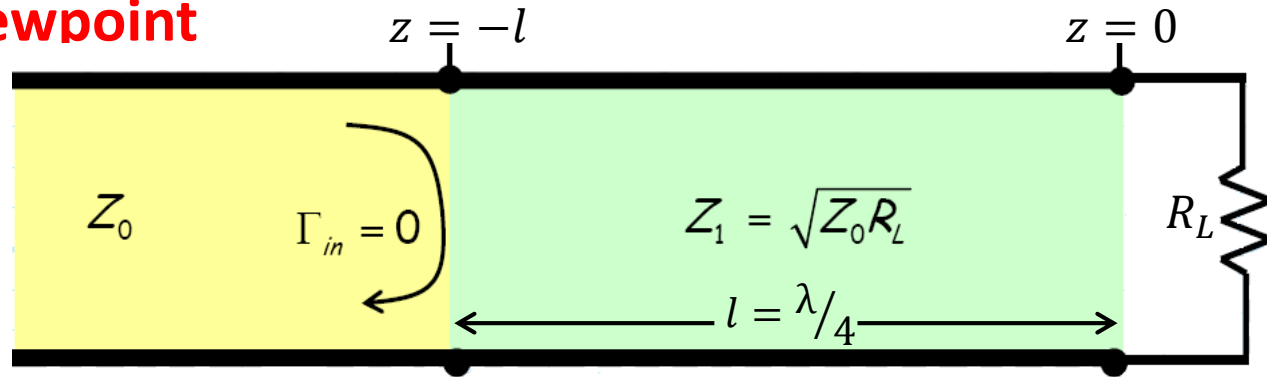
## Multiple Reflection Viewpoint


- The  $\lambda/4$  - transformer brings up an interesting question in  $\mu$ -wave engineering.



**Q: Why** is there **no** reflection at  $z = -l$ ? It appears that the line is **mismatched** at both  $z = 0$  and  $z = -l$ .

**A:** there **are** reflections at the mismatched interfaces—an **infinite** number of them!

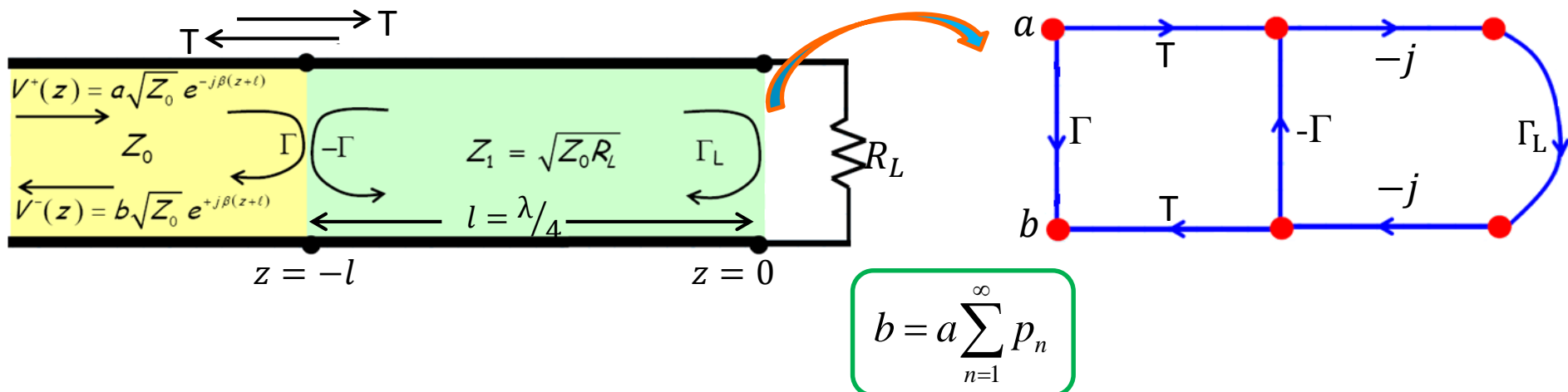
We can use **signal flow graph** to determine the propagation series, once we determine all the **propagation paths** through the quarter-wave transformer.


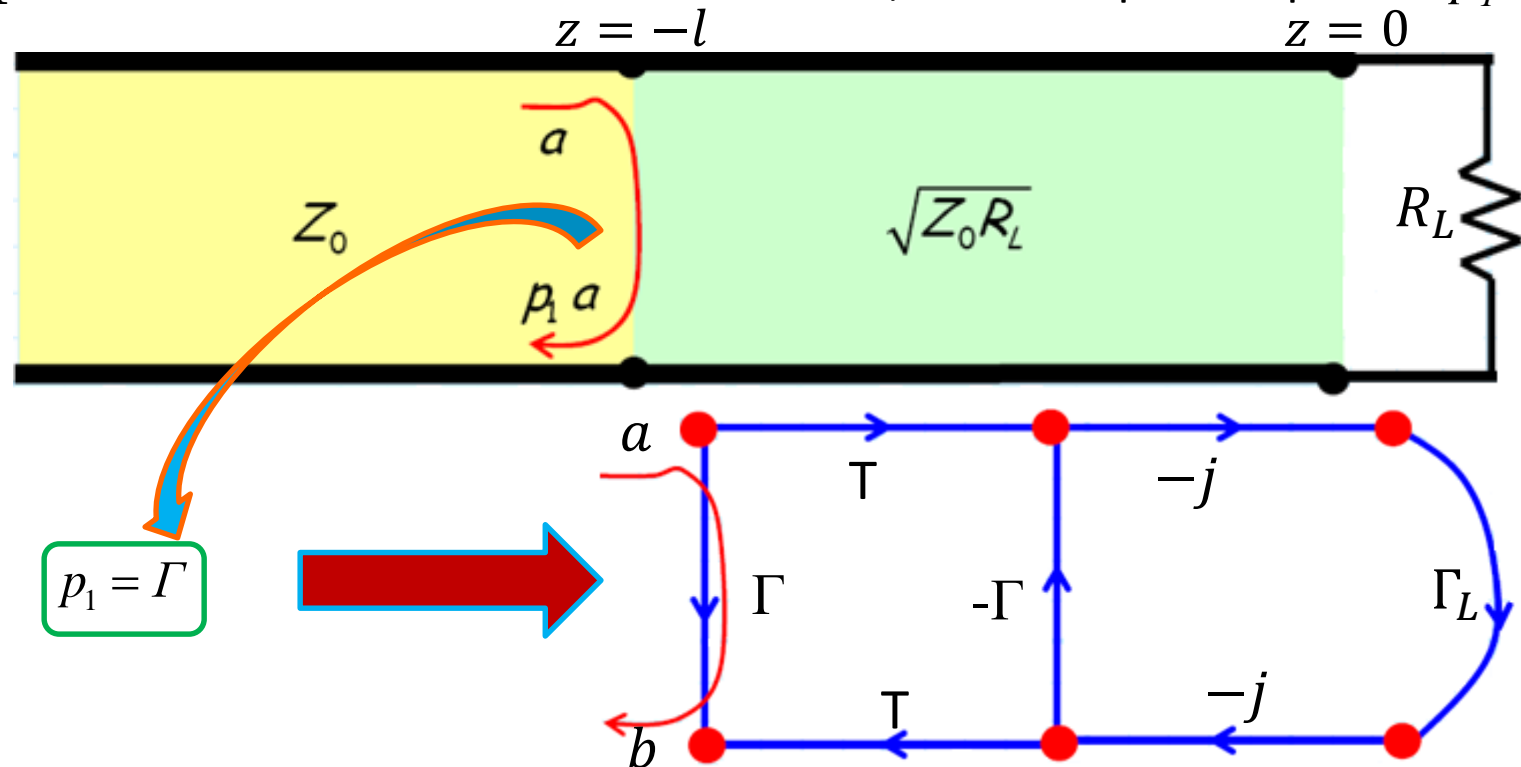
## Multiple Reflection Viewpoint (contd.)


- Now, let's try to interpret what **physically** happens when the **incident** voltage wave reaches the interface at  $z = -l$ .
- We find that there are **two forward paths** through the quarter-wave transformer signal flow graph.

**Path 1.** At  $z = -l$ , the characteristic impedance of the transmission line changes from  $Z_0$  to  $Z_1$ . This mismatch creates a **reflected** wave, with complex amplitude  $p_1 a$ :


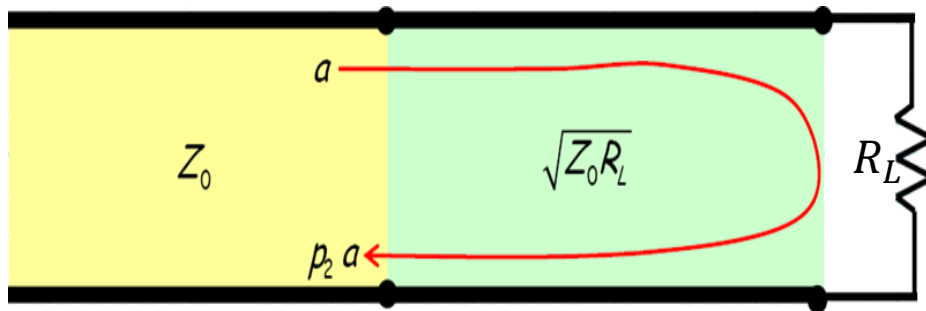
## Multiple Reflection Viewpoint (contd.)

**Path 2.** However, a **portion** of the incident wave is transmitted ( $T$ ) across the interface at  $z = -l$ , this wave travels a distance of  $\beta l = 90^\circ$  to the load at  $z = 0$ , where a portion of it is reflected ( $\Gamma_L$ ). This wave travels back  $\beta l = 90^\circ$  to the interface at  $z = -l$ , where a portion is again transmitted ( $T$ ) across into the  $Z_0$  transmission line—**another** reflected wave !




- So the **second direct path** is:

$$p_2 = T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T = -T^2 \Gamma_L$$

note that traveling  $2\beta l = 180^\circ$  has produced a **minus** sign in the result.



$$b = p_2 a$$

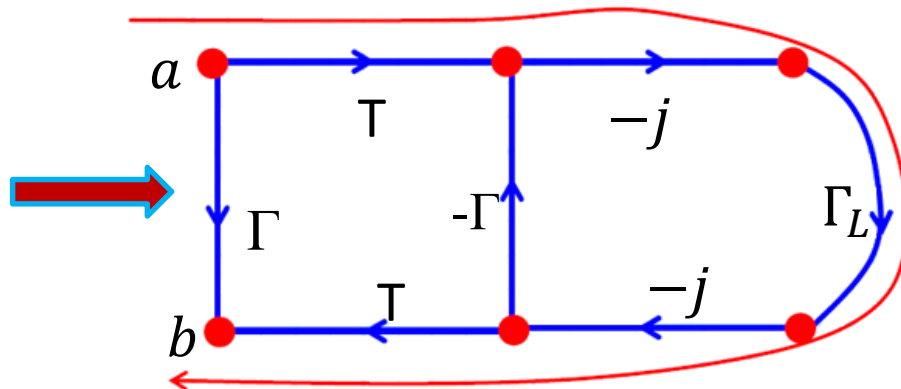


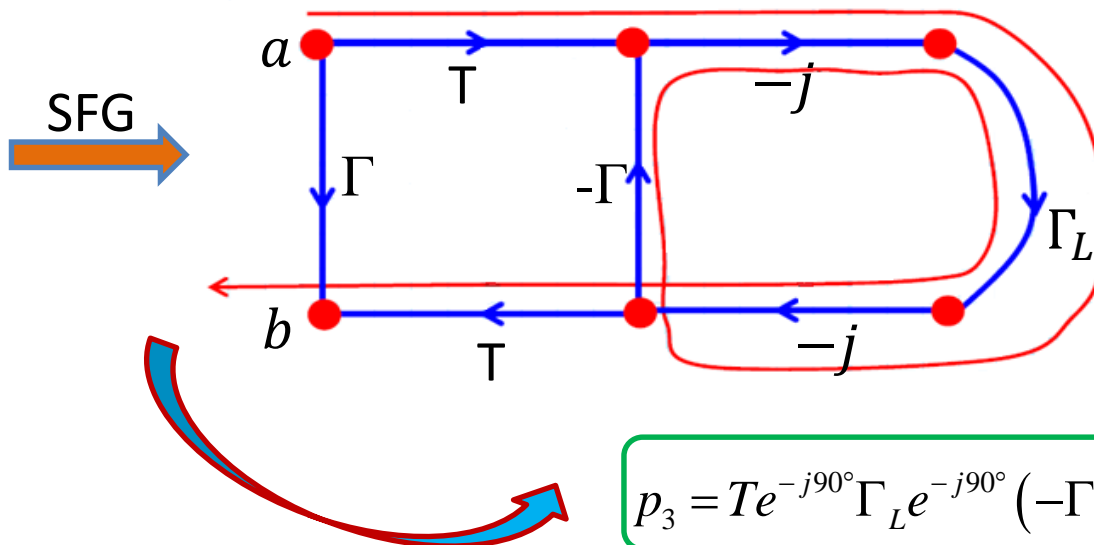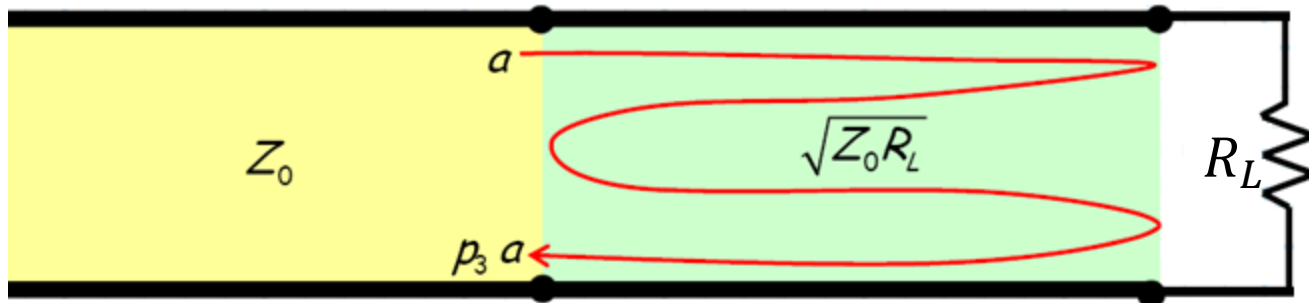
## Multiple Reflection Viewpoint (contd.)

**Path 3.** However, a **portion** of this **second** wave is also **reflected** ( $\Gamma$ ) back into the  $Z_1$  transmission line at  $z = -l$ , where it again travels by  $\beta l = 90^\circ$  to the load, is partially reflected ( $\Gamma_L$ ), travels  $\beta l = 90^\circ$  back to  $z = -l$ , and is partially transmitted into  $Z_0(T)$ —our **third** reflected wave!



Note that path 3 is  
**not** a direct path!

$$p_3 = T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} (-\Gamma) e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T = -T^2 (\Gamma_L)^2 \Gamma$$

## Multiple Reflection Viewpoint (contd.)

**Path n.** We can see that this “bouncing” back and forth can go on **forever**, with each trip launching a **new** reflected wave into the  $Z_0$  transmission line.

Note however, that the **power** associated with each successive reflected wave is **smaller** than the previous, and so eventually, the power associated with the reflected waves will **diminish** to insignificance!

**Q:** But, why then is  $\Gamma = 0$  ?

**A:** Each reflected wave is a **coherent** wave. That is, they all oscillate at same frequency  $\omega$ ; the reflected waves differ only in terms of their **magnitude** and **phase**.

- Therefore, to determine the **total** reflected wave, we must perform a **coherent summation** of each reflected wave—this summation results in our **propagation series**, a series that must converge for passive devices.

$$b = a \sum_{n=1}^{\infty} p_n$$

- It can be shown that the infinite propagation series for **this** quarter-wavelength structure **converges** to the closed-form expression:

$$\frac{b}{a} = \sum_{n=1}^{\infty} p_n = \frac{\Gamma - \Gamma^2 \Gamma_L - T^2 \Gamma_L}{1 - \Gamma^2}$$

- Thus, the **input** reflection coefficient is:

$$\Gamma_{in} = \frac{b}{a} = \frac{\Gamma - \Gamma^2 \Gamma_L - T^2 \Gamma_L}{1 - \Gamma^2}$$

## Multiple Reflection Viewpoint (contd.)

- Using our definitions, it can be shown that the **numerator** of this expression is:

$$\Gamma - \Gamma^2 \Gamma_L - T^2 \Gamma_L = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)}$$

- It is evident that the numerator (and therefore  $\Gamma_{in}$ ) will be **zero** if:

$$Z_1^2 - Z_0 R_L = 0$$



$$Z_1 = \sqrt{Z_0 R_L}$$



**Just** as we  
expected!


Physically, this result ensures that all the reflected waves add coherently together to produce a **zero value**!

Note **all** of our transmission line analysis has been **steady-state** analysis. We assume our signals are **sinusoidal**, of the form  $\exp(j\omega t)$ . This signal exists for **all time**  $t$ —the signal is assumed to have been “on” **forever**, and assumed to continue “on” forever.

In other words, in steady-state analysis, **all** the multiple reflections have long since occurred, and thus have reached a steady state—the reflected wave is **zero**!
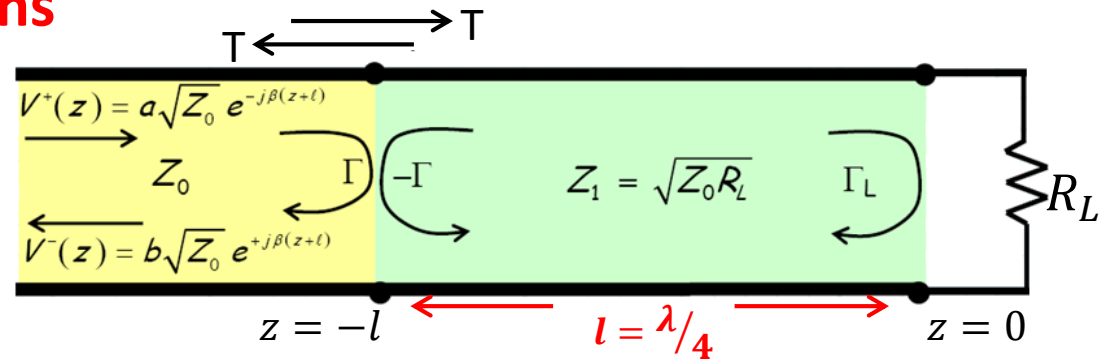
## The Theory of Small Reflections

- Recall that we analysed a **quarter-wave** transformer using the multiple reflection view point.




- We found that the solution could be written as an **infinite** summation of terms (the **propagation series**):

$$b = a \sum_{n=1}^{\infty} p_n$$

where each term had a specific **physical** interpretation, in terms of reflections, transmissions, and propagations.

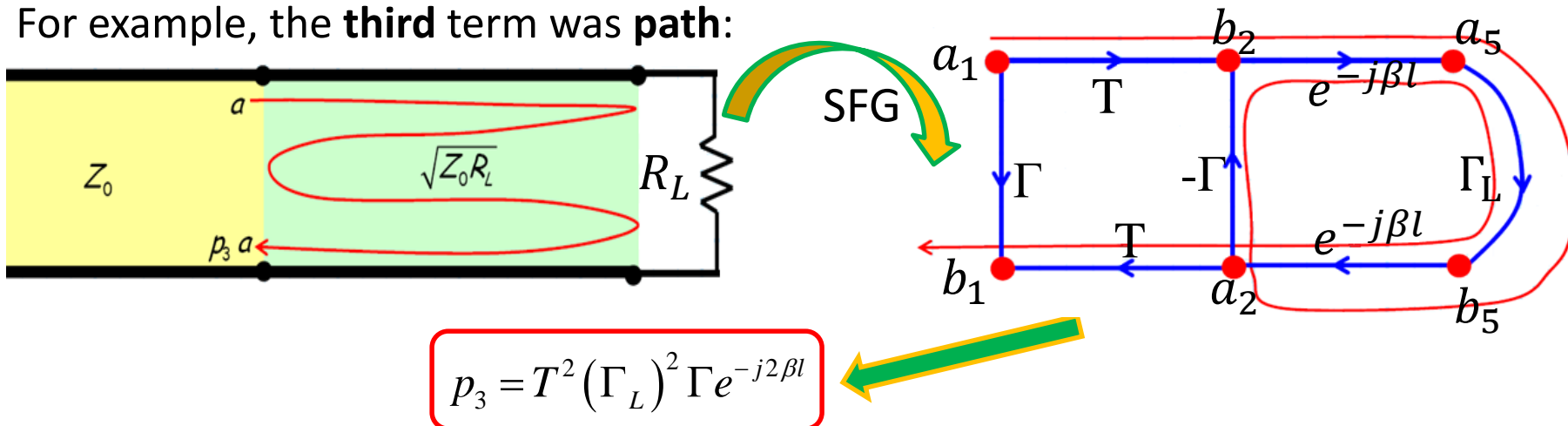- For example, the **third** term was **path**:



$$p_3 = T^2 (\Gamma_L)^2 \Gamma e^{-j2\beta l}$$



## The Theory of Small Reflections (contd.)

- Now let's consider the **magnitude** of this path:  $|p_3| = |T|^2 |\Gamma_L|^2 |\Gamma| |e^{-j2\beta l}| \Rightarrow |p_3| = |T|^2 |\Gamma_L|^2 |\Gamma|$
- Recall that  $\Gamma = \Gamma_L$  for a **properly designed** quarter-wave transformer:  $\Gamma = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L \Rightarrow |p_3| = |T|^2 |\Gamma_L|^3$
- For the case where values  $R_L$  and  $Z_1$  are numerically **"close"**,  $|R_L - Z_1| \ll |R_L + Z_1|$ , the magnitude of the reflection coefficient will be **very** small:  $|\Gamma_L| = \left| \frac{R_L - Z_1}{R_L + Z_1} \right| \ll 1.0$
- As a result, the value  $|\Gamma_L|^3$  will be **very, very, very** small.
- Moreover, we know (since the connector is **lossless**) that:  $|\Gamma|^2 + |T|^2 = |\Gamma_L|^2 + |T|^2 = 1$
- We can thus conclude that the **magnitude** of path  $p_3$  is likewise **very, very, very** small:  $|p_3| = |T|^2 |\Gamma_L|^3 \approx |\Gamma_L|^3 \ll 1$

This is a **classic case** where we can approximate the propagation series using only the **forward paths!!**
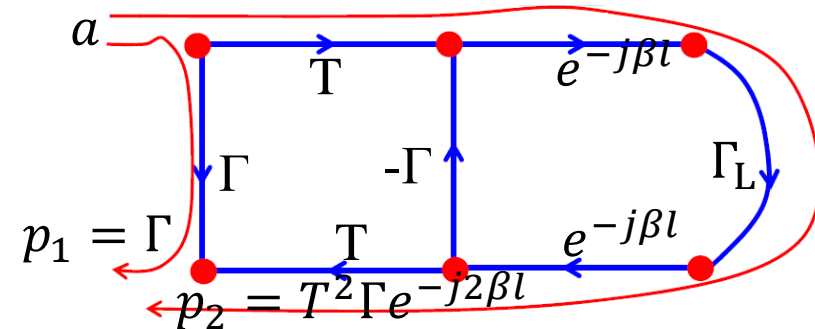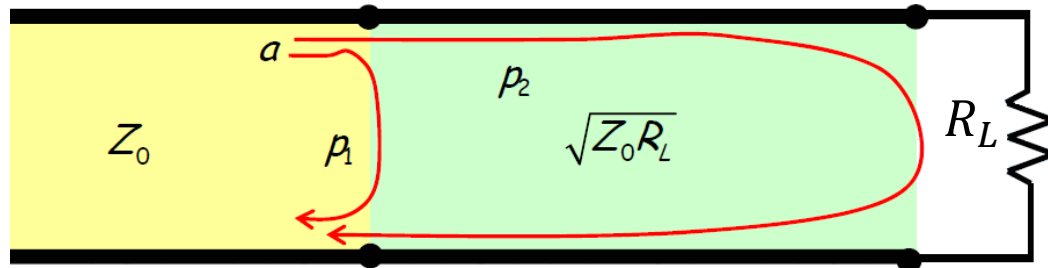
## The Theory of Small Reflections (contd.)

- Recall there are **two** forward paths:



- Therefore if  $Z_0$  and  $R_L$  are very **close** in value, the **approx** reflected wave using only the **direct paths** of the infinite series can be found from the SFG:
- Now, if we likewise apply the **approximation** that  $|T| \cong 1.0$ , we conclude for this quarter wave transformer (at the design frequency):

$$b \simeq (p_1 + p_2)a = (\Gamma + T^2 \Gamma_L e^{j2\beta l})a$$

$$b \simeq (p_1 + p_2)a = (\Gamma + \Gamma_L e^{j2\beta l})a$$


This **approximation**, where we:

1. use only the **direct paths** to calculate the propagation series,
2. approximate the **transmission** coefficients as **one** (i.e.,  $|T| = 1.0$ ).



is known as the **Theory of Small Reflections**, and allows us to use the propagation series as an **analysis** tool (we don't have to consider an **infinite** number of terms!).
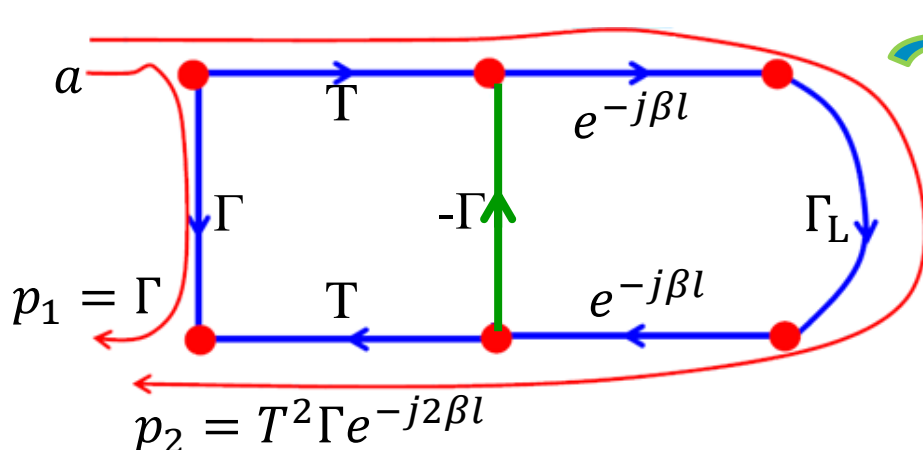
## The Theory of Small Reflections (contd.)

- Consider again the quarter-wave matching network SFG. Note there is **one branch** ( $-\Gamma = S_{22}$  of the connector), that is **not included** in either **direct path**.



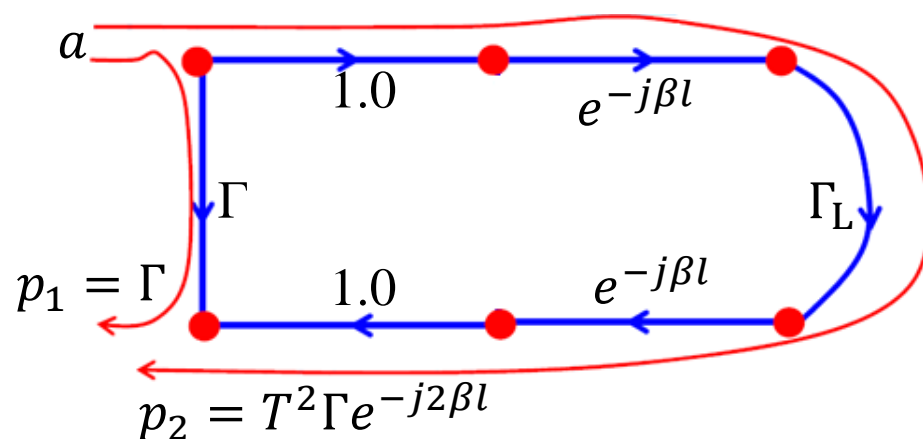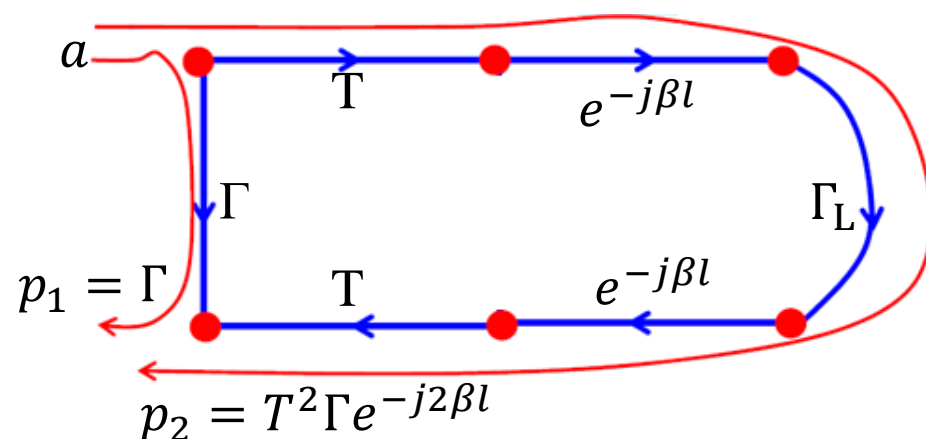With respect to the theory of small reflections (where **only** direct paths are considered), this branch can be **removed** from the SFG **without affect**.




Moreover, the theory of small reflections implements the **approximation**,  $|T| = 1.0$ , so that the SFG becomes:
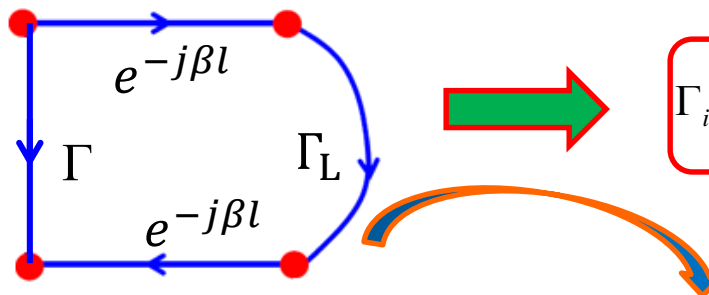
## The Theory of Small Reflections (contd.)

- Reducing this SFG by combining the 1.0 branch and the  $e^{-j\beta l}$  branch via the **series rule**, we get the following **approximate** SFG:

The approximate SFG when applying the theory of small reflections !



$$\Gamma_{in} = \frac{b}{a} \approx \Gamma + \Gamma_L e^{-j2\beta l}$$

Note this **approx** SFG provides **precisely** the results of the theory of small reflections!

**Q:** But wait! The quarter-wave transformer is a **matching** network, therefore  $\Gamma_{in} = 0$ . The **theory of small reflections**, however, provides the **approximate result**:

$$\Gamma_{in} \approx \Gamma + \Gamma_L e^{-j2\beta l}$$

Is this **approximation** very **accurate**? How **close** is this **approximate** value to the correct answer of  $\Gamma_{in} = 0$ ?

**A:** Let's find out!

- Recall that  $\Gamma = \Gamma_L$  for a properly designed quarter-wave matching network, and so:

$$\Gamma_{in} \approx \Gamma + \Gamma_L e^{-j2\beta l} = \Gamma_L (1 + e^{-j2\beta l})$$



## The Theory of Small Reflections (contd.)

- Likewise,  $l = \lambda/4$  (but **only** at the design frequency!) so that:

$$2\beta l = 2\left(\frac{2\pi}{\lambda}\right)\frac{\lambda}{4} = \pi$$

where **you** of course recall that  $\beta = 2\pi/\lambda$ !

- Thus:

$$\Gamma_{in} \approx \Gamma + \Gamma_L e^{j2\beta l} = \Gamma_L (1 + e^{-j\pi}) = \Gamma_L (1 - 1) = 0$$

**Q: Wow!** The theory of small reflections appears to be a **perfect** approximation—**no error** at all!?!

**A: Not so fast.**

The **theory of small reflections** most definitely provides an **approximate** solution (e.g., it **ignores** most of the terms of the propagation series, and it **approximates** connector transmission as  $T = 1$ , when in fact  $T \neq 1$ ).

As a result, the solutions derived using the **theory of small reflections** will—generally speaking—exhibit **some** (hopefully small) **error**.

## The Theory of Small Reflections (contd.)




We just got a bit “**lucky**” for the quarter-wave matching network; the “approximate” result  $\Gamma_{in} = 0$  was exact for this one case!

➡ The **theory of small reflections** is an **approximate** analysis tool!
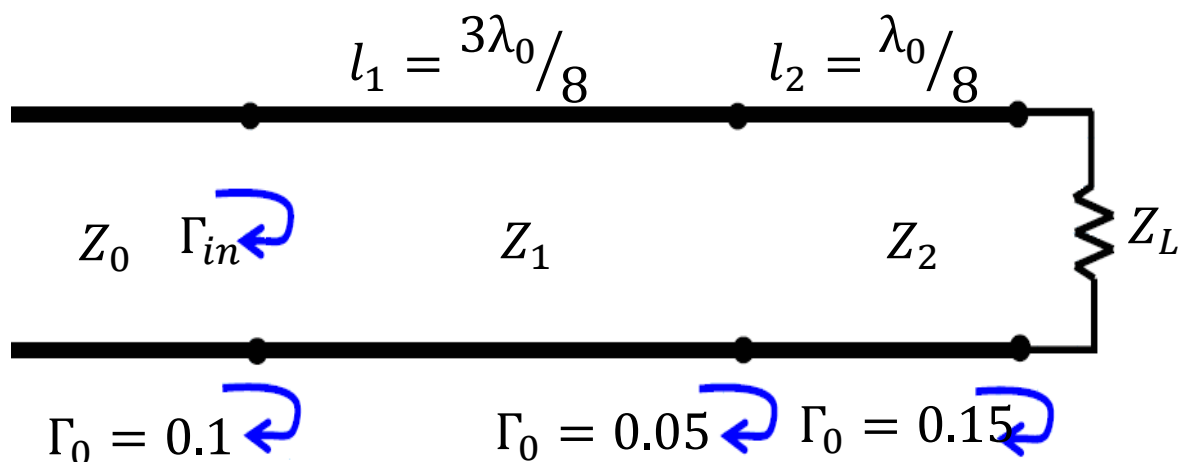
### Example – 1

- Use the **theory of small reflections** to determine a **numeric** value for the **input** reflection coefficient  $\Gamma_{in}$ , at the design frequency  $\omega_0$ .



Note that the transmission line sections have **different lengths**!