

ECE321/521

<u>RF Circuit Design</u>





ECE321/521

RF Circuit Design (ECE321/521)

Instructor: Dr. Mohammad S. Hashmi

Class Timings: Monday & Thursday (10:00 – 11:30)

Lab/Project Timings: TBA

Office Hours: Thursday (17:00 – 18:00)

TAs: Dinesh Rano and Deepayan Banerjee





Date: 02.01.2017

- Introduction
- Differentiating factor between low and high frequency circuits
- Behavior of Passive Components at High Frequency
- Transmission Line (Intro.)

RF Circuit Design

Teacher: *"Mogli,* do you even know your multiplication tables?" **Mogli:** *"Well,* I know of them".

Like Mogli and his multiplication tables, many electrical engineers know of the concepts of RF Circuit Design.

However, Concepts such as characteristic impedance, scattering parameters, Smith charts and the like are familiar, but we often find that a **complete**, **thorough**, and **unambiguous** understanding of these concepts can be somewhat lacking.

Thus, the goals of this class are for you to:

- Obtain a complete, thorough, and unambiguous understanding of the fundamental concepts on RF and High Frequency Engineering
- Apply these concepts to the design and analysis of useful high frequency devices



Pre-requisites:

Circuit Theory Fundamentals, Fields and Waves Fundamentals

Course Focus:

High Frequency Circuit and System Design for Cellular, WIFI, WLAN, and Bluetooth Applications

Lab Components:

- Introduction to ADS, CST and SystemVue (mostly self learning, required for course projects) – Rahul and TAs can help
- Introduction to VNA and Spectrum Analyzer and their Usage
- Rahul Gupta will be your contact point for Labs

Course Outline and Details:

http://www.iiitd.edu.in/~mshashmi/teaching



Evaluation Mechanism

- Assignments (20%)
- [Pen & Paper + ADS] based
- Surprise Quizzes (15%)
- all compulsory!
 - Exams and Project
 - Project (30%)
 - Mid-Sem (20%)
 - End-Sem (15%)

Other Recommended Resources:

- Microwave Engineering <u>by</u> D. M. Pozar, 4th Ed., John Wiley and Sons Inc.
- RF Circuit Design <u>by</u> C. Bowick, 2nd Ed., Newnes
- Secrets of RF Circuit Design <u>by</u> Joseph J. Carr, 3rd Ed., McGraw Hill
- RF Transistor Amplifier <u>by</u> G. Gonzalez, 2nd Ed., Prentice Hall
- IEEE Xplore, IEL, etc.

Text Book:

"RF Circuit Design: Theory and Applications" <u>by</u> R. Ludwig, 2nd Ed., Pearson International







ECE321/521

Motivation

- Importance of RF Circuit Design
 - Wireless/Wirebased Communication Circuits → multi-band and multi-standard transceivers
 - Global Positioning System (GPS)
 - Increased clock speeds in ASICs/SoCs
 - Automotive Electronics





ECE321/521

Some design examples from Lab

















Motivation (contd.)

Frequency Spectrum





Why this course?

- Lumped components (wires, resistors, capacitors, inductors, connectors etc.) behave differently at low and high frequencies.
- Why?
 - current and voltage vary spatially over the component size
 - Leads to the concept of distributed components!

The KCL and KVL are no more applicable

• What do we mean by distributed? :-> Example – Inductor

Low Frequency (Lumped)



High Frequency (Distributed)



Z = ?



RF Behavior of Passive Components

- Why do inductors, capacitors, and resistors behave differently at Radio Frequency?
- What is skin effect?
- Equivalent Circuit Model?

For conventional AC circuit analysis:

- R is considered frequency independent
- Ideal Inductor (L) possesses an impedance $(X_L = j\omega L)$
- Ideal capacitor (C) possesses an impedance $(X_C = \frac{1}{i\omega C})$

Capacitor behaves as open circuit at DC and low frequency <u>whereas</u> an Inductor behaves as short circuit at DC and low frequencies



DC, current flows uniformly distributed over the entire conductor cross-sectional area.

DC Current Density:

$$J_{z0} = \frac{I}{\pi a^2}$$

ECE321/521



RF Behavior of Resistors (contd.)

 At AC, the alternating charge carrier flow establishes a magnetic field that induces an electric field (Faraday's Law) whose associated current density opposes the initial current flow → this effect is very strong at the center (r=0) where the impedance is substantially increased → as a result the current flow resides at the outer periphery with the increasing frequency.







RF Behavior of Resistors (contd.)

- J_z drops with decrease in r (proximity to the center)
- δ decreases with increase in frequency (skin depth from periphery reduces with increased frequency) → the path for current conduction remains nearer to the periphery (skin effect) → current density towards center decreases with increase in frequency and increase in conductivity





RF Behavior of Resistors (contd.)

Frequency sweep: For a fixed wire radius of a = 1mm, the plot $|J_z|/|J_{z0}|$ as a function of depth r:





Resistors at High Frequencies

1. Carbon-composition resistors:



- Consists of densely packed dielectric particulates or carbon granules.
- Between each pair of carbon granules <u>is</u> very small parasitic capacitor.
- These parasitics, in aggregate, are significant → primarily responsible for notoriously poor performance at high frequencies.



Indraprastha Institute of Information Technology Delhi

ECE321/521

Resistors at High Frequencies (contd.)



- Exhibit widely varying impedances over various frequencies.
- The inductor *L* is much larger here as compared to carbon-composition resistor.
- These resistors look like inductors → impedances will increase with increase in frequency.
- At some frequency F_r, the inductance will resonate with shunt capacitance → leads to decrease in impedance.

L₂: lead inductance L₁: inductance of resistive wires C₂: Interlead Capacitance





ECE321/521

Resistors at High Frequencies (contd.)

3. Metal-film Resistors:





- Seems to exhibit very good characteristics over frequency.
- Values of L and C are much smaller as compared to wire-wound and carbon-composition resistors.
- It works well up to 10 MHz \rightarrow useful up to 100 MHz



Resistors at High Frequencies (contd.)

- 4. Thin-film Chip Resistors:
 - The idea is to eliminate or reduce the stray capacitances associated with the resistors
 - Good enough up to 2 GHz.





Resistors at High Frequencies (contd.)

What is the reason for following behavior of a 2000Ω thin-film resistor?





Capacitors at High Frequencies

Equivalent Circuit Representation of a Capacitor → for a parallel-plate





Capacitors at High Frequencies (contd.)



- Above F_r , the capacitor behaves as an inductor.
- In general, larger-value capacitors tend to exhibit more internal inductance than smaller-value capacitors.
- Therefore, it may happen that a $0.1\mu F$ may not be as a good as a 300pF capacitor in a bypass application at 250 MHz.
- The issue is due to significance of lead inductances at higher frequencies.



Capacitors at High Frequencies (contd.) Chip Capacitors





Inductors at High Frequencies

Equivalent Circuit Representation of an Inductor \rightarrow coil type



Indraprastha Institute of Information Technology Delhi

Inductors at High Frequencies (contd.)



- Initially the reactance of inductor follows the ideal but soon departs from it and increases rapidly until it reaches a peak at the inductor's resonant frequency (F_r) . Why?
- Above F_r , the inductor starts to behave as a capacitor.





Chip Inductors



Surface mounted inductors still come as wire-wound coil →these are comparable in size to the resistors and capacitors



ECE321/521

Transmission Line

 It is a standard practice to use metallic conductors for transporting electrical energy from one point of a circuit to another. These conductors are called interconnects.



Therefore cables, wires, conductive tracks on printed circuit boards (PCBs), sockets, packaging, metallic tubes etc are all examples of interconnect.



- For <u>short interconnect</u>, the moment the switch is closed, a voltage will appear across R_L as current flows through it. The effect is instantaneous.
- Voltage and current are due to electric charge movement along the interconnect.
- Associated with the electric charges are static electromagnetic (EM) field in the space surrounding the short interconnect.
- The short interconnect system can be modelled by lumped RLC circuit.





ECE321/521

Transmission Line (contd.)

If the interconnection is <u>long</u> (in comparison to the wavelength of the signal frequency), it takes some time for the voltage and current to appear on the R_L when the switch is closed.



Electric charges move from V_s to the R_L . As the charge move, there is an associated EM field which travels along with the charges

In effect, there is propagating EM field along the interconnect. The propagating EM field is called wave and the interconnect guiding the wave is called transmission line.

A transmission line is a two-conductor system that is used to transmit a signal from one point to another point.



 Variations in current and voltage across the circuit dimensions → KCL and KVL can't be directly applied → This anomaly can be remedied if the line is subdivided into elements of small (infinitesimal) length over which the current and voltage do not vary.



 $\lim_{\Delta z \to 0} \Rightarrow$ Infinite number of infinitesimal sections

Indraprastha Institute of Information Technology Delhi

ECE321/521

Transmission Lines (contd.)



Apply KVL:



KCL on this line segment gives: $i(z,t) - i(z + \Delta z, t) = G\Delta zv(z + \Delta z, t) + C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t}$

Simplification results in: $\underbrace{\frac{\partial i(z,t)}{\partial z} = -Gv(z,t) - C\frac{\partial v(z,t)}{\partial t}}_{\partial t}$ For $\Delta z \to 0$

Describes the current along the transmission lines

Solution for Voltage and Current:

For a sinusoidal excitation [i.e, $V_{s}(t) =$ $V_{s}{cos(\omega t)}$, the steady state voltages and currents along the transmission line are also sinusoidal functions of time whose dependence $i(z,t) = g(z)\cos(\omega t + \eta(z))$ on position and time can be expressed as:

$$v(z,t) = f(z)\cos(\omega t + \varphi(z))$$

• f(z) and g(z) are real functions of position and $\varphi(z)$ and $\eta(z)$ describe the positional dependence of the phase.

• Alternatively,

$$v(z,t) = f(z)\cos(\omega t + \varphi(z)) = \operatorname{Re}\left[f(z)e^{j\varphi(z)}e^{j\omega t}\right]$$

 $i(z,t) = g(z)\cos(\omega t + \eta(z)) = \operatorname{Re}\left[g(z)e^{j\eta(z)}e^{j\omega t}\right]$

Let us define these phasors: $V(z) = f(z)e^{j\varphi(z)}$ $I(z) = g(z)e^{j\eta(z)}$

The phasors I(z) and V(z) are complex functions of position and express the variations of current/voltage as a function of position along the transmission line.

- Therefore the current and voltage functions can be $v(z,t) = \operatorname{Re}\left[V(z)e^{j\omega t}\right]$ $i(z,t) = \operatorname{Re}\left[I(z)e^{j\omega t}\right]$ expressed as:
- The time-harmonic form of the telegrapher equations are:

$$\operatorname{Re} \frac{\partial \left(f(z)e^{j\varphi(z)}e^{j\omega t} \right)}{\partial z} = -\operatorname{Re} \left(R.g(z)e^{j\eta(z)}e^{j\omega t} + j\omega L.g(z)e^{j\eta(z)}e^{j\omega t} \right)$$
$$\operatorname{Re} \frac{\partial \left(g(z)e^{j\eta(z)}e^{j\omega t} \right)}{\partial z} = -\operatorname{Re} \left(G.f(z)e^{j\varphi(z)}e^{j\omega t} + j\omega C.f(z)e^{j\varphi(z)}e^{j\omega t} \right)$$

 With the substitution of phasors, the equations of voltage and current wave result in:

$$\operatorname{Re} \frac{\partial \left(V(z) e^{j\omega t} \right)}{\partial z} = -\operatorname{Re} \left(\operatorname{RI}(z) e^{j\omega t} + j\omega LI(z) e^{j\omega t} \right)$$
$$\operatorname{Re} \frac{\partial \left(I(z) e^{j\omega t} \right)}{\partial z} = -\operatorname{Re} \left(\operatorname{GV}(z) e^{j\omega t} + j\omega CV(z) e^{j\omega t} \right)$$



• The differential equations for current and voltage along the transmission line can be expressed in phasor form as:



• The equations can be simplified as:

Indraprastha Institute of Information Technology Delhi

Indraprastha Institute of Information Technology Delhi

ECE321/521

Transmission Lines (contd.)

 For lossless transmission line (i.e, transmission line where R and G are negligible) - most common scenario in our transmission line based circuit design:

 $\gamma = j\beta = j\omega\sqrt{LC}$ No Attenuation
Phase Constant is also Propagation Constant for a Lossless Line
Oh please, continue wasting my valuable time.
We both know that a lossless transmission line is a physical impossibility.

True! However, a **low-loss** line **is** possible – in fact it is **typical!** If $R \ll \omega L$ and $G \ll \omega C$, we find that the lossless transmission line equations are excellent **approximations!!!**

Similarly the current phasor for a lossless line can be described:

 $I(z) = -\frac{1}{j\omega L} \frac{dV(z)}{dz} = -\frac{1}{j\omega L} \frac{d}{dz} \left[V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \right]$ $\Rightarrow I(z) = \frac{\beta}{\omega I} \left[V_0^+ e^{-j\beta z} - V_0^- e^{j\beta z} \right]$ Gives the Definition of Characteristic Impedance

Indraprastha Institute of Information Technology Delhi

• The time dependent form of the voltage and current along the transmission line can be derived from phasors as:

$$v(z,t) = \operatorname{Re}\left[V(z)e^{j\omega t}\right] = \operatorname{Re}\left[V_0^+ e^{-j(\beta z - \omega t)} + V_0^- e^{j(\beta z + \omega t)}\right]$$
$$i(z,t) = \operatorname{Re}\left[I(z)e^{j\omega t}\right] = \operatorname{Re}\left[\frac{V_0^+}{Z_0}e^{-j(\beta z - \omega t)} - \frac{V_0^-}{Z_0}e^{j(\beta z + \omega t)}\right]$$

• For the simple case of V_0^+ and V_0^- being real, the voltage and current along the transmission line can be expressed as:

$$v(z,t) = V_0^+ \cos(\omega t - \beta z) + V_0^- \cos(\omega t + \beta z)$$
$$i(z,t) = \frac{V_0^+}{Z_0} \cos(\omega t - \beta z) - \frac{V_0^-}{Z_0} \cos(\omega t + \beta z)$$

$$V_0^+\cos(\omega t - \beta z)$$

$$V_0^-\cos(\omega t + \beta z)$$

Wave Functions

• Let us examine the wave characteristics of

$$v_1(z,t) = V_0^+ \cos(\omega t - \beta z)$$