

Lecture – 6

Date: 23.01.2017

- Smith Chart – Examples
- Admittance Transformation

Example-1


Given:

$$\Gamma_0 = 0.5 \angle 45^\circ$$

$$Z_0 = 50\Omega$$

What is load
impedance, Z_L ?

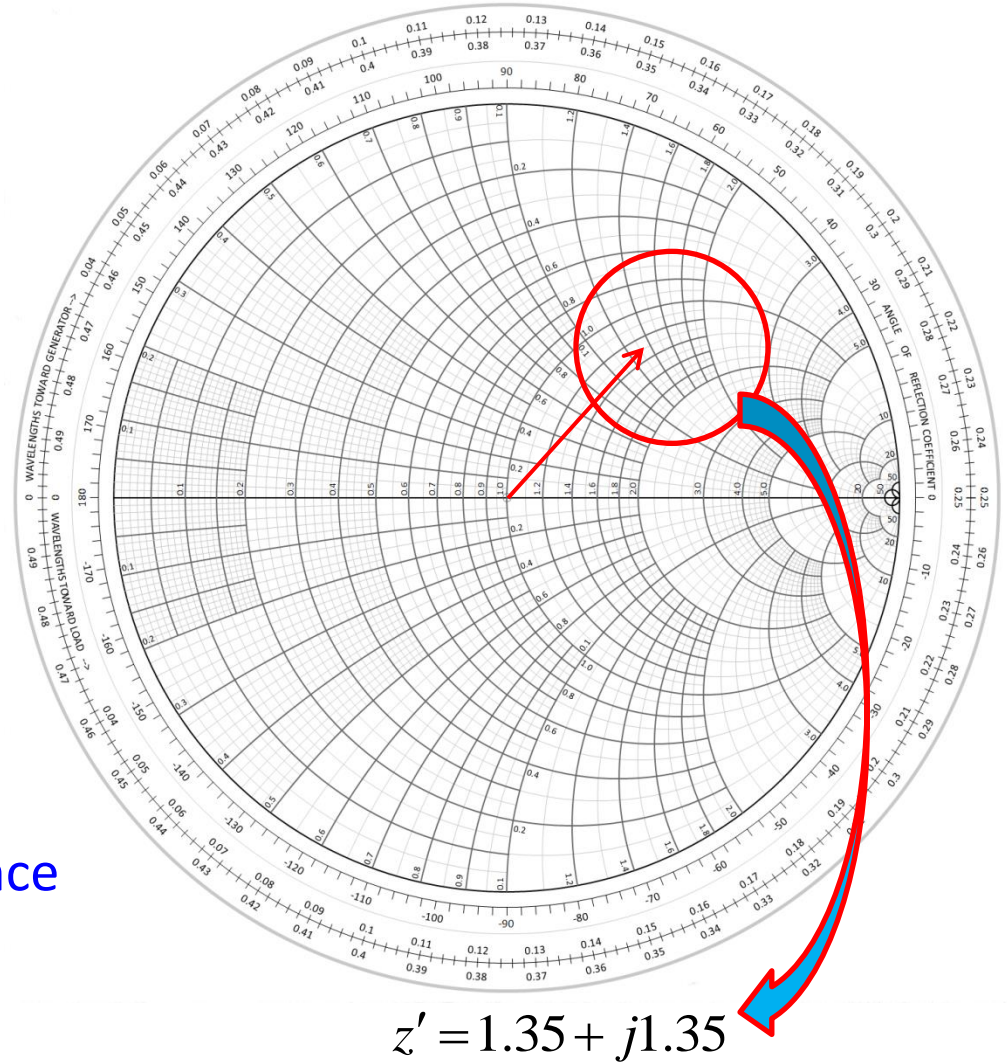- Locate Γ_0 on the smith chart
- Read the normalized impedance
- Then multiply the identified normalized impedance by Z_0



$$\therefore Z_L = 50\Omega * (1.35 + j1.35) = 67.5\Omega + j67.5\Omega$$

Example-2


Given:

$$Z_L = (15 - j25)\Omega$$

$$Z_0 = 50\Omega$$


What is load
impedance, Γ_0 ?

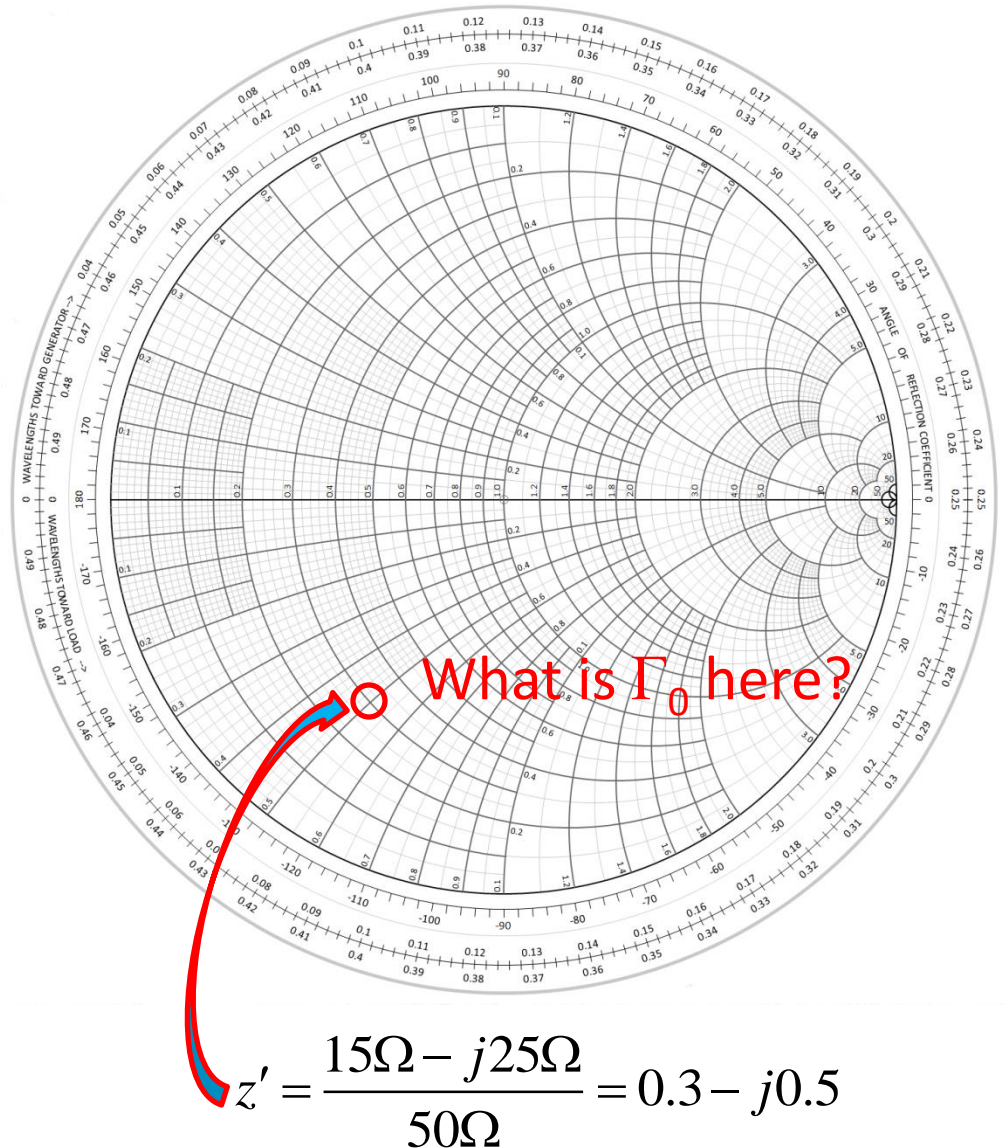- Normalize the given Z_L
- Mark the normalized impedance Smith chart
- Read the value of Γ_0 from Smith chart



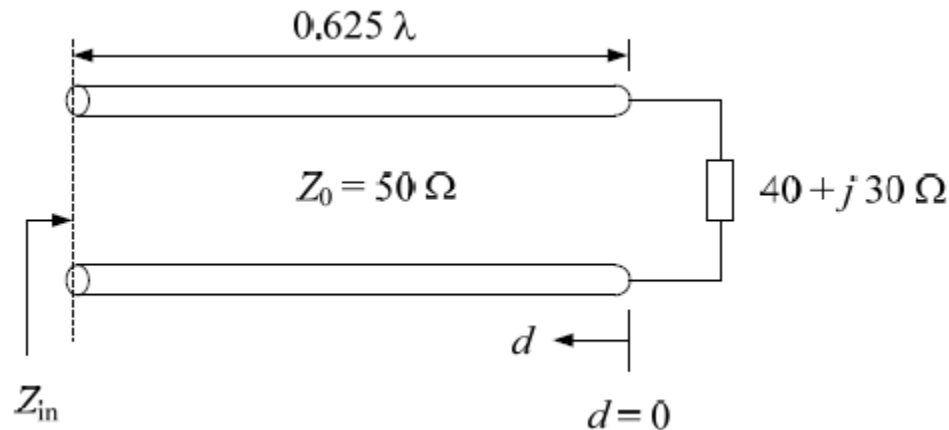Example-3

- Using Smith chart, determine the voltage reflection coefficient at the load and the input impedance of the following TL



$$1. \quad z_L'(d=0) = \frac{Z(d=0)}{Z_0} = \frac{Z_L}{Z_0} = 0.8 + j0.6 \quad \leftarrow \text{Mark this on Smith chart}$$

2. What is Γ_0 ? Read this directly from Smith chart.

$$|\Gamma_0| = 0.33 \quad \angle \Gamma_0 = 90^\circ$$


Example-3 (contd.)

3. For Z_{in}' , rotate the load reflection coefficient point clockwise (towards generator) by $d = 0.625\lambda$ (it is full rotation and then additional rotation of 0.125λ) \rightarrow Then read normalized input impedance from Smith chart

$$z_{in}' = 2 + j0$$

Therefore the
input
impedance of
the TL is:

$$Z_{in} = 50 * z_{in}' = 100\Omega$$

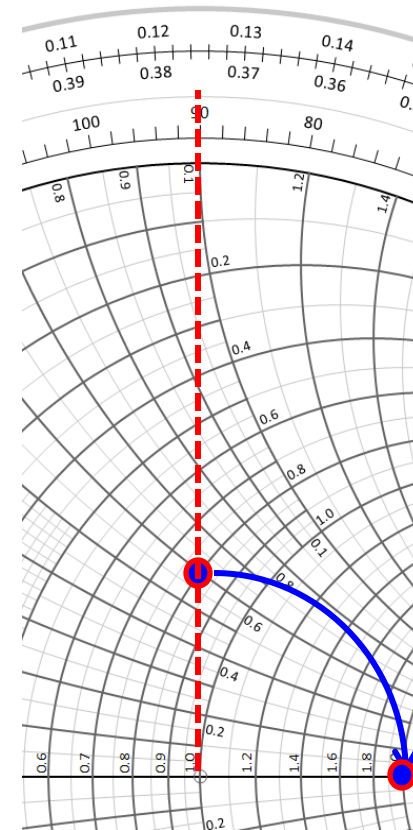

Example – 4

- $Z_L = (30 + j60)\Omega$ is connected to a 50Ω TL of 2cm length and operated at 2 GHz. Use the reflection coefficient concept and find the input impedance Z_{in} under the assumption that the phase velocity is 50% of the speed of light

First Approach

- We first determine the load reflection coefficient:

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 + j60 - 50}{30 + j60 + 50} = 0.2 + j0.6 = \sqrt{.40}e^{j71.56^\circ}$$

- Next we compute Γ ($l = 2\text{cm}$) based on the fact that:

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{v_p} = \frac{2\pi f}{0.5c} = 83.77\text{m}^{-1} \quad \Rightarrow 2\beta l = 192^\circ \quad \text{How?}$$

- Therefore, reflection coefficient at the other end of the TL is:

$$\Gamma = \Gamma_0 e^{-j2\beta l} = \sqrt{.40}e^{-120.4^\circ} = -0.32 - j0.55$$

- The corresponding input impedance is:

$$Z_{in} = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = R + jX = (14.7 - j26.7)\Omega$$

Second Approach

Using Smith chart


Example – 4 (contd.)

Using Smith Chart


1. The normalized load impedance is:

$$z_L' = (30 + j60)\Omega / 50\Omega = 0.6 + j1.2$$

2. This point on the Smith chart can be identified as the intersection of the circle of constant resistance $r = 0.6$ with the circle of constant reactance $x = 1.2$
3. The straight line connecting the origin to *normalized load impedance* determines the load reflection coefficient Γ_0 . The associated angle is recorded with respect to the positive real axis. From Smith chart we can find that $|\Gamma_0| = 0.6325$ and *phase of $\Gamma_0 = 71.56^\circ$* .
4. Rotate clockwise this by $2\beta l = 192^\circ$ to obtain Γ_{in}

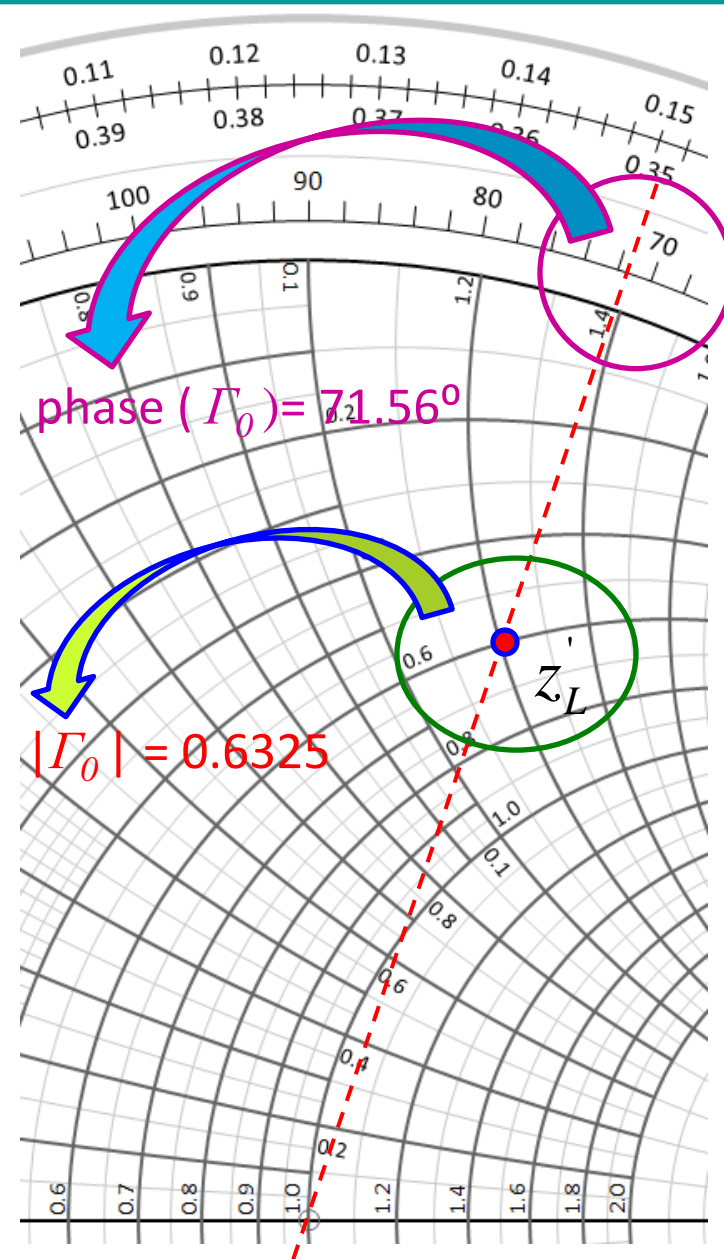

Example – 4 (contd.)

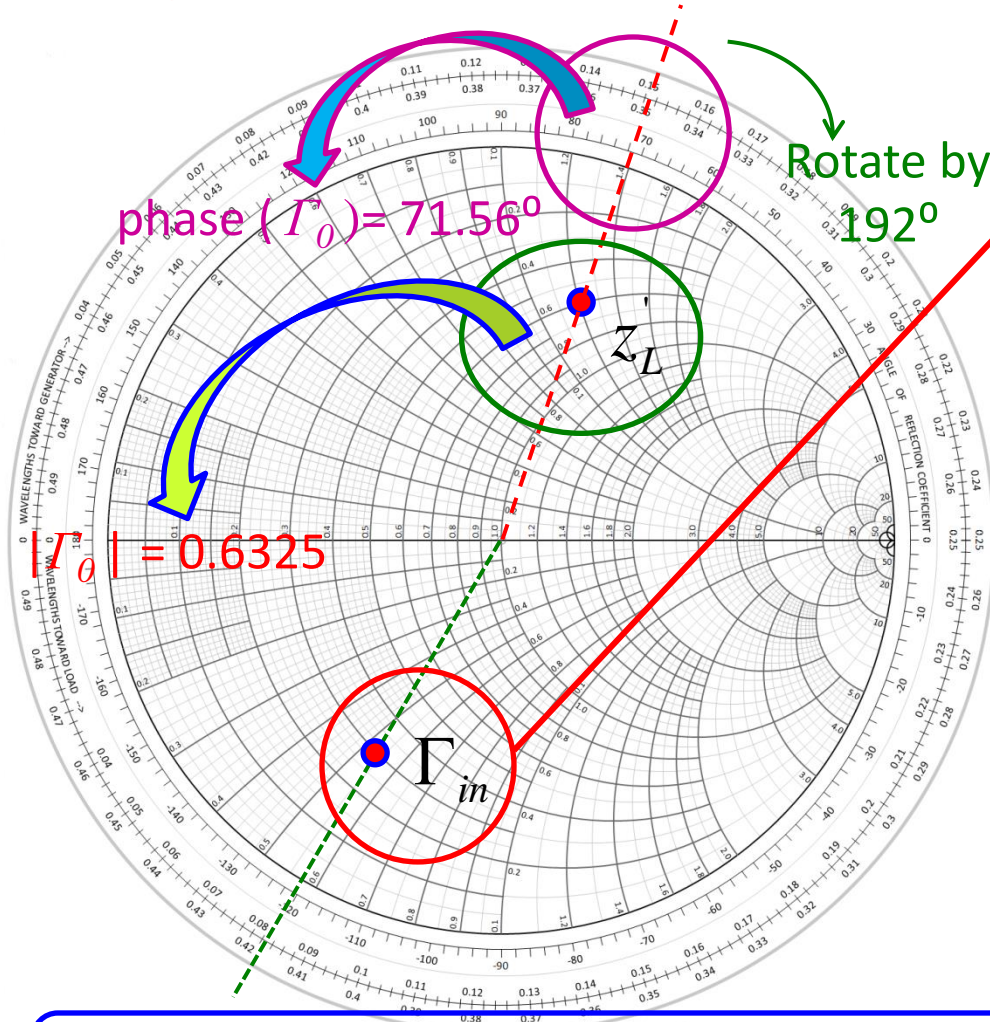

This point uniquely identifies the associated normalized input impedance $z_{in}' = 0.3 - j0.53$

5. The Γ_{in} uniquely identifies the associated normalized input impedance $z_{in}' = 0.3 - j0.53$
6. The preceding normalized impedance can be converted back to actual input impedance values by multiplying it by $Z_0 = 50\Omega$, resulting in the final solution $Z_{in} = (15 - j26.5)\Omega$

The exact value of Z_{in} computed earlier was $(14.7 - j26.7)\Omega$. The small anomaly is expected considering the approximate processing of graphical data in Smith chart

Special Transformation Conditions in Smith Chart

- The rotation angle of the normalized TL impedance around the Smith chart is regulated by the length of TL or operating frequency
- Thus, both capacitive and inductive impedances can be generated based on the length of TL and the termination conditions at a given frequency
- The open- and short-circuit terminations are very popular in generating inductive and capacitive elements

Open Circuit Transformations

- For an arbitrary terminated line the input impedance is:

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta z)}{Z_0 + jZ_L \tan(\beta z)}$$

For an open circuit 

$$Z_{in}(z) = -jZ_0 \cot(\beta z)$$

- For a capacitive impedance of $X_C = 1/j\omega C$ we get:

$$\frac{1}{j\omega C} \cdot \frac{1}{Z_0} \equiv z'_{in} = -j \cot(\beta z_1) \quad \xrightarrow{\text{green arrow}} \quad z_1 = \frac{1}{\beta} \left[\cot^{-1} \left(\frac{1}{\omega C Z_0} \right) + n\pi \right]$$

- For an inductive impedance of $X_L = j\omega L$ we get:

$$j\omega L \frac{1}{Z_0} \equiv z'_{in} = -j \cot(\beta z_2) \quad \xrightarrow{\text{blue arrow}} \quad z_2 = \frac{1}{\beta} \left[\pi - \cot^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$

Special Transformation Conditions in Smith Chart (contd.)

Short Circuit Transformations

- For an arbitrary terminated line the input impedance is:

$$Z_{in}(z) = Z_0 \frac{Z_L + jZ_0 \tan(\beta z)}{Z_0 + jZ_L \tan(\beta z)} \quad \xrightarrow{\text{For a short circuit}} \quad Z_{in}(z) = jZ_0 \tan(\beta z)$$

- For a capacitive impedance of $X_C = 1/j\omega C$ we get:

$$\frac{1}{j\omega C} \cdot \frac{1}{Z_0} \equiv z'_{in} = j \tan(\beta z_1) \quad \xrightarrow{\quad} \quad z_1 = \frac{1}{\beta} \left[\pi - \tan^{-1} \left(\frac{1}{\omega C Z_0} \right) + n\pi \right]$$

- For an inductive impedance of $X_L = j\omega L$ we get:

$$j\omega L \frac{1}{Z_0} \equiv z'_{in} = j \tan(\beta z_2) \quad \xrightarrow{\quad} \quad z_2 = \frac{1}{\beta} \left[\tan^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$

Example – 5

- For an open-circuited 50Ω TL operated at 3GHz and with a phase velocity of 77% of speed of light, find the line lengths to create a 2pF capacitor and 5.3nH inductor. Use Smith Chart for solving this problem.

Example – 5 (contd.)

- For the given phase velocity, the propagation constant is:

$$\beta = \frac{2\pi f}{v_p} = \frac{2\pi f}{0.77c} = 81.6m^{-1}$$

- We know that an open-circuit can create a capacitor as per following equation:

$$z_1 = \frac{1}{\beta} \left[\cot^{-1} \left(\frac{1}{\omega C Z_0} \right) + n\pi \right]$$

$$\beta = 81.6m^{-1}$$

$$C = 2pF$$

$$f = 3GHz$$

$$z_1 = 13.27 + n38.5$$

- We know that an open-circuit can create an inductor as per following equation:

$$z_2 = \frac{1}{\beta} \left[\pi - \cot^{-1} \left(\frac{\omega L}{Z_0} \right) + n\pi \right]$$

$$\beta = 81.6m^{-1}$$

$$L = 5.3nH$$

$$f = 3GHz$$

$$z_2 = 32.81 + n38.5$$

Using Smith Chart

- At 3GHz, the reactance of a 2pF capacitor is: $X_c = \frac{1}{j\omega C} = -j26.5\Omega$
- Therefore, the normalized capacitive reactance is: $z'_c = \frac{X_c}{Z_0} = -j0.53$

Example – 5 (contd.)

- The wavelength is:


$$\lambda = \frac{v_p}{f} = 77\text{mm}$$

- At 3GHz, the reactance of a 5.3nH inductor is:

$$X_L = j\omega L = j100\Omega$$


- Therefore, the normalized inductive reactance is:

$$z_L = \frac{X_L}{Z_0} = j2$$

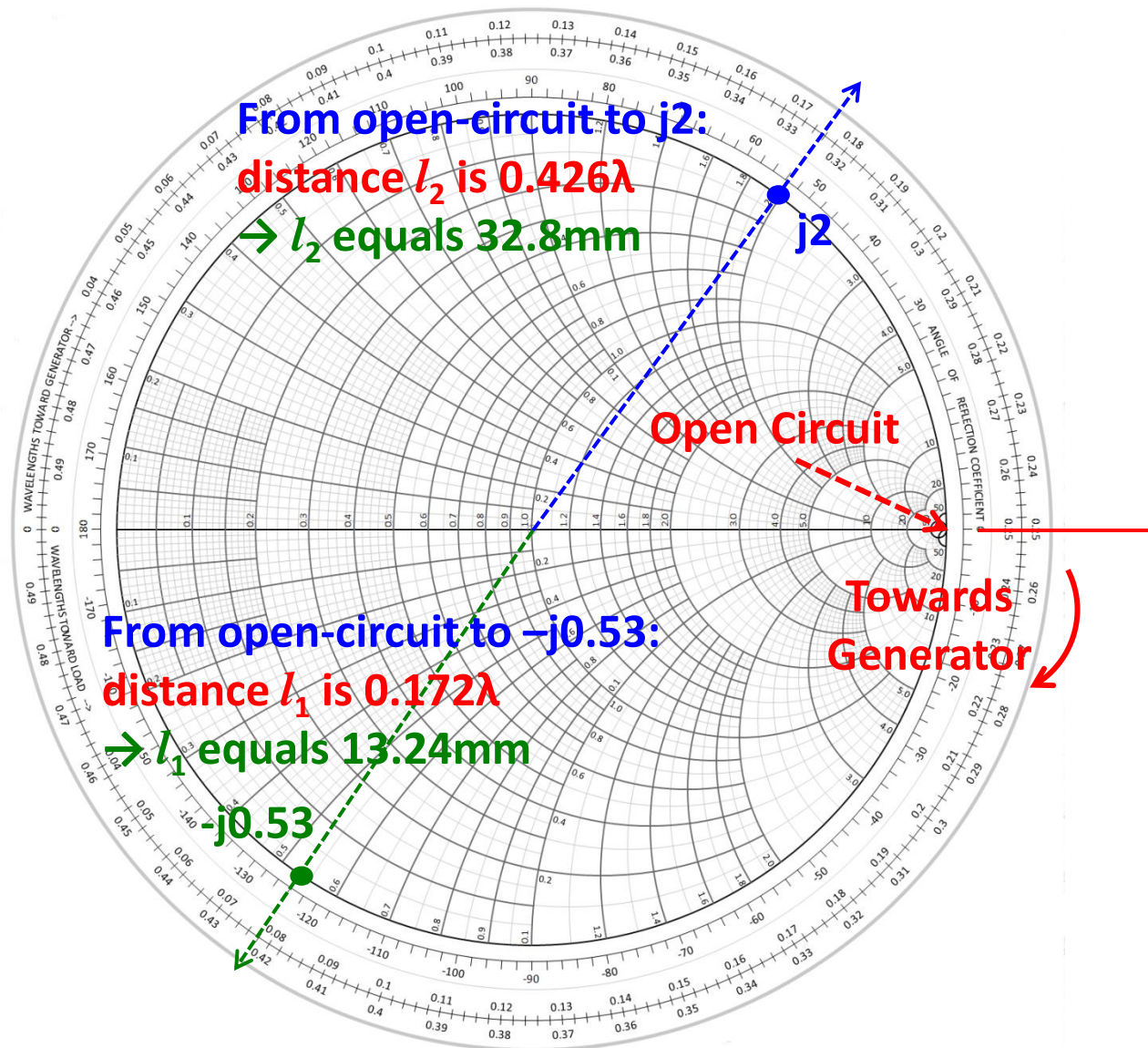

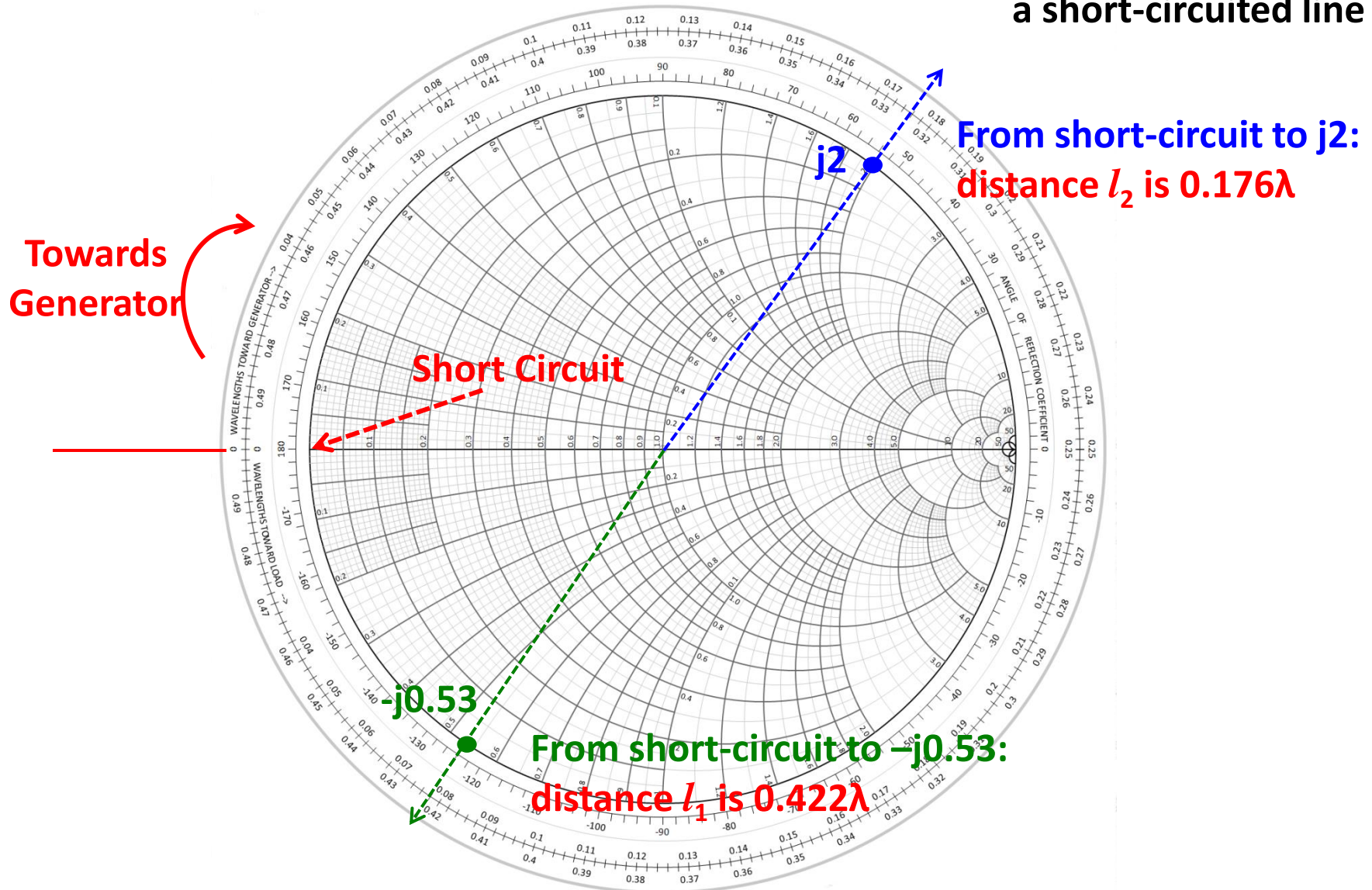Example – 6

- Same problem but for a short-circuited line




Special Transformation Conditions in Smith Chart (contd.)

Summary

- It is apparent that both open-circuit and short-circuit TLs can achieve desired capacitance or inductance. Which configuration is more useful?
- At high frequencies, it's difficult to maintain perfect open-circuit conditions → due to changing temperatures, humidity, and other parameters of the medium surrounding the open TL → short-circuit TLs are, therefore, more popular
- However, short-circuit TL is problematic at higher frequencies → through-hole short connections create parasitic inductances (why?)
- Sometimes board size regulates the choice of open or short TL → for example, an open-circuit TL will always require smaller TL segment for realizing any specified capacitance as compared to a short-circuit TL segment

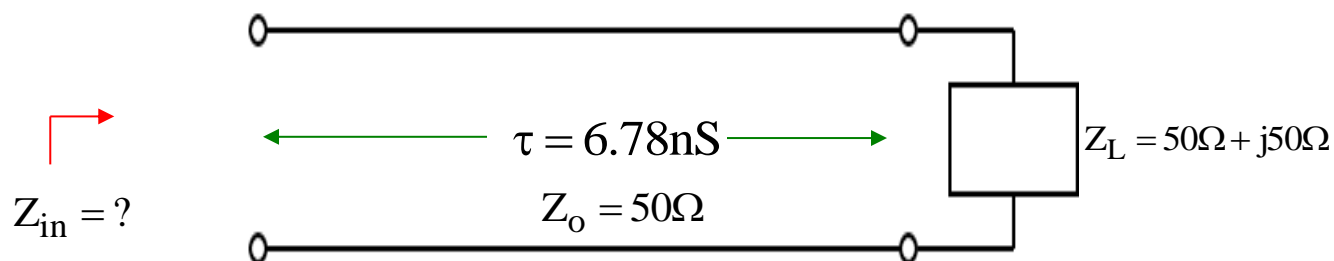Example – 7

What is Z_{in} at 50 MHz for the following circuit?



1. Normalized Impedance: $z_L' = \frac{50 \Omega + j50 \Omega}{50 \Omega} = 1.0 + j1.0$
2. Mark the normalized impedance on the Smith chart
3. Read reflection coefficient from Smith Chart: $\Rightarrow \Gamma_0 = 0.445 \angle 64^\circ$
4. Transform the load reflection coefficient to the input:

$$\Gamma_{in} = \Gamma_0 e^{-j2\beta l} = \Gamma_0 e^{-j2\omega\tau}$$

$2\omega\tau = 244^\circ$


Rotate clockwise (towards generator)

$$\Rightarrow \Gamma_{in} = 0.445 \angle 180^\circ$$

Read the normalized input impedance in the Smith chart

$$z_{in}' = 0.38 + j0.0$$

Example – 7 (contd.)

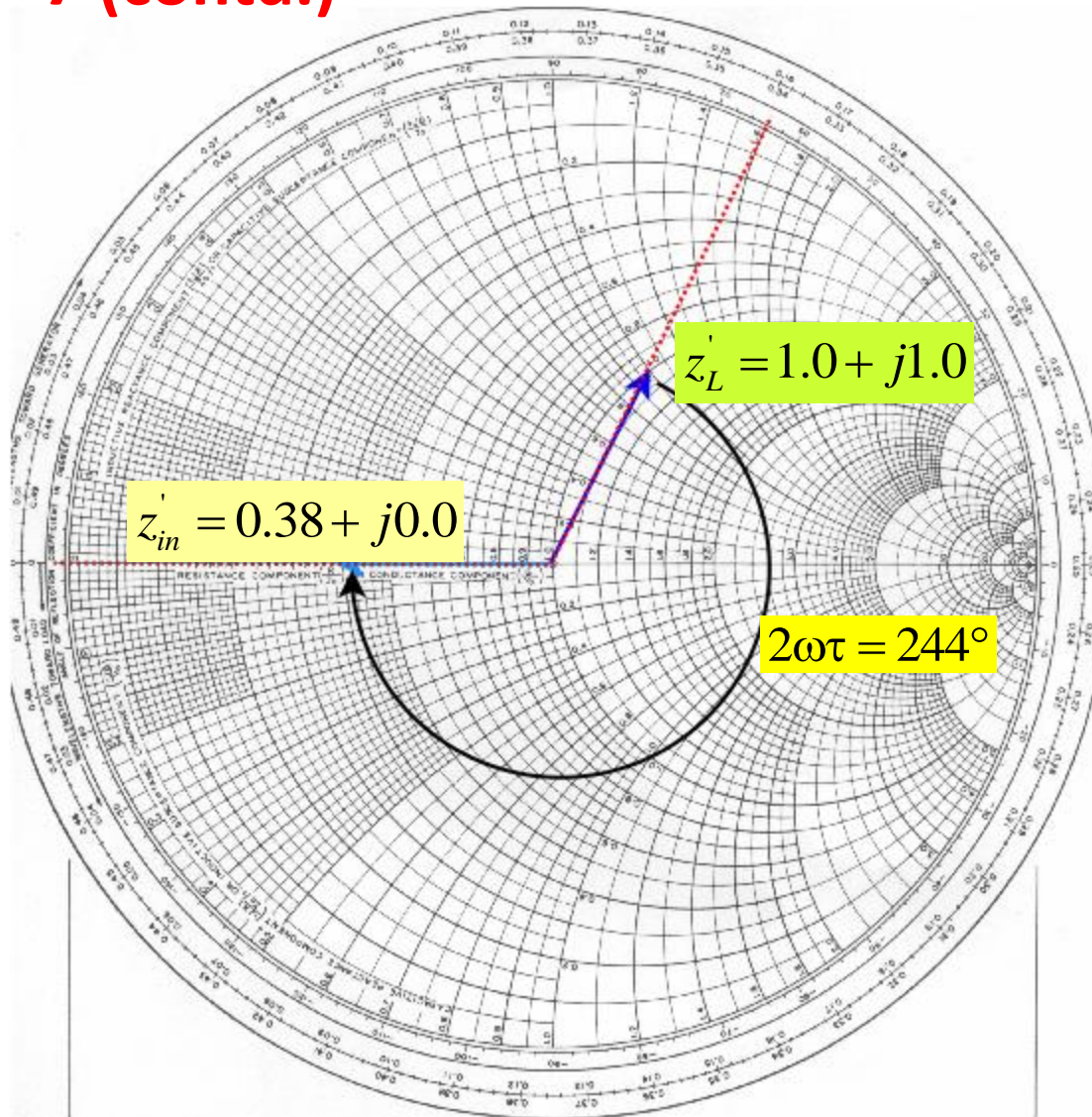


Example – 8

- determine the input impedance of a transmission line that is terminated in a **short circuit**, and whose length is:

$$a) l = \lambda/8 = 0.125\lambda \quad \Rightarrow \quad 2\beta l = 90^\circ$$
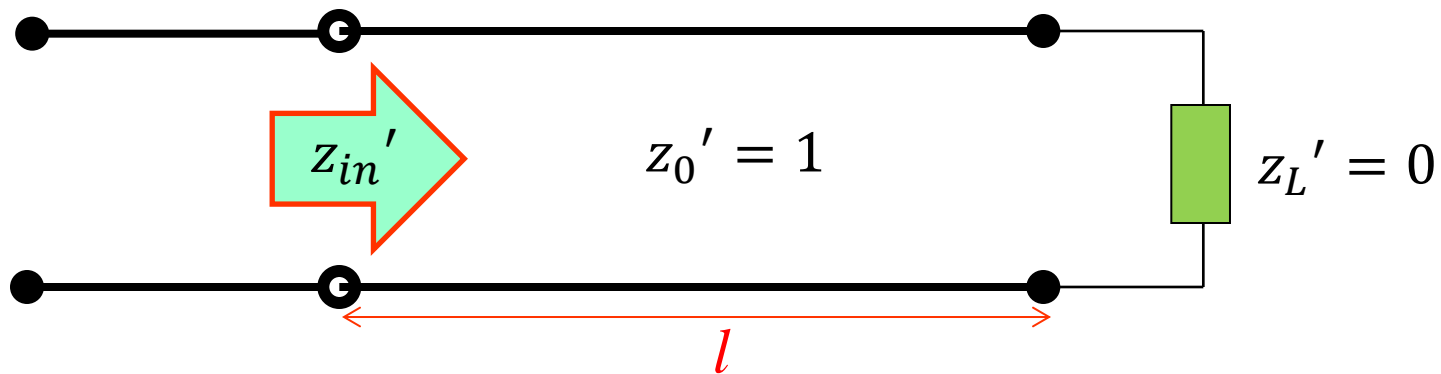
$$b) l = 3\lambda/8 = 0.375\lambda \quad \Rightarrow \quad 2\beta l = 270^\circ$$



Solution:

- a) Rotate **clockwise** 90° from $\Gamma = -1.0 = e^{j180^\circ}$ and find Z_{in}' .

$$Z_{in}' = j$$

- b) Rotate **clockwise** 270° from $\Gamma = -1.0 = e^{j180^\circ}$ and find Z_{in}' .

$$Z_{in}' = -j$$

Example – 9

- A load **terminating** at transmission line has a normalized impedance $z_L' = 2.0 + j2.0$. What should the **length** l of transmission line be in order for its input impedance to be:
 - Purely **real** (i.e., $X_{in} = 0$)
 - Have a real (resistive) part equal to **one** (i.e., $r_{in} = 1.0$)
- Solution:**
 - Find $z_L' = 2.0 + j2.0$ on your Smith Chart, and then rotate **clockwise** until you “bump into” the contour $x = 0$ (recall this contour lies on the Γ_r – **axis!**).
 - When you reach the $x = 0$ contour—**stop!** Lift your pen and note that the impedance value of this location is **purely real** (after all, $x = 0$!).
 - measure the **rotation angle** that was required to move clockwise from $z_L' = 2.0 + j2.0$ to an impedance on the $x = 0$ contour—this **angle** is equal to $2\beta l$!

You can now **solve** for l , or use the **electrical length scale** surrounding the Smith Chart.

One more important point—there are **two** possible solutions!

$$z_{in}' = 4.2 + j0$$



$$2\beta l = 30^\circ$$



$$l = 0.042\lambda$$

$$z_{in}' = 0.24 + j0$$



$$2\beta l = 210^\circ$$



$$l = 0.292\lambda$$

Example – 9 (contd.)

- b)** Find $z_L' = 2.0 + j2.0$ on your Smith Chart, and then rotate **clockwise** until you “bump into” the **circle** $r = 1$ (recall this circle intersects the **center** point of the Smith Chart!).
- When you reach the $r = 1$ circle—**stop!** Lift your pencil and note that the impedance value of this location has a real value equal to **one** (after all, $r = 1$!).
 - measure the **rotation angle** that was required to move clockwise from $z_L' = 2.0 + j2.0$ to an impedance on the $r = 1$ circle—this **angle** is equal to $2\beta l$!
 - Thus, for impedances where $r = 1$ (i.e., $z' = 1 + jx$):

$$\Gamma = \frac{z' - 1}{z' + 1} = \frac{(1 + jx) - 1}{(1 + jx) + 1} = \frac{jx}{2 + jx}$$
 - and therefore:

$$|\Gamma|^2 = \frac{|jx|^2}{|2 + jx|^2} = \frac{x^2}{4 + x^2} \rightarrow x^2 = \frac{4|\Gamma|^2}{1 - |\Gamma|^2} \rightarrow x = \pm \frac{2|\Gamma|}{\sqrt{1 - |\Gamma|^2}}$$

there are **two** equal but opposite solutions!

for **this** example gives us solutions $x = \pm 1.6$.