

Lecture – 7

Date: 28.01.2017

- Admittance Smith Chart
- High Frequency Network Analysis (intro)
- Impedance, Admittance and Scattering Matrix
- Matched, Lossless, and Reciprocal Networks



Admittance Transformation

- RF/Microwave network, similar to any electrical network, has impedance elements in series and parallel
- Impedance Smith chart is well suited while working with series configurations while admittance Smith chart is more useful for parallel configurations
- The impedance Smith chart can easily be used as an admittance calculator

Hence,
$$y_{in}(z) = \frac{1 - \Gamma(z)}{1 + \Gamma(z)}$$
 $y_{in}(z) = \frac{1 + e^{-j\pi}\Gamma(z)}{1 - e^{-j\pi}\Gamma(z)}$

It means, to obtain normalized admittance \rightarrow take the normalized impedance and multiply associated reflection coefficient by $-1 = e^{-j\pi} \rightarrow$ it is equivalent to a 180° rotation of the reflection coefficient in complex Γ -plane



Example – 1

• Convert the following normalized input impedance z_{in}' into normalized input admittance y_{in}' using the Smith chart:

$$z_{in} = 1 + j1 = \sqrt{2}e^{j(\pi/4)}$$

First approach: The normalized admittance can be found by direct inversion as:

$$y_{in} = \frac{1}{z_{in}} = \frac{1}{1+j1} = \frac{1}{\sqrt{2}}e^{-j(\pi/4)} = \frac{1}{2} - j\frac{1}{2}$$

Alternative approach:

- Mark the normalized impedance on Smith chart
- Identify phase angle and magnitude of the associated reflection coefficient
- Rotate the reflection coefficient by 180^o
- Identify the x-circle and r-circle intersection of the rotated reflection coefficient

Indraprastha Institute of Information Technology Delhi

ECE321/521





Example – 2

<u>Given:</u> $z_{in} = 1 + j2$

• Find the normalized admittance $\lambda/8$ away from the load

Steps:

- 1. Mark the normalized impedance on Smith Chart
- 2. Clockwise rotate it by 180°
- 3. Identify the normalized admittance and the phase angle of the associated reflection coefficient
- 4. Clockwise rotate the reflection coefficient (associated with the normalized admittance) by $2\beta l$ (here $l = \lambda/8$)
- 5. The new location gives the required normalized admittance

Indraprastha Institute of Information Technology Delhi

ECE321/521

Example – 2 (contd.)





Admittance Smith chart

- Alternative approach to solve parallel network elements is through 180° rotated Smith chart
- This rotated Smith chart is called **admittance Smith chart <u>or</u> Y-Smith chart**
- The corresponding normalized resistances become normalized conductances & normalized reactances become normalized suceptances

$$r = \frac{R}{Z_0} \Longrightarrow g = \frac{G}{Y_0} = Z_0 G$$
$$x = \frac{X}{Z_0} \Longrightarrow b = \frac{b}{Y_0} = Z_0 B$$

- The Y-Smith chart preserves:
 - The direction in which the angle of the reflection coefficient is measured
 - The direction of rotation (either toward or away from the generator)





ECE321/521

Combined Z- and Y- Smith Charts





ECE321/521

Example – 3

• Identify (a) the normalized impedance z' = 0.5 + j0.5, and (b) the normalized admittance value y' = 1 + j2 in the combined ZY-Smith Chart and find the corresponding values of normalized admittance and impedance





High Frequency Networks

<u>Requirement of Matrix Formulation</u>



Impedance or Admittance Matrix. Right?

In principle, N by N impedance matrix completely characterizes a linear Nport device. Effectively, the impedance matrix defines a multi-port device the way a Z_L describes a single port device (e.g., a load)

Linear networks can be completely characterized by parameters measured at the network ports without knowing the content of the networks.



Multiport Networks

 Networks can have any number of ports – however, analysis of a 2-port, 3-port or 4-port network is sufficient to explain the theory and the associated concepts



- The ports can be characterized with many parameters (Z, Y, S, ABCD). Each has a specific advantage.
- For 2-port Network, each parameter set is related to 4 variables:
 - 2 independent variables for excitation
 - 2 dependent variables for response





The Impedance Matrix (contd.)

• In principle, the current and voltages at the port-n of networks are given as:

$$V_n(z_n = z_{nP}) \qquad I_n(z_n = z_{nP})$$

 However, the simplified formulations are:

$$V_n = V_n(z_n = z_{nP})$$
 $I_n = I_n(z_n = z_{nP})$

- If we want to say that there exists a non-zero current at port-1 and zero current at all other $I_1 \neq 0$ $I_2 = I_3 = I_4 = 0$ ports then we can write as:
- In order to define the elements of impedance matrix, there will be need to measure/determine the associated voltages and currents at the respective ports. Suppose, if we measure/determine current at port-1 and then voltage at port-2 then we can define:



- Similarly, the trans-impedance $Z_{31} = \frac{V_3}{I_1}$ $Z_{41} = \frac{V_4}{I_1}$ **Trans-impedance** parameters Z_{31} and Z_{41} are:
- We can also define other trans-impedance parameters such as Z_{34} as the ratio between the complex values I_4 (the current into port-4) and V_3 (the voltage at port-3), given that the currents at all other ports (1, 2, and 3) are zero.

Indraprastha Institute of ECE321/521 Information Technology Delhi The Impedance Matrix (contd.) Therefore, the more generic $Z_{mn} = \frac{\mathbf{v}_m}{\mathbf{I}}$ (given that $I_k = 0$ for all $k \neq n$) form of trans-impedance is: How do we ensure that all but **one port** current is zero? 7 Port-2 the Open ports where the current needs to be zero: **4-port Linear** +The ports should + Z_0 V_1 Microwave Z_0 be opened! not Network the TL connected Port-1 to the ports Port-3 ----Port-4 <u>____</u> then define the respective Z_{mn} (given that all ports k≠n are open) trans-impedances as:



Impedance Matrix

The Impedance Matrix (contd.)

- Once we have defined the trans-impedance terms by opening various ports, it is time to formulate the impedance matrix
- Since the network is **linear**, the voltage at any port due to all the port currents is simply the coherent sum of the voltage at that port due to each of the currents
- For example, the voltage at **port-3** is: $V_3 = Z_{34}I_4 + Z_{33}I_3 + Z_{32}I_2 + Z_{31}I_1$
- Therefore we can generalize the voltage for **N-port** network as: $V_m = \sum_{n=1}^N Z_{mn} I_n \implies \mathbf{V} = \mathbf{Z}\mathbf{I}$
- Where I and V are $\mathbf{V} = [\mathbf{V}_1, \mathbf{V}_2, \mathbf{V}_3, ..., \mathbf{V}_N]^T$ $\mathbf{I} = [\mathbf{I}_1, \mathbf{I}_2, \mathbf{I}_3, ..., \mathbf{I}_N]^T$ vectors given as: The term Z is matrix given by: $Z = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1n} \\ Z_{21} & & & \vdots \\ \vdots & & & & \\ Z_{-1} & Z_{m2} & \dots & Z_{mn} \end{bmatrix}$

 - $\mathbf{Z}(\omega) = \begin{bmatrix} Z_{11}(\omega) & Z_{12}(\omega) & \dots & Z_{1n}(\omega) \\ Z_{21}(\omega) & & & \vdots \\ \vdots & & & \\ Z_{m1}(\omega) & Z_{m2}(\omega) & \dots & Z_{mn}(\omega) \end{bmatrix}$ The values of elements in the impedance matrix are frequency dependents and often it is advisable to describe impedance matrix as:

Indraprastha Institute of Information Technology Delhi

ECE321/521

The Admittance Matrix





- Now, since the network is linear, the current at any one port due to all the port voltages is simply the coherent sum of the currents at that port due to each of the port voltages.
- For example, the current at **port-3** is:
- Therefore we can generalize the current for N-port network as:

:
$$I_3 = Y_{34}V_4 + Y_{33}V_3 + Y_{32}V_2 + Y_{31}V_1$$

 $I_m = \sum_{n=1}^N Y_{mn}V_n$ \Rightarrow **I** = **YV**

Indraprastha Institute of Information Technology Delhi

The Admittance Matrix (contd.)

- Where I and V are $\mathbf{V} = [V_1, V_2, V_3, ..., V_N]^T$ $\mathbf{I} = [I_1, I_2, I_3, ..., I_N]^T$ vectors given as:
- The term **Y** is matrix given by:



The values of elements in the admittance matrix are frequency dependents and it is advisable to describe admittance matrix as:

$$\mathbf{Y}(\omega) = \begin{bmatrix} Y_{11}(\omega) & Y_{12}(\omega) & \dots & Y_{1n}(\omega) \\ Y_{21}(\omega) & & \vdots \\ \vdots & & & \\ Y_{m1}(\omega) & Y_{m2}(\omega) & \dots & Y_{mn}(\omega) \end{bmatrix}$$

Answer: Let us see if we can figure it out!



The Admittance Matrix (contd.)

• Recall that we can determine the inverse of a matrix. Denoting the matrix inverse of the admittance matrix as Y^{-1} , we find: I = YV

$$\Rightarrow \mathbf{Y}^{-1}\mathbf{I} = \mathbf{Y}^{-1}(\mathbf{Y}\mathbf{V}) \qquad \qquad \mathbf{Y}^{-1}\mathbf{I} = (\mathbf{Y}^{-1}\mathbf{Y})\mathbf{V} \qquad \qquad \mathbf{Y}^{-1}\mathbf{I} = \mathbf{V}$$

• We also know: $\mathbf{V} = \mathbf{Z}\mathbf{I}$ $\qquad \qquad \mathbf{Z} = \mathbf{Y}^{-1} \quad \mathbf{OR} \quad \mathbf{Y} = Z^{-1}$

Reciprocal and Lossless Networks

- We can classify multi-port devices or networks as either lossless or lossy; reciprocal or non-reciprocal. Let's look at each classification individually.
 Lossless Network
- A lossless network/device is simply one that cannot absorb power. This does not mean that the delivered power at every port is zero; rather, it means the total power flowing into the device must equal the total power exiting the device.
- A lossless device exhibits an impedance matrix with an interesting **property**. Perhaps not surprisingly, we find for a lossless device that the **elements** of its impedance matrix will be **purely reactive**:

 $Re(Z_{mn}) = 0$ For a lossless
device



Reciprocal and Lossless Networks

- If the device is lossy, then the elements of the impedance matrix must have at least one element with a real (i.e., resistive) component.
- Furthermore, we can similarly say that if the elements of an admittance matrix are all purely imaginary (i.e., Re{Y_{mn}} =0), then the device is lossless.

Reciprocal Network

- Ideally, most passive, linear microwave components will turn out to be reciprocal—regardless of whether the designer intended it to be or not!
- Reciprocity is a tremendously important characteristic, as it greatly simplifies an impedance or admittance matrix!
- Specifically, we find that a reciprocal device will result in a symmetric impedance and admittance matrix, meaning that:

$$Z_{mn} = Z_{nm}$$
 $Y_{mn} = Y_{nm}$ For a reciprocal device

• For example, we find for a reciprocal device that $Z_{23} = Z_{32}$, and $Y_{12} = Y_{21}$.

Indraprastha Institute of Information Technology Delhi

ECE321/521

Reciprocal and Lossless Networks (contd.)





EXAMPLE - 4 (contd.) Step-1: Place a short at port 2 $I_1 \rightarrow R = I_2 + I$

<u>Step-2</u>: Determine currents I_1 and I_2

 Note that after the short was placed at port 2, both resistors are in parallel, with a potential V₁ across each



• The current I_2 equals the portion of current I_1 through R but with opposite sign

$$I_2 = -\frac{V_1}{R}$$

Indraprastha Institute of Information Technology Delhi

ECE321/521

Example – 4 (contd.)

<u>Step-3</u>: Determine the trans-admittances Y_{11} and Y_{21}

$$Y_{11} = \frac{I_1}{V_1} = \frac{3}{2R}$$

$$Y_{21} = \frac{I_2}{V_1} = -\frac{1}{R}$$
Note that Y₂₁ is real and negative

This is **still** a valid physical result, **although** you will find that the **diagonal** terms of an impedance or admittance matrix (e.g., Y_{22} , Z_{11} , Y_{44}) will **always** have a real component that is **positive**

To find the **other two** trans-admittance parameters, we must **move** the short and then **repeat** each of our previous steps!



<u>Step-2</u>: Determine currents I_1 and I_2

 Note that after a short was placed at port 1, resistor 2R has zero voltage across it—and thus zero current through it!

Therefore:

Step-3:

Determine the trans-admittances Y_{12} and Y_{22}

 $Y_{12} = \frac{I_1}{V_2} = -\frac{1}{R}$

$$Y_{22} = \frac{I_2}{V_2} = \frac{1}{R}$$

Therefore the admittance matrix is:

 $\mathbf{Y} = \begin{bmatrix} 3/2R & -1/R \\ -1/R & 1/R \end{bmatrix}$ Is it lossless or reciprocal?



• determine all port **voltages** V₁, V₂, V₃ and all **currents** I₁, I₂, I₃.



Scattering Matrix

- At "low" frequencies, a linear device or network can be fully characterized using an impedance or admittance matrix, which relates the currents and voltages at each device terminal to the currents and voltages at all other terminals.
- But, at high frequencies, it is not feasible to measure total currents and voltages!
- Instead, we can measure the magnitude and phase of each of the two transmission line waves V⁺(z) and V⁻(z) → enables determination of relationship between the incident and reflected waves at each device terminal to the incident and reflected waves at all other terminals
- These relationships are completely represented by the scattering matrix that completely describes the behavior of a linear, multi-port device at a given frequency ω, and a given line impedance Z₀



 $V_{1}^{+}(z_{1})$

 $V_{1}^{-}(z_{1})$

ECE321/521

Scattering Matrix (contd.)

Note that we have now characterized transmission line activity in terms of incident and "reflected" waves. The negative going "reflected" waves can be viewed as the waves **exiting** the multi-port network or device.



Viewing transmission line activity this way, we can fully characterize a multi-port device by its scattering parameters!



Say there exists an incident wave on port 1 (i.e., V₁⁺ (z₁) ≠ 0), while the incident waves on all other ports are known to be zero (i.e., V₂⁺(z₂) =V₃⁺(z₃) =V₄⁺(z₄) =0).



Say we measure/determine the voltage of the wave flowing **into port 1**, at the port 1 **plane** (i.e., determine $V_1^+(z_1 = z_{1P})$).

Say we then measure/determine the voltage of the wave flowing **out** of **port 2**, at the port 2 plane (i.e., determine $V_2^{-}(z_2 = z_{2P})$).



The ratio between $V_1^+(z_1 = z_{1P})$ and $V_2^-(z_2 = z_{2P})$ is known as the scattering parameter S_{21}^-

Therefore:
$$S_{21} = \frac{V_2^-(z_2 = z_{2P})}{V_1^+(z_1 = z_{1P})} = \frac{V_2^- e^{+j\beta z_{2P}}}{V_1^+ e^{-j\beta z_{1P}}} = \frac{V_2^-}{V_1^+} e^{+j\beta(z_{2P}+z_{1P})}$$



Similarly:

$$S_{31} = \frac{V_3^-(z_3 = z_{3P})}{V_1^+(z_1 = z_{1P})}$$

$$S_{41} = \frac{V_4^-(z_4 = z_{4P})}{V_1^+(z_1 = z_{1P})}$$

- We of course could **also** define, say, scattering parameter S_{34} as the ratio between the complex values $V_3^{-}(z_3 = z_{3P})$ (the wave **out of** port 3) and $V_4^{+}(z_4 = z_{4P})$ (the wave **into** port 4), given that the input to all other ports (1,2, and 3) are zero
- more generally, the ratio of the wave incident on port n to the wave emerging from port m is:

$$S_{mn} = \frac{V_m^-(z_m = z_{mP})}{V_n^+(z_n = z_{nP})} \qquad V$$

$$V_k^+(z_k) = 0$$
 for all $k \neq n$

- Note that, frequently the port positions are assigned a **zero** value (e.g., $z_{1P}=0$, $z_{2P}=0$). This simplifies the scattering parameter calculation: $S_{mn} = \frac{V_m^-(z_m=0)}{V_n^+(z_n=0)} = \frac{V_m^+e^{+j\beta 0}}{V_n^-e^{-j\beta 0}} = \frac{V_m^+}{V_n^-}$
 - We will generally assume that the port locations are defined as z_{nP}=0, and thus use the above notation. But remember where this expression came from!

Indraprastha Institute of Information Technology Delhi

ECE321/521



Indraprastha Institute of Information Technology Delhi

ECE321/521

Scattering Matrix (contd.)

Obviously, there is **no way** that **both** statements can be correct!

Actually, **both** statements are correct! You must be careful to understand the **physical definitions** of the plus and minus directions—in other words, the propagation directions of waves $V_n^+(z_n)$ and $V_n^-(z_n)!$

For this current case, the situation is reversed. The wave incident on the load is now denoted as V_n⁻(z_n) (coming out of port n), while the wave reflected off the load is now denoted as V_n⁺(z_n) (going into port n).

• **back** to our discussion of **S-parameters**. We found that **if** $z_{nP} = 0$ for all ports n, the scattering parameters could be directly written in terms of wave **amplitudes** V_n^+ and V_m^-

$$S_{mn} = \frac{V_m^-}{V_n^+} \qquad V_k^+(z_k) = 0$$

for all $k \neq n$

• Which we can now **equivalently** state as:

$$S_{mn} = \frac{V_m^-}{V_n^+}$$
 (all ports, except port *n*, are terminated in matched loads)

 One more important note—notice that for the ports terminated in matched loads (i.e., those ports with no incident wave), the voltage of the exiting wave is also the total voltage!

For all

$$V_m(z_m) = V_m^+ e^{-j\beta z_m} + V_m^- e^{+j\beta z_m} = 0 + V_m^- e^{+j\beta z_m} = V_m^- e^{+j\beta z_m} \quad \text{terminated} \quad \text{ports!}$$

- We can use the scattering matrix to determine the solution for a more general circuit—one where the ports are **not** terminated in matched loads!
- Since the device is **linear**, we can apply **superposition**. The output at any port due to **all** the incident waves is simply the coherent **sum** of the output at that port due to **each** wave!
- For example, the **output** wave at port 3 can be determined by (assuming z_{nP} = 0):
- More generally, the output at port m of an N-port device is:

 $V_m^- = \sum S_{mn} V_n^+ \qquad \mathbf{z_{nP}} = \mathbf{0}$

 $V_{3}^{-} = S_{34}V_{4}^{+} + S_{33}V_{3}^{+} + S_{32}V_{2}^{+} + S_{31}V_{1}^{+}$

 This expression of Scattering parameter can be written in **matrix** form as:

 $V^- = SV^+$

$$\mathbf{V}^{-} = \mathbf{S}\mathbf{V}^{+}$$
Scattering Matrix
$$S = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1n} \\ S_{21} & & & \vdots \\ \vdots & & & \\ S_{m1} & S_{m2} & \dots & S_{mn} \end{bmatrix}$$

- The scattering matrix is N by N matrix that completely characterizes a linear, Nport device. Effectively, the scattering matrix describes a multi-port device the way that Γ_0 describes a single-port device (e.g., a load)!
- The values of the scattering matrix for a particular device or network, like Γ_0 , are frequency dependent! Thus, it may be more instructive to explicitly write:

$$S(\omega) = \begin{bmatrix} S_{11}(\omega) & S_{12}(\omega) & \dots & S_{1n}(\omega) \\ S_{21}(\omega) & & \vdots \\ \vdots & & & \\ S_{m1}(\omega) & S_{m2}(\omega) & \dots & S_{mn}(\omega) \end{bmatrix}$$

- Also realize that—also just like Γ_0 —the scattering matrix is dependent on **both** the **device/network** and the Z₀ value of the **TL connected** to it.
- Thus, a device connected to transmission lines with $Z_0 = 50\Omega$ will have a **completely different scattering matrix** than that same device connected to transmission lines with $Z_0 = 100\Omega$
- A device can be lossless or reciprocal. In addition, we can also classify it as being matched.
- Let's examine each of these three characteristics, and how they relate to the scattering matrix.