

ECE321/521

Lecture – 9

Date: 01.02.2017

- Even- and Odd-mode Analysis
- Generalized S-Parameters
- Example
- T-Parameters



Odd/Even Mode Analysis

Q: Although symmetric **circuits** appear to be plentiful in microwave engineering, it seems **unlikely** that we would often encounter symmetric **sources**. Do virtual shorts and opens typically ever occur?

A: One word—superposition!

If the elements of our circuit are **independent** and **linear**, we can apply superposition to analyze **symmetric circuits** when **non-symmetric** sources are attached.

ECE321/521

Odd/Even Mode Analysis (contd.)

 For example, we wish to determine the admittance matrix of this circuit. We would place a voltage source at port 1, and a short circuit at port 2—a set of asymmetric sources if there ever was one!



 Here's the really neat part. Actually the source on port 1 can be modelled as two equal voltage sources in series, whereas the source at port 2 can be modelled as two equal but opposite sources in series.



above circuit (due to the

sources) is obviously asymmetric—

no virtual ground, **nor** virtual short

is present. But, let's say we **turn off**

(i.e., set to V =0) the **bottom** source

on each side of the circuit:

ECE321/521

Odd/Even Mode Analysis (contd.)

Therefore equivalent an circuit is:

the

100Ω 100Ω 100Ω 100Ω V_s/2 (V_s/2 100Ω 100Ω $-V_{s}/2$ 100Ω 100Ω 100Ω 100Ω V_{s} V_{s} 100Ω 100Ω

Our **symmetry** has been **restored**! The symmetry plane is a **virtual open**.

 $V_s/2$

The circuit is referred to as its even mode, and analysis of it is known as the even **mode analysis**. The solutions are known as the even mode **currents** and **voltages**!

ECE321/521

Odd/Even Mode Analysis (contd.)

 Evaluating the resulting even mode half circuit we find:

$$I_1^e = \frac{V_s}{2} \frac{1}{200} = \frac{V_s}{400} = I_2^e$$



- Now, let's turn the bottom sources **back on**—but turn **off** the **top two**!
- We now have a circuit with odd symmetry—the symmetry plane is a virtual short!

This circuit is referred to as its **odd mode**, and analysis of it is known as the **odd mode analysis**.





Odd/Even Mode Analysis (contd.)

• Evaluating the resulting **odd mode** half circuit we find:

$$I_1^o = \frac{V_s}{2} \frac{1}{50} = \frac{V_s}{100} = -I_2^o$$



Q: But what good is this "even mode" and "odd mode" analysis? After all, the source on port 1 is $V_{s1} = V_s$, and the source on port 2 is $V_{s2} = 0$. What are the currents $I_1 = I_2$ for **these** sources?

A: Recall that these sources are the **sum** of the even and odd mode sources:

$$V_s = \frac{V_s}{2} + \frac{V_s}{2}$$

Second Source:

$$V_s = \frac{V_s}{2} - \frac{V_s}{2}$$

and thus—since all the devices in the circuit are linear—we know from superposition that the currents I₁ and I₂ are simply the sum of the odd and even mode currents !

$$I_{1} = I_{1}^{e} + I_{1}^{o}$$
$$I_{2} = I_{2}^{e} + I_{2}^{o}$$

ECE321/521



• And then the **admittance parameters** for this two port network is:

$$y_{11} = \frac{I_1}{V_{s1}} \Big|_{V_{s2}=0} = \frac{V_s}{80} \frac{1}{V_s} = \frac{1}{80}$$

$$y_{21} = \frac{I_2}{V_{s1}} \Big|_{V_{s2}=0} = -\frac{3V_s}{400} \frac{1}{V_s} = \frac{-3}{400}$$
And from the **symmetry** of the device we know: $y_{22} = y_{11} = \frac{1}{80}$

$$y_{12} = y_{21} = \frac{-3}{400}$$
Thus, the full **admittance matrix** is: $Y = \begin{bmatrix} 1/80 & -3/400\\ -3/400 & 1/80 \end{bmatrix}$

Odd/Even Mode Analysis (contd.)

- **Q:** What happens if **both** sources are **non-zero**? Can we use symmetry then?
- **A:** Absolutely! Consider this problem, where **neither** source is equal to zero:



 $V_{s1} + V_{s2}$

 V_{s2}

 $=\frac{V_{s1}-V_{s2}}{V_{s2}}$

 V_s^{e}

 $-V_s^{\prime}$

 In this case we can define an even mode and an odd mode source as:





Odd/Even Mode Analysis (contd.)

- We can then analyze the even mode circuit:
- 100Ω 100Ω I_1 100Ω 100Ω V_s^{e} V_{s}^{e} ໄ00Ω 100Ω 100Ω 100Ω *I*₁ 100Ω 100Ω 100Ω 100Ω $-V_s^o$ V_s^o
- And then the **odd mode** circuit:

And then combine these results in a **linear superposition**!

Odd/Even Mode Analysis (contd.)

Q: What about **current sources**? Can I likewise consider them to be a **sum** of an odd mode source and an even mode source?

A: Yes, but be very careful! The current of two source will add if they are placed in parallel—not in series! Therefore:





 One final word (I promise!) about circuit symmetry and even/odd mode analysis: precisely the same concept exits in electronic circuit design!



Specifically, the **differential** (odd) and **common** (even) **mode** analysis of bilaterally symmetric electronic circuits, such as **differential amplifiers**!



Example – 1

• Carefully (very carefully) consider the symmetric circuit below:



Use odd-even mode analysis to determine the value of voltage V_1 .







Generalized Scattering Parameters (contd.)

Yikes! You said the s-parameters are **dependent** on transmission line characteristic impedance Z₀. If these values are **different** for each port, **which** Z₀ do we use?

For this **general** case, we must use **generalized scattering parameters**! First, we define a slightly new form of complex wave amplitudes

$$a_n = \frac{V_n^+}{\sqrt{Z_{0n}}} \qquad b_n =$$

• <u>The key things to note are:</u>

D

variable a (e.g., a₁,a₂, ...) denotes the complex amplitude of an **incident (i.e., plus)** wave.

variable b (e.g., a₁,a₂, ...) denotes the complex amplitude of an **exiting (i.e., minus)** wave.

We now get to rewrite all our transmission line knowledge in terms of these generalized complex amplitudes!



Indraprastha Institute of ECE321/521 Information Technology Delhi Generalized Scattering Parameters (contd.) First, our two propagating wave amplitudes $V_n^+ = a_n \sqrt{Z_{0n}}$ $V_n^- = b_n \sqrt{Z_{0n}}$ Therefore: $V_n^+(z_n) = a_n \sqrt{Z_{0n}} \cdot e^{-j\beta z_n}$ $V_n^-(z_n) = b_n \sqrt{Z_{0n}} \cdot e^{+j\beta z_n}$ $\Gamma(z_n) = \frac{b_n}{a_n} e^{+j2\beta z_n}$ • Similarly, the total voltage, current, and $V_{n}(z_{n}) = \sqrt{Z_{0n}} \left(a_{n} \cdot e^{-j\beta z_{n}} + b_{n} e^{+j\beta z_{n}} \right)$ impedance at the **nth** port are: $I_{n}(z_{n}) = \frac{\left(a_{n} \cdot e^{-j\beta z_{n}} - b_{n} e^{+j\beta z_{n}}\right)}{\sqrt{Z_{n}}}$ $Z(z_n) = \frac{a_n \cdot e^{-j\beta z_n} + b_n e^{+j\beta z_n}}{a \cdot e^{-j\beta z_n} - b \cdot e^{+j\beta z_n}}$ Assuming that our port planes are defined with $V_n \doteq V_n (z_n = 0) = \sqrt{Z_{0n} (a_n + b_n)}$ $z_{nP} = 0$, we can determine the total voltage, current, and impedance **at port n** as:



Generalized Scattering Parameters (contd.)

• Similarly, the **power** associated with each wave is:

$$P_n^+ = \frac{\left|V_n^+\right|^2}{2Z_{0n}} = \frac{\left|a_n\right|^2}{2}$$

$$P_n^- = \frac{\left|V_n^-\right|^2}{2Z_{0n}} = \frac{\left|b_n\right|^2}{2}$$

 As such, the power delivered to port n (i.e., the power absorbed by port n) is:

$$P_{n} = P_{n}^{+} - P_{n}^{-} = \frac{|a_{n}|^{2} - |b_{n}|^{2}}{2}$$

So what's the **big deal**? This is yet **another way** to express transmission line activity.

Do we **really** need to know this, or is this simply a strategy for making the next quiz **even harder**?

- You may have noticed that this notation (a_n, b_n) provides descriptions that are a bit "cleaner" and more symmetric between current and voltage.
- However, the main reason for this notation is for evaluating the scattering parameters of a device with dissimilar transmission line impedance (e.g., $Z_{01} \neq Z_{02} \neq Z_{03} \neq Z_{04}$).

ECE321/521

Generalized Scattering Parameters (contd.)

• For these cases we must use generalized scattering parameters:

$$S_{mn} = \frac{V_m^-}{V_n^+} \frac{\sqrt{Z_{0n}}}{\sqrt{Z_{0m}}} \qquad \text{when } V_k^+(z_k) = 0 \text{ for}$$

all $k \neq n$



ECE321/521

Generalized Scattering Parameters (contd.)

 generalized s-parameters can be more compactly written in terms of our new wave amplitude notation:



generalized form of scattering parameter—**always** provides the correct answer, **regardless** of the values of Z_{0m} or Z_{0n}!

But why can't we define the scattering parameter as S_{mn} =V_m⁻/V_n⁺, regardless of Z_{0m} or Z_{0n}?? Who says we must define it with those awful Z_{0n} values in there?

Recall that a lossless device will **always** have a **unitary** scattering matrix. As a result, the scattering parameters of a lossless device will **always** satisfy, for example:

 $\sum |S_{mn}|$

This is true only if generalized scattering parameters are used The scattering parameters of a lossless device will form a unitary matrix **only** if defined as $S_{mn} = b_m/a_n$. If we use $S_{mn} = V_m^-/V_n^+$, the matrix will be unitary **only** if the connecting transmission lines have the **same** characteristic impedance.



Example – 2

 let's consider a perfect connector—an electrically very small two-port device that allows us to connect the ends of different transmission lines together.



Determine the S-matrix of this ideal connector:

- 1. First case: it connects two transmission lines with same characteristic impedance of Z_0 .
- 2. Second case: it connects two transmission lines with characteristic impedances of Z_{01} and Z_{02} respectively.



Shifting of Planes

- It is not often easy or feasible to match network ports for determination of Sparameters → in such a situation S-parameters are determined through transmission lines of finite length.
- Let us consider a 2-port network to understand these situations.





Shifting of Planes (contd.)

• The equations can be combined to form following matrix

 $\begin{cases} V_{in}^{+}(-l_{1}) \\ V_{out}^{+}(-l_{2}) \end{cases} = \begin{bmatrix} e^{-j\beta_{1}l_{1}} & 0 \\ 0 & e^{-j\beta_{2}l_{2}} \end{bmatrix} \begin{cases} V_{1}^{+} \\ V_{2}^{+} \end{cases}$ Links the incident waves at the network ports shifted by TL segments

 $\begin{cases} V_{in}^{-}(-l_{1}) \\ V_{out}^{-}(-l_{2}) \end{cases} = \begin{bmatrix} e^{+j\beta_{1}l_{1}} & 0 \\ 0 & e^{+j\beta_{2}l_{2}} \end{bmatrix} \begin{cases} V_{1}^{-} \\ V_{2}^{-} \end{cases}$ Links the incident waves at the network ports shifted by TL segments

- We can also deduce that S-parameters are linked to the generalized coefficients a_n and b_n (which in turn can be expressed through voltages) through following $\begin{cases} V_1^- \\ V_2^- \end{cases} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{cases} V_1^+ \\ V_2^+ \end{cases}$ expressions (if we assume $Z_{01} = Z_{02}$)
 - Simplification of these three matrix expression results in:

$$\begin{cases} V_{in}^{-}(-l_{1}) \\ V_{out}^{-}(-l_{2}) \end{cases} = \begin{bmatrix} e^{+j\beta_{1}l_{1}} & 0 \\ 0 & e^{+j\beta_{2}l_{2}} \end{bmatrix} \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} e^{+j\beta_{1}l_{1}} & 0 \\ 0 & e^{+j\beta_{2}l_{2}} \end{bmatrix} \begin{cases} V_{in}^{+}(-l_{1}) \\ V_{out}^{+}(-l_{2}) \end{cases}$$

S-parameters of the shifted network [S]^{SHIFT}



Shifting of Planes (contd.)

$$\begin{bmatrix} S \end{bmatrix}^{SHIFT} = \begin{bmatrix} S_{11}e^{+j2\beta_{1}l_{1}} & S_{12}e^{+j(\beta_{1}l_{1}+\beta_{2}l_{2})} \\ S_{21}e^{+j(\beta_{1}l_{1}+\beta_{2}l_{2})} & S_{22}e^{+j2\beta_{2}l_{2}} \end{bmatrix}$$
 Physical Meaning (S₁₁) reveals that we have to take into account twice the travel time for

The first term (S₁₁) reveals that we have to take into account twice the travel time for the incident voltage to reach port-1 and, upon reflection, return to the end of the TL segment. Similarly for S₂₂ at port-2. The cross terms (S₁₂ and S₂₁) require additive phase shifts associated with TL segments at port-1 and port-2





The Transmission Matrix (contd.)

$$\begin{bmatrix} V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DI_2 \end{bmatrix}$$

- Similar to the impedance and admittance matrices, we determine the elements of the transmission matrix using shorts and opens.
 - Note when I₂ = 0 then: V₁ =AV₂
 Note when V₂ = 0 then: V₁ =BI₂
 Note when I₂ = 0 then: I₁ =CV₂
 Note when V₂ = 0 then: I₁ =DI₂
 Note when V₂ = 0 then: I₁ =DI₂ $D = \frac{I_1}{I_2}$ A is unitless (i.e., it is a coefficient)
 B has unit of impedance (i.e., Ohms)
 Note when V₂ = 0 then: I₁ =DI₂
 D is unitless (i.e., it is a coefficient)

ECE321/521

The Transmission Matrix (contd.)

Crying out loud! We already have the impedance matrix, the scattering matrix, and the admittance matrix. Why do we need the transmission matrix? Is it somehow uniquely useful?



Let us consider the case where a 2-port network is created by connecting (i.e., cascading) two networks:







The Transmission Matrix (contd.)

• Combining the first two equations we get:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \boldsymbol{T}_A \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \boldsymbol{T}_A \boldsymbol{T}_B \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

• Combining this combined relationship to the third we get:

$$\begin{cases} \boldsymbol{V}_1 \\ \boldsymbol{I}_1 \end{cases} = \boldsymbol{T}_{\boldsymbol{A}} \begin{cases} \boldsymbol{V}_2 \\ \boldsymbol{I}_2 \end{cases} = \boldsymbol{T}_{\boldsymbol{A}} \boldsymbol{T}_{\boldsymbol{B}} \begin{cases} \boldsymbol{V}_3 \\ \boldsymbol{I}_3 \end{cases} = \boldsymbol{T} \begin{cases} \boldsymbol{V}_3 \\ \boldsymbol{I}_3 \end{cases}$$

 Similarly, for N cascaded networks, the total transmission matrix T can be determined as the product of all N networks!

$$T = T_1 T_2 T_3 \dots T_N = \prod_{n=1}^N T_n$$

- Note this result is only true for the transmission matrix T. No equivalent result exists for S ,Z ,Y !
- Thus, the transmission matrix can greatly simplify the analysis of complex networks constructed from two-port devices. We find that the T matrix is particularly useful when creating design software for CAD applications.