
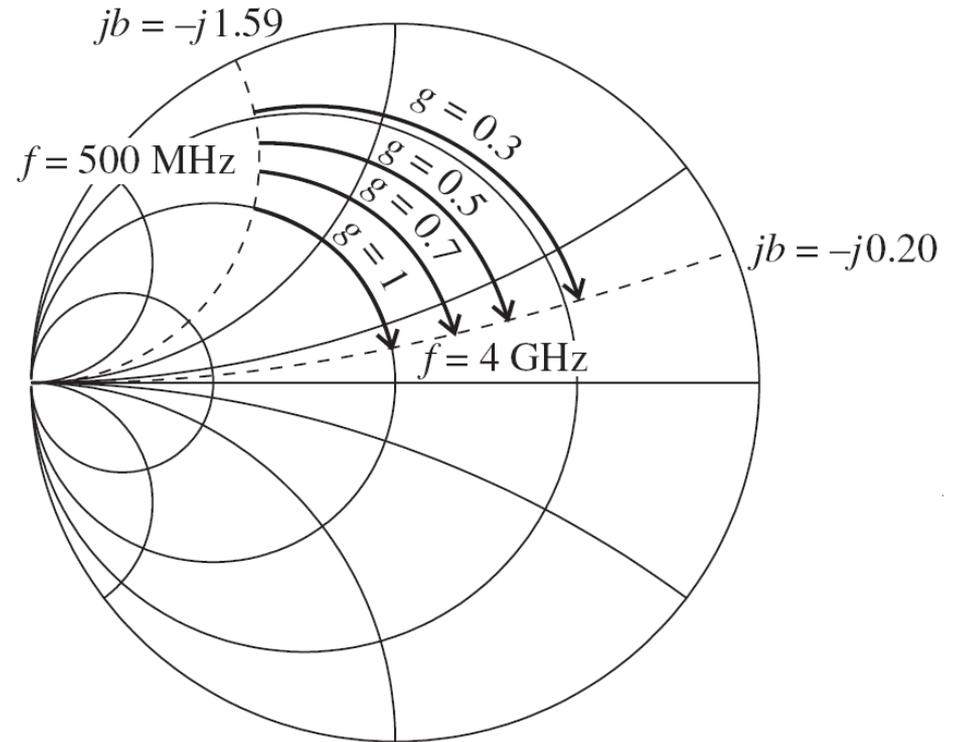




HA # 2

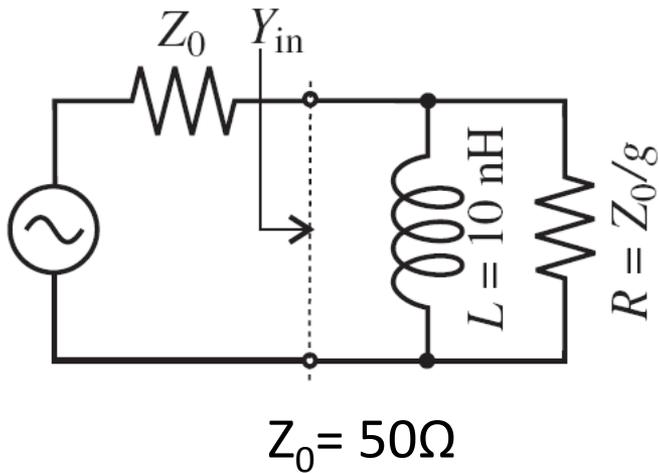Part-1: For the parallel connection of R and L, demonstrate using MATLAB and ADS:





HA # 2

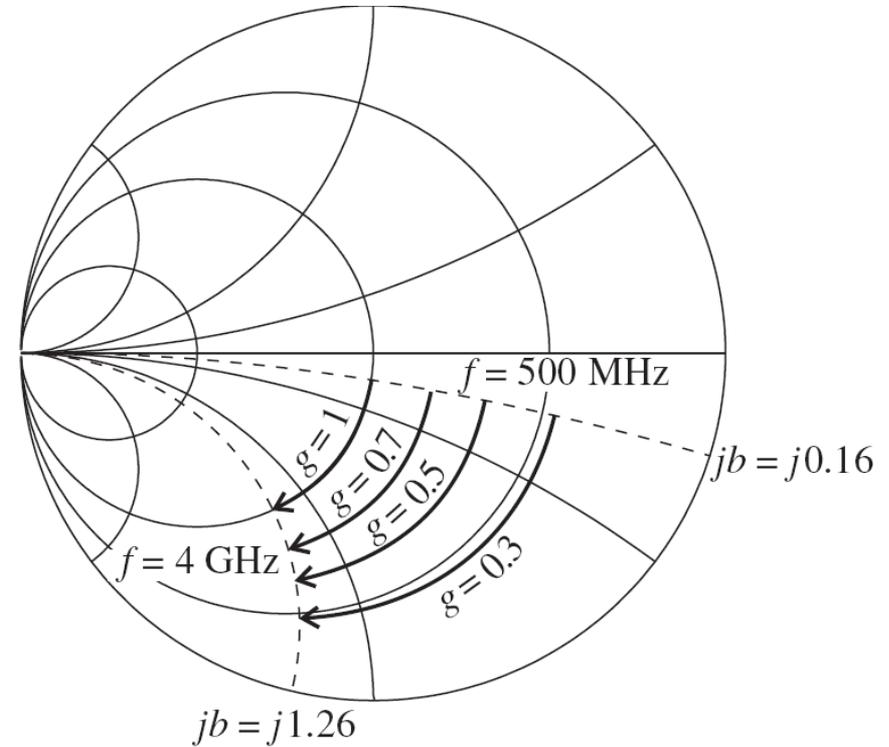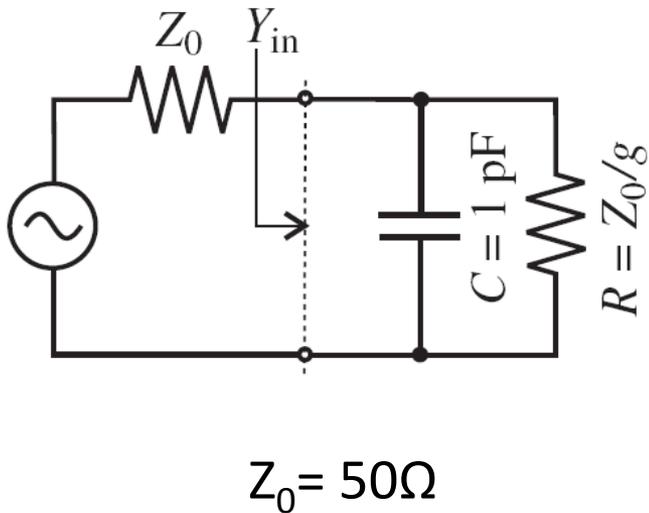Part-2: For the parallel connection of R and C, demonstrate using MATLAB and ADS:





HA # 2

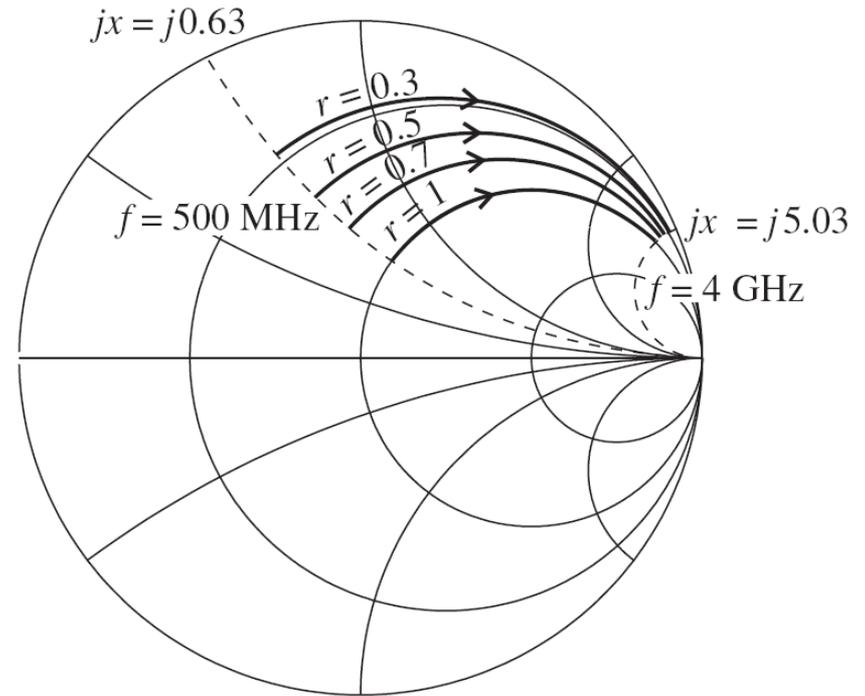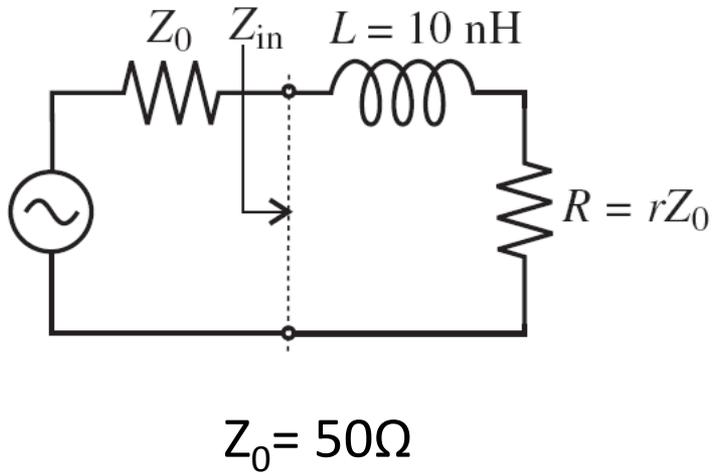Part-3: For the series connection of R and L, demonstrate using MATLAB and ADS:




HA # 2

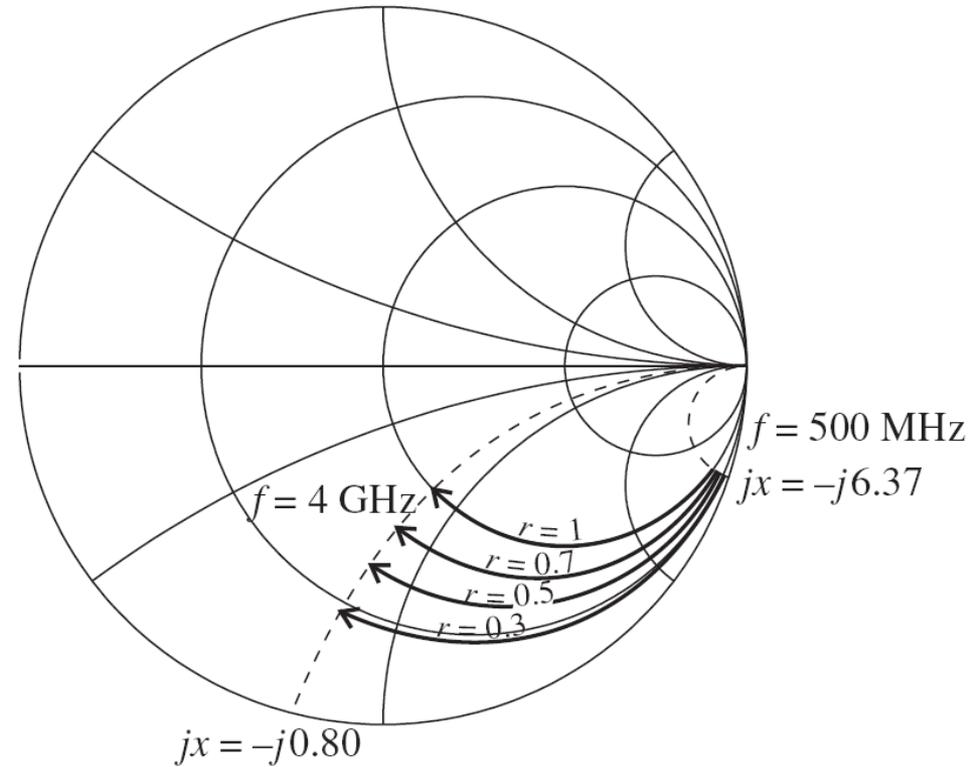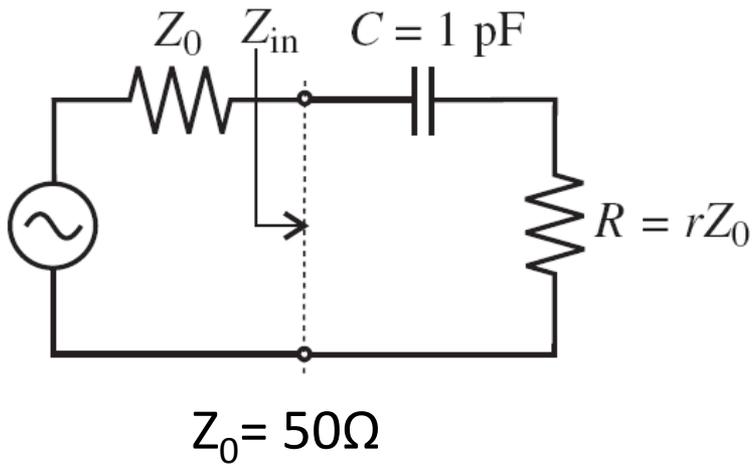Part-4: For the series connection of R and C, demonstrate using MATLAB and ADS:



HA # 2

Part-5: Consider the following circuit:

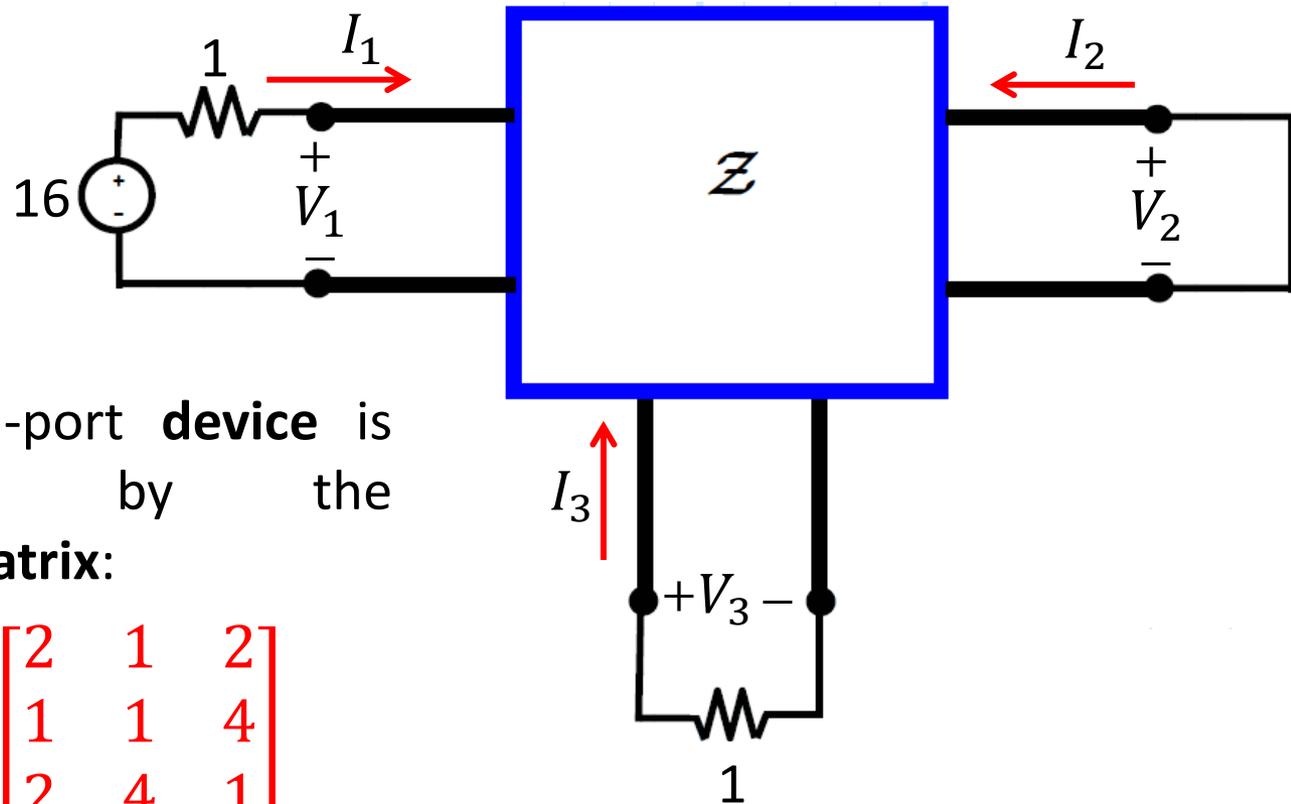

- Where the 3-port **device** is characterized by the **impedance matrix**:

$$\mathbf{Z} = \begin{bmatrix} 2 & 1 & 2 \\ 1 & 1 & 4 \\ 2 & 4 & 1 \end{bmatrix}$$

determine all port **voltages** V_1 , V_2 , V_3 and all **currents** I_1 , I_2 , I_3 .

HA # 2

Part-6: determine the scattering matrix of this two-port device:

