

## Lecture – 12


Date: 13.09.2014

- The Signal Flow Graph

## Signal Flow Graph

**Q:** Using individual device scattering parameters to analyze a complex microwave network results in a lot of **messy** math! Isn't there an **easier** way?

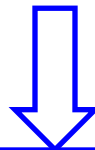**A:** Yes! We can represent a microwave network with its **signal flow graph** and then decompose this graph using a standard set of rules → **results into simpler analysis.**




It provides a sort of a **graphical** way to do algebra!



Signal Flow Graph (SFG) can also help us understand the fundamental **physical behavior** of a network or device. It can even help us **approximate** the network in a way that makes it simpler to analyze and/or design!
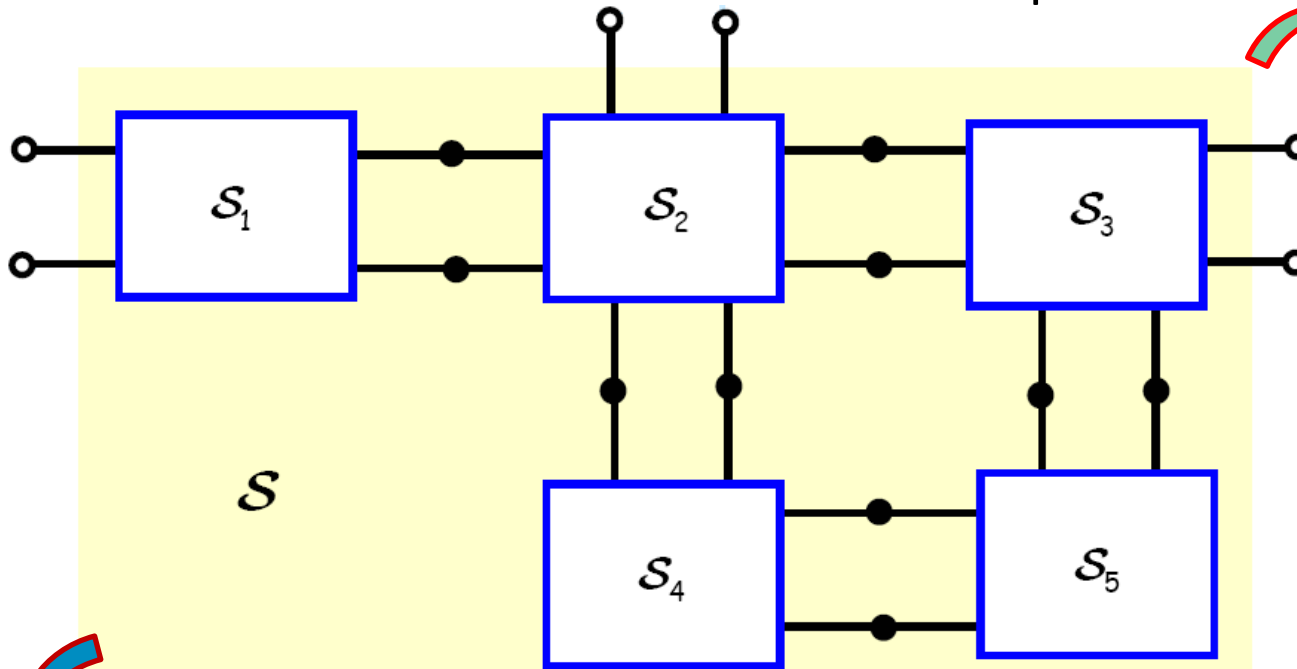
## Signal Flow Graph (contd.)

- To understand the significance of SFG, let us consider a complex **3-port** microwave network constructed of **5** simpler microwave devices



$S_n$  is the **scattering matrix** of each device, and **S** is the **overall scattering matrix** of the **entire 3-port network**

The S-parameter (S) of the whole network can be obtained from the knowledge of S-parameter of individual devices

**Tedious Algebra!**

**Alternative is SFG based solution!**

## Signal Flow Graph (contd.)

### Signal flow graphs are helpful in three ways!

**Way 1** – It provide us with a **graphical** means of **solving** large systems of simultaneous equations.

**Way 2** – We'll see that it can provide us with a **road map** of the wave **propagation paths** throughout a HF device or network. If we're paying attention, we can glean great **physical insight** as to the inner working of the device represented by the graph.

**Way 3** – It provide us with a quick and accurate method for **approximating** a network or device. We will find that we can often replace a rather complex graph with a much **simpler** one that is **almost** equivalent.




We find this to be very helpful when **designing** microwave components. From the analysis of these approximate graphs, we can often determine **design rules** or equations that are tractable, and allow us to design components with (near) optimal performance.

## Signal Flow Graph (contd.)
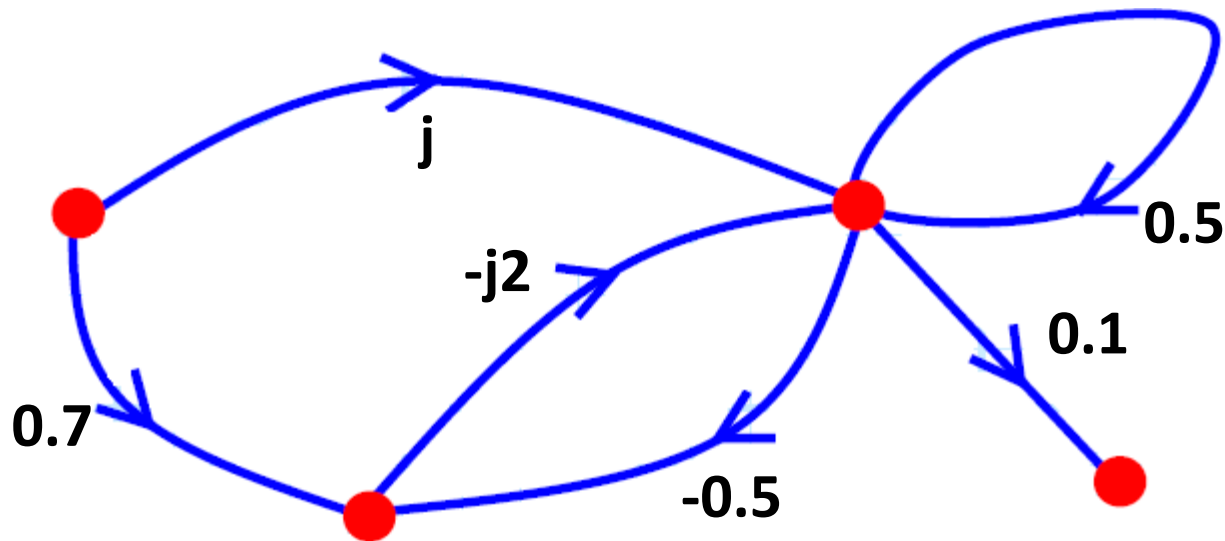
### Some definitions!

Every SFG consists of a set of **nodes**. These nodes are connected by **branches**, which are simply contours with a specified **direction**. Similarly, each branch has an associated complex **value**.



**Q:** What could this possibly have to do with **RF/microwave engineering**?

## Signal Flow Graph (contd.)

- In high frequency applications, each **port** of a device is represented by **two nodes**—the “a” node and the “b” node. The “a” node simply represents the value of the **normalized amplitude** of the wave incident on that port, evaluated **at** the plane of that port:

$$a_n = \frac{V_n^+ (z_n = z_{nP})}{\sqrt{Z_{0n}}}$$

- Similarly, the “b” node simply represents the **normalized amplitude** of the wave **exiting** that port, evaluated **at** the plane of that port:


$$b_n = \frac{V_n^- (z_n = z_{nP})}{\sqrt{Z_{0n}}}$$

- Note then that the **total voltage** at a port is simply:

$$V_n (z_n = z_{nP}) = (a_n + b_n) \sqrt{Z_{0n}}$$
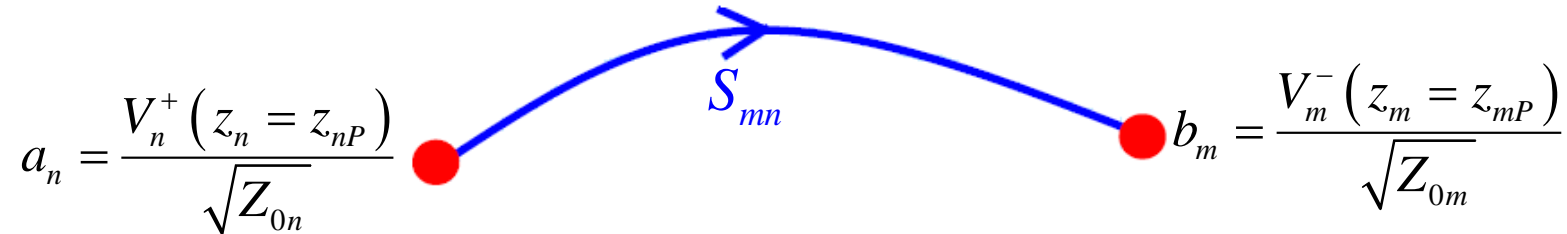
## Signal Flow Graph (contd.)


- The value of the **branch** connecting two nodes is simply the value of the **scattering parameter** relating these two voltage values.



- The signal flow graph above is simply a **graphical** representation of the equation:

$$b_m = a_n S_{mn}$$

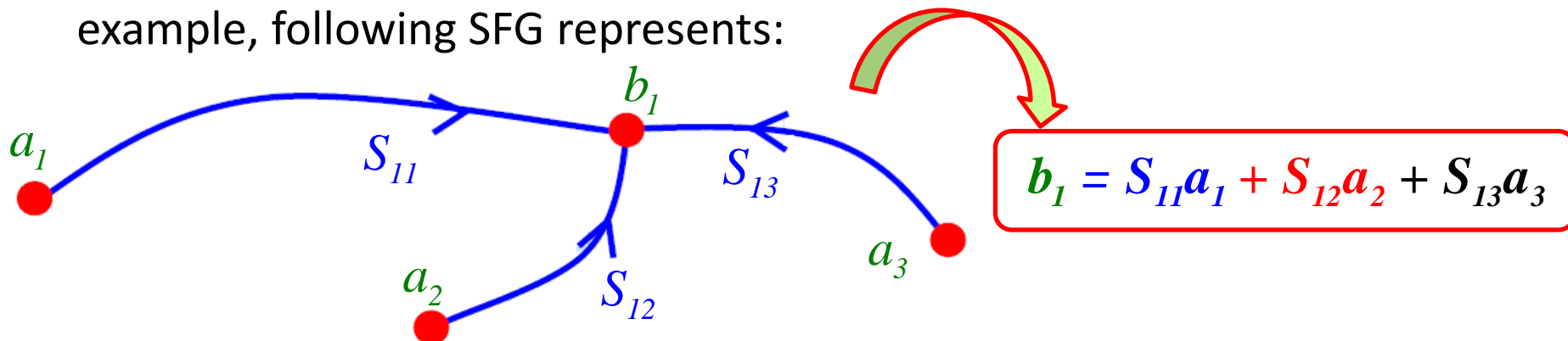- Moreover, if **multiple** branches enter a node, then the voltage represented by that node is the **sum** of the values from each branch. For example, following SFG represents:



## Signal Flow Graph (contd.)

- Now, consider a **two-port device** with a scattering matrix **S**:


$$S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

So that:

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

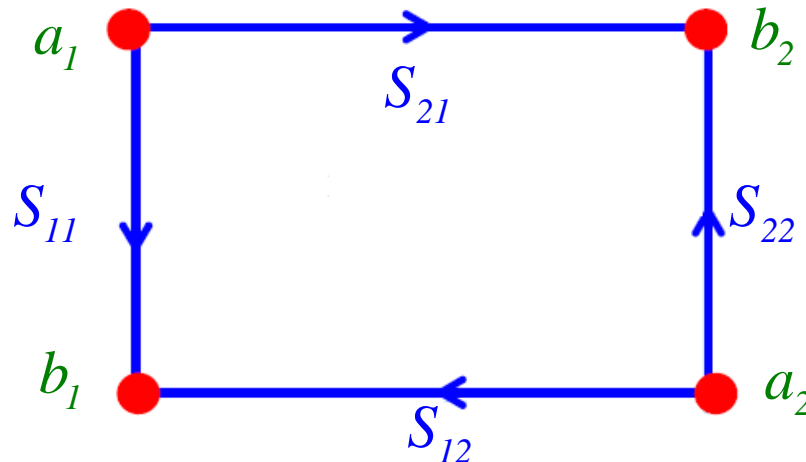
- We can then **graphically** represent a **two-port device** as:




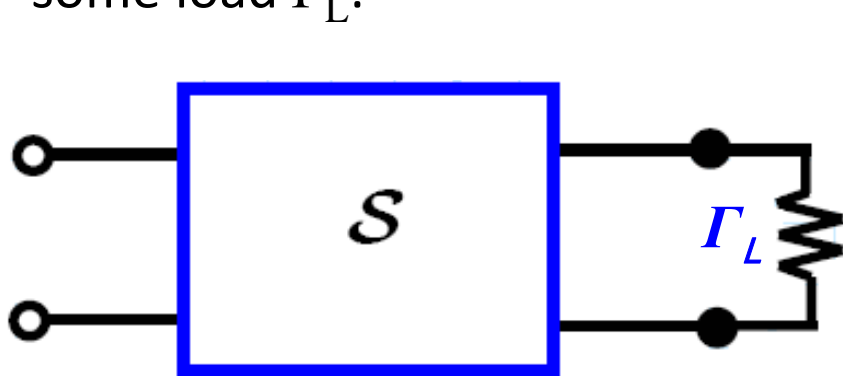
## Signal Flow Graph (contd.)

- Now, consider a two-port device where the second port is **terminated** by some load  $\Gamma_L$ :




**Additional  
Equation**

$$V_2^+ (z_2 = z_{2P}) = \Gamma_L V_2^- (z_2 = z_{2P})$$


$$\Rightarrow a_2 = \Gamma_L b_2$$

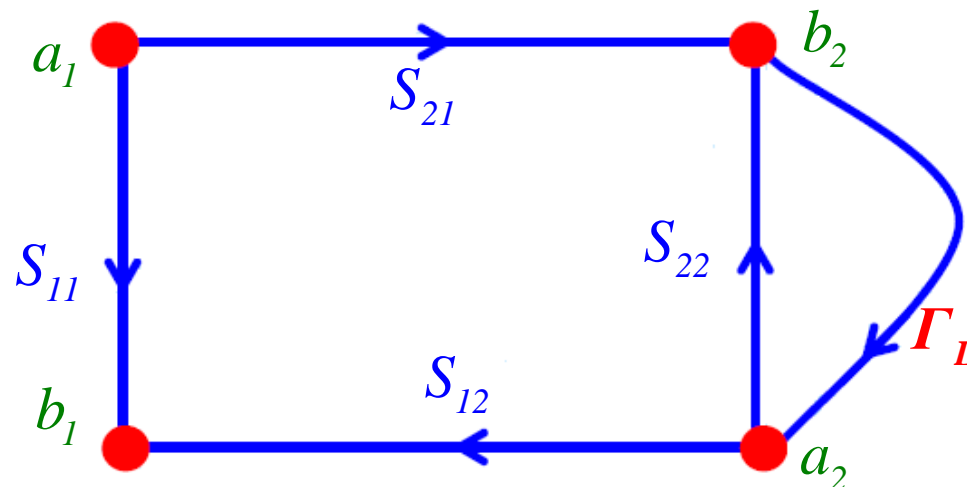- Therefore, the signal flow graph of this **terminated** network is:



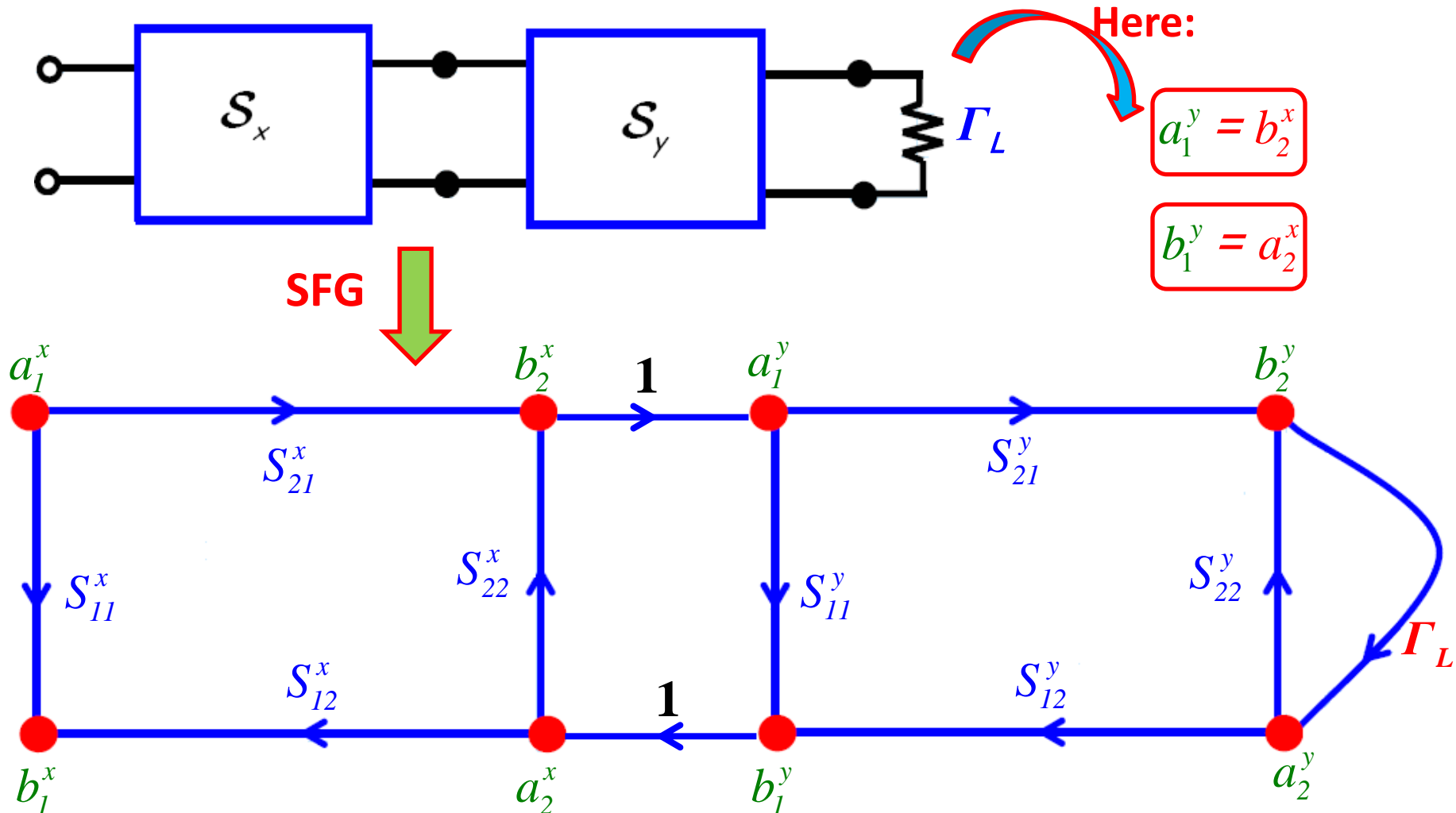
## Signal Flow Graph (contd.)

- Now consider cascading of **two different** two-port networks



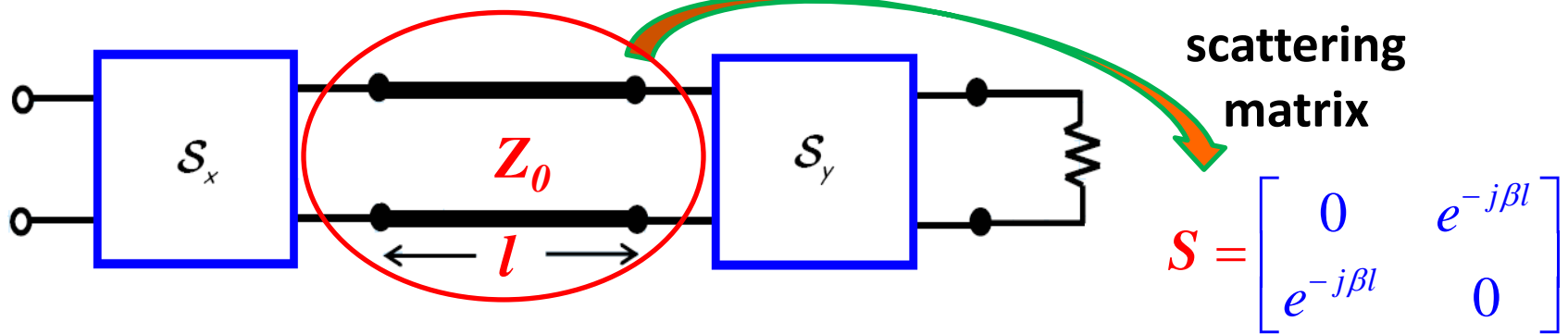
## Signal Flow Graph (contd.)


- Now consider networks connected with a transmission line segment:



SFG

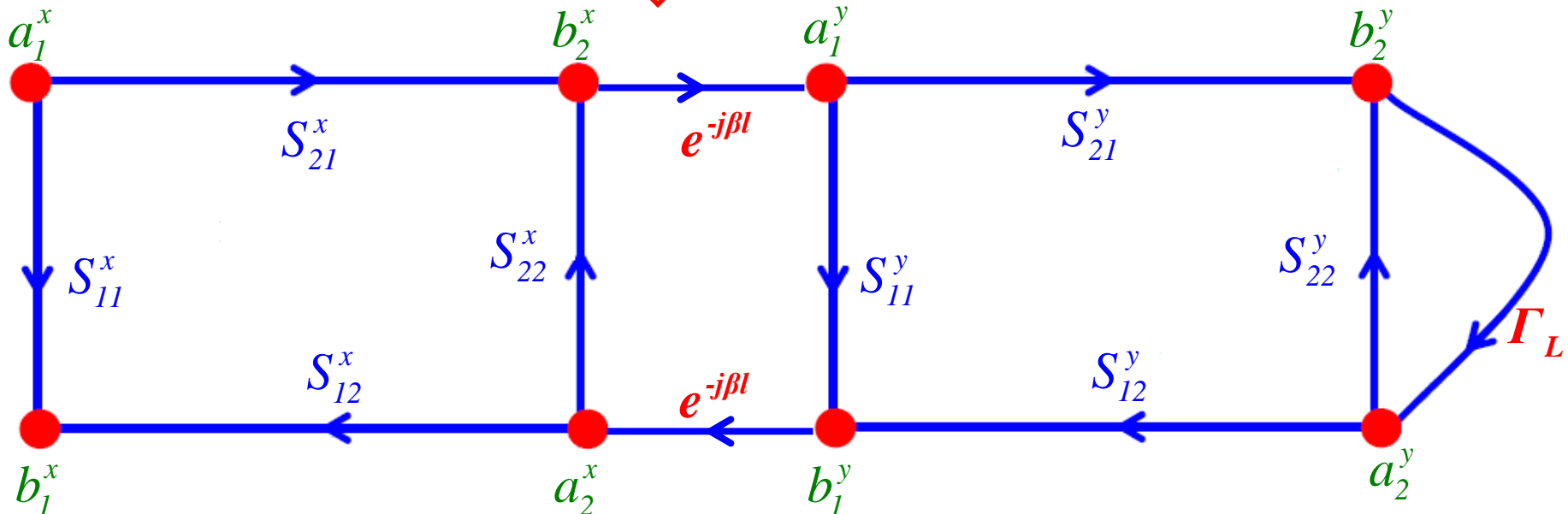

## Signal Flow Graph (contd.)

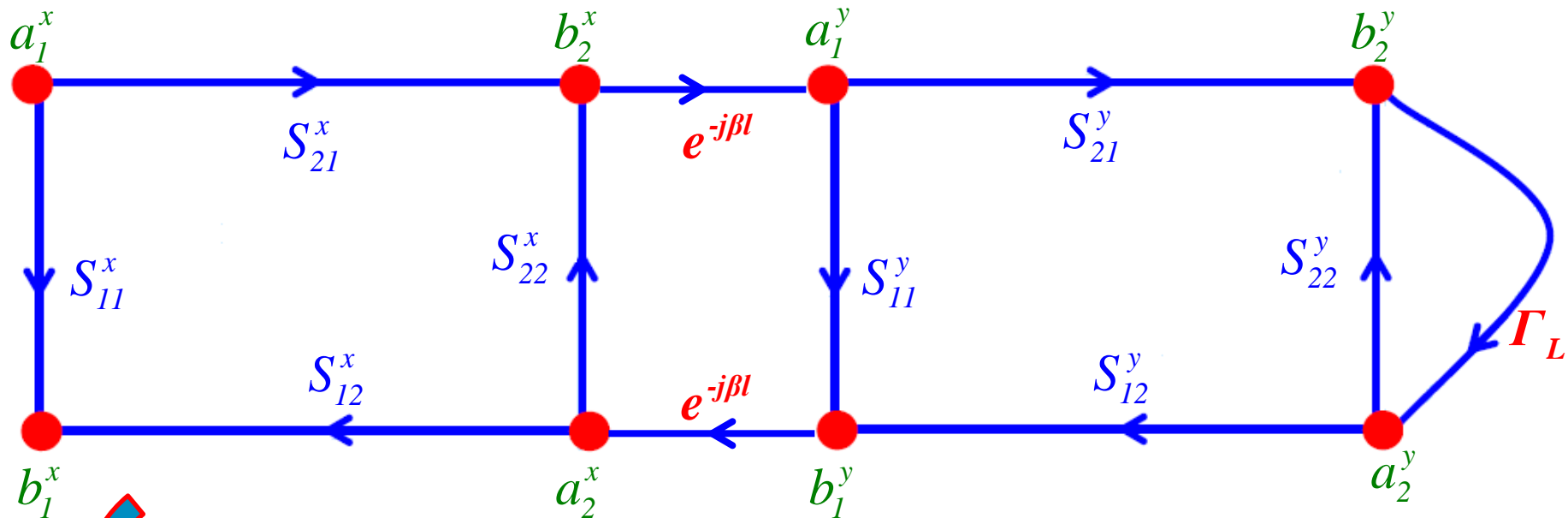

Note that there is **one (and only one!)** independent variable in this graphical representation (i.e., SFG)  $\rightarrow a_1^x$

This is the only node of the SFG that does **not** have any **incoming** branches. As a result, its value depends on **no other** node values in the SFG

**Independent nodes in the SFG are called sources!**

## Signal Flow Graph (contd.)



Independent nodes in the SFG are called sources!

- This makes sense physically (do **you** see why?)
- The node value  $a_1^x$  represents the complex amplitude of the wave **incident** on the one-port network. If this value is **zero**, then **no power** is incident on the network—the rest of the nodes (i.e., wave amplitudes) will be **zero**!

Now, say we wish to determine, for example:

1. The **reflection coefficient**  $\Gamma_{in}$  of the one-port device
2. The **total current** at port 1 of second network (i.e., network **y**)
3. The **power absorbed** by the load at port 2 of the **second (y) network**.

## Signal Flow Graph (contd.)

- In the first case, we need to determine the value of dependent node  $b_1^x$ :

$$\Gamma_{in} = \frac{b_1^x}{a_1^x}$$

- For the second case, we must determine the value of wave amplitudes  $a_1^y$  and  $b_1^y$ :

$$I_1^y = \frac{a_1^y - b_1^y}{\sqrt{Z_0}}$$

- For the third and final case, the values of nodes  $a_2^y$  and  $b_2^y$  are required:

$$P_{abs} = \frac{|b_2^y|^2 - |a_2^y|^2}{2}$$

How do we **determine** the values of these wave amplitude “nodes”?

solve the **simultaneous equations** that describe this network.

**Decompose (reduce)** the SFG!

## Signal Flow Graph (contd.)

- SFG **reduction** is a method for **simplifying** the **complex** paths of that SFG into a more **direct (but equivalent!)** form.
  - Reduction is really just a **graphical** method of **decoupling** the simultaneous equations that are **described** by the SFG.
- SFGs can be reduced by applying one of **four simple rules**.

**Q:** Can these rules be applied in **any order**?

**A: YES!** The rules can only be applied when/where the structure of the SFG allows. You must **search** the SFG for structures that allow a rule to be applied, and the SFG will then be (a little bit) reduced. You then search for the **next** valid structure where a rule can be applied. Eventually, the SFG will be **completely reduced!**

It's a bit like solving a **puzzle**. Every SFG is different, and so each requires a different reduction procedure. It requires a little **thought**, but with a little practice, the reduction procedure can be **easily** mastered → **You may find its kind of a fun! (TRUST ME)**


## Signal Flow Graph (contd.)

### Series Rule

- Consider these two complex equations:  $b_1 = \alpha a_1$        $a_2 = \beta b_1$
- These two equations can be combined to form an **equivalent set** of equations:

$$b_1 = \alpha a_1 \qquad a_2 = \beta b_1 = \beta(\alpha a_1) = \alpha\beta a_1$$

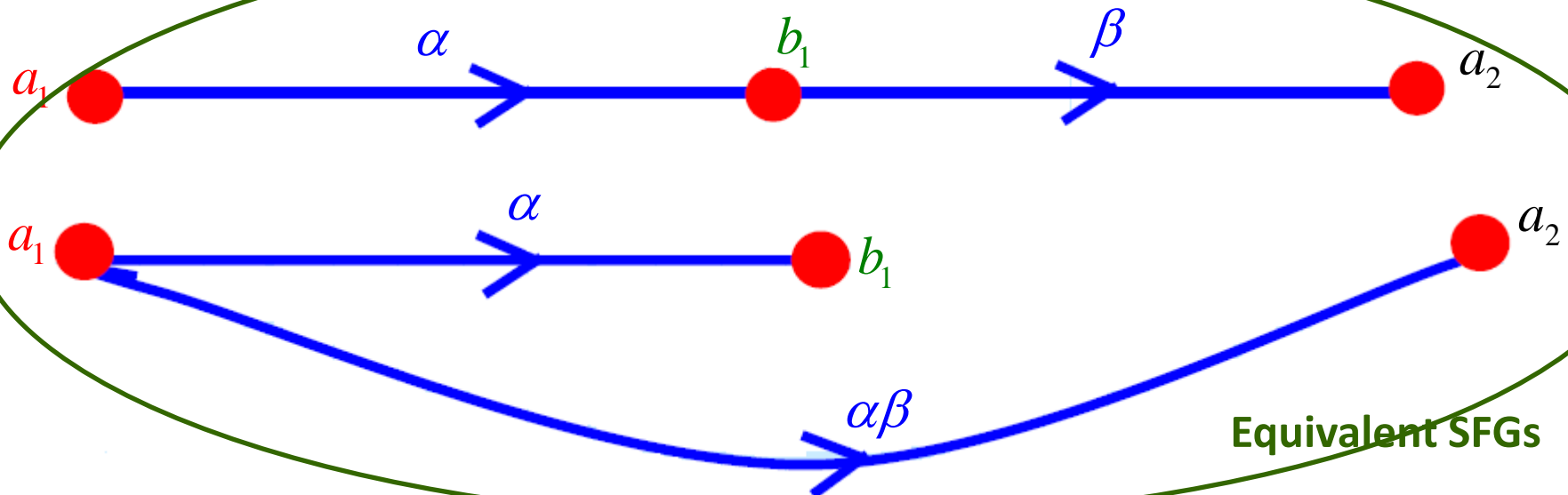- Graphically they can be represented as:






## Signal Flow Graph (contd.)

This last discussion leads us to our **first SFG reduction rule**:

### Rule 1 - Series Rule

If a node has **one** (and only one!) incoming branch, and **one** (and only one!) outgoing branch, the node can be eliminated and the two branches can be combined, with the new branch having a value equal to the product of the original two.


### Example:

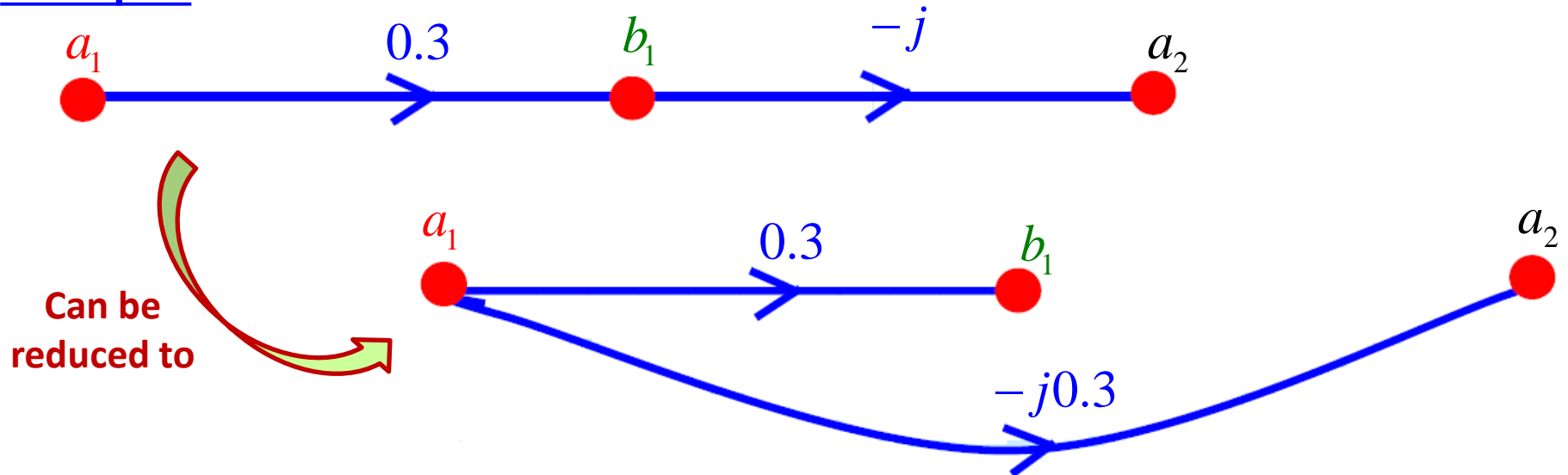

## Signal Flow Graph (contd.)
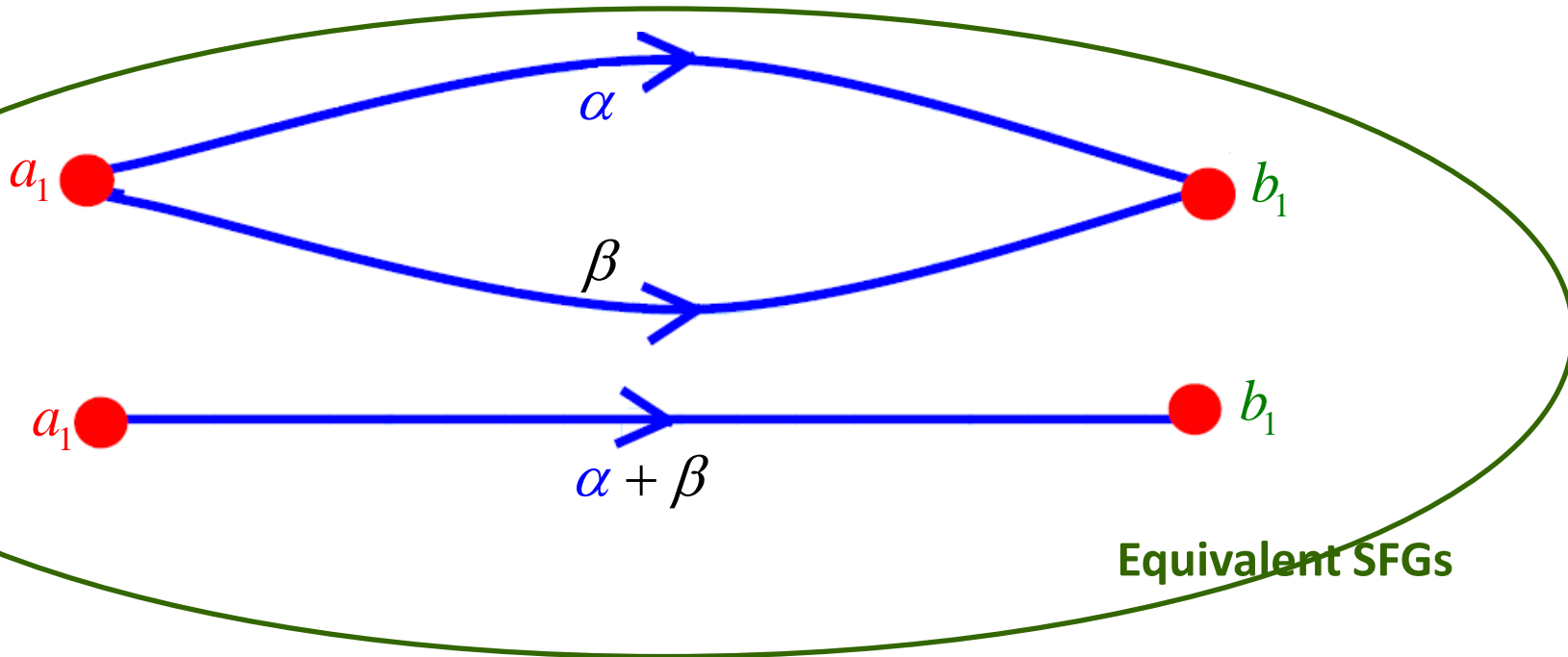
### Parallel Rule

- Consider these two complex equations:  $b_1 = \alpha a_1 + \beta a_1$
- The equation can also be expressed as:  $b_1 = (\alpha + \beta) a_1$
- These equations can be expressed in terms of SFG as:




## Signal Flow Graph (contd.)

This last discussion leads us to our **second SFG reduction rule**:

### Rule 2 - Parallel Rule


If two nodes are connected by parallel branches—and the branches have the **same direction**—the branches can be combined into a single branch, with a value equal to the **sum** of each two original branches.

### Example:

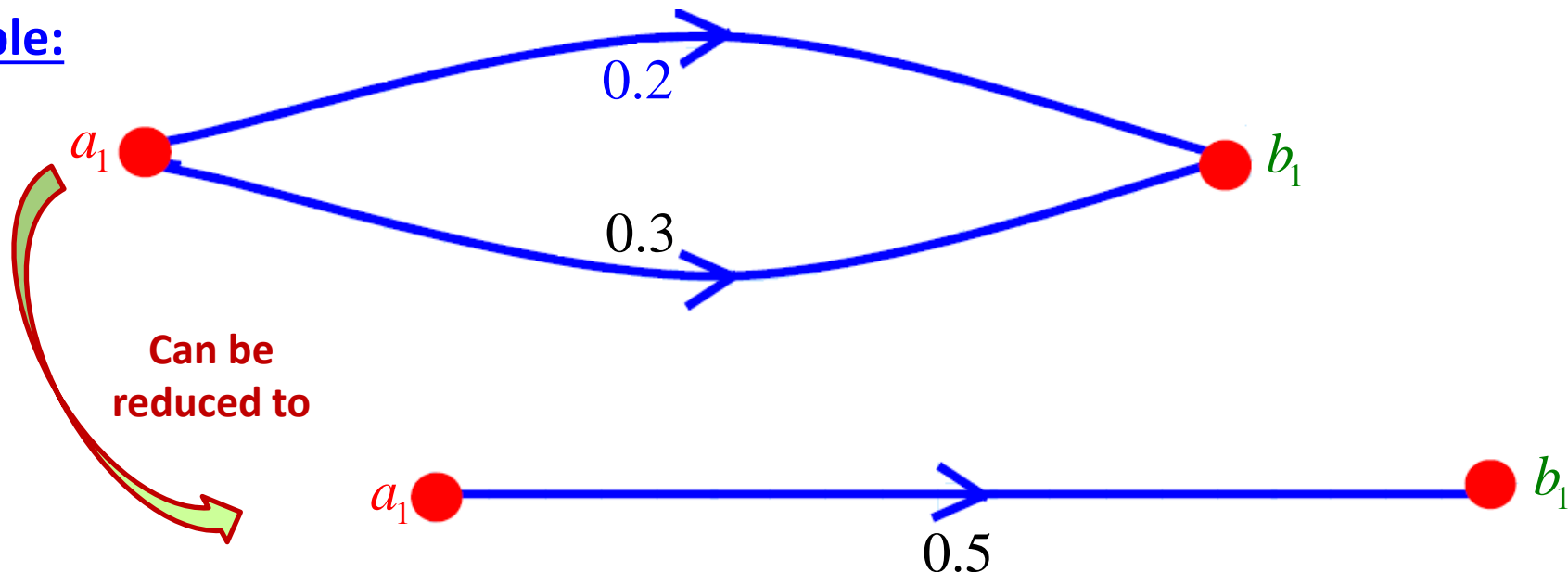


## Signal Flow Graph (contd.)


What about **this** signal flow graph?

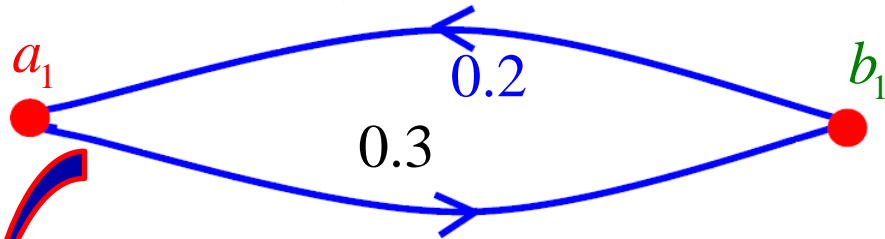


Can it be transformed into

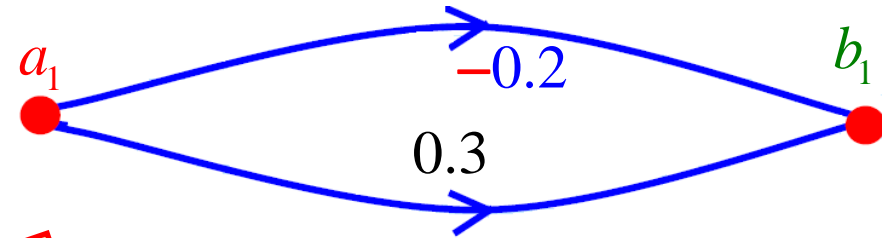

So that

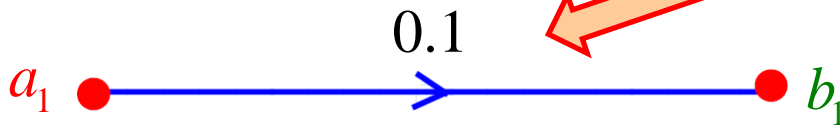

How about:

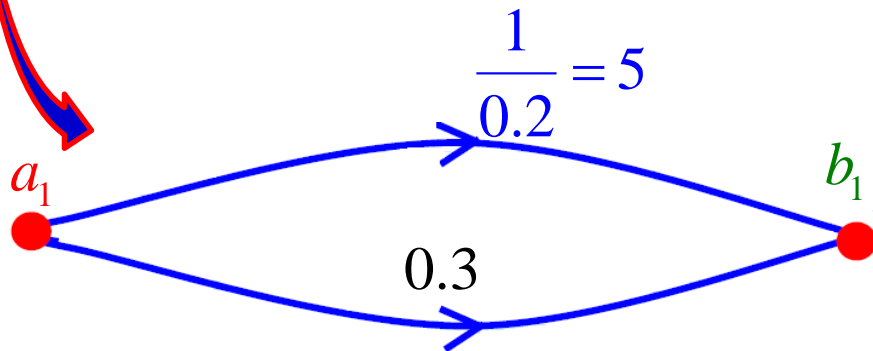


Absolutely not!  
**NEVER DO THIS!!**



Absolutely not! **NEVER DO THIS EITHER!!**

## Signal Flow Graph (contd.)

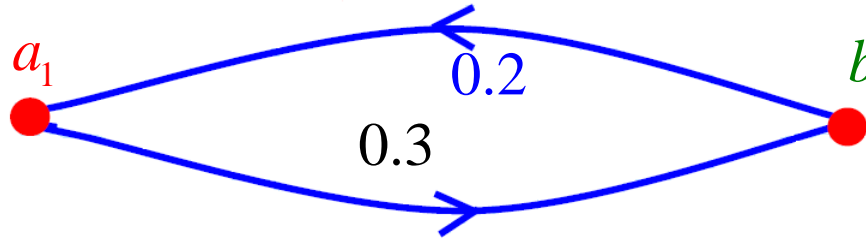

Actually from this SFG we  
can only conclude that


$$b_1 = 0.3a_1$$

$$a_1 = 0.2b_1$$

$$a_1 = 0.06a_1$$

$$b_1 = 0.3a_1$$

SFG can be  
of the form

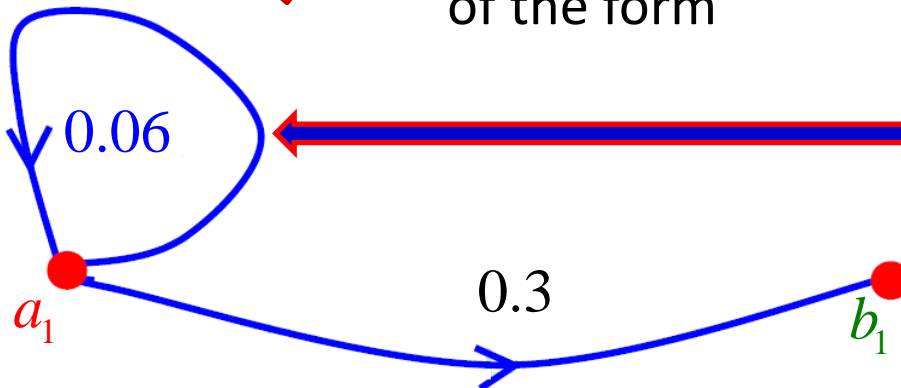


Branches that begin and  
end at the same node are  
called self-loops

In practical situations, self-loop node will **always** have at least **one other incoming branch**
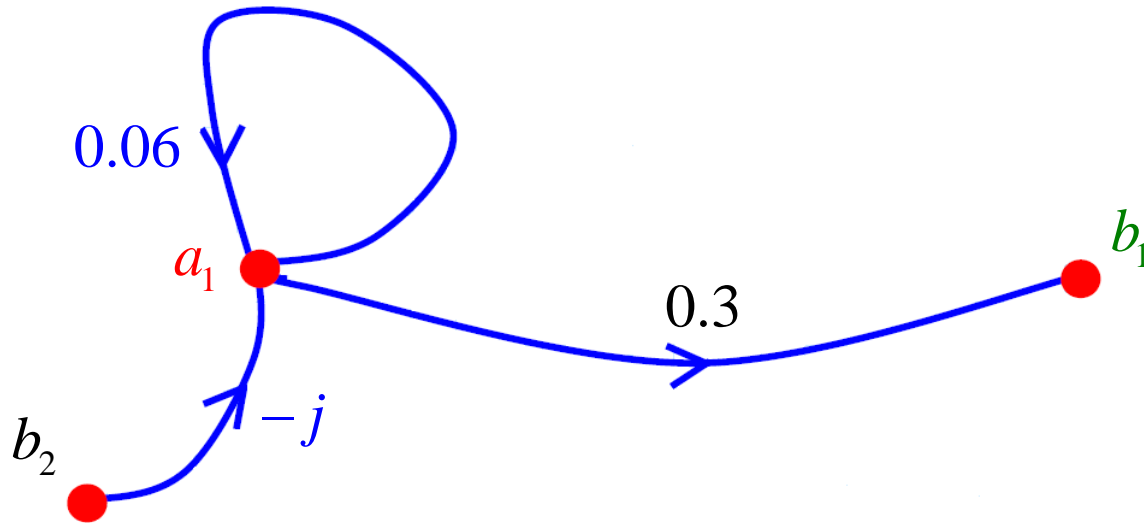
## Signal Flow Graph (contd.)

Practical example of node with self-loop:



## Signal Flow Graph (contd.)


### Self-Loop Rule

- Consider the complex equation:

$$b_1 = \alpha a_1 + \beta a_2 + \gamma b_1$$

- A little bit of **algebra** allows us to determine the value of node  $b_1$ :
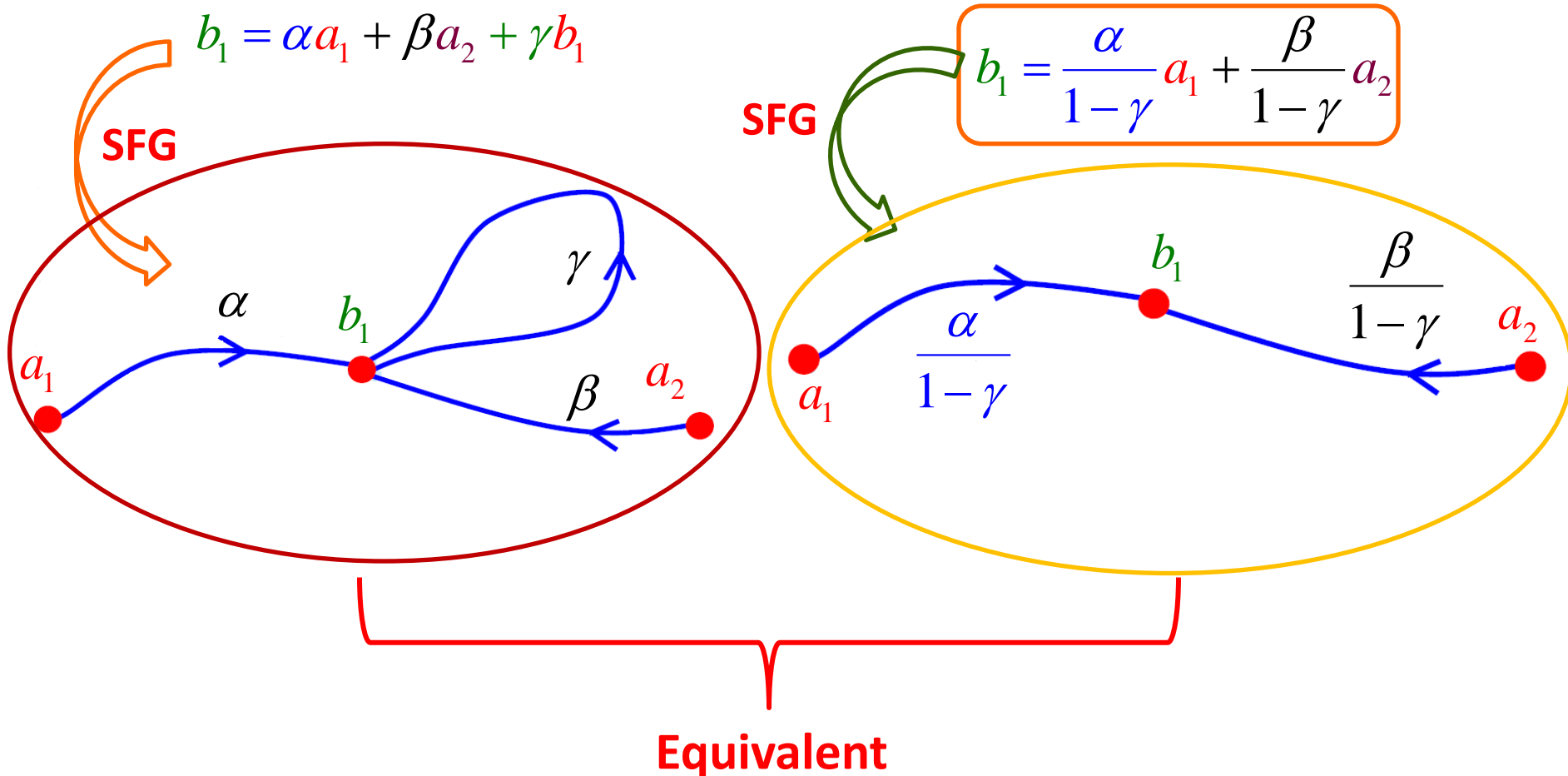
$$b_1 = \frac{\alpha}{1-\gamma} a_1 + \frac{\beta}{1-\gamma} a_2$$




## Signal Flow Graph (contd.)

This last discussion leads us to our **third SFG reduction rule**:

### Rule 3 – Self-Loop Rule

A self-loop can be eliminated by multiplying **all** of the branches “**feeding**” the self-loop node by  $1(1-S_{sl})$ , where  $S_{sl}$  is the value of the self loop branch.


### Example

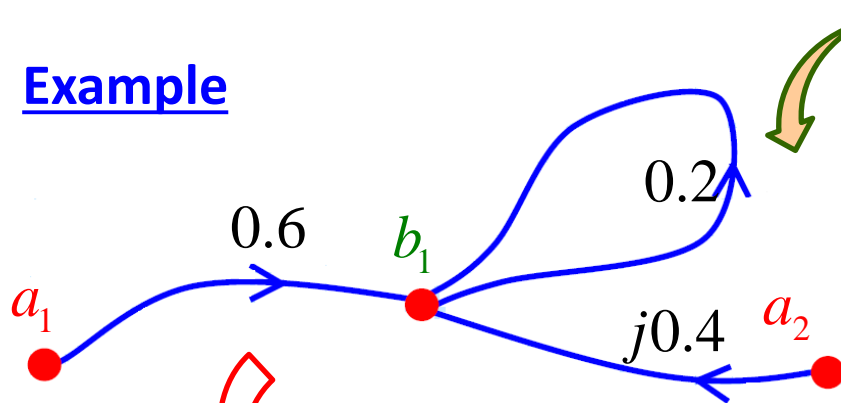

can be simplified by **eliminating the self-loop** → multiply **both** of the two branches **feeding** the self-loop node by:

$$\frac{1}{1-S_{sl}} = \frac{1}{1-0.2} = 1.25$$


**Simplified and Reduced**

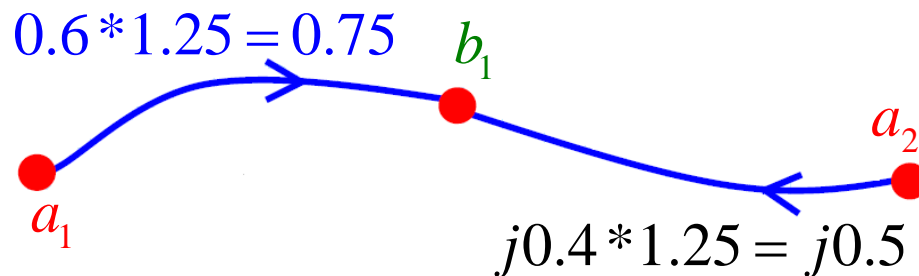



## Signal Flow Graph (contd.)

### Example

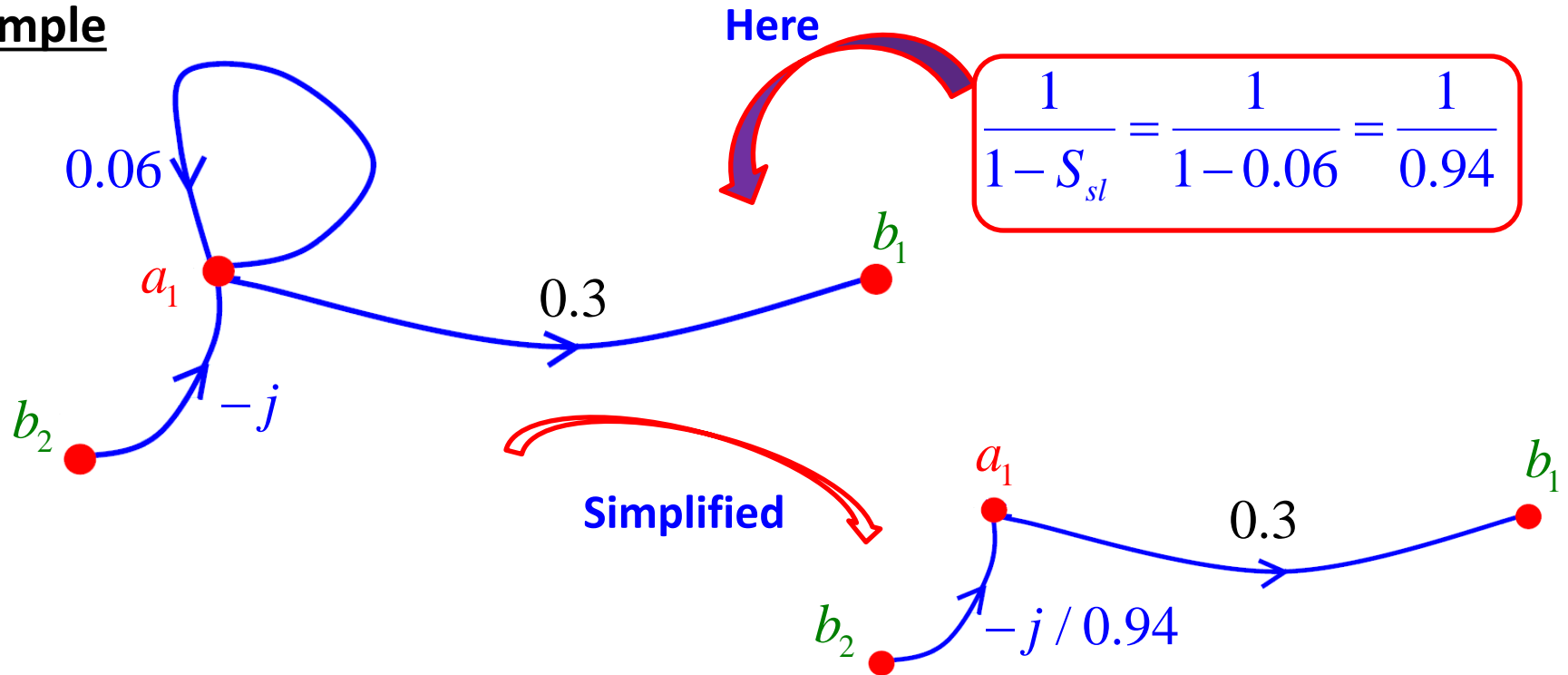

Only the incoming branches are modified by the self-loop rule! Here, the 0.3 branch is **exiting** the self-loop node  $a_1$  and therefore doesn't get modified. **Only** the  $-j$  branch (incoming at node  $a_1$ ) to the self-loop node are modified by the self-loop rule!