



## Lecture – 15

Date: 30.09.2014

- Stub Matching
- Double-Stub Matching Networks
- Quarter-wave Impedance Transformer
- The Theory of Small Reflections

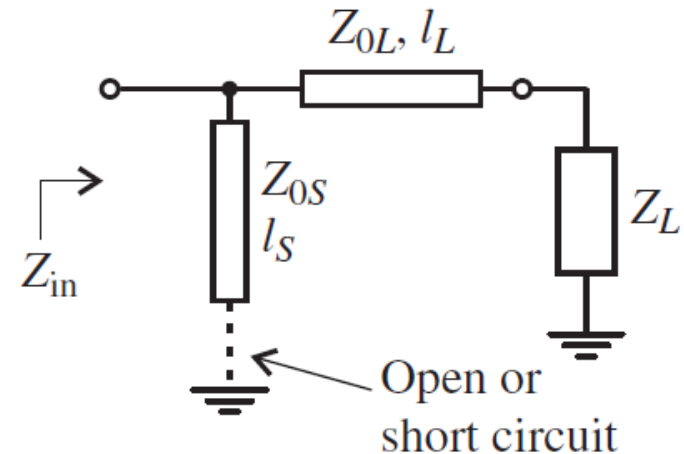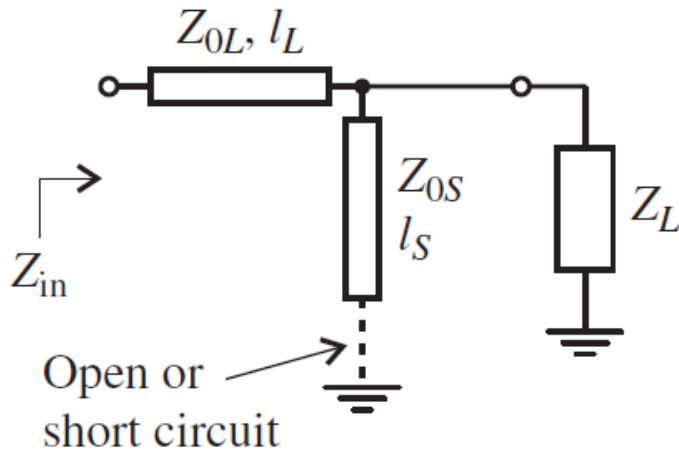
## Stub Matching Networks

- The next logical step in the transition from lumped to distributed element networks is the complete elimination of all lumped components → this can be achieved by employing open – and/or short – circuited stub lines


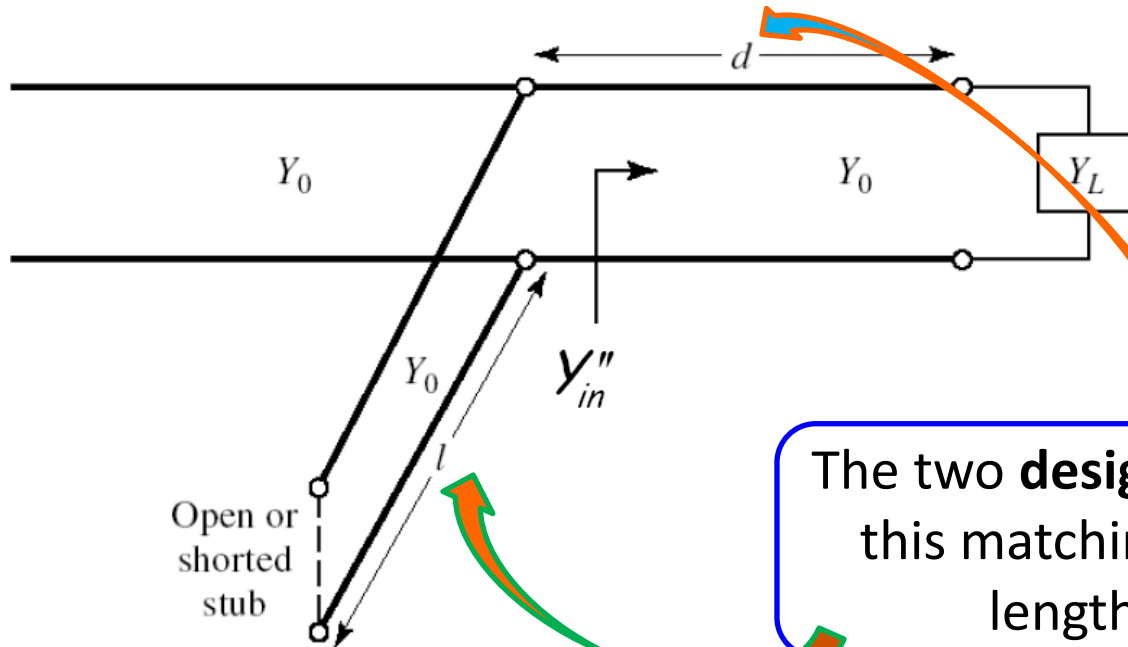
## Shunt-stub Matching Networks


- Let us consider the following TL configuration with shunt stub.



The two **design parameters** of this matching network are lengths  $l$  and  $d$ .
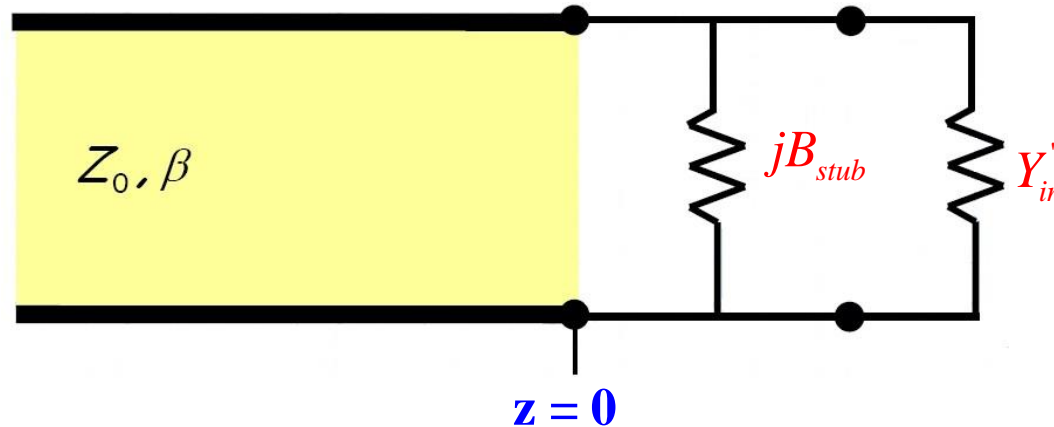
## Shunt-stub Matching Networks (contd.)

- An equivalent circuit for the shunt-tub TL can be:



Where:

$$Y_{in}'' = Y_0 \left( \frac{Y_L + jY_0 \tan(\beta d)}{Y_0 + jY_L \tan(\beta d)} \right)$$

$$jB_{stub} = \begin{cases} jY_0 \tan(\beta l) & \text{For open-stub} \\ -jY_0 \cot(\beta l) & \text{For short-stub} \end{cases}$$

## Shunt-stub Matching Networks (contd.)

- Therefore, for a matched circuit, we require:

$$jB_{stub} + Y_{in}'' = Y_0$$

- Note this complex equation is actually **two real equations!**

$$\text{Re}\{Y_{in}''\} = Y_0$$

$$\text{Im}\{jB_{stub} + Y_{in}''\} = 0 \quad \Rightarrow \quad B_{stub} = -B_{in}''$$

Where:

$$-B_{in}'' = \text{Im}\{Y_{in}''\}$$

- Since  $Y_{in}''$  is dependent on  $d$  only, our **design procedure** is:

- 1) Set  $d$  such that  $\text{Re}\{Y_{in}''\} = Y_0$ .

- 2) Then set  $l$  such that  $B_{stub} = -B_{in}''$ .

We have two choice, either **Analytical** or **Smith** chart for finding out the lengths  $d$  and  $l$

## Shunt-stub Matching Networks (contd.)

### Use of the Smith Chart to determine the lengths!

- Rotate **clockwise** around the Smith Chart from  $y_l$  until you intersect the  $g_s=1$  circle. The “length” of this rotation determines the value  $d$ . Recall there are **two** possible solutions!
- Rotate **clockwise** from the short/open circuit point around the  $g = 0$  circle, until  $b_{stub}$  equals  $-b_{in}$ . The “length” of this rotation determines the stub length  $l$ .

### Example – 1


Let us take the case where we want to match a load of  $Z_L = (60 - j80)\Omega$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .

## Example – 1 (contd.)
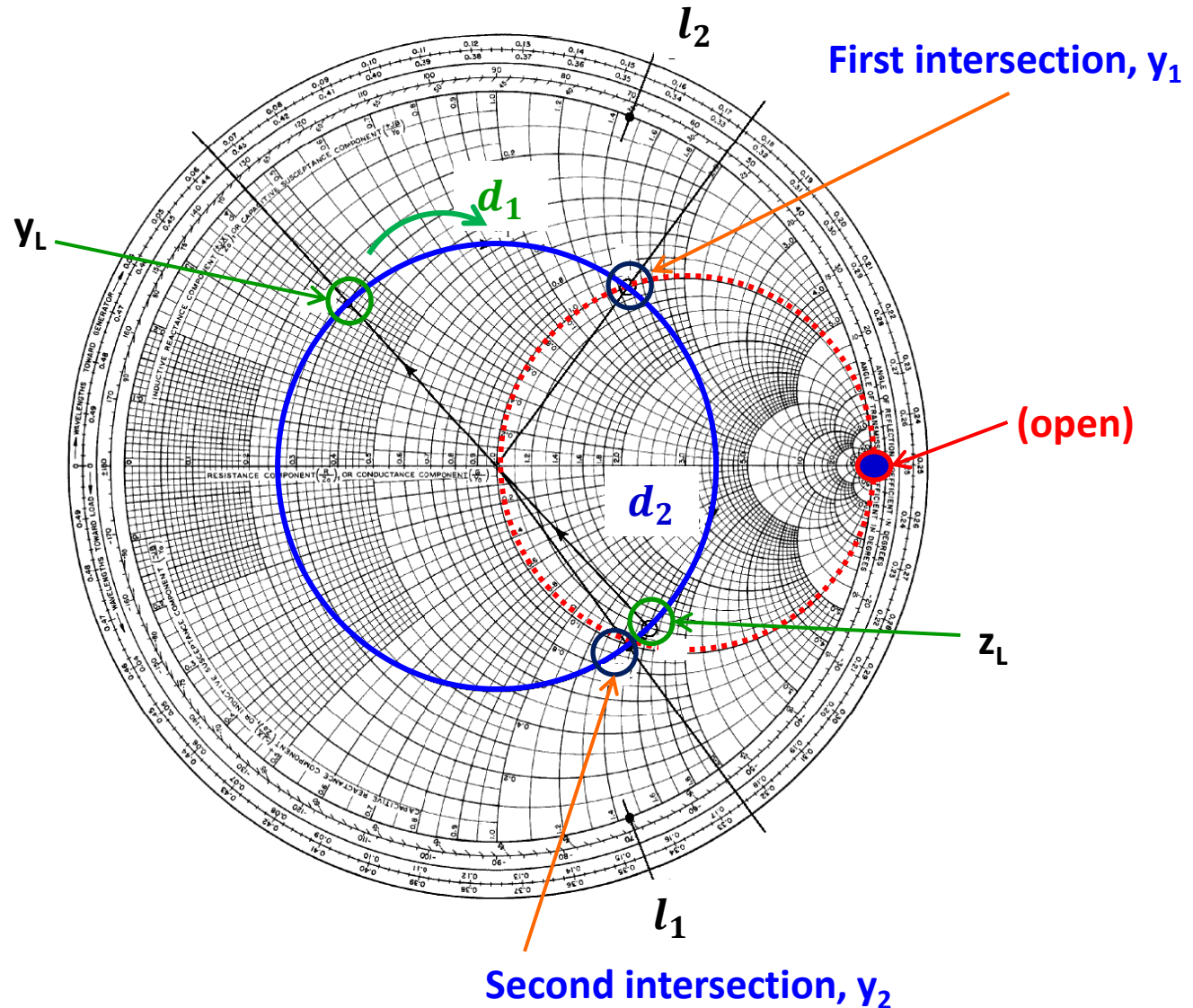
### Solution



$y_L$  to  $y_1$  towards  
generator  
(clockwise) gives  
length  $d_1$  (first  
solution)

$y_L$  to  $y_2$  towards  
generator  
(clockwise) gives  
length  $d_2$  (second  
solution)


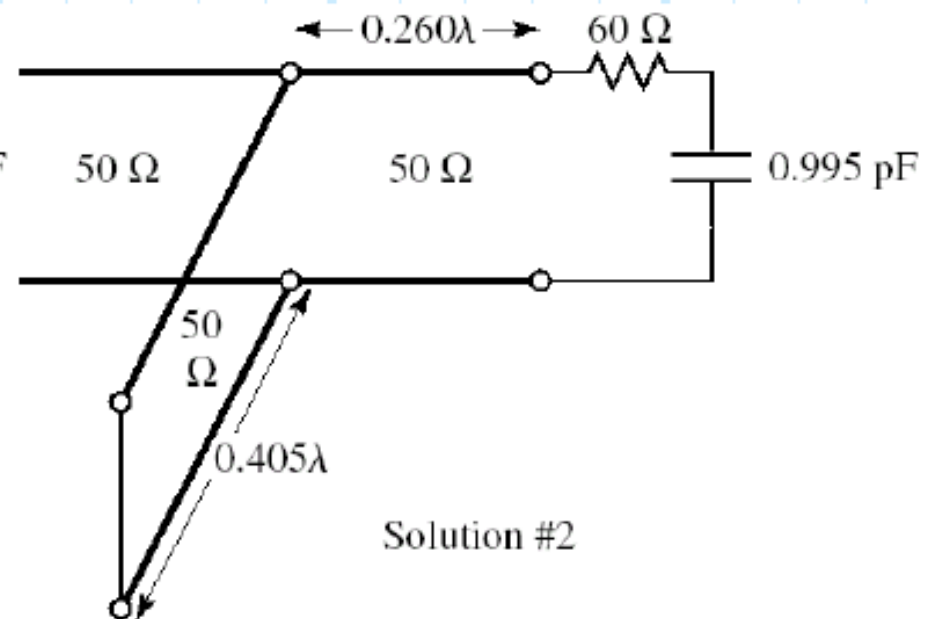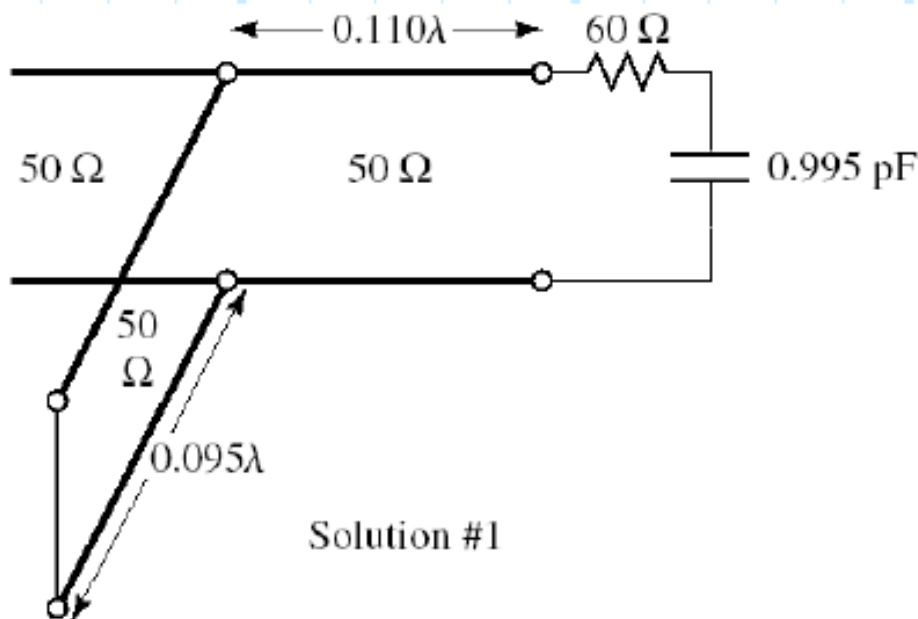
## Example – 1 (contd.)

- Determine the respective admittances at the two intersection points
- These are of the form  $1 + jx$  and  $1 - jx$
- Cancel these imaginary part of the admittances by introducing shunt-stubs of length  $l_1$  and  $l_2$  respectively
- $l_1$  and  $l_2$  are the lengths from open circuit point in the Smith chart (if open stub is used) along the  $g = 0$  circle until the achieved admittances are of opposite signs to those at the intersection points in the earlier step





## Example – 1 (contd.)


**Q:** Two solutions! Which one do we use?

**A:** The one with the **shortest** lengths of transmission line!

**Q:** Oh, I see! Shorter transmission lines provide **smaller** and (slightly) cheaper matching networks.

**A:** True! But there is a more **fundamental** reason why we select the solution with the **shortest** lines—the matching **bandwidth** is **larger**!

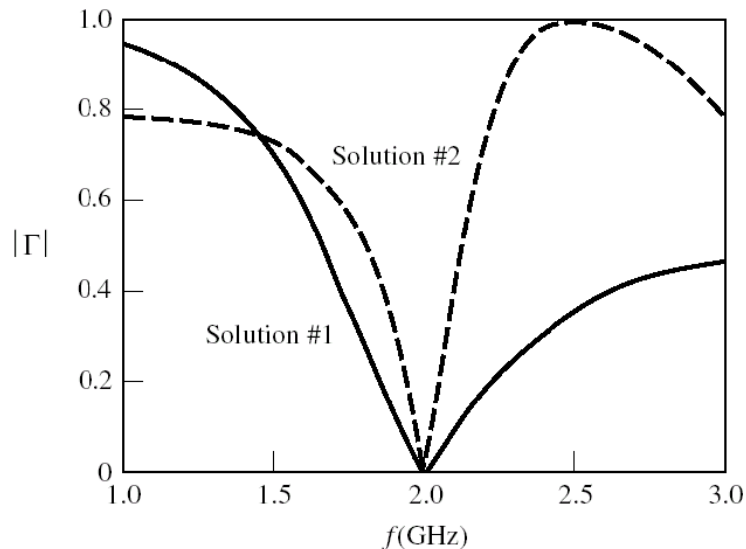
- For example, consider the **frequency response** of the two solutions:



Clearly, solution 1 provides a **wider** bandwidth!
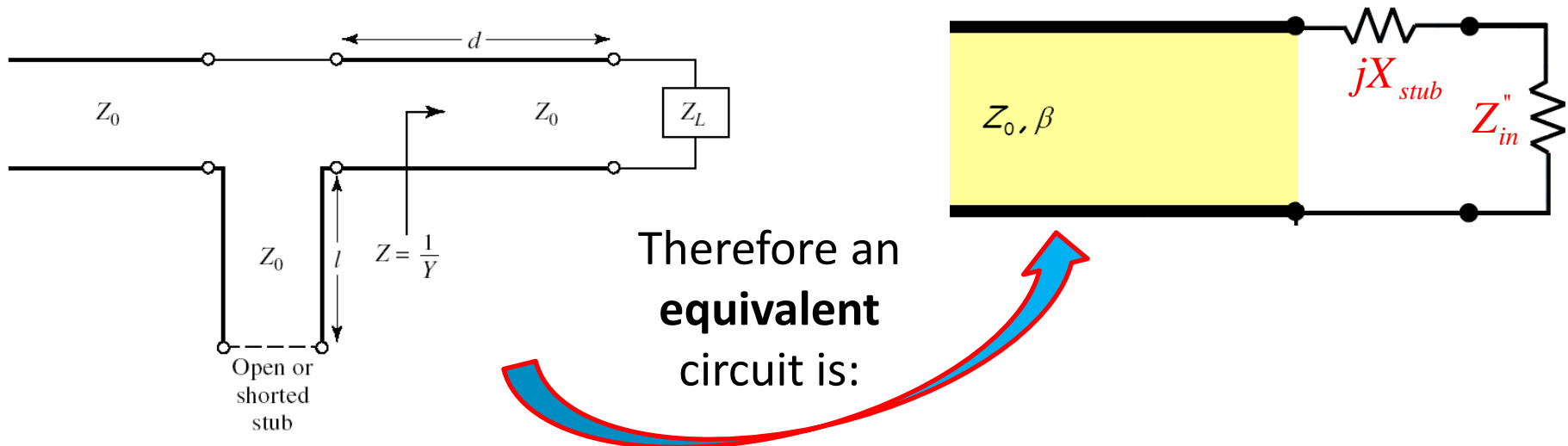
## Series-stub Matching Networks

- Consider the following transmission line structure, with a **series stub**:



where of course:

$$Z_{in}'' = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right)$$

$$jX_{stub} = \begin{cases} -jZ_0 \cot(\beta l) & \text{For open-stub} \\ jZ_0 \tan(\beta l) & \text{For short-stub} \end{cases}$$


## Example – 2

Let us take the case where we want to match a load of  $Z_L = (100 + j80)\Omega$  (at 2 GHz) to a transmission line of  $Z_0 = 50\Omega$ .
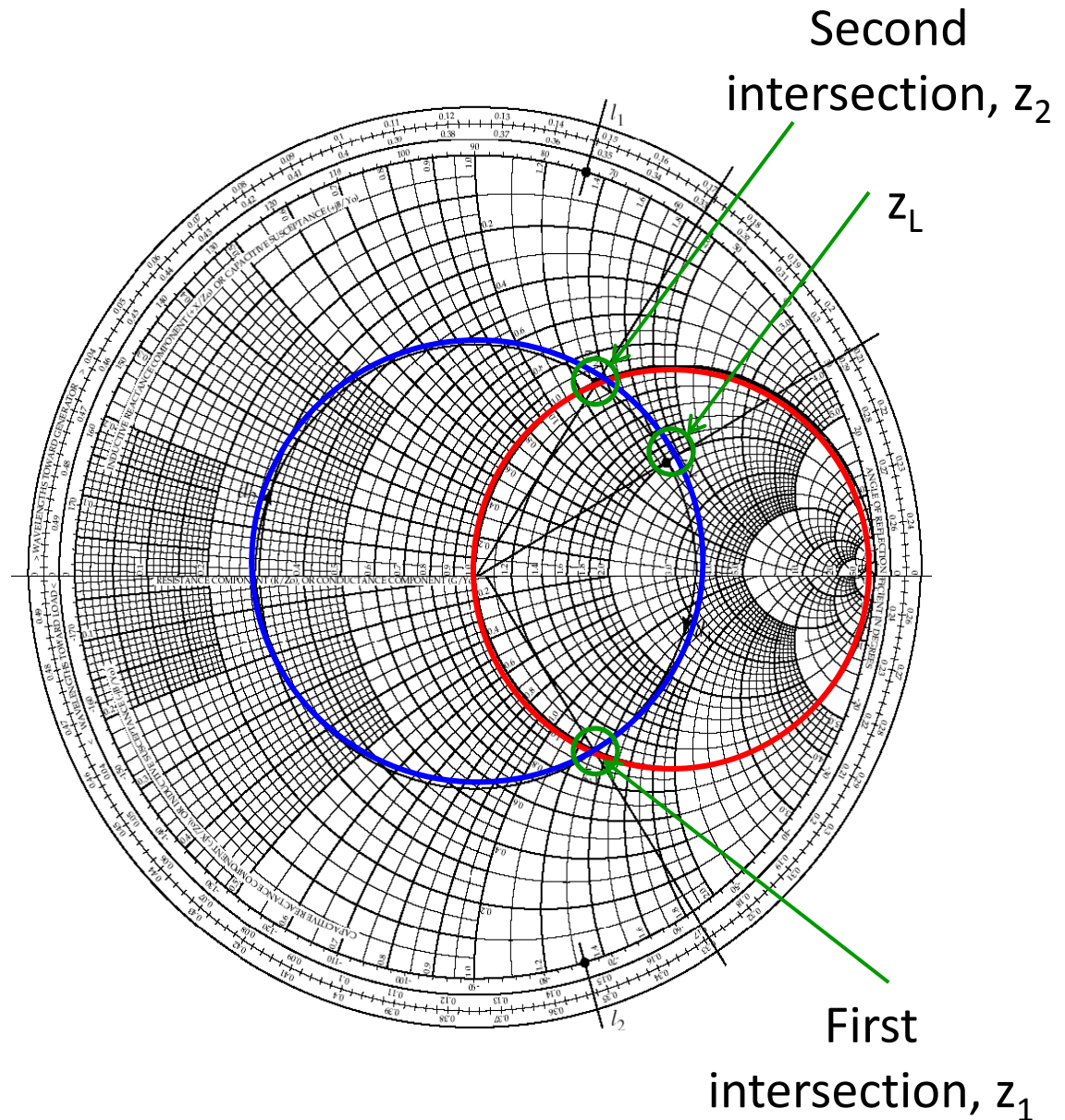
## Example – 2 (contd.)


$z_l$  to  $z_1$  towards  
generator  
(clockwise) gives  
length  $d_1$  (first  
solution)

$z_l$  to  $z_2$  towards  
generator  
(clockwise) gives  
length  $d_2$  (second  
solution)




## Example – 2 (contd.)

- Determine the respective impedances at the two intersection points and these are of the form  $1 + jx$  and  $1 - jx$
- Cancel these imaginary part of the impedances by introducing series-stubs of length  $l_1$  and  $l_2$  respectively
- $l_1$  and  $l_2$  are the lengths from open circuit point in the Smith chart (if open stub is used) along the  $r = 0$  circle until the achieved impedances are of opposite signs to those at the intersection points in the earlier step

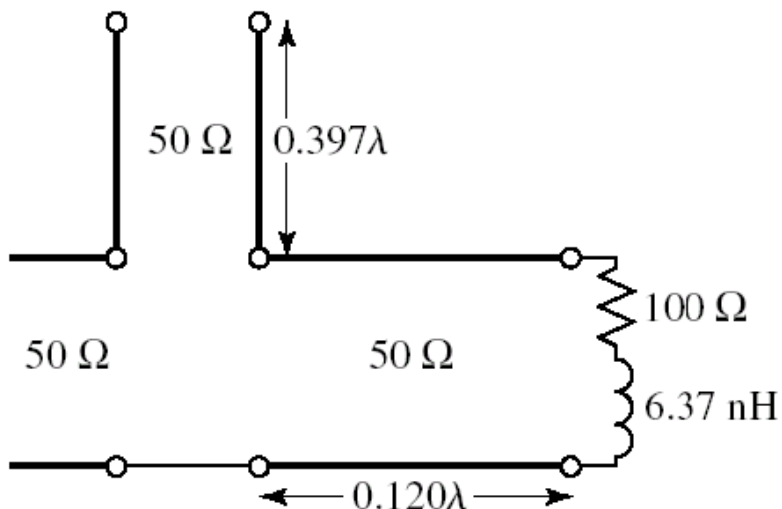



Solution 1

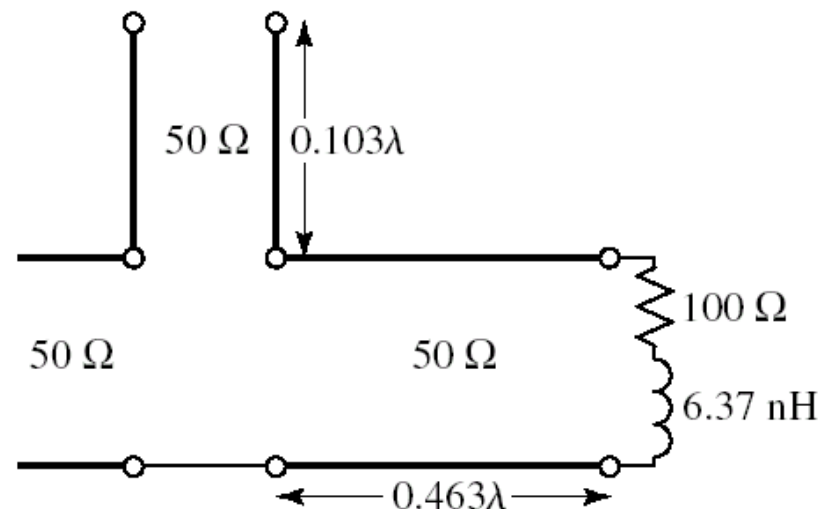

Solution 2
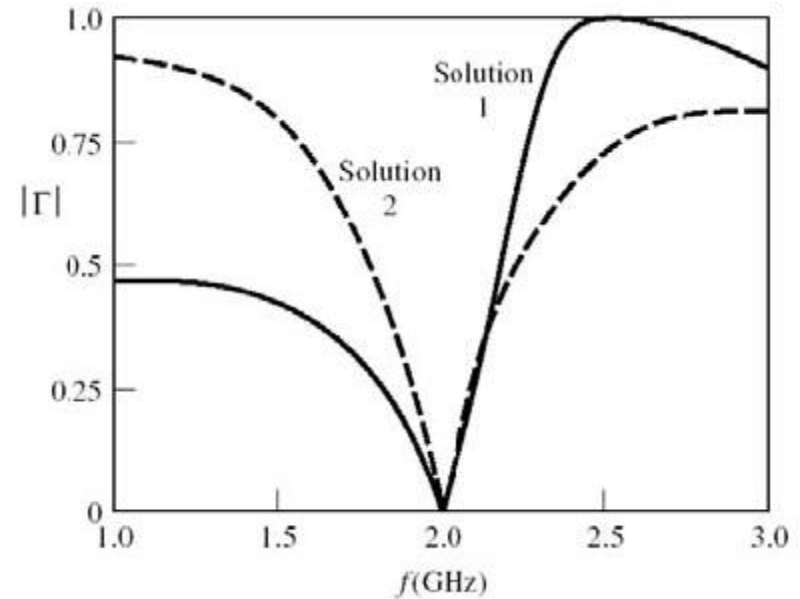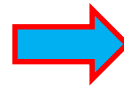
## Example – 2 (contd.)

Again, we should use the solution with the **shortest** transmission lines, although in **this** case that distinction is a bit **ambiguous**. As a result, the bandwidth of each design is about the same (depending on how **you** define **bandwidth!**).



## Example – 3

For a load impedance of  $Z_L = (60 - j45)\Omega$ , design single-stub (shunt) matching networks that transform the load to a  $Z_{in} = (75 + j90)\Omega$  input impedance. Assume both the stub and transmission line have a characteristic impedance of  $Z_0 = 75\Omega$

### Solution

- Normalize the  $Z_L$  and  $Z_{in}$  with  $75\Omega$
- Mark these normalized impedances on the Z-Smith chart
- Move to Y-Smith chart or better use ZY-Smith chart
- Plot constant conductance ( $g_L$ ) circle
- Plot SWR circle for normalized input impedance ( $z_{in}$ )
- Two intersection points between constant conductance circle and SWR circle can be observed
- **Rotation from intersection points to  $z_{in}$**  give the lengths  $d_1$  and  $d_2$  and corresponding changes in admittance
- Look for cancelling the additional admittances **using shunt stub** by equating corresponding stub lengths from **'open'** in Smith chart


## Example – 3 (contd.)

Here:

$$z_L = 1.2 - j0.9$$

$y_{in}$  to A towards  
generator  
(clockwise) gives  
length  $d_1$  (first  
solution)

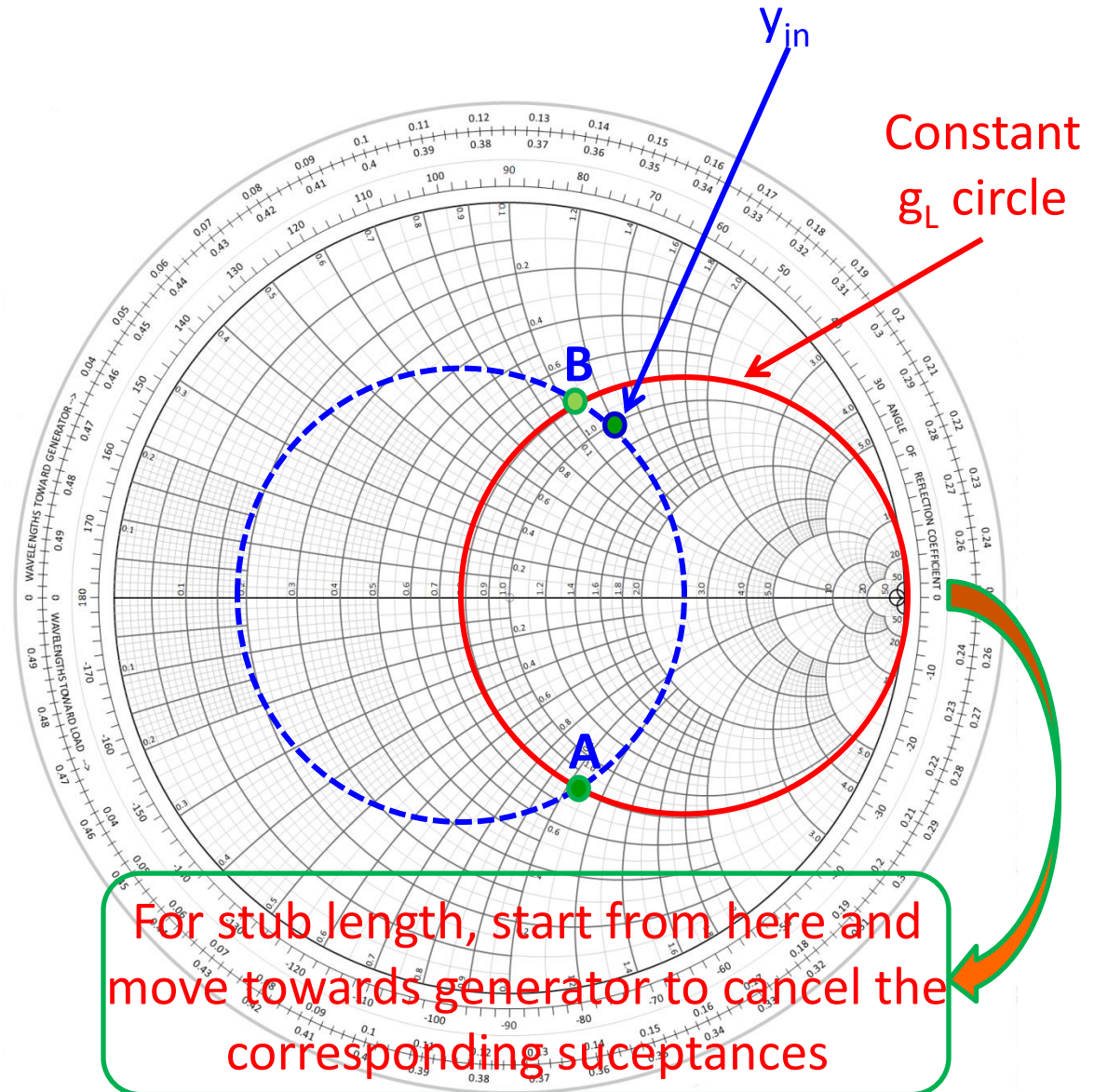
$y_{in}$  to B towards  
generator  
(clockwise) gives  
length  $d_2$  (second  
solution)




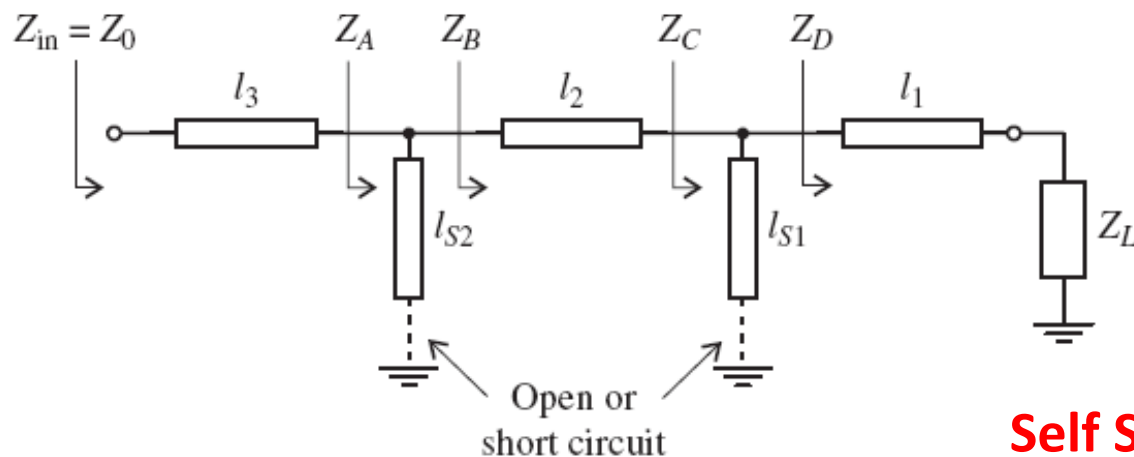
## Double-stub Matching Networks

- The single-stub matching networks are quite versatile → allows matching between any input and load impedances, so long as they have a non-zero real part.
- Main drawback is the requirement of variable length TL between the stub and the input port or the stub and the load impedance → many a times problematic when variable impedance tuner is needed.
- In a double-stub matching networks, **two short- or open-circuited stubs are connected in shunt with a fixed-length TL separating them** → the usual separation is  $\lambda/8$ ,  $3\lambda/8$  or  $5\lambda/8$ .



Self Study


## The Quarter Wave Transformer

- By now you must have noticed that a **quarter-wave length** of transmission line ( $l = \lambda/4$ ,  $2\beta l = \pi$ ) appears **often** in RF/microwave engineering problems.
- Another application of the  $l = \lambda/4$  transmission line is as an **impedance matching network**.

**Q: Why** does the quarter-wave matching network work — after all, the quarter-wave line is **mismatched** at both ends?

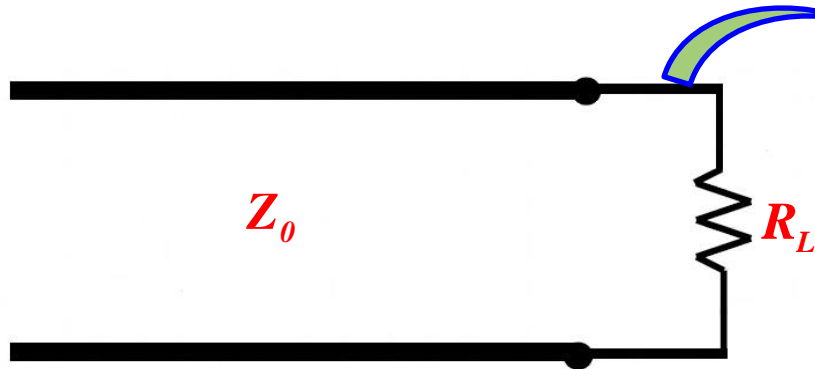
## The Quarter Wave Transformer (contd.)

- Let us consider a TL (with characteristic impedance  $Z_0$ ) where the end is terminated with a **resistive** (i.e., real) load:



Unless  $R_L = Z_0$ , the resistor is **mismatched** to the line, and thus some of the incident power will be **reflected**.

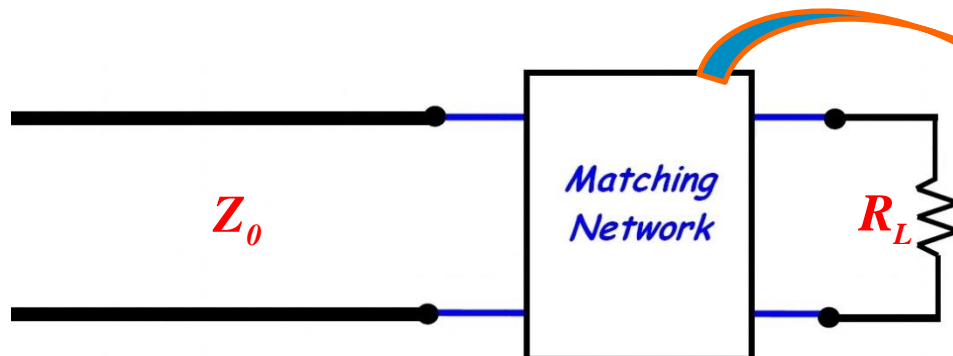
- We can of course correct this situation by placing a matching network between the line and the load:



In addition to the designs we have just studied (e.g., L-networks, stub tuners), one of the simplest matching network designs is the **quarter-wave transformer**.
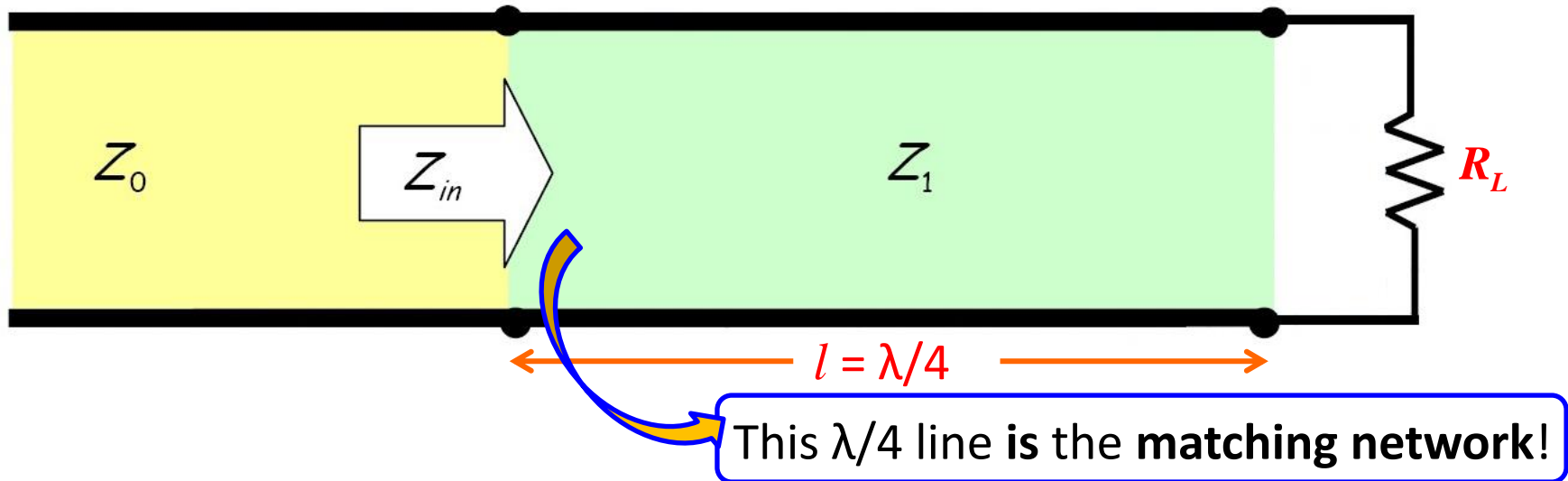
## The Quarter Wave Transformer (contd.)

- The quarter-wave transformer is simply a transmission line with characteristic impedance  $Z_1$  and length  $l = \lambda/4$  (i.e., a quarter-wave line).



**Q:** But what about the characteristic impedance  $Z_1$ ; what **should** its value be??

## The Quarter Wave Transformer (contd.)

**A:** Remember, the quarter wavelength case is one of the **special** cases that we studied. We know that the **input** impedance of the quarter wavelength line is:

$$Z_{in} = \frac{(Z_1)^2}{Z_L} = \frac{(Z_1)^2}{R_L}$$

- Thus, if we wish for  $Z_{in}$  to be numerically equal to  $Z_0$ , we find:

$$Z_{in} = \frac{(Z_1)^2}{R_L} = Z_0$$


- Solving for  $Z_1$ , we find its **required** value to be:

$$Z_1 = \sqrt{Z_0 R_L}$$

In other words, the characteristic impedance of the quarter wave line is the **geometric average** of  $Z_0$  and  $R_L$ !
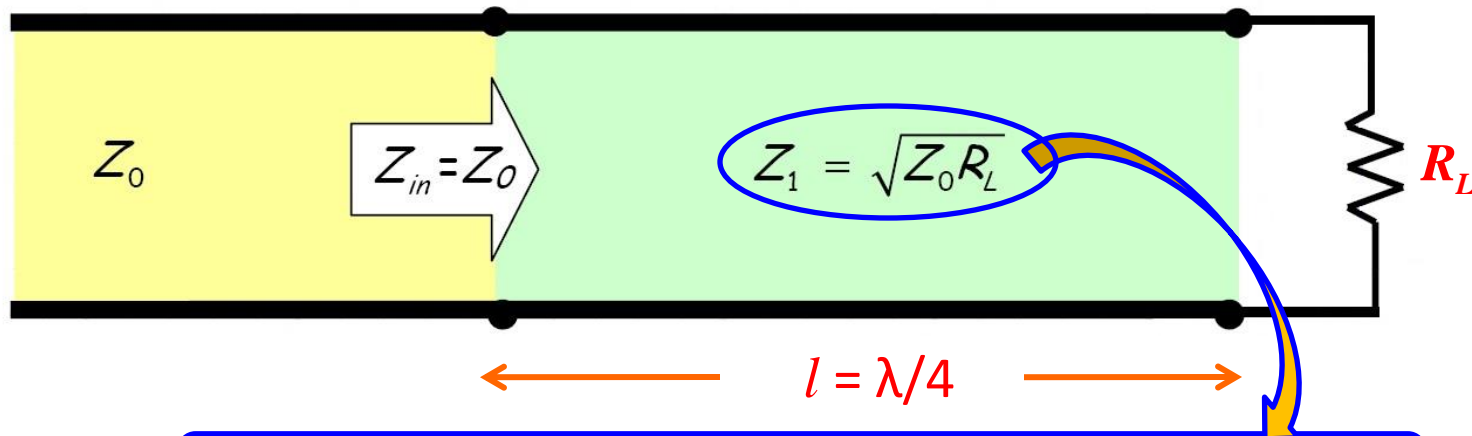
## The Quarter Wave Transformer (contd.)

Therefore, a  $\lambda/4$  line with characteristic impedance  $Z_1 = \sqrt{Z_0 R_L}$  will **match** a transmission line with characteristic impedance  $Z_0$  to a resistive load  $R_L$



This ensures that **all power** is delivered to load  $R_L$ !

Alas, the quarter-wave transformer (like all our designs) have a few problems!

## The Quarter Wave Transformer (contd.)

### Problem #1

- The matching **bandwidth** is **narrow** !
- In other words, we obtain a **perfect** match at precisely the frequency where the length of the matching transmission line is a **quarter-wavelength**.

remember, this length can be a quarter-wavelength at just **one** frequency!

- **Wavelength** is related to **frequency** as:

$$\lambda = \frac{v_p}{f} = \frac{1}{f\sqrt{LC}}$$



$v_p$  is propagation velocity of wave


- For **example**, assuming that  $v_p = c$  ( $c$  = the speed of light in a vacuum), one wavelength at 1 GHz is 30 cm ( $\lambda = 0.3\text{m}$ ), while one wavelength at 3 GHz is 10 cm ( $\lambda = 0.1\text{m}$ ). As a result, a TL length  $l = 7.5\text{cm}$  is a quarter wavelength for a signal at 1GHz **only**.

**Thus, a quarter-wave transformer provides a perfect match ( $\Gamma_{in} = 0$ ) at one and only one signal frequency!**
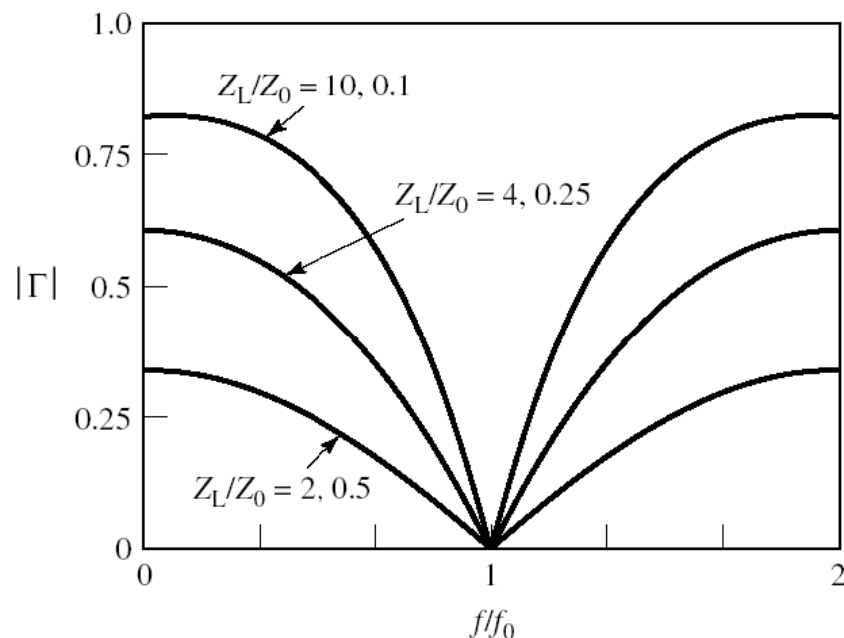
## The Quarter Wave Transformer (contd.)

In other words, as the signal frequency (i.e., wavelength) changes, the **electrical** length of the matching TL segment changes. It will **no longer** be a **quarter** wavelength, and thus we **no longer** will have a **perfect** match

It can be observed that the **closer**  $R_L$  (or  $R_{in}$ ) is to characteristic impedance  $Z_0$ , the **wider** the bandwidth of the quarter wavelength transformer



In principle, the bandwidth can be **increased** by adding **multiple**  $\lambda/4$  sections!



# The Quarter Wave Transformer (contd.)


## Problem #2

Recall the matching solution was limited to loads that were **purely real!** i.e.:

$$Z_L = R_L + j0$$

Obviously, this is a **BIG** problem, as most loads will have a **reactive** component!

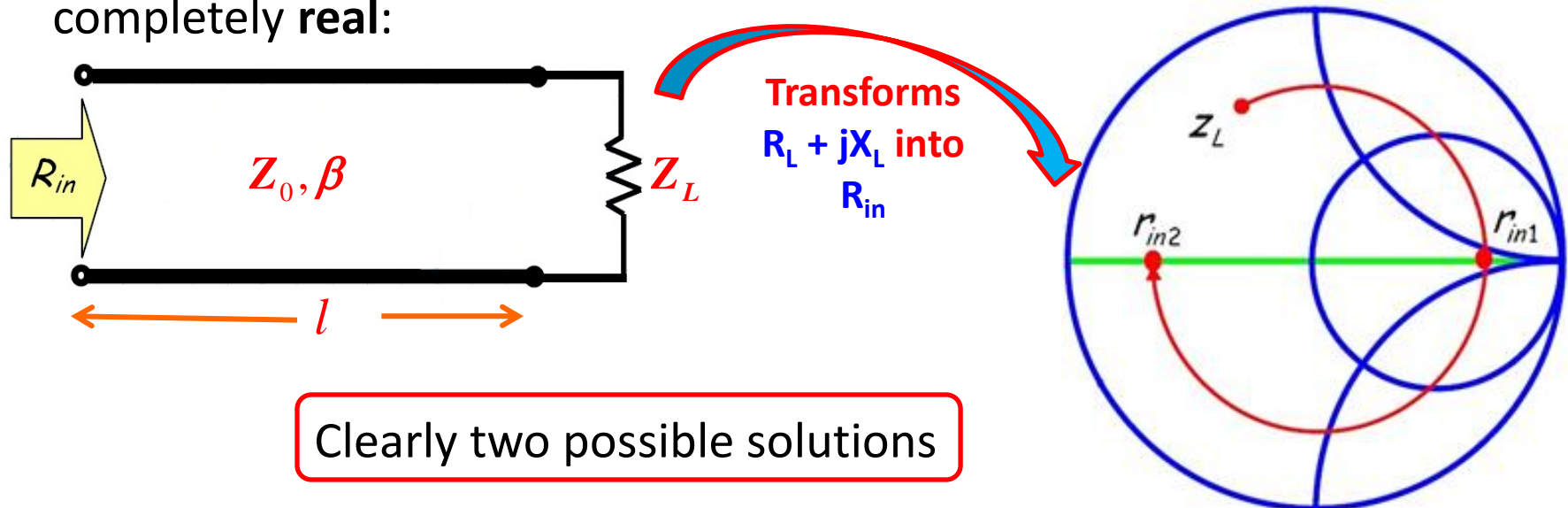
- Fortunately, we have a relatively easy **solution** to this problem, as we can always add some **length**  $l$  of TL to the load to make the impedance completely **real**:


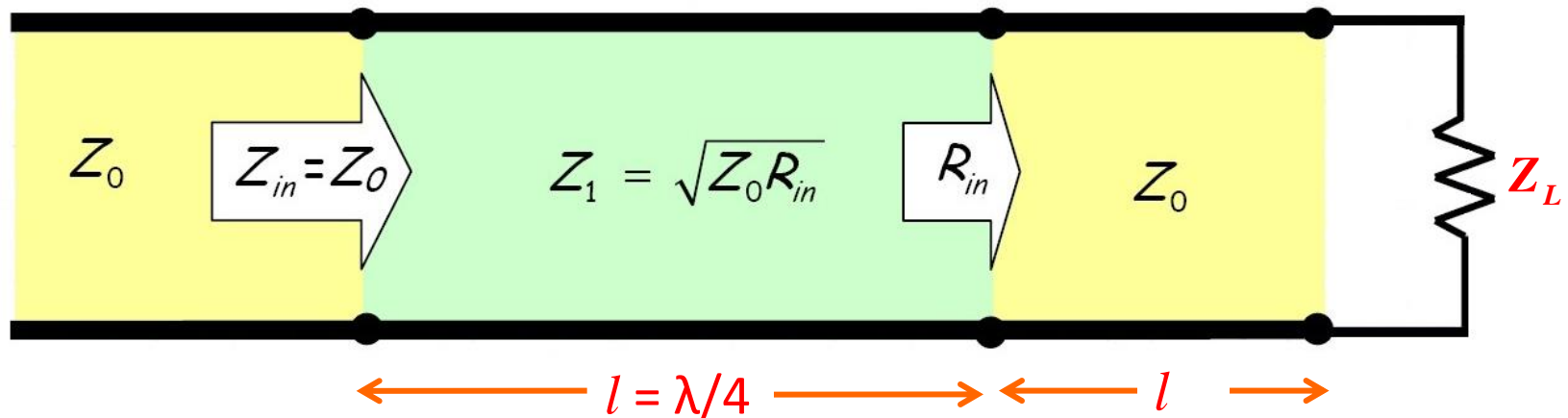
## The Quarter Wave Transformer (contd.)

However, it should be understood that the input impedance will be purely real at only **one** frequency!


Once the output impedance has been converted to purely real, one can then build a quarter-wave transformer to **match** the line  $Z_0$  to resistance  $R_{in}$



Again, since the transmission lines are lossless, **all** of the incident power is delivered to the **load**  $Z_L$ .
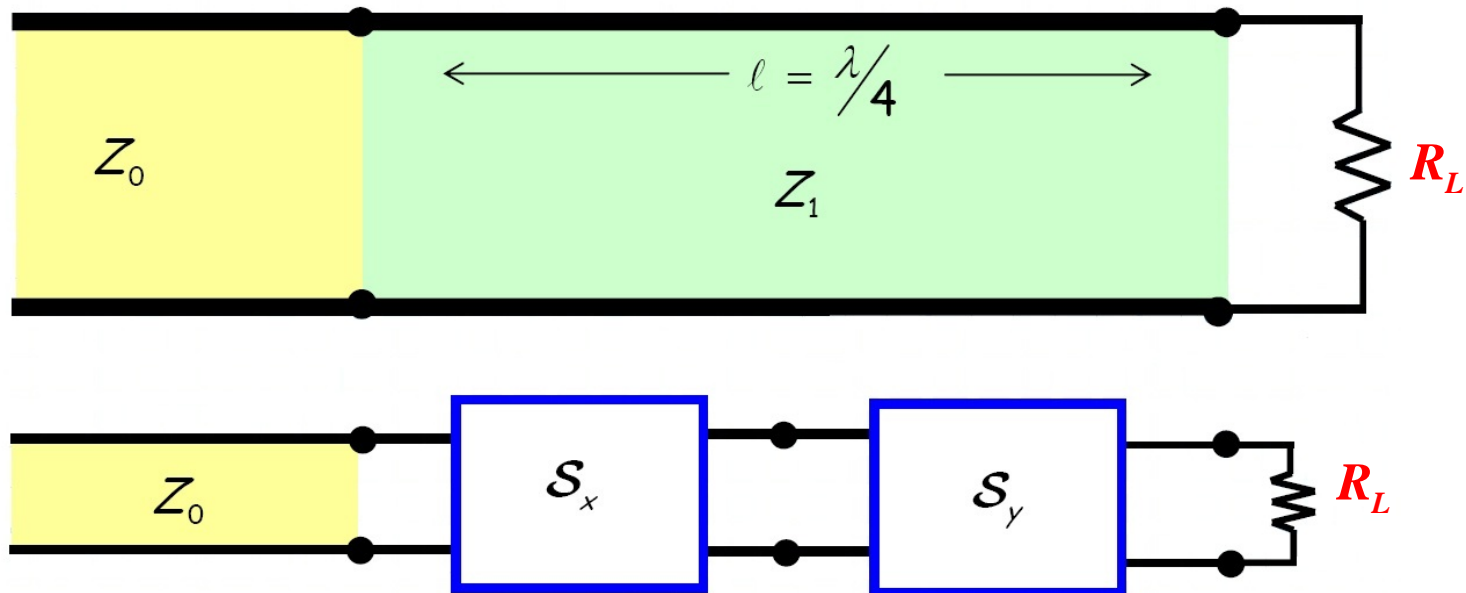
## The Quarter Wave Transformer (contd.)


- A quarter wave transformer can be thought of as a cascaded series of **two** two-port devices, terminated with a load  $R_L$ :



**Q:** **Two** two-port devices? It appears to me that a quarter-wave transformer is **not** that complex. What **are** the **two** two-port devices?

**A:** The **first** is a “**connector**”. Note a connector is the interface between one transmission line (characteristic impedance  $Z_0$ ) to a second transmission line (characteristic impedance  $Z_1$ ).

## The Quarter Wave Transformer (contd.)

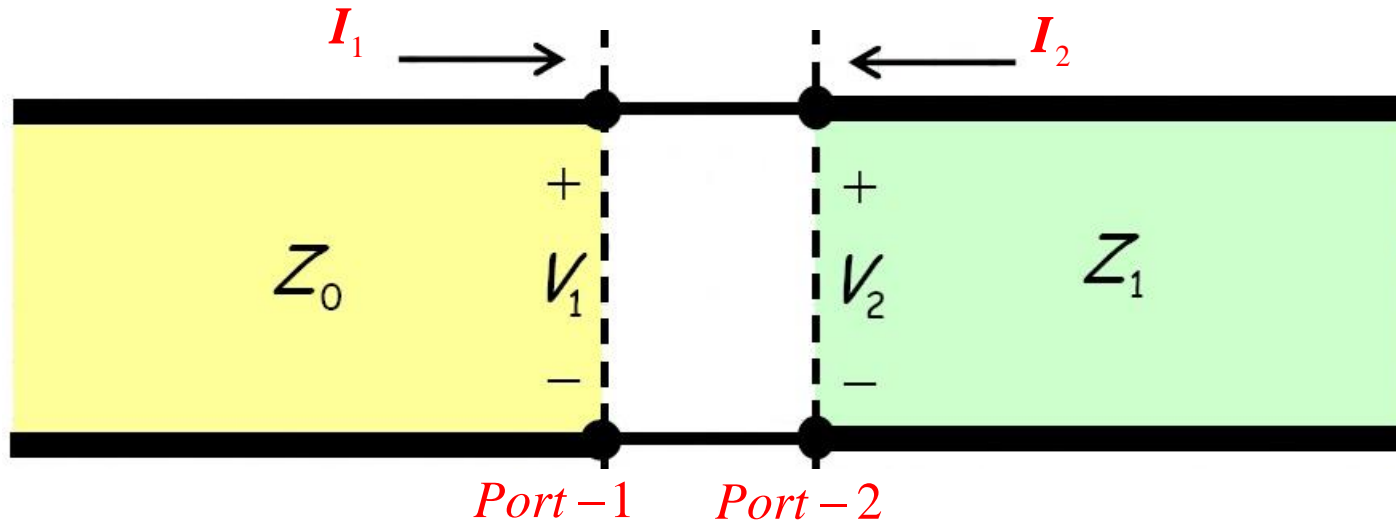

- we **earlier** determined the scattering matrix of this two-port device as:

$$S_x = \begin{bmatrix} \frac{Z_1 - Z_0}{Z_1 + Z_0} & \frac{2\sqrt{Z_0 Z_1}}{Z_1 + Z_0} \\ \frac{2\sqrt{Z_0 Z_1}}{Z_1 + Z_0} & \frac{Z_0 - Z_1}{Z_1 + Z_0} \end{bmatrix}$$


Compact Form




$$S_x = \begin{bmatrix} \Gamma & T \\ T & -\Gamma \end{bmatrix}$$
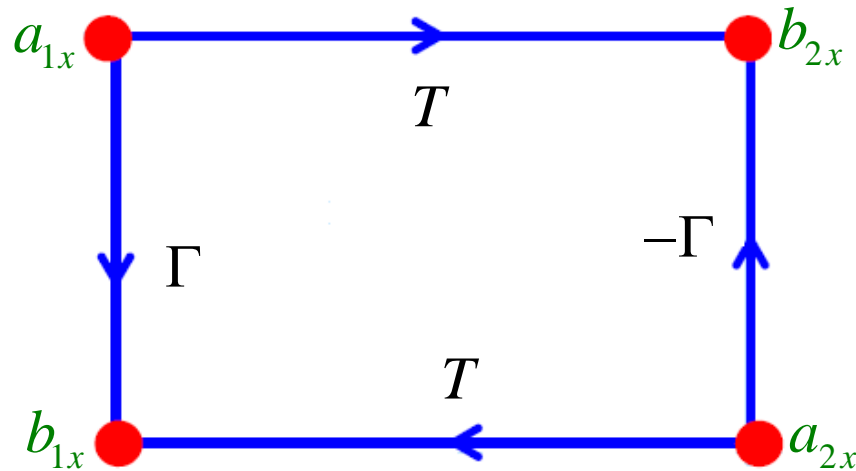
## The Quarter Wave Transformer (contd.)

- Therefore signal flow graph of the connector can be given as:



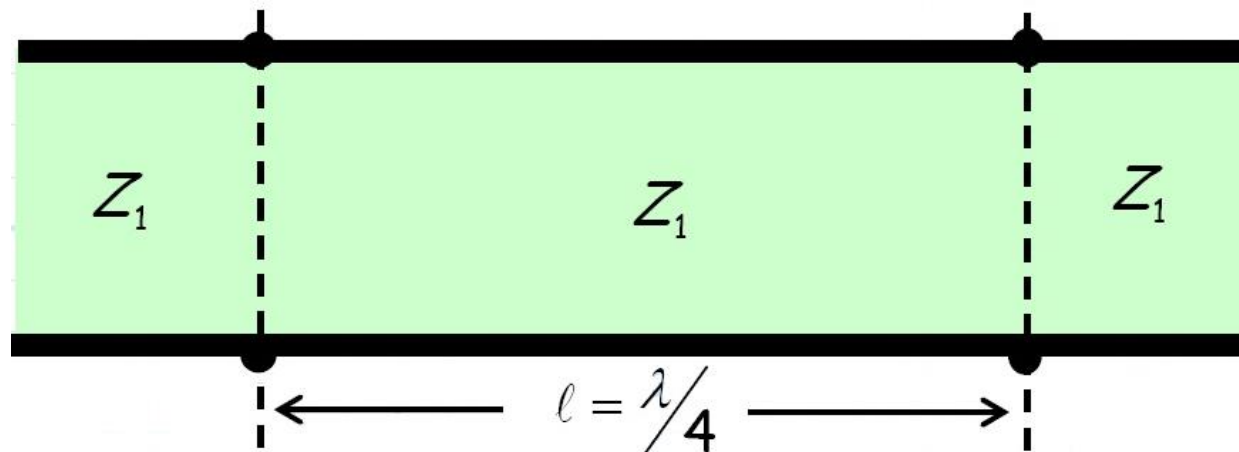
- Now, the **second** two-port device is a quarter wavelength of TL:


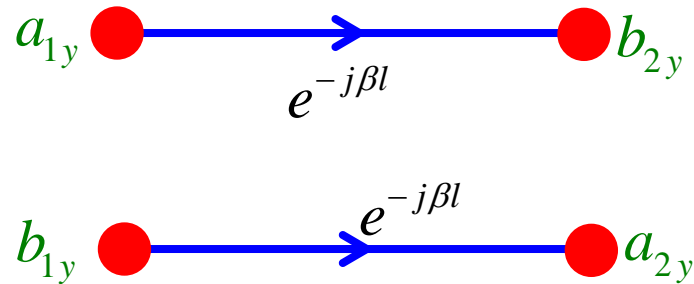
## The Quarter Wave Transformer (contd.)

- The second device has the scattering matrix and SFG as:


$$S_y = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$



- Finally, a **load** has a “scattering matrix” and SFG as:



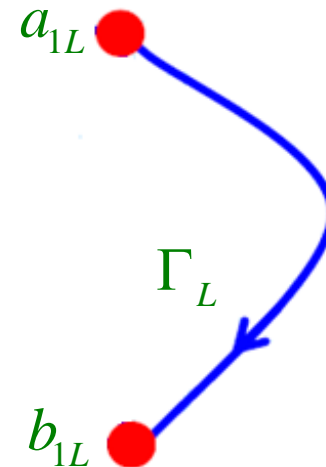
$$S = \left[ \frac{R_L - Z_1}{R_L + Z_1} \right] = \Gamma_L$$


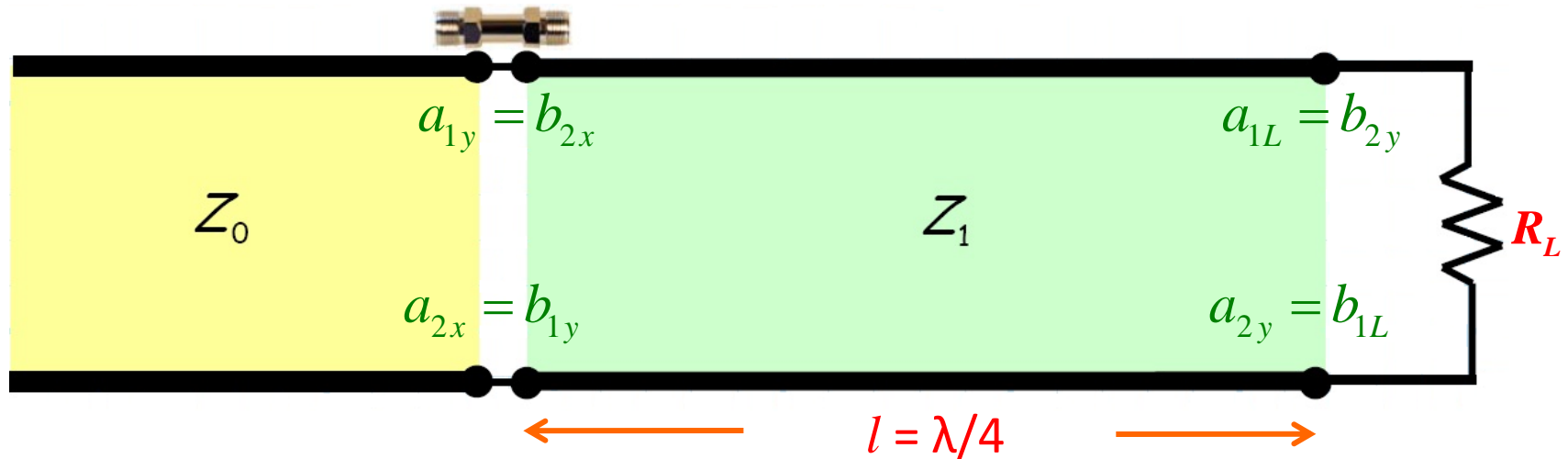
## The Quarter Wave Transformer (contd.)

- Of course, if we connect the ideal connector to a quarter wavelength of transmission line, and terminate the whole thing with load  $R_L$ , we have formed a **quarter wave matching network!**



- The boundary conditions associated with these connections are likewise:

$$a_{1y} = b_{2x}$$


$$a_{2x} = b_{1y}$$

$$a_{1L} = b_{2y}$$


$$a_{2y} = b_{1L}$$
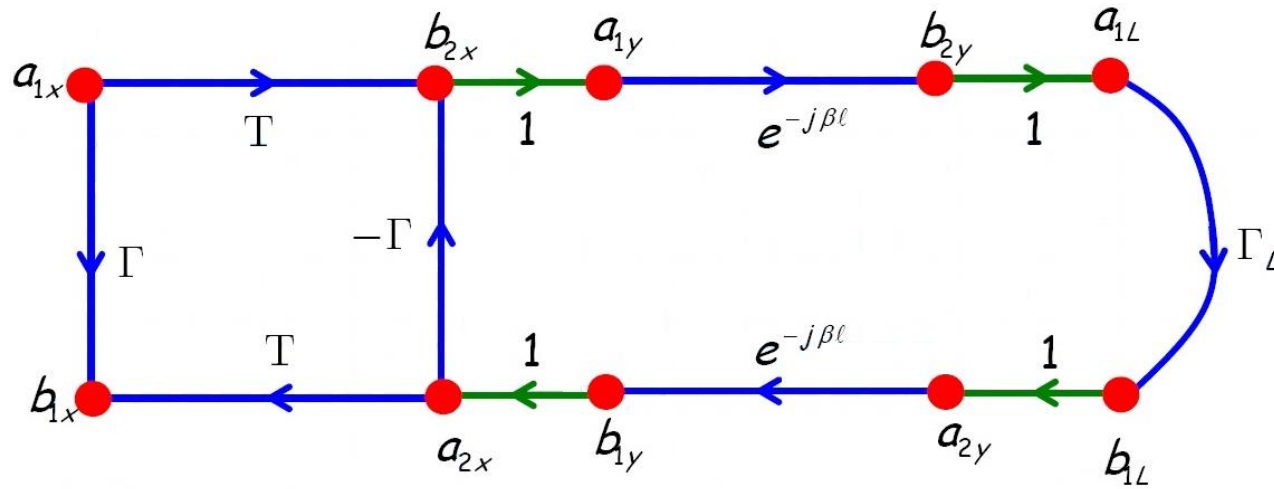
## The Quarter Wave Transformer (contd.)

- Therefore, we can put the signal-flow graph pieces together to form the **signal-flow graph** of the quarter wave network:



- Simplification gives:**

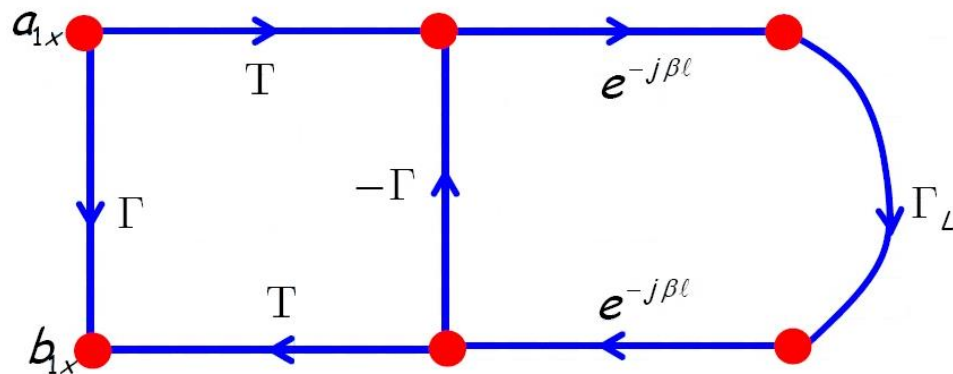



## The Quarter Wave Transformer (contd.)

### Simplification:



### Therefore:

$$\Gamma_{in} \doteq \frac{b_{1x}}{a_{1x}} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta l}}{1 - \Gamma \Gamma_L}$$

**Q:** Hey wait! If the quarter-wave transformer is a **matching network**, shouldn't  $\Gamma_{in} = 0$ ??

**A:** Who says it isn't! Consider now **three important facts**.

## The Quarter Wave Transformer (contd.)

- For a **quarter wave transformer**, we set  $Z_1$  such that:


$$Z_1^2 = Z_0 R_L \quad \Rightarrow \quad Z_0 = \frac{Z_1^2}{R_L}$$

- Inserting** this into the scattering parameter  $S_{11}$  of the connector, we find:

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{Z_1 - Z_1^2 / R_L}{Z_1 + Z_1^2 / R_L} = \frac{R_L - Z_1}{R_L + Z_1}$$

- For the quarter-wave transformer, the **connector**  $S_{11}$  value (i.e.,  $\Gamma$ ) is the **same** as the **load** reflection coefficient  $\Gamma_L$ :

$$\Gamma = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L$$

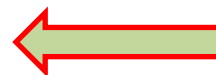

**Fact 1**

- Since the connector is **lossless** (unitary scattering matrix!), we can conclude (and likewise show) that:

$$1 = |S_{11}|^2 + |S_{21}|^2 = |\Gamma|^2 + |T|^2$$

## The Quarter Wave Transformer (contd.)

- Since  $Z_0$ ,  $Z_1$ , and  $R_L$  are all real, the values  $\Gamma$  and  $T$  are also **real valued**. As a result,  $|\Gamma|^2 = \Gamma^2$  and  $|T|^2 = T^2$ , and we can likewise conclude:

$$|\Gamma|^2 + |T|^2 = \Gamma^2 + T^2 = 1$$



**Fact 2**

- Likewise, the  $Z_1$  transmission line has  $l = \lambda/4$ , so that:

$$2\beta l = 2 \left( \frac{2\pi}{\lambda} \right) \frac{\lambda}{4} = \pi$$



$$e^{-j\beta l} = e^{-j\pi} = -1$$



**Fact 3**

- As a result:

$$\Gamma_{in} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta l}}{1 - \Gamma \Gamma_L} = \Gamma - \frac{T^2 \Gamma_L}{1 - \Gamma \Gamma_L}$$

- And using the **newly discovered** fact that (for a correctly designed transformer)  $\Gamma_L = \Gamma$ :

$$\Gamma_{in} = \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2}$$

## The Quarter Wave Transformer (contd.)


- We also have a **recent** discovery that says  $T^2 = 1 - \Gamma^2$ , therefore:

$$\Gamma_{in} = \Gamma - \frac{T^2\Gamma}{1-\Gamma^2} = \Gamma - \frac{T^2\Gamma}{T^2} = 0$$

A **perfect match!** The quarter-wave transformer does indeed work!
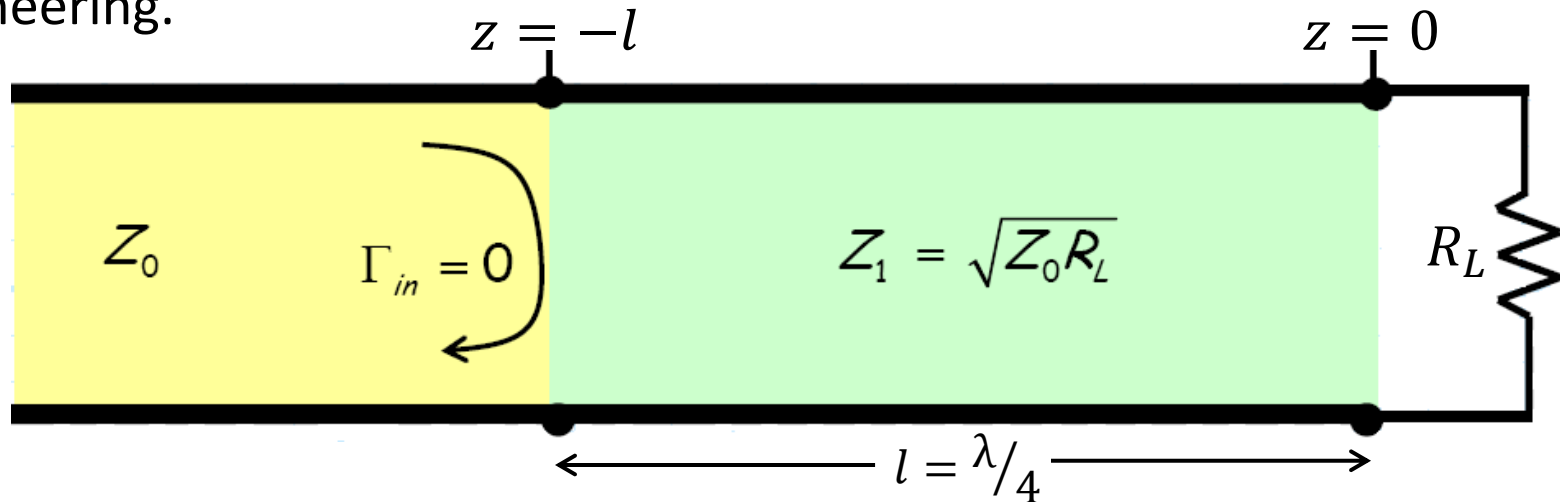
## Multiple Reflection Viewpoint

- The **quarter-wave** transformer brings up an interesting question in  $\mu$ -wave engineering.




**Q:** Why is there **no** reflection at  $z = -l$ ? It appears that the line is **mismatched** at both  $z = 0$  and  $z = -l$ .

**A:** In fact there **are** reflections at these mismatched interfaces—an **infinite** number of them!

We can use **signal flow graph** to determine the propagation series, once we determine all the **propagation paths** through the quarter-wave transformer.

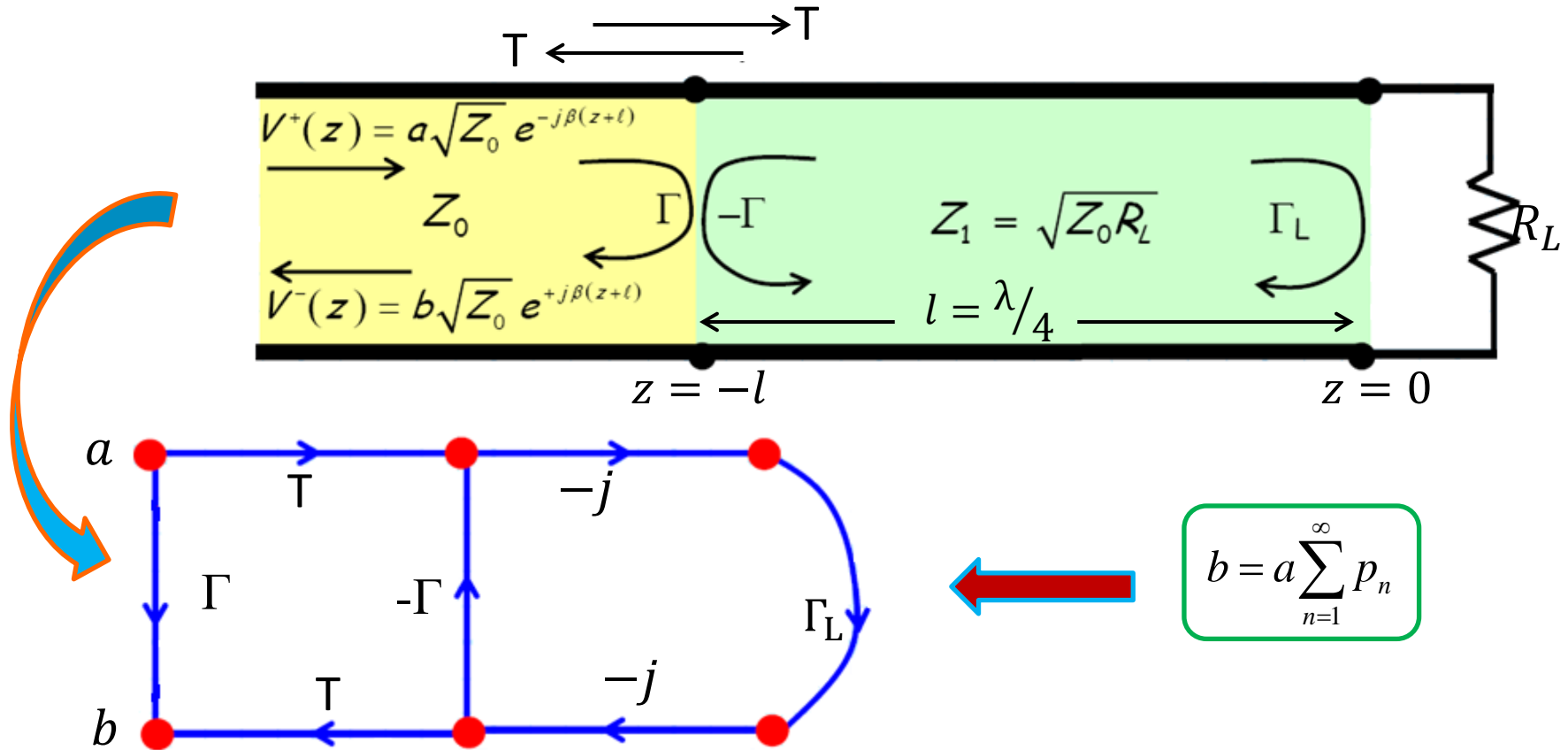
## Multiple Reflection Viewpoint (contd.)



- Now, let's try to interpret what **physically** happens when the **incident** voltage wave reaches the interface at  $z = -l$ .
- We find that there are **two forward paths** through the quarter-wave transformer signal flow graph.

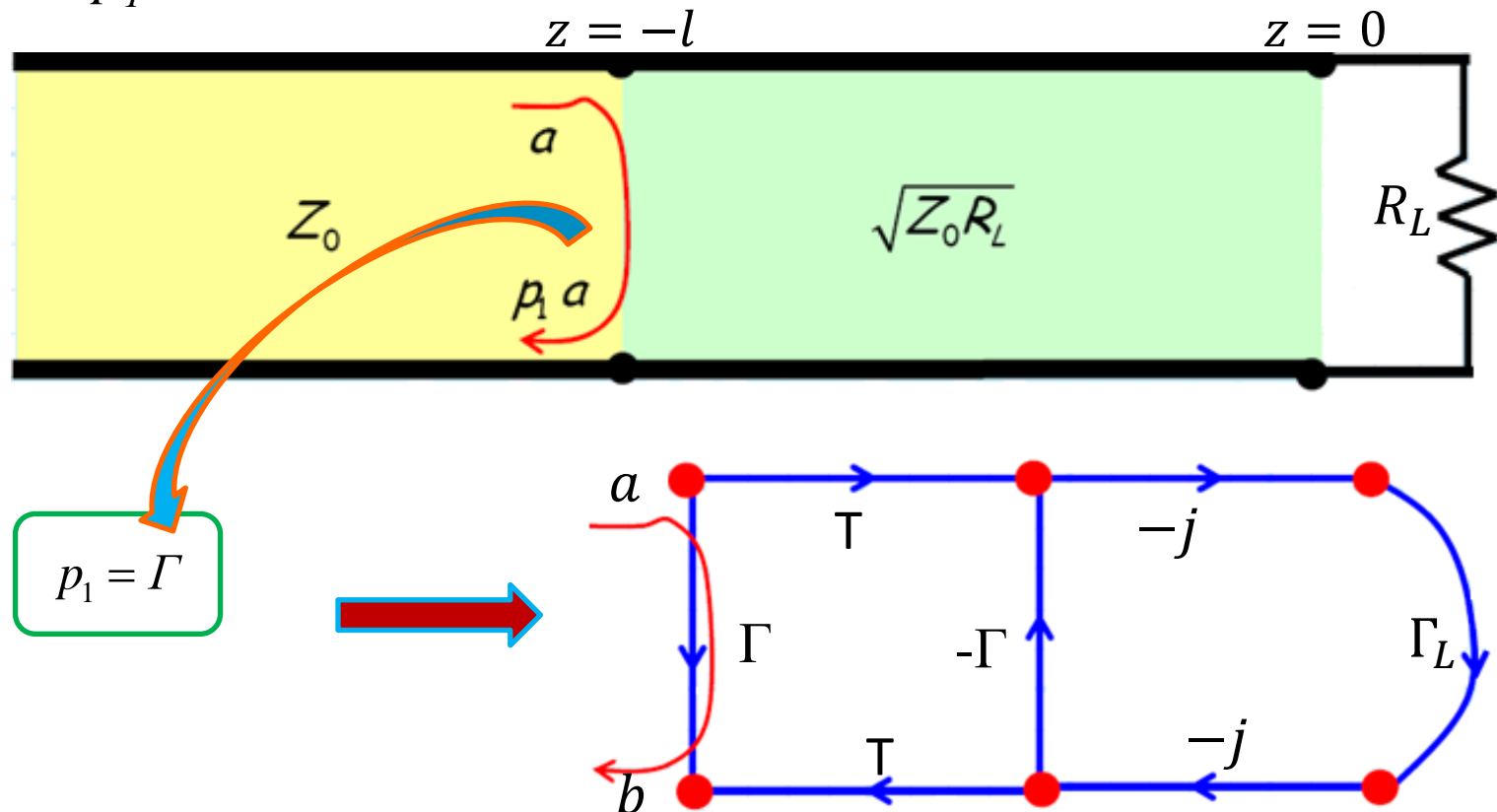
## Multiple Reflection Viewpoint (contd.)

**Path 1.** At  $z = -l$ , the characteristic impedance of the transmission line changes from  $Z_0$  to  $Z_1$ . This mismatch creates a **reflected** wave, with complex amplitude  $p_1 a$  :


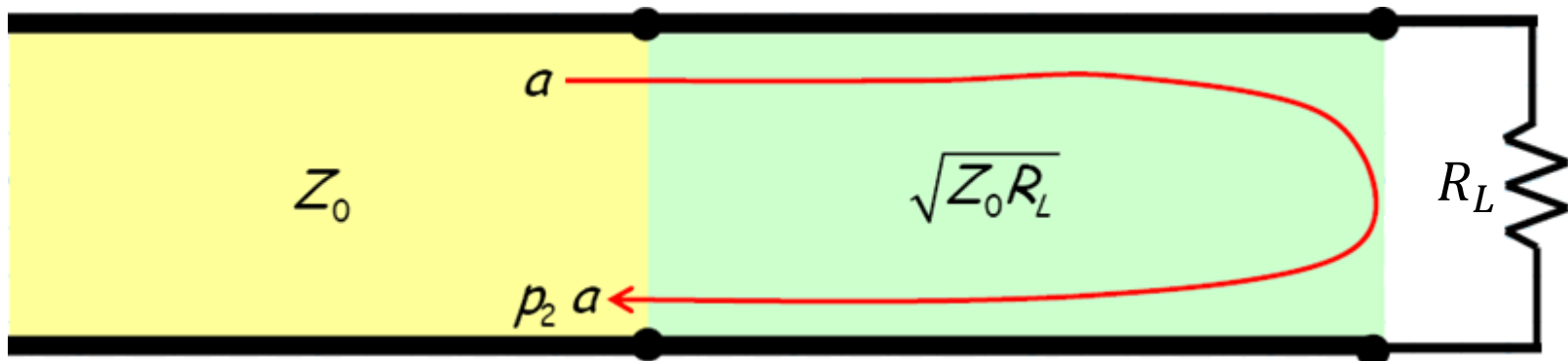
## Multiple Reflection Viewpoint (contd.)

**Path 2.** However, a **portion** of the incident wave is transmitted ( $T$ ) across the interface at  $z = -l$ , this wave travels a distance of  $\beta l = 90^\circ$  to the load at  $z = 0$ , where a portion of it is reflected ( $\Gamma_L$ ). This wave travels back  $\beta l = 90^\circ$  to the interface at  $z = -l$ , where a portion is again transmitted ( $T$ ) across into the  $Z_0$  transmission line—**another** reflected wave !




- So the **second direct path** is:

$$p_2 = T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T = -T^2 \Gamma_L$$


note that traveling  $2\beta l = 180^\circ$  has produced a **minus** sign in the result.



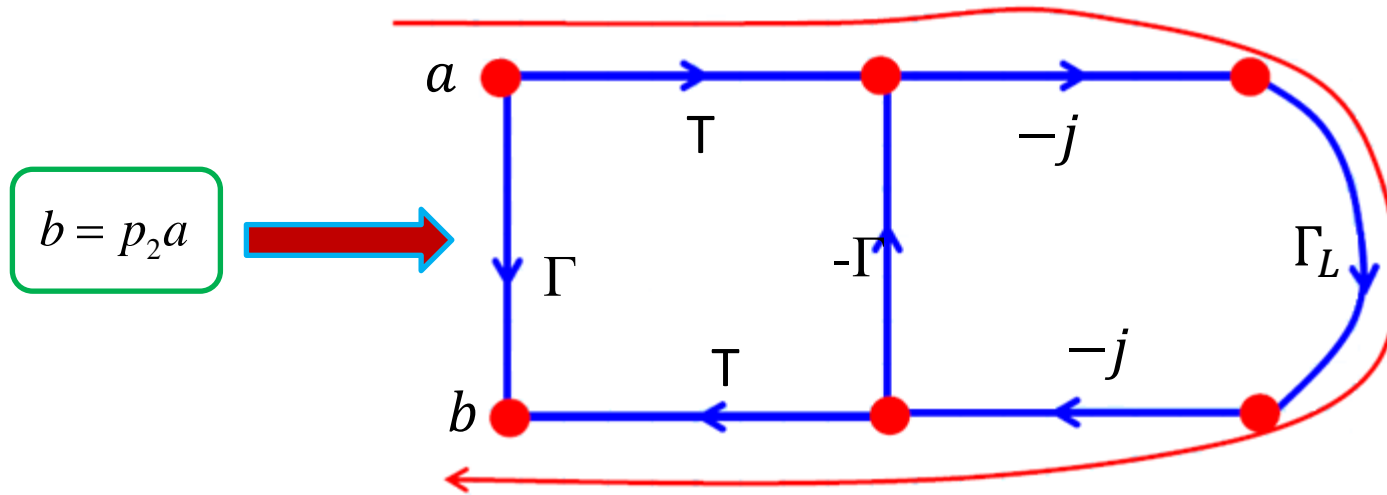
## Multiple Reflection Viewpoint (contd.)



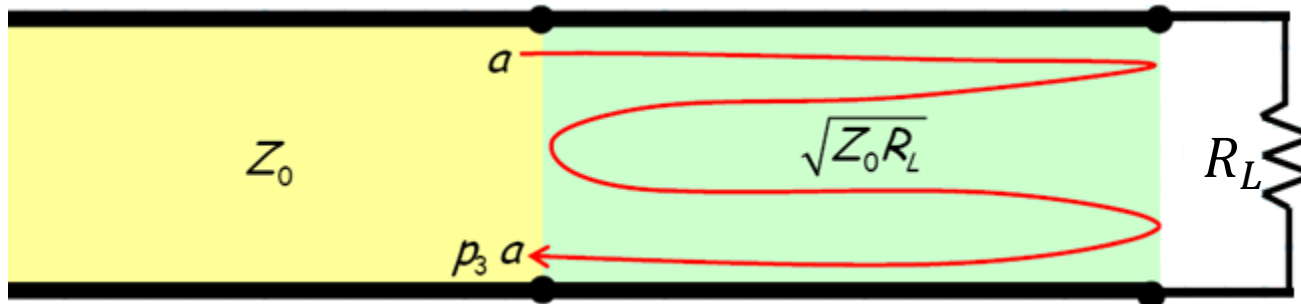**Path 3.** However, a **portion** of this **second** wave is also **reflected** ( $\Gamma$ ) back into the  $Z_1$  transmission line at  $z = -l$ , where it again travels to  $\beta l = 90^\circ$  the load, is partially reflected ( $\Gamma_L$ ), travels  $\beta l = 90^\circ$  back to  $z = -l$ , and is partially transmitted into  $Z_0$  ( $T$ )—our **third** reflected wave!


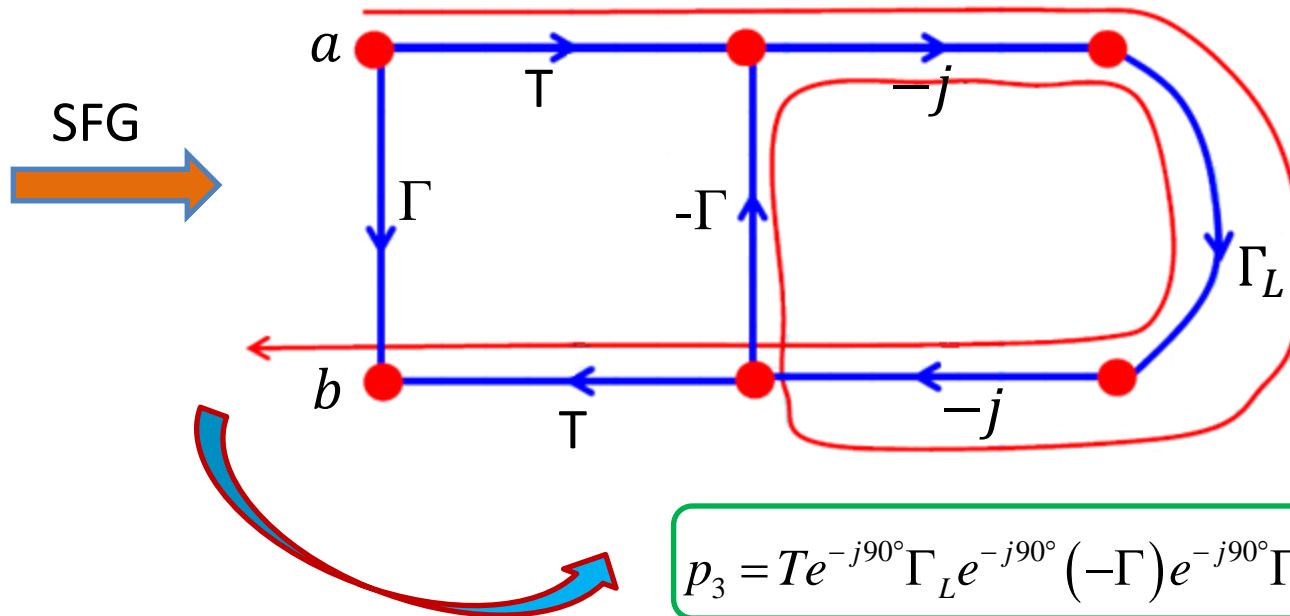
## Multiple Reflection Viewpoint (contd.)



Note that path 3 is  
**not** a direct path!

**Path n.** We can see that this “bouncing” back and forth can go on **forever**, with each trip launching a **new** reflected wave into the  $Z_0$  transmission line.

Note however, that the **power** associated with each successive reflected wave is **smaller** than the previous, and so eventually, the power associated with the reflected waves will **diminish** to insignificance!

## Multiple Reflection Viewpoint (contd.)

**Q:** But, why then is  $\Gamma = 0$  ?

**A:** Each reflected wave is a **coherent** wave. That is, they all oscillate at same frequency  $\omega$ ; the reflected waves differ only in terms of their **magnitude** and **phase**.

- Therefore, to determine the **total** reflected wave, we must perform a **coherent summation** of each reflected wave—this summation results in our **propagation series**, a series that must converge for passive devices.

$$b = a \sum_{n=1}^{\infty} p_n$$

- It can be shown that the infinite propagation series for **this** quarter-wavelength structure **converges** to the closed-form expression:

$$\frac{b}{a} = \sum_{n=1}^{\infty} p_n = \frac{\Gamma - \Gamma^2 \Gamma_L - T^2 \Gamma_L}{1 - \Gamma^2}$$

- Thus, the **input** reflection coefficient is:

$$\Gamma_{in} = \frac{b}{a} = \frac{\Gamma - \Gamma^2 \Gamma_L - T^2 \Gamma_L}{1 - \Gamma^2}$$

- Using our definitions, it can be shown that the **numerator** of this expression is:

$$\Gamma - \Gamma^2 \Gamma_L - T^2 \Gamma_L = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)}$$

## Multiple Reflection Viewpoint (contd.)

- It is evident that the numerator (and therefore  $\Gamma_{in}$ ) will be **zero** if:

$$Z_1^2 - Z_0 R_L = 0 \quad \longrightarrow \quad Z_1 = \sqrt{Z_0 R_L} \quad \longleftarrow \quad \text{Just as we expected!}$$


Physically, this result ensures that all the reflected waves add coherently together to produce a **zero value**!

Note **all** of our transmission line analysis has been **steady-state** analysis. We assume our signals are **sinusoidal**, of the form  $\exp(j\omega t)$ . This signal exists for **all time**  $t$ —the signal is assumed to have been “on” **forever**, and assumed to continue on forever.

In other words, in steady-state analysis, **all** the multiple reflections have long since occurred, and thus have reached a steady state—the reflected wave is **zero**!
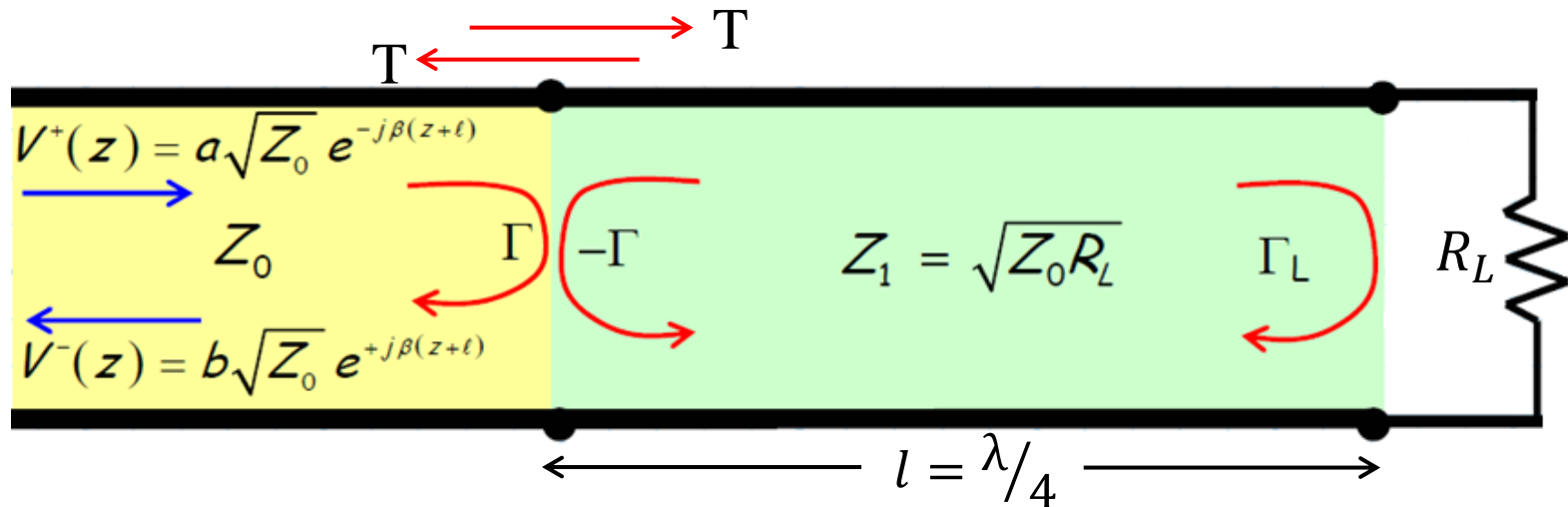
## The Theory of Small Reflections

- Recall that we analysed a **quarter-wave** transformer using the multiple reflection view point.




- We found that the solution could be written as an **infinite** summation of terms (the **propagation series**):

$$b = a \sum_{n=1}^{\infty} p_n$$

where each term had a specific **physical** interpretation, in terms of reflections, transmissions, and propagations.
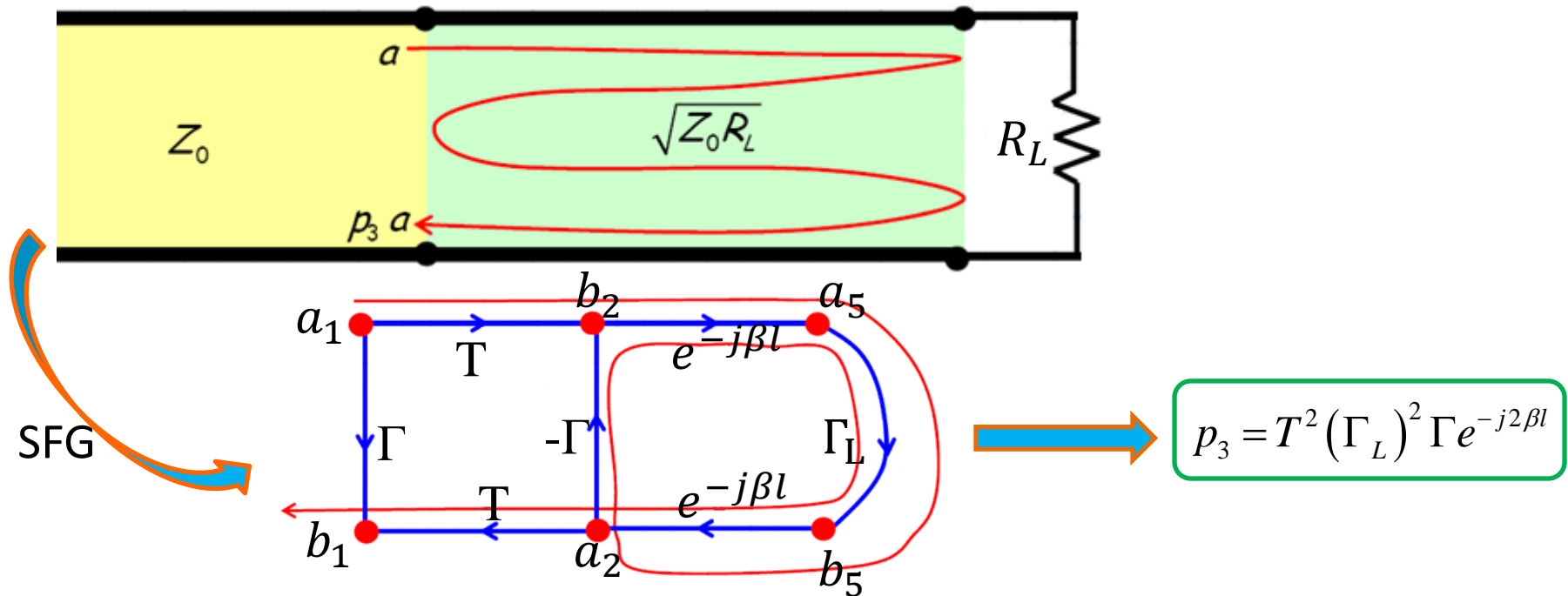
## The Theory of Small Reflections (contd.)

- For example, the **third** term was path:



- Now let's consider the **magnitude** of this path:

$$|p_3| = |T|^2 |\Gamma_L|^2 |\Gamma| |e^{-j2\beta l}|$$



$$|p_3| = |T|^2 |\Gamma_L|^2 |\Gamma|$$

## The Theory of Small Reflections (contd.)

- Recall that  $\Gamma = \Gamma_L$  for a **properly designed** quarter-wave transformer :

$$\Gamma = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L \quad \longrightarrow \quad |p_3| = |T|^2 |\Gamma_L|^3$$

- For the case where values  $R_L$  and  $Z_1$  are numerically **“close”**, i.e.:

$$|R_L - Z_1| \ll |R_L + Z_1|$$

- We find that the magnitude of the reflection coefficient will be **very** small:

$$|\Gamma_L| = \left| \frac{R_L - Z_1}{R_L + Z_1} \right| \ll 1.0$$

- As a result, the value  $|\Gamma_L|^3$  will be **very, very, very** small.

- Moreover, we know (since the connector is **lossless**) that:

$$|\Gamma|^2 + |T|^2 = |\Gamma_L|^2 + |T|^2 = 1$$



- We can thus conclude that the **magnitude** of path  $p_3$  is likewise **very, very, very** small:

$$|p_3| = |T|^2 |\Gamma_L|^3 \approx |\Gamma_L|^3 \ll 1$$

This is a **classic case** where we can approximate the propagation series using only the **forward paths!!**
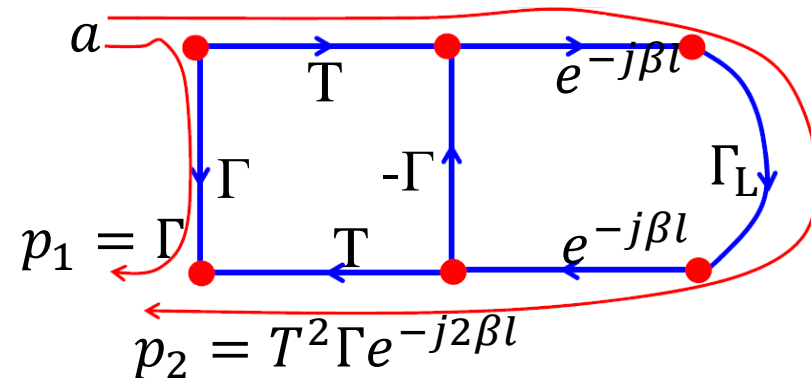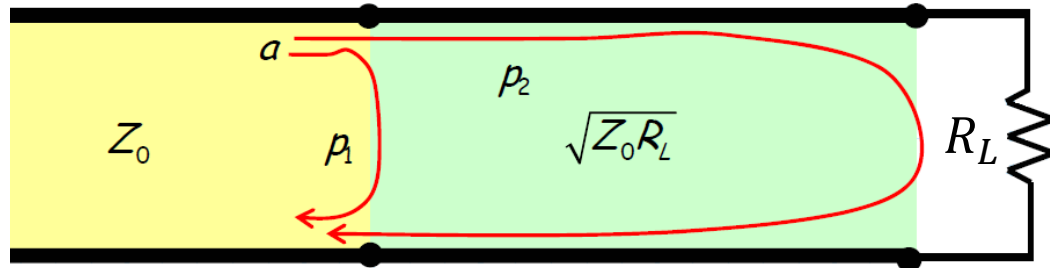
## The Theory of Small Reflections (contd.)

- Recall there are **two** forward paths:



- Therefore **if**  $Z_0$  and  $R_L$  are very **close** in value, the **approximate** reflected wave using only the **direct paths** of the infinite series can be found from the SFG:

$$b \simeq (p_1 + p_2)a = (\Gamma + T^2\Gamma_L e^{j2\beta l})a$$

- Now, if we likewise apply the **approximation** that  $|T| \cong 1.0$ , we conclude for this quarter wave transformer (at the design frequency):

$$b \simeq (p_1 + p_2)a = (\Gamma + \Gamma_L e^{j2\beta l})a$$



## The Theory of Small Reflections (contd.)


This **approximation**, where we:

1. use only the **direct paths** to calculate the propagation series,
2. approximate the **transmission** coefficients as **one** (i.e.,  $|T| = 1.0$ ).



is known as the **Theory of Small Reflections**, and allows us to use the propagation series as an **analysis** tool (we don't have to consider an **infinite** number of terms!).
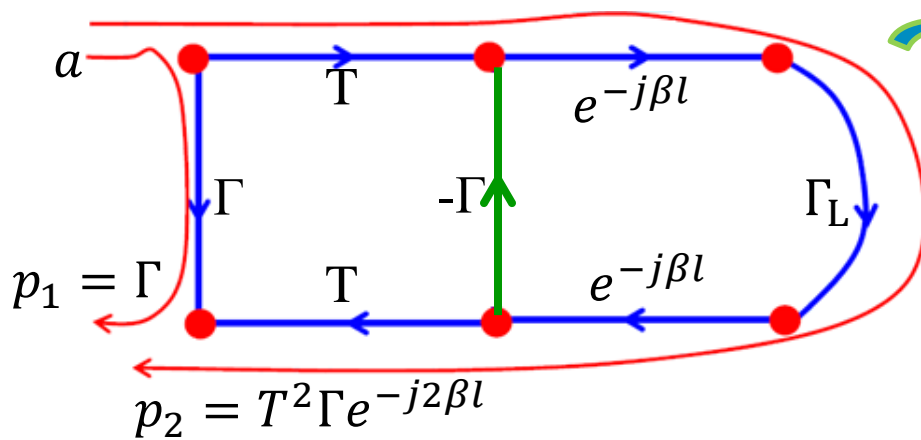
## The Theory of Small Reflections (contd.)

- Consider again the quarter-wave matching network SFG. Note there is **one branch** ( $-\Gamma = S_{22}$  of the connector), that is **not included** in either **direct path**.



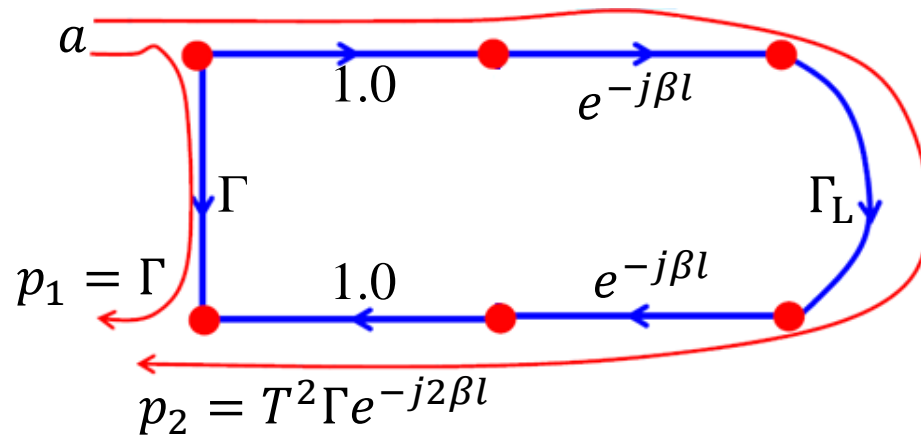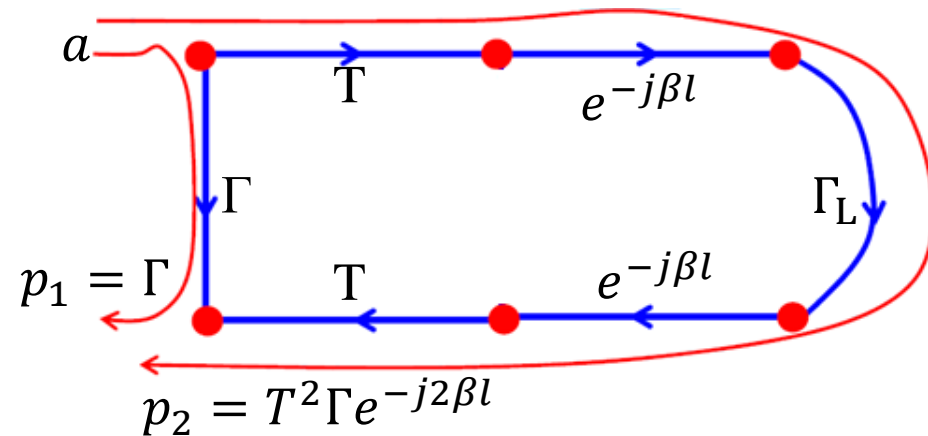
With respect to the theory of small reflections (where **only** direct paths are considered), this branch can be **removed** from the SFG **without affect**.



Moreover, the theory of small reflections implements the **approximation**,  $|T| = 1.0$ , so that the SFG becomes:
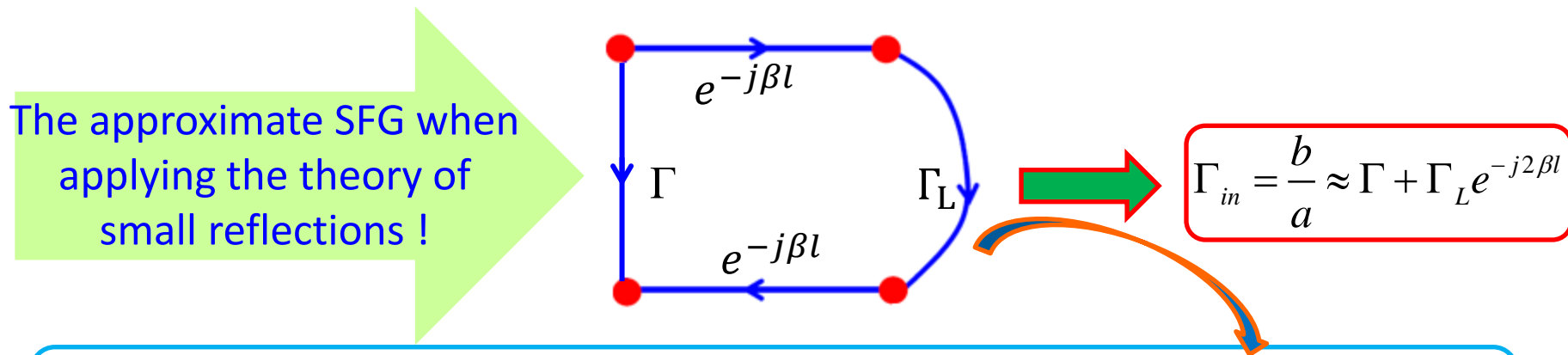
## The Theory of Small Reflections (contd.)

- Reducing this SFG by combining the 1.0 branch and the  $e^{-j\beta l}$  branch via the **series rule**, we get the following **approximate SFG**:



Note this **approximate** SFG provides **precisely** the results of the theory of small reflections!

**Q:** But wait! The quarter-wave transformer is a **matching** network, therefore  $\Gamma_{in} = 0$ . The **theory of small reflections**, however, provides the **approximate result**:

$$\Gamma_{in} \approx \Gamma + \Gamma_L e^{-j2\beta l}$$

Is this **approximation** very **accurate**? How **close** is this **approximate** value to the correct answer of  $\Gamma_{in} = 0$ ?

## The Theory of Small Reflections (contd.)

**A:** Let's find out!

- Recall that  $\Gamma = \Gamma_L$  for a properly designed quarter-wave matching network, and so:

$$\Gamma_{in} \approx \Gamma + \Gamma_L e^{j2\beta l} = \Gamma_L (1 + e^{-j2\beta l})$$

- Likewise,  $l = \lambda/4$  (but **only** at the design frequency!) so that:

$$2\beta l = 2 \left( \frac{2\pi}{\lambda} \right) \frac{\lambda}{4} = \pi$$

where **you** of course recall that  
 $\beta = 2\pi/\lambda!$

- Thus:  $\Gamma_{in} \approx \Gamma + \Gamma_L e^{j2\beta l} = \Gamma_L (1 + e^{-j\pi}) = \Gamma_L (1 - 1) = 0$

**Q: Wow!** The theory of small reflections appears to be a **perfect** approximation—**no error** at all!?!

**A: Not so fast.**

## The Theory of Small Reflections (contd.)

The **theory of small reflections** most definitely provides an **approximate** solution (e.g., it **ignores** most of the terms of the propagation series, and it **approximates** connector transmission as  $T = 1$ , when in fact  $T \neq 1$ ).

As a result, the solutions derived using the **theory of small reflections** will—generally speaking—exhibit **some** (hopefully small) **error**.




We just got a bit “**lucky**” for the quarter-wave matching network; the “approximate” result  $\Gamma_{in} = 0$  was exact for this one case!

➔ The **theory of small reflections** is an **approximate** analysis tool!
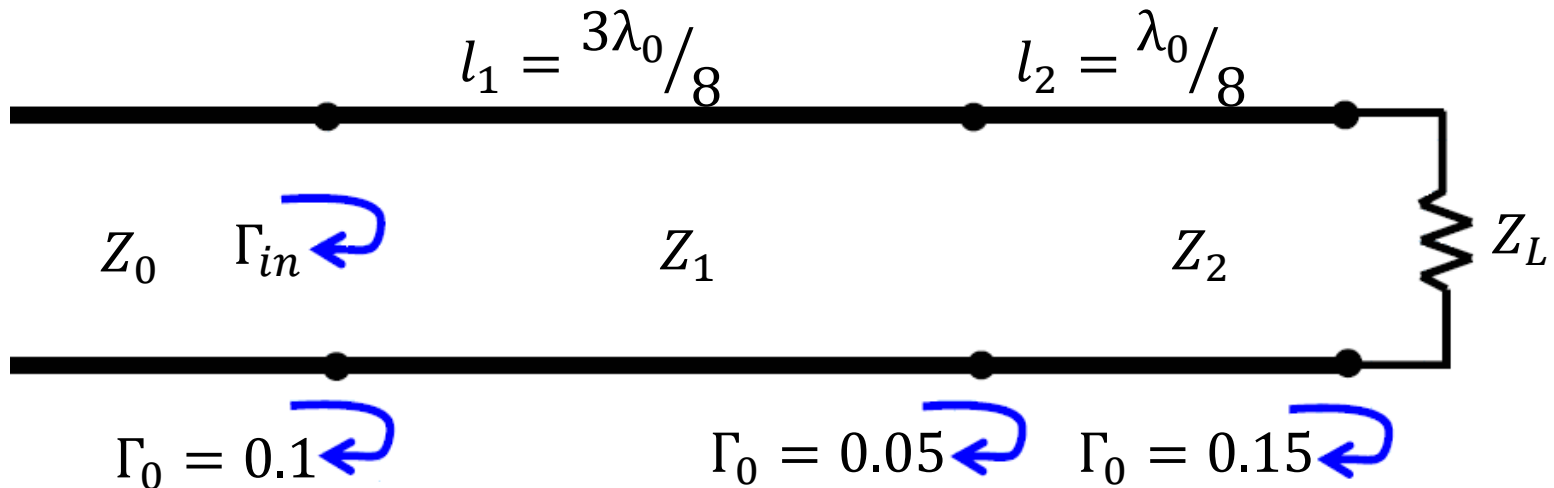
## Example – 4

- Use the **theory of small reflections** to determine a **numeric** value for the **input** reflection coefficient  $\Gamma_{in}$ , at the design frequency  $\omega_0$ .



Note that the transmission line sections have **different lengths!**