

Lecture – 18

Date: 16.10.2014

- Wilkinson Power Divider
- Wilkinson Power Divider Analysis



# The (Nearly) Ideal T- Junction Power Divider

- Recall that we cannot build a matched, lossless reciprocal three-port device.
- So, let's **mathematically try and determine the scattering** matrix of the best possible T-junction 3 dB **power divider.**



- To efficiently divide the power incident on the input port, the port (port 1) must first be matched (i.e., all incident power should be delivered to port 1):  $S_{11} = 0$
- Likewise, this delivered power to port 1 must be divided efficiently (i.e., without loss) between ports 2 and 3.
- Mathematically, this means that the first column of the scattering matrix must have magnitude of 1.0:

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$$
  $|S_{21}|^2 + |S_{31}|^2 = 1$ 



# The (Nearly) Ideal T- Junction Power Divider (contd.)

Provided that we wish to evenly divide the input power, we can conclude from the expression above that:



Note that this device would take the power into port 1 and divide into two equal parts—half exiting port 2, and half exiting port3 (provided ports 2 and 3 are terminated in matched loads!).

$$P_2^- = |S_{21}|^2 P_1^+ = 0.5P_1^+$$
  $P_3^- = |S_{31}|^2 P_1^+ = 0.5P_1^+$ 

In addition, it is desirable that ports 2 and 3 be matched (the whole device is thus matched):

$$S_{22} = S_{33} = 0$$

And also desirable that ports 2 and 3 be isolated:





## The (Nearly) Ideal T- Junction Power Divider (contd.)

• The ideal 3 dB power divider **could therefore have the form**:



Since we can describe this ideal power divider mathematically, we can potentially build it physically!

**Q: Huh!? I thought you said that a matched, lossless,** reciprocal three-port device is **impossible?** 

A: It is! This divider is clearly a lossy device. The magnitudes of both column 2 and 3 are less than one:

$$\begin{aligned} \left|S_{12}\right|^{2} + \left|S_{22}\right|^{2} + \left|S_{32}\right|^{2} = \left|-j/\sqrt{2}\right|^{2} + 0 + 0 = 0.5 < 1 \\ \left|S_{13}\right|^{2} + \left|S_{23}\right|^{2} + \left|S_{33}\right|^{2} = \left|-j/\sqrt{2}\right|^{2} + 0 + 0 = 0.5 < 1 \end{aligned}$$

Indraprastha Institute of Information Technology Delhi

### The (Nearly) Ideal T- Junction Power Divider (contd.)

Note then that **half the power incident on port 2 (or port 3)** of this device would **exit port 1 (i.e., reciprocity), but no power** would exit port 3 (port2), since ports 2 and 3 are **isolated. i.e.,** 

 $P_{1}^{-} = |S_{12}|^{2} P_{2}^{+} = 0.5P_{2}^{+} \qquad P_{3}^{-} = |S_{32}|^{2} P_{2}^{+} = 0 * P_{2}^{+} = 0$  $P_{1}^{-} = |S_{13}|^{2} P_{3}^{+} = 0.5P_{3}^{+} \qquad P_{2}^{-} = |S_{23}|^{2} P_{3}^{+} = 0 * P_{3}^{+} = 0$ 

**Q**: Any ideas on how to build this thing?

A: Note that the first column of the scattering matrix is precisely the same as that of the lossless 3 dB divider.

Also note that since the device is **lossy, the design must** include some **resistors.** 

Lossless Divider + resistors = The Wilkinson Power Divider



## Wilkinson Power Divider

- Wilkinson power divider is the nearly ideal T-junction power divider → It is lossy, matched and reciprocal.
- Therefore, the scattering matrix and SFG of Wilkinson power divider is of the form:



- Note this device is matched at port 1 (S<sub>11</sub> = 0), and we find that magnitude of column 1 is:  $|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$
- Just like the lossless divider, the incident power on port 1 is evenly and efficiently divided between the outputs of port 2 and port 3

 $P_2^- = |S_{21}|^2 P_1^+ = 0.5P_1^+$   $P_3^- = |S_{31}|^2 P_1^+ = 0.5P_1^+$ 



### Wilkinson Power Divider (contd.)

• It is also apparent that the ports 2 and 3 of this device are matched !

 $S_{22} = S_{33} = 0$ 

• We also note that ports 2 and ports 3 are **isolated**:  $S_{23} = S_{32} = 0$ 

**Q**: Ok, so it is a (nearly) ideal divider  $\rightarrow$  but how do we make this Wilkinson power divider?

A: It looks a lot like a **lossless 3dB divider**, only with an additional **resistor** of value  $2Z_0$  between ports 2 and 3:





# Wilkinson Power Divider (contd.)

- This resistor is the secret to the Wilkinson power divider, and is the reason that it is matched at ports 2 and 3, and the reason that ports 2 and 3 are isolated.
- Note however, that the quarter-wave transmission line sections make the Wilkinson power divider a narrow-band device.





### **Analysis of Wilkinson Power Divider**

• Consider a matched Wilkinson power divider, with a source at port 2:



A: Use Even-Odd mode analysis!



Remember, even-odd mode analysis uses two important principles:

- a) superposition
- b) circuit symmetry
- To see how we apply these principles, let's first rewrite the circuit with four voltage sources:





• Note the circuit has **odd symmetry**, and thus the plane of symmetry becomes a **virtual short**, and in this case, a virtual **ground**!





 Analyzing the first half-circuit, we find that the transmission line is terminated in a short circuit in parallel with a resistor of value 2Z<sub>0</sub>. Thus, the transmission line is terminated in a short circuit!





 Now, let's turn off the odd mode sources, and turn back on the even mode sources.





### ECE321/521

### Analysis of Wilkinson Power Divider (contd.)

• Dividing the circuit into two **half-circuits**, we get:





 Analyzing the first circuit, we find that the transmission line is terminated in an **open** circuit in **parallel** with a **resistor** of value 2Z<sub>0</sub>. Thus, the transmission line is terminated in a **resistor** valued 2Z<sub>0</sub>.



• Then due to the **even symmetry** of the circuit, we can say:

$$V_3^e = \frac{V_s}{4}$$



there's no direct or easy way to find V<sub>1</sub><sup>e</sup>. We must apply TL theory (i.e., the solution to the telegrapher's equations + boundary conditions) to find this value. This means applying the knowledge and skills acquired during our scholarly examination of TL Theory!

 $2Z_{0} \checkmark 4 \longrightarrow 2Z_{0} \land 2Z_{0}$ 

 This completes our symmetry analysis and then from superposition, the voltages within the circuit is simply found from the sum of the solutions of each mode:

$$V_1 = V_1^o + V_1^e = 0 + \frac{(-jV_s)}{2\sqrt{2}} = -\frac{jV_s}{2\sqrt{2}}$$

Indraprastha Institute of Information Technology Delhi

#### ECE321/521

#### **Analysis of Wilkinson Power Divider (contd.)**



 Note that the voltages we calculated are total voltages—the sum of the incident and exiting waves at each port:

$$V_{1} \doteq V_{1} \left( z_{1} = z_{1p} \right) = V_{1}^{+} \left( z_{1} = z_{1p} \right) + V_{1}^{-} \left( z_{1} = z_{1p} \right)$$
$$V_{2} \doteq V_{2} \left( z_{2} = z_{2p} \right) = V_{2}^{+} \left( z_{2} = z_{2p} \right) + V_{2}^{-} \left( z_{2} = z_{2p} \right)$$
$$V_{3} \doteq V_{3} \left( z_{3} = z_{3p} \right) = V_{3}^{+} \left( z_{3} = z_{3p} \right) + V_{3}^{-} \left( z_{3} = z_{3p} \right)$$

Indraprastha Institute of Information Technology Delhi

## Analysis of Wilkinson Power Divider (contd.)

• Since ports 1 and 3 are terminated in **matched loads**, and we also know that the **incident** wave on those ports are **zero**. As a result, the **total** voltage is equal to the value of the exiting waves at those ports.

$$V_{1}^{+}(z_{1}=z_{1p})=0 \qquad V_{1}^{-}(z_{1}=z_{1p})=\frac{-jV_{s}}{2\sqrt{2}} \qquad V_{3}^{+}(z_{3}=z_{3p})=0 \qquad V_{3}^{-}(z_{3}=z_{3p})=0$$

- The problem now is to determine the values of the incident and exiting waves at port 2.
- For this purpose, let us consider the following circuit where the **source impedance** is **matched** to TL characteristic impedance (i.e.,  $Z_s = Z_0$ ). We can find, the incident wave "launched" by the source **always** has the value  $V_s/2$  at the start of the line.

$$V_{s} \stackrel{+}{\hookrightarrow} V_{s} \stackrel{+}{\bigvee} V_{s} \stackrel{+}{(z = z_{s})} = \frac{V_{s}}{2} Z_{0}$$



• Now, if the length of the transmission line connecting the source to a port (or load) is **electrically very small** (i.e.,  $\beta l \ll 1$ ), then the source is effectively **connected directly** to the source (i.e,  $\beta z_s = \beta z_p$ ):



• Therefore, for port 2 of the Wilkinson power divider we can write:

$$V_{2}^{+}(z_{2}=z_{2p}) = \frac{V_{s}}{2} \qquad \qquad V_{2}^{-}(z_{2}=z_{2p}) = V_{2} - \frac{V_{s}}{2} = \frac{V_{s}}{2} - \frac{V_{s}}{2} = 0$$



• Now, we can **finally** determine the following scattering parameters:

$$S_{12} = \frac{V_1^{-}(z_1 = z_{1p})}{V_2^{+}(z_2 = z_{2p})} = \left(\frac{-jV_s}{2\sqrt{2}}\right)\frac{2}{V_s} = \frac{-j}{\sqrt{2}}$$
$$S_{22} = \frac{V_2^{-}(z_2 = z_{2p})}{V_2^{+}(z_2 = z_{2p})} = (0)\frac{2}{V_s} = 0$$
$$S_{32} = \frac{V_3^{-}(z_3 = z_{3p})}{V_2^{+}(z_2 = z_{2p})} = (0)\frac{2}{V_s} = 0$$

**Q:** Wow! That seemed like a **lot** of hard work, and we're only 1/3 of the way done. Do we **have** to move the source to port 1 and then port 3 and perform similar analyses?

A: Nope! Using the bilateral symmetry of the circuit  $(1 \rightarrow 1, 2 \rightarrow 3, 3 \rightarrow 2)$ , we can conclude:

$$S_{13} = S_{12} = \frac{-j}{\sqrt{2}}$$
  $S_{33} = S_{22} = 0$   $S_{23} = S_{32} = 0$ 



### ECE321/521

### Analysis of Wilkinson Power Divider (contd.)

• and from **reciprocity** we can say:

$$S_{21} = S_{12} = \frac{-j}{\sqrt{2}}$$
  $S_{31} = S_{13} = \frac{-j}{\sqrt{2}}$ 

We thus have determined 8 of the 9 scattering parameters needed to characterize this 3-port device. The remaining is the scattering parameter S<sub>11</sub>. To find this value, we must move the source to port 1 and analyze.



This source does **not** alter the bilateral symmetry of the circuit. We can thus use this symmetry to **help analyze** the circuit, **without** having to specifically define odd and even mode sources.



• Since the circuit has bilateral symmetry, we know that the symmetry plane forms a **virtual open**.



Note the **value** of the voltage sources. They have a value of  $V_s$  (as **opposed** to, say,  $2V_s$  or  $V_s/2$ ) because two equal voltage sources in **parallel** is equivalent to one voltage source of the **same value**.

• **Splitting** the circuit into **two** half-circuits, we find the **top** half-circuit to be:





### ECE321/521

### Analysis of Wilkinson Power Divider (contd.)

• Which simplifies to:



• **Transforming** the load resistor at the end of the  $\lambda/4$  line back to the start:





#### ECE321/521

#### **Analysis of Wilkinson Power Divider (contd.)**



• And since the **source is matched**:

$$V_1^+(z_1 = z_{1p}) = \frac{V_s}{2}$$
$$V_1^-(z_1 = z_{1p}) = V_1 - \frac{V_s}{2} = \frac{V_s}{2} - \frac{V_s}{2} = 0$$

• So our **final** scattering element is revealed!

$$S_{11} = \frac{V_1^-(z_1 = z_{1p})}{V_1^+(z_1 = z_{1p})} = (0)\frac{2}{V_s} = 0$$



• So the scattering matrix of a **Wilkinson power divider** has been **confirmed**:

$$S = \begin{bmatrix} 0 & -j/\sqrt{2} & -j/\sqrt{2} \\ -j/\sqrt{2} & 0 & 0 \\ -j/\sqrt{2} & 0 & 0 \end{bmatrix}$$



#### ECE321/521

