

ASSIGNMENT #1

Analog CMOS Circuit Design (ECE315 /ECE515)

All the simulation must be carried out in Cadence 180nm.

Submission Deadline: 21 August 2016.

1. A three terminal Non linear device shown in Figure - 1 exhibits definite I_1 vs V_1 , I_1 vs V_2 , I_2 vs V_2 and I_2 vs V_1 characteristics.

Assume that the Non Linear Device shown in Figure (1) can be modelled as,

$$I_1 = f(V_1, V_2)$$

$$I_2 = g(V_1, V_2)$$

 


Figure1

Now answer the following Questions (Your Answers must be Qualitative. An intuitive answer leads blunders)

- a. Figure (2) shown below depicts I_1 vs V_1 characteristics of two Non Linear devices (Device (i) and Device (ii)). Assume that the characteristics I_1 vs V_2 , I_2 vs V_2 and I_2 vs V_1 are identical for both the amplifiers. Find out which of the Non Linear devices will yield maximum gain at the given operating point shown in the figure (Green Circle).

 


Figure2

 


Figure3

- b. Figure (3) shown below depicts I_2 vs V_1 characteristics of two Non Linear devices (Device (i) and Device (ii)). Assume that the characteristics I_1 vs V_2 , I_2 vs V_2 and I_1 vs V_1 are identical for both the amplifiers. Find out which of the Non Linear devices will yield maximum gain at the given operating point shown in the figure (Green Circle).

2. For the circuit shown in **Figure 4**: ($R_s = 50K\Omega$, $R_g = 50M\Omega$, $R_L = 100K\Omega$, $I = 128 \mu A$, $V_t = 1V$, $\mu C_{ox}(W/L) = 100\mu A/V^2$)
- For the same circuit an Input signal is applied with a frequency of 10 KHz. Find the values of C_1 and C_2 .
 - Implement the same using Cadence simulator for the values you got in **Part a** and compare the gain of the amplifier with theoretical gain.

 


Figure 4

3. Sketch I_x versus V_x for each of the composite structure shown in **Figure 5** with V_G as a parameter. Also, sketch the equivalent transconductance. Assume $\lambda = 0$. Maximum value of V_x voltage is 3 Volt.

 


Figure 5

4. Sketch V_x as a function of time for each circuit in the **Figure 6**.

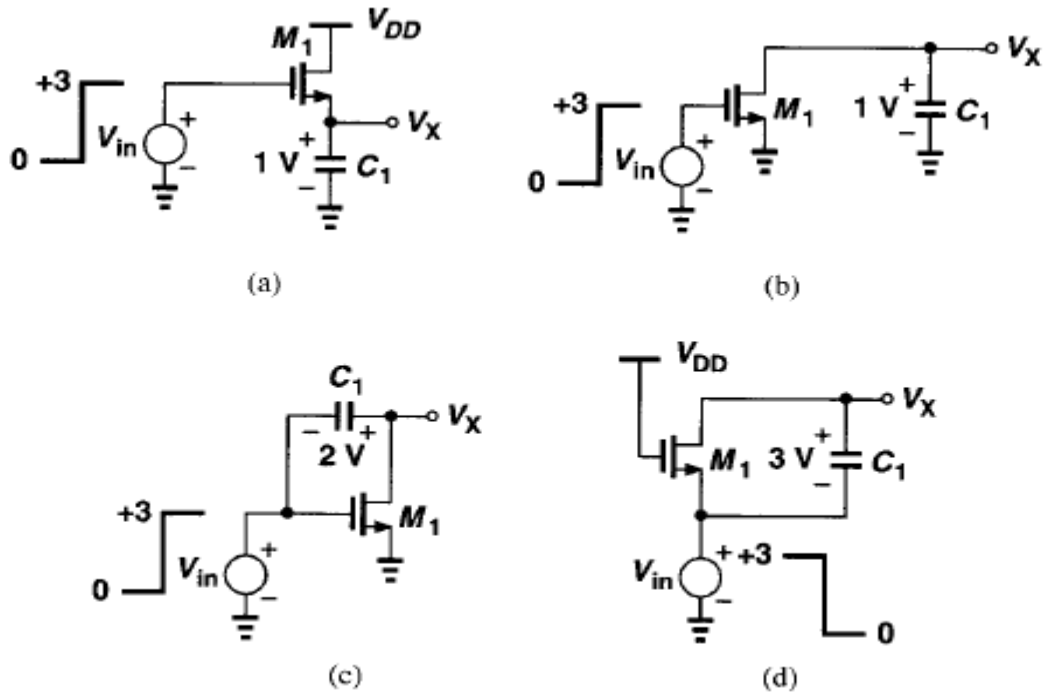


Figure 6